

## Effect of the Operating Mode on the Magnetics of Boost and Flyback Converters: TM v. CCM

Isaac Cohen Lucas Nicieza, Frenetic Al





## **Quantitative Criteria Needed!**

- Which is a better system solution: TM or CCM?
  - -Smaller/cheaper
  - -More efficient





## **Part One: Boost Converters**

- Lower RMS currents, lower switch conduction/copper(?) losses
- Lower peak to peak AC ripple, lower input DM EMI
- Switch turn ON and Boost diode reverse recovery loss

# TM

- Higher RMS currents, higher switch conduction/copper (?) losses
- Valley turn ON (ZVS for Vin<1/2Vout), Boost diode ZCS turn off, lower switching loss.



# Analog

## **Calibrating expectations: The RMS current reduction**

# For perfect CCM (zero ripple current):



3 
$$\frac{\text{Irms.tm}}{\text{Irms.ccm}} = \frac{2}{\sqrt{3}} = 1.155$$

# The maximum possible (15.5%) Irms reduction requires infinite inductance!!!





## **Discussion: Increasing inductance**

- Switching frequency is typically maintained below 150kHz (the fundamental outside the EMI band)
  - A good ferrite can operate at  $\sim$ 100kHz with  $\Delta$ B of 300mT (0-300mT peak, close to saturation)
- If the inductor is designed to operate in TM close to saturation, the inductance cannot be increased by decreasing the air gap.
- The inductance can be increased by increasing the number of turns and the air gap





## From TM to CCM







k: Inductor ripple reduction factor (=L<sub>ccm</sub>/<sub>Ltm</sub>)

Iped: DC Pedestal of the inductor current

lave: Average output current

- $\Delta$  I: PTP inductor ripple current
- $N_{ccm}$ : Turns of the CCM inductor
- N<sub>tm</sub>: Turns of the TM inductor







# Quantitative analysis: CCM Values normalized to TM values (Mathcad file available)

1 
$$N_{.ccm}(k) \coloneqq \frac{k+1}{2}$$
  
2  $Rdc_{.ccm}(k) \coloneqq \left[\frac{(k+1)}{2}\right]^2$   
3  $Irms_{max}(k) \coloneqq \frac{\sqrt{\frac{1}{k^2}+3}}{2}$ 









# Analog DC Resistance v ripple attenuation factor (CCM Depth)







## **Copper Loss v CCM Depth (gross estimate!)**

$$\operatorname{Cu}_{.\operatorname{ccm}}(k) \coloneqq \operatorname{Rdc}_{.\operatorname{ccm}}(k) \cdot \operatorname{Irms}_{.\operatorname{ccm}}(k)^2$$

In reality, the effective resistance of the winding does not increase as fast as the DC resistance, but <u>the</u> <u>rapid Rdc increase with k is a</u> <u>big red flag!</u>

The accurate loss value will be calculated numerically



Texas Instruments



# TM v CCM inductor loss factors

- Fundamentals: TM inductor is the benchmark, core is the same or smaller for the CCM inductor.
- CCM:
  - More turns of thinner wire, more layers, larger air gap
  - Lower AC flux swing, lower core loss
  - Lower AC ripple, same DC current
- No simple analytical way to design the inductors and calculate losses



## Switching losses and DM EMI considerations

## **Switching Loss:**

In TM with input voltage lower than 1/2 the output voltage, the Boost switch can be turned ON with zero voltage across it.

### Switching loss will be essentially zero.

In CCM operation, the Vds of the switch at turn ON is always equal to output voltage.

Switching loss may be substantial.

The full switching loss occurs immediately upon entering CCM – long before any noticeable RMS current reduction is realized.

### EMI:

Although the amplitude of the current ripple decreases as the frequency increases, the fundamental moves move into the EMI band, resulting in a worse DM EMI than at the lower frequency (example 100kHz v 200kHz)





## **CCM By Frequency Increase**



- Frequency doubled from 100kHz to 200kHz
- Ripple attenuated 2x
- Inductor loss may actually be lower, but:
  - Substantial switching loss added
  - DM EMI will actually be worse (the fundamental now inside the EMI band)



# CCM Turn ON switching loss estimate (from an EVM)

Hardware, Software, Testing Requirements, and Test Results





NOTE: CH2: PFC switch node voltage (100 V/div, bandwidth: 20 MHz); CH4: PFC inductor current (2 A/div, bandwidth: 20 MHz); Test condition: VIN = 230-V AC/60 Hz; IOUT = 100% load Switching node ringing period to: **1.77usec Boost inductor L value:** 269uH Calculated switching node capacitance C<sub>sw</sub>: C<sub>sw</sub>=(To/2π)<sup>2</sup><sub>\*</sub>1/L=295pF Switching Node Energy:  $E_{sw} = V^{2*}C_{sw}/2 = 23.6 \text{uJ}$ Switching Loss @ Fsw=100kHz: 2.36W!!! This analysis neglects additional switching losses that may be caused by the reverse recovery of the boost diode



TM operation enables recovery of the switching node energy, while CCM dissipates the switching node energy as a result of the inherent hard switching operation The switching node capacitance and energy may be dominated by factors other than the capacitances of the switch and of the boost diode.

Replacing Si SJ with WBG may not provide substantial improvement.

The loss associated with dissipating the switching node energy may be <u>substantial</u>, <u>rendering CCM operation w/o</u> ZVS unattractive at frequency > 100kHz





# Part Two: Flyback Converters

## "Perfect" CCM:

- Also requires Infinite inductance!
- Winding currents still pulsed, (not DC as for Boost), high frequency current present
  - proximity and skin loss not eliminated
    - DM EMI benefit from CCM less than for Boost (rectangular v. sawtooth currents)
- V<sub>ds</sub> of primary switch is lower at low input voltage, so the turn ON loss in CCM lower than for Boost converter.

# Use Frenetic tool to compare CCM to TM transformer on same core.





- Methodology:
  - Optimize inductor design in TM
  - Search for minimum inductor loss in CCM (on same or smaller core) for increasing values of the ripple attenuation factor k and compare to losses in TM.

**Remember the added switching losses when entering CCM** (particularly onerous for Boost applications with low Vin, high Vout) **!!!** 



#### High-Performance Analog Time Time

- Well known that a Boost converter operating in TM with fixed ON time presents a resistive load to the rectified line voltage..
- TI has developed a control method that allows extension of the simple fixed ON time method to CCM operation.
  - The converter will be aresistive load in both TM and CCM.



## **TM Inductor Optimization**

#### <u>1 - Design Requirements</u>

#### **Boost Case**

- Input Voltage = 90V
- Output Voltage = 390V
- Output Power = 300W
- T ambient = 25°C
- Cooling = Free Convection
- Fsw = 120 kHz



#### PFC Case

- Input Voltage = 90V
- Output Voltage = 390V
- Output Power = 150W
- T ambient = 25°C
- Cooling = Free Convection
- Fsw\_max\_TM = 120kHz
- Fsw\_CCM = 120kHz



#### 2 - Design Constraints

- Custom cores could be used to get the smallest possible size
- Best in class wires
- Distributed gaps are allowed
- Any combination of material and shape could be used

#### 3 - Procedure of the analysis

- Minimize the inductor size in TM mode
- Change to CCM mode keeping the fsw constant (in the PFC case fsw\_ccm = min\_fsw\_TM)
- Keep the TM Inductor Core fixed
- Optimize the winding for the CCM operation
- Increase inductance and optimize again



All dimensions can be customized to minimize the size and maximize the performance





## **300 W Boost TM v. CCM results**

#### <u>TM – Boost</u>



L = 142 uH 20 Turns Custom PQ 25/17 Material Ferrite 3C97 Litz 40x0,1 mm Rdc = 57 mOhms

Total Losses = 1,32W  $\Delta I = 4,94A$ 

#### Simulation Results

BpkT (mT)=	334
Core Losses (W)=	0.712
Winding Losses (W)=	0.606
Total Losses (W)=	1.32
Max Temp (°C)=	67
Core Surface Temp (°C)=	61
Winding Surface Temp (°C)=	67
Central Leg Surface Temp (°C)=	64

# Control of the second s

Itage [V] Current [A



#### $\Delta I = 2,52 A$

#### Simulation Results

CCM - Boost

BpkT (mT)=	328.652
Core Losses (W)=	0.234
Winding Losses (W)=	1.142
Total Losses (W)=	1.38
Max Temp (°C)=	76
Core Surface Temp (°C)=	60
Winding Surface Temp (°C)=	76
Central Leg Surface Temp (°C)=	65

#### <u>CCM – Boost</u>



#### L = 1281 uH 56 Turns Custom PQ 25/17 Powder Edge 125 Round 0,56 mm Rdc = 198 mOhms

Total Losses = 2,07W  $\Delta I = 0,56 A$ 

#### Simulation Results

BpkT (mT)=	616
Core Losses (W)=	0.436
Winding Losses (W)=	1.634
Total Losses (W)=	2.07
Max Temp (°C)=	95
Core Surface Temp (°C)=	75
Winding Surface Temp (°C)=	95
Central Leg Surface Temp (°C)=	78





## **150 W PFC TM V.CCM Results**

#### <u>TM - PFC</u>



L = 142 uH 20 Turns Custom PQ 25/17 Material Ferrite 3C97 Litz 40x0,1 mm Rdc = 57 mOhms

Total Losses = 0,6W  $\Delta I = 4,71 A$ 

L = 274 uH 30 Turns Custom PQ 25/17 Material Ferrite 3C97 Litz 25x0,1 mm Rdc = 138 mOhms

Total Losses = 0,84W  $\Delta I = 2,61 A$ 

# CCM – PFC (not viable Bmax)



#### Simulation Results

BpkT (mT)=	326.57
Core Losses (W)=	0.333
Winding Losses (W)=	0.268
Total Losses (W)=	0.6
Max Temp (°C)=	45
Core Surface Temp (°C)=	43
Winding Surface Temp (°C)=	45
Central Leg Surface Temp (°C)=	44

# BpkT (mT)= 324 Core Losses (W)= 0.314 Winding Losses (W)= 0.522 Total Losses (W)= 0.84 Max Temp (°C)= 55

Simulation Results

CCM – PFC

 Max Temp (°C)=
 55

 Core Surface Temp (°C)=
 49

 Winding Surface Temp (°C)=
 55

 Central Leg Surface Temp (°C)=
 51

#### Simulation Results

BpkT (mT)=	492.324
Core Losses (W)=	0.315
Winding Losses (W)=	0.579
Total Losses (W)=	0.89
Max Temp (°C)=	56
Core Surface Temp (°C)=	50
Winding Surface Temp (°C)=	56
Central Leg Surface Temp (°C)=	51





- CCM needs larger inductance and therefore larger number of turns. As the number of turns increases given the fix window space the DC resistance increases and the conduction losses increase
- Going from TM to CCM with ferrite does not add major benefit because the current ripple attenuation achieved with bigger power loss is very small.
- Going from TM to CCM with powder cores could add some benefit from the current ripple attenuation perspective but it does not add any benefit from the losses perspective. Although the high frequency losses go down with smaller current ripple the larger RDC implies larger winding conduction losses
  - At low power CCM does not provide any benefit in the inductor size or performance.

# Is there any chance for the CCM at higher power?





## 3kW & 12kW PFC Results

#### <u>TM – PFC – 3kW 50 kHz</u>



L = 34 uH 12 Turns Custom EQ47 Material Ferrite 3C92 Litz 675x0,1 mm Rdc = 4 mOhms **Total Losses = 3,43W**  $\Delta I = 36, 86 A$ 

#### TM – PFC – 3kW 20 kHz



L = 84 uH 21 Turns Custom EQ56 Material Ferrite 3C92 Litz 338x0,1 mm Rdc = 14 mOhms **Total Losses = 5,34W**  $\Delta I = 36,58 A$ 

#### CCM - PFC - 3kW 20 kHz



L = 672 uH32 Turns Custom EQ56 Powder Edge 125 Round 2,24mm Rdc = 18,75 mOhmsTotal Losses = 6,6 W $\Delta I = 8,96 \text{ A}$ 

#### TM – PFC – 12kW 20 kHz



L = 84 uH 22 Turns Custom E63 Material Ferrite 3C97 Litz 1121x0,071mm Rdc = 16 mOhms **Total Losses = 25,6W**  $\Delta I = 84, 5A$ 

#### CCM - PFC - 12kW 20 kHz



L = 672 uH 26 Turns Custom E63 Powder Edge 125 Round 3,15 mm Rdc = 10,38 mOhms Total Losses = 23,1 W  $\Delta I = 31, 33 A$ 

#### CCM - PFC - 3kW 50 kHz



L = 340 uH 32 Turns Custom EQ47 Powder Edge 125 Round 2 x 1,6 mm Rdc = 15 mOhms Total Losses = 6,6 W  $\Delta I = 7,34 A$ 





## **High power conclusions**

- CCM can provide better performance and larger attenuation ratio when the power is high and the frequency is relatively low.
- For medium frequencies the TM inductors can still provide better performance than CCM ones. However the large current ripple should then be paid at the DM inductor and input capacitor size.
- For high frequency and large power the CCM does not help because with medium attenuation ratios the high frequency winding losses are too excessive and with large attenuation ratios the DC losses are too large.
- For the same magnetic size, the larger the size of the core and the better performance the powder core would offer because with the same number of turns it will offer a much larger inductance and therefore attenuation ratio.







# **Flyback Results**

- The same procedure followed with the boost and PFC inductor has been done with a Flyback transformer. The transformer has been optimized for the TM operation and then the inductance has been doubled and tripled for CCM operation.
- As it happened with the inductors the CCM does not add any benefit for the transformer since larger number of turns and conduction losses are required.



Input voltage = 70V Output voltage = 20V Output power = 65W Fsw = 76kHz Turns ratio = 7,5





# **Flyback Results**

#### TM - Flyback



L = 237 uH 23 Turns Custom PQ 24/15 Material Ferrite 3C95 Pri – 2xRound 0,25 mm Sec – TIW Litz 45x0,1 mm Rdc pri = 195 mOhms RDC sec = 4 mOhms **Total Losses = 1,17W** 

#### Simulation Results

BpkT (mT)=	288
Core Losses (W)=	0.279
Winding Losses (W)=	0.894
Total Losses (W)=	1.17
Max Temp (°C)=	113
Core Surface Temp (°C)=	101
Winding Surface Temp (°C)=	113
Central Leg Surface Temp (°C)=	104

#### CCM – Flyback





L = 483 uH 38 Turns Custom PQ 24/15 Material Ferrite 3C95 Pri – Round 1x0,375 mm Sec – 2xTIW Round 0,63 mm Rdc pri = 295 mOhms RDC sec = 7 mOhms **Total Losses = 1,73W** 

Simulation Results	
BpkT (mT)=	268
Core Losses (W)=	0.083
Winding Losses (W)=	1.644
Total Losses (W)=	1.73
Max Temp (°C)=	137
Core Surface Temp (°C)=	112
Winding Surface Temp (°C)=	137
Central Leg Surface Temp (°C)=	119

#### CCM – Flyback





L = 718 uH 45 Turns Custom PQ 24/15 Material Ferrite 3C95 Pri – Round 0,335 mm Sec - 2xTIW Round 0,5 mm Rdc pri = 424 mOhms RDC sec = 12 mOhms **Total Losses = 2,18W** 

#### Simulation Results

BpkT (mT)=	302
Core Losses (W)=	0.056
Winding Losses (W)=	2.12
Total Losses (W)=	2.18
Max Temp (°C)=	150
Core Surface Temp (°C)=	120
Winding Surface Temp (°C)=	150
Central Leg Surface Temp (°C)=	127





- Entering CCM by increasing frequency increases power throughput without transformer saturation
  - Doubling the frequency increases power by a factor of 1.5
- The efficiency will deteriorate significantly, but this may not be a problem for high power delivery at a low duty cycle.
- A variety of applications will benefit for intermittent CCM (printers, audio amps, etc.)





- At sub-kW, CCM operation of both Boost and Flyback converters is unlikely to offer power density or efficiency improvements
- CCM becomes attractive at >kW power levels
- CCM operation is beneficial for converters delivering pulsed power at low duty cycle.
  - Improved power density over TM.

