

Conducted EMI

Nidcom



WURTH ELECTRONICS MIDCOM INC.

2010

Retlif Labs




Presented by: Douglas Toth

Topics

Nidcom

1. EMI/EMC – General Information – Why need EMI reduction?
2. Materials – Frequencies for Effectiveness
3. Shielded and Un-shield comparison
4. Inductors vs. Ferrites
5. Common Mode and Differential Mode
6. Conducted EMI emission analysis
7. Information on Transformers

Switching Regulator Topologies

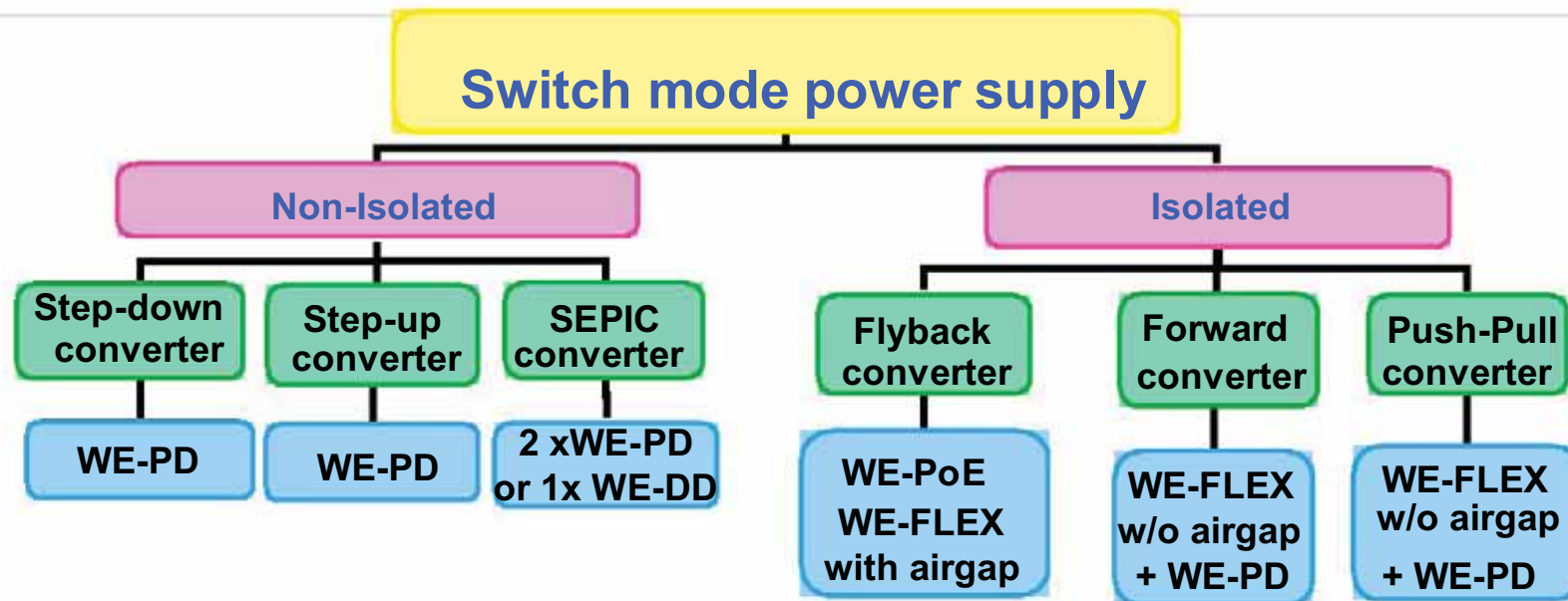

Insulation Voltage
 → 0-100V ----- → 0-500V ----- → WE-PoE
 ≥1500V



Switching Regulator Topologies

Nidcom



Switching Regulator Topology	Inductive Components
Step-down-converter (Buck-Converter)	Storage inductor => WE-SI/FI or WE-HC-/ or WE-PD-Series
Step-up-Converter (Boost-Converter)	Storage inductor => WE-SI/FI or WE-HC-/ or WE-PD-Series
SEPIC Single ended primary inductance converter CUK converter	Coupled storage inductor with two windings or two identical storage inductors => WE-DD or WE-FLEX (with airgap !)
Flyback-Converter	Flyback-transformer => WE-FLEX (gap !)
Forward-Converter	Transformer and storage inductor => WE-FLEX (no gap !)
Push-pull Converter	Transformer and storage inductor => WE-FLEX (no gap !)

Inductor Selector Guide

Nidcom



WE Inductor Selector Version 1.1.1

File Service ?

www.we-online.com

more than you expect

WE Inductor Selector
Easy Inductor Selection for DC/DC Converter

Select Converter Topology: ☒ Buck Converter ☐ Boost Converter ☐ SEPIC Converter ☐ Manual Selection

Calculations:

$L_{opt} = 24.263 \mu\text{H}$
 $I_{rms} = 3.000 \text{ A}$
 $I_{peak} = 3.300 \text{ A}$
 $\Delta I_L = 0.600 \text{ A}$
 $V_t = 0.286$
 $t_{on} = 1.429 \mu\text{s}$


Series **Size** **Ordercode** **L** **RDCtyp** **I_N** **I_{Sat}** **L** **W** **H** **Core Mat** **T_{amb}** **T_{max}** **Shielded**

min **max**

Sorting (Type | Sequence) **↑ 1** **↑ 2** **↑** **↑** **↑** **↑** **↑**


WE-PD	XXL	7447709220	22.000	33.300	5.300	6.500	12.00	12.00	10.00	Nickel12n	85	125	yes
WE-PD	L	744771122	22.000	31.000	3.370	3.770	12.00	12.00	6.00	Nickel12n	85	125	yes
WE-PD	XL	744770122	22.000	33.000	4.100	5.000	12.00	12.00	8.00	Nickel12n	85	125	yes
WE-PD	XL	744770127	27.000	35.000	3.700	3.800	12.00	12.00	8.00	Nickel12n	85	125	yes
WE-PD	XXL	7447709330	33.000	36.800	4.200	5.500	12.00	12.00	10.00	Nickel12n	85	125	yes
WE-PD	XL	744770133	33.000	47.000	3.200	3.600	12.00	12.00	8.00	Nickel12n	85	125	yes

Interference - Transmitter / Receiver

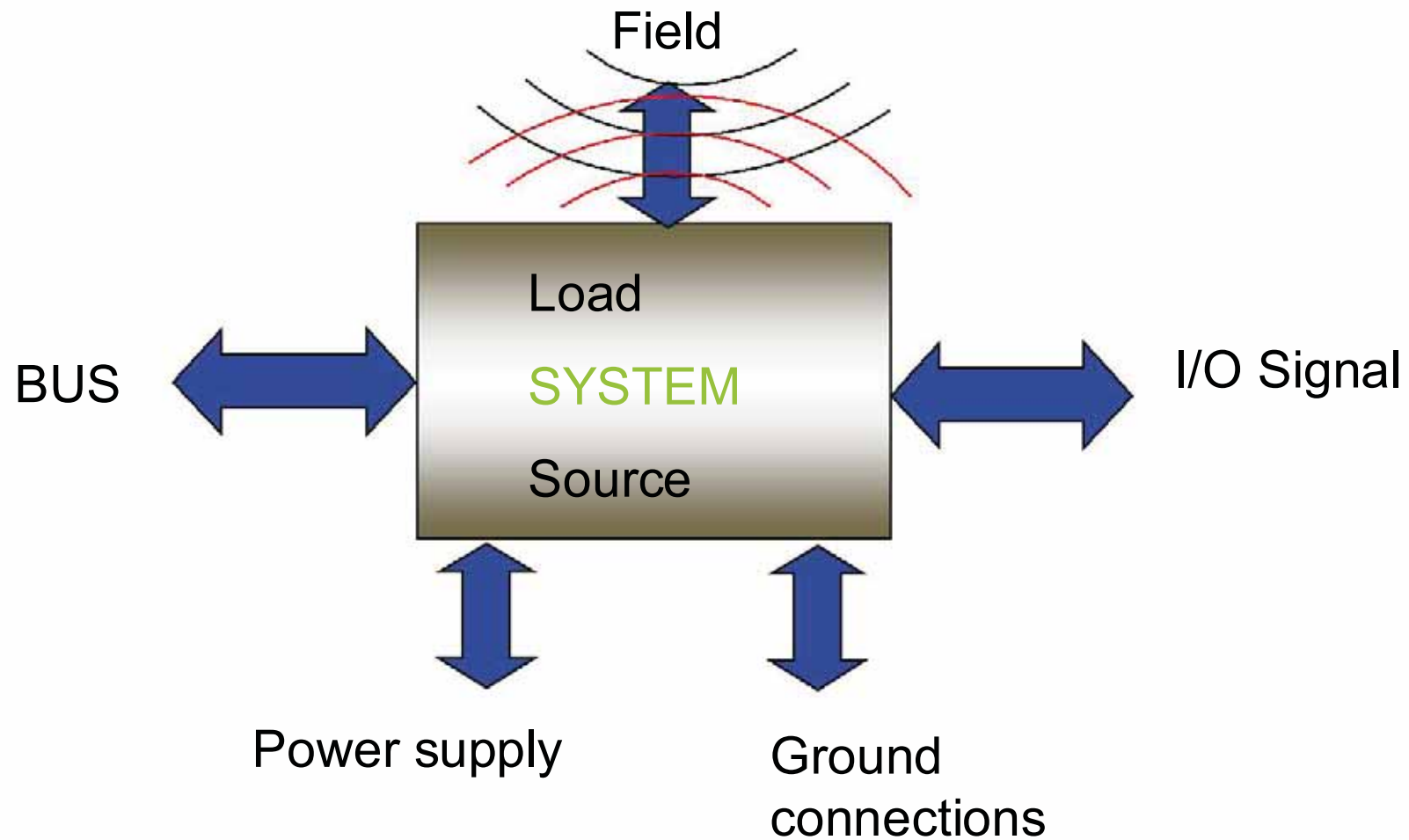


Interference - Frequency Range for EMI Tests

Nidcom

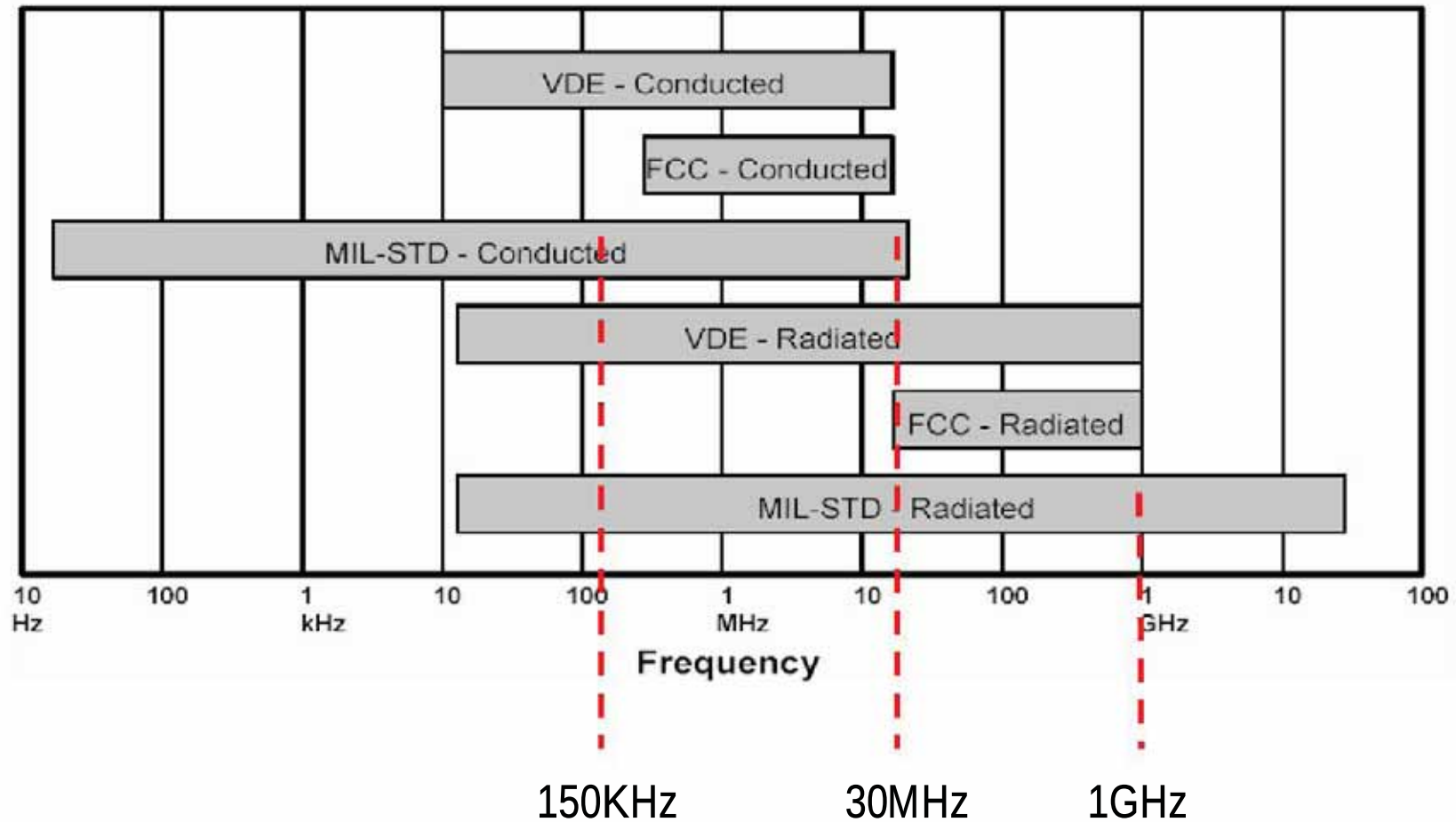


Interference Characteristics

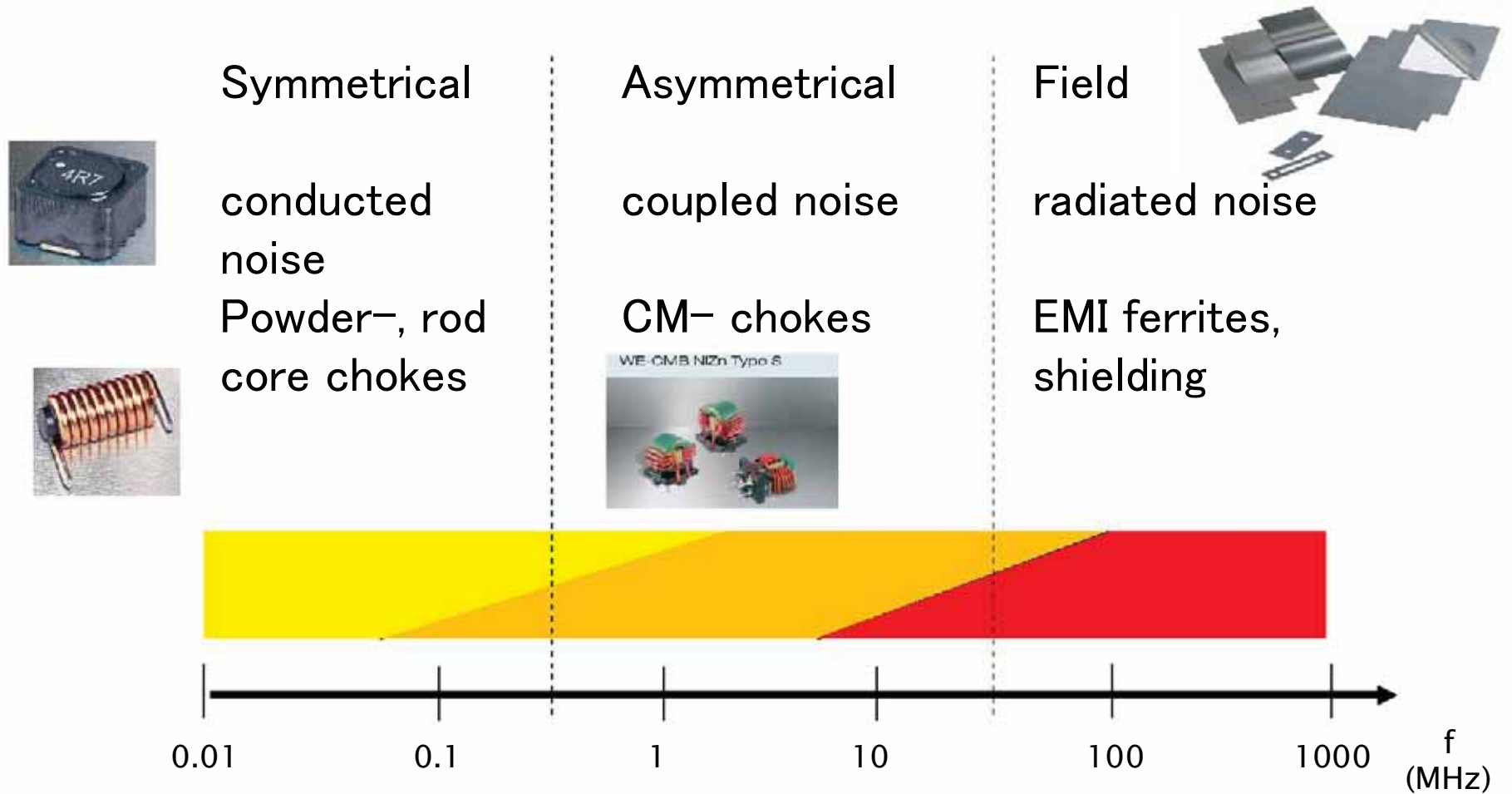

Comparison of Core Materials: Inductive behavior


Nidcom

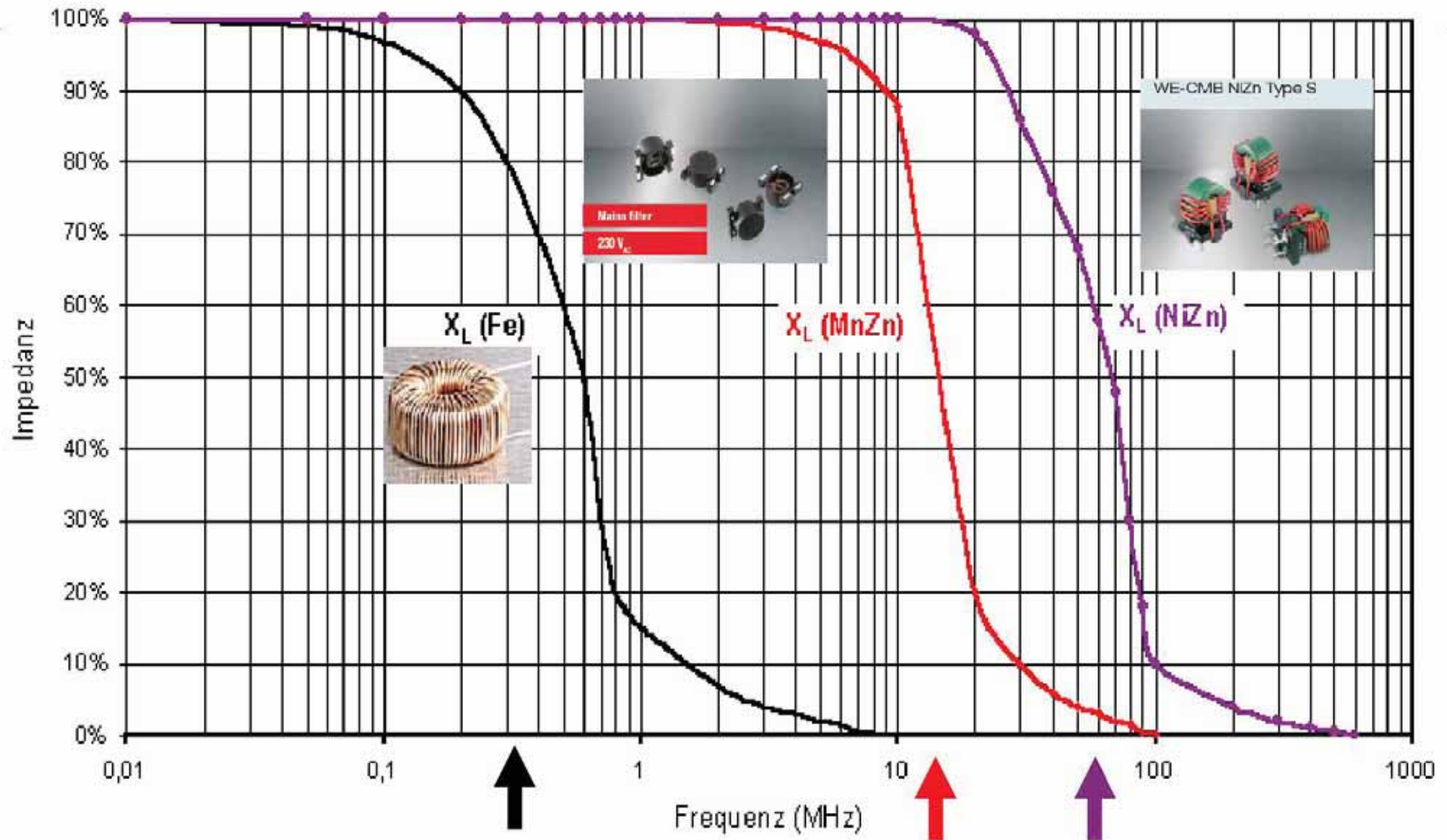


EMI: Conducted Emission Measurement



- Power supply V 1.0

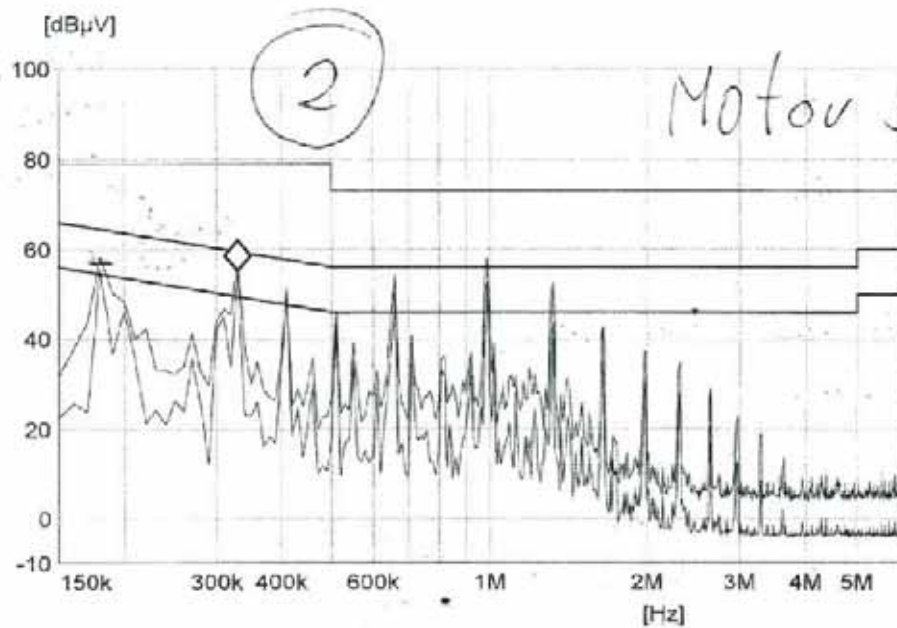

PCB


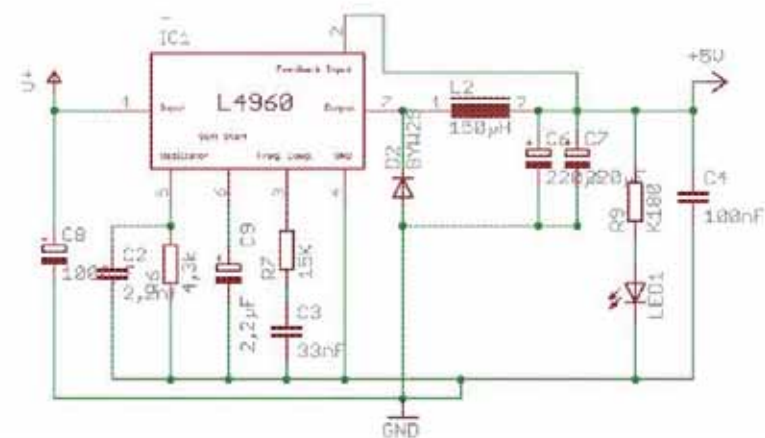


Buck Converter ST L4960/2.5A/fs 85-115KHz


EMI: Conducted Emission Measurement



- Power supply V 1.1

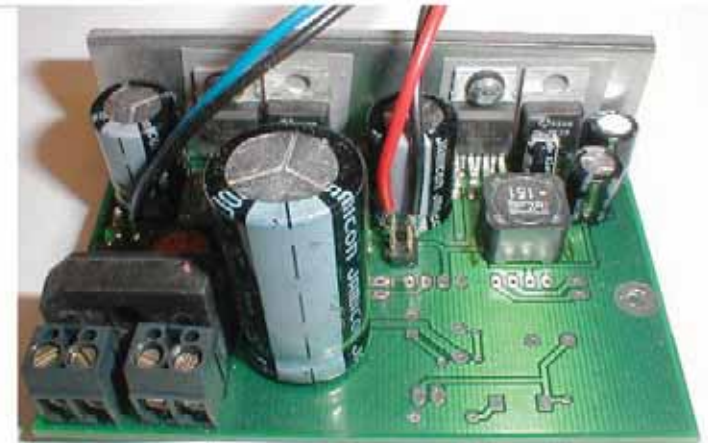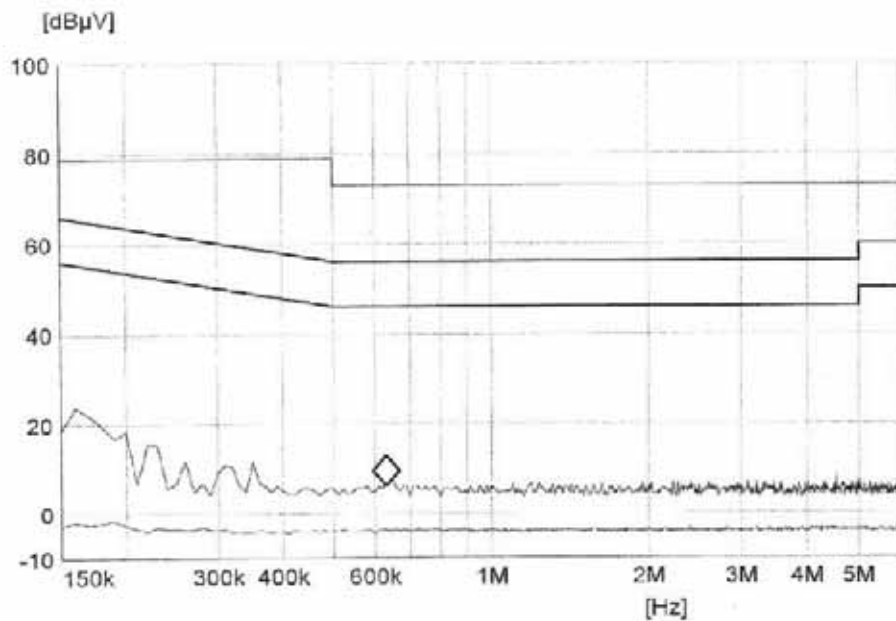

PCB

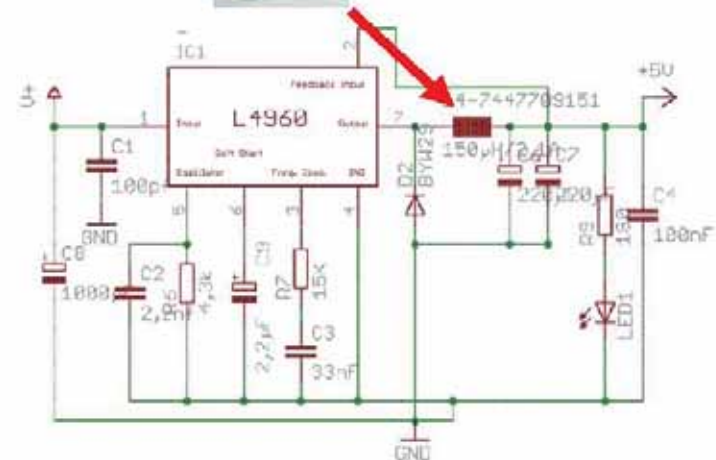

Schematic

EMI: Be Aware:

Nidcom

- Select the right parts for your application
- Do not always look on cost

Very easy solution with a dramatic result!!!



Choke before





Choke after

or





EMI: Shielded vs. Unshielded Power Inductor

Nidcom

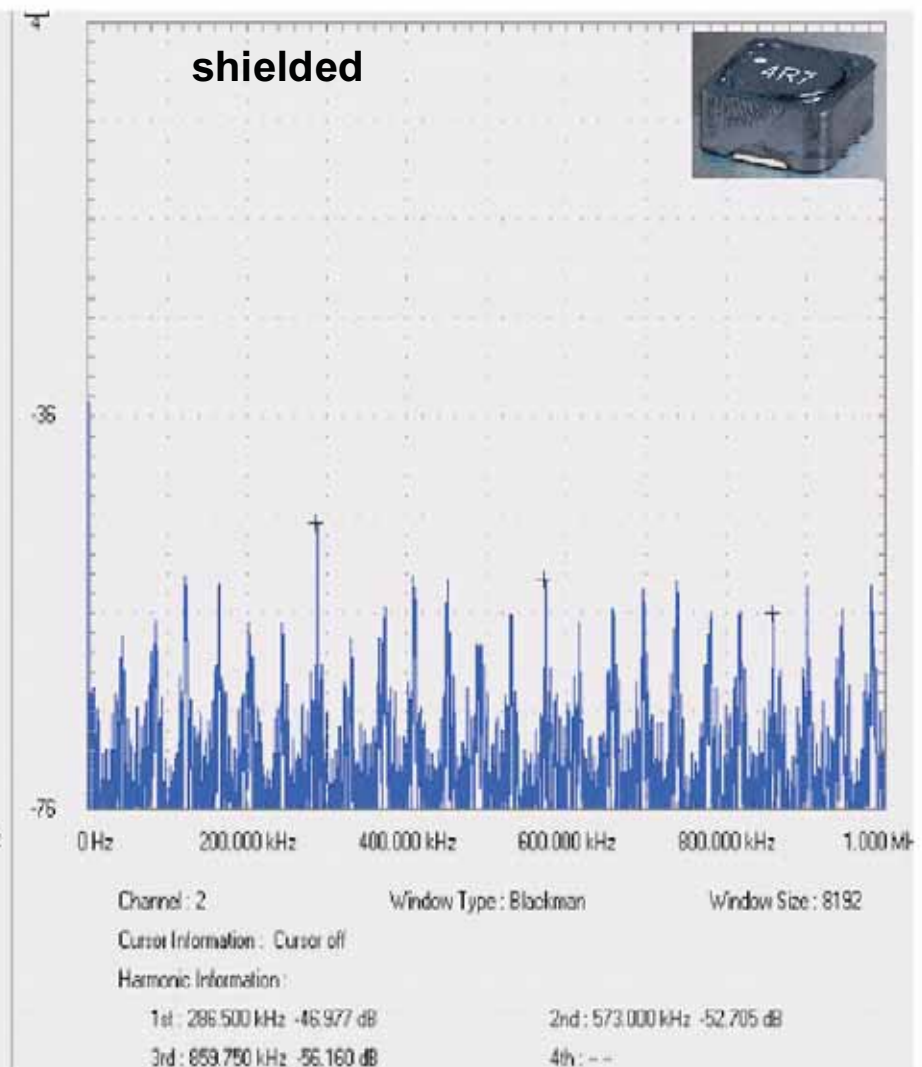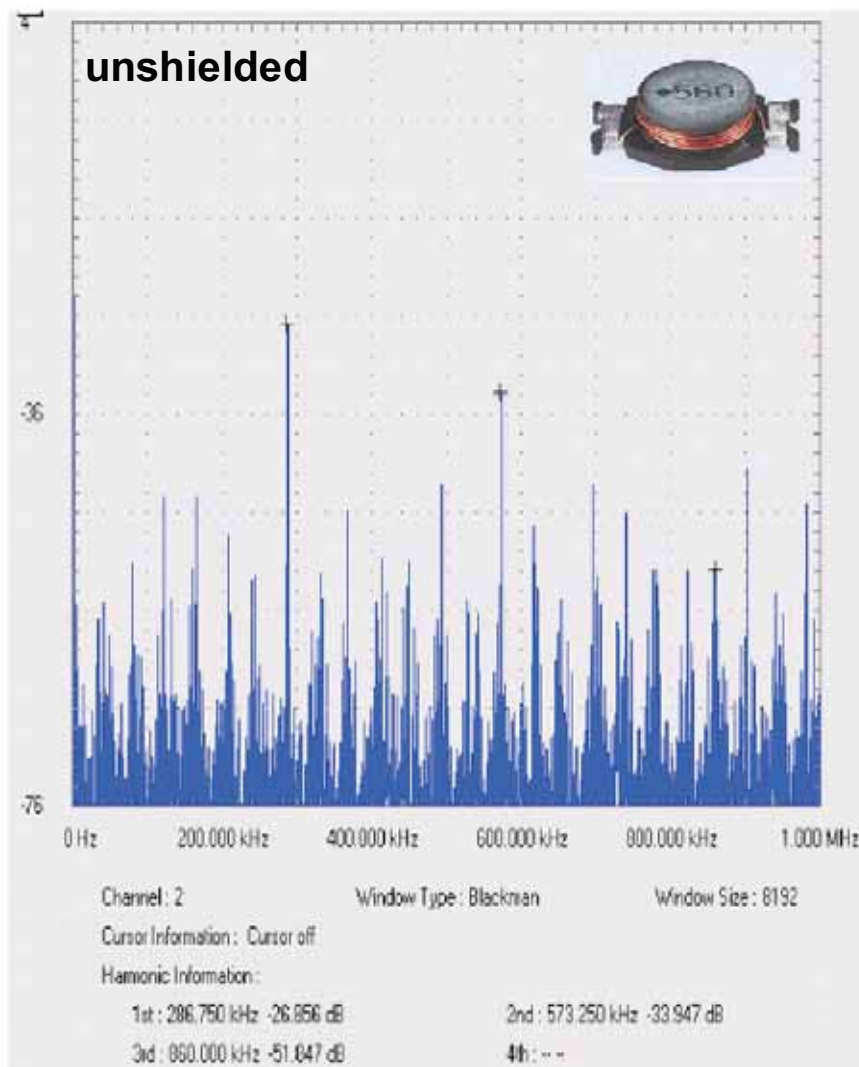

EMI: Shielded vs. Unshielded Power Inductor

Nidcom

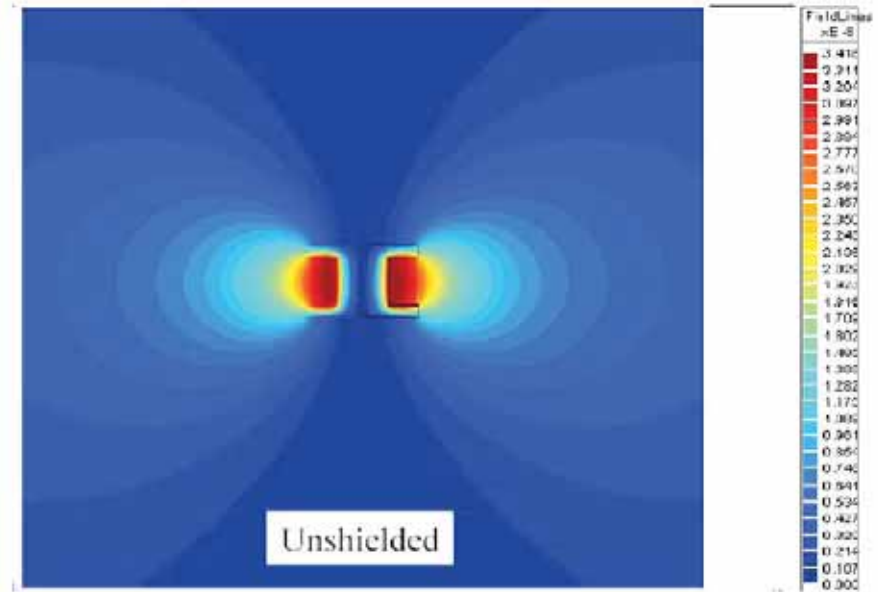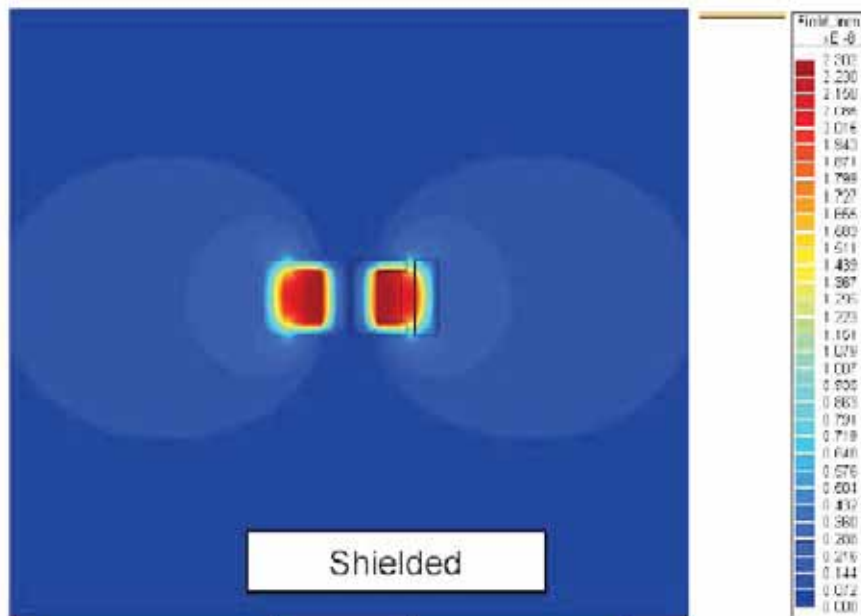


EMI: Shielded vs. Unshielded Power Inductor

Nidcom



- Magnetic field

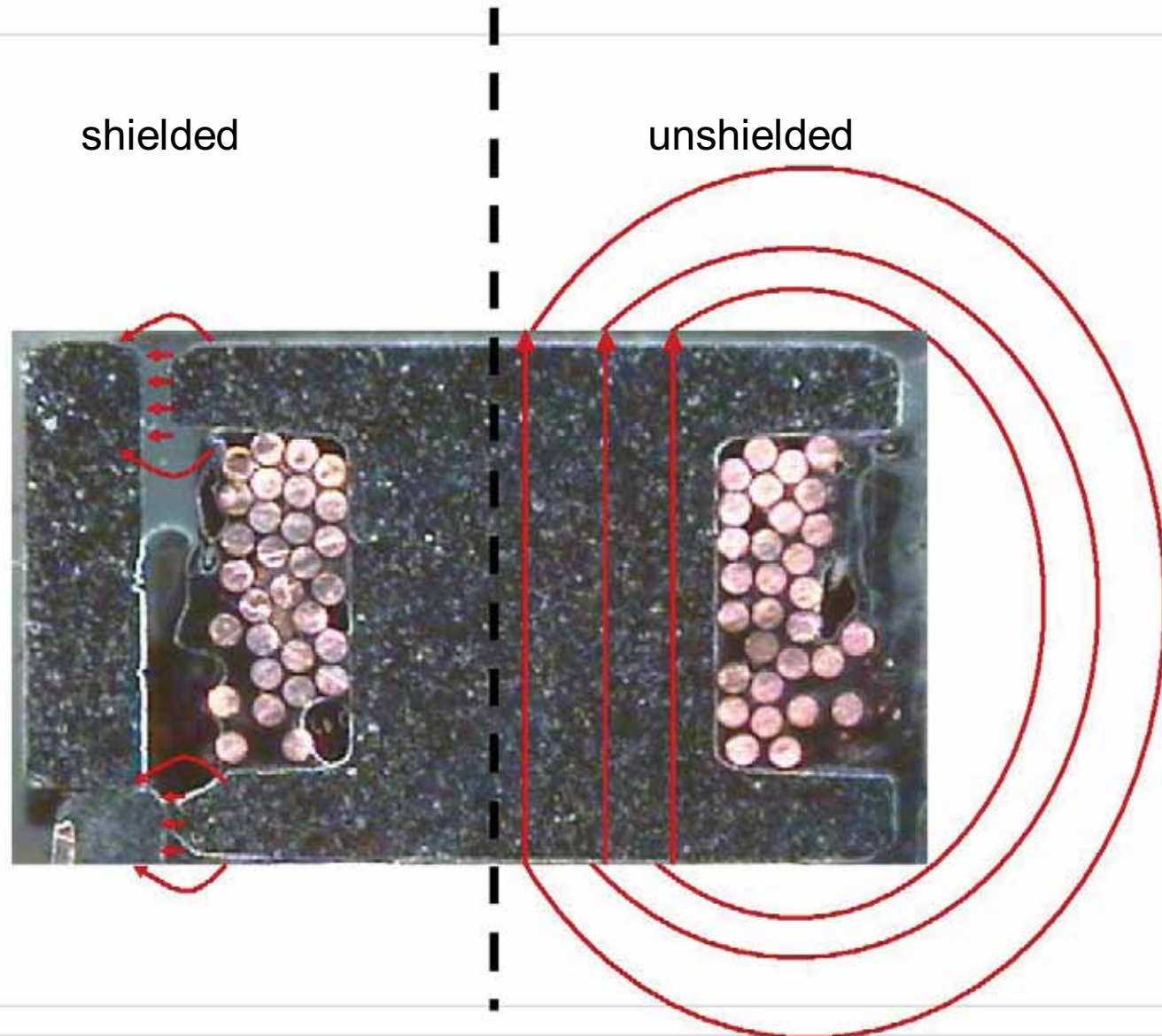

What is the main different between a Inductor and EMC-Ferrite?

Nidcom



=> Application **Storage Choke**: (Inductor)

Request: **lowest possible losses** at application frequency

high Q-factor

=> Application as **absorber-filter**: (EMC Ferrite)

Request: **highest losses possible** at application frequency range





low Q-factor

Ferrite Material


Nidcom



Ferrite Inductors WE-CBF

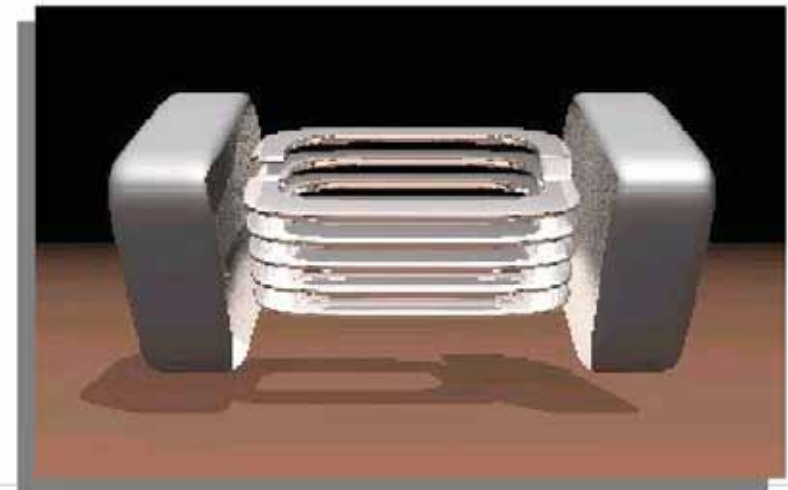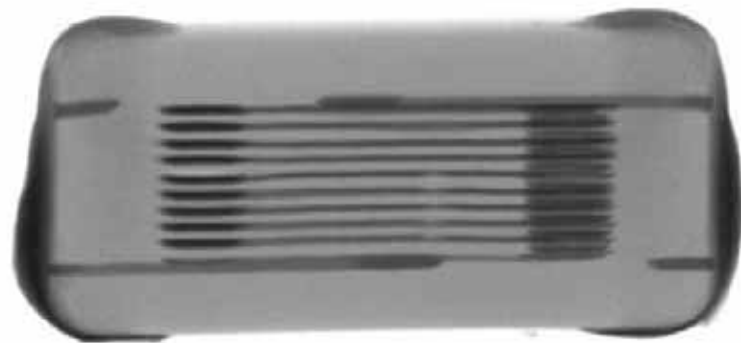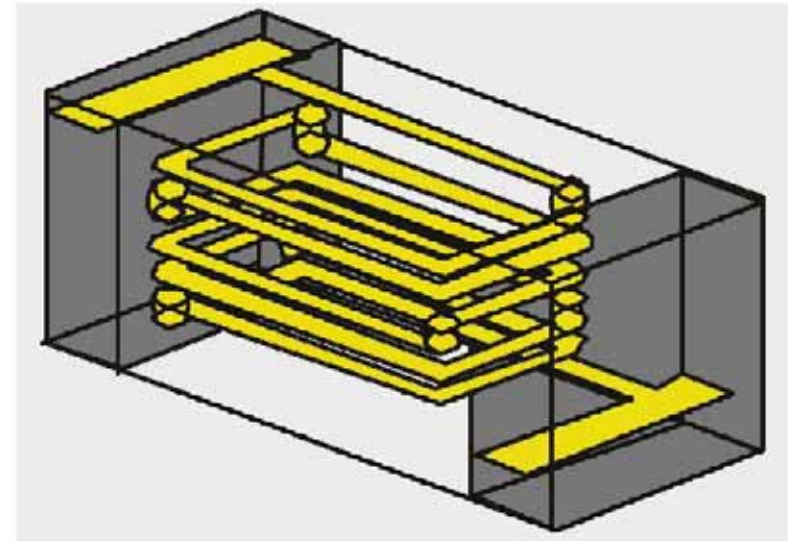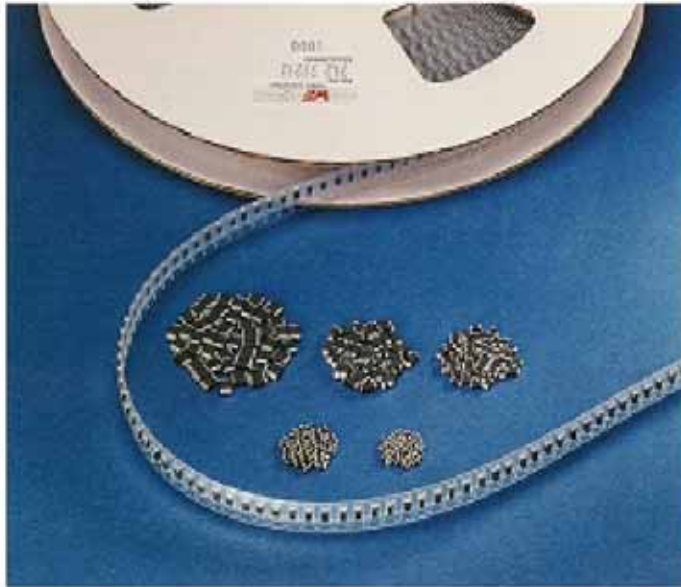



Inductor vs. EMI-Ferrite:

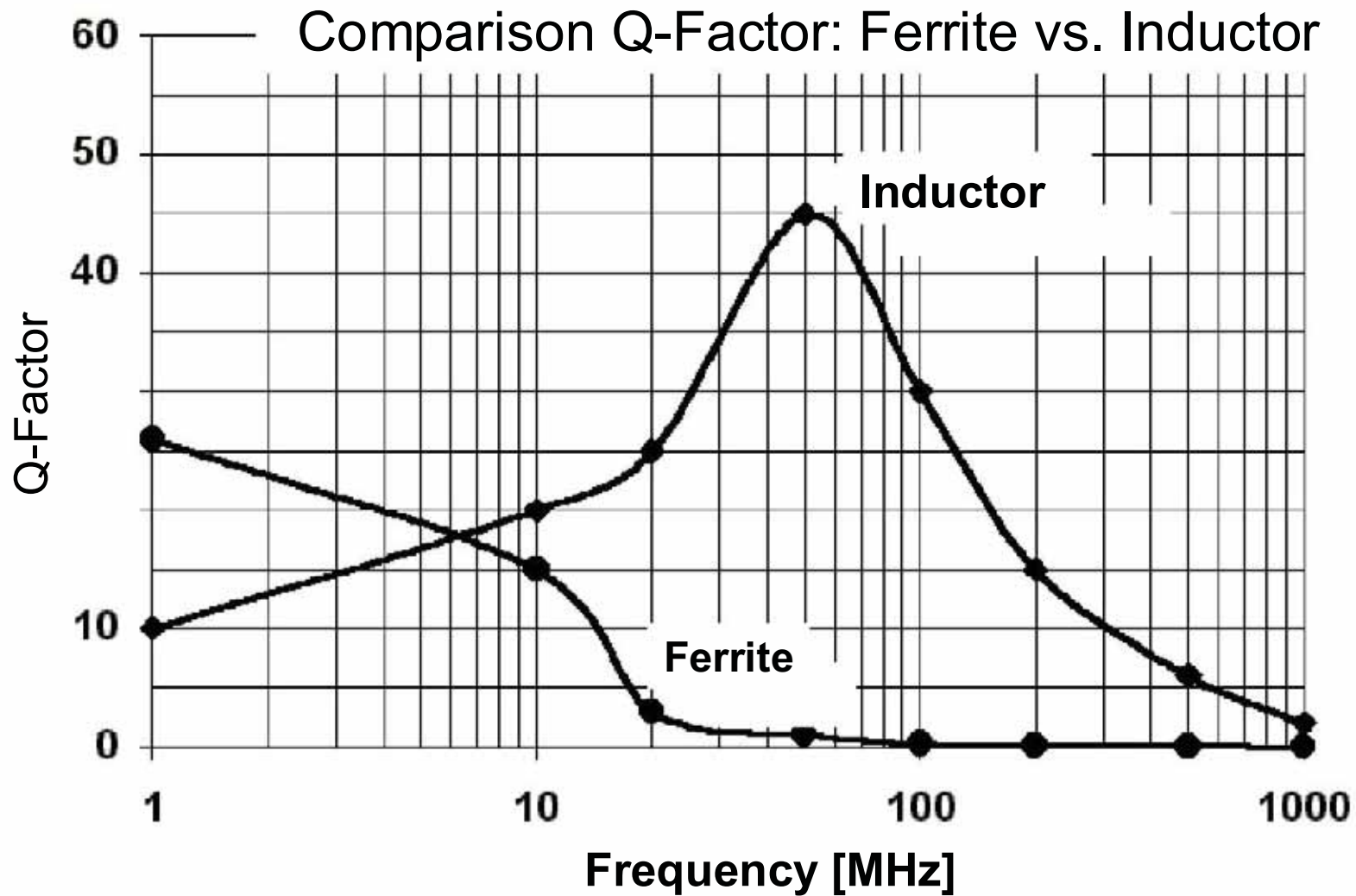

$$Q = \frac{X_L}{R_{\text{Losses}}}$$

Impedance increase vs. numbers of turns

Nidcom

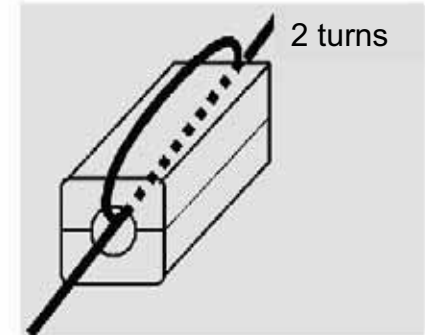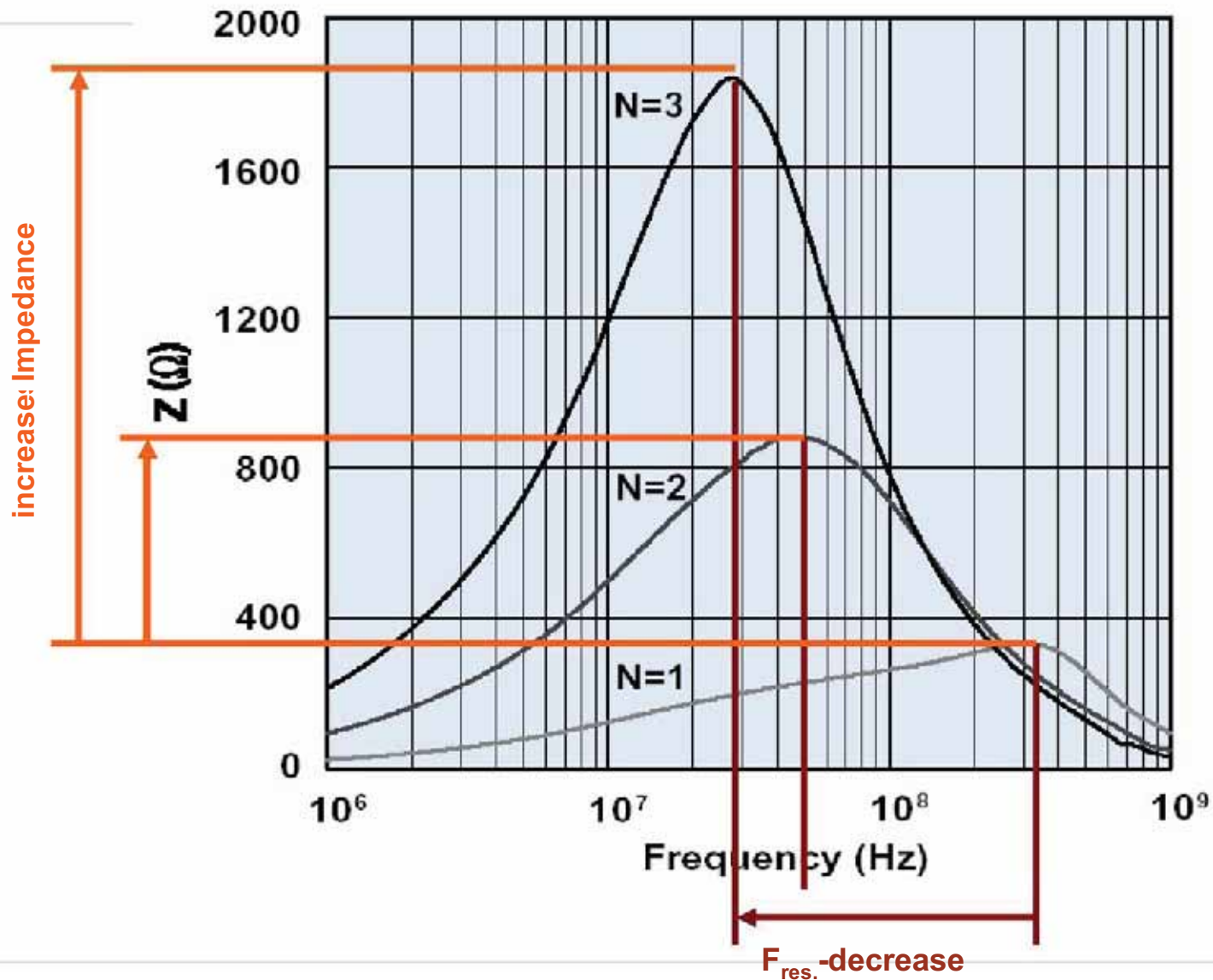


Why CMC's instead of Chip Beads

Nidcom




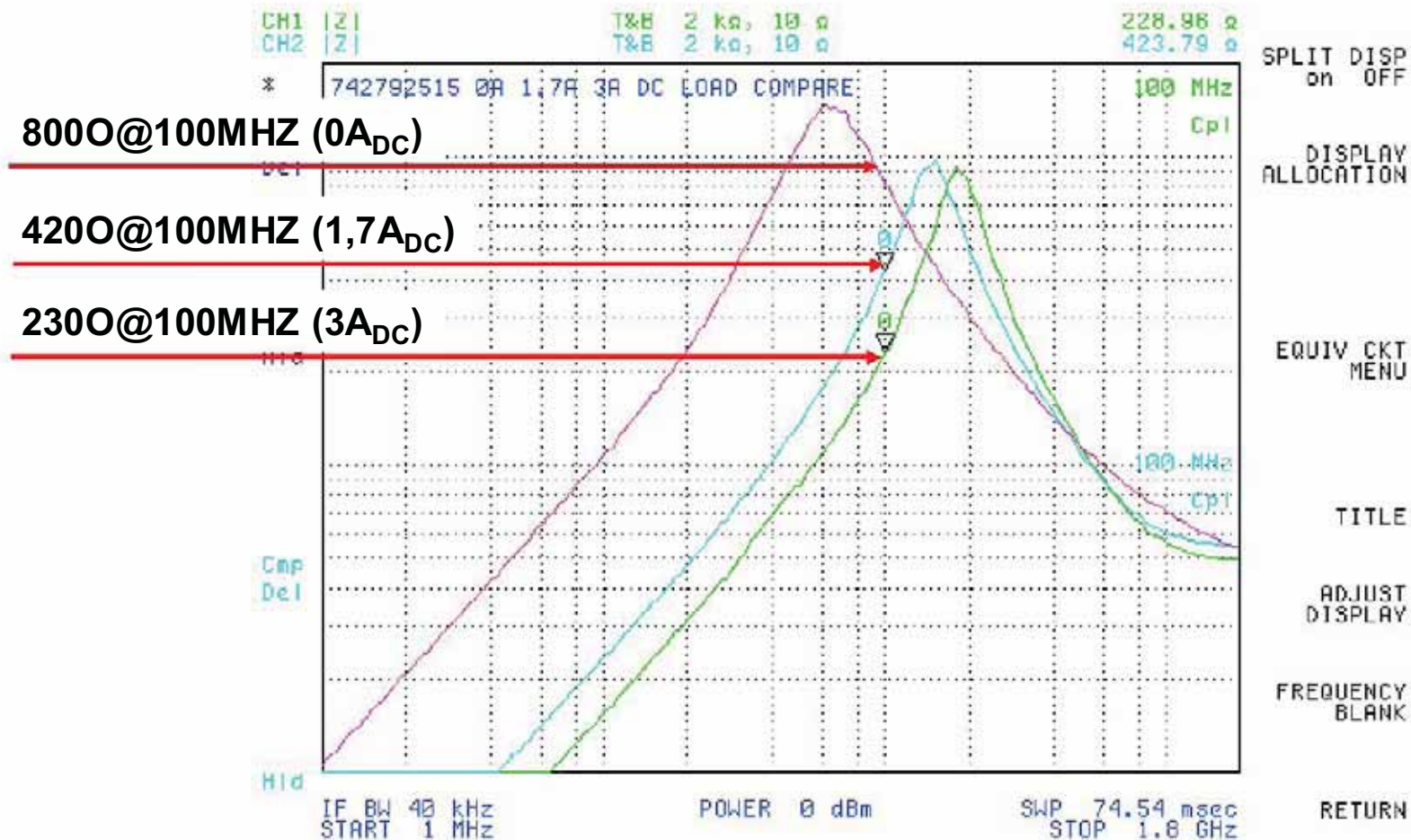
Impact of DC-bias (pre-magnetization (saturation))



742792515 (3A typ)

Impact of DC-Bias (pre-magnetization (saturation))

Nidcom

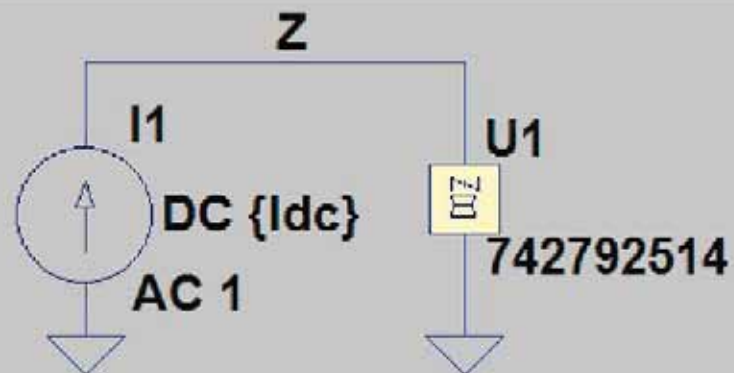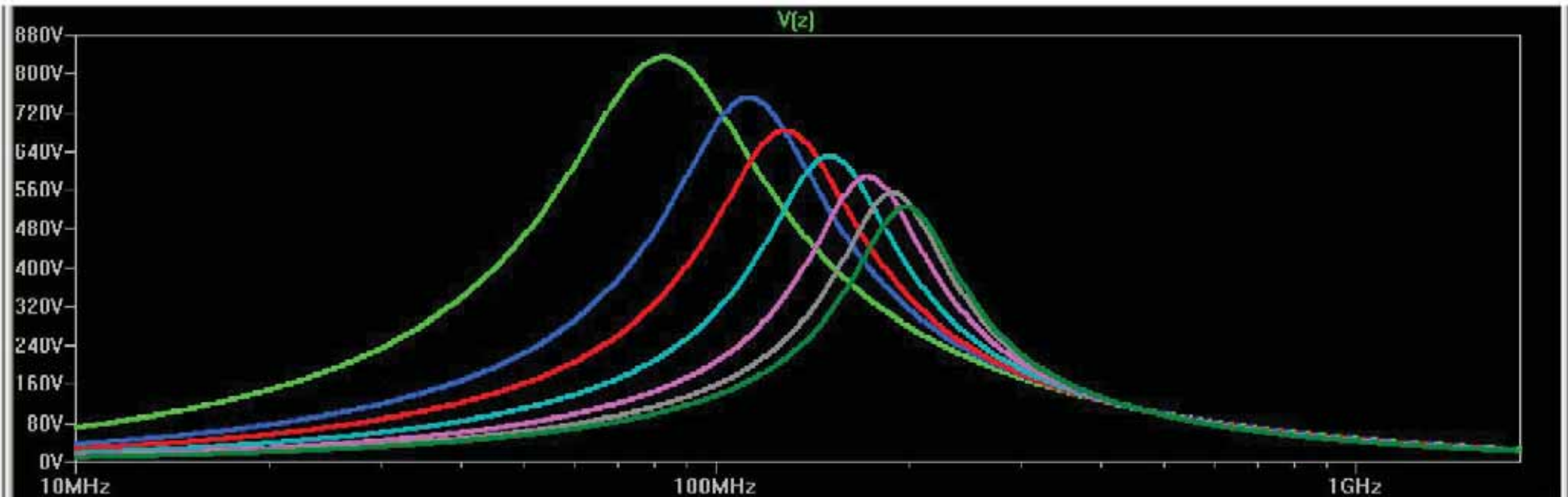


Common Mode Choke

Nidcom



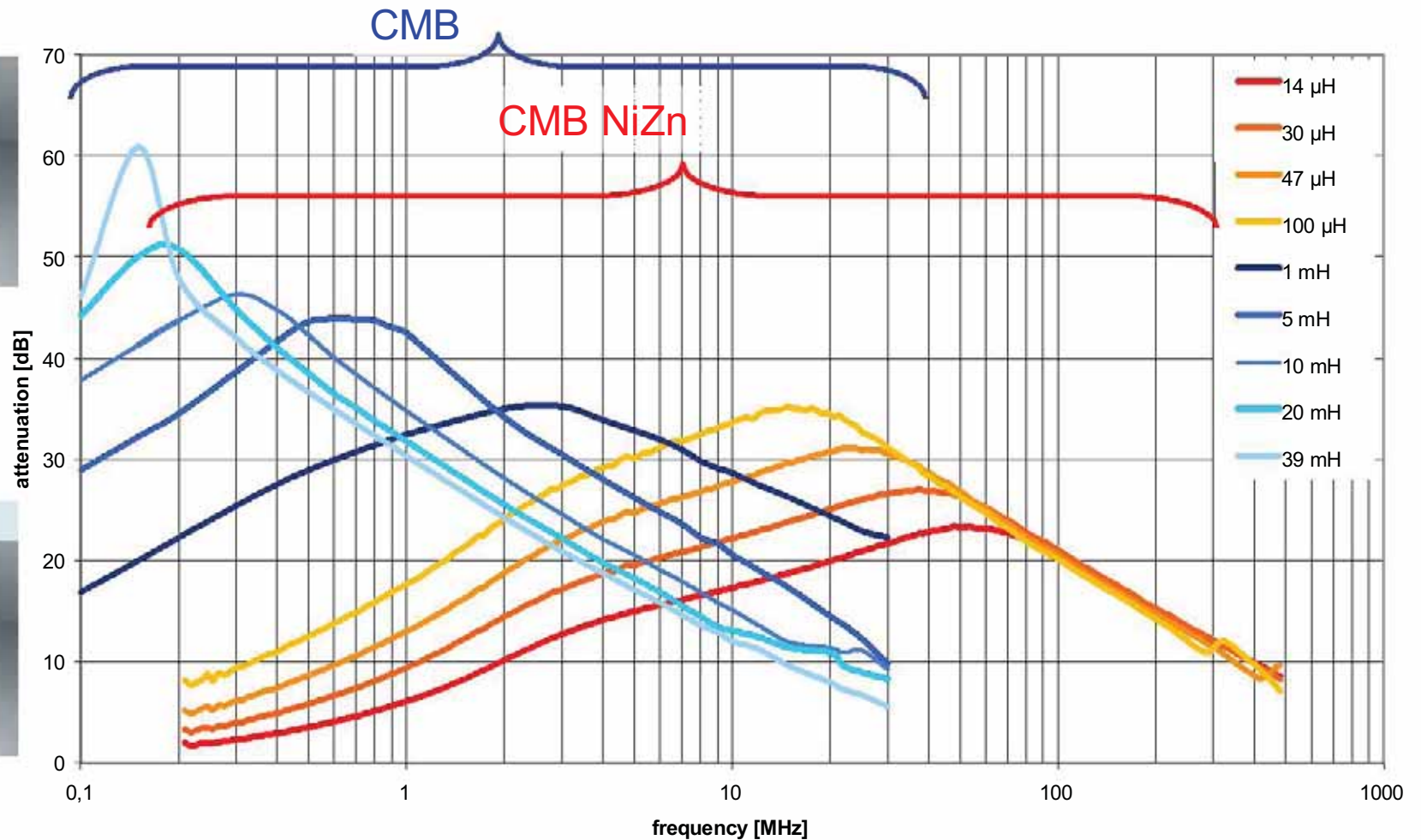- comparison common mode chokes CMB – CMB NiZn



Advantage of a Common Mode Choke


Nidcom



Filtering with two inductors or chip beads

Signal before filtering

after filtering

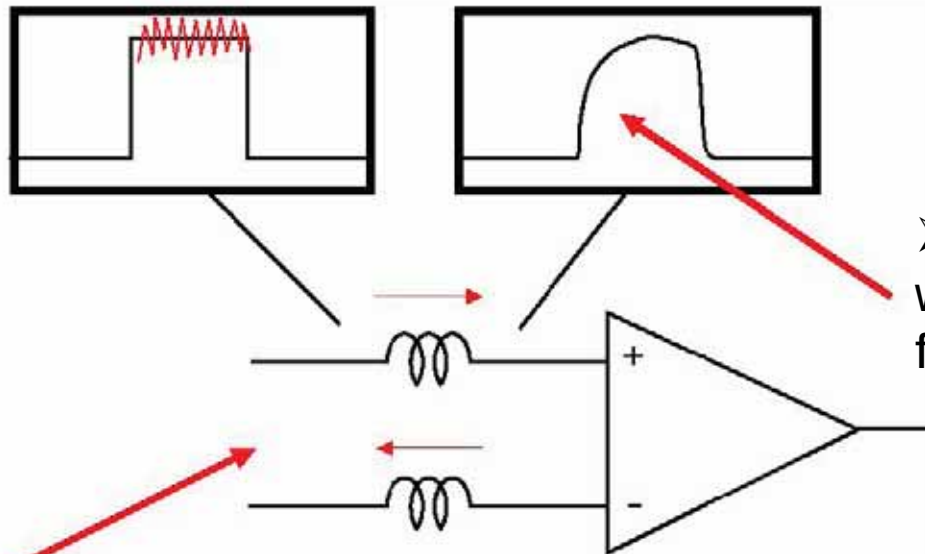

➤ Rise-time of the signal is affected, which could cause problems for fast data and signal lines

which occurs from the DC current the filtering performance is shortened.

➤ because of the pre-magnetization (saturation)


Advantage of a Common Mode Choke

Nidcom




Filtering with a Common Mode Choke


Signal before filtering

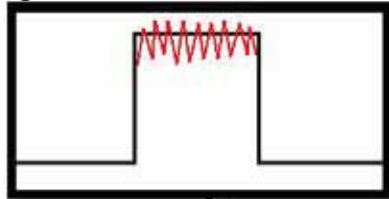

after filtering

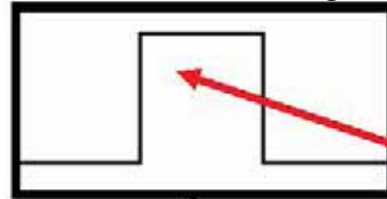

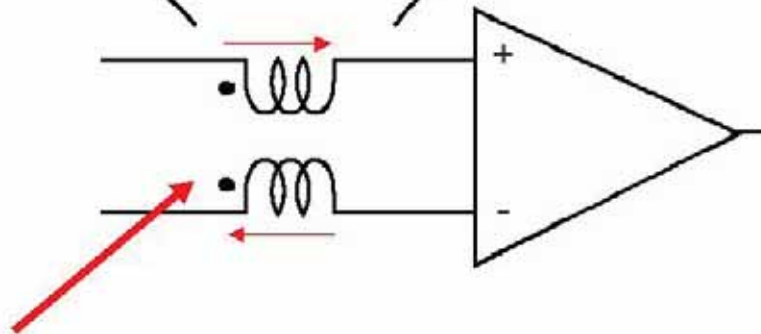- no affect on the signal rise-time, because of magnetic field compensation
- no influence of the wanted signal (the two windings are magnetically coupled)




- no pre-magnetization (saturation) occurs from the DC current, because of magnetic coupling
- much better performance vs. two separate inductors or ferrites

Differential Noise Example: Flyback Converter

Nidcom



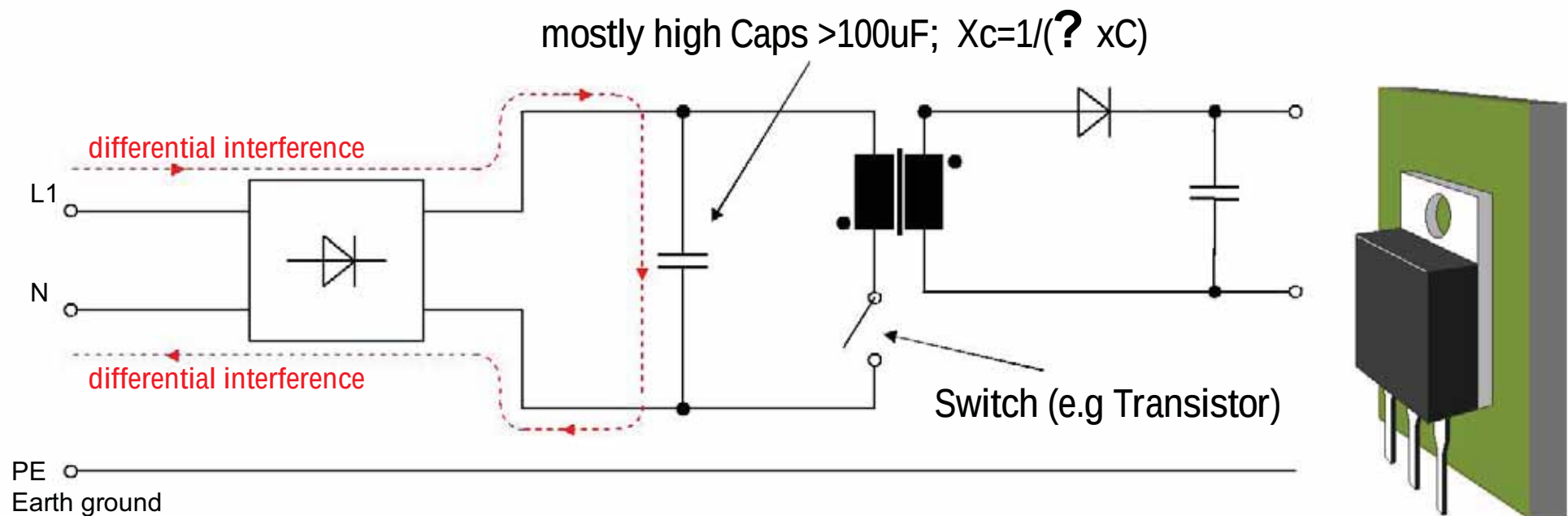Appearance of **differential noises** on the input line of a Flyback Converter




➔ differential interference occurs mainly at **lower** frequencies

Common Mode Noise Example: Flyback Converter

Nidcom




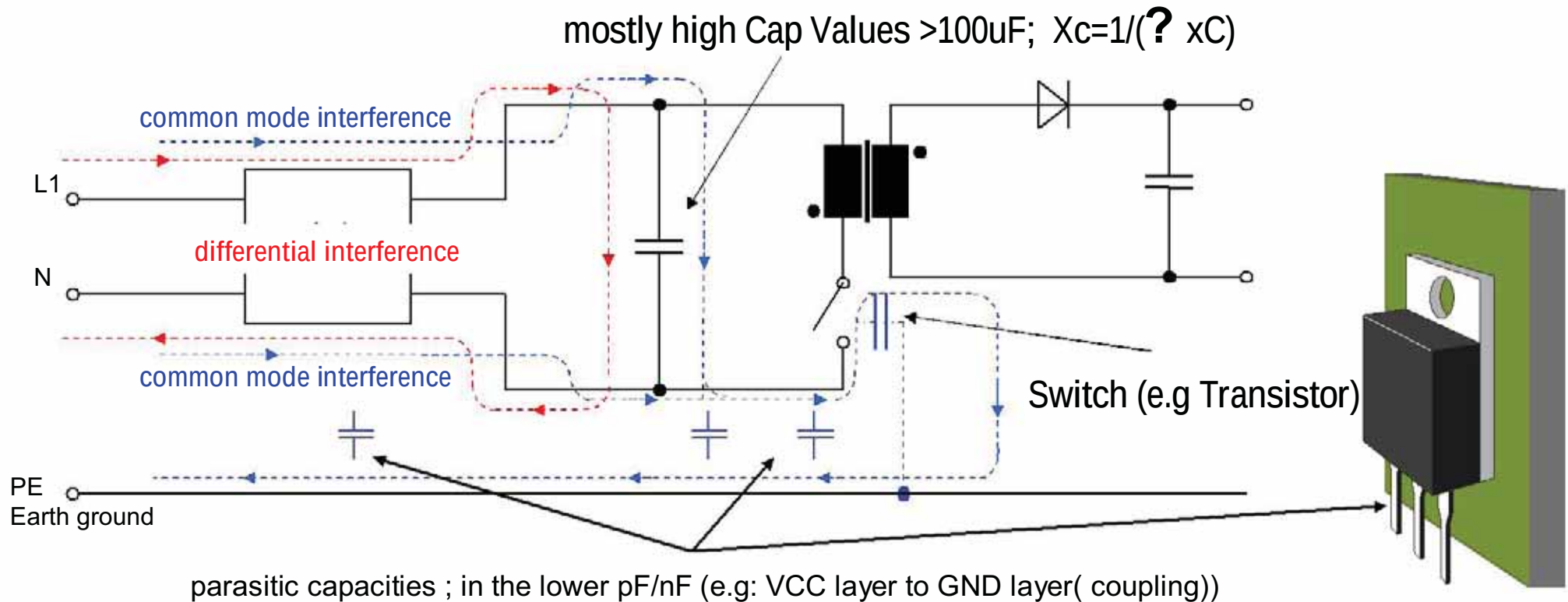Appearance of **common mode noises** on the input line of a Flyback Converter



common mode interference occurs mainly at *higher* frequencies

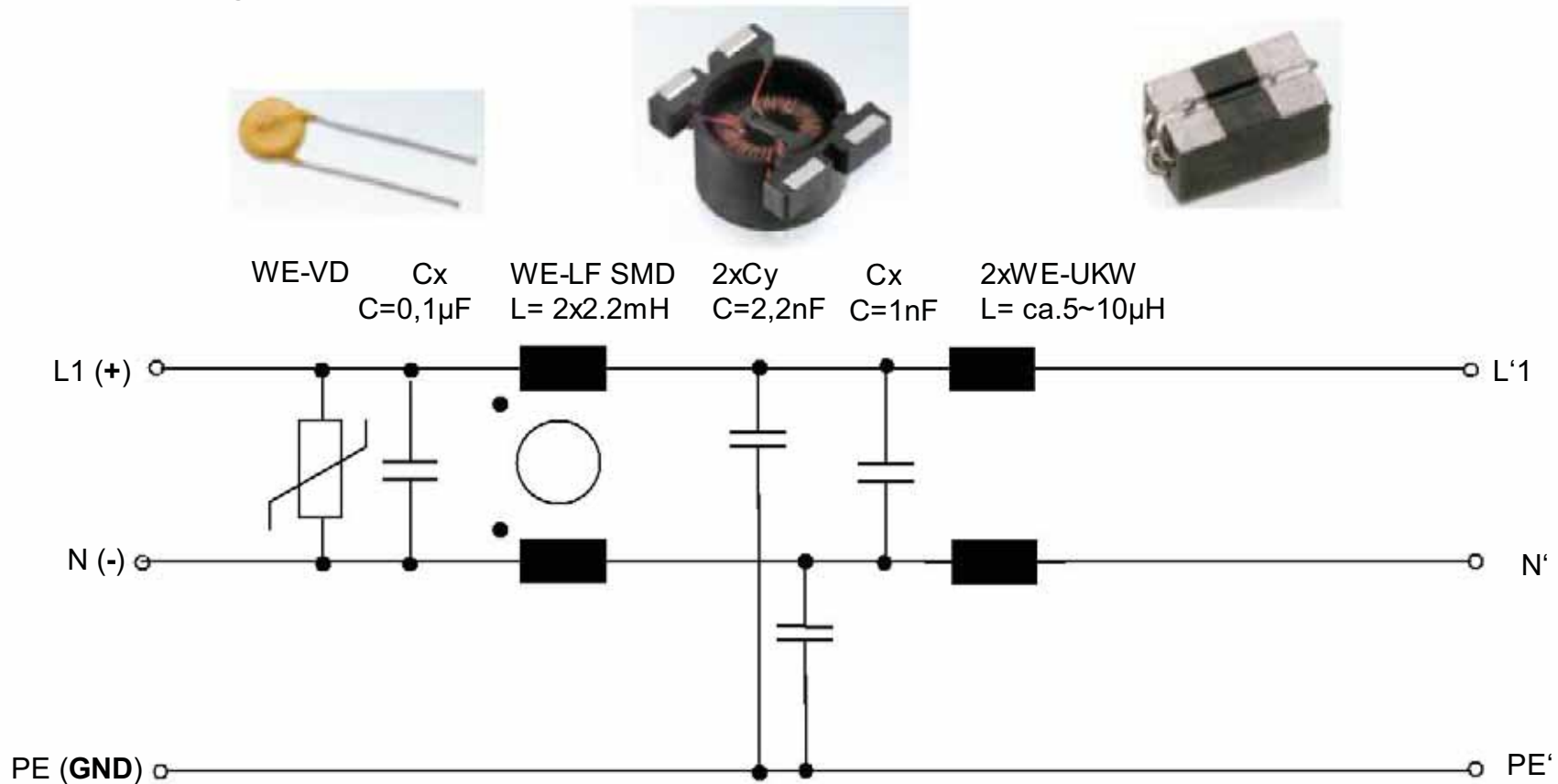Filtering the mains power line for common mode and differential mode




Common mode / Differential mode



Interference source

interference sink

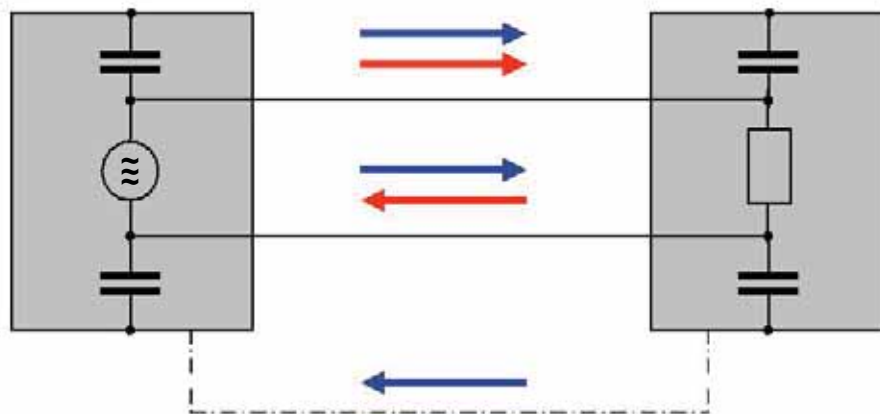

differential mode current

symmetrical interference voltage

Common mode current


Asymmetrical interference voltage

The DIFFERENTIAL Mode Signal creates a Flux in opposite directions – Thereby canceling

The COMMON MODE signal does not cancel and an Inductive Impedance is created thereby acting as a filter

Functionality of a common mode choke:

Nidcom

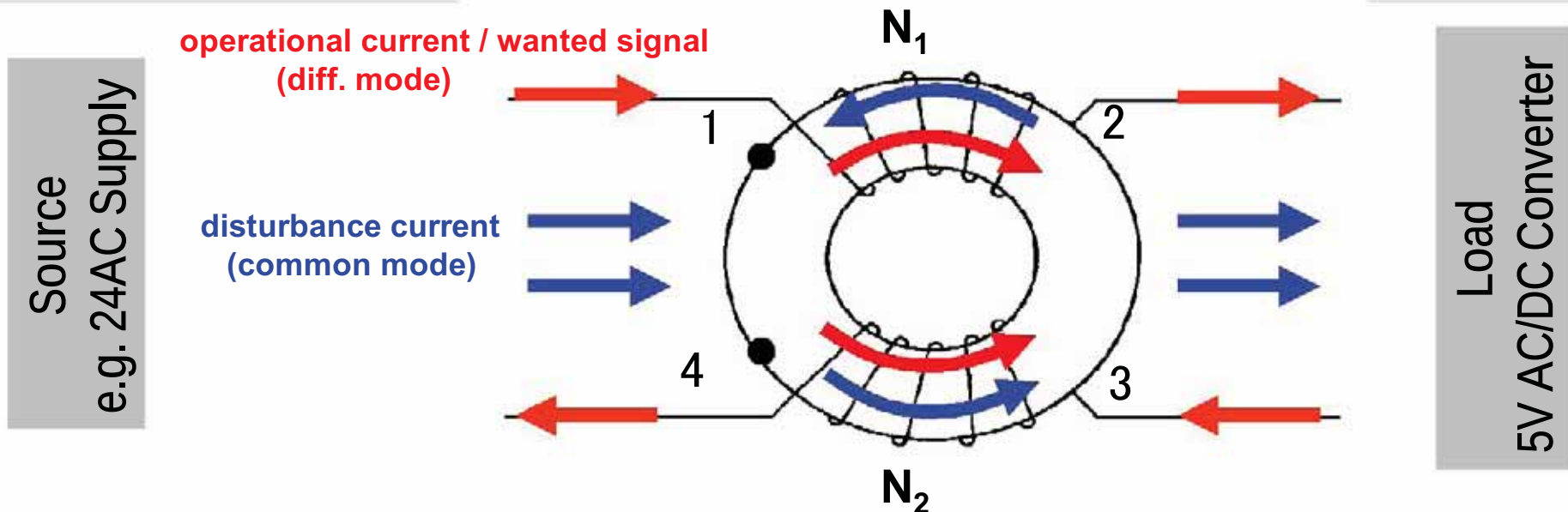

The DIFFERENTIAL Mode Signal creates a Flux in opposite directions – Thereby canceling
 The operational current (diff. mode) is routed by all relevant conductors through the core (e.g. +/- or L/N). That's why the magnetic fields of these two conductors compensate each other to zero => no influence on the wanted signal

The COMMON MODE signal does not cancel and an Inductive Impedance is created thereby acting as a filter


The disturbance current flows on both wires in the same direction and generates a magnetic field in the toroidal core => the choke is able to filter unwanted noises.

Unbalanced Current

Nidcom




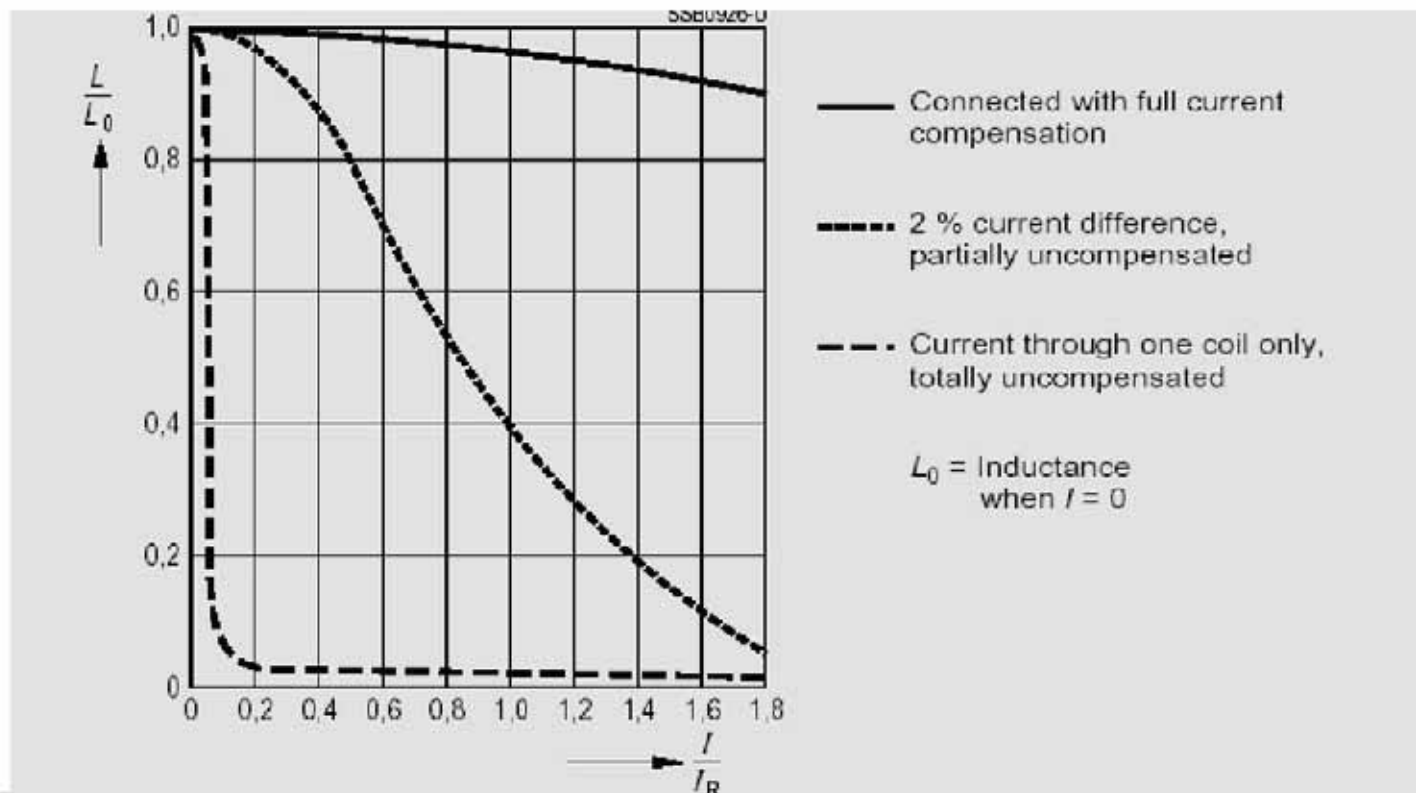- the operating current on both conductors is almost the same. When the difference between input and output current is too big, the common mode choke is no longer compensated and starts saturating very fast !




Common Mode Choke

sectional winding

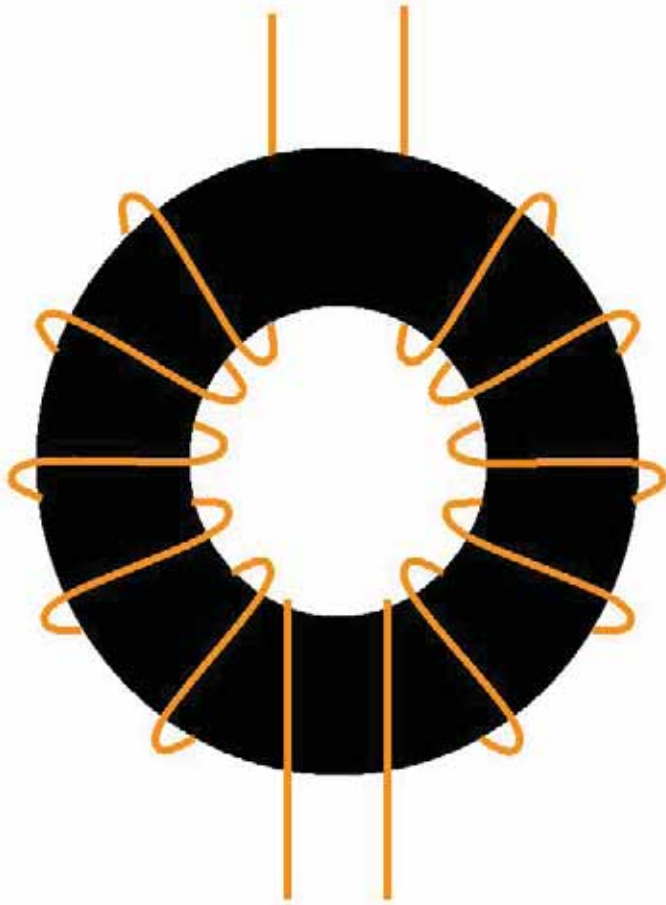

< advantage? >

bifilar winding

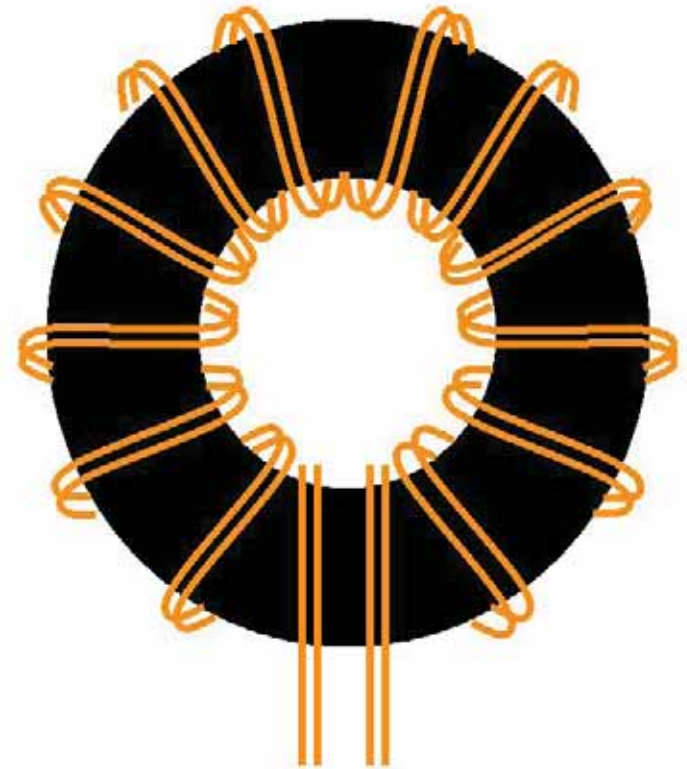


Stray inductance: Bifilar / Sectional

Nidcom




Sectional

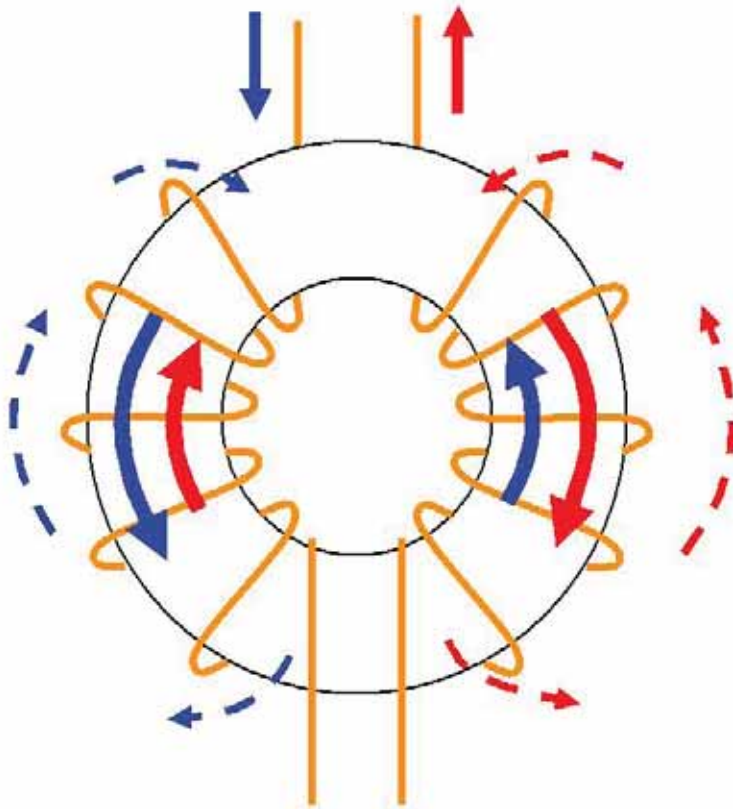

$$L_S \sim 0,5 \dots 2\% * L_R$$

Bifilar

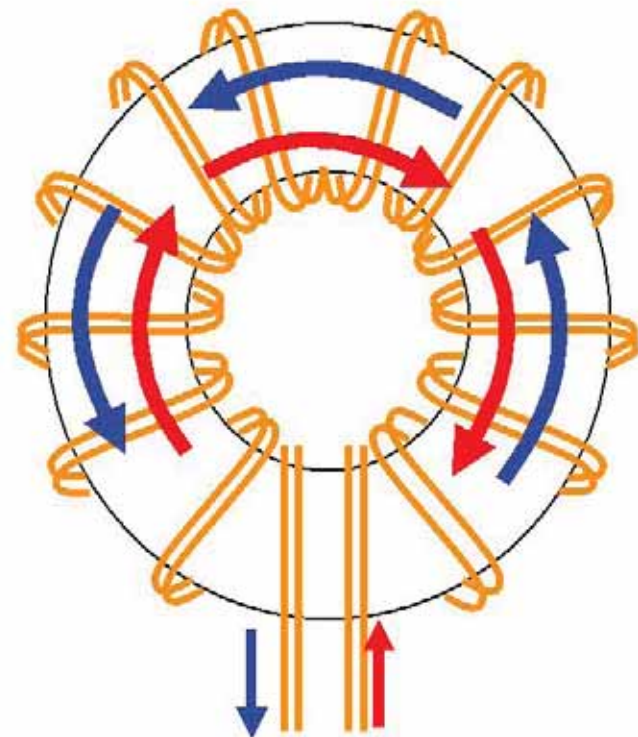

$$L_S \sim 0,1 \dots 1,0 \text{ ‰} * L_R$$

Sectional winding:

Nidcom





For example: WE-SL2 744227S

Common Mode suppression



Differential Mode suppression is high!

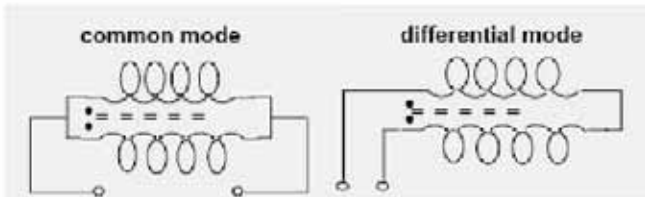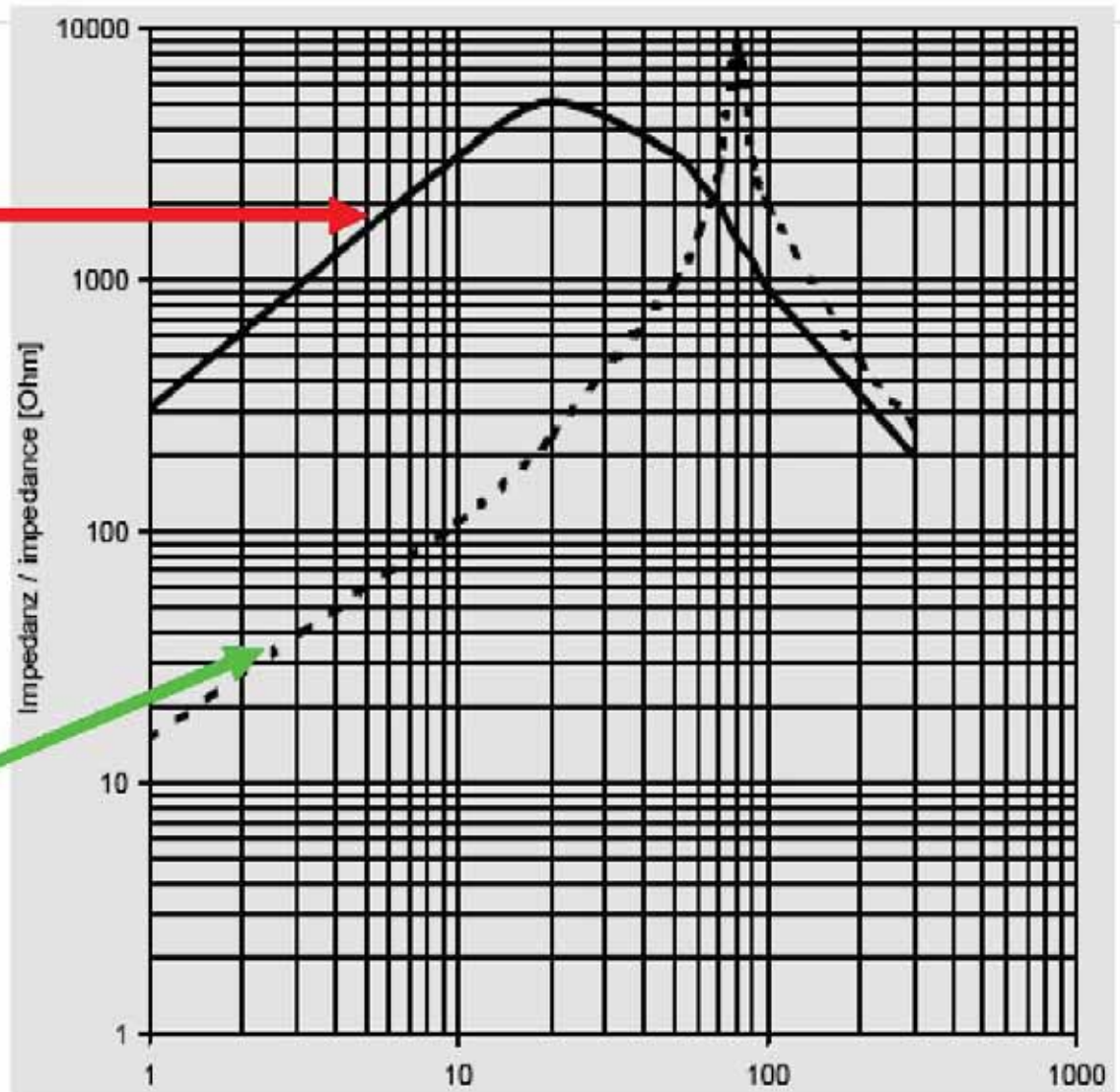

Bifilar winding vs. Sectional winding

Nidcom




For example: WE-SL2 744227

Common Mode suppression



Differential Mode S-Type

Differential Mode suppression is low!

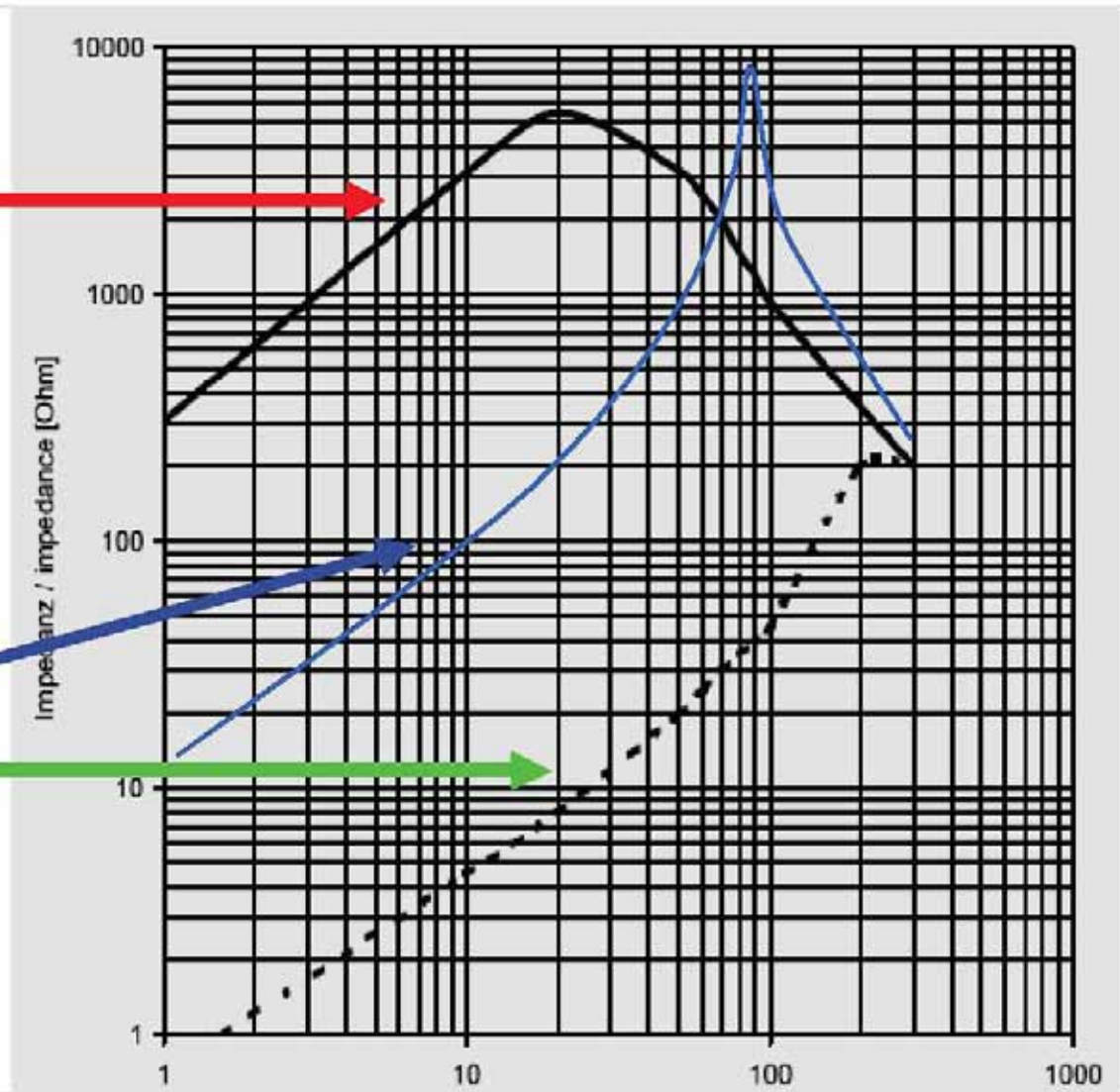

Common mode chokes for SMD:

Nidcom

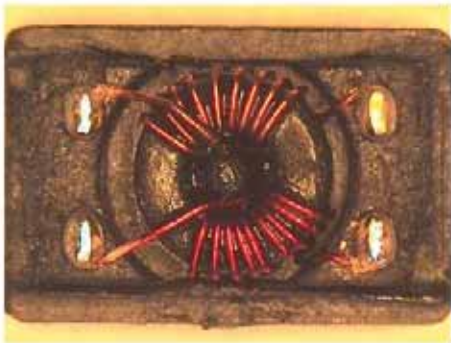

		Size [mm]	Impedance [Ω]	Current [A]	Application
WE-CNSW		2.0 x 1.2 x 1.2 3.2 x 1.6 x 1.9	130 – 910 60 – 400	0.28 – 0.4 0.20 – 0.37	USB 2.0 Firewire/ high speed dataline
WE-SL		12.7 x 10.5 x 5,75	1100 – 14400	0.20 – 2.70	ISDN Telecom Applications
WE-SL 1 744212xxx		6.5 x 3.6 x 1.65	300 – 2000	0.30	PCMCIA cards
WE-SL 2		9.2 x 6.0 x 5.0	1000 – 20000	0.40 – 1.60	VCC Power & Datalines
WE-SL 3 744252/253xxx		9.2 x 6.6 x 2.5	1250 – 5000	0.50 – 0.70	VCC Power & Datalines higher current ratings
WE-SL 5 744272xxx		10.0 x 8.2 x 6.5	290 – 13000	0.35 – 2.50	VCC Power Lines

Common Mode Choke



Nidcom

- different designs


WE-SL2 744226S
sectional winding





WE-SL2 7442276
bifilar winding

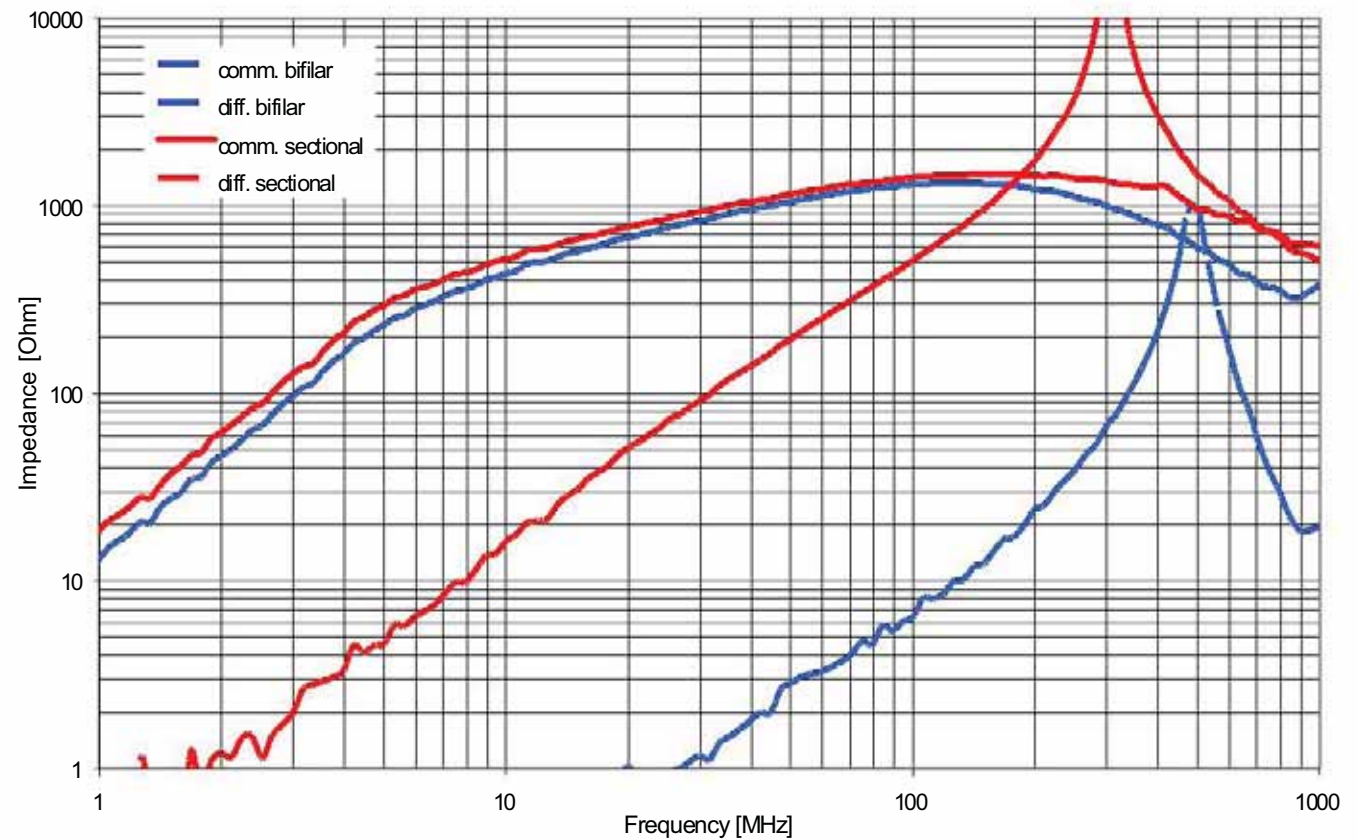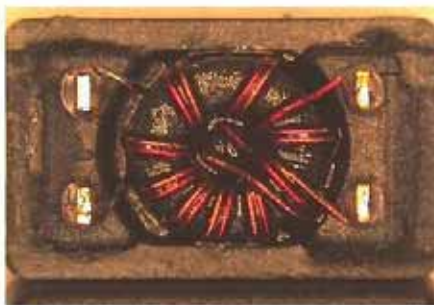


CMC - USB 2.0 Filtering for Common Mode Noise

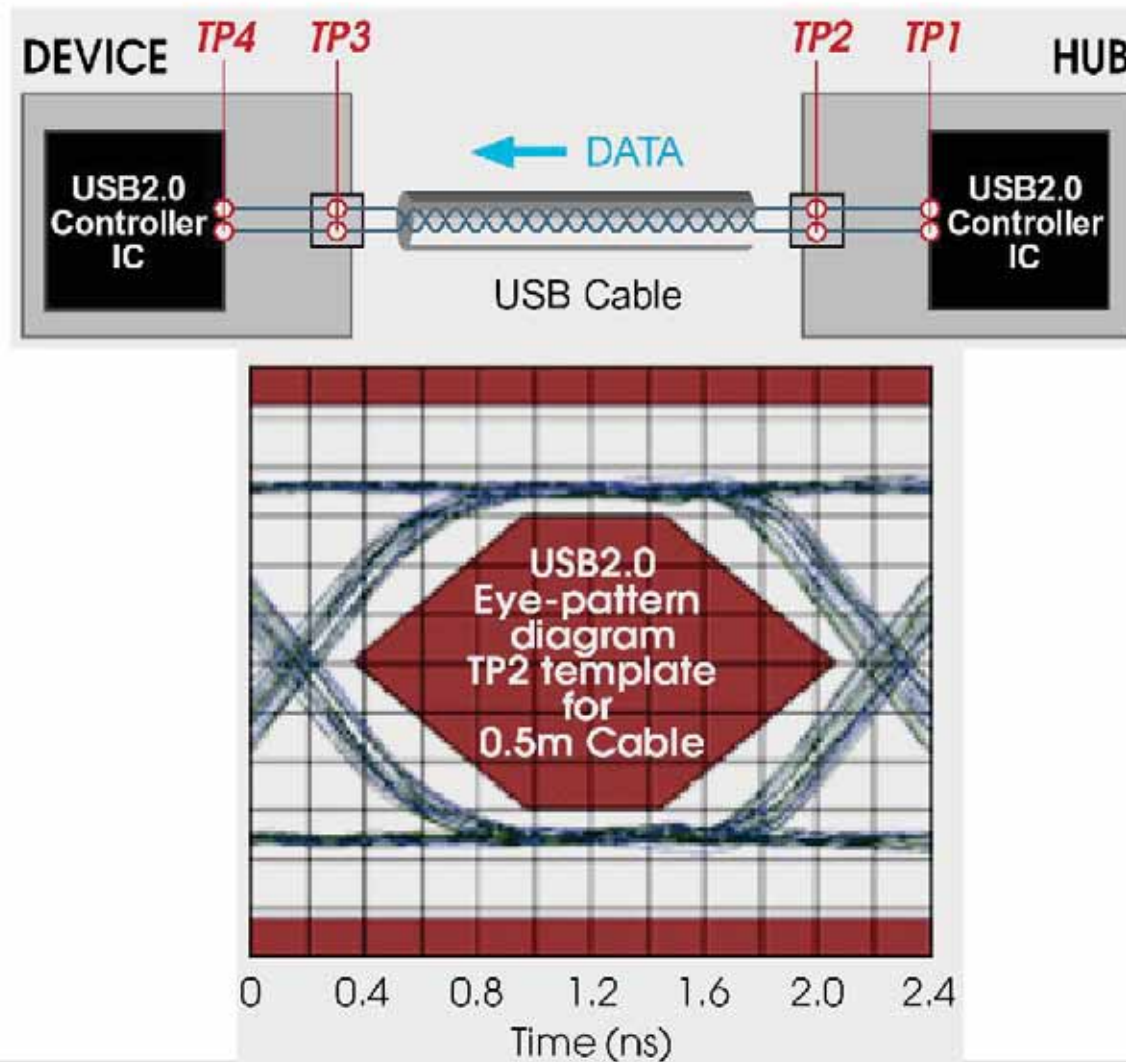Nidcom


CMC- USB 2.0 Filtering with WE-CNSW

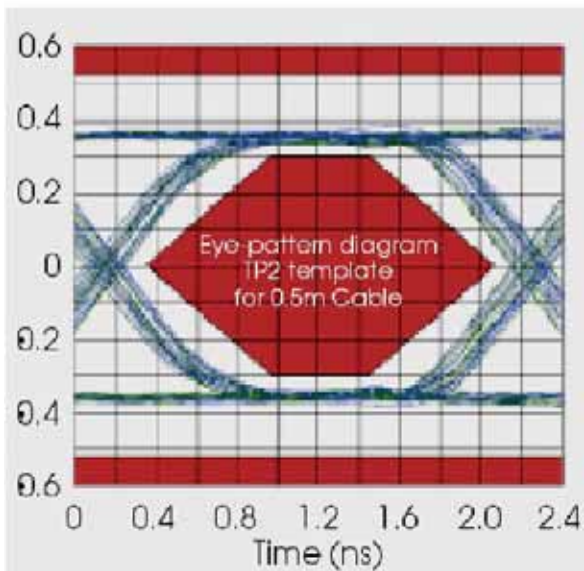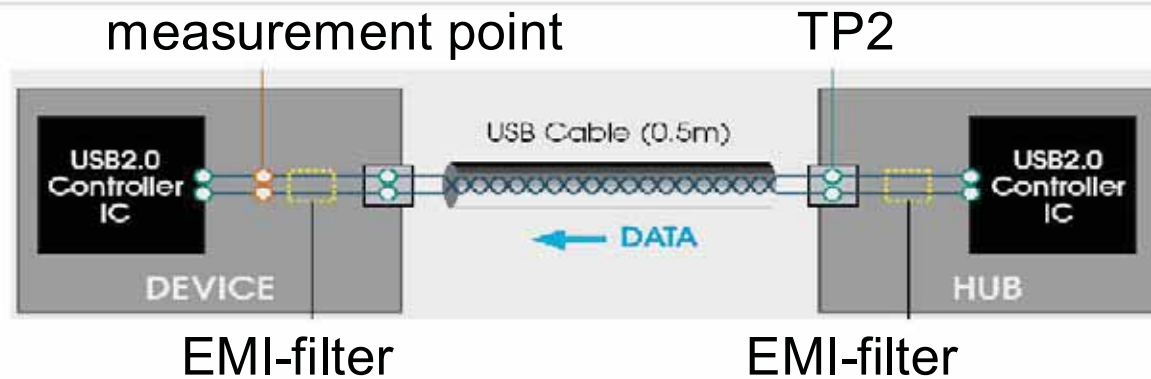

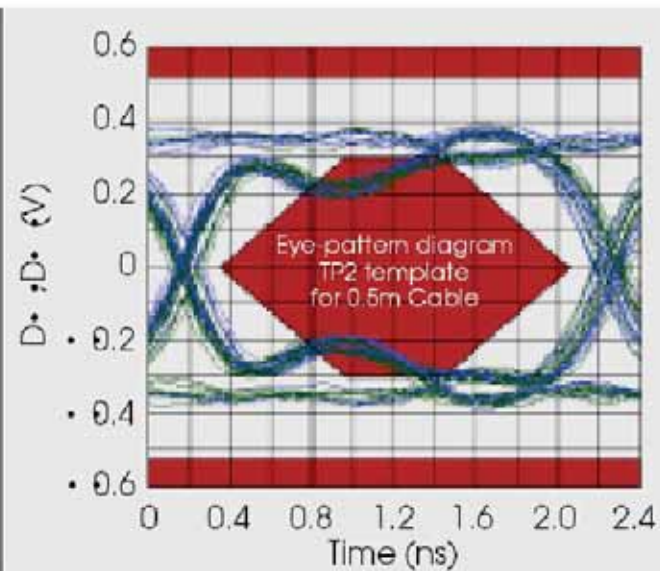90 Ohm @ 100 MHz C.M.
20 Ohm @ 240 MHz D.M.



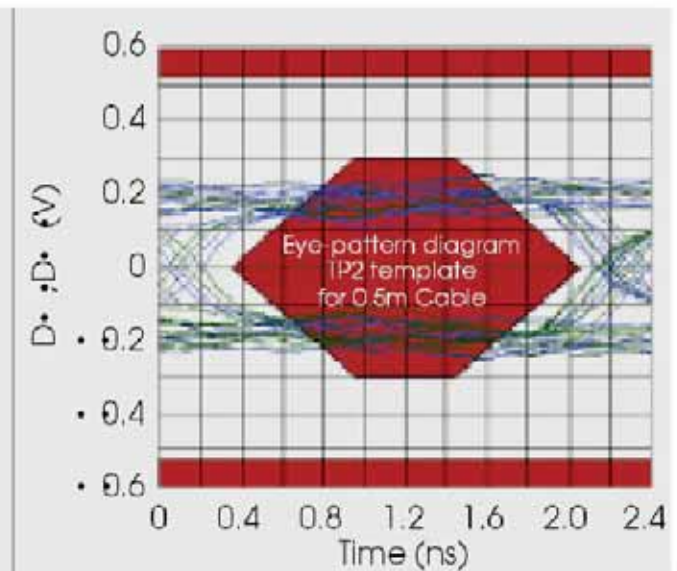
600 Ohm @ 100 MHz C.M.
40 Ohm @ 240 MHz D.M.




WE-CBF
120 Ohm @ 100 MHz

How Much Inductance is Needed?

Nidcom

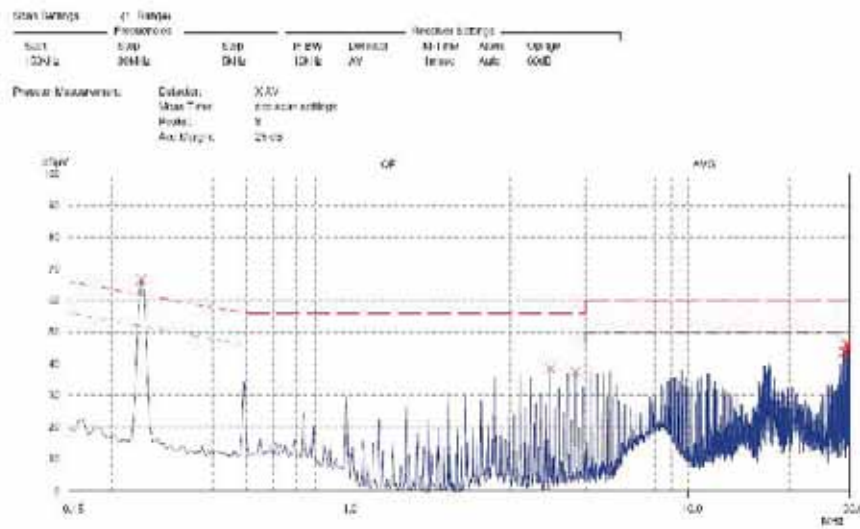

before

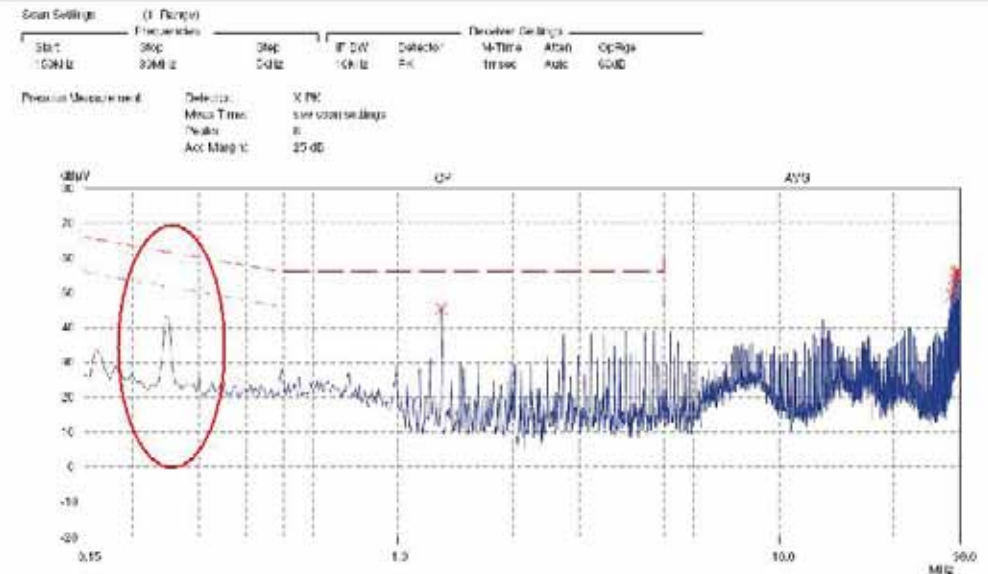

after

only changed one component



30mH!


Common Mode Choke (Sectional)

Nidcom



- When do we offer a sectional winding?

sectional

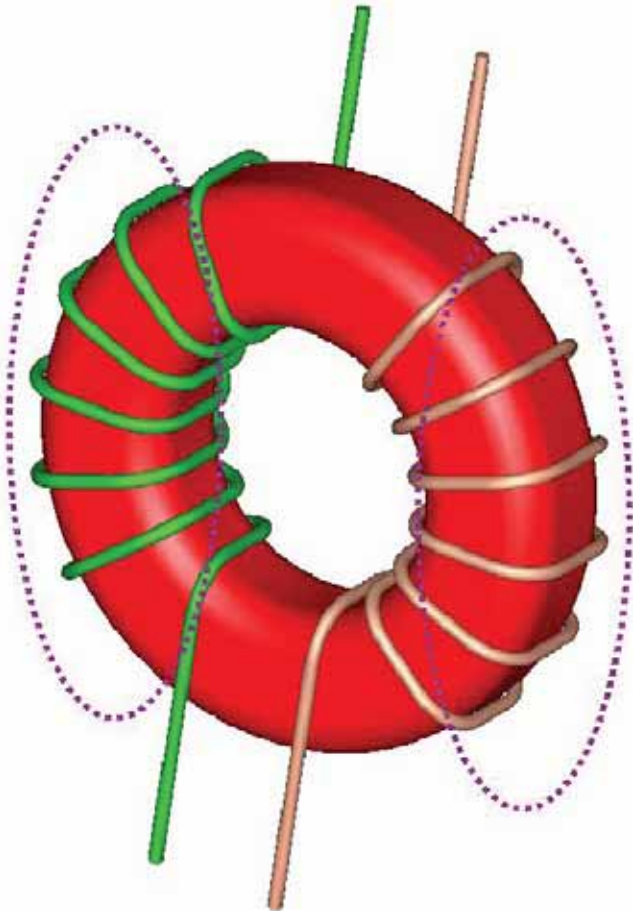


- power supply : "high" voltage application

- signal : low and high speed signal

→ only solution to guarantee distances between the two winding according to IEC60938 or UL1283
max. voltage application : 250 VAC / DC

→ high leakage inductor

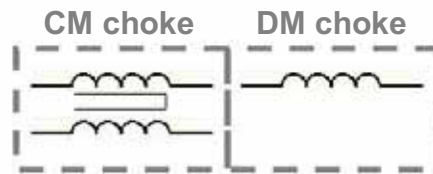

→ two products in one
(preferred for power supplies)

→ max. voltage : print in data sheet

Common Mode Choke (Bifilar)



- data signal application

bifilar → low leakage inductor




- power supply : low voltage application
- signal : only low speed signal

→ low voltage application
(42 VAC / 80V DC)


Common Mode Choke



- comparison Common Mode to Single Choke

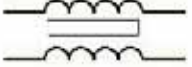	current compensated or common mode choke 	single choke 
common mode impedance	high	low to medium
differential mode impedance	low	medium
dependency of impedance from load current	independent	depends on “core”
attenuation of used signal	low	high

What Impedance is Needed?

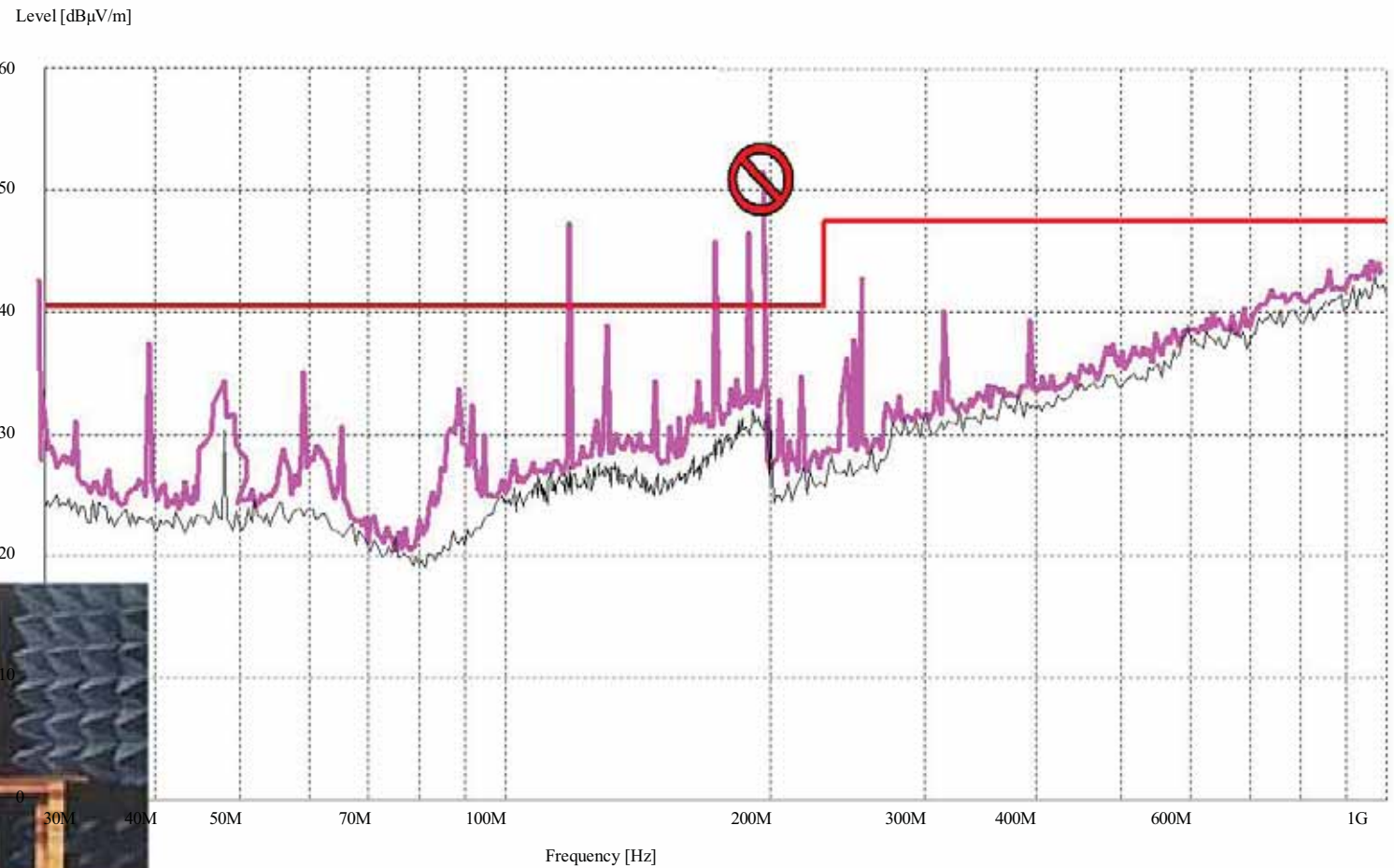Nidcom


Conducted Emissions Example – Test and Compare



- Chip Bead
- Differential Choke
- Bifilar Wound Common Mode Choke
- Sector Wound Common Mode Choke



Conducted Emissions Example - Test Setup

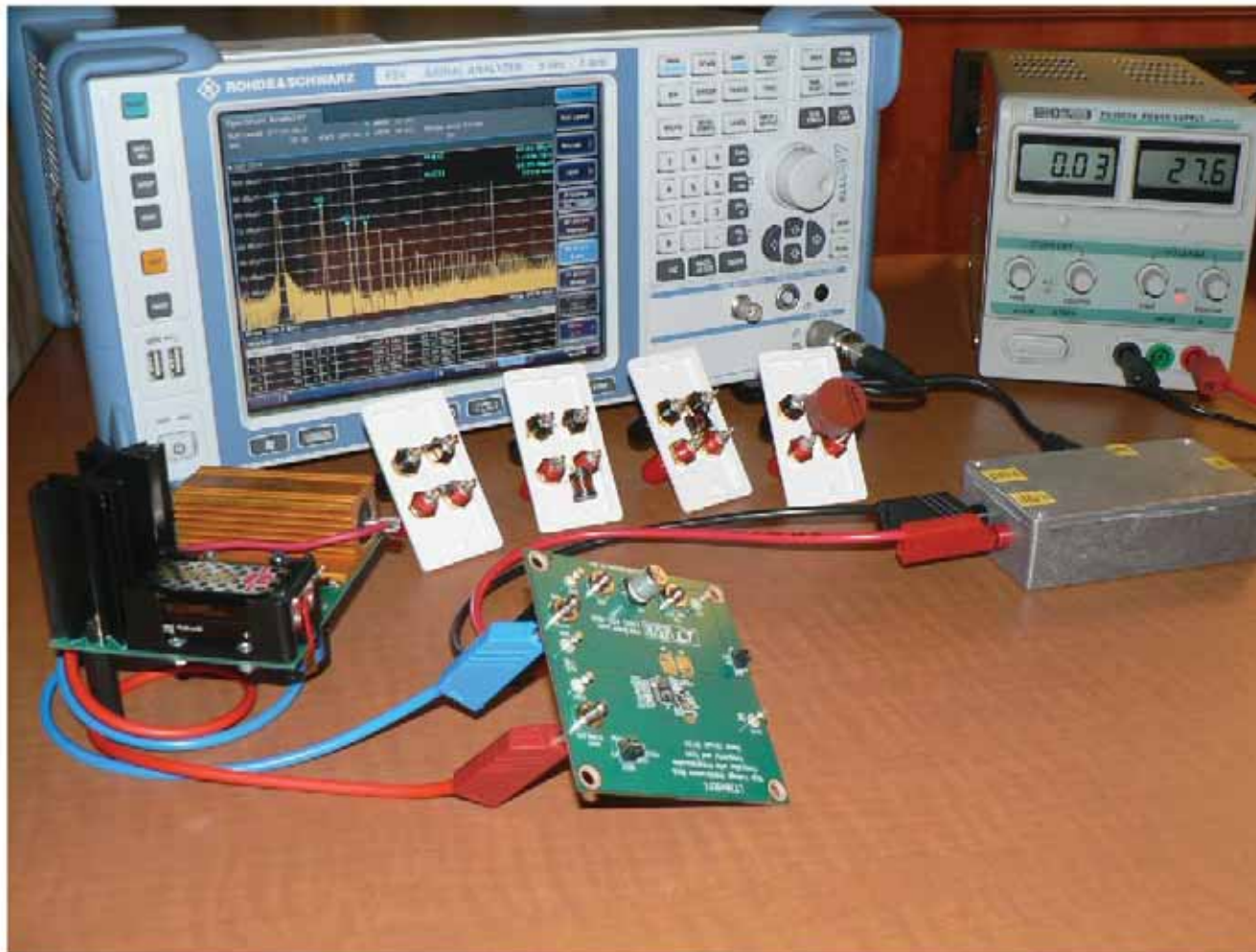


- a) no load
 - b) 1.5A load
- 300KHz fsw.

Conducted Emissions Example – Demo Board

Nidcom



FCC Class B limit

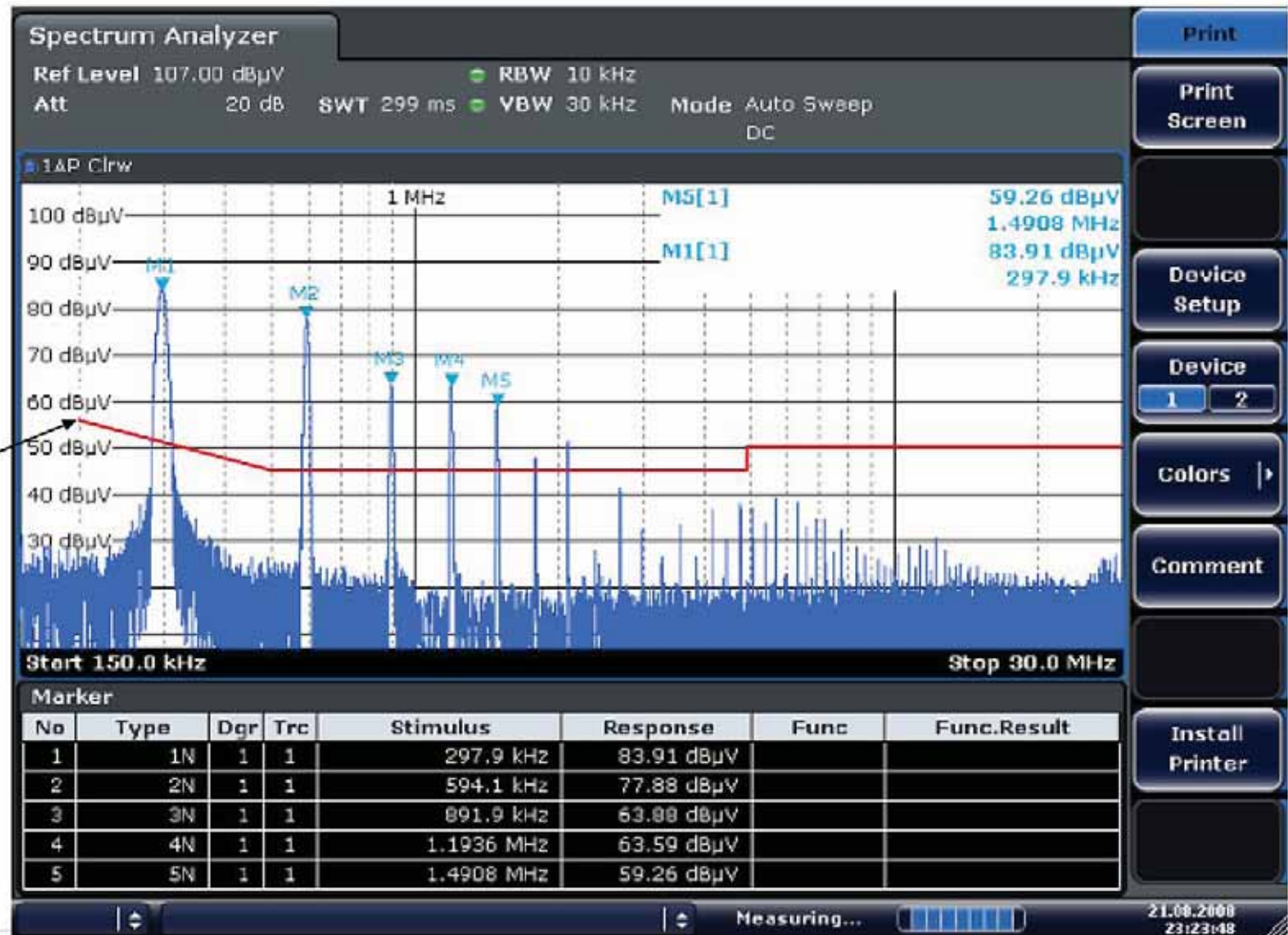


Conducted Emissions Example - LISN

Nidcom



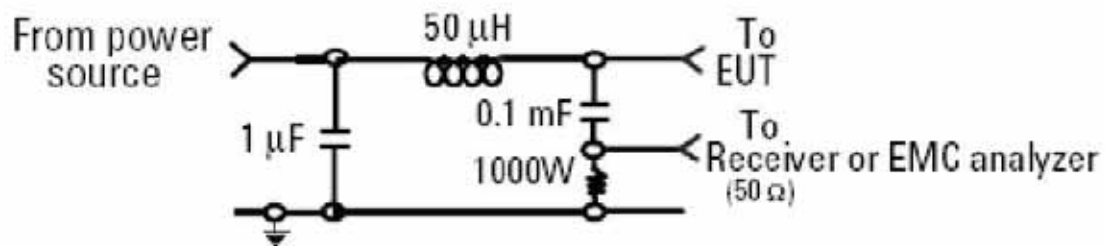
Line Impedance Stabilization Network (LISN)



- Isolates DUT (device under test) from Power Source (typically mains) Noise
- Provide characteristic Impedance to DUT (50ohms in this case)
- Path for Conducted noise from DUT to Spectrum Analyzer

The 1 μF in combination with the 50 μH inductor is the filter that isolates the mains from the EUT. The 50 μH inductor isolates the noise generated by the EUT from the mains. The 0.1 μF couples the noise generated by the EUT to the EMC analyzer or receiver. At frequencies above 150 kHz, the EUT signals are presented with a 50- Ω impedance.

Conducted Emissions Example – Electrical Load

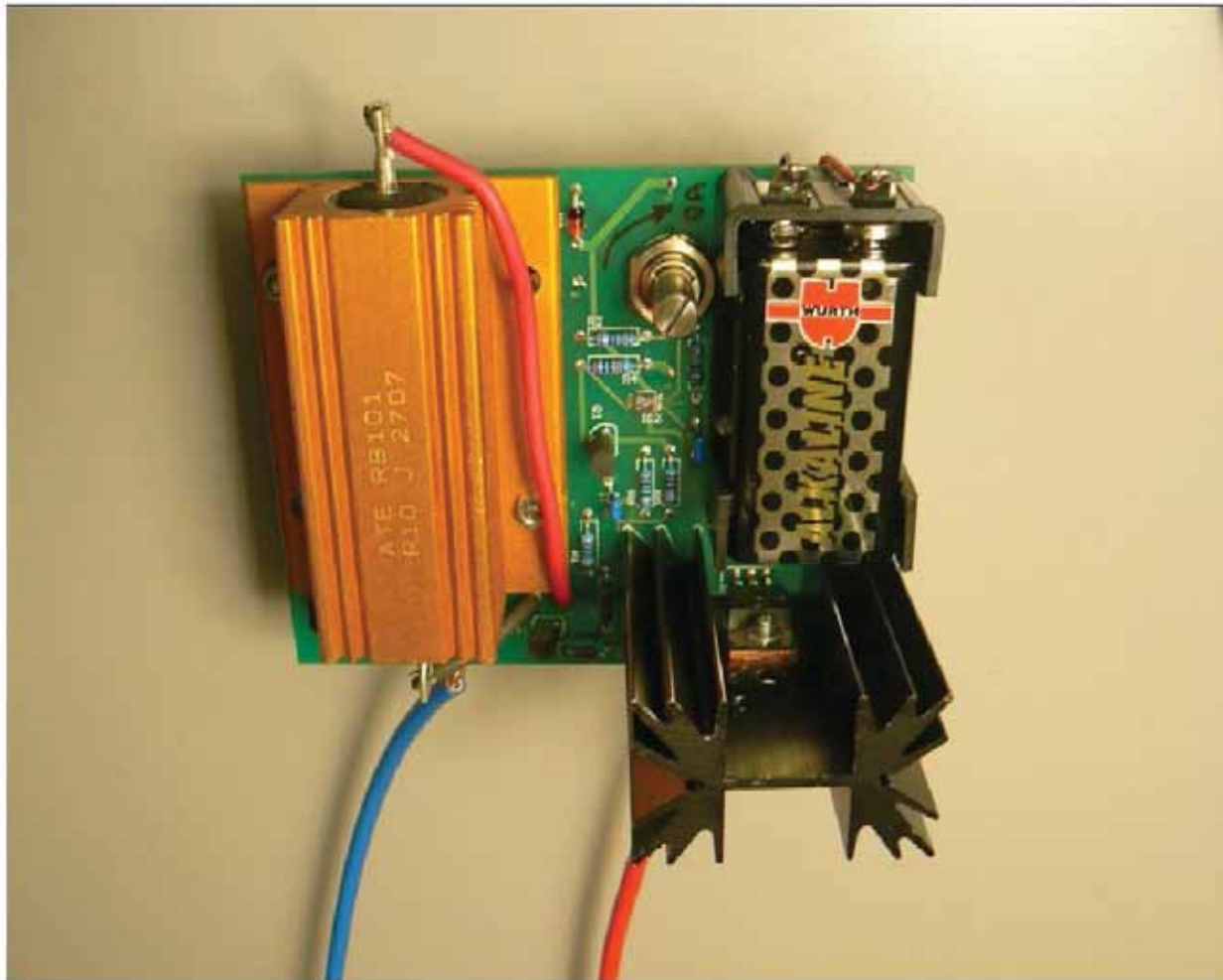Nidcom

Conducted Emissions Example – Test Board

Nidcom



- DC/DC Converter
- Input Voltage 20V-25V
- Output Voltage 12V/6.25A
- Fsw: 300KHz

Testcondition:

- no load
- max. load 1.5A




Conducted Emissions Example – No Filter

Nidcom



FCC Class B limit

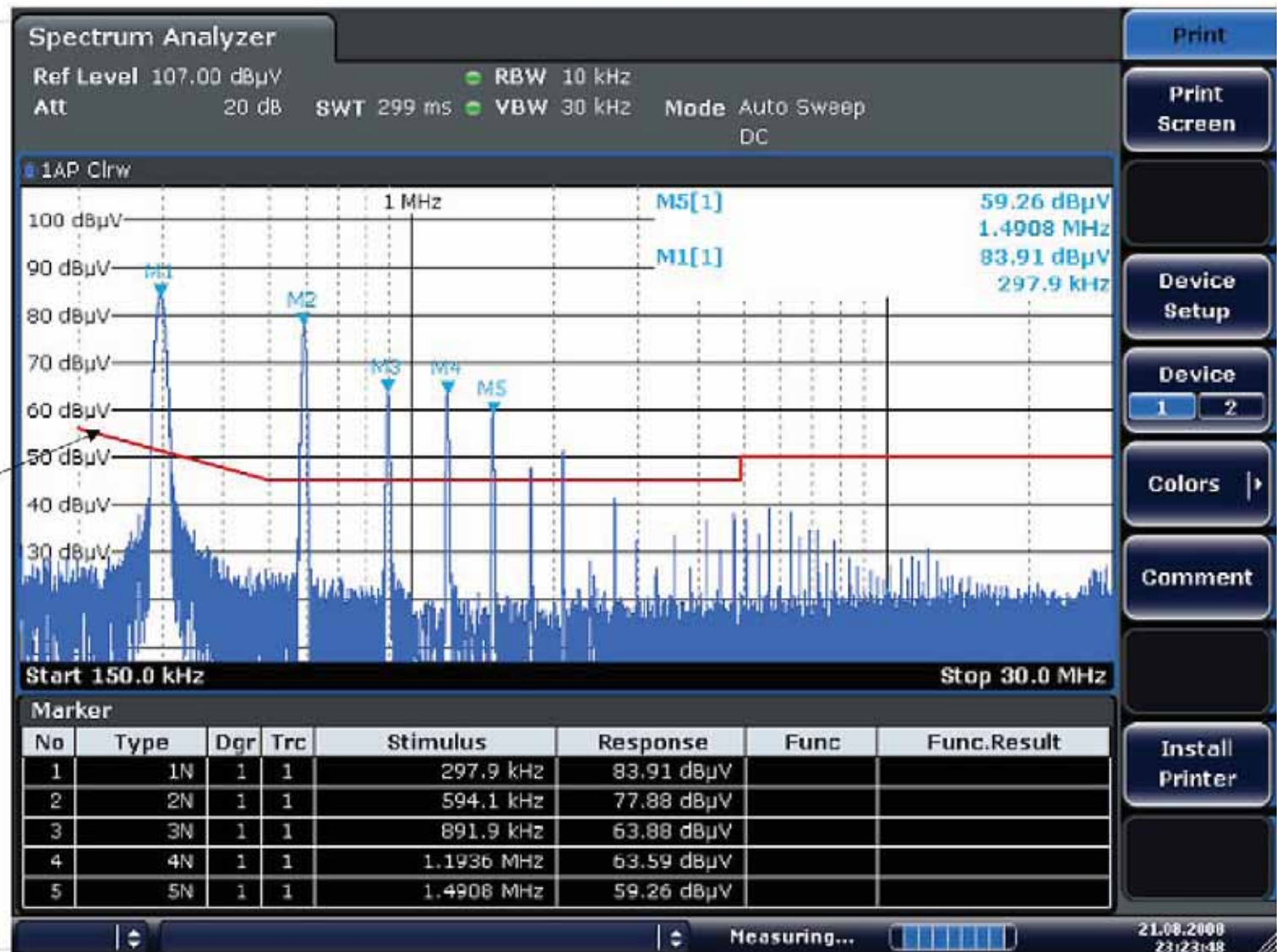

Conducted Emissions Example – Chip Bead

Nidcom


Chip Bead 530? / 3A

Conducted Emissions Example – Chip Bead Results

Midcom



no load >

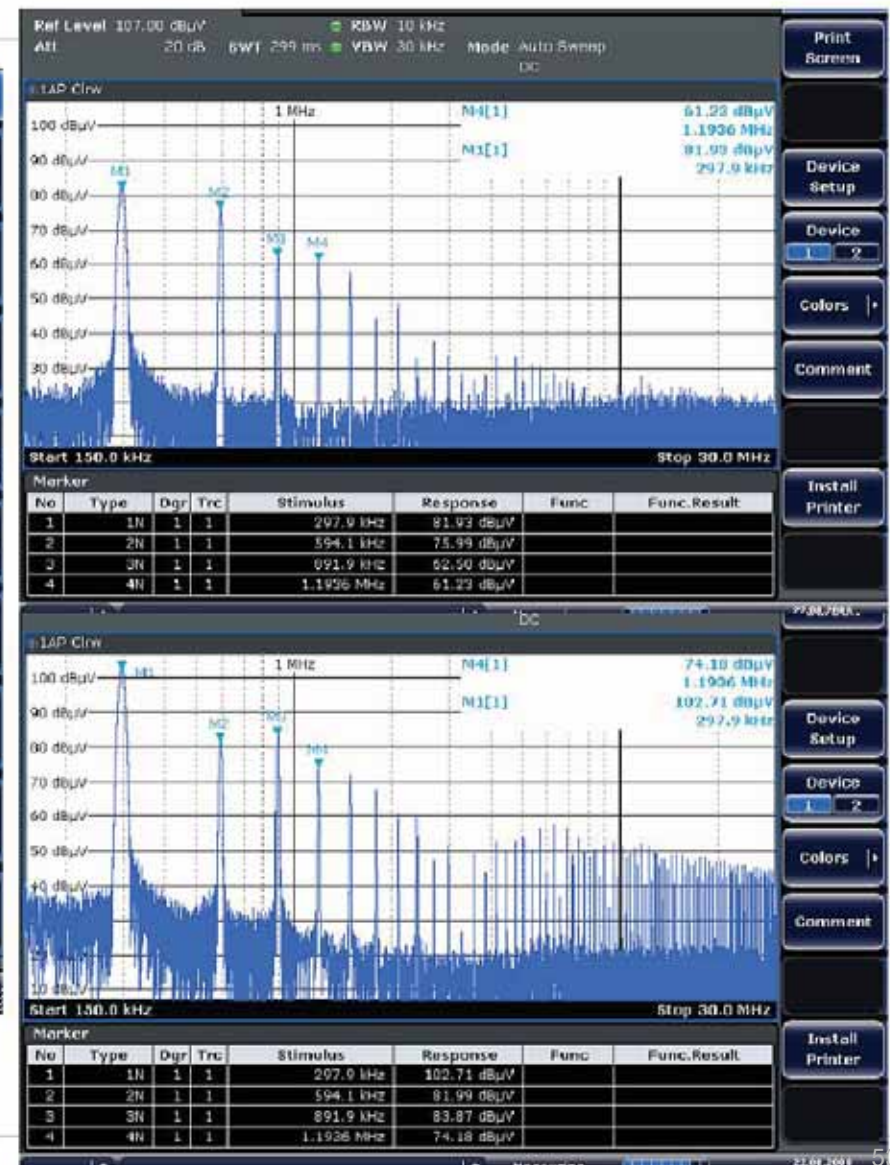



Chip Bead 530? / 3A

load 1.5A>

Nidcom




Conducted Emissions Example – Chip Bead

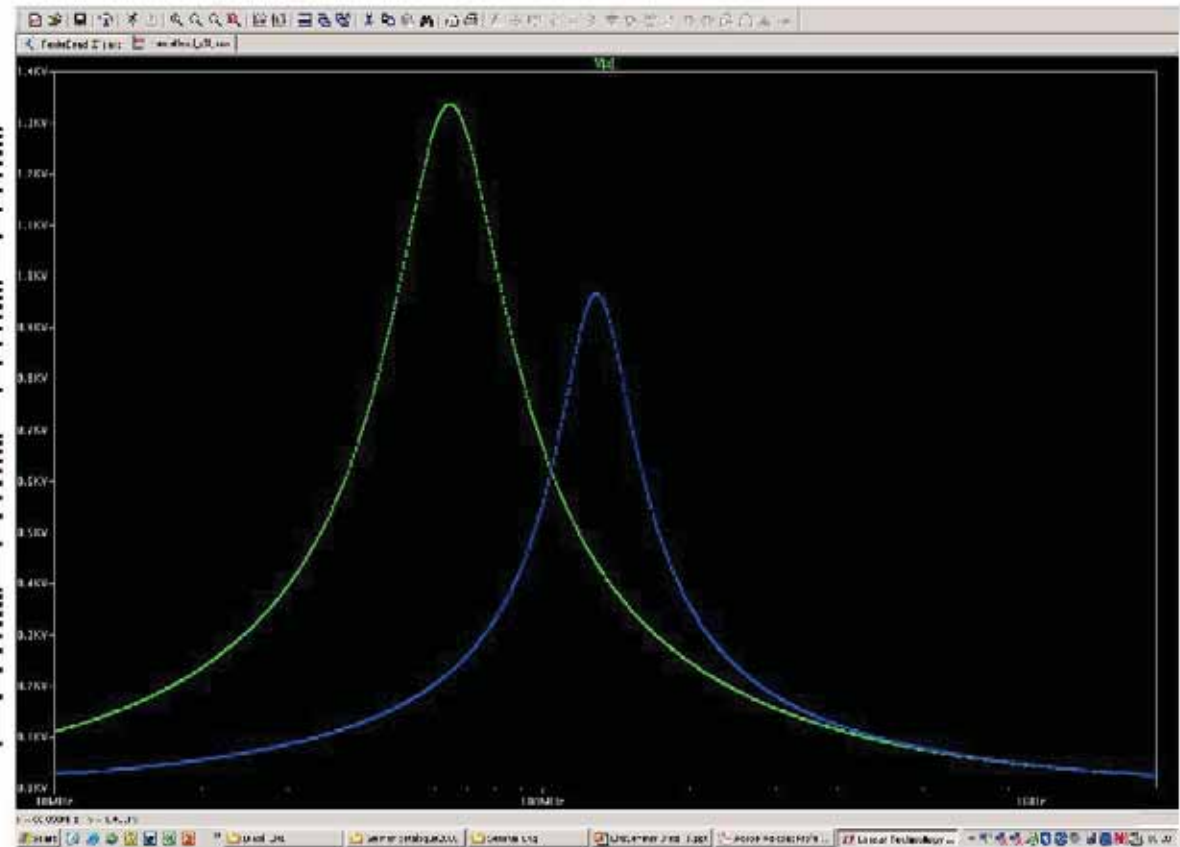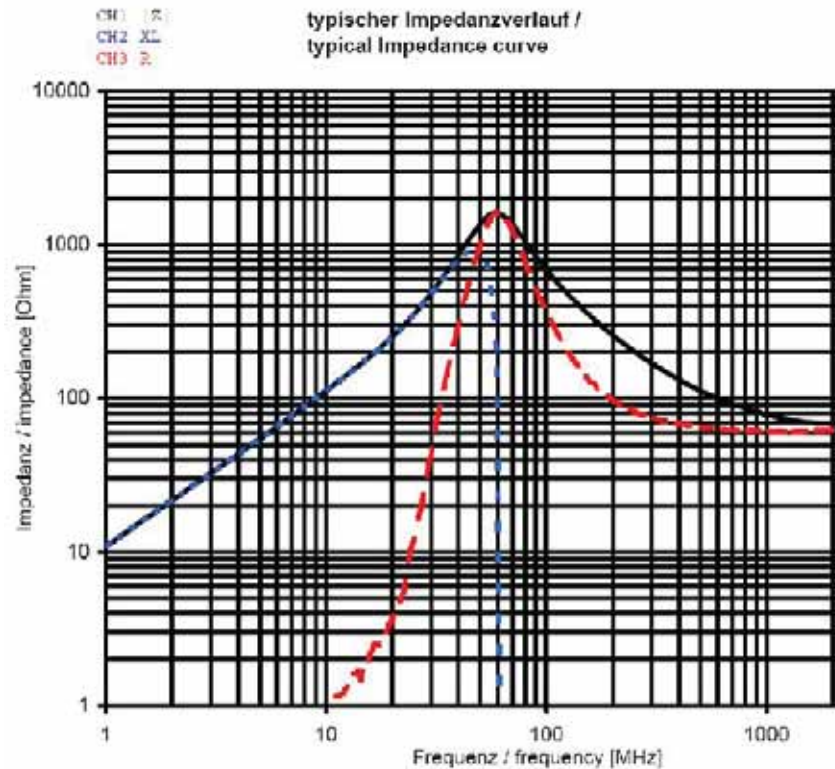

Chip Bead 530? / 3A

Conducted Emissions Example – Differential Choke

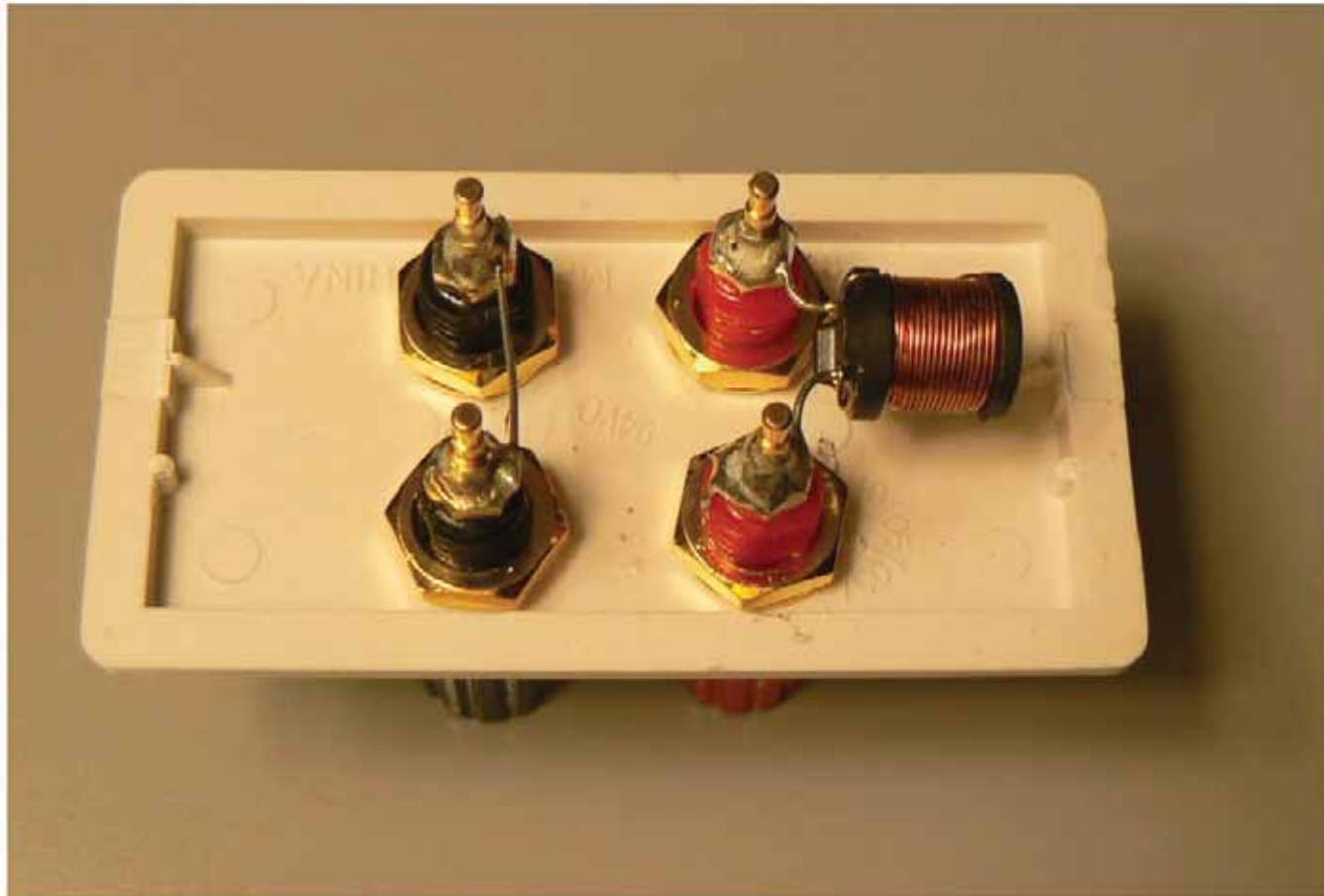Nidcom

Differential Line Choke 220uH


Conducted Emissions Example – Differential Choke Results



no load >



load 1.5A>

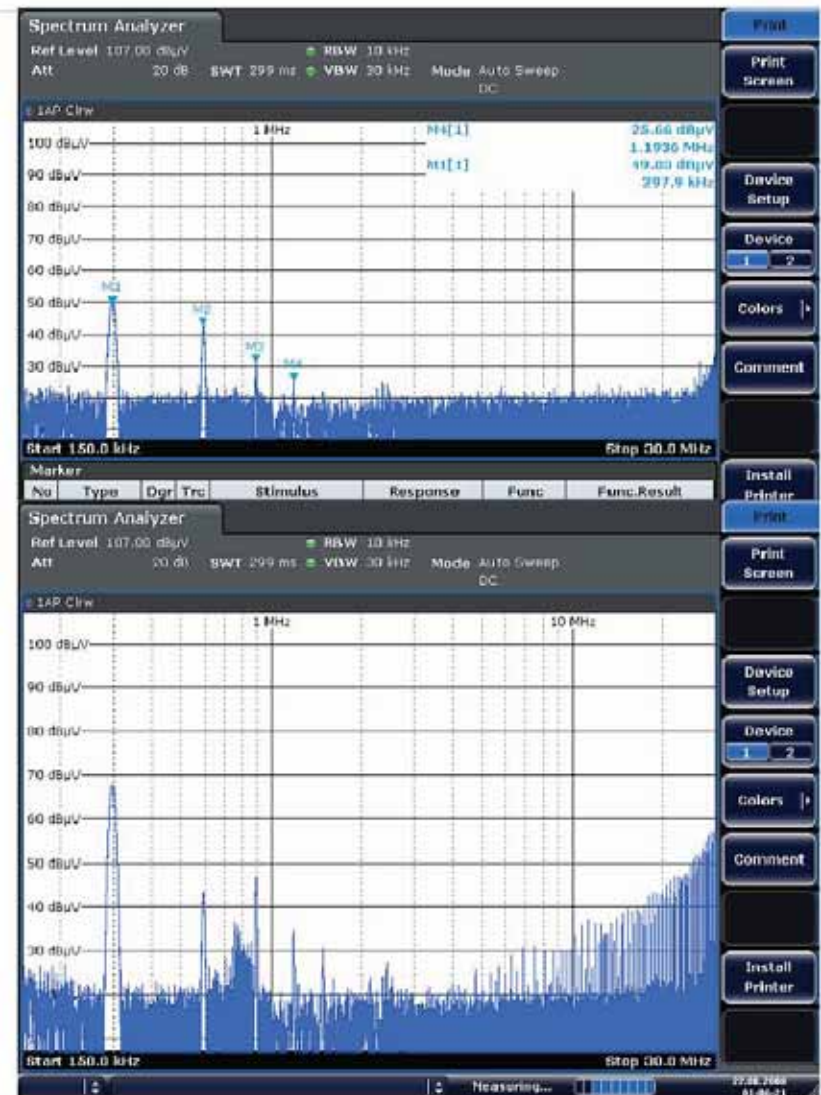

Conducted Emissions Example – Bifilar CMC

Nidcom

CMC 4.7mH Bifilar Winding


Conducted Emissions Example – Bifilar CMC

Nidcom



Artikel-Nr.	Induktivität (μH)	R _{DC} (Ω)	I _N (mA)	Impedanz max. (Ω)
744272121	2 x 120	0,025	2500	400
744272221	2 x 220	0,032	2200	780
744272251	2 x 250	0,035	2000	970
744272471	2 x 470	0,065	1600	1750
744272102	2 x 1000	0,180	950	3600
744272222	2 x 2200	0,300	750	7500
744272332	2 x 3300	0,360	650	8900
744272392	2 x 3900	0,540	520	9600
744272472	2 x 4700	0,720	350	13000

744 272 472

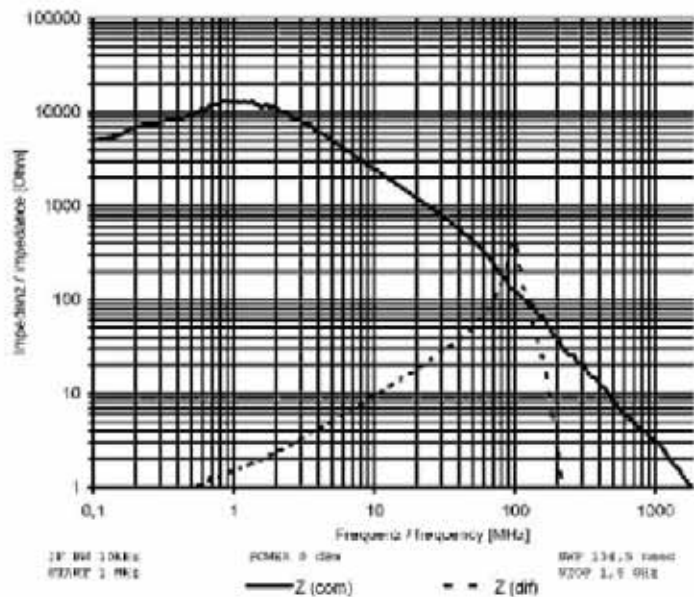

Warning: Don't try this at home!

For Demonstration Purposes Only!



Load is 1.5A

And..... CMC



CMC 4.7mH Bifilar Winding

Conducted Emissions Example – Bifilar CMC Results

Midcom




no load >

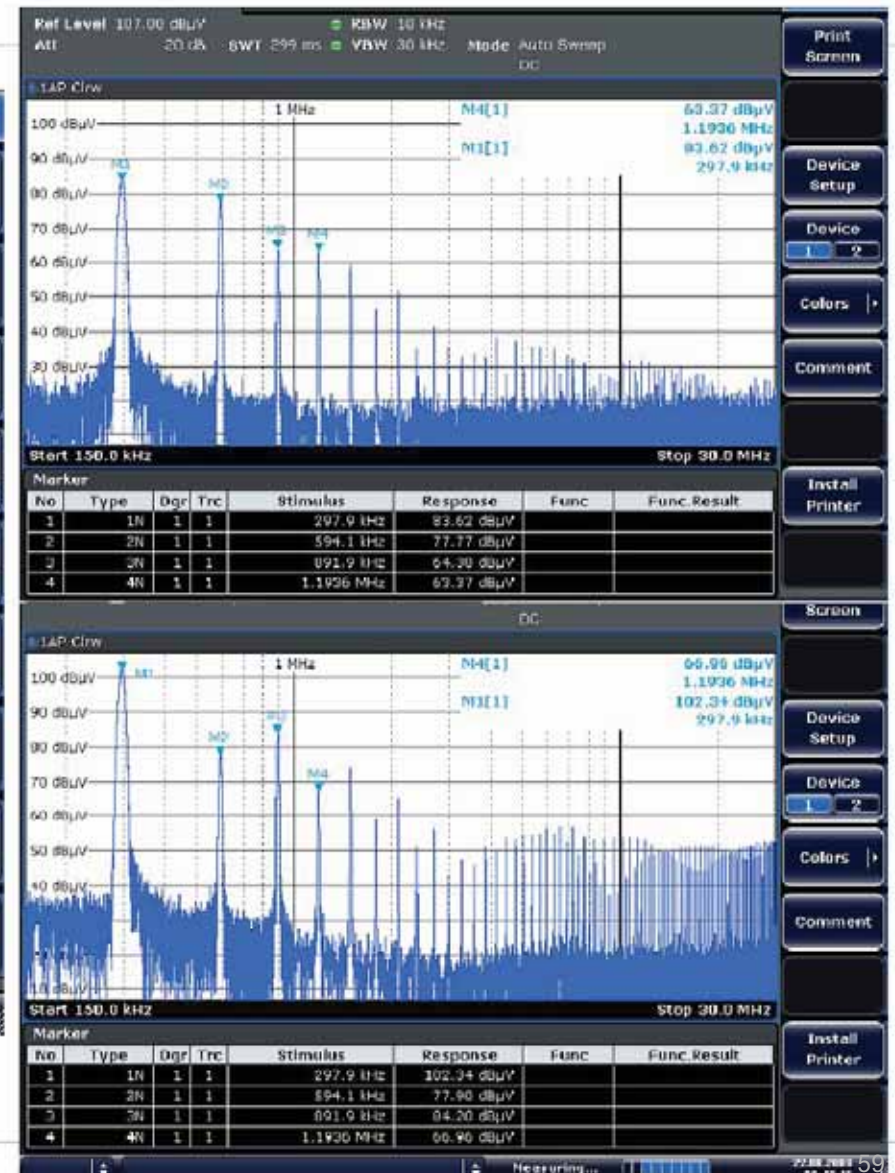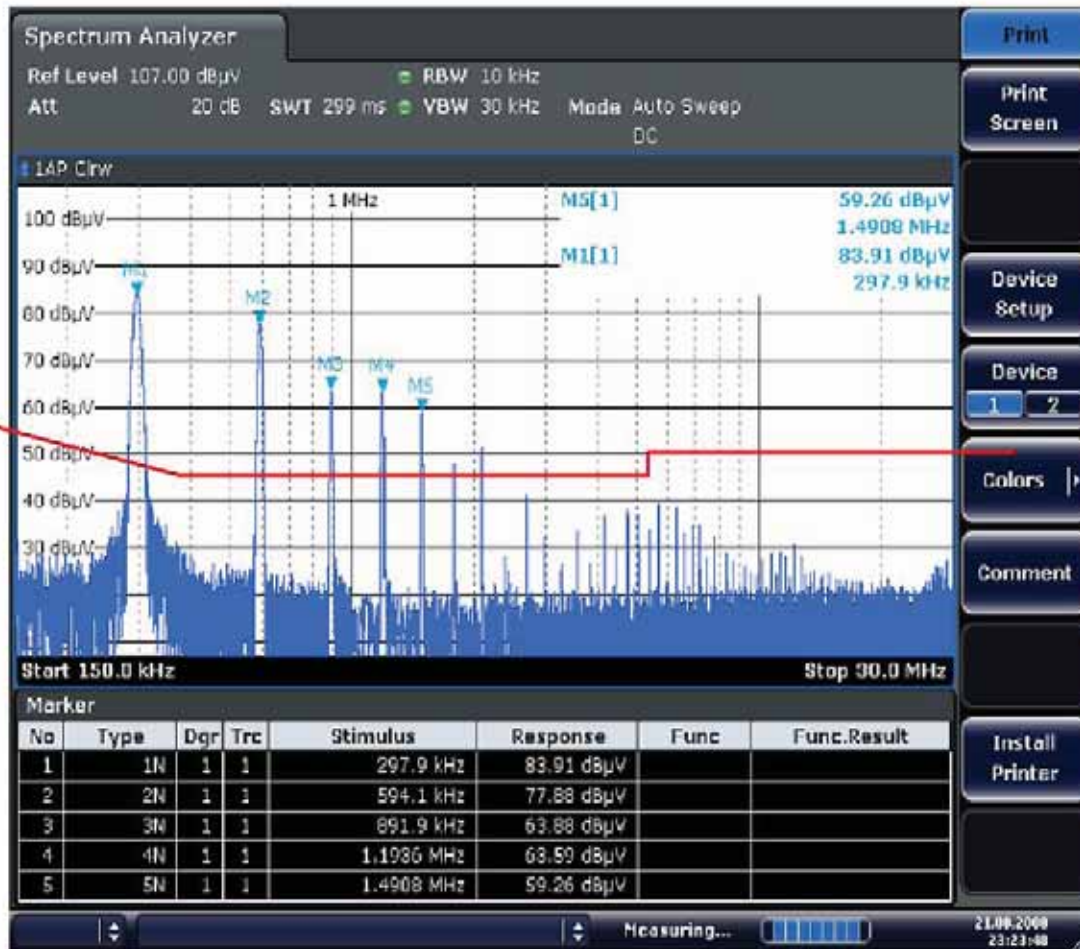

CMC 4.7mH Bifilar Winding load 1.5A>

Conducted Emissions Example – Sector CMC

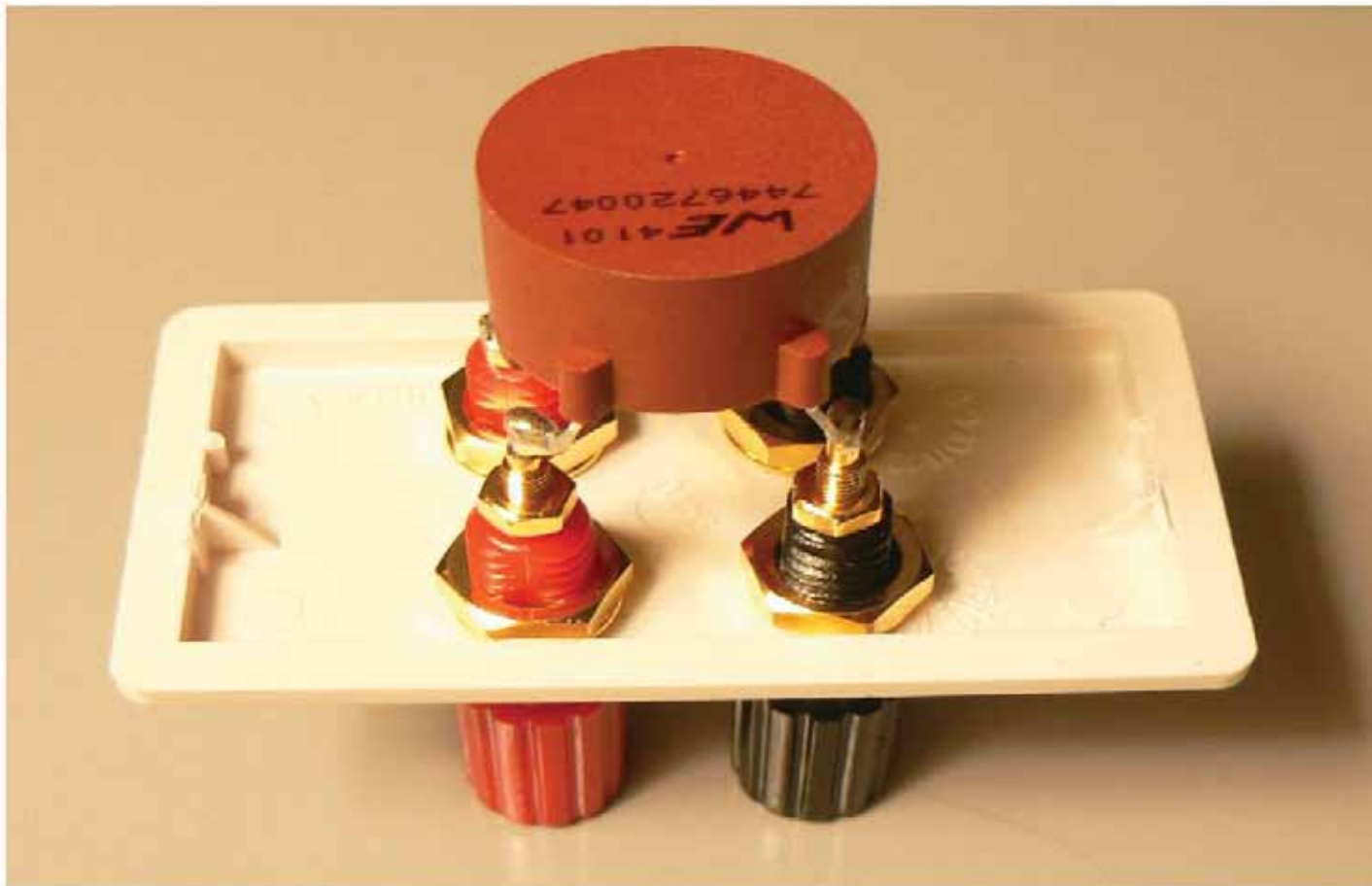
Nidcom

CMC 47mH sectional winding

Conducted Emissions Example – Sector CMC

Nidcom

Einfügedämpfung im Frequenzverlauf

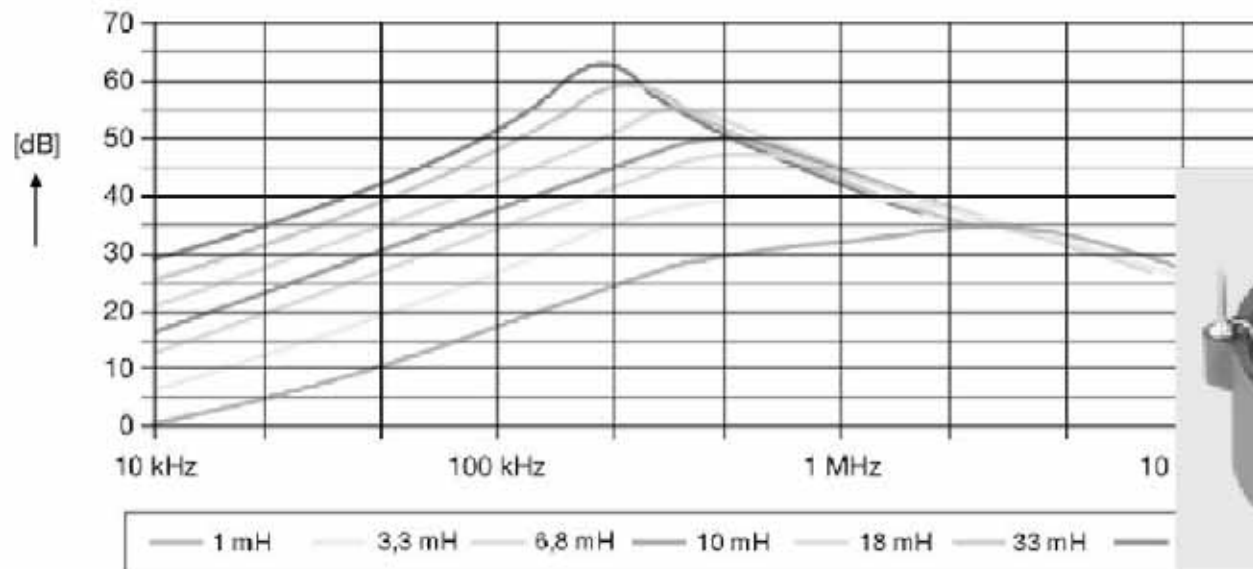



CMC 47mH Sectional Winding
Leakage Inductance $L_s \sim 250\mu\text{H}$ (5% of L)

Conducted Emissions Example – Sector CMC Results

Nidcom



no load >

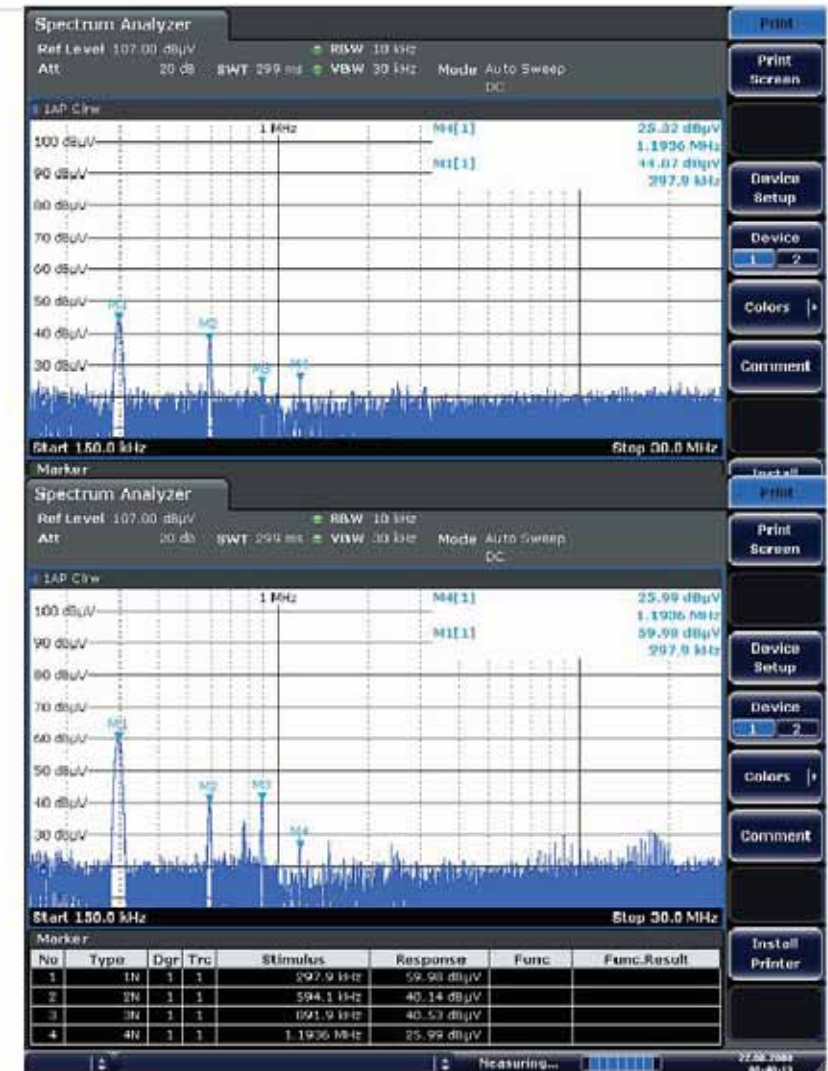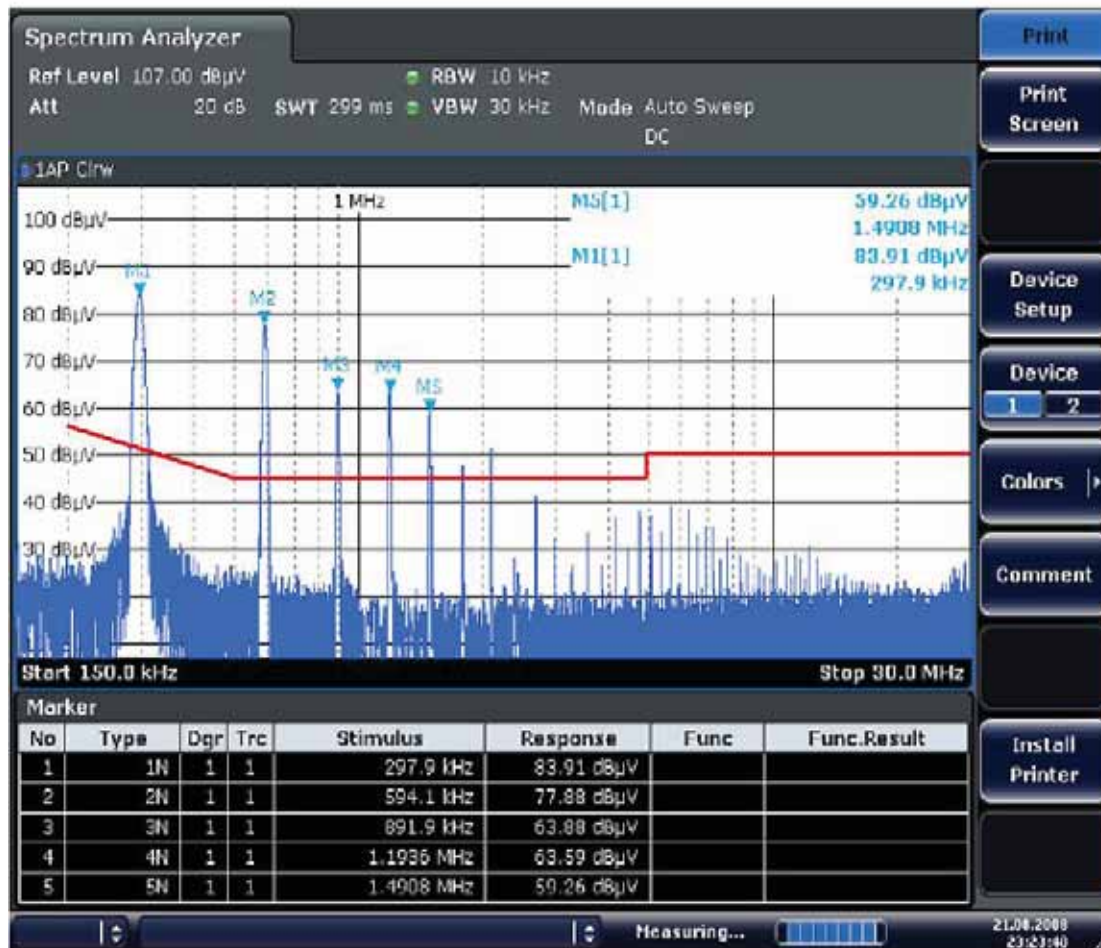

CMC 47mH sectional winding

load 1.5A>



Conducted Emissions Example - Conclusions



- **High Frequency Noise Appears Under Load**
- **Noise is Differential Mode**
- **Differential Choke**
 - Attenuates low frequency noise because of SRF
- **Bifilar CMC**
 - Does not attenuate because of very low leakage inductance.
- **Sector CMC**
 - Attenuates both high and low because of leakage inductance with high SRF.
- **Chip Bead**
 - Without a load there is some affect at high frequencies, but with a load the bead pre-magnetizes and there is no affect at all.



Transformers for EMC – What to Choose

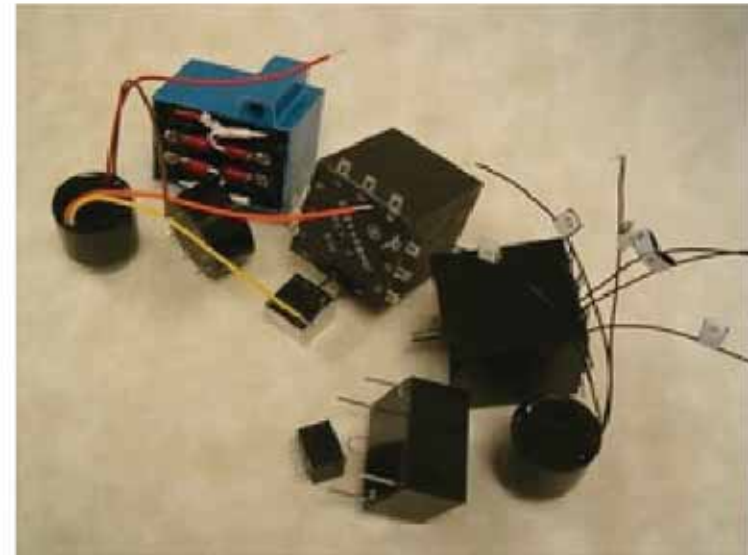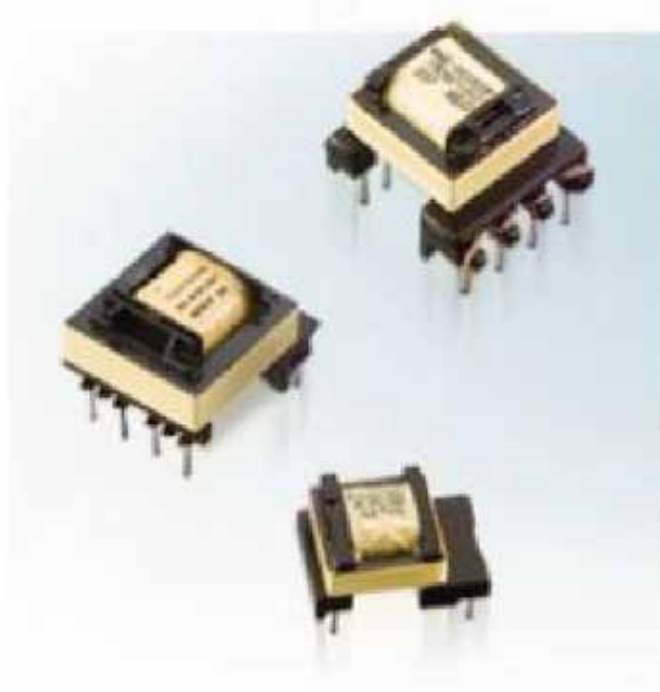Nidcom

Transformers for EMC – No Antennas Please!



Enough Said!



Flying Leads Make Great Antennas.


Estimate Component Losses

Nidcom



- Efficiency is ~ 75-85% Typical
 - 33% Switch
 - 57% Output Rectifiers
 - 5% Magnetics
 - 5% Miscellaneous

So where are your losses?

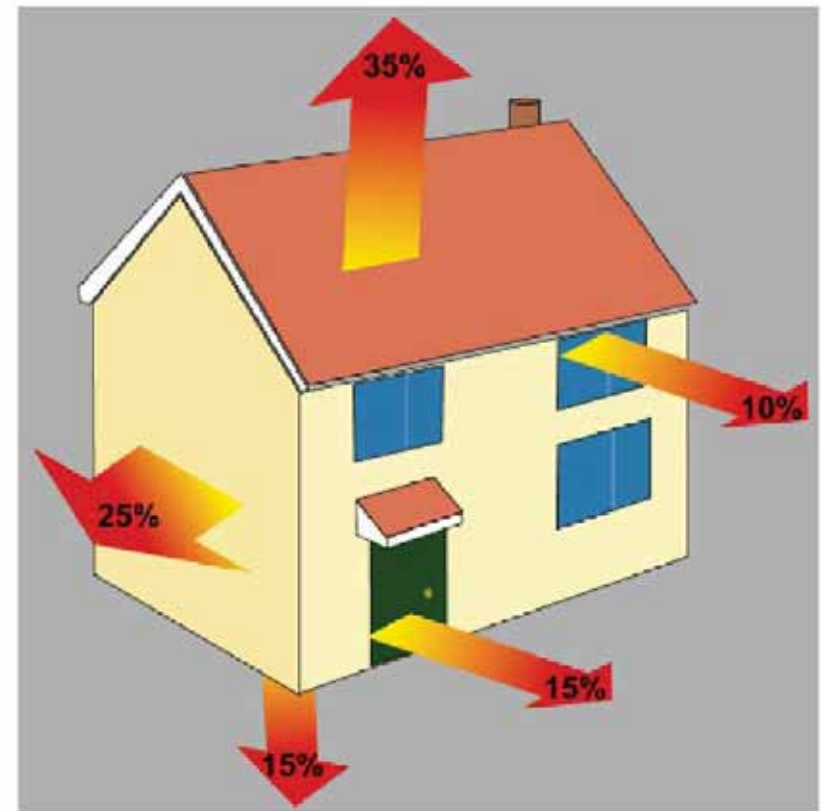

Where are the losses ?

Midcom



50

Environment:

Operating Conditions

Vin: 22.00 V

Iout: 2.00 A

Ambient Temperature

On Bottom: 25 °C

On Top: 25 °C

Board Conditions

Copper Weight

1.02. (0.03556 mm)

Board Orientation:

Component Side Up

Cu Area #Vias

2.8436 Sq In 0

Air Flow


Direction Velocity:

of Air flow:

No Fan



Edge 4
Insulated

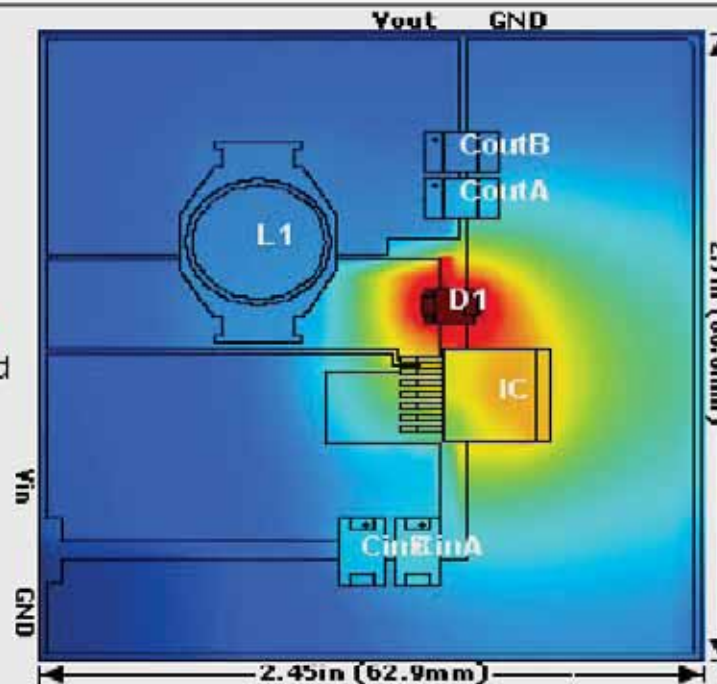

Edge 3
Insulated

Edge 2
Insulated

Temperature Bar Scaling

Click [here](#) to recolor your thermal image.

Max Colorbar Temperature 62 °C

Min Colorbar Temperature 32 °C

Losses in transformers and inductors



$$P_{total} = P_{Cu} + P_{FE}$$

- **Copper losses**
 - DC losses
 - AC losses
 - Skin Effect
 - Proximity Effect
- **Core losses**
 - Hysteresis loss
 - Eddy current losses

Practical Formulas for Calculation of Temperature Rise ΔT for WE-PD, WE-DD

Nidcom



WE-PD Typ „S“ (744778_, 7447789_); WE-DD „S“:

$$\Delta T \approx \left(\frac{P_{tot}}{2,875} \right)^{0,826} \quad P_{tot} \text{ in (mW) and } \Delta T \text{ in } (^\circ\text{C})$$

WE-PD Typ „M“ (744777_, 7447779_); WE-DD „M“:

$$\Delta T \approx \left(\frac{P_{tot}}{3,218} \right)^{0,826} \quad P_{tot} \text{ in (mW) and } \Delta T \text{ in } (^\circ\text{C})$$

WE-PD Typ „L“ (744771_); WE-DD „L“:

$$\Delta T \approx \left(\frac{P_{tot}}{6,321} \right)^{0,826} \quad P_{tot} \text{ in (mW) and } \Delta T \text{ in } (^\circ\text{C})$$

WE-PD Typ „XL“ (744770_); WE-DD „XL“:

$$\Delta T \approx \left(\frac{P_{tot}}{8,045} \right)^{0,826} \quad P_{tot} \text{ in (mW) and } \Delta T \text{ in } (^\circ\text{C})$$

Example: As calculated:

744 770 147

$P_{tot}=233\text{mW}$

$$\Delta T = \frac{233^{0,826}}{8.045} \div$$

$$= 16,1^\circ\text{C}$$


Trilogy of Inductors
Pages 222–223

Core/Copper Losses & Efficiency

Nidcom



Copper Losses

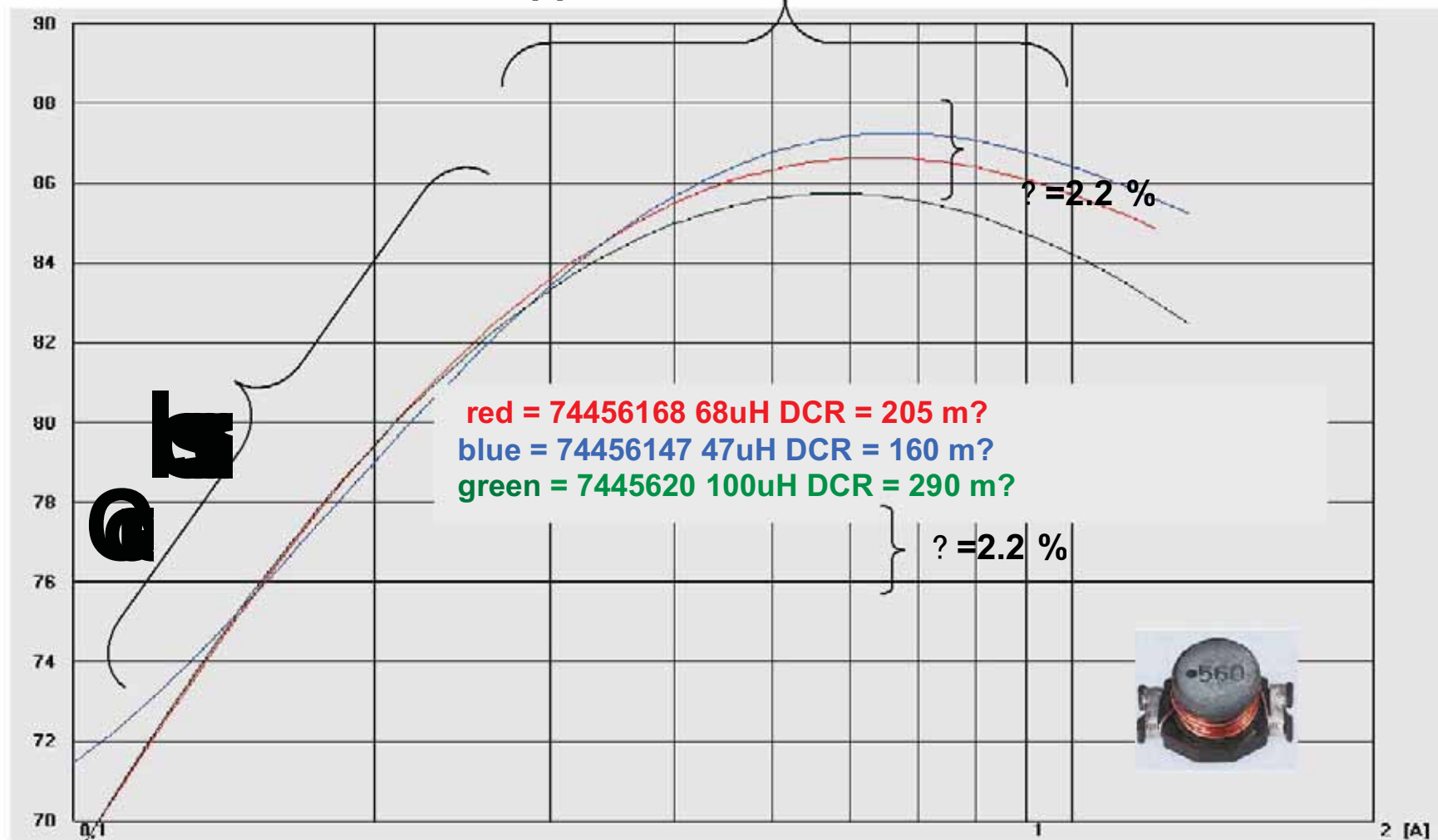

Practical way for core loss calculation P_{core} by using I_{max} and ripple current ΔI for WE-PD

Nidcom



PD size XL

$$P_{\text{core (mW)}}_{744770} \cdot x = 12 \cdot f_{(\text{kHz})}^{1,274} \cdot \left(\frac{\Delta I}{I_{\text{max}}} \right)^{1,9}$$

PD size L

$$P_{\text{core (mW)}}_{744771} \cdot x = 7,2 \cdot f_{(\text{kHz})}^{1,274} \cdot \left(\frac{\Delta I}{I_{\text{max}}} \right)^{1,9}$$

PD size M

$$P_{\text{core (mW)}}_{744777} \cdot x = 2 \cdot f_{(\text{kHz})}^{1,274} \cdot \left(\frac{\Delta I}{I_{\text{max}}} \right)^{1,9}$$

PD size S

$$P_{\text{core (mW)}}_{744778} \cdot x = 1,6 \cdot f_{(\text{kHz})}^{1,274} \cdot \left(\frac{\Delta I}{I_{\text{max}}} \right)^{1,9}$$

Trilogy of Inductors
Pages 220–221

What more do you need?

Nidcom

Look at our Book:

Chap.1: Basics

keep it simple, stupid

Chap.2: Components

Descriptions, Applications, Simulation
Models and many more

Chap.3: Filter-Circuits

Design, Grounding, Layout, Tips

Chap.4: Applications


Circuit, suggested parts, Layout

Chap.5: Appendices

from A to Z

Transformers for EMC – No External Gaps

Nidcom

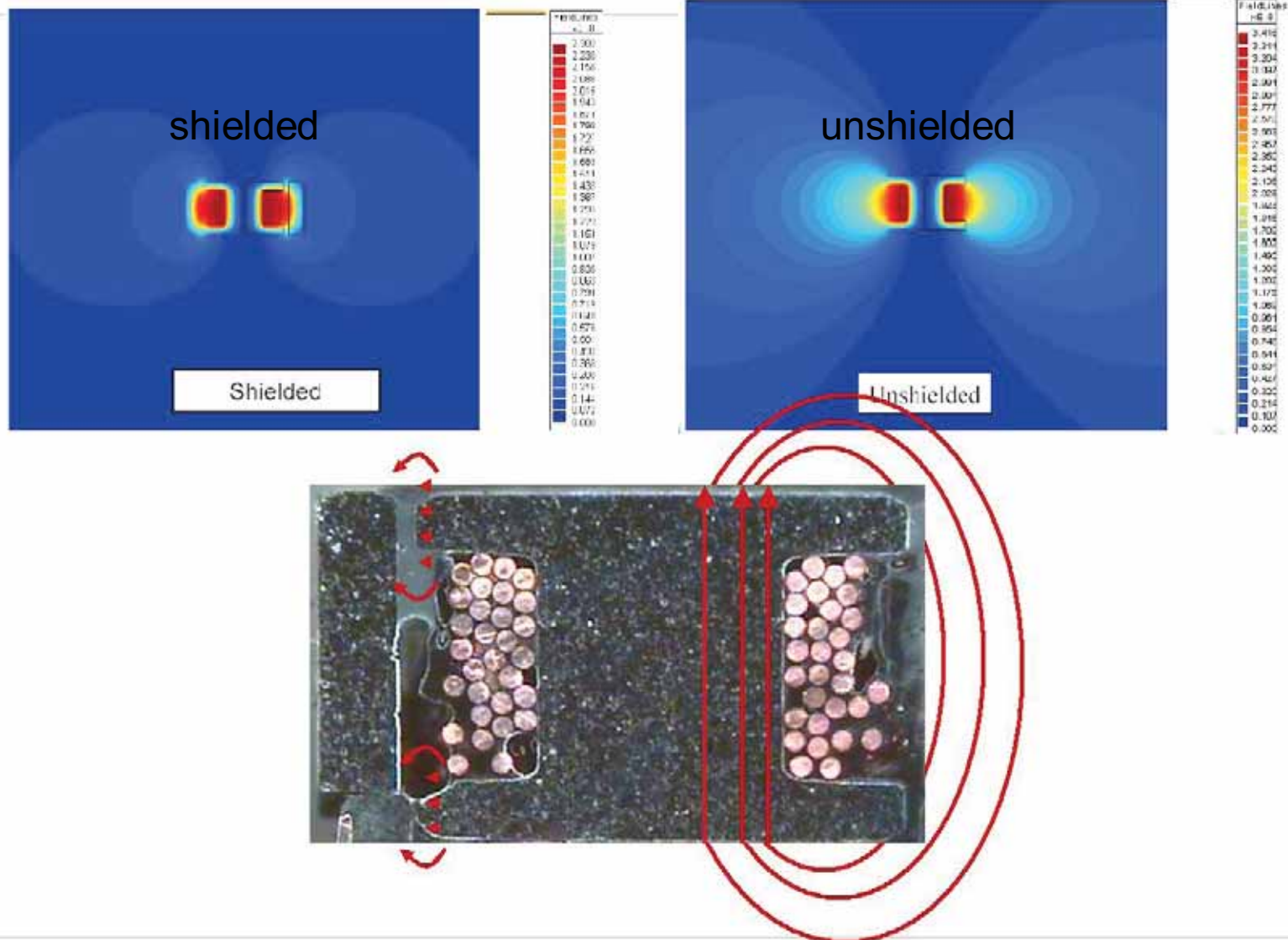

Transformers for EMC – No External Gaps


Nidcom



- Center Leg Gap Only
 - Windings Shield
- No Gaps in Outer Legs
 - Nothing to Shield

No Gaps Here

Gap Here

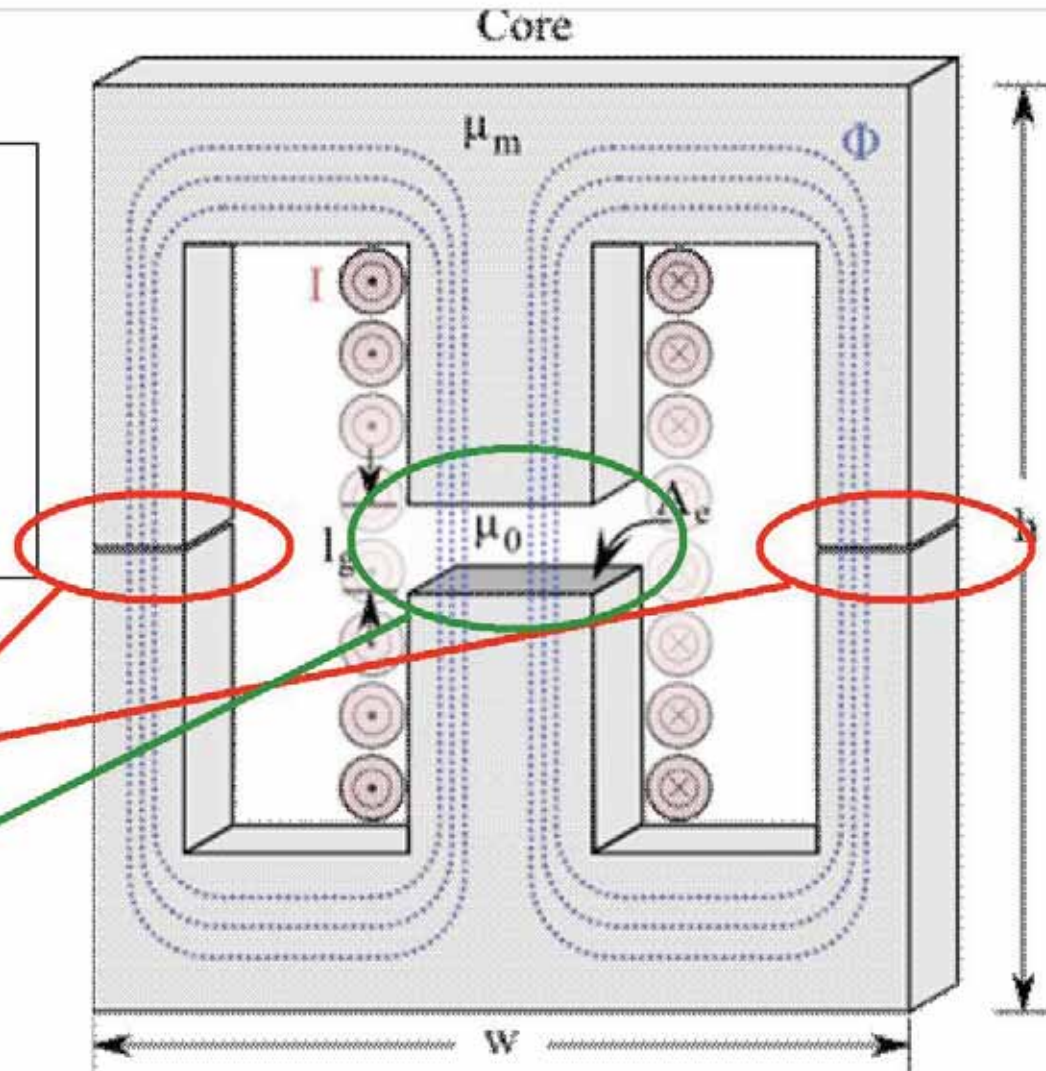


Transformers for EMC – No EI Core



- EI Core Style
- Mylar or Tape Used for Gap
- Three Unshielded Gaps


Not a good solution!

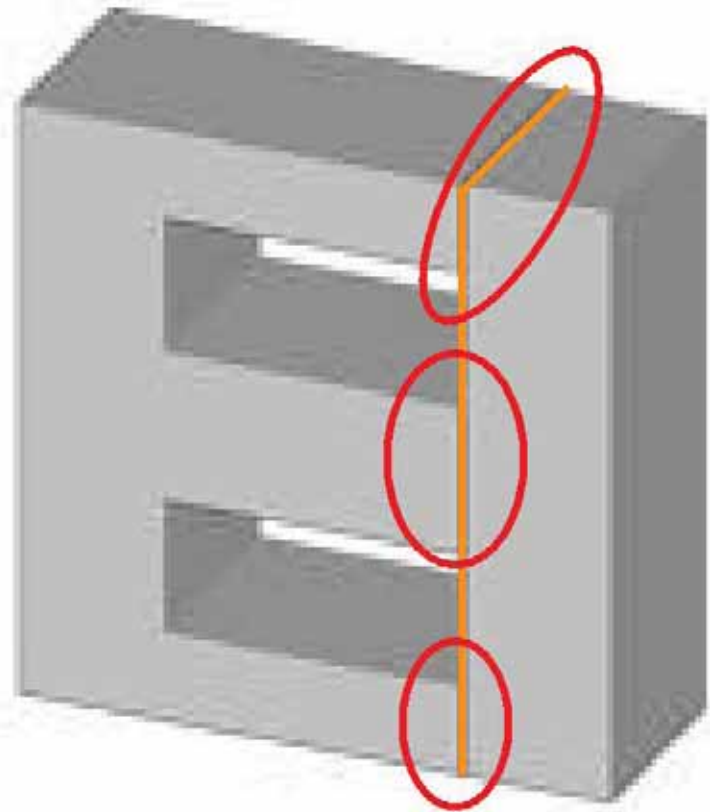

Transformers for EMC – Gap




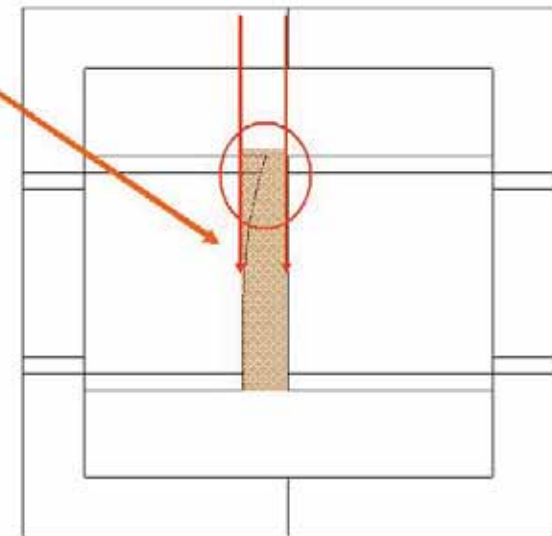
- **Gap Must be Perpendicular to Flux Lines**
 - Here Only One Side is Gapped
- **Uneven Gaps Are Inefficient, Why?**
 - Core Saturates at Minimum Gap.
 - Requires a Larger Gap
- **Also Larger Gap – More Potential EMI**



Transformers for EMC – Internal Shields

Nidcom

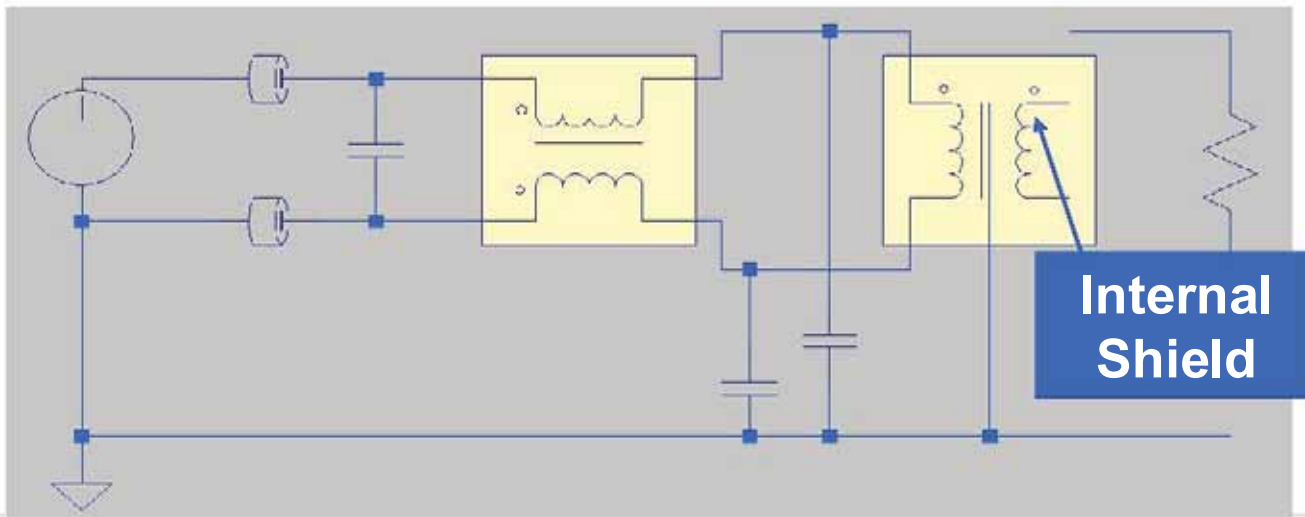
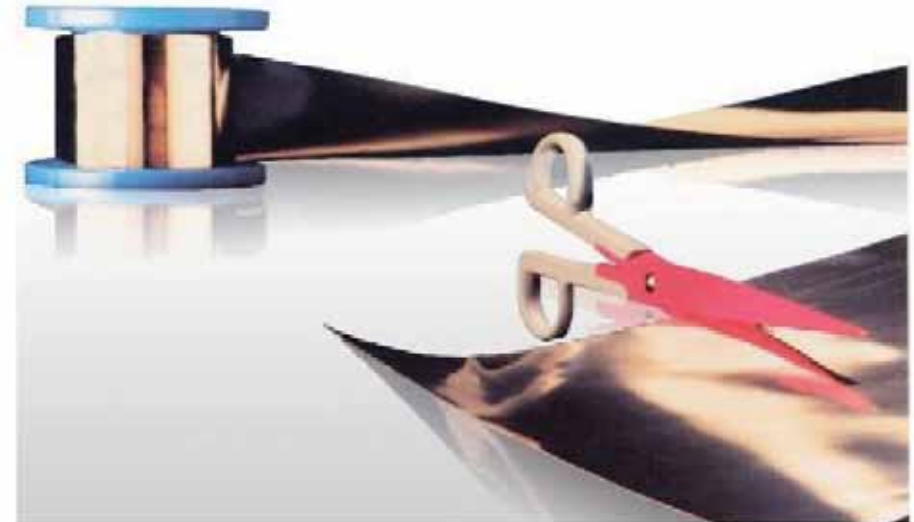
- Shield both Conducted and Radiated Noise
- Copper Foil or Wound Magnet Wire?
- Copper Foil Shields – Expensive, Why?
 - Must Build Shield
 - Must be Cuffed with Tape
 - Winding Machine Stopped to Apply
- All Shields Take Away from Winding Area



Transformers for EMC – External Shields



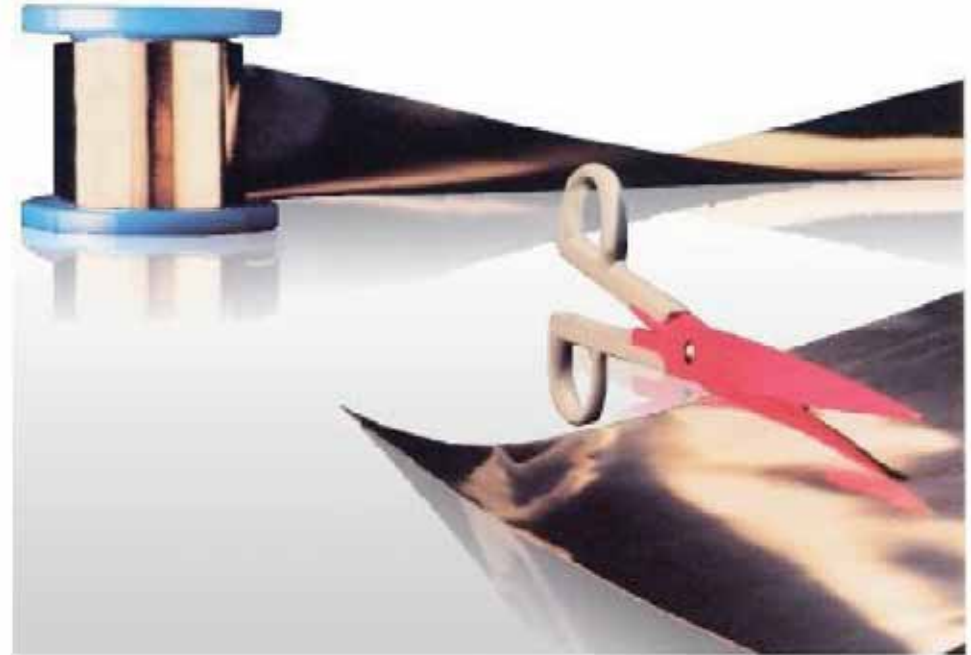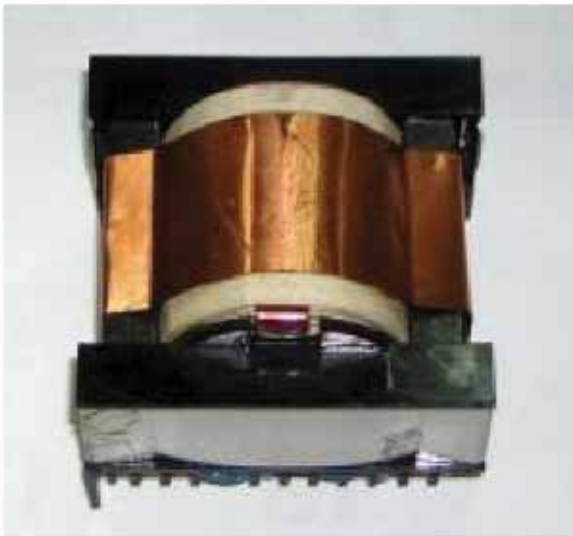- How Do External Shields Differ from Internal Shields?
- Shields Radiated Noise ONLY!
- As Expensive as Internal Shields




Transformers for EMC – Multi-layer Primary Termination


Nidcom



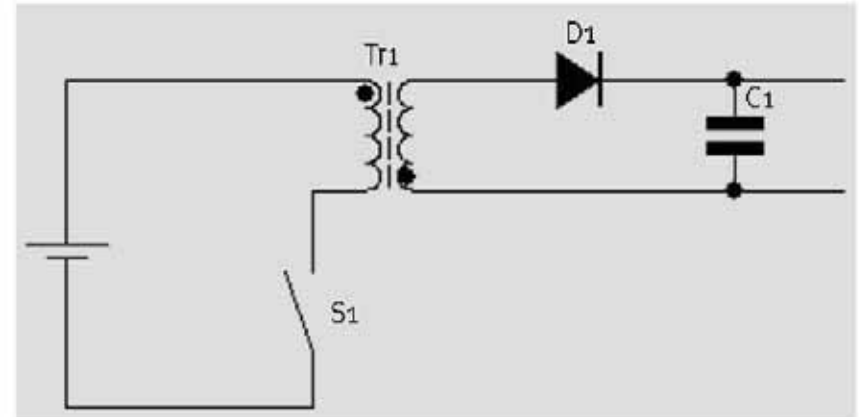- How does One Terminate a Multi-layer Primary?
- Terminate Start to Switch so Subsequent Layer/s Shield High dv/dt Windings from outside world.




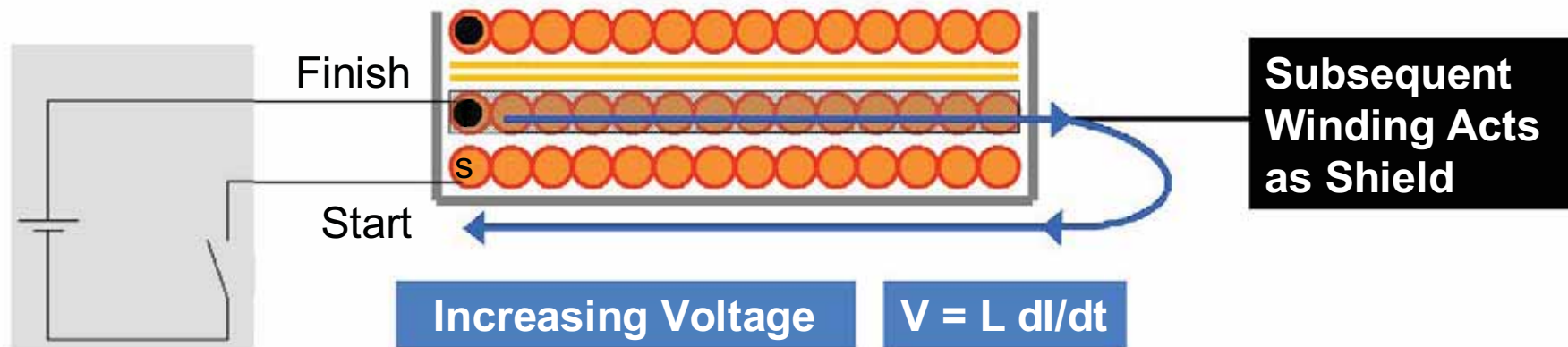Note Perfectly Dots on
Finish Contention Okay?



Transformers for EMC – Y-Cap Termination

Nidcom

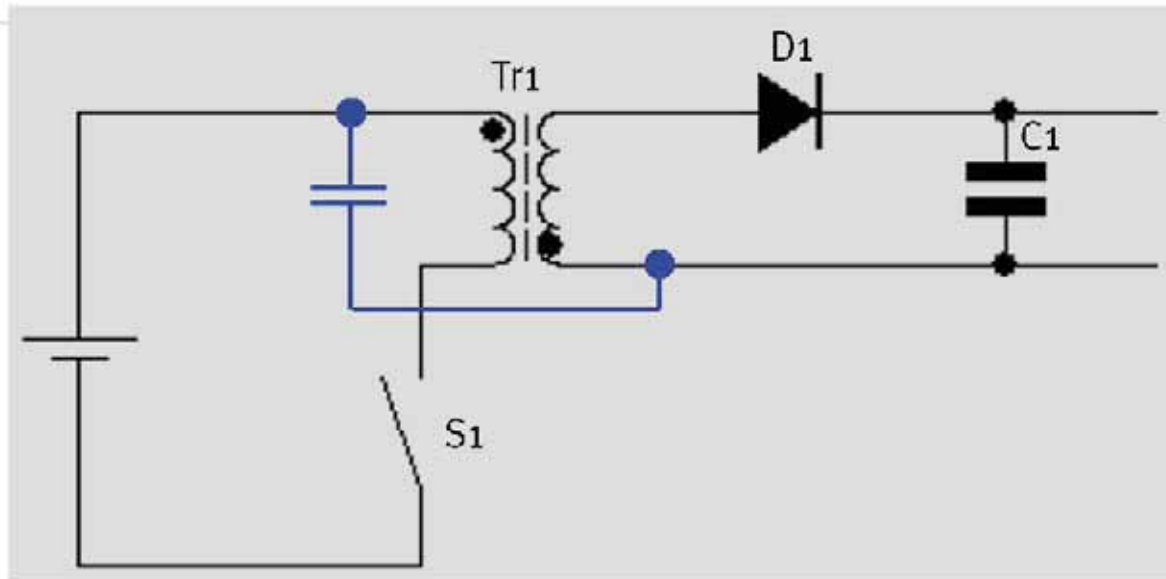

- Noise Couples Through the Transformer via C_{ww}
 - Noise Seeks Path to Primary Circuit
 - Without Path, Noise May Become Conducted Emissions
- Y-Cap Across Transformer Reduces Noise
 - Tune the Capacitor for Optimum Loss vs. Noise Reduction
 - Capacitor Usually in the 2.2nF to 4.7nF range
 - Y-Caps to Transformer Terminals not on Switch nor on Diode
 - Close to Transformer as Possible

What Can We Do?

Decrease C_{ww} ?


What Else Can We Do?

Transformers for EMC – No Varnish or Potting

Nidcom



Radiated Emissions

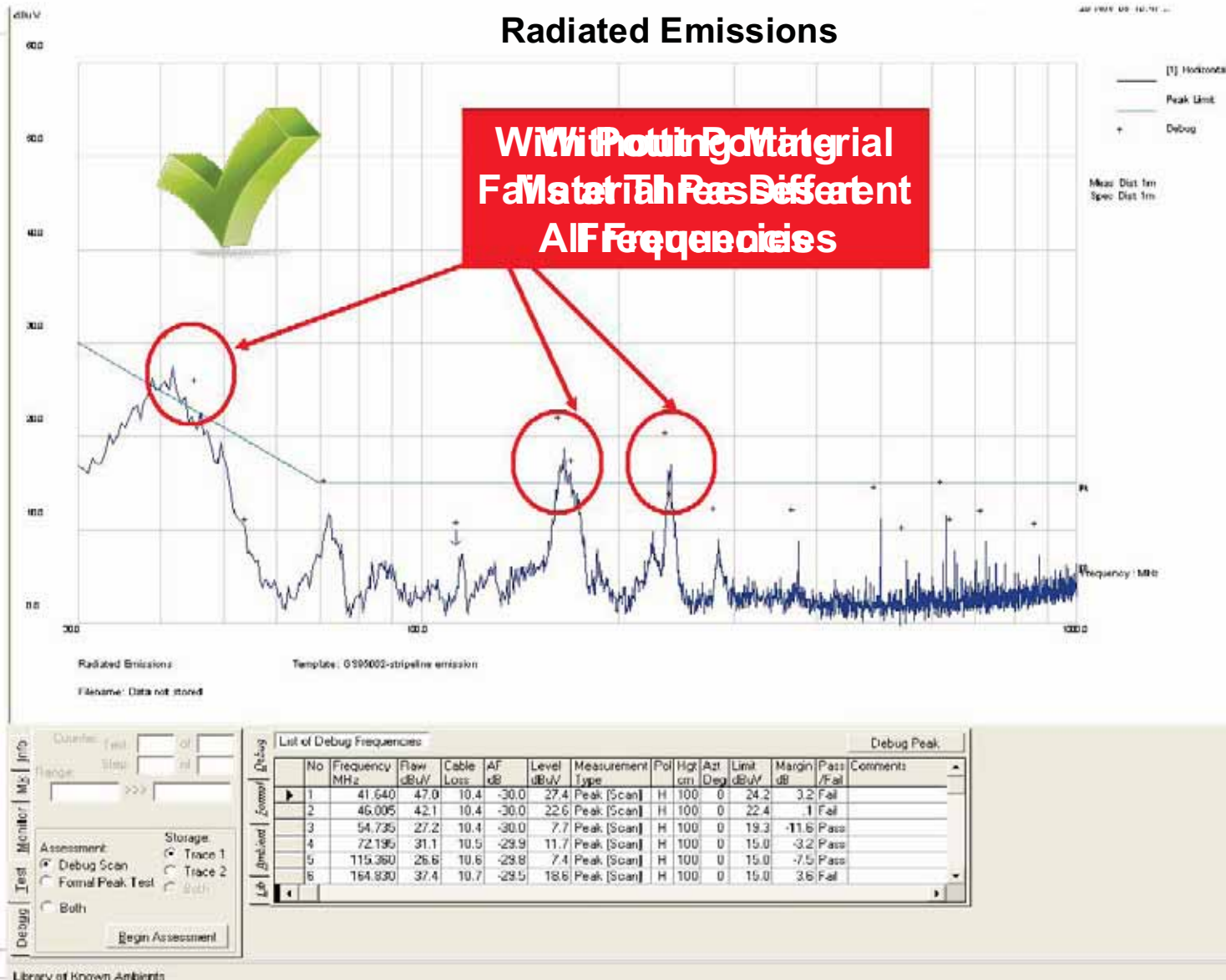


Transformers for EMC - Small Designs


Nidcom

Why Build Smaller Designs?

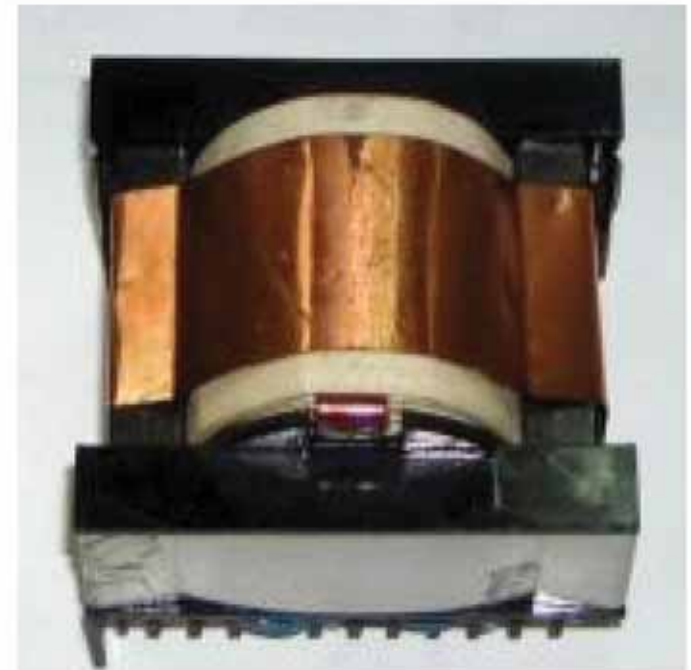- **Build Smaller More Compact Transformers**
- **Smaller Transformers have less Parasitics**
 - Less Capacitance
 - Smaller Leads (ie. Smaller Antennas)
 - Smaller Gaps
 - Less Leakage Inductance
- **Less Conducted and Less Radiated Noise**



Transformers for EMC – Power Supply

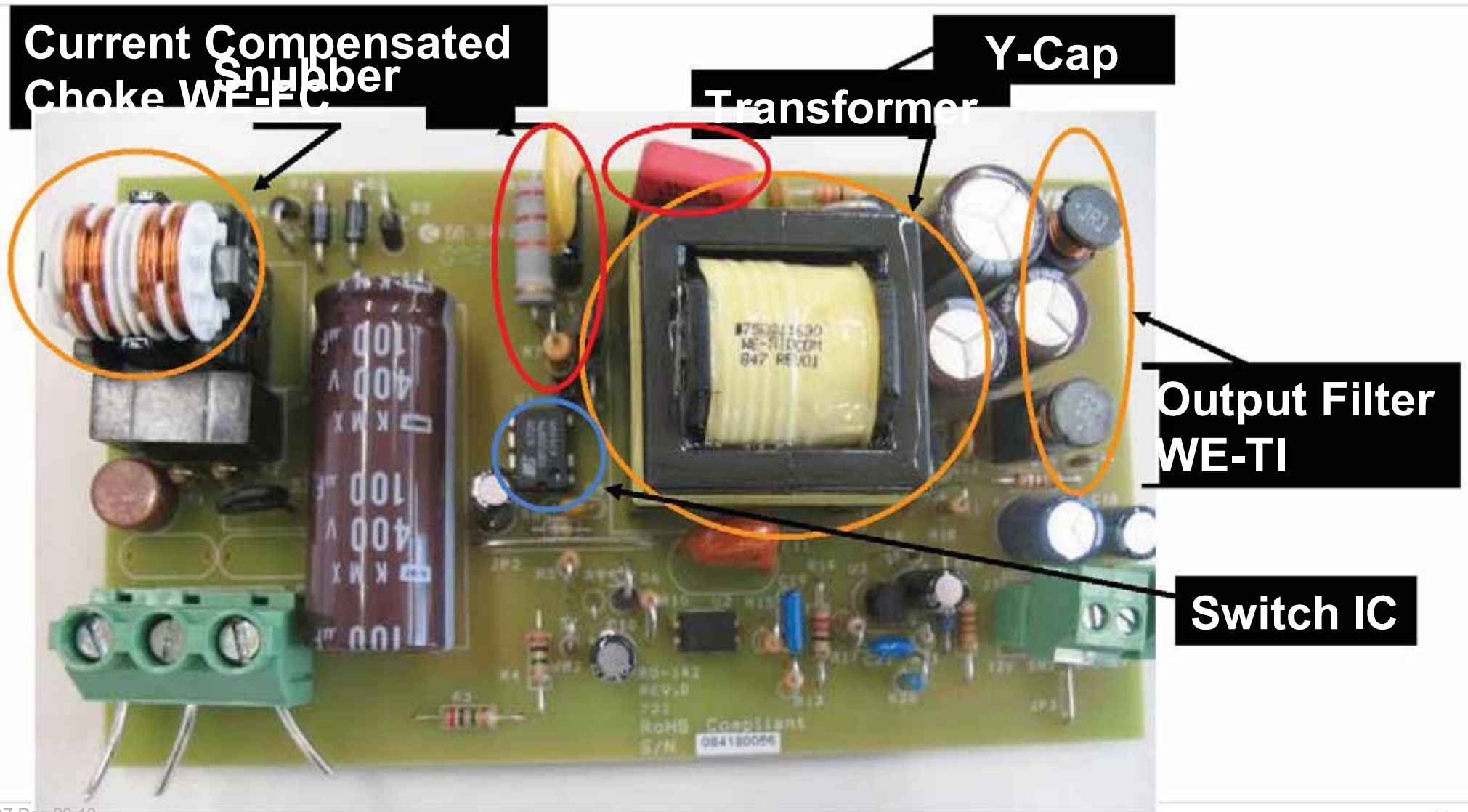

Transformers for EMC – Schematic

Midcom




Current Compensated


Snubber Transformer

Y-Cap

Output Filter

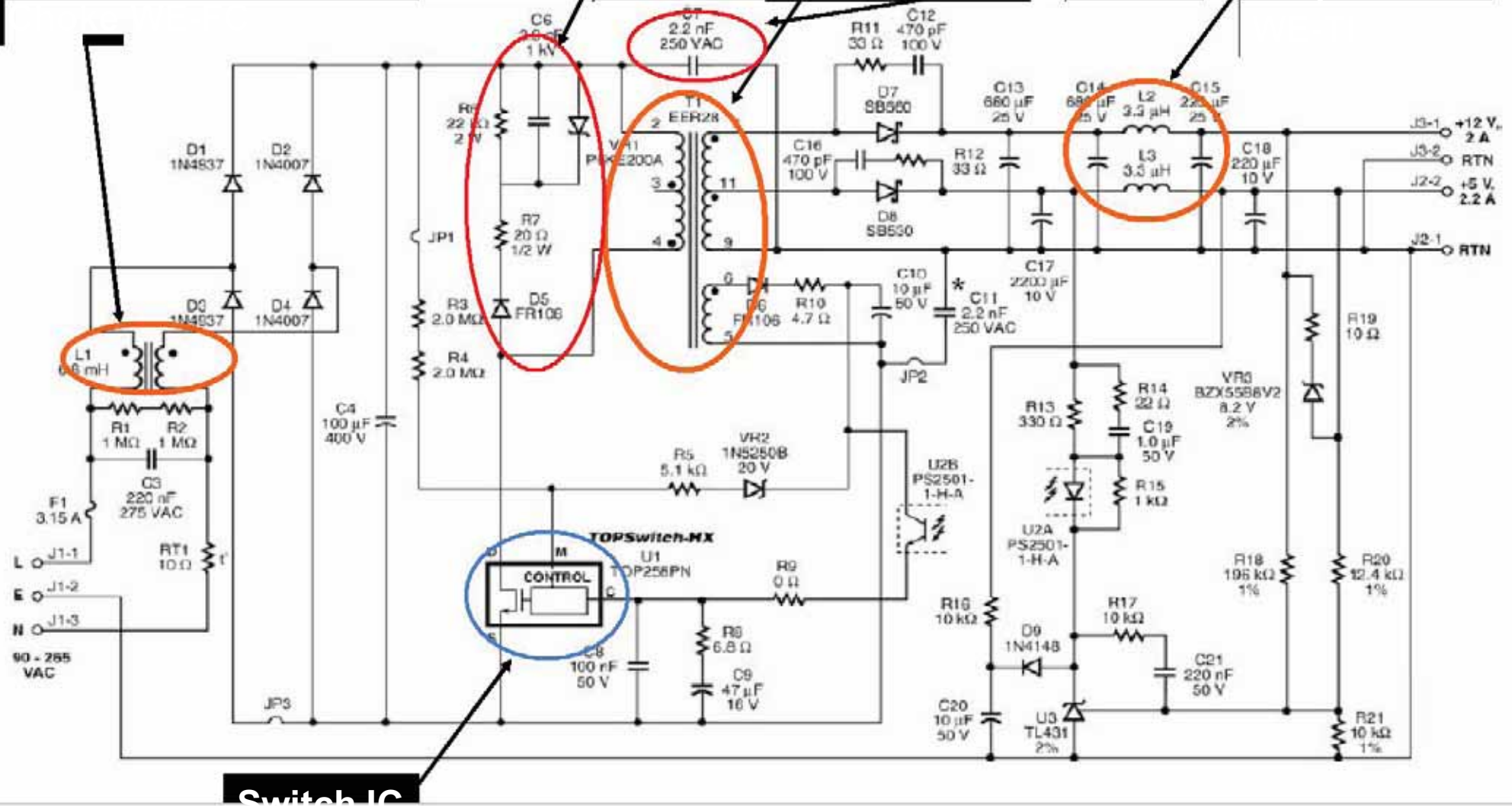

Transformers for EMC – Example 1

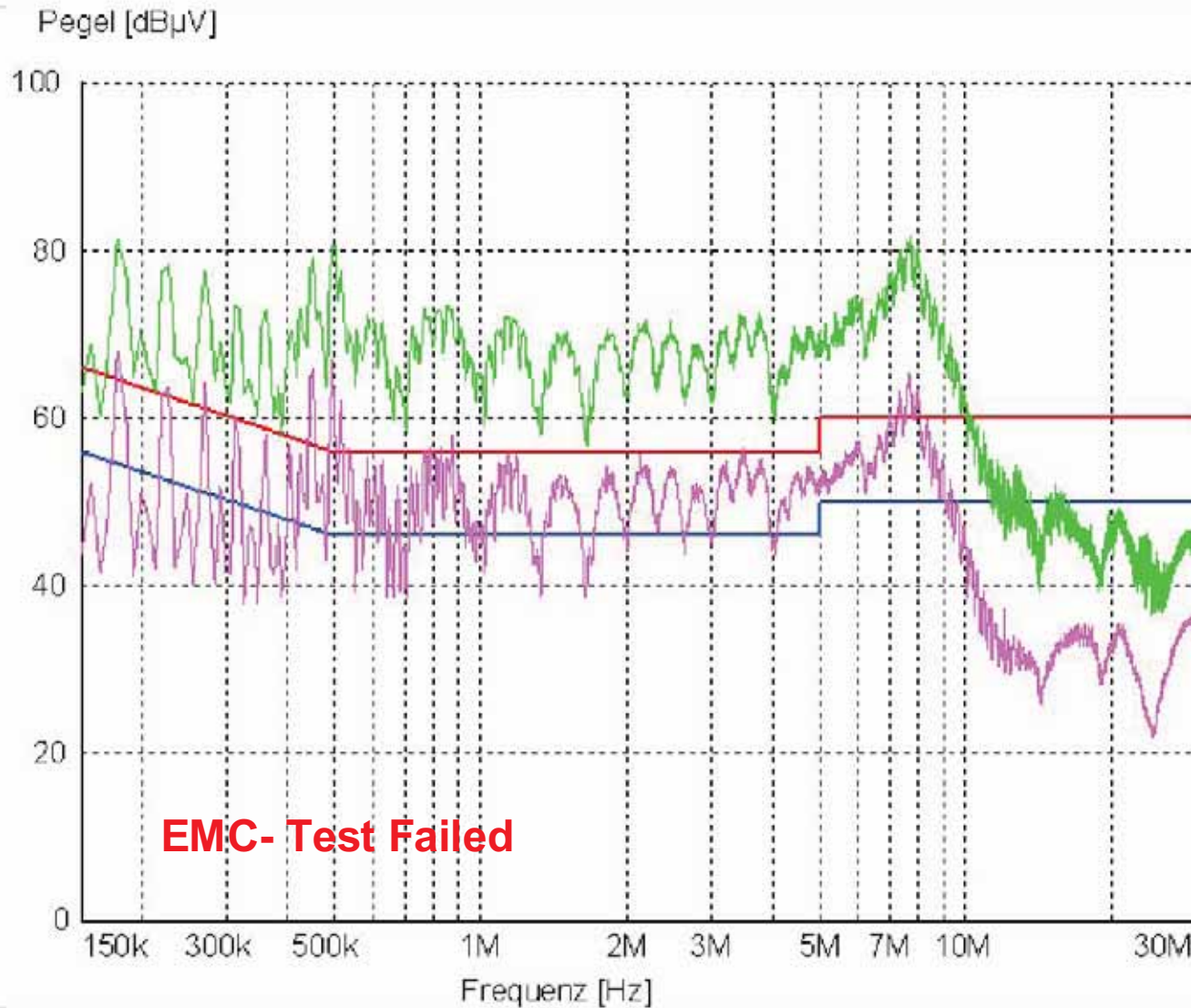Nidcom

- Without Current Compensated Choke
- With Adjusted Snubber
- Without Adjusted Y-Cap

Peak


Avg.

Peak

Avg.

Transformers for EMC – Example 2

Nidcom

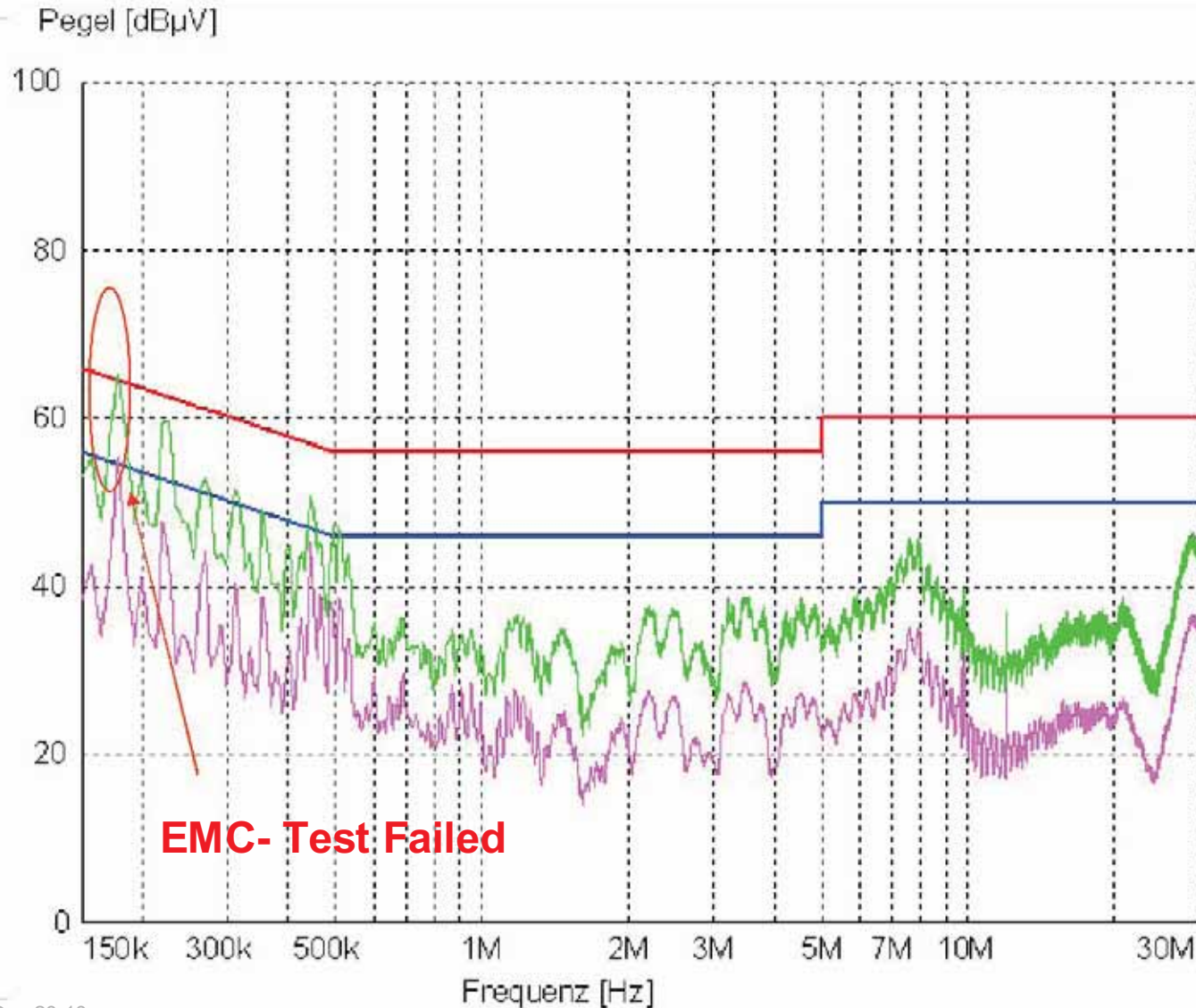

- With Current Compensated Choke
- With Adjusted Snubber
- Without Adjusted Y-Cap

Peak


Avg.

Peak

Avg.

Transformers for EMC – Example 3

Nidcom

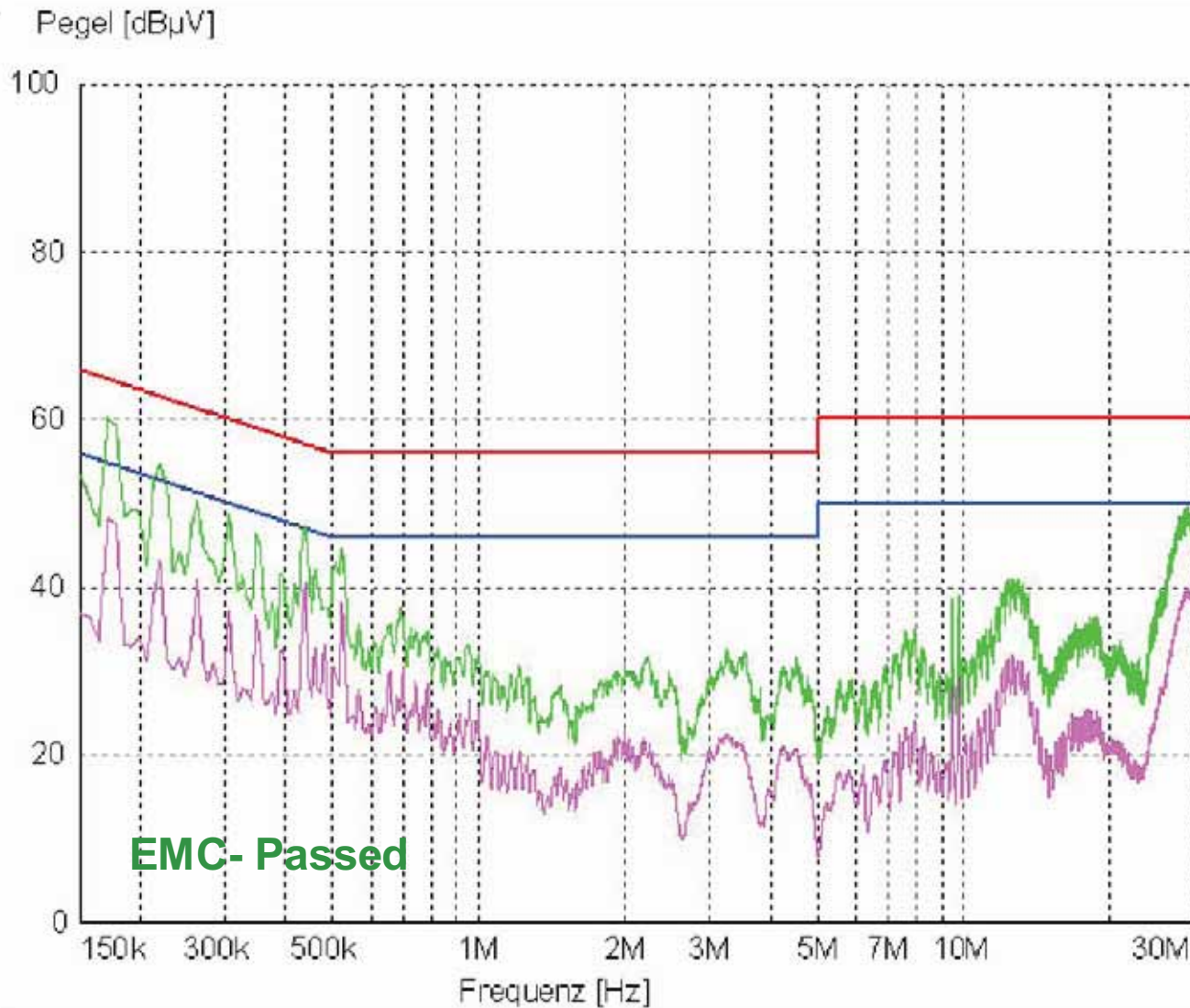

- With Current Compensated Choke
- With Adjusted Snubber
- With Adjusted Y-Cap

Peak


Avg.

Peak

Avg.

Transformers for EMC – Example 4

Nidcom

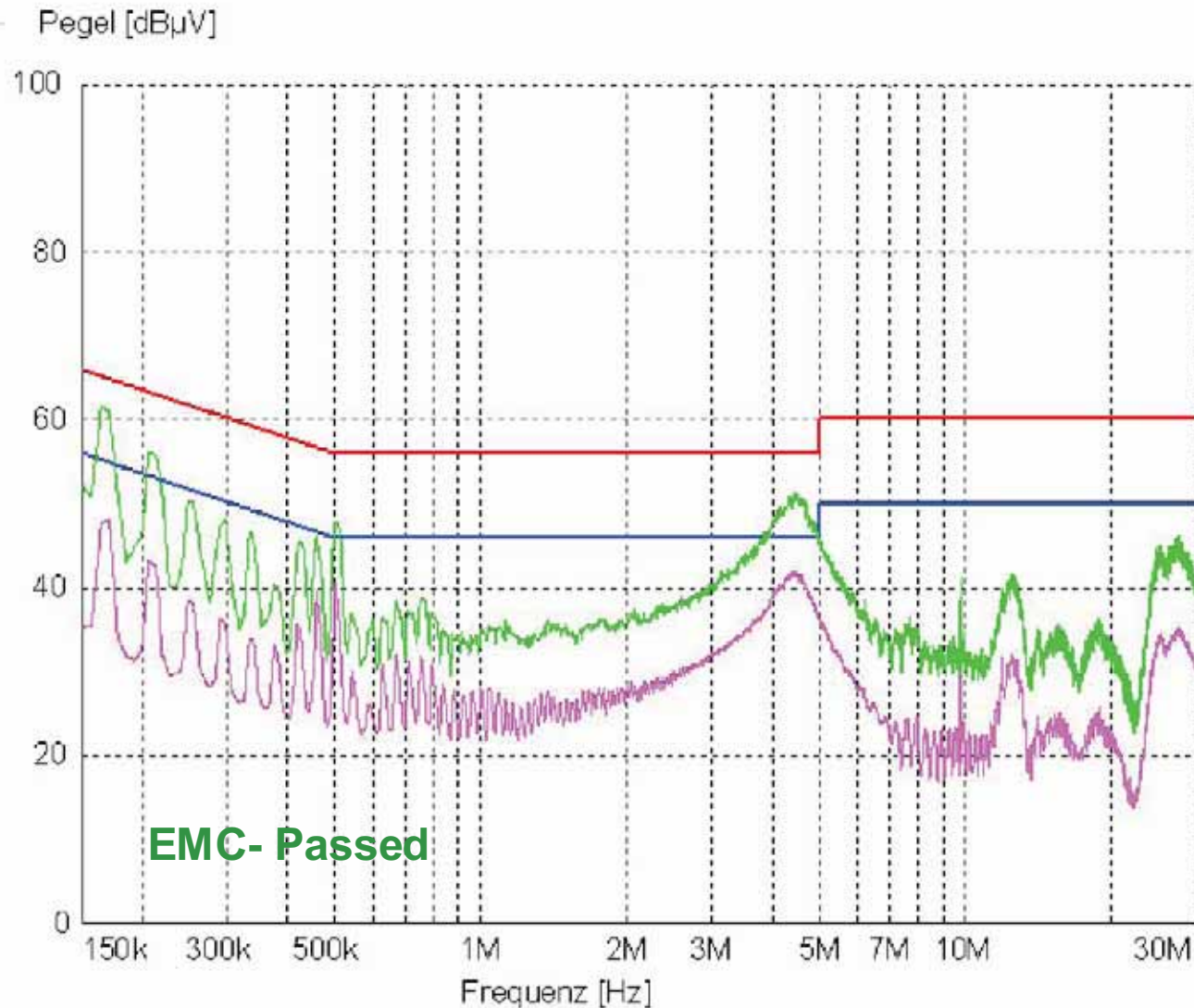

- With Current Compensated Choke
- Without Adjusted Snubber
- With Adjusted Y-Cap

Peak


Avg.

Peak

Avg.

Transformer for EMC – Conclusion for this Supply

Nidcom

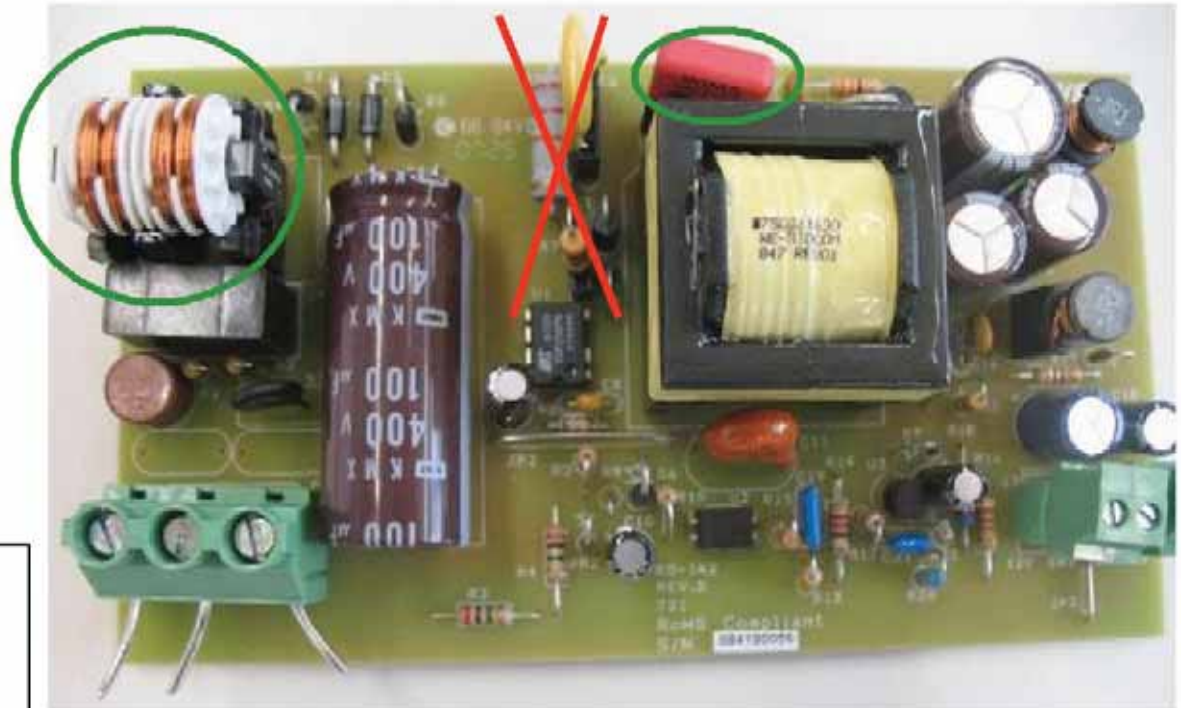WE
WÜRTH ELEKTRONIK

- **Necessary to Pass**
 - Current Compensated Choke
 - Y-Caps
- **Not Necessary to Pass**
 - Optimized Snubber

Online:

Nidcom



EMC & Inductive Solutions

Zur Unternehmensgruppe

suchen

more than you expect

www.we-online.com



Firmenprofil

more than you expect

Produkte

Kontakt

Termine

Jobs & Karriere

English

Français

Produktkatalog bestellen

Kostenlose
Musterbestellung



Herzlich willkommen bei der
Würth Elektronik eiSos GmbH & Co. KG

24 h eMail Service

← Zurück



Neuer Katalog 2003 ab sofort



Partnerschaft mit IC-Herstellern



Fachbuch "Trilogie der Induktivitäten"

Inductor Selector Guide

Nidcom



WE Inductor Selector Version 1.1.1

File Service ?

www.we-online.com

more than you expect

WE Inductor Selector
Easy Inductor Selection for DC/DC Converter

Select Converter Topology: ☒ Buck Converter ☐ Boost Converter ☐ SEPIC Converter ☐ Manual Selection

Calculations:

$L_{opt} = 24.263 \mu H$
 $I_{rms} = 3.000 A$
 $I_{peak} = 3.300 A$
 $\Delta I_L = 0.600 A$
 $V_t = 0.286$
 $t_{on} = 1.429 \mu s$

$U_{in} = 10 \text{ V}$
 $U_{out} = 3.3 \text{ V}$
 $f = 200 \text{ kHz}$
 $\Delta I = 20 \%$
 $I_{out} = 3 \text{ A}$
 $U_F = 0.7 \text{ V}$

Series	Size	Ordercode	L [μH]	RDCtyp [mΩ]	I _N [A]	I _{Sat} [A]	L [mm]	W [mm]	H [mm]	Core Mat	T _{amb} [°C]	T _{max} [°C]	Shielded
WE-PD	XXL	7447709220	22.000	33.300	5.300	6.500	12.00	12.00	10.00	Nickel12n	85	125	yes
WE-PD	L	744771122	22.000	31.000	3.370	3.770	12.00	12.00	6.00	Nickel12n	85	125	yes
WE-PD	XL	744770122	22.000	33.000	4.100	5.000	12.00	12.00	8.00	Nickel12n	85	125	yes
WE-PD	XL	744770127	27.000	35.000	3.700	3.800	12.00	12.00	8.00	Nickel12n	85	125	yes
WE-PD	XXL	7447709330	33.000	36.800	4.200	5.500	12.00	12.00	10.00	Nickel12n	85	125	yes
WE-PD	XL	744770133	33.000	47.000	3.200	3.600	12.00	12.00	8.00	Nickel12n	85	125	yes

Würth Electronics Midcom Inc.



What more do you need?

Nidcom

Look at our Book:

Chap.1: Basics

keep it simple, stupid

Chap.2: Components

Descriptions, Applications, Simulation
Models and many more

Chap.3: Filter-Circuits

Design, Grounding, Layout, Tips

Chap.4: Applications

Circuit, suggested parts, Layout

Chap.5: Appendices

from A to Z



Any Questions?

Nidcom



Thank you from – the Würth Electronics Midcom East Coast

