

2009




WURTH ELECTRONICS MIDCOM INC. EMI Compliance Solutions & Inductive Materials

Speaker: Dean Huumala
Dean.Huumala@we-online.com

How To Control EMI?



For our customers:

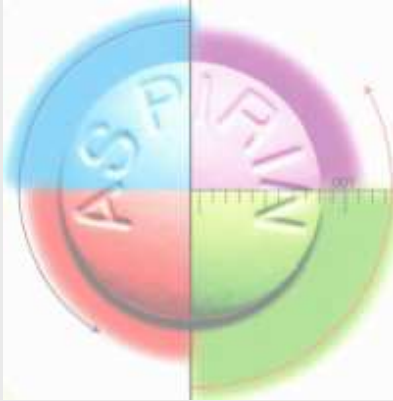

„Headache“



„ like a fight: Bull (noise) and red cloth (application)“




A mystery.....

Interference - Transmitter / Receiver

1. Coupling mode

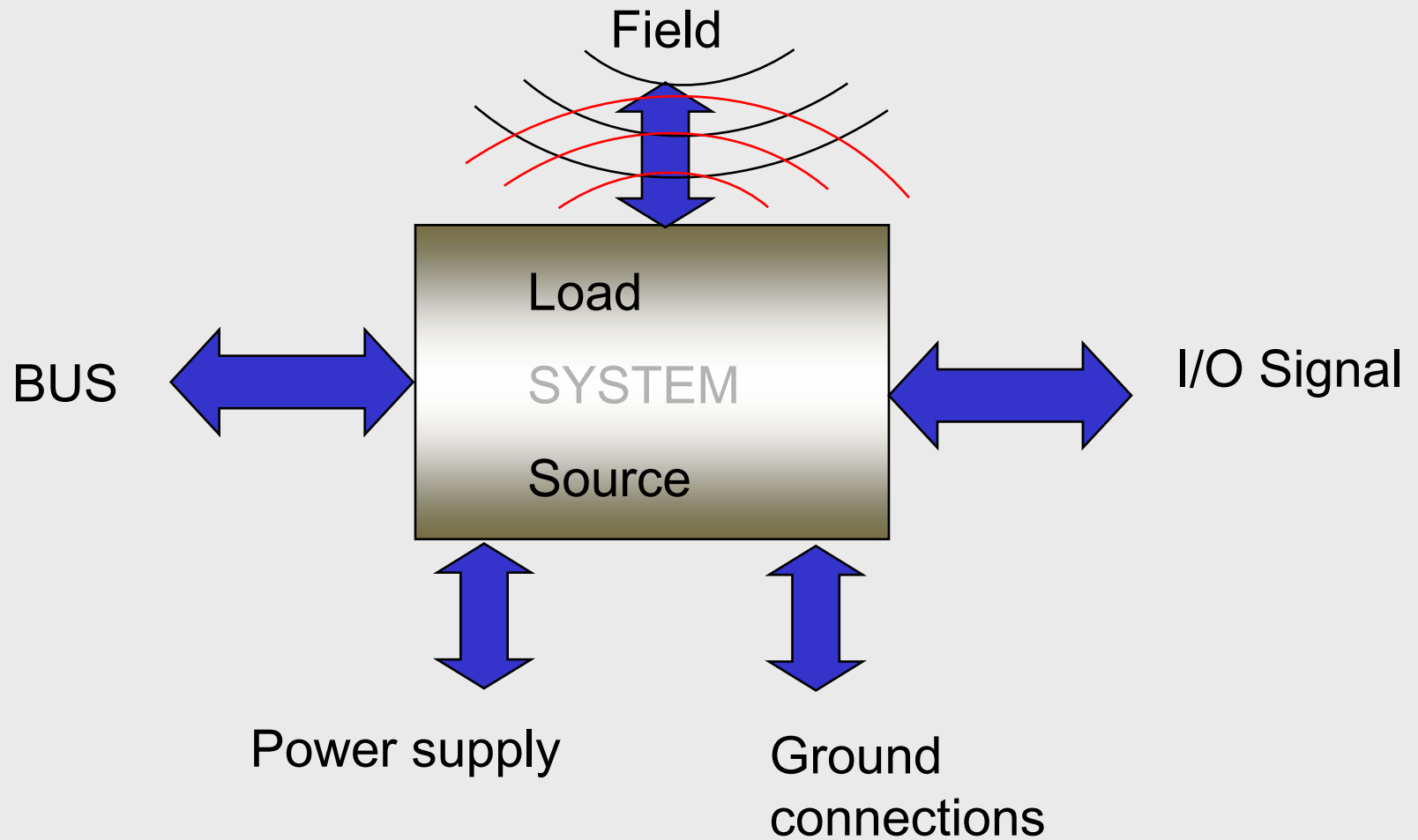2. Attenuation
3. Emissions
4. Transformers



Interference Characteristics

1. Coupling mode

2. Attenuation

3. Emissions

4. Transformers

Symmetrical

conducted
noise

Powder-, rod
core chokes

Asymmetrical


coupled noise

CM- chokes

Field

radiated noise

EMI ferrites,
shielding

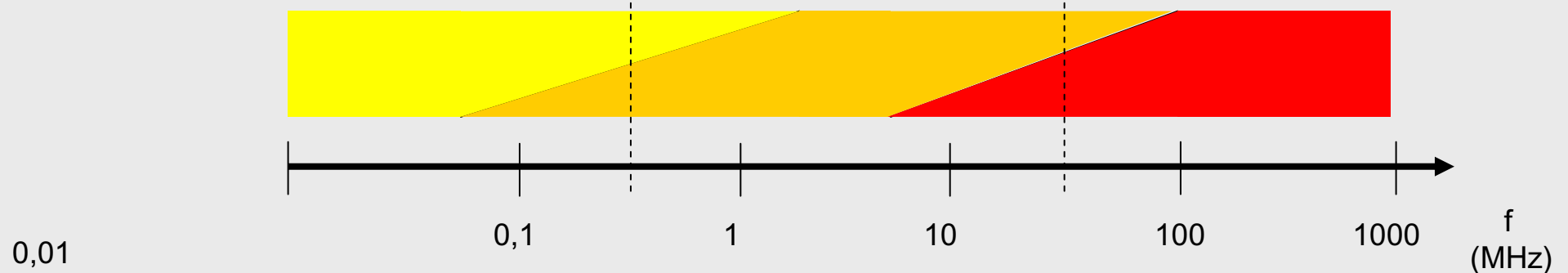


Interference - Frequency Range for EMI Tests




1. Coupling mode

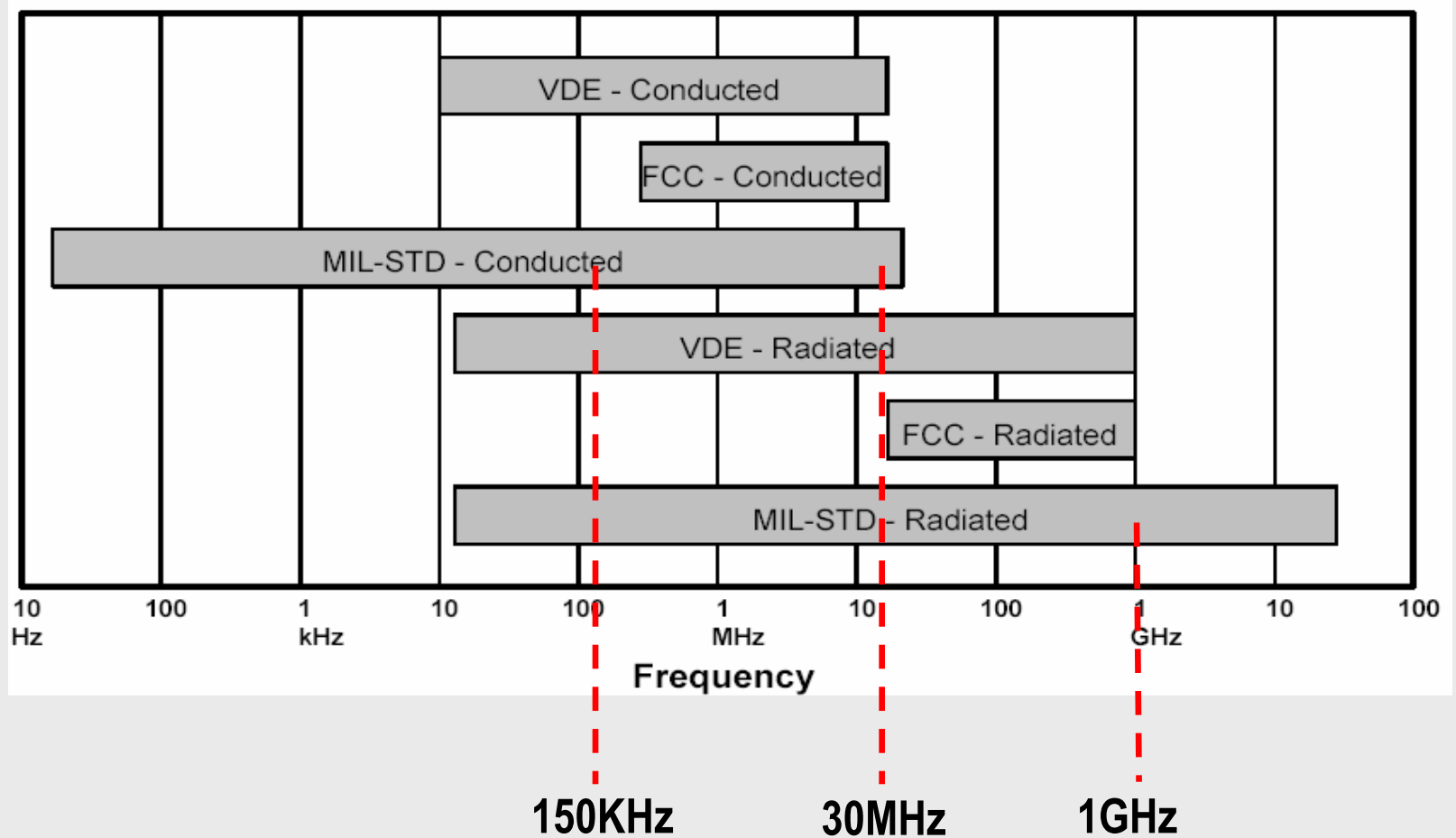
2. Attenuation
3. Emissions
4. Transformers



How Much Inductance is Needed?

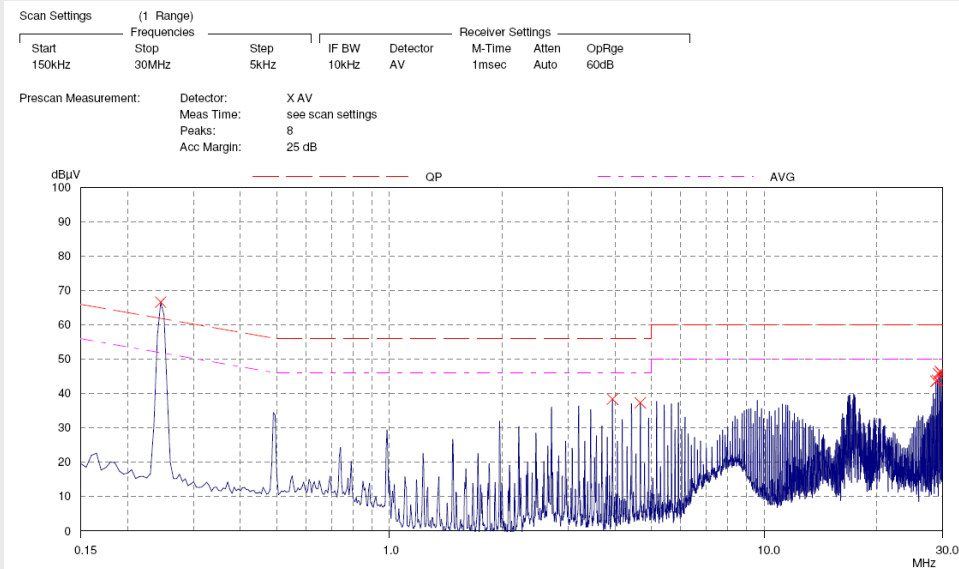


before

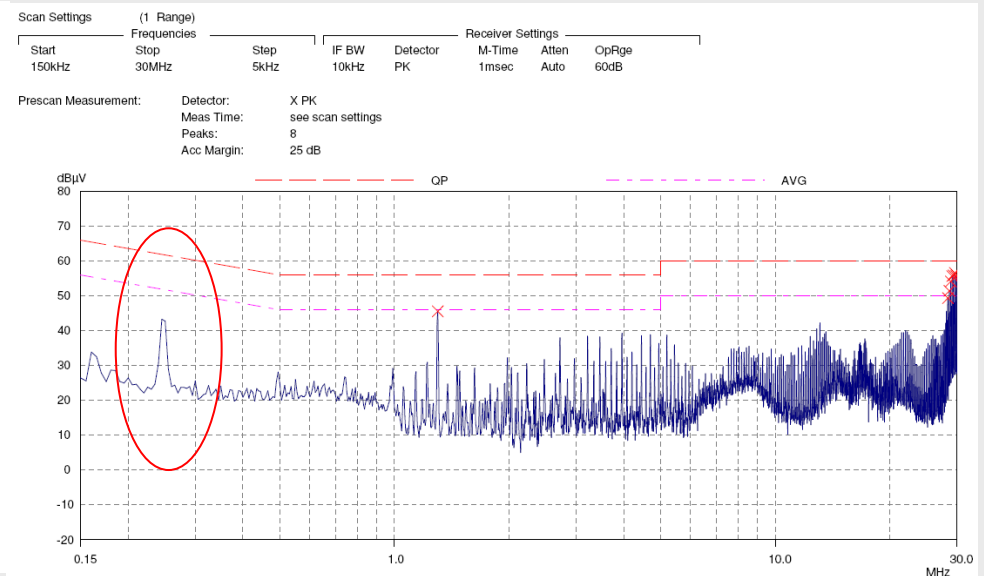

after

only changed one component

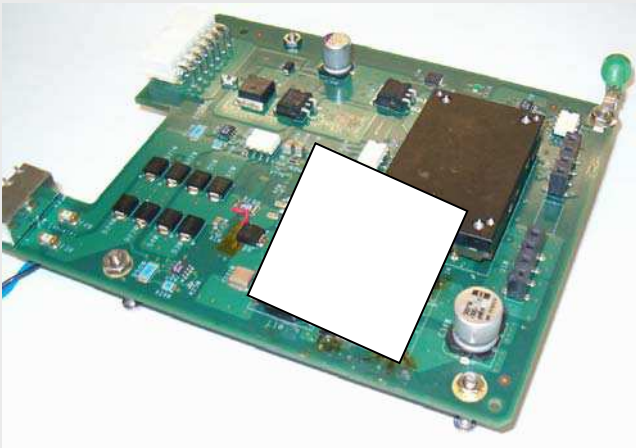

30mH μ !


What Impedance is Needed?

1. Coupling mode


2. Attenuation

3. Emissions

4. Transformers

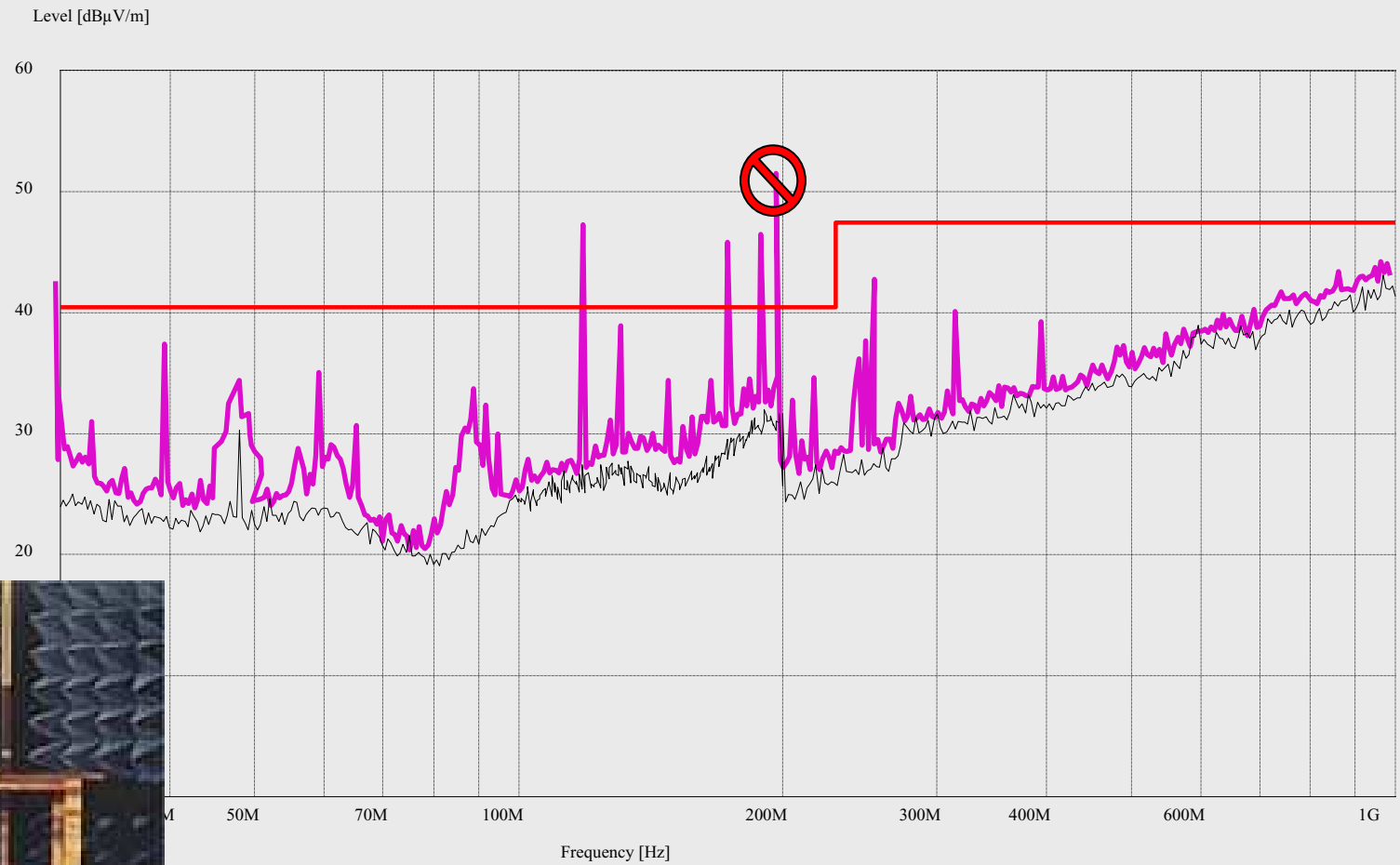


Insertion Loss Model

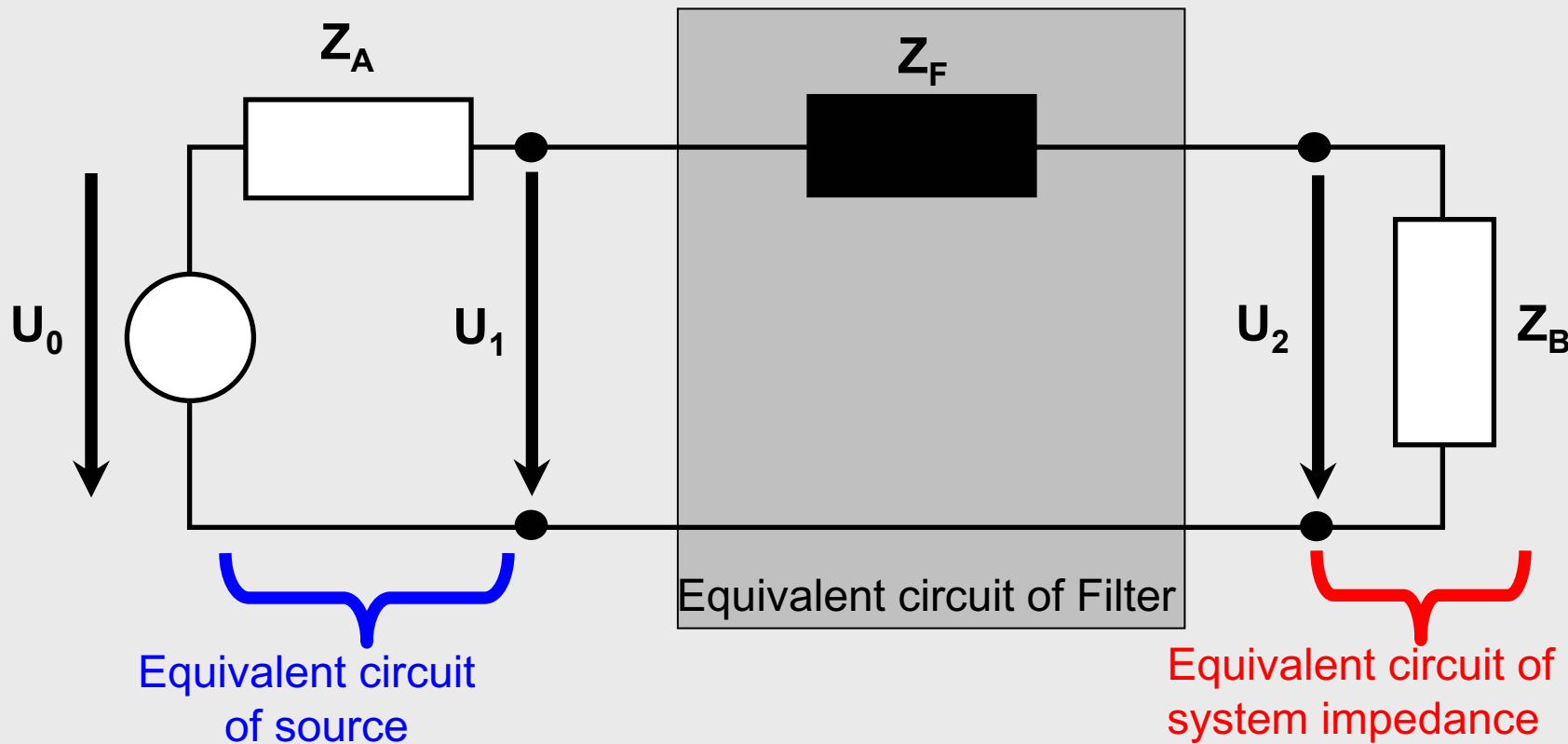


Insertion Loss =>
$$A = 20 \log \frac{Z_A + Z_F + Z_B}{Z_A + Z_B} \quad \text{in } (dB)$$

The Real World..... !

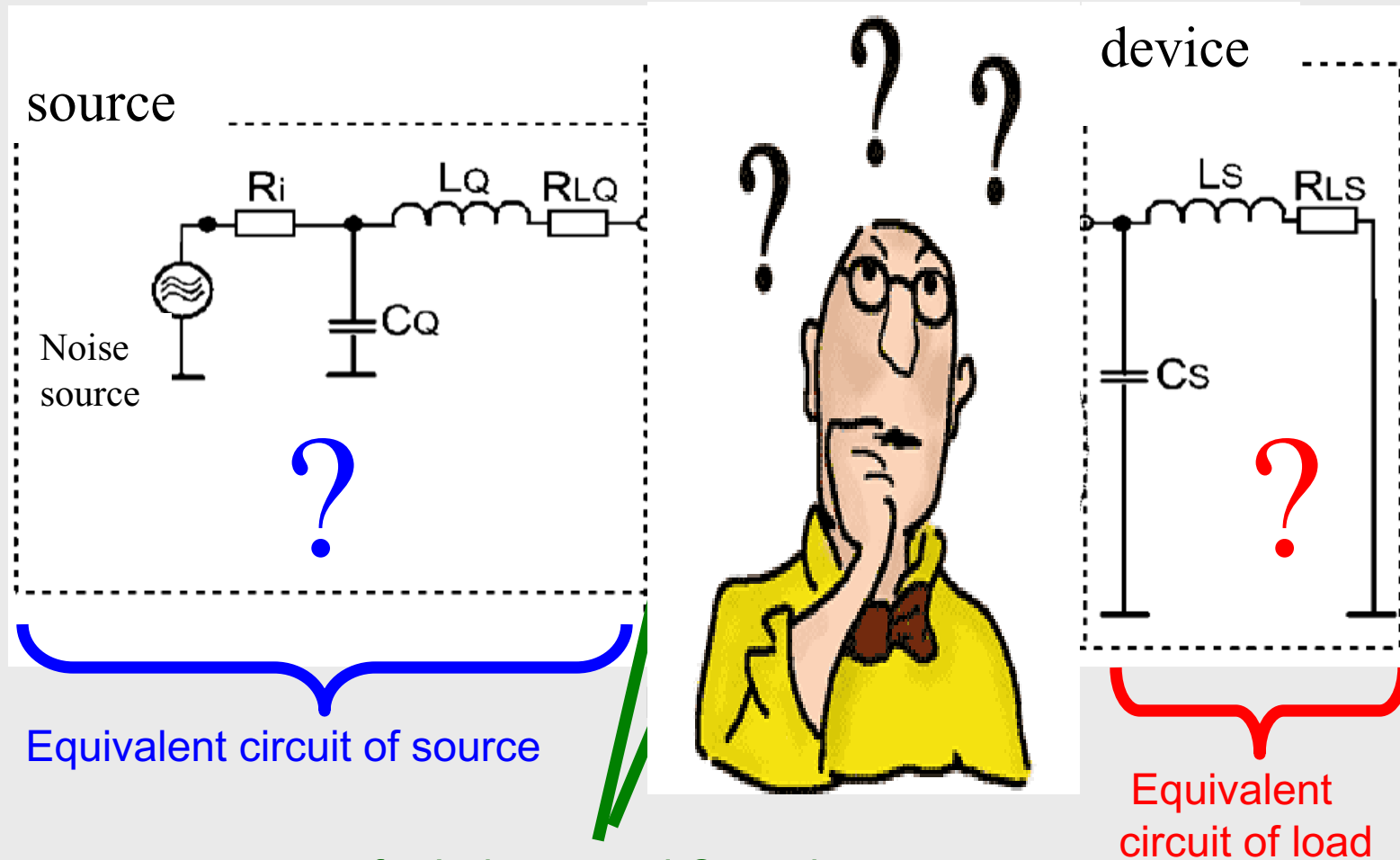

for Inductor and Capacitor one
can find Simulation-Models

Which Impedance Z_F is Needed ?

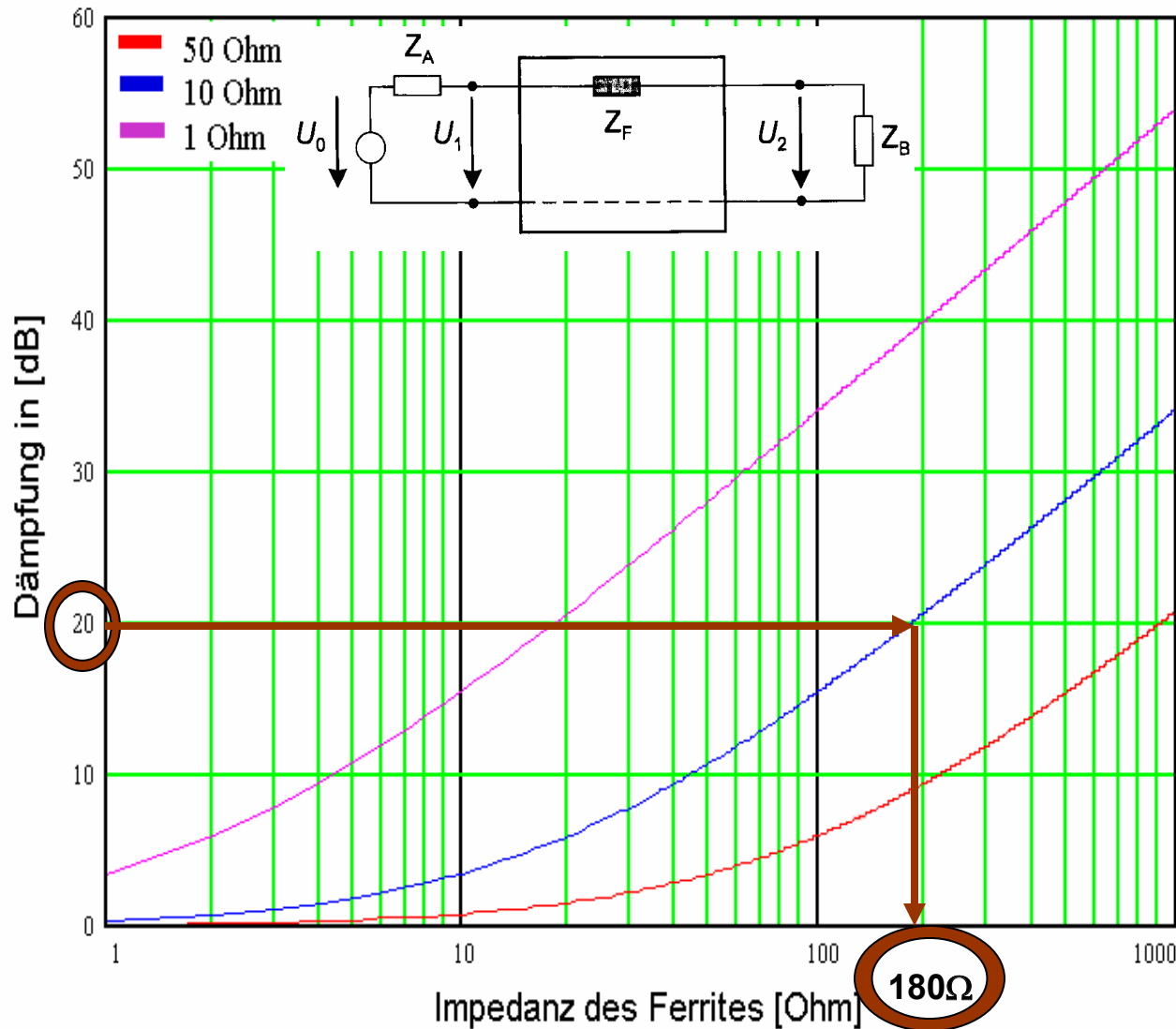

Example 1: required attenuation
= 20dB @ 200 MHz

VCC-Distribution


System impedance ca. 10 Ohm

=> goto Nomogramm:

180 Ω => choose: 220 Ω

Case 1: Attenuation Reached

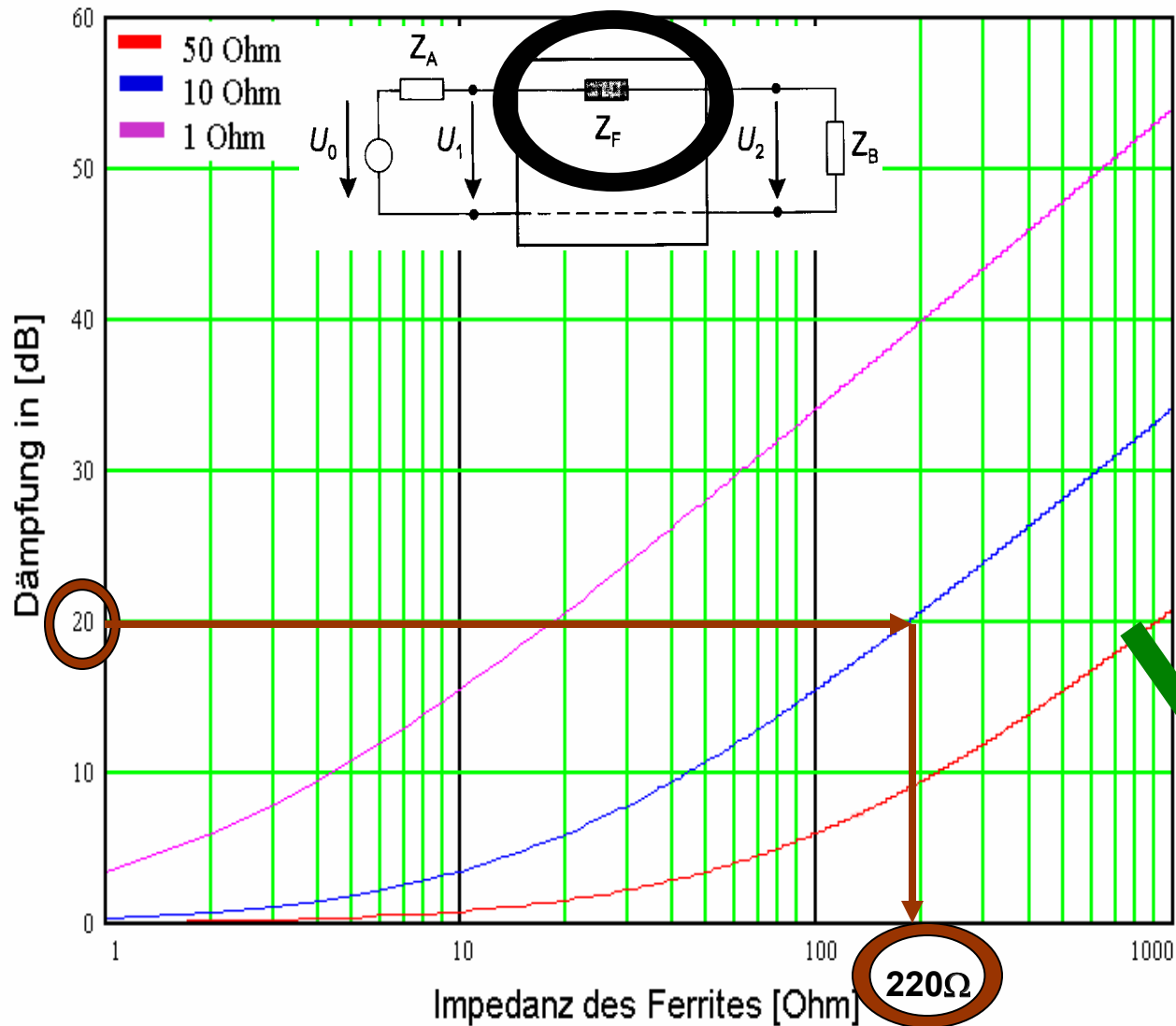
1. Coupling mode
- 2. Attenuation**
3. Emissions
4. Transformers



The initial setup that System Impedance is around 10 Ohm at 200 MHz is true !

Case 2: More Attenuation

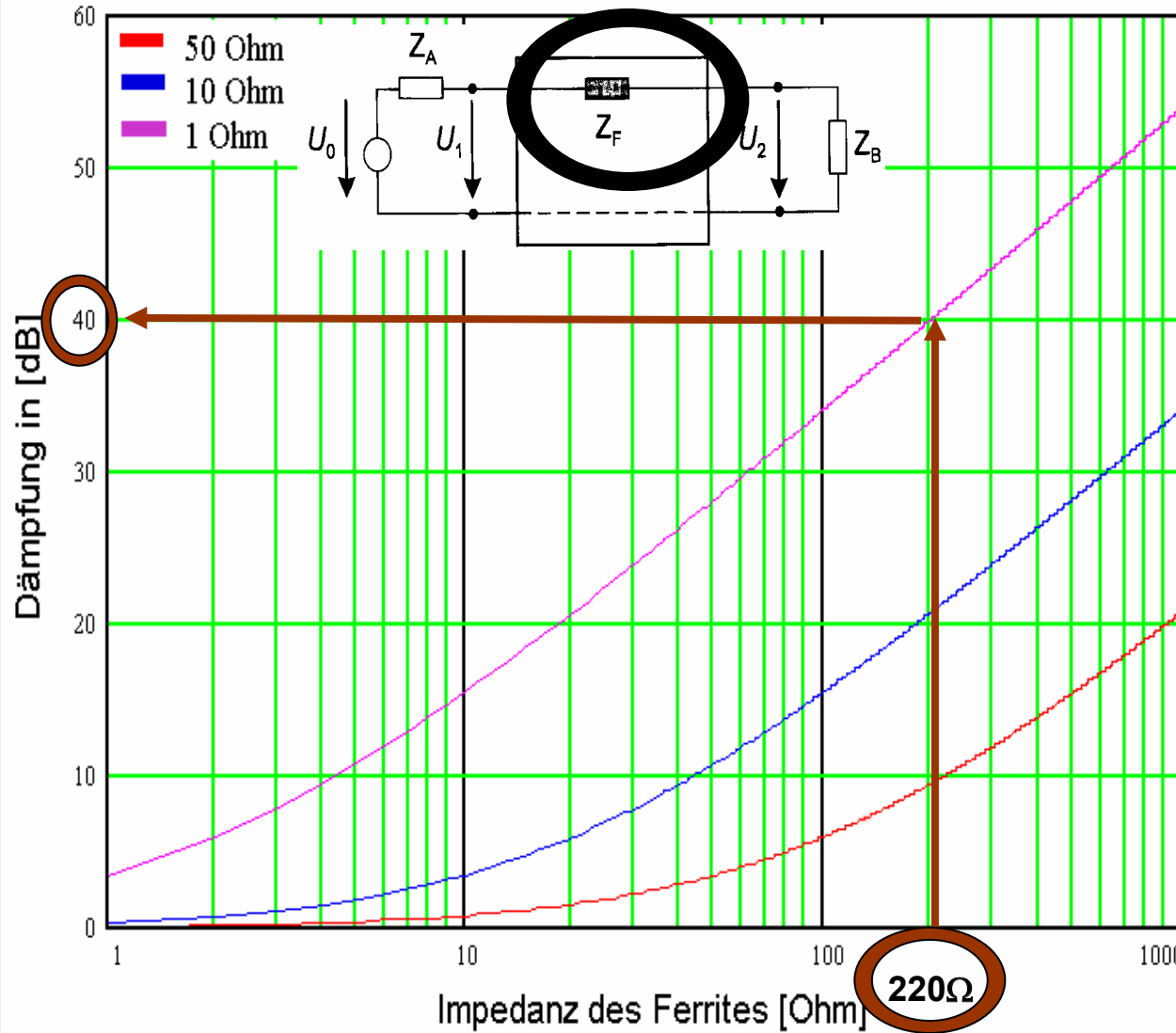- 1. Coupling mode
- 2. Attenuation**
- 3. Emissions
- 4. Transformers




Measurement of e.g. 40dB with Ferrit.

The System-impedance Z_A and Z_B are much lower (at around 1 Ohm)!



Case 3: Less Attenuation

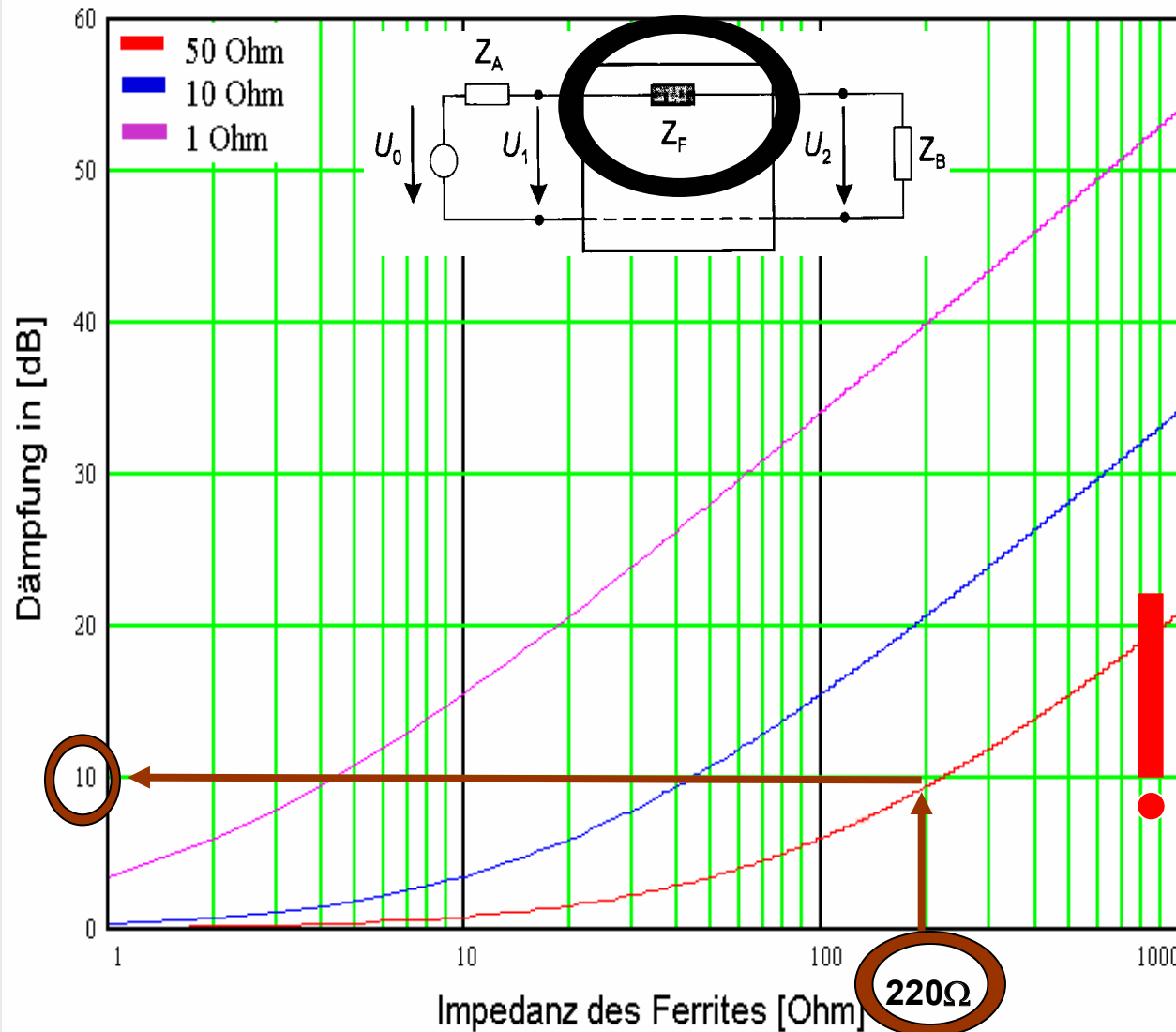1. Coupling mode
- 2. Attenuation**
3. Emissions
4. Transformers



Measured only
e.g. 10dB
with Ferrite.

The System-
impedances ZA
and ZB are
much higher
than expected
(around
50 Ohm) !

OR

Additional
coupling paths
not taken into
account !

Analyse the Results




1. Coupling mode


2. Attenuation

3. Emissions

4. Transformers

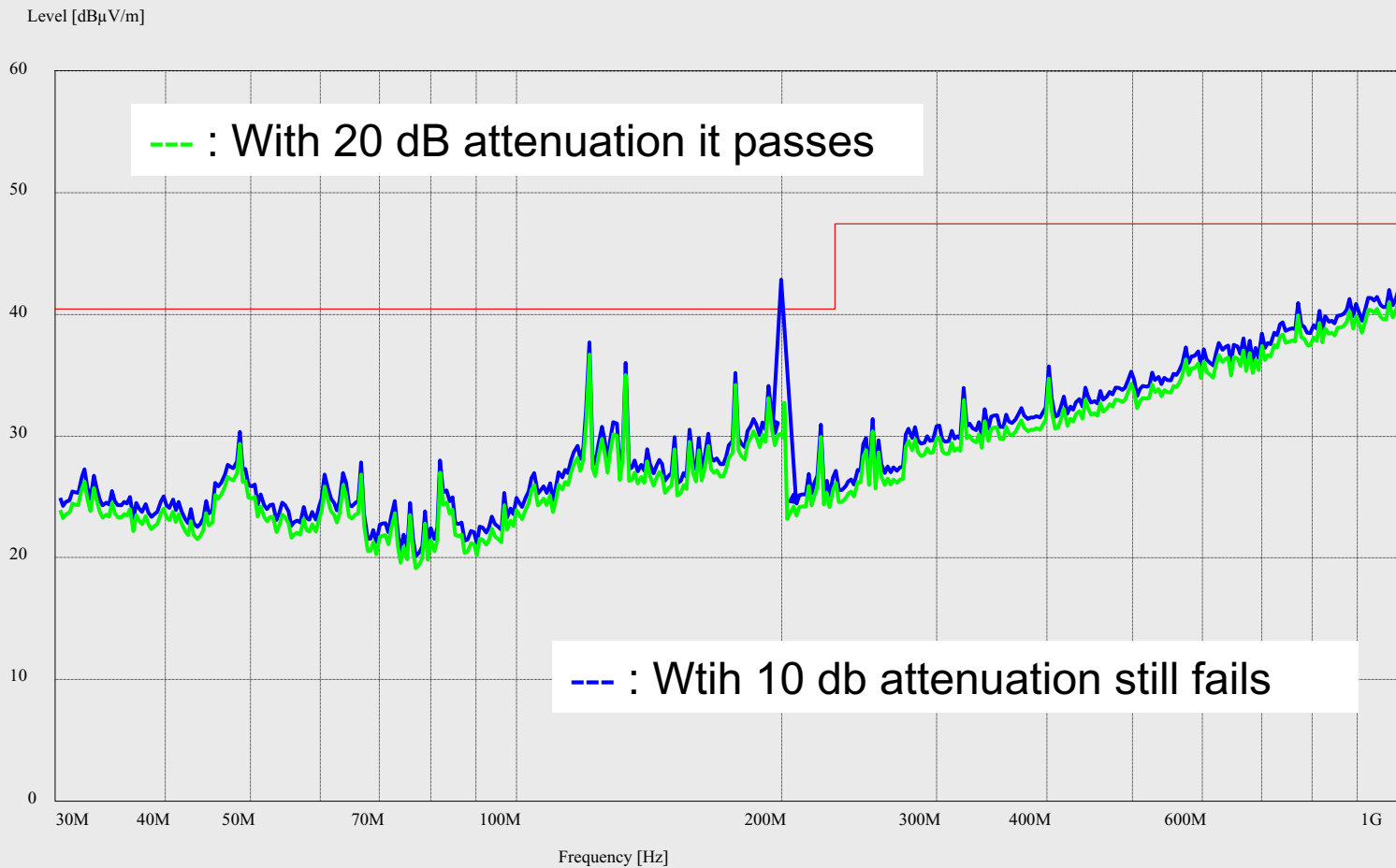

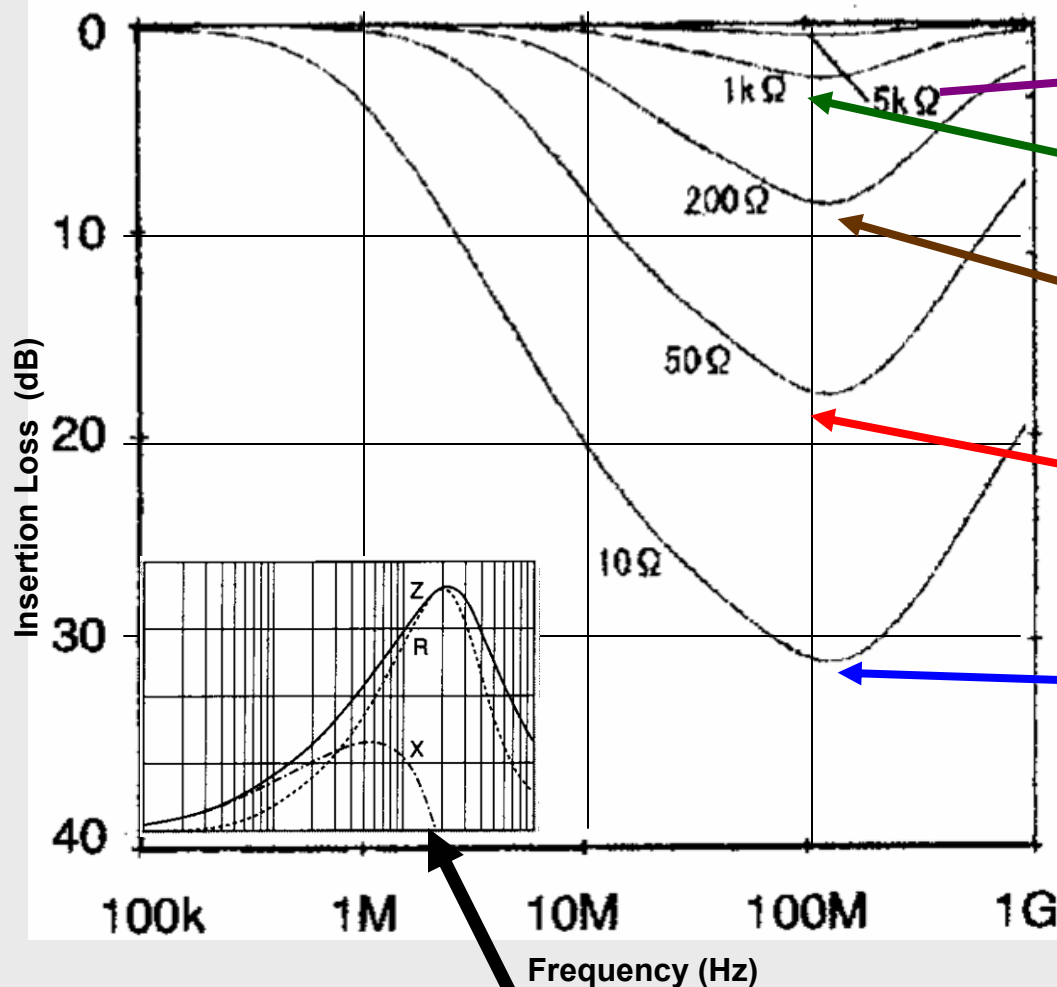Insertion Loss vs. Impedance of Source/ Load (Z_A / Z_B)




with $Z_A = Z_B = 5000 \Omega = \text{constant}$
no effect in filtering!

$A = -3 \text{ dB max.}$
 with $Z_A = Z_B = 1000 \Omega = \text{constant}$

$A = -8 \text{ dB max.}$
 with $Z_A = Z_B = 200 \Omega = \text{constant}$

$A = -18 \text{ dB max.}$
 with $Z_A = Z_B = 50 \Omega = \text{constant}$

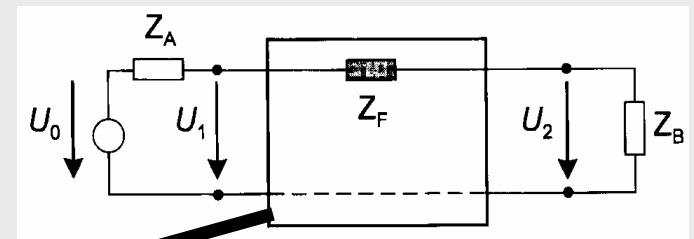$A = -32 \text{ dB max.}$
 with $Z_A = Z_B = 10 \Omega = \text{constant}$



SMD-Ferrite $Z_F = 600 \text{ Ohm @ } 100 \text{ MHz}$


V_{CC} Decoupling Example - Test Board

1. Coupling mode

2. Attenuation

3. Emissions


4. Transformers

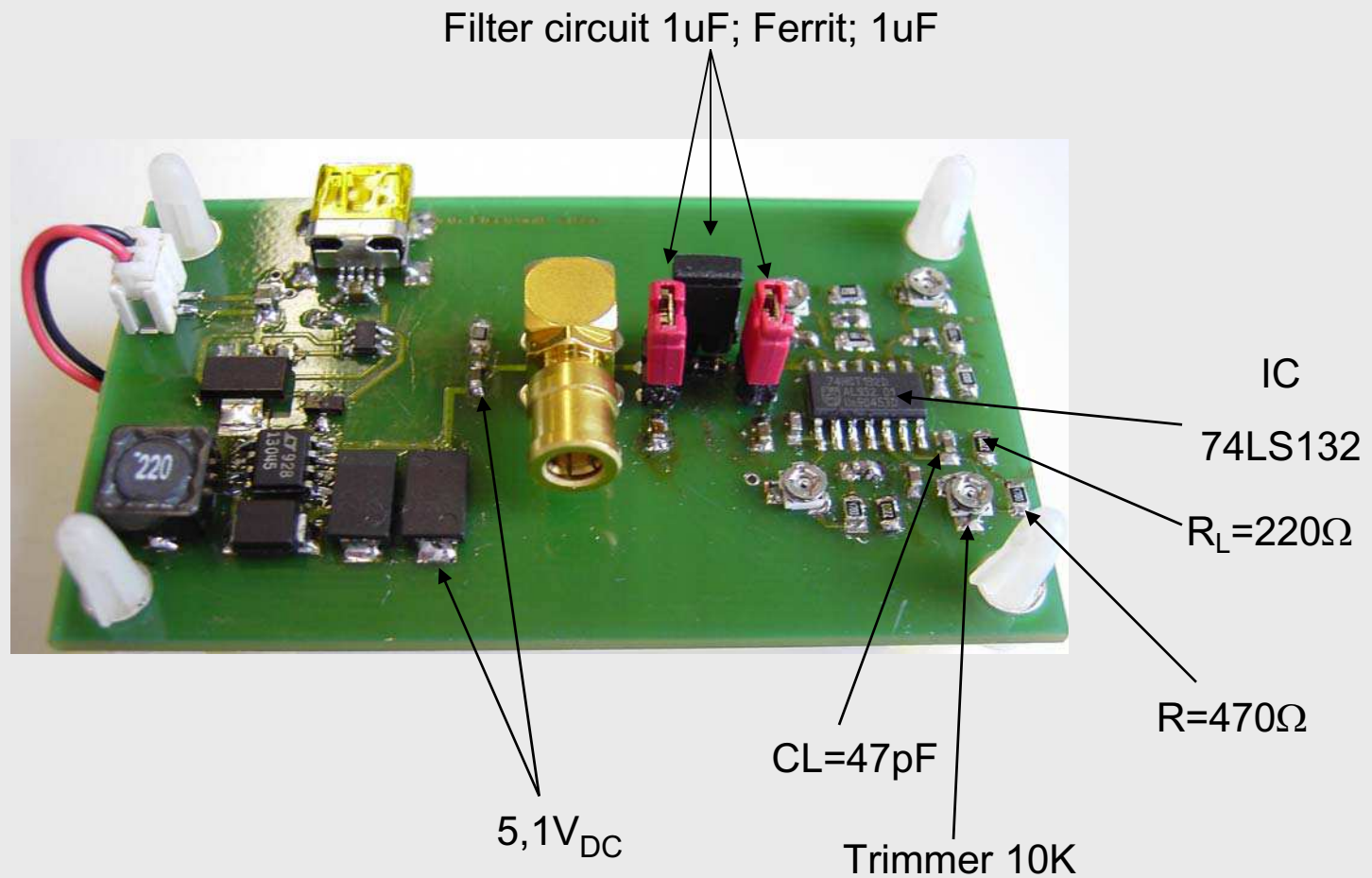


V_{CC} Decoupling Example – Discrete π -Filter




π -Filter: 1 μ F-742792093-1 μ F

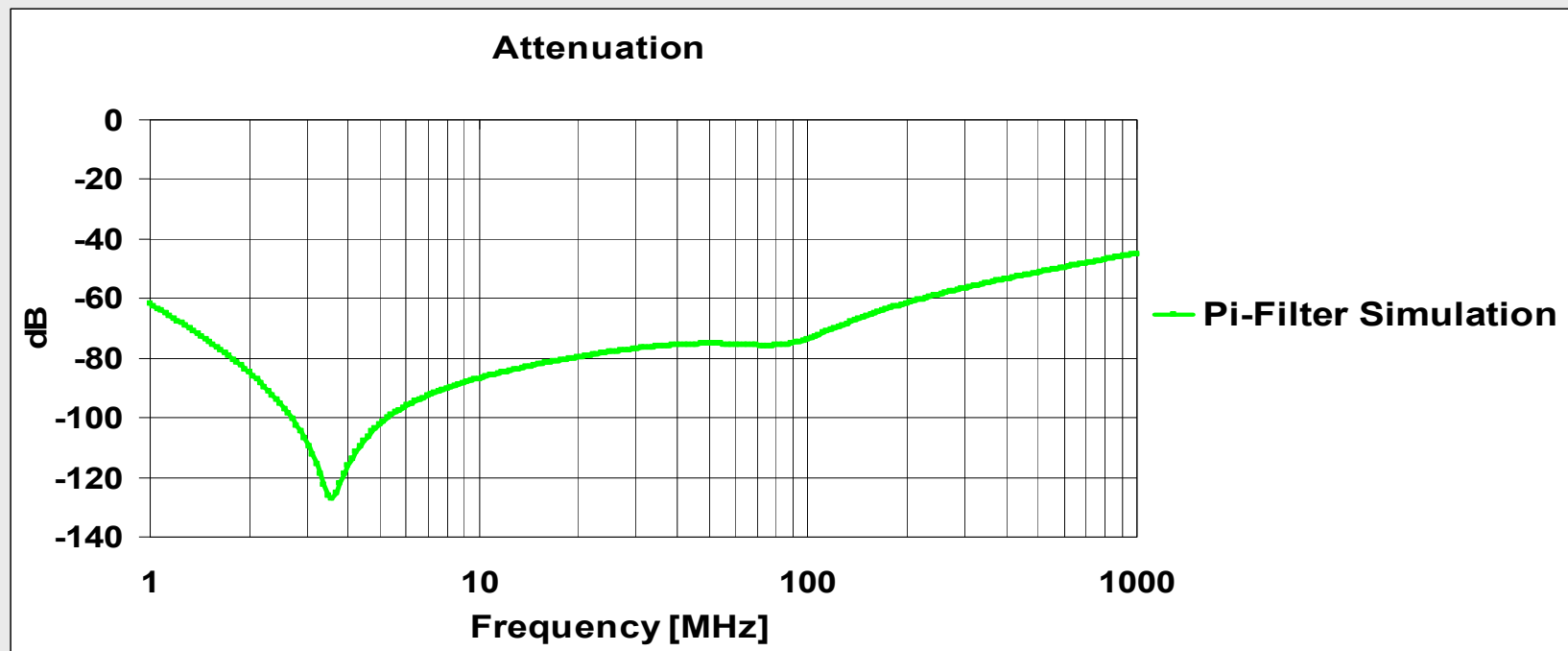

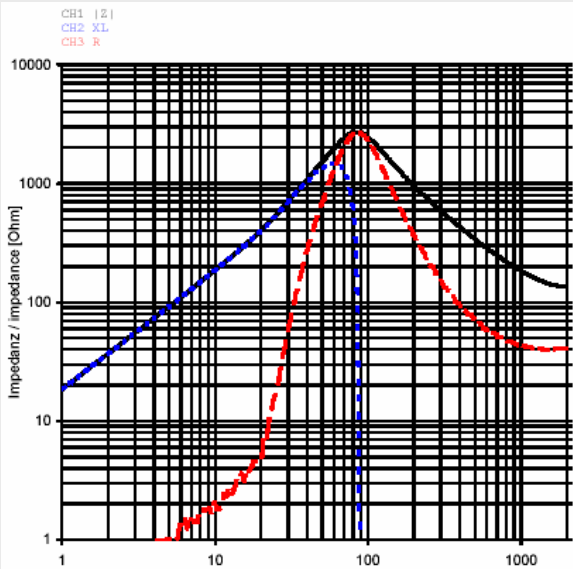V_{CC} Decoupling Example – Filter Simulation Circuit




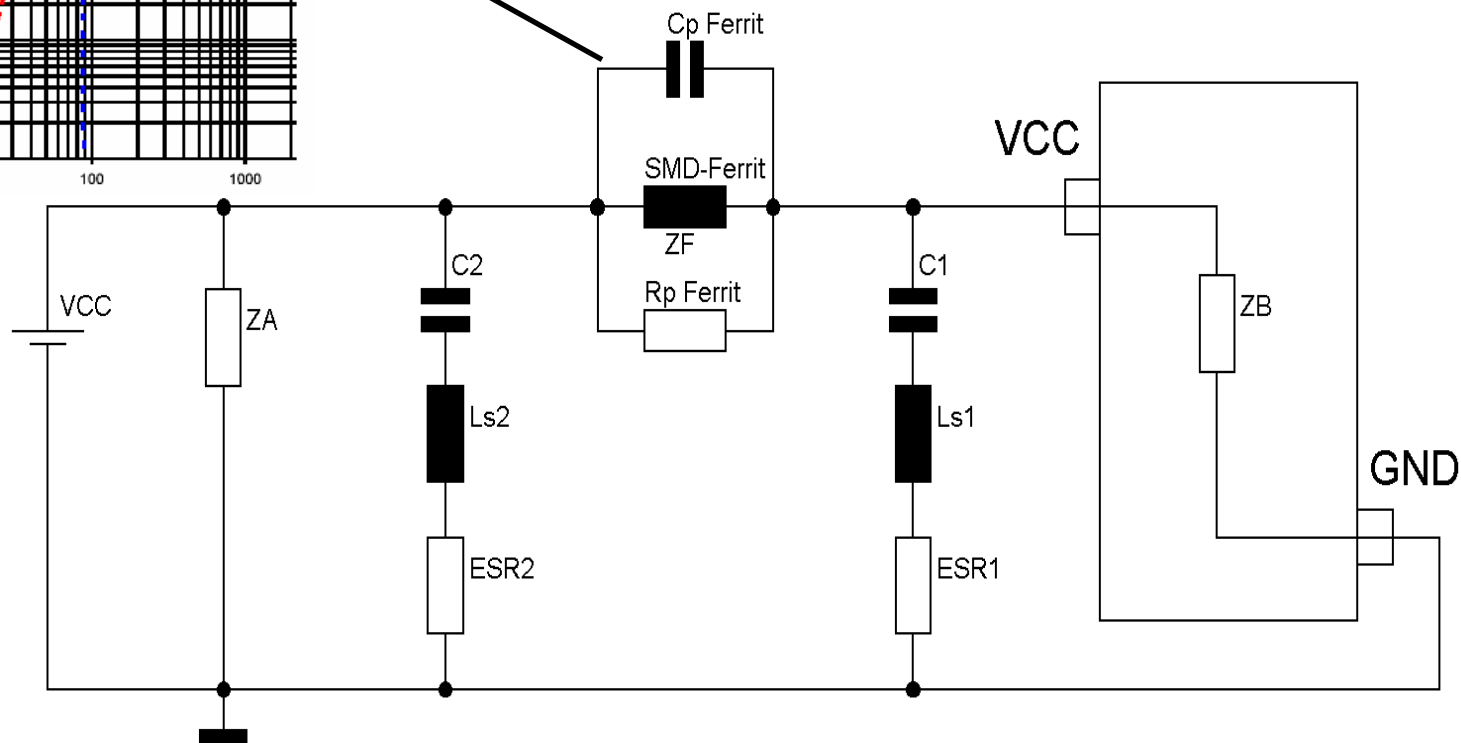Impedance Characteristic Z_{max}@100MHz
742792093



V_{CC} Decoupling Example – Noise without Filter

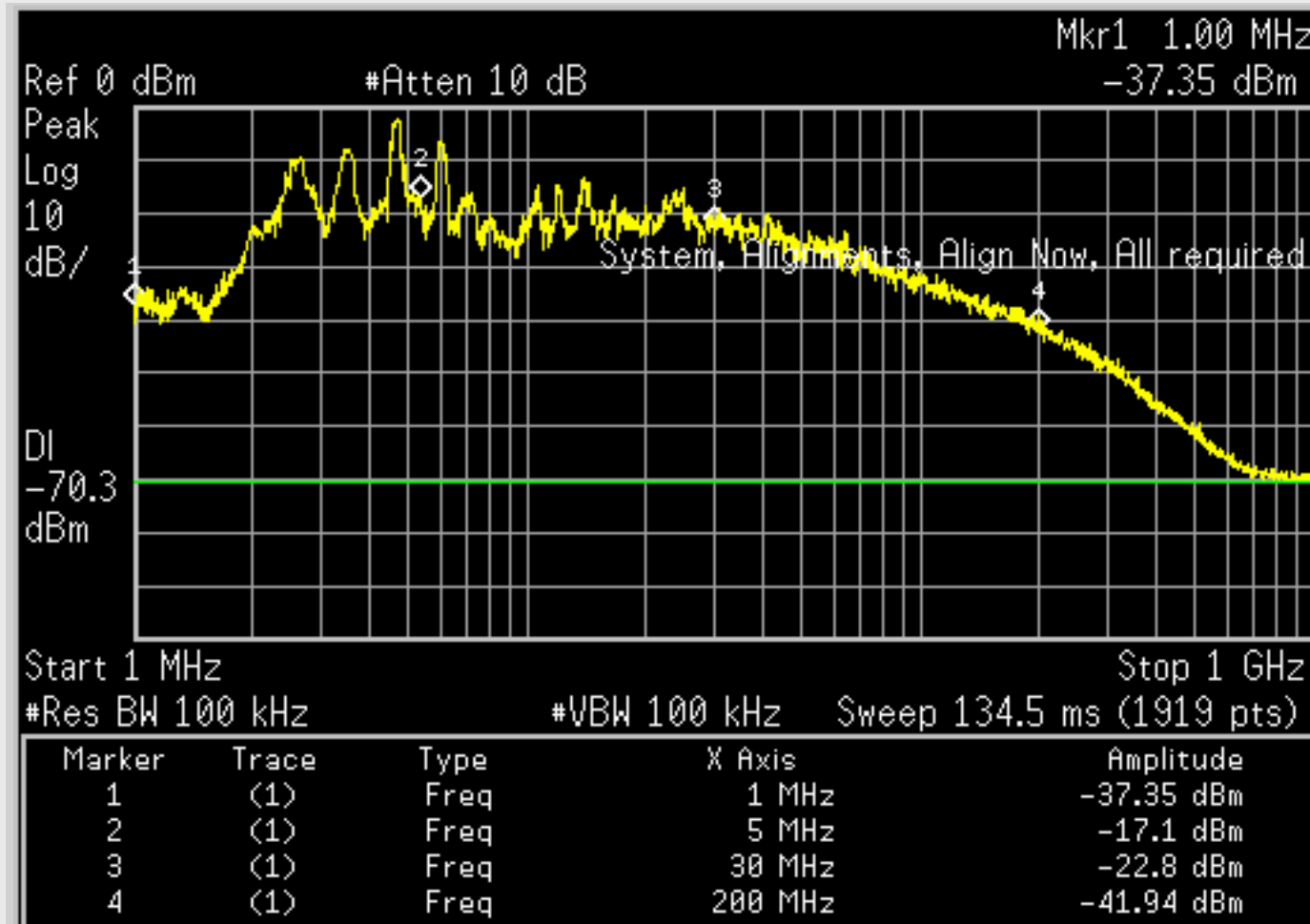no filtering on V_{CC}
(condition: max. Hold)




V_{CC} Decoupling Example – 1uF Simulation



Step 1:
1uF Cap.



C-Filter with 1uF

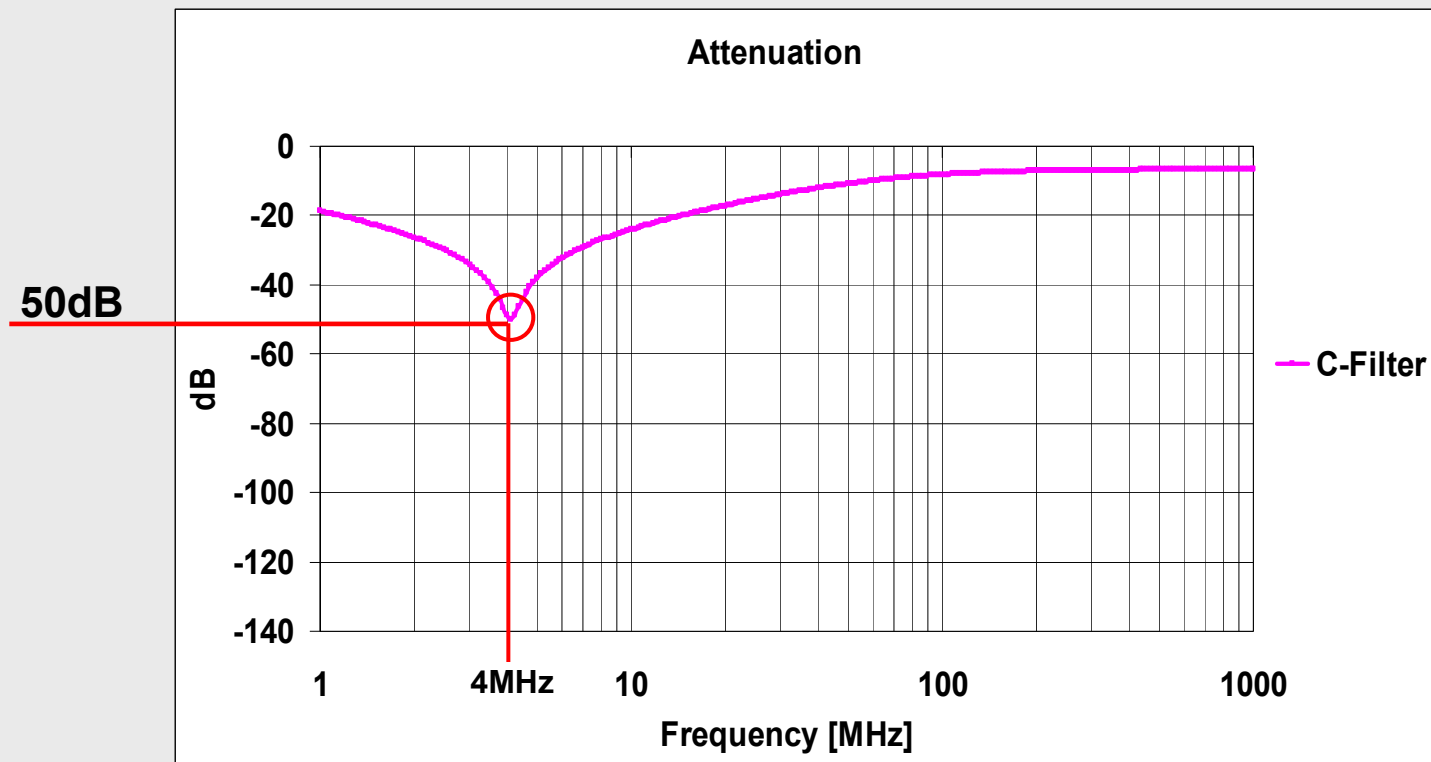

V_{CC} Decoupling Example – 1uF Results




Step 1:
1uF Cap.

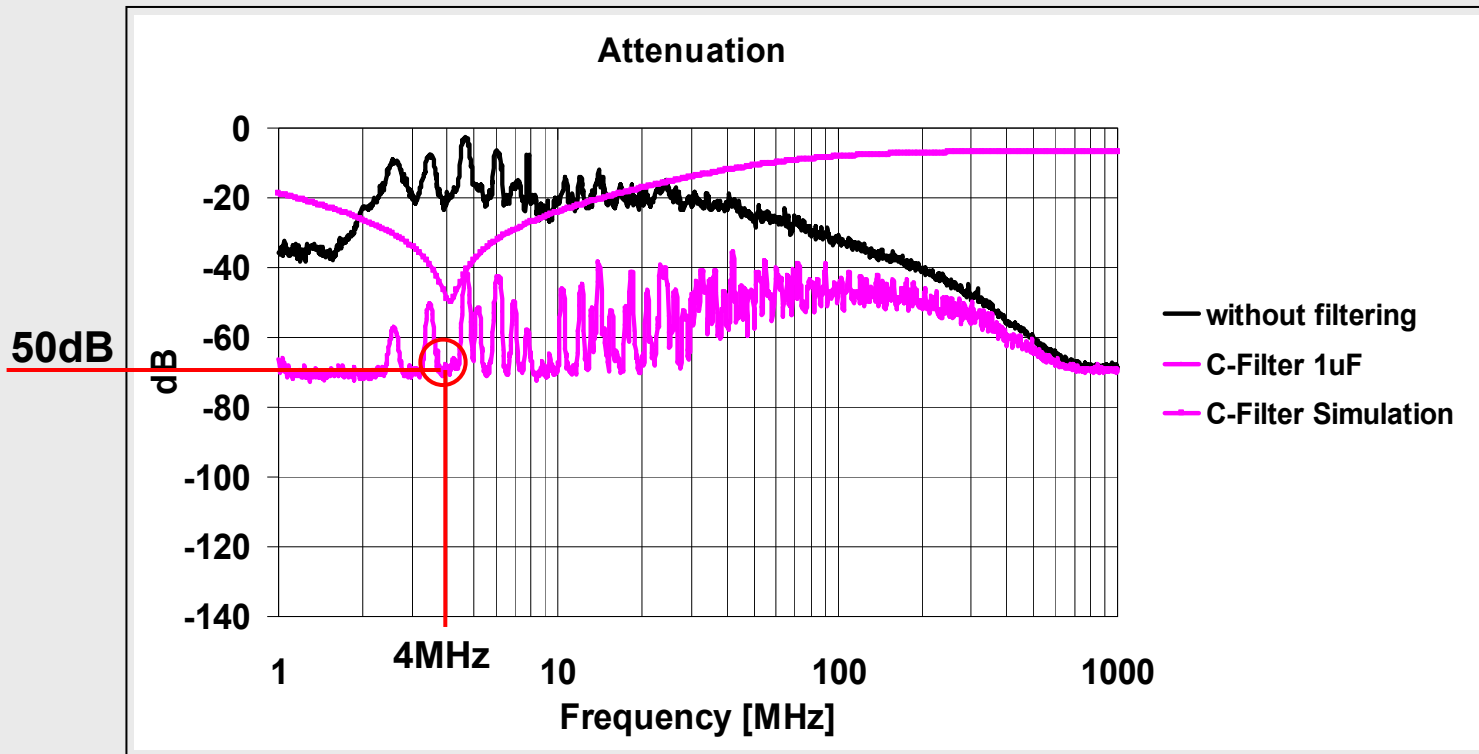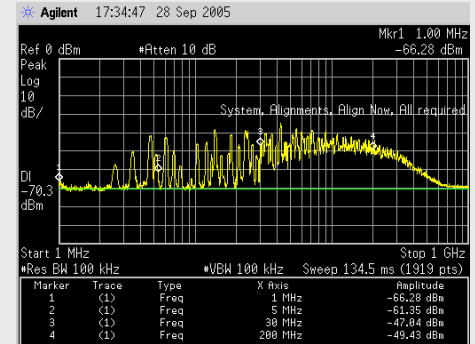

V_{CC} Decoupling Example – 1uF and Ferrite Simulation





Step 2:
1uF Cap.
& Ferrite

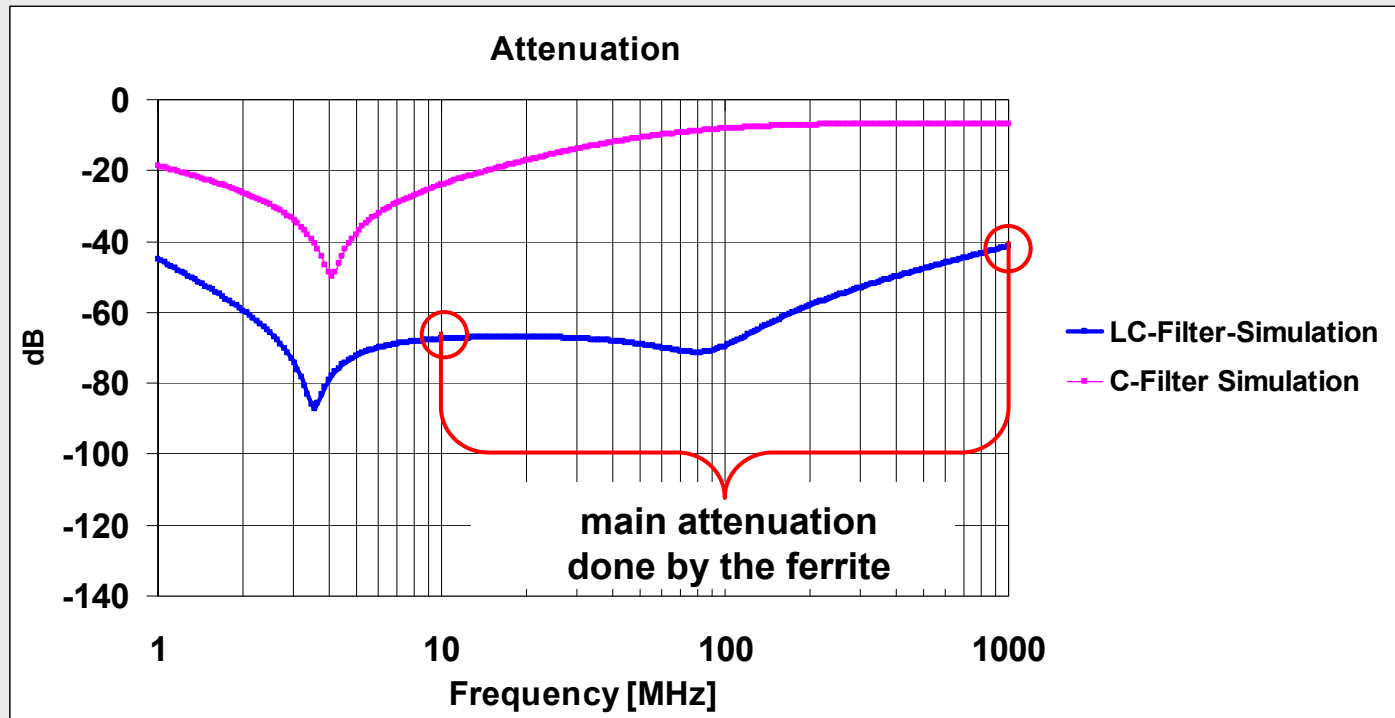

V_{CC} Decoupling Example – 1uF and Ferrite Results

Step 2:
1uF Cap.
& Ferrite

LC-Filter: 1uF-742792093

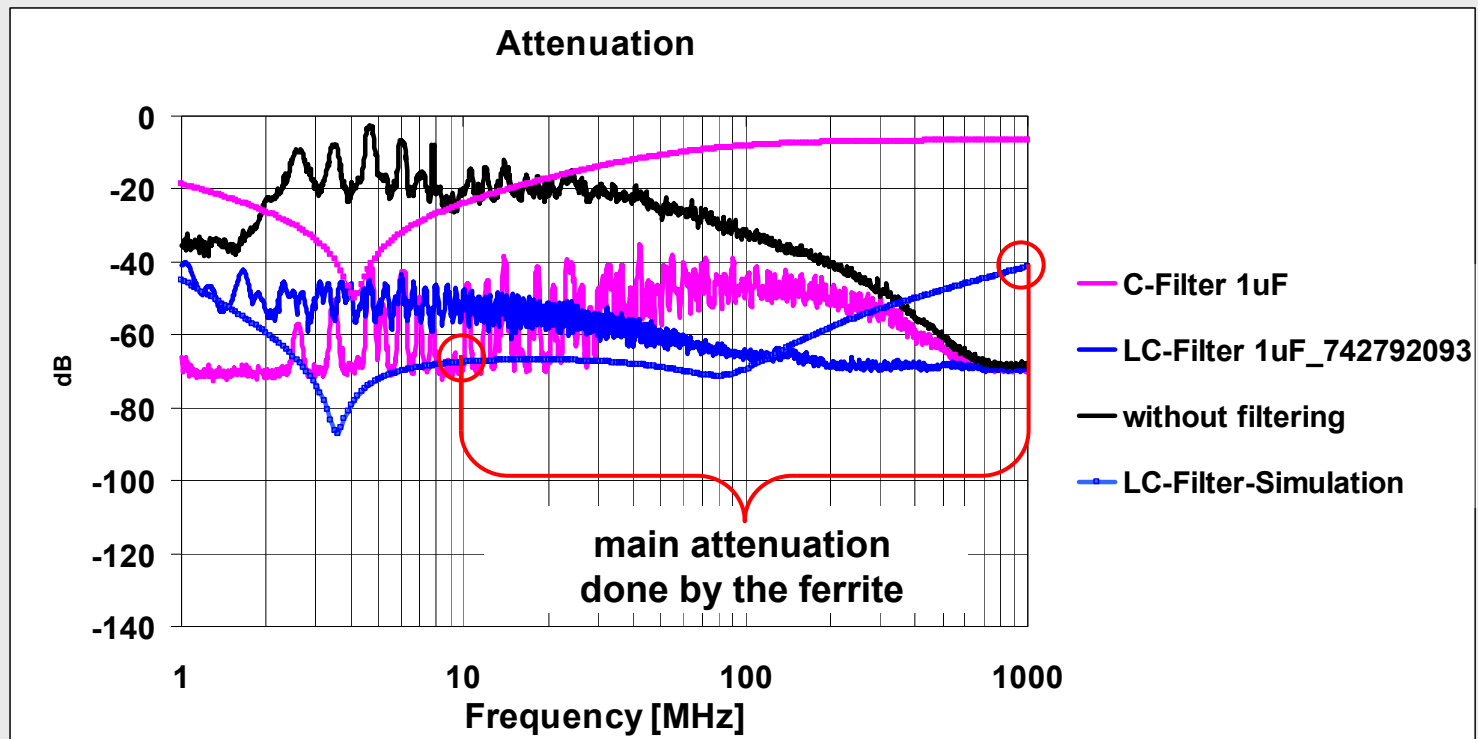
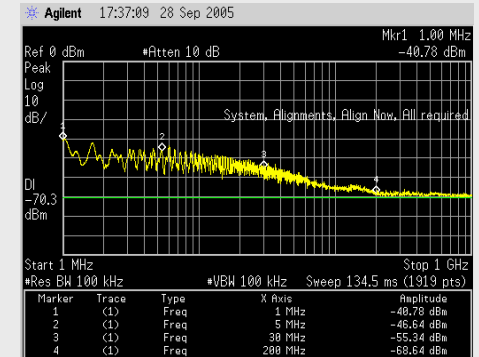


V_{CC} Decoupling Example – Pi Filter Simulation



Step 3:
1uF//1uF Cap.
& Ferrite

π -Filter: 1uF-742792093-1uF

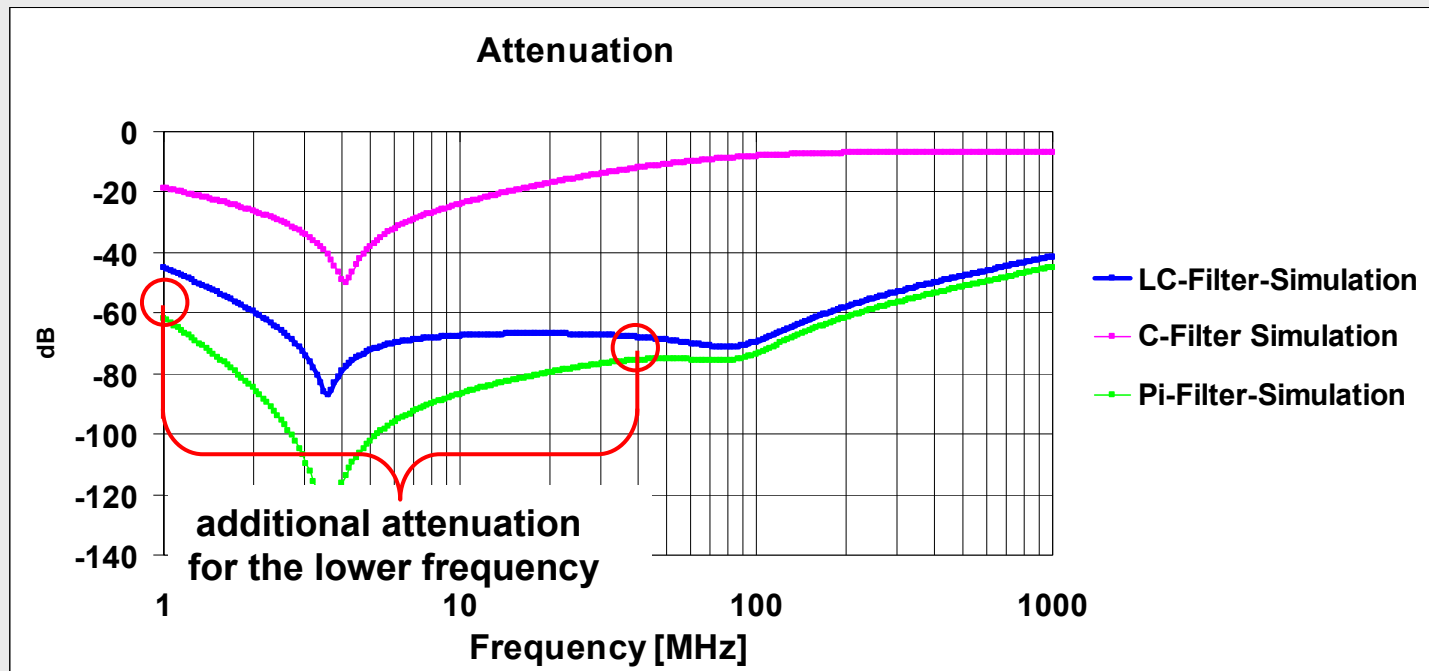
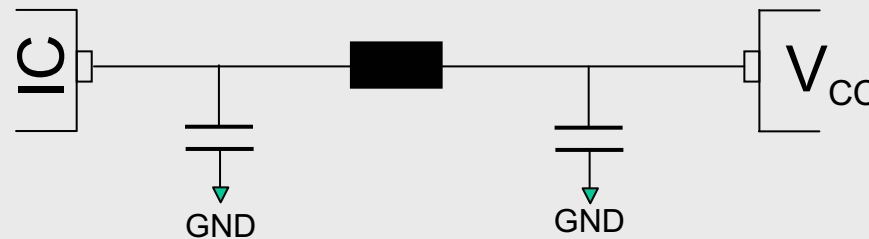


V_{CC} Decoupling Example – Pi Filter Results



Step 3:
1uF//1uF Cap.
& Ferrite

π -Filter: 1uF-742792093-1uF

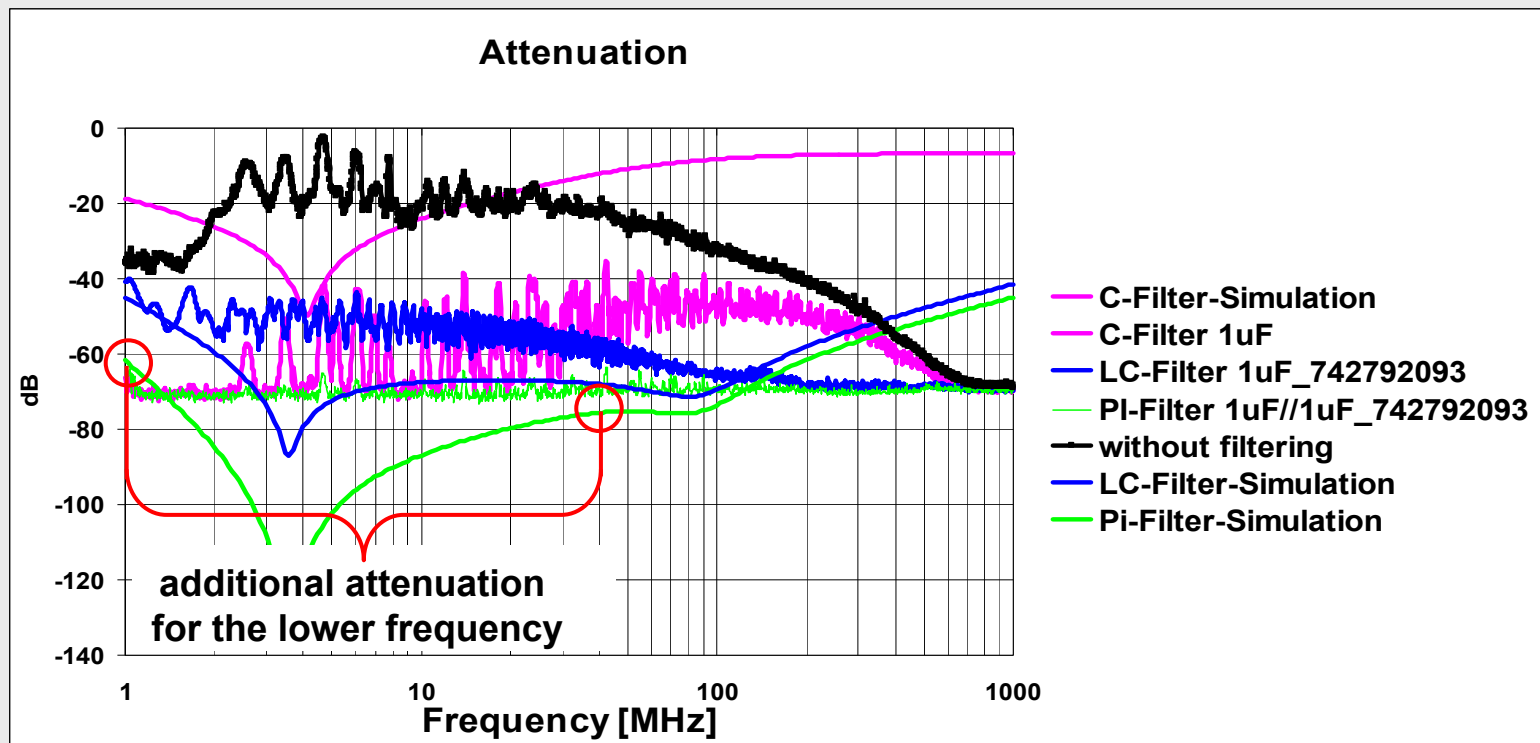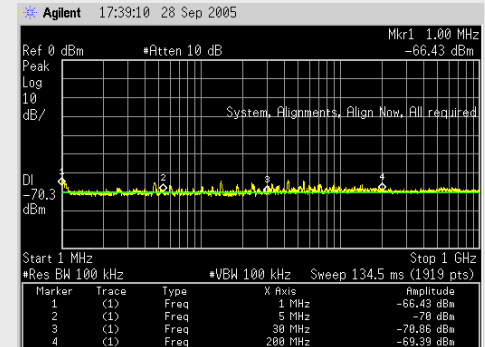





V_{CC} Decoupling Example – Final Result

π-Filter: 1uF-742792093-1uF



no filtering on Vcc

filtering on Vcc

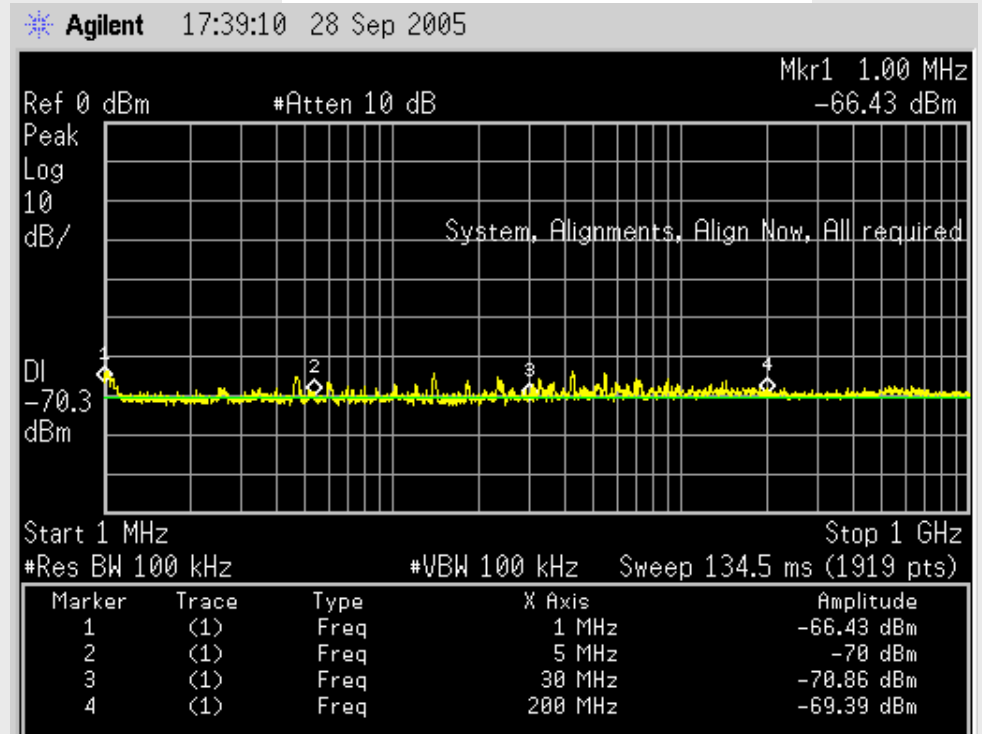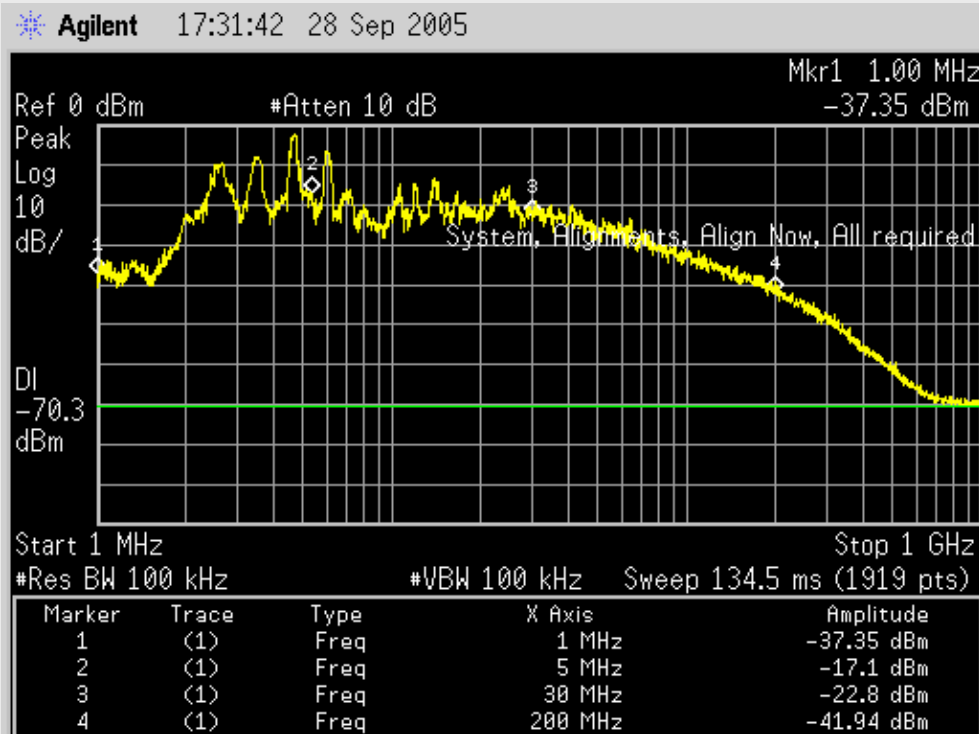


EMI: Conducted Emission w/o Filter



LT3481EMSE Demo Board
24V to 3.3V @2A
fsw=800kHz
CEM 0.15 – 30 MHz

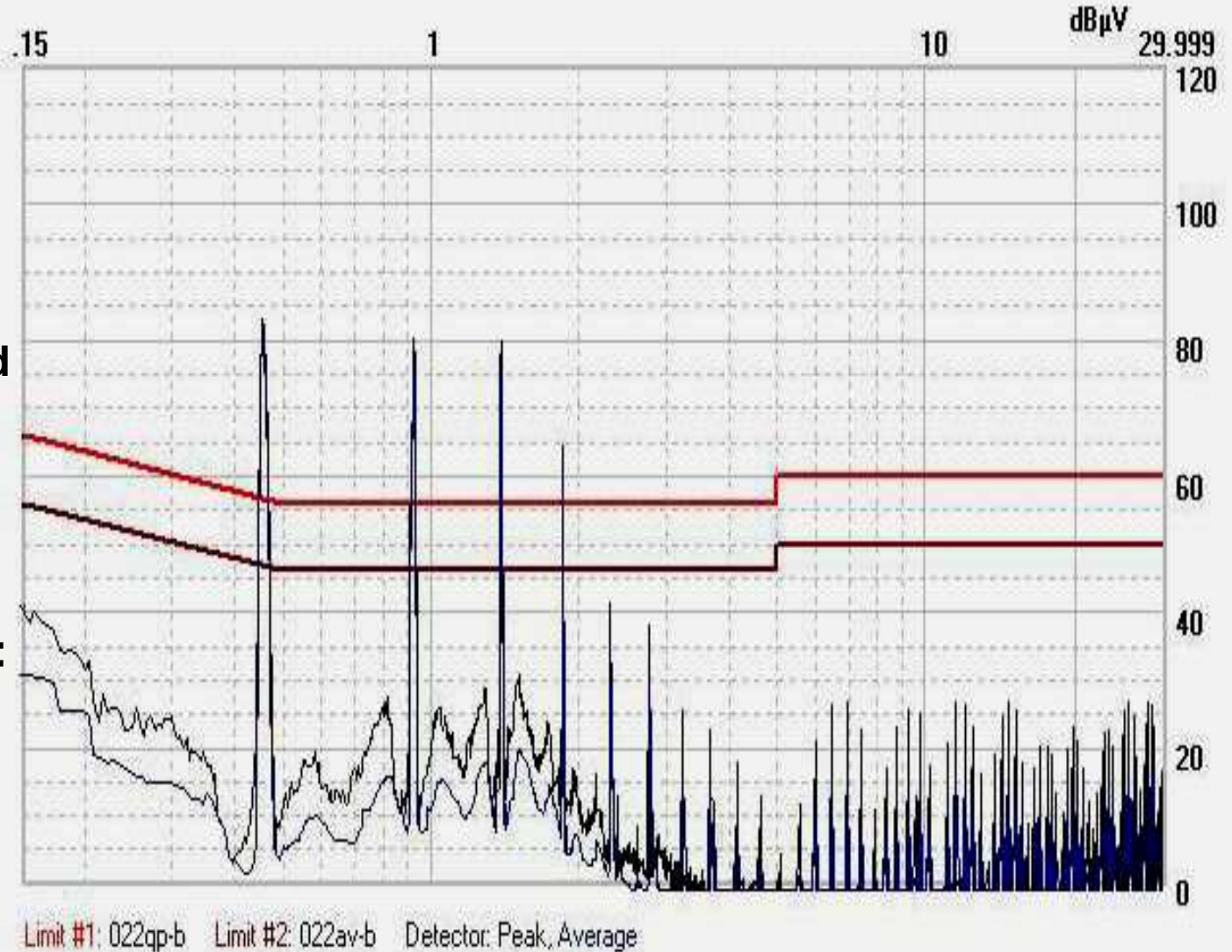
Test without EMC filter:
Peak 82dB μ V
→ 26dB above limit



EMI: Conducted Emission with Filter

Ferrite bead


High ESR Elco
to damp cable

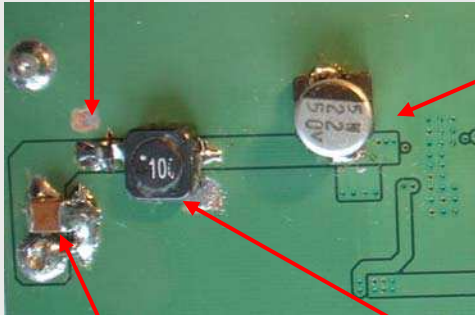

Test with additional $L=10\mu\text{H}$,
 $C=3.3\mu\text{F}$ 50V 1210 input filter

Peak=42dB $\mu\text{V}/\text{m}$
 $\emptyset=32\text{dB}\mu\text{V}/\text{m}$

Peak & \emptyset 14dB below limit

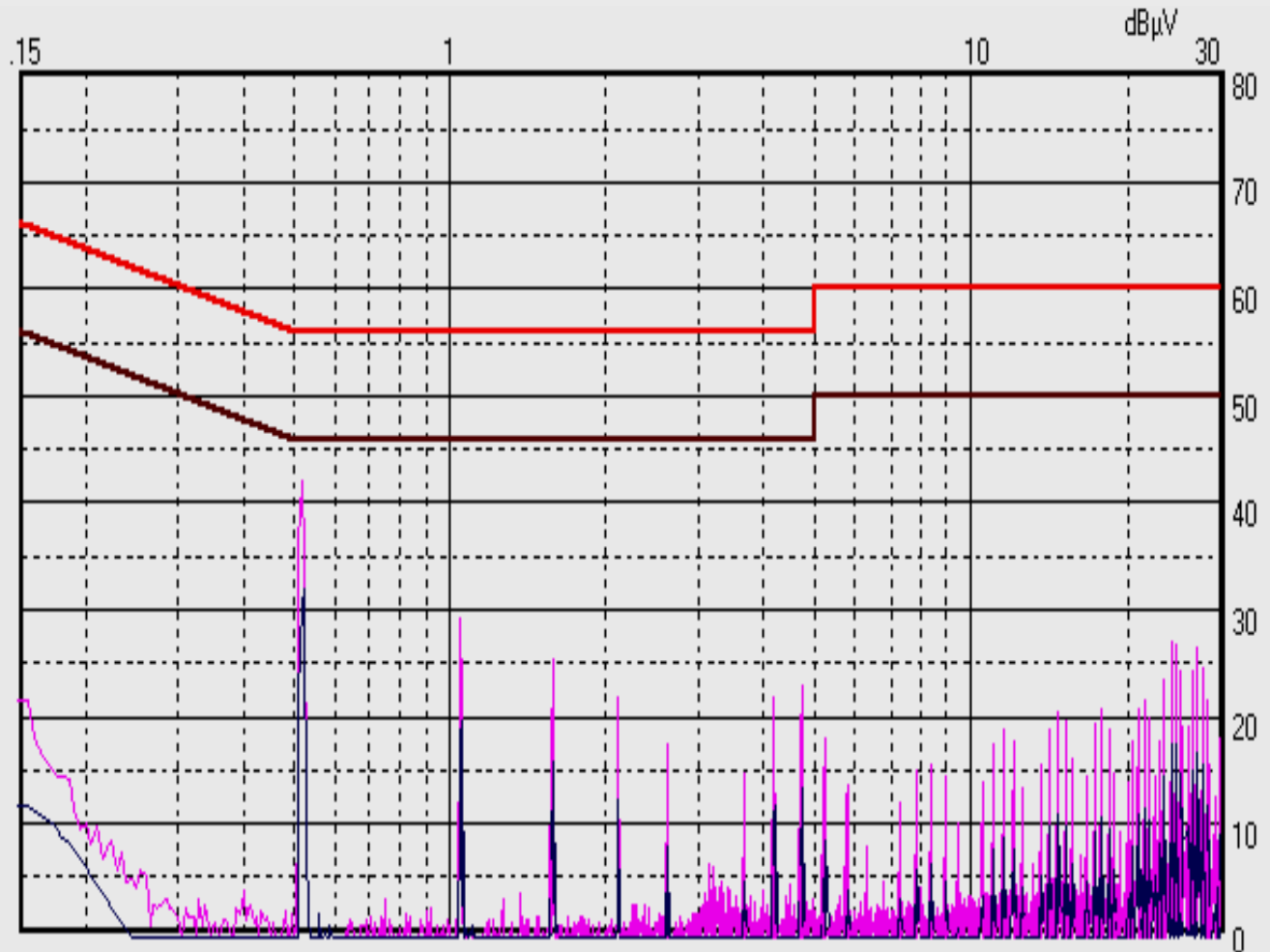


EMI: Conducted Emission Measurement




1. Coupling mode
2. Attenuation
- 3. Emissions**
4. Transformers

- Power supply V 1.0

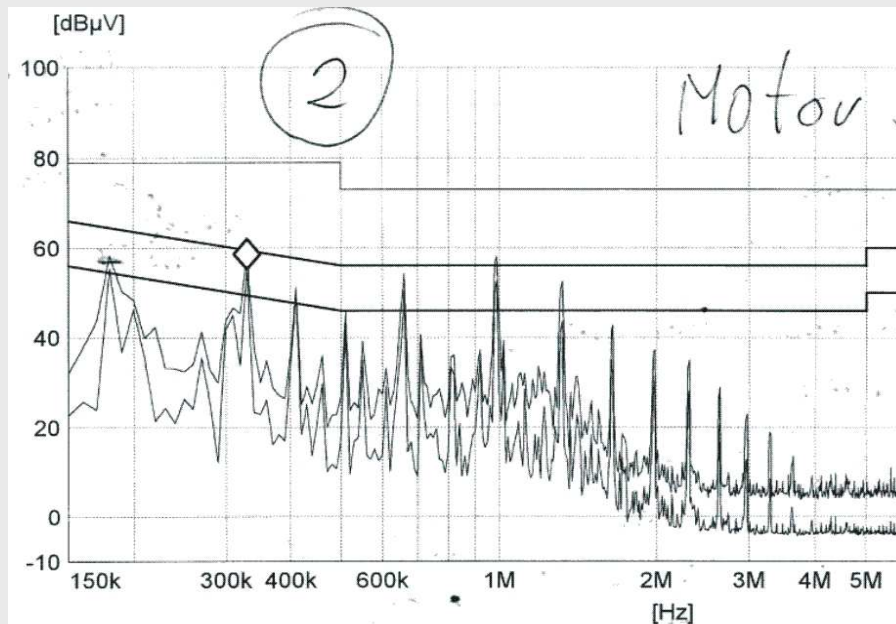

PCB


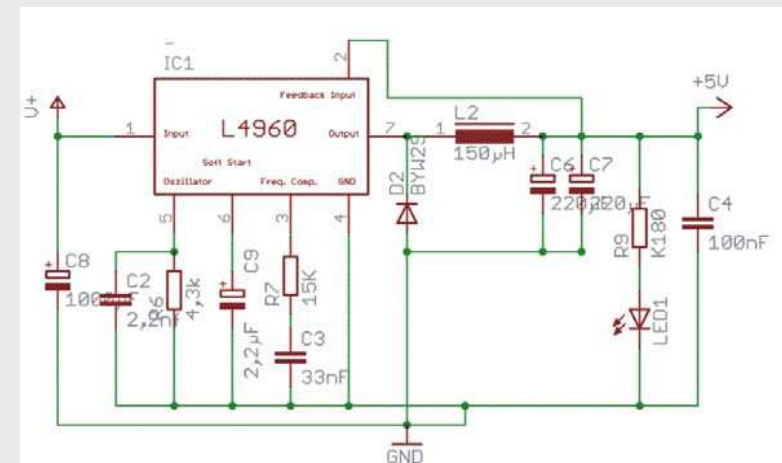


Buck Converter ST L4960/2.5A/fs 85-115KHz


EMI: Conducted Emission Measurement

- 1. Coupling mode
- 2. Attenuation
- 3. Emissions**
- 4. Transformers

- Power supply V 1.1

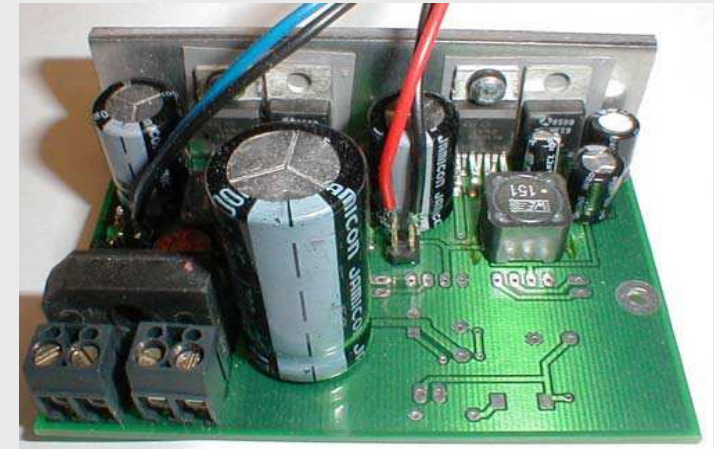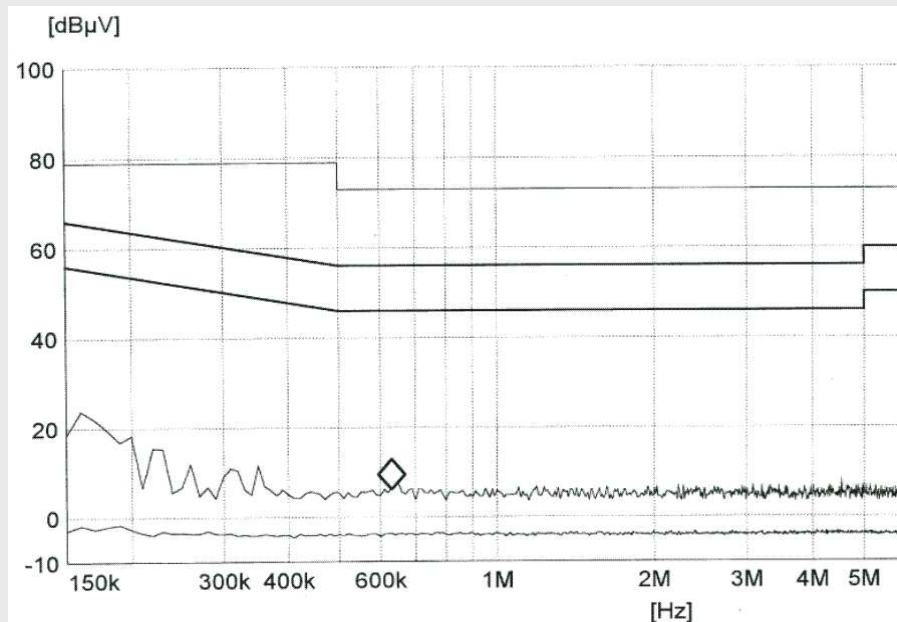

PCB

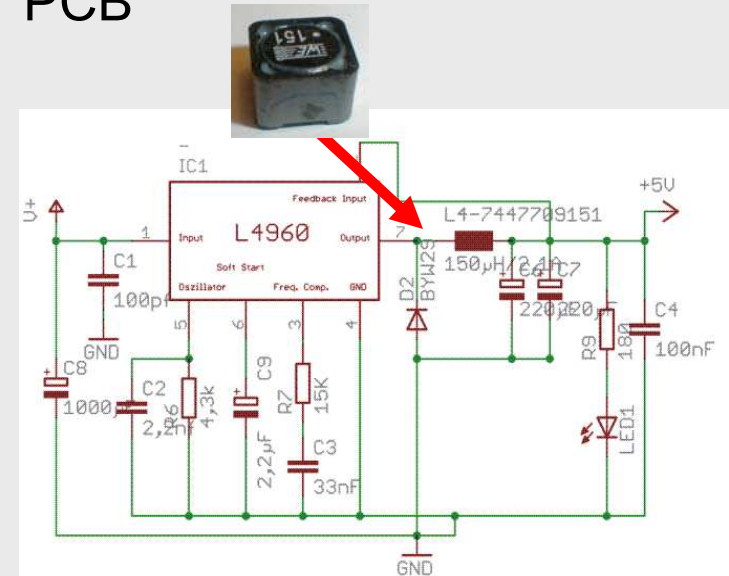

Schematic

EMI: Be Aware:



1. Coupling mode

2. Attenuation

3. Emissions


4. Transformers

- **Select the right parts for your application**
- **Do not always look on cost**

Very easy solution with a dramatic result!!!



Choke before


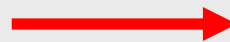


Choke after






or

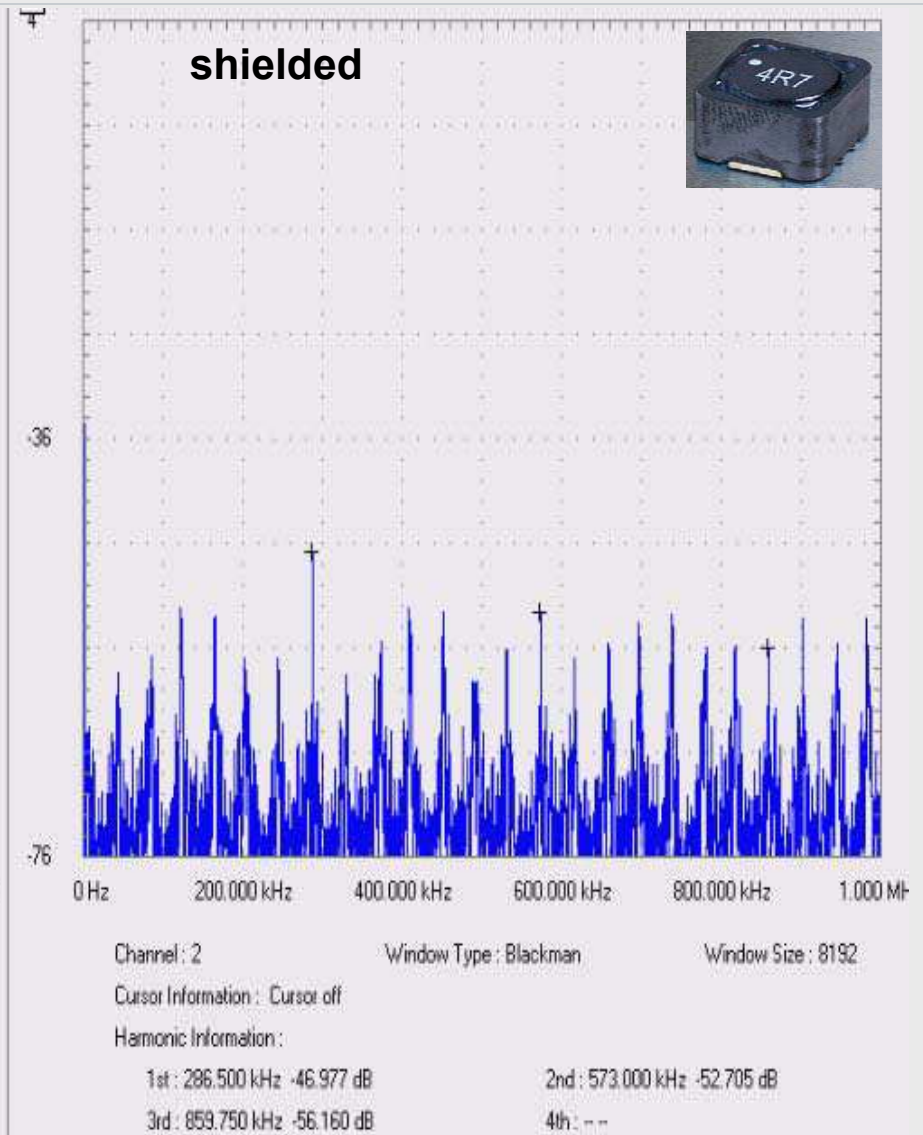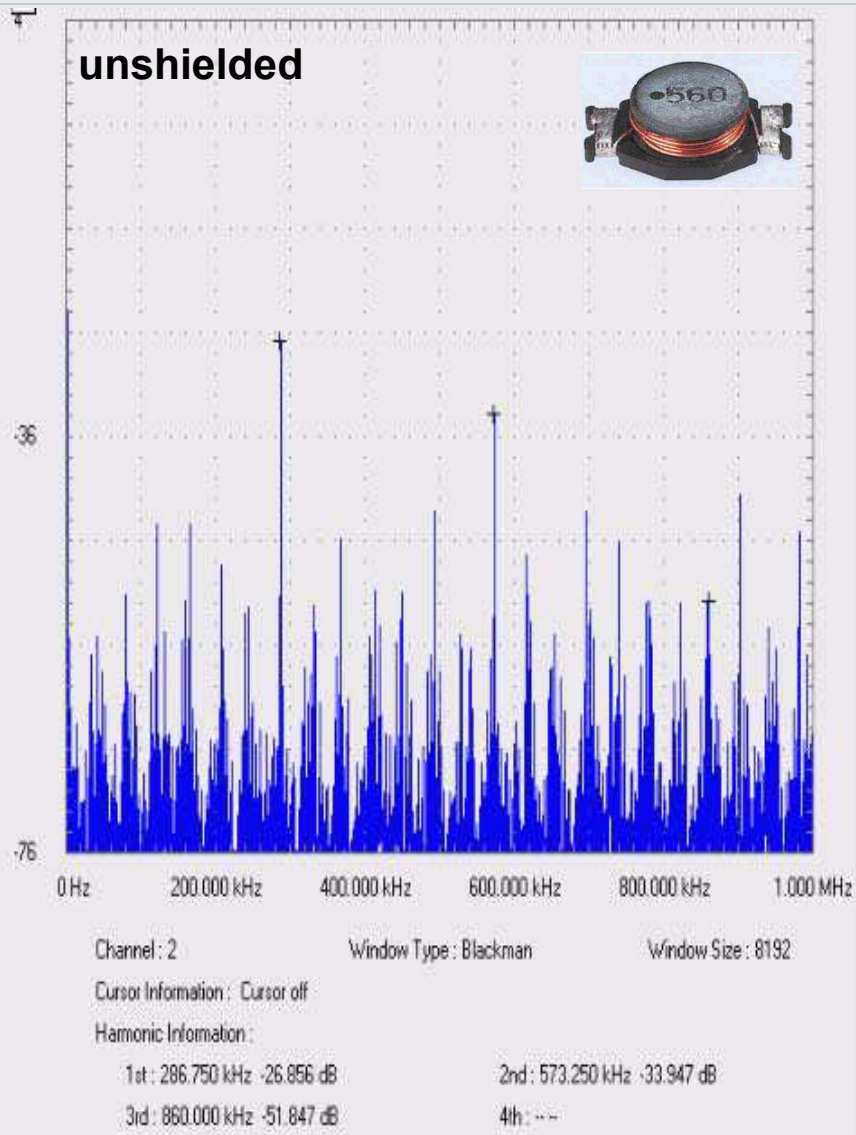EMI: Shielded vs. Unshielded Power Inductor





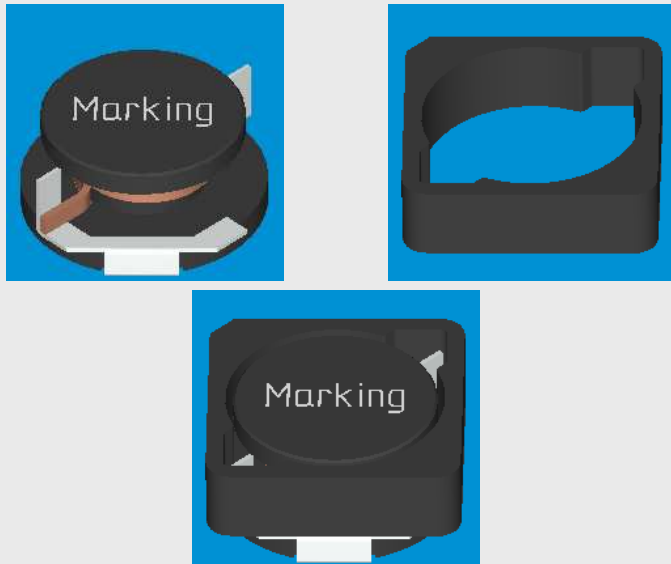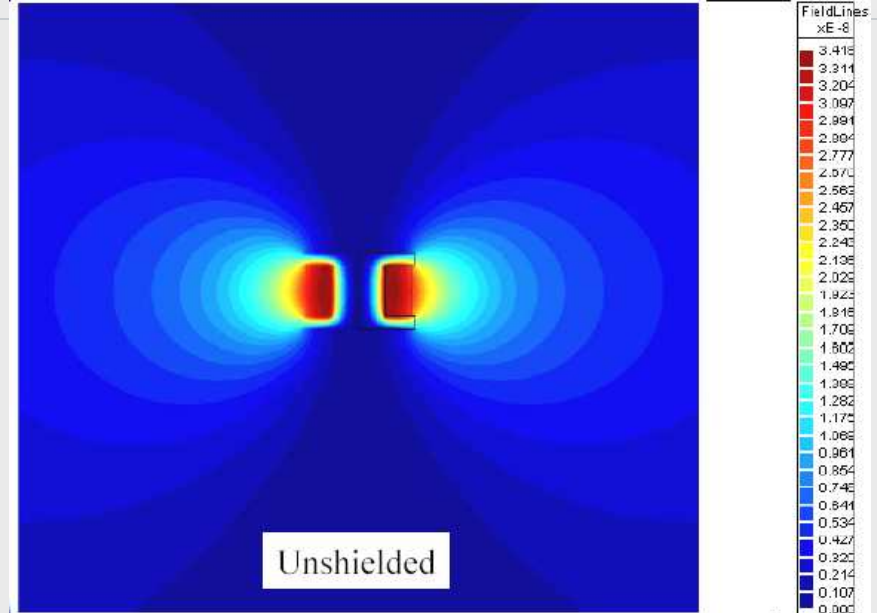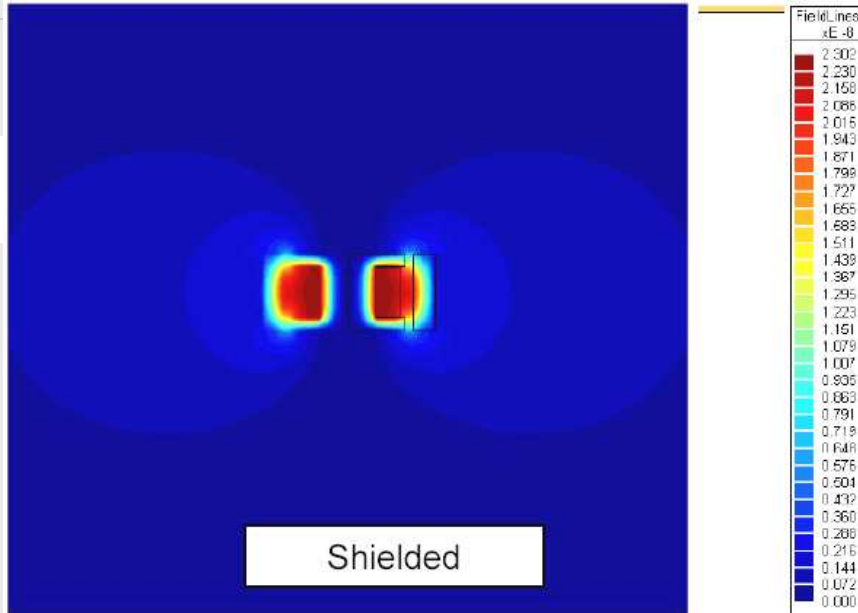
EMI: Shielded vs. Unshielded Power Inductor



EMI: Shielded vs. Unshielded Power Inductor




- Magnetic field

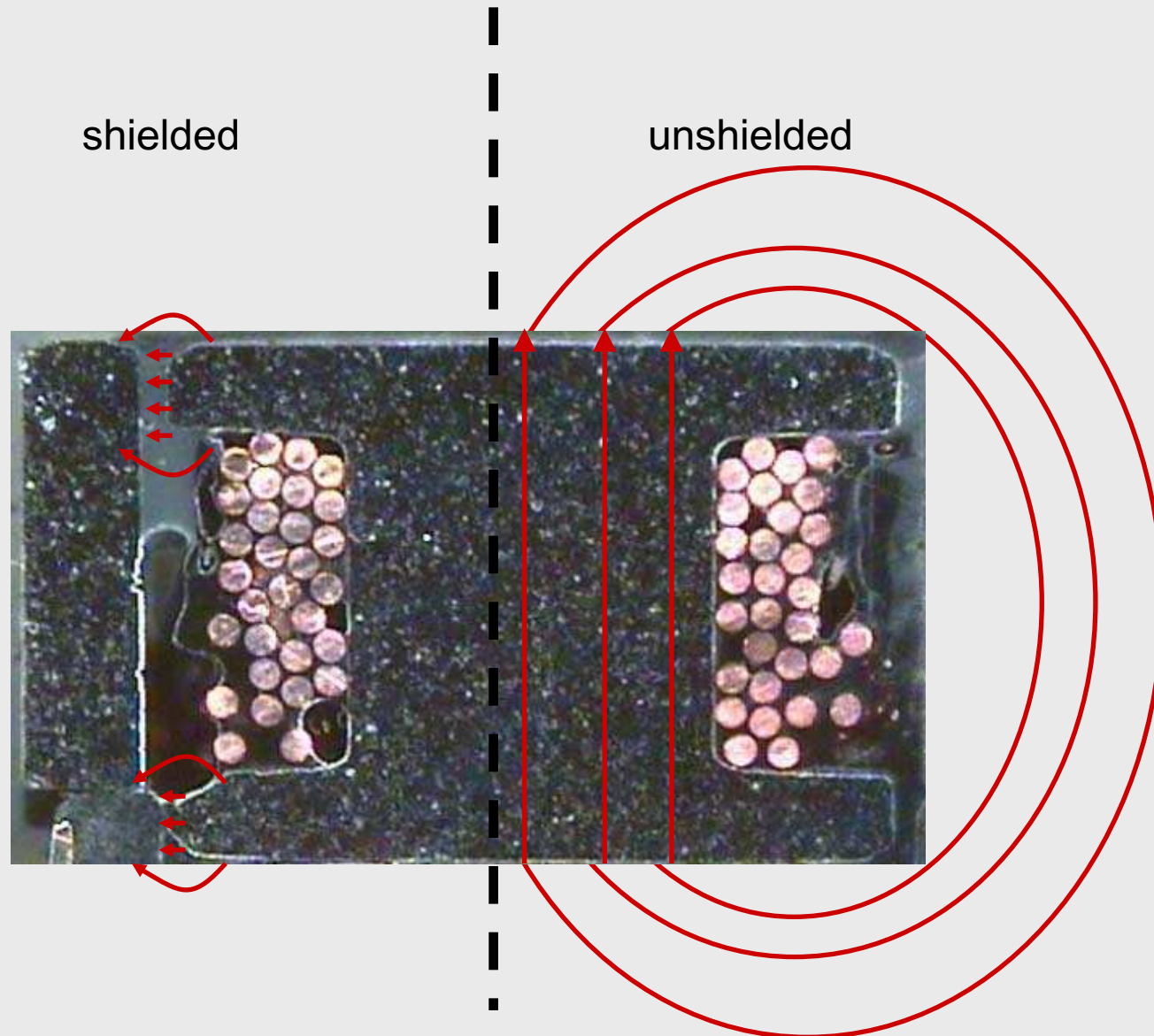


Conducted Emissions Example – Test and Compare

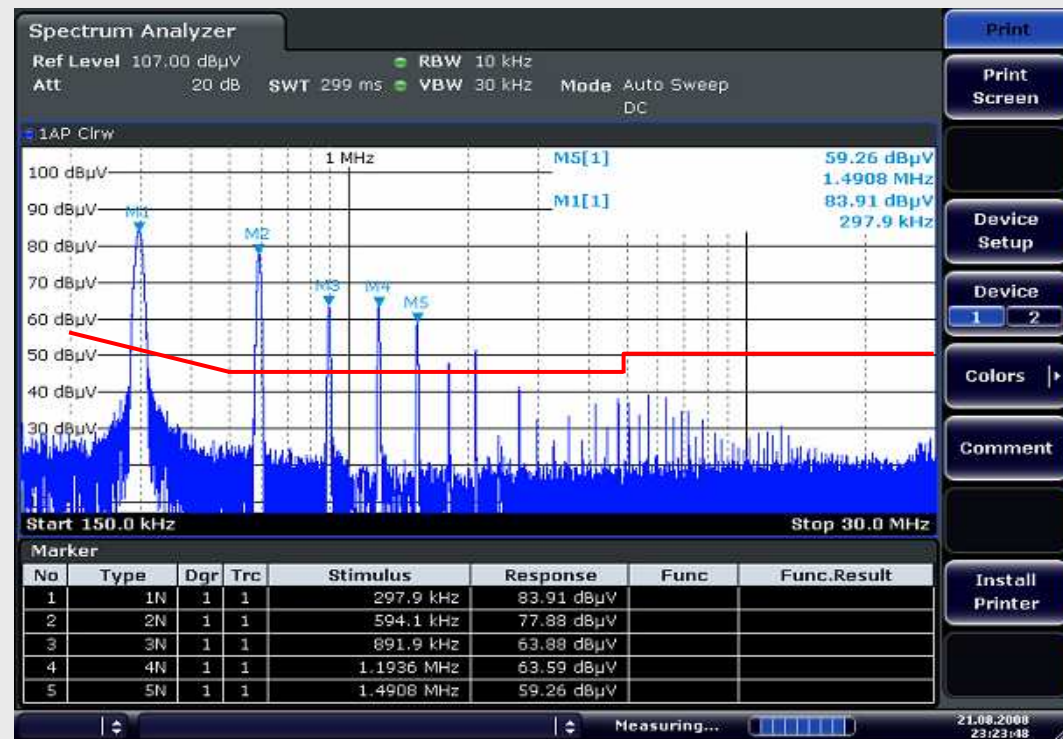- Differential Choke
- Bifilar Wound Common Mode Choke
- Sector Wound Common Mode Choke
- Chip Bead




Conducted Emissions Example - Test Setup

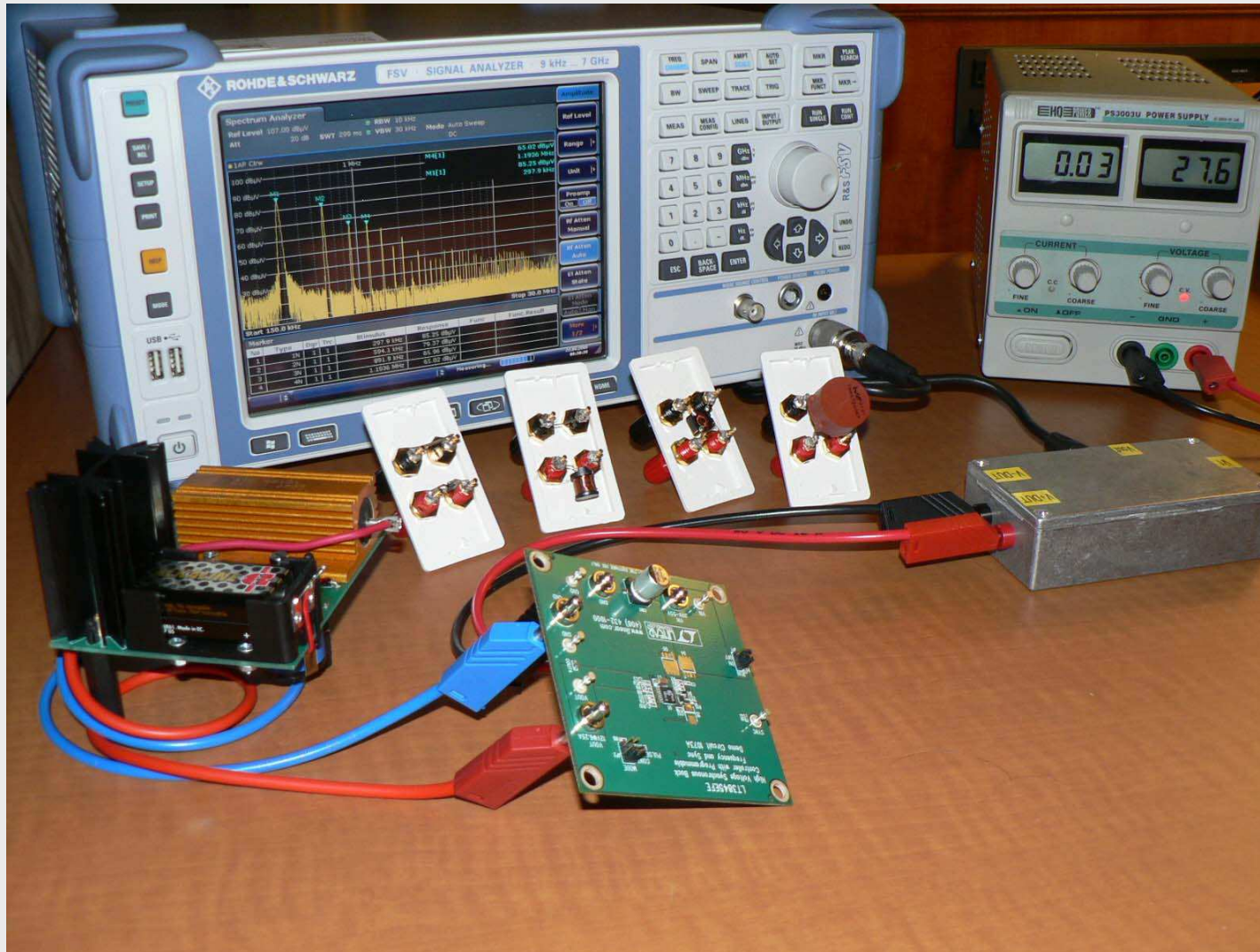

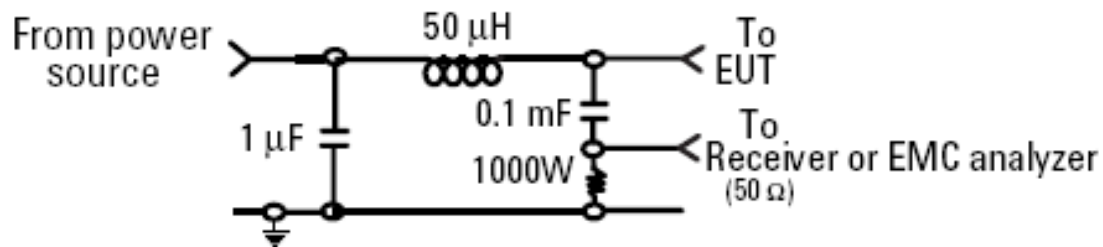- a) no load
 - b) 1.5A load
- 150KHz fsw.

Conducted Emissions Example - LISN

Line Impedance Stabilization Network (LISN)



- Isolates DUT from Power Source (typically mains) Noise
- Provide characteristic Impedance to DUT (50ohms in this case)
- Path for Conducted noise from DUT to Spectrum Analyser




The 1 μF in combination with the 50 μH inductor is the filter that isolates the mains from the EUT. The 50 μH inductor isolates the noise generated by the EUT from the mains. The 0.1 μF couples the noise generated by the EUT to the EMC analyzer or receiver. At frequencies above 150 kHz, the EUT signals are presented with a 50- Ω impedance.

Conducted Emissions Example – Demo Board



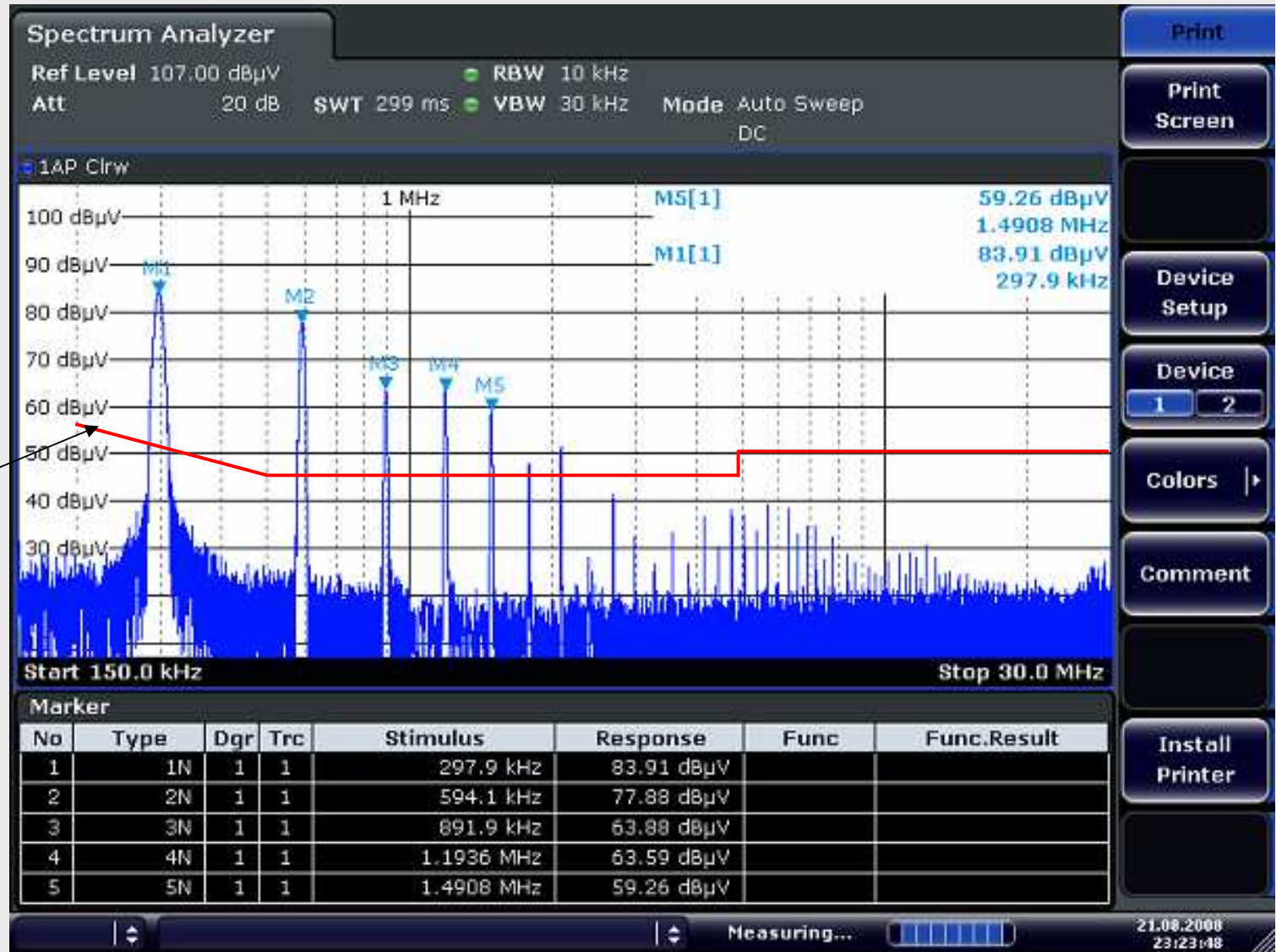- 1. Coupling mode
- 2. Attenuation
- 3. Emissions**
- 4. Transformers



FCC Class B limit

Conducted Emissions Example – Electrical Load




1. Coupling mode

2. Attenuation

3. Emissions

4. Transformers

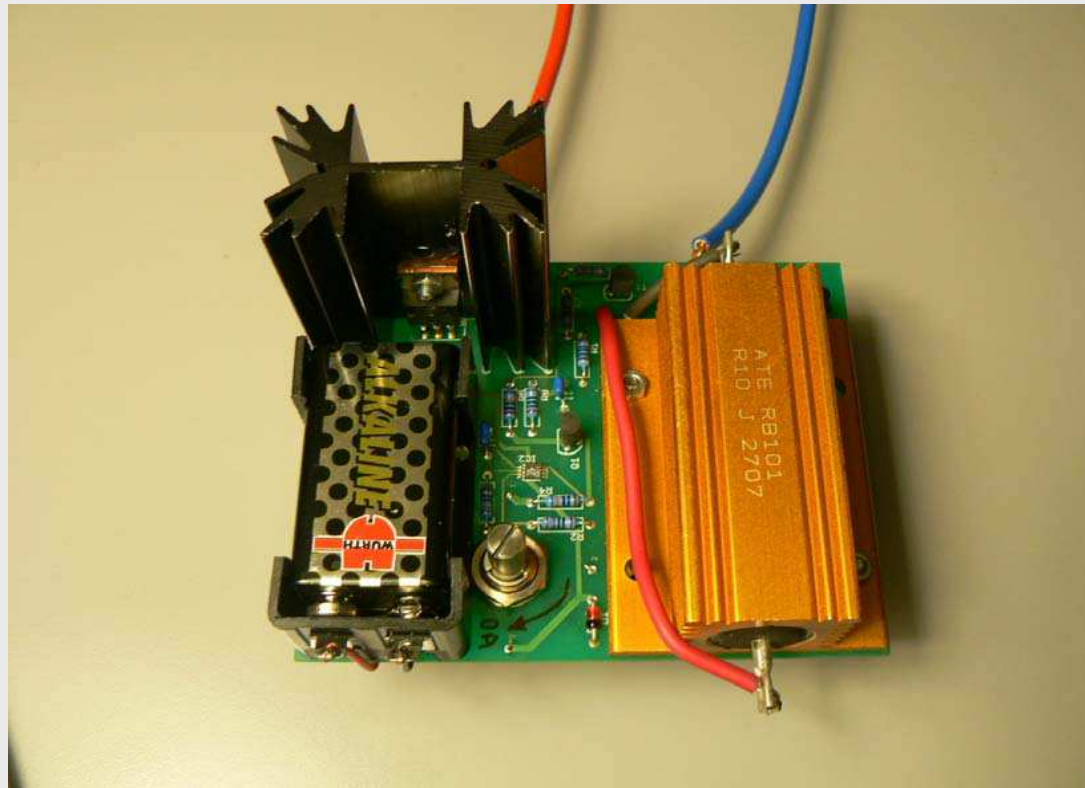


Conducted Emissions Example – Test Board



- DC/DC Converter
- Input Voltage 20V-25V
- Output Voltage 12V/6.25A
- Fsw: 150KHz

Testcondition:


- no load
- max. load 1.5A

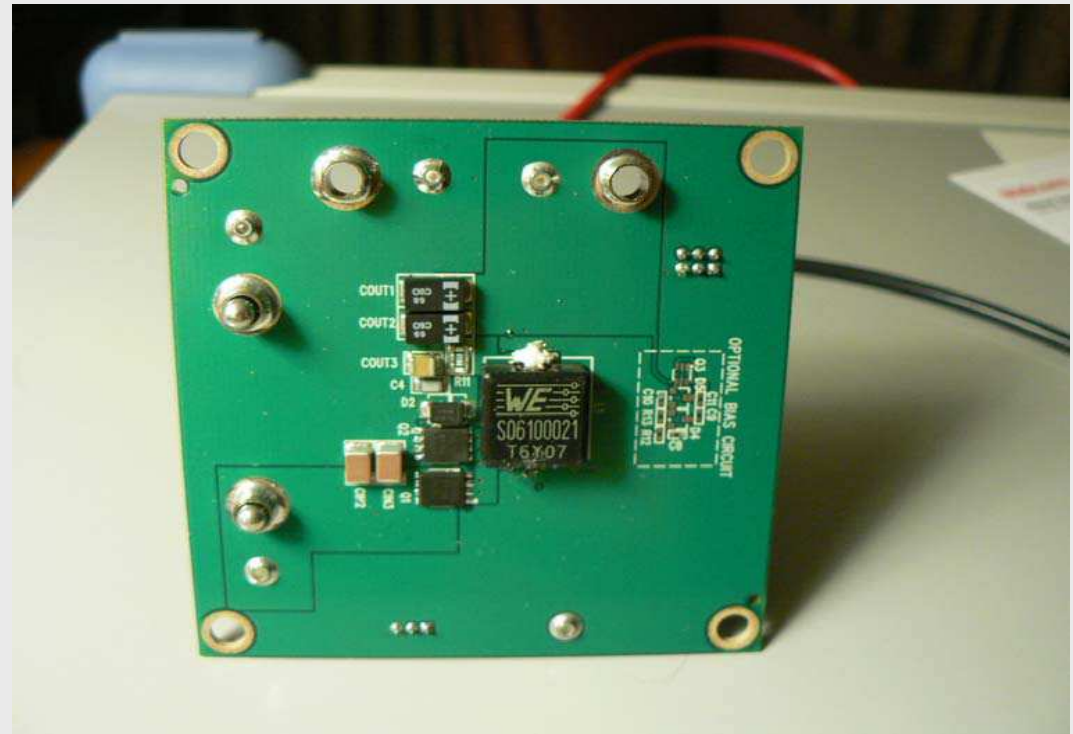

Conducted Emissions Example – No Filter



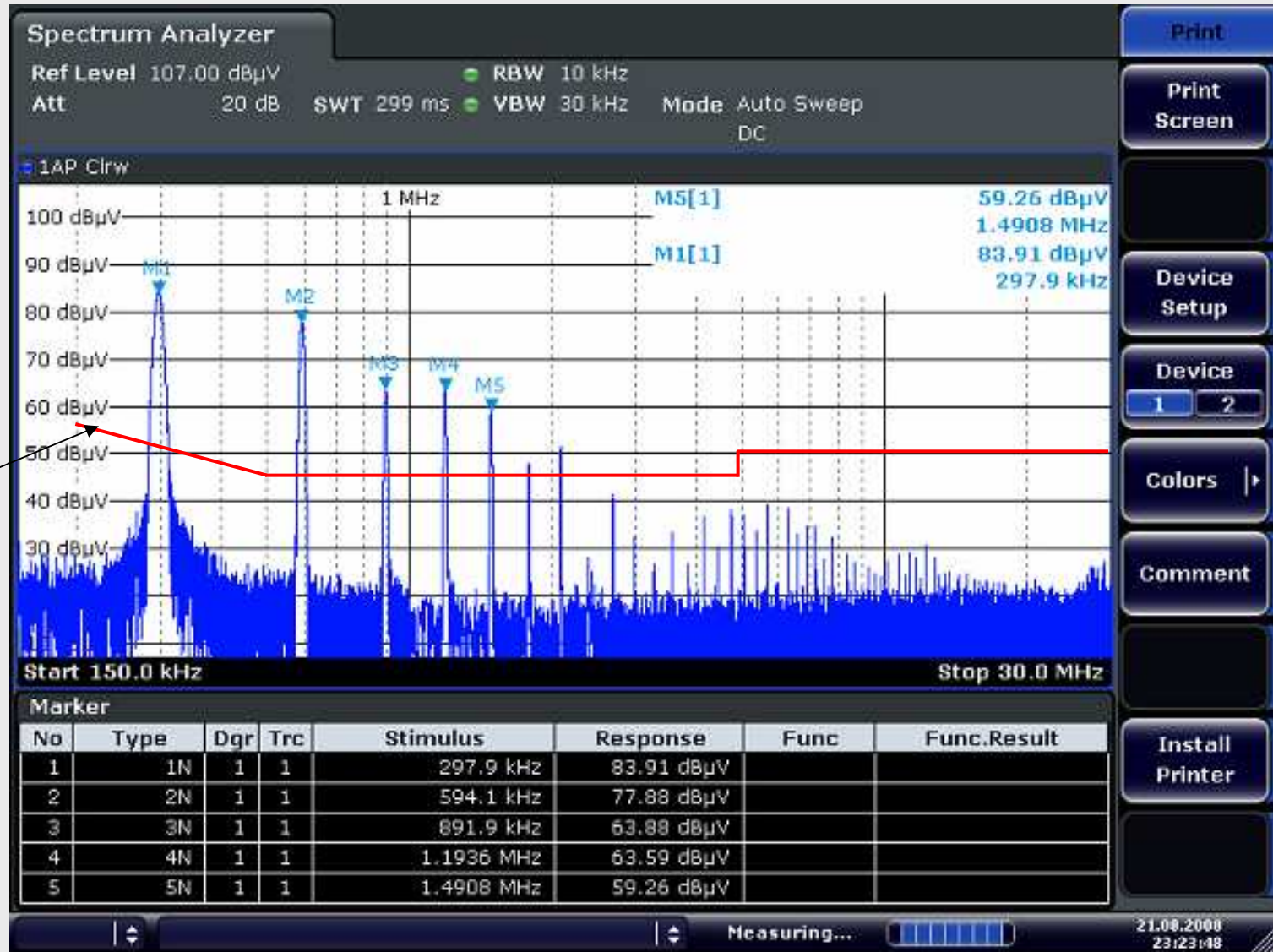1. Coupling mode
2. Attenuation
- 3. Emissions**
4. Transformers



FCC Class B limit

Conducted Emissions Example – Differential Choke



1. Coupling mode

2. Attenuation

3. Emissions

4. Transformers





Differential Line Choke 220uH




Conducted Emissions Example – Differential Choke Results

no load >

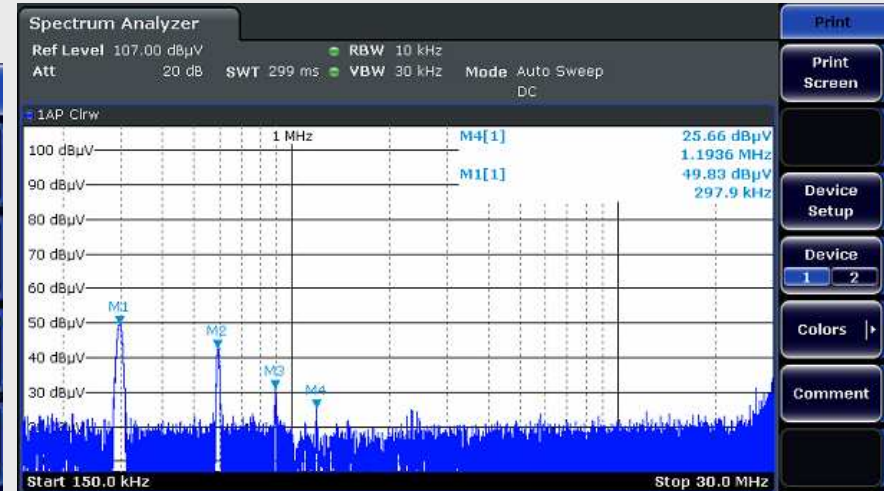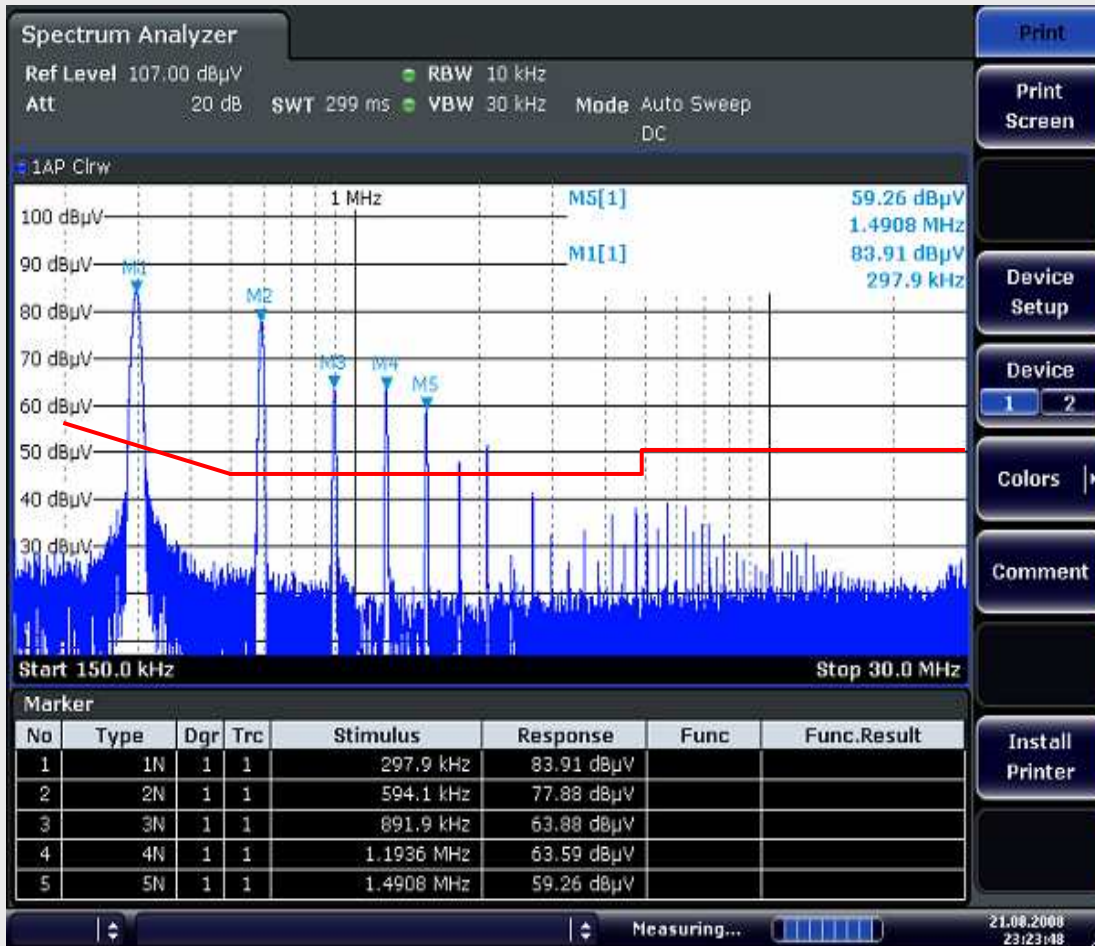

load 1.5A >

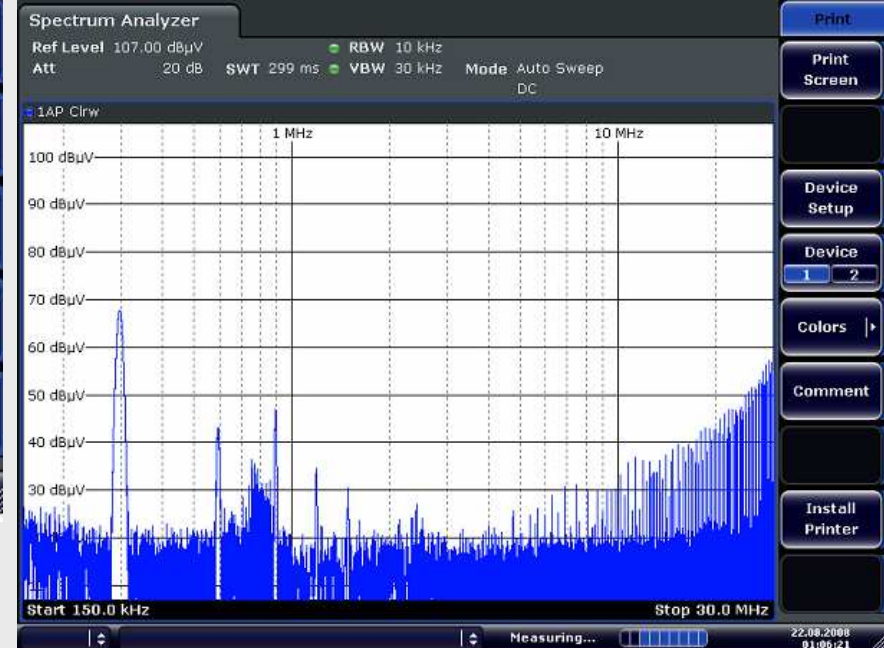

Conducted Emissions Example – Bifilar CMC




1. Coupling mode

2. Attenuation

3. Emissions

4. Transformers

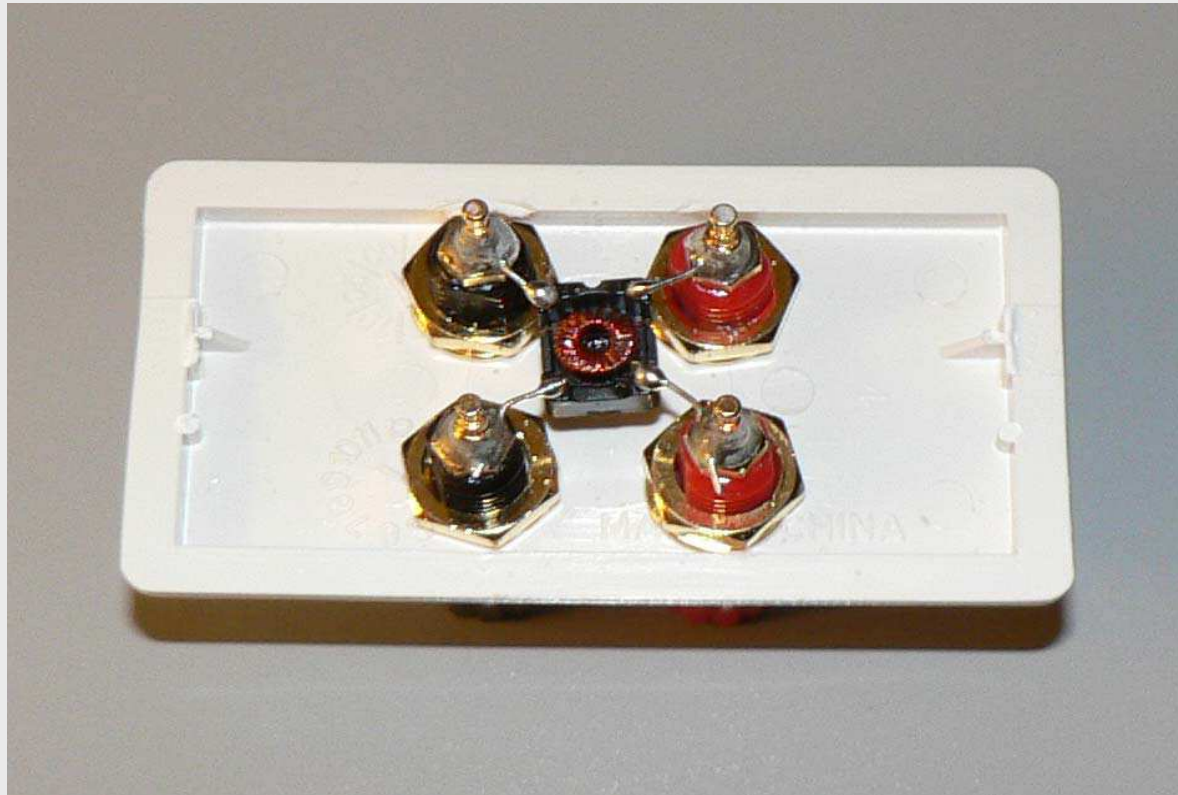

CMC 4.7mH Bifilar Winding

Conducted Emissions Example – Bifilar CMC



1. Coupling mode


2. Attenuation

3. Emissions

4. Transformers

Artikel-Nr.	Induktivität (μH)	R _{DC} (Ω)	I _N (mA)	Impedanz max. (Ω)
744272121	2 x 120	0,025	2500	460
744272221	2 x 220	0,032	2200	780
744272251	2 x 250	0,035	2000	970
744272471	2 x 470	0,065	1600	1750
744272102	2 x 1000	0,180	950	3600
744272222	2 x 2200	0,300	750	7500
744272332	2 x 3300	0,360	650	8900
744272392	2 x 3900	0,540	520	9600
744272472	2 x 4700	0,720	350	13000

744 272 472

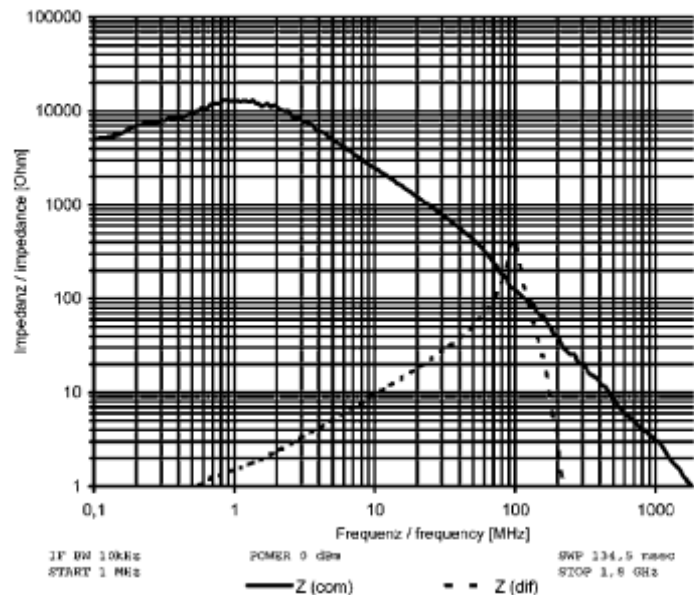

Warning: Don't try this at home!
For Demonstration Purposes Only!



Load is 1.5A




And..... CMC

CMC 4.7mH Bifilar Winding



Conducted Emissions Example – Bifilar CMC Results

no load >

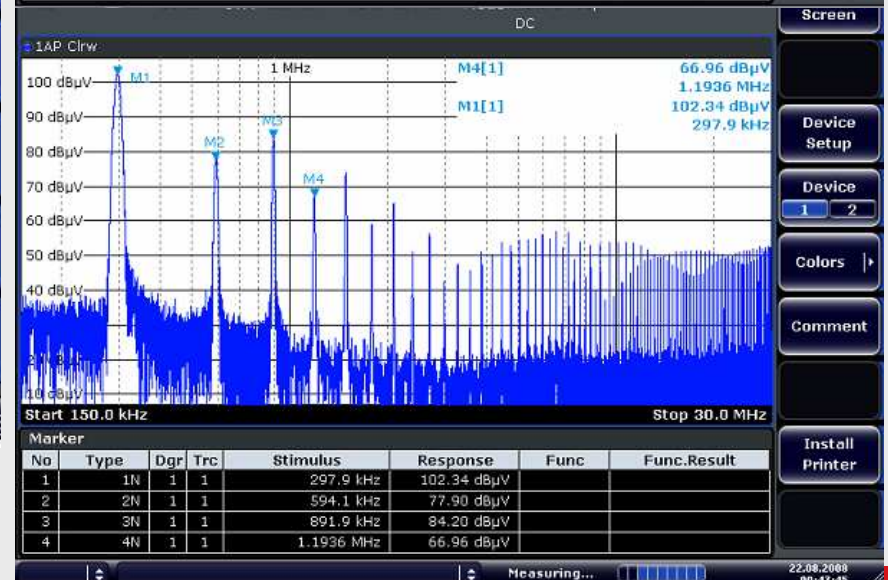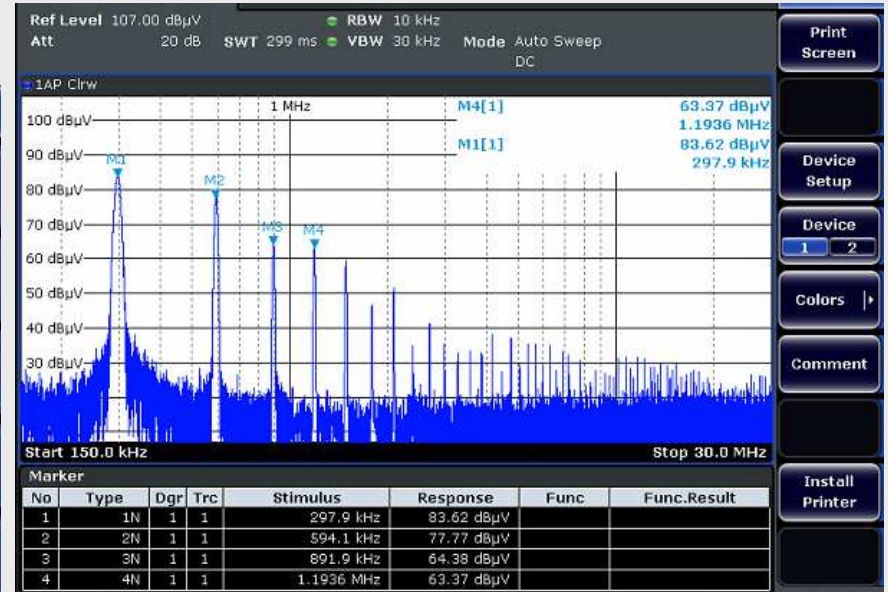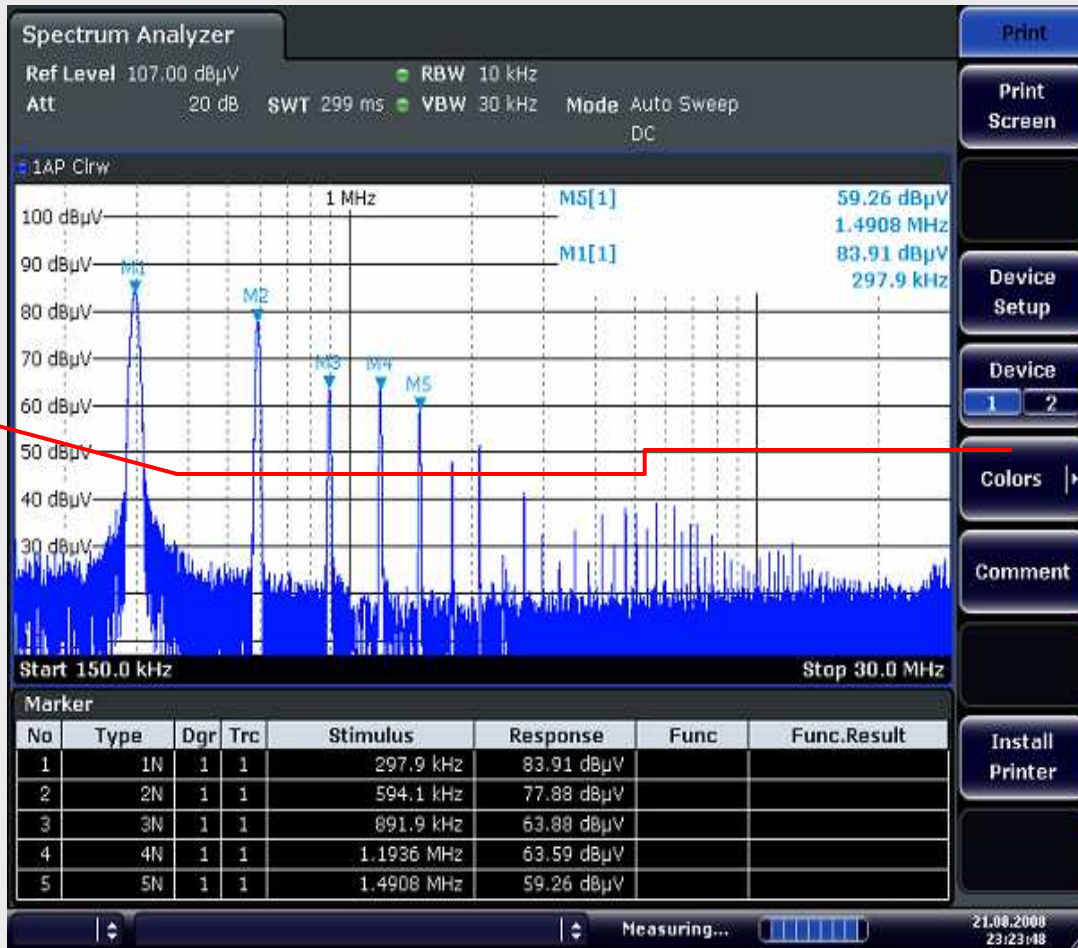

CMC 4.7mH Bifilar Winding load 1.5A>

Conducted Emissions Example – Sector CMC



1. Coupling mode

2. Attenuation

3. Emissions

4. Transformers



CMC 47mH sectional winding

Conducted Emissions Example – Sector CMC




1. Coupling mode

2. Attenuation

3. Emissions

4. Transformers


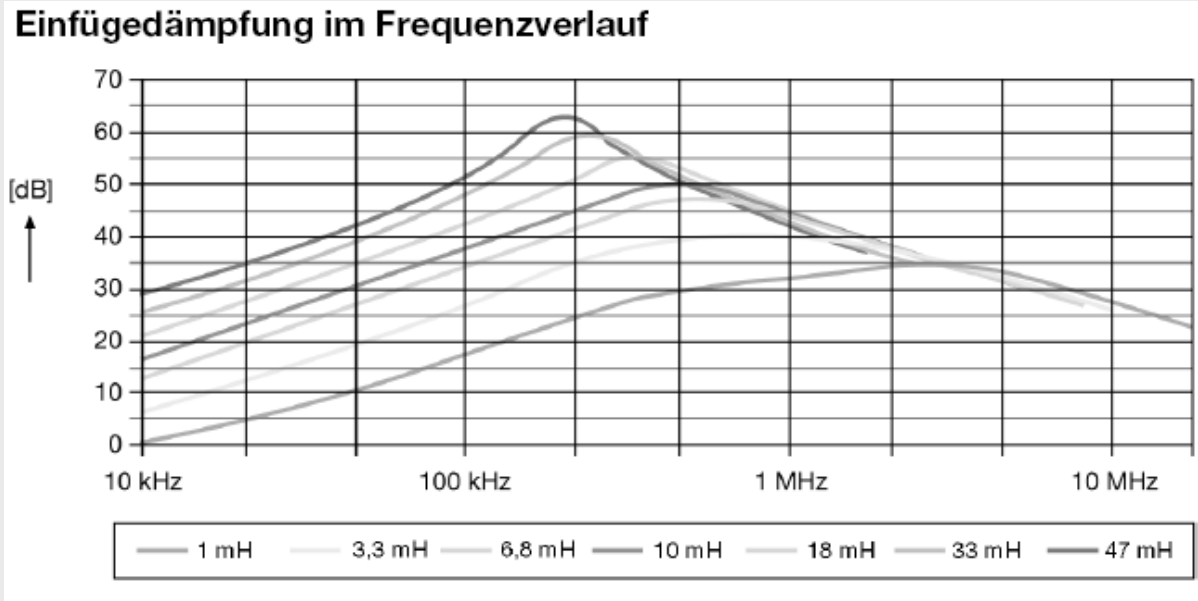


CMC 47mH Sectional Winding
 Leakage Inductance $L_s \sim 250\mu\text{H}$ (5% of L)



Conducted Emissions Example – Sector CMC Results

no load >

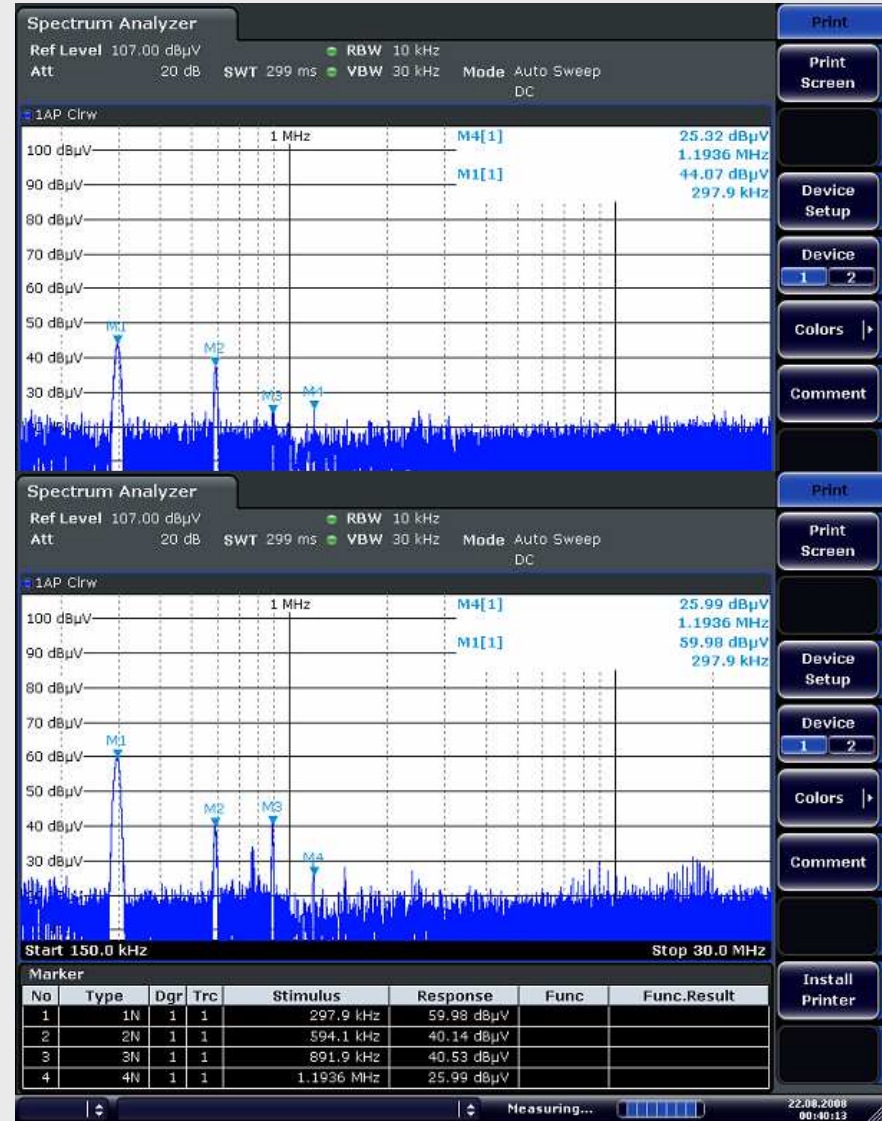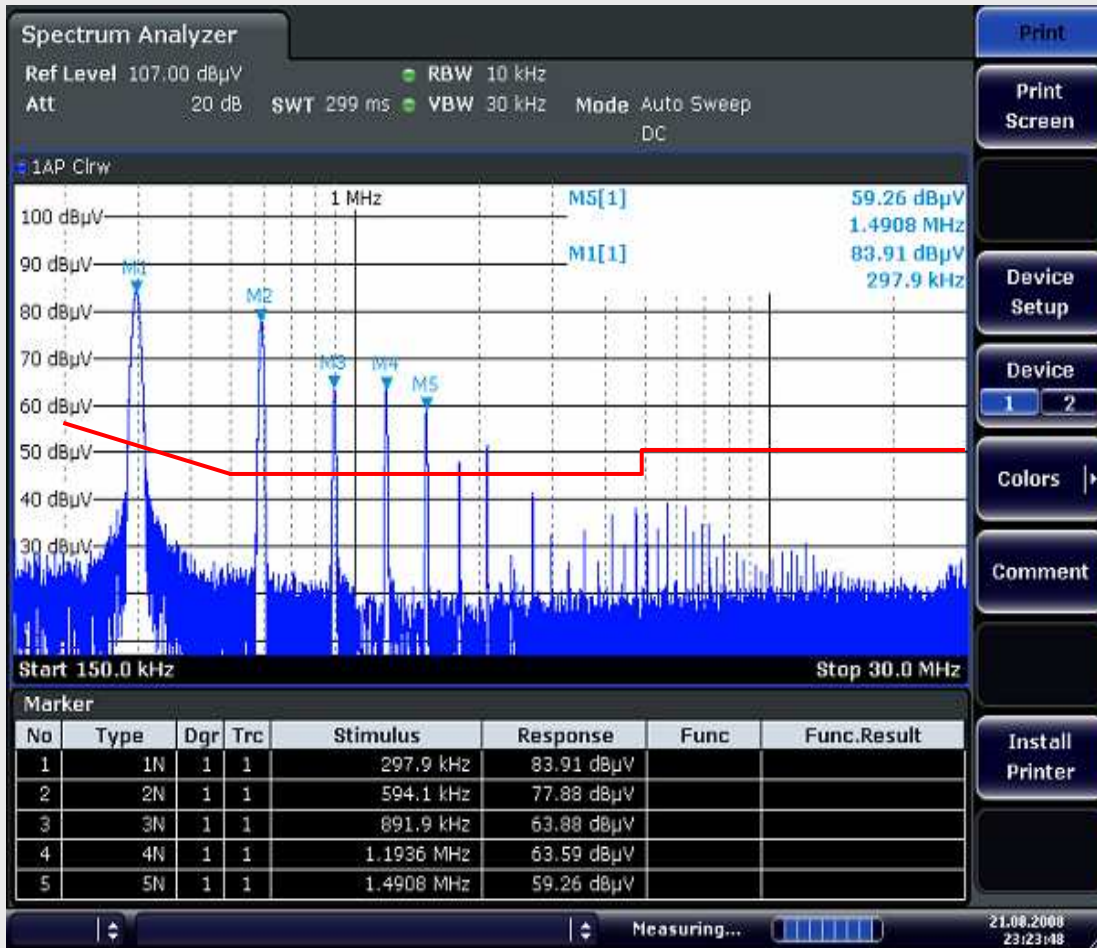

CMC 47mH sectional winding

load 1.5A>

Conducted Emissions Example – Chip Bead

1. Coupling mode

2. Attenuation

3. Emissions

4. Transformers




Chip Bead 530 Ω / 3A




Conducted Emissions Example – Chip Bead Results

no load >


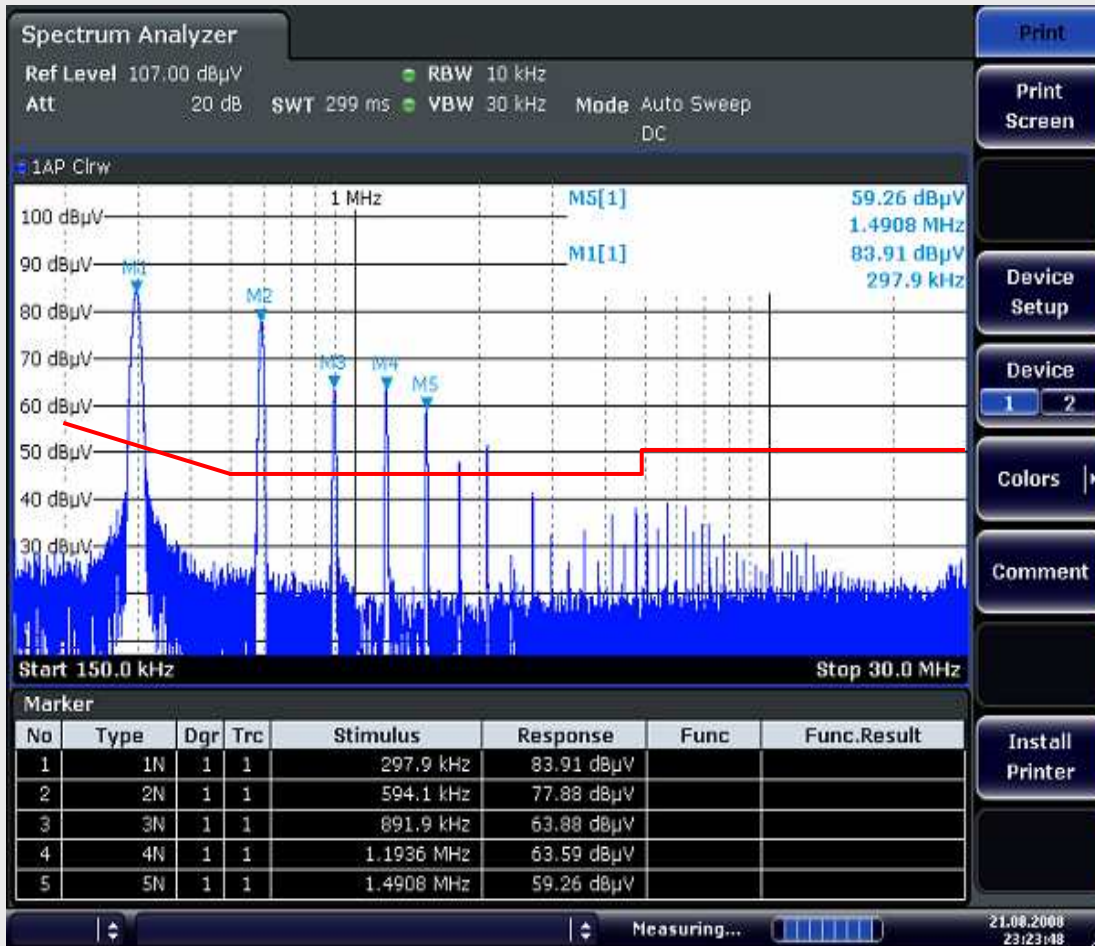


Chip Bead 530Ω / 3A

load 1.5A >

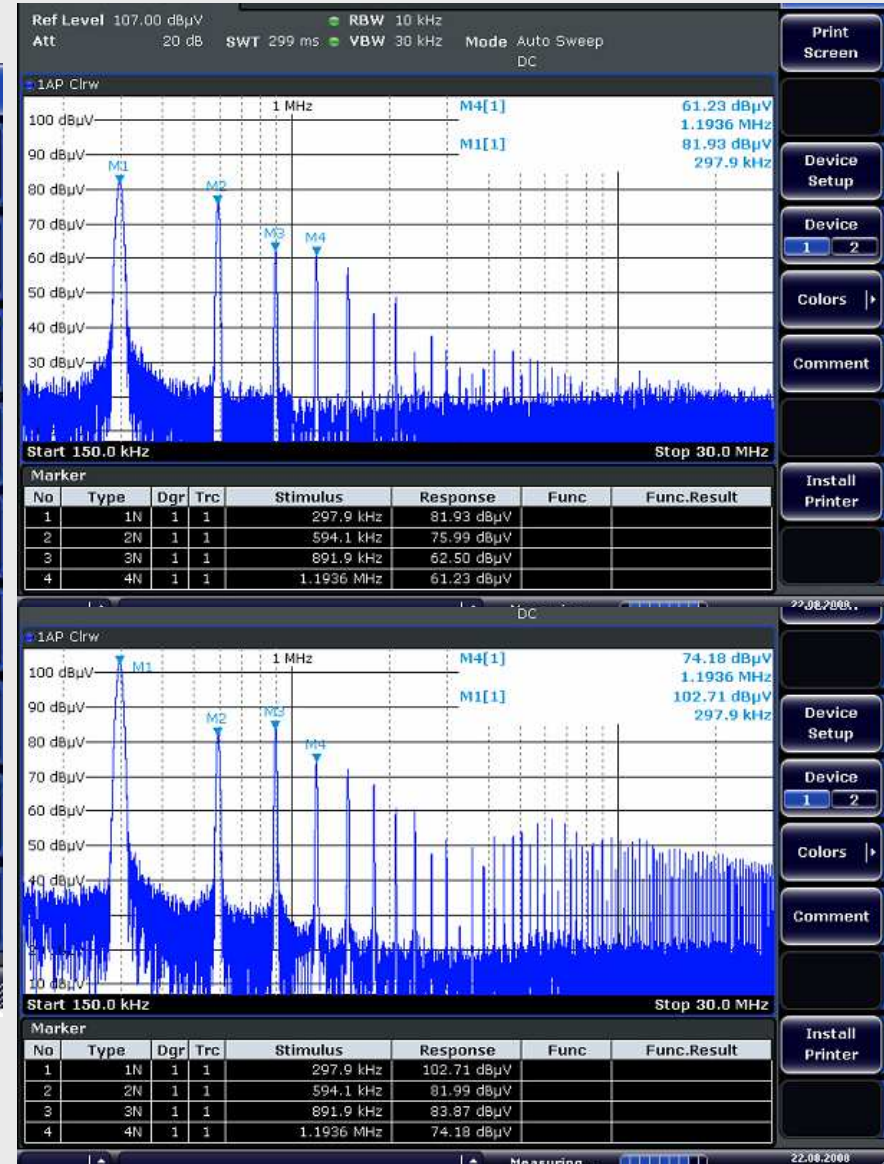


Conducted Emissions Example – Chip Bead

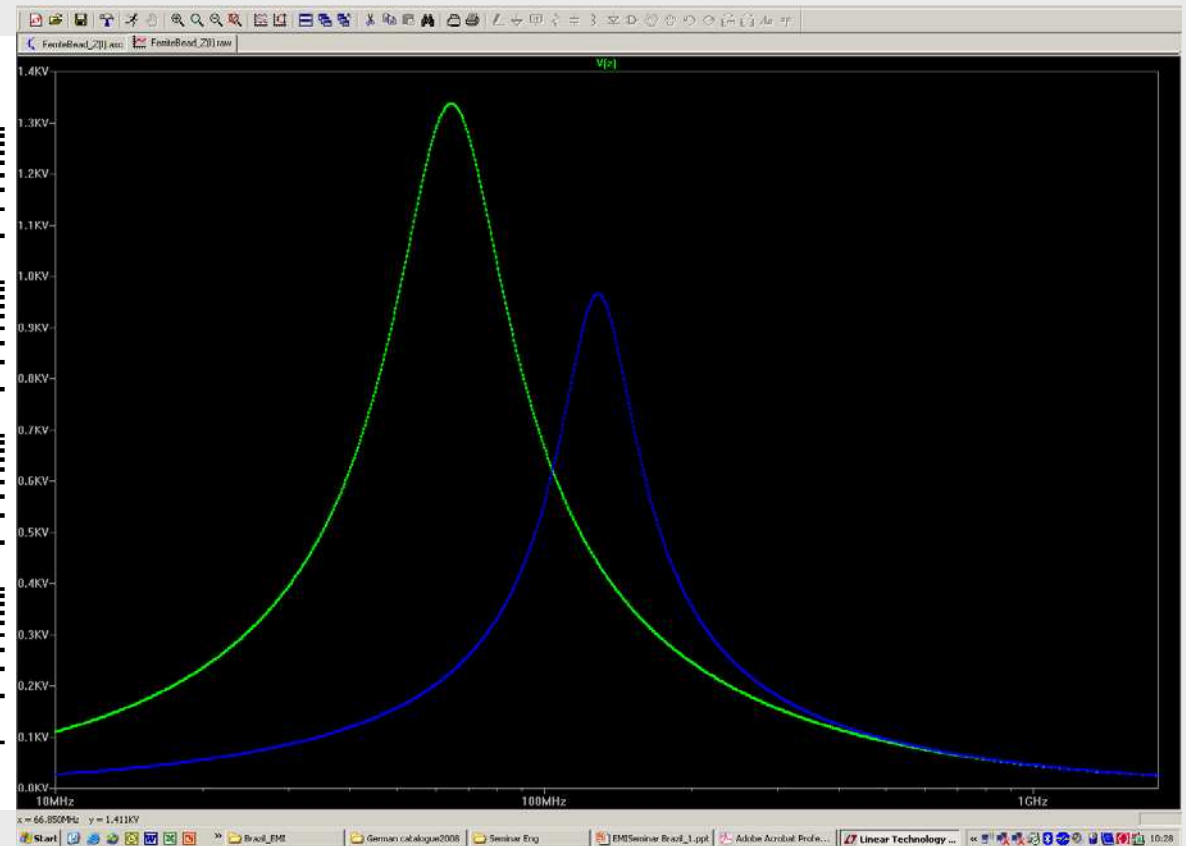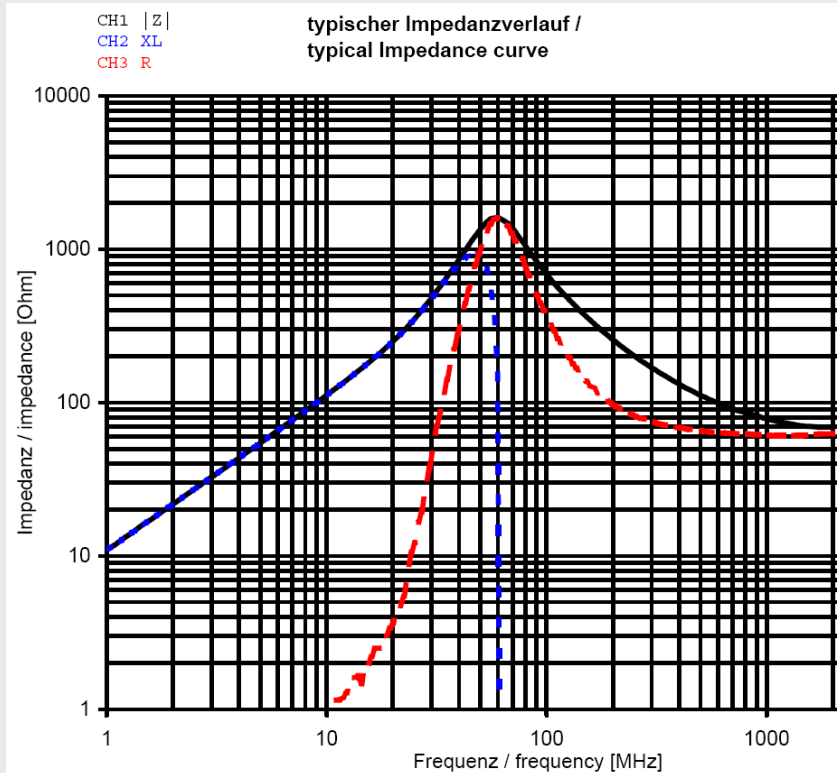

Chip Bead 530Ω / 3A

Conducted Emissions Example - Conclusions


- High Frequency Noise Appears Under Load
- Noise is Differential Mode
- Differential Choke
 - Attenuates low frequency noise because of SRF
- Bifilar CMC
 - Does not attenuate because of very low leakage inductance.
- Sector CMC
 - Attenuates both high and low because of leakage inductance with high SRF.
- Chip Bead
 - Without a load there is some affect at high frequencies, but with a load the bead pre-magnetizes and there is no affect at all.

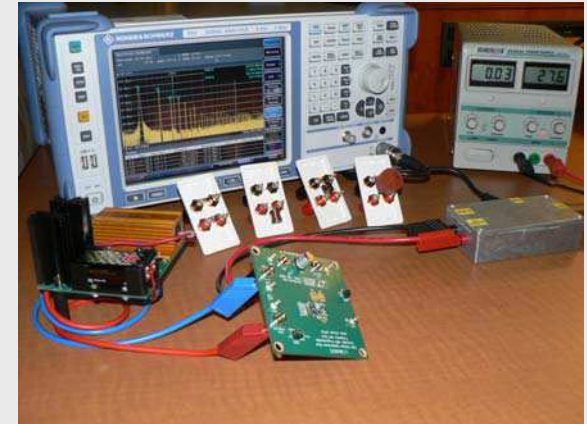

Transformers for EMC – What to Choose



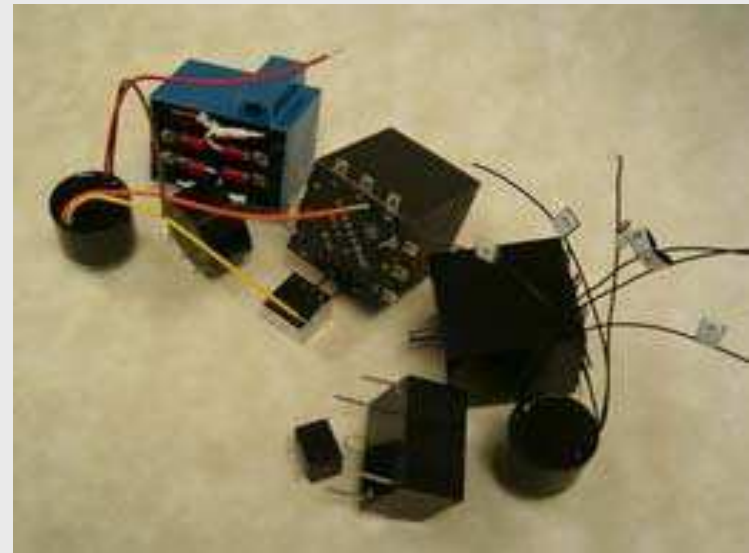1. Coupling mode
2. Attenuation
3. Emissions
- 4. Transformers**



Transformers for EMC – No Antennas Please!






1. Coupling mode
2. Attenuation
3. Emissions
- 4. Transformers**

Enough Said!



Flying Leads Make Great Antennas.

Transformers for EMC – No External Gaps

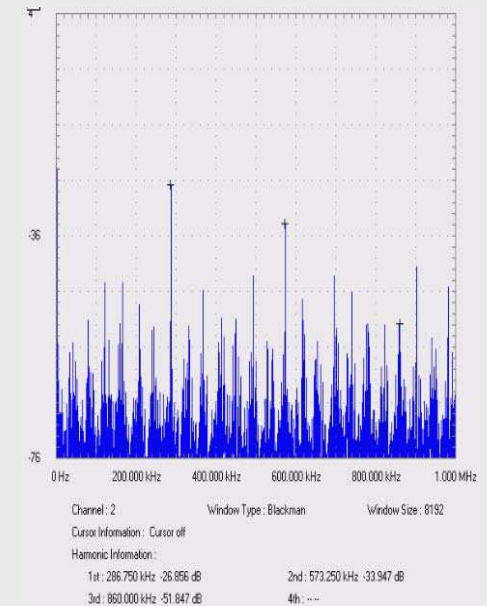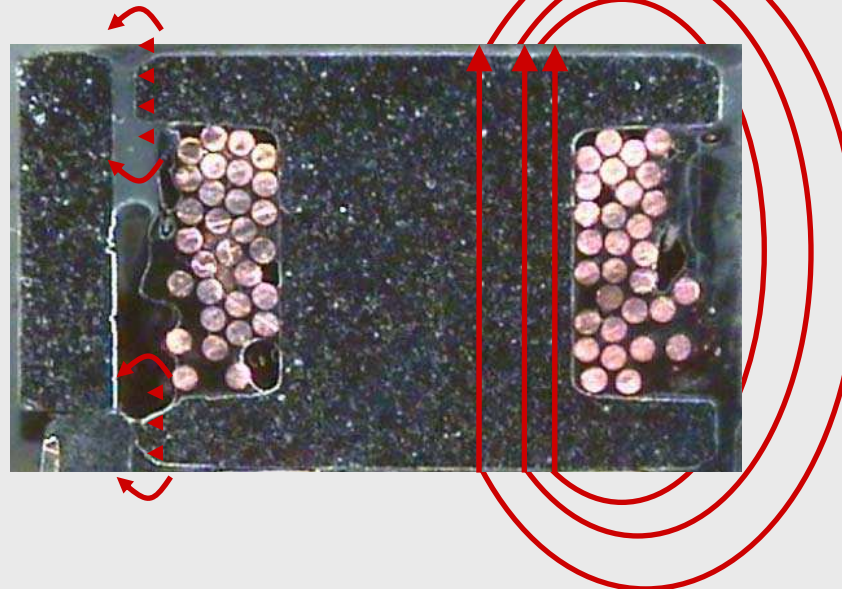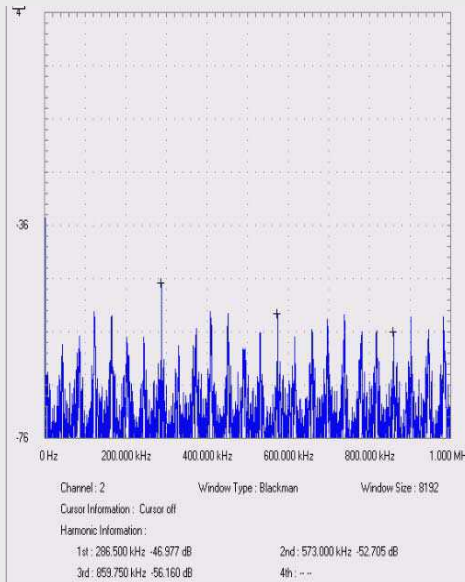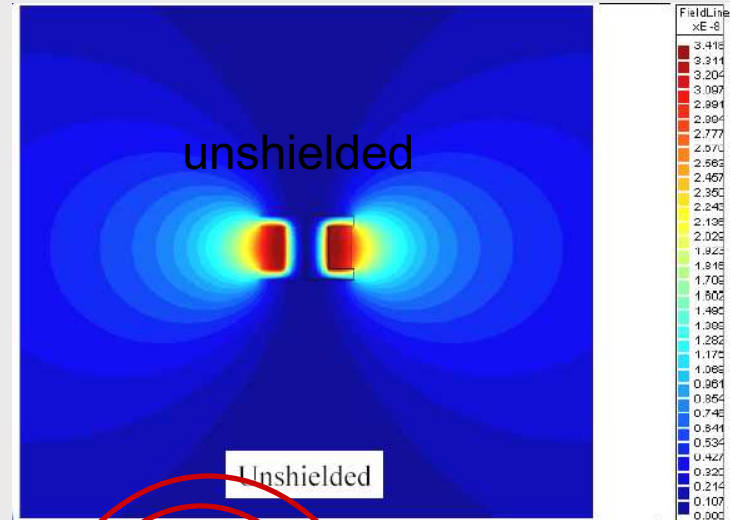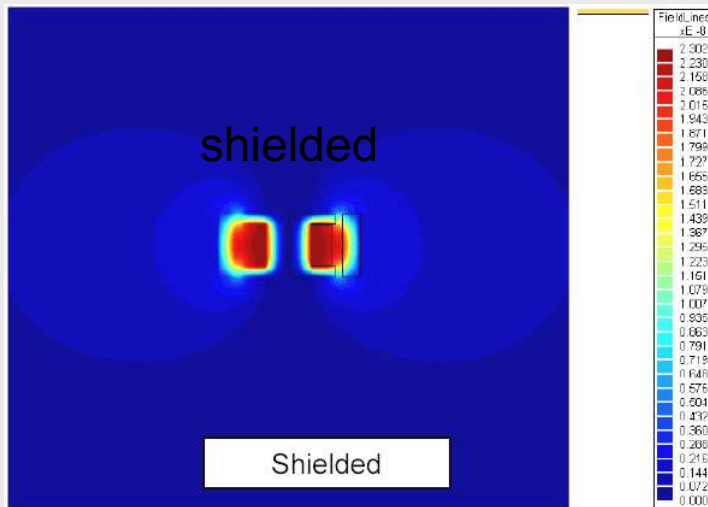


Transformers for EMC – No External Gaps

- Center Leg Gap Only
 - Windings Shield
- No Gaps in Outer Legs
 - Nothing to Shield

No Gaps Here

Gap Here

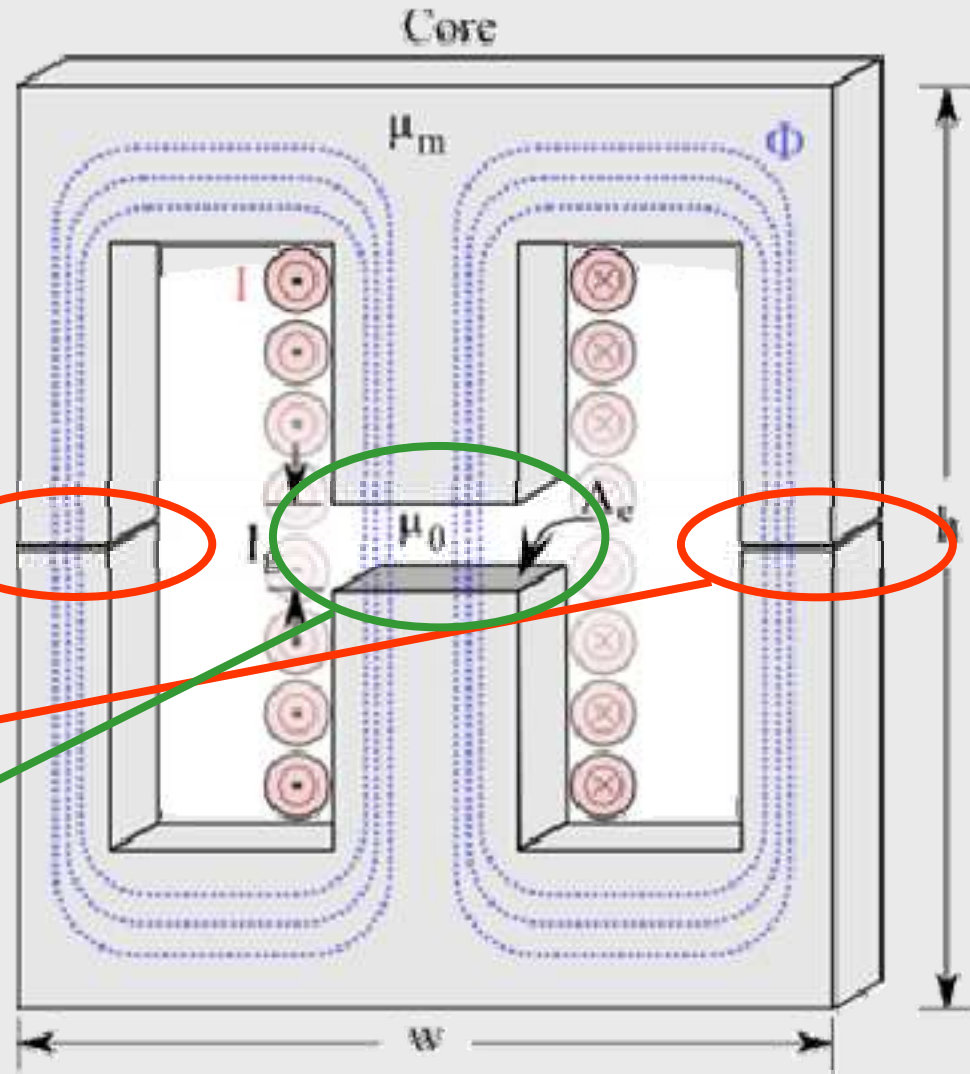


Transformers for EMC – No Drum Cores



1. Coupling mode
2. Attenuation
3. Emissions
- 4. Transformers**

- Drum Core Style
- Very Large Gap
- Much Radiation

Not a good solution!

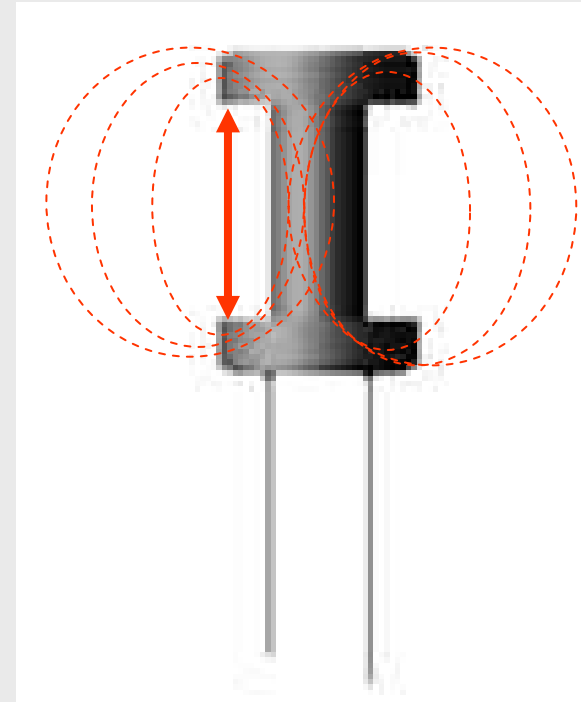

Transformers for EMC – No Rod Cores


1. Coupling mode
2. Attenuation
3. Emissions
- 4. Transformers**

- Rod Core Style
- Huge Gap – Much Radiation
- This is an AM Antenna

So Where is the Gap?

Not a good solution!

What is this?

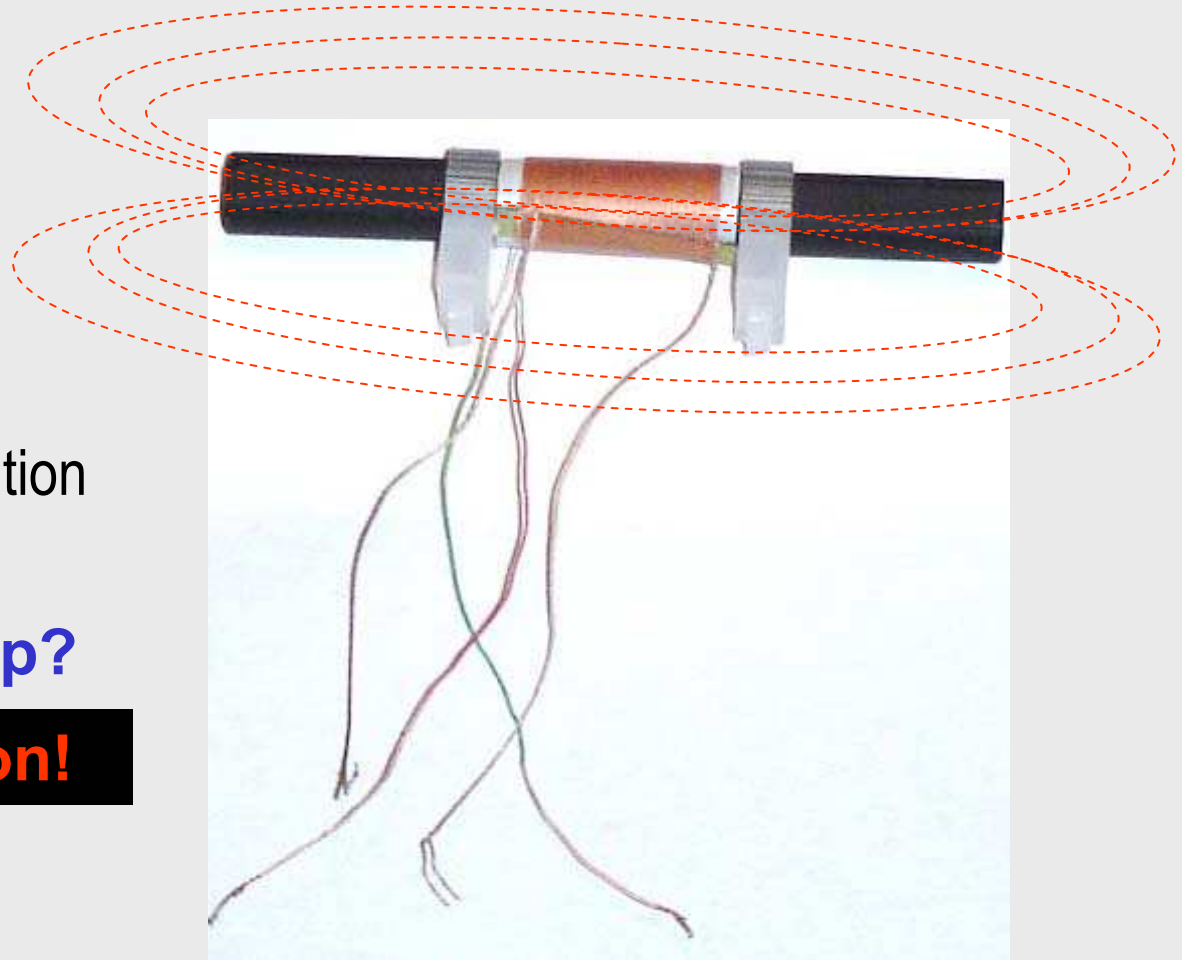


Transformers for EMC – No EI Core



1. Coupling mode
2. Attenuation
3. Emissions
- 4. Transformers**


- EI Core Style
- Mylar or Tape Used for Gap
- Three Unshielded Gaps

Not a good solution!

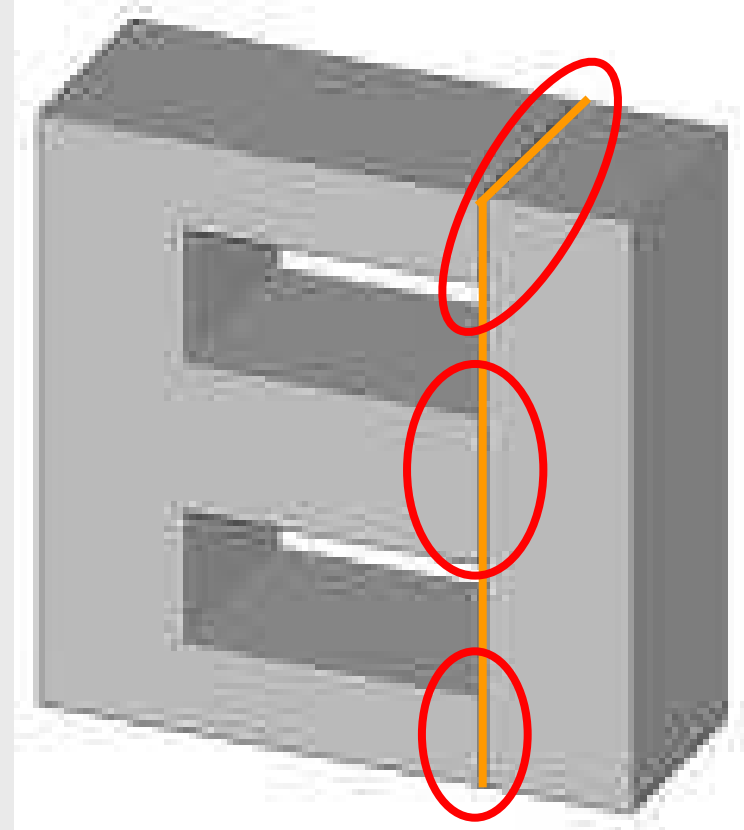

Transformers for EMC – Gap

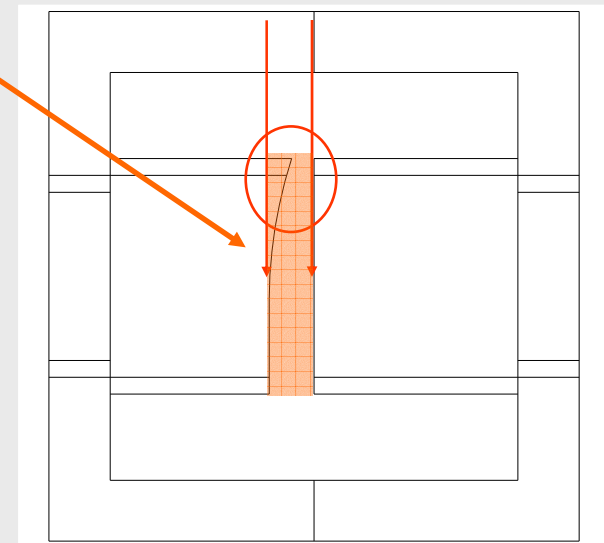- Gap Must be Perpendicular to Flux Lines
 - Here Only One Side is Gapped
- Uneven Gaps Are Inefficient, **Why?**
 - Core Saturates at Minimum Gap.
 - Requires a Larger Gap
- Also Larger Gap – More Potential EMI




Transformers for EMC - Fringing Affect



1. Coupling mode
2. Attenuation
3. Emissions
- 4. Transformers**

Turns Over Gap May Not “Count”

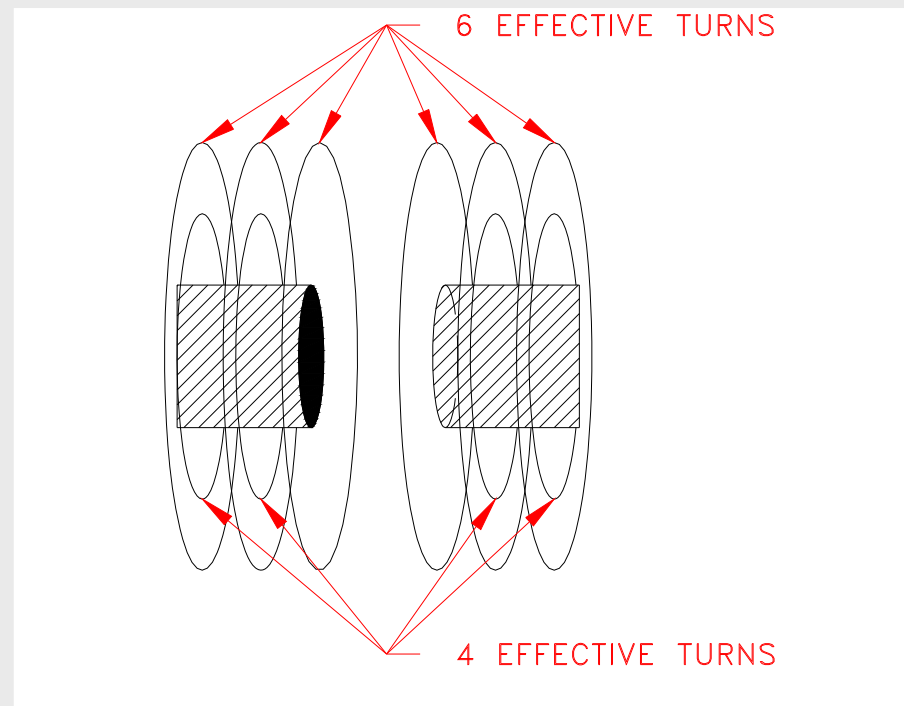

Large Gaps over Two Section Coil – May Need Symmetrical Gap


Transformers for EMC - Fringing Effect




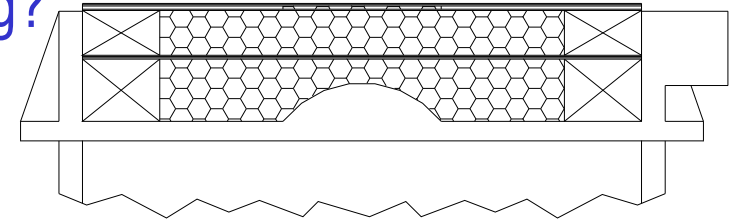
- 1. Coupling mode
- 2. Attenuation
- 3. Emissions
- 4. Transformers**

How Can We Compensate for Fringing?


- Adjust Turns Ratio
- Symmetrical Gap
- New Design with Smaller Gap
- Avoid Gap with Winding



TAPE DETAIL

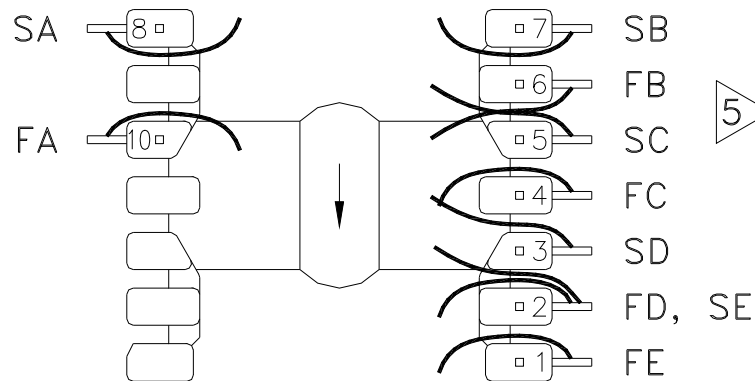
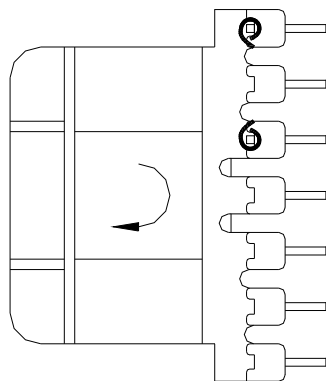


KEY LOCATES TERM. #1-5 SIDE

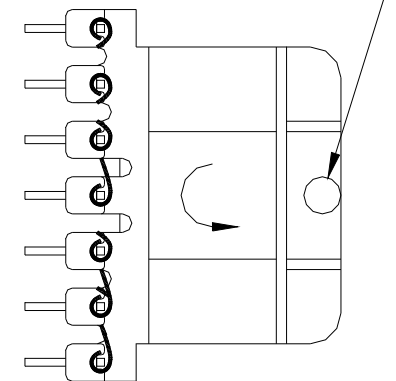

Transformers for EMC – Internal Shields

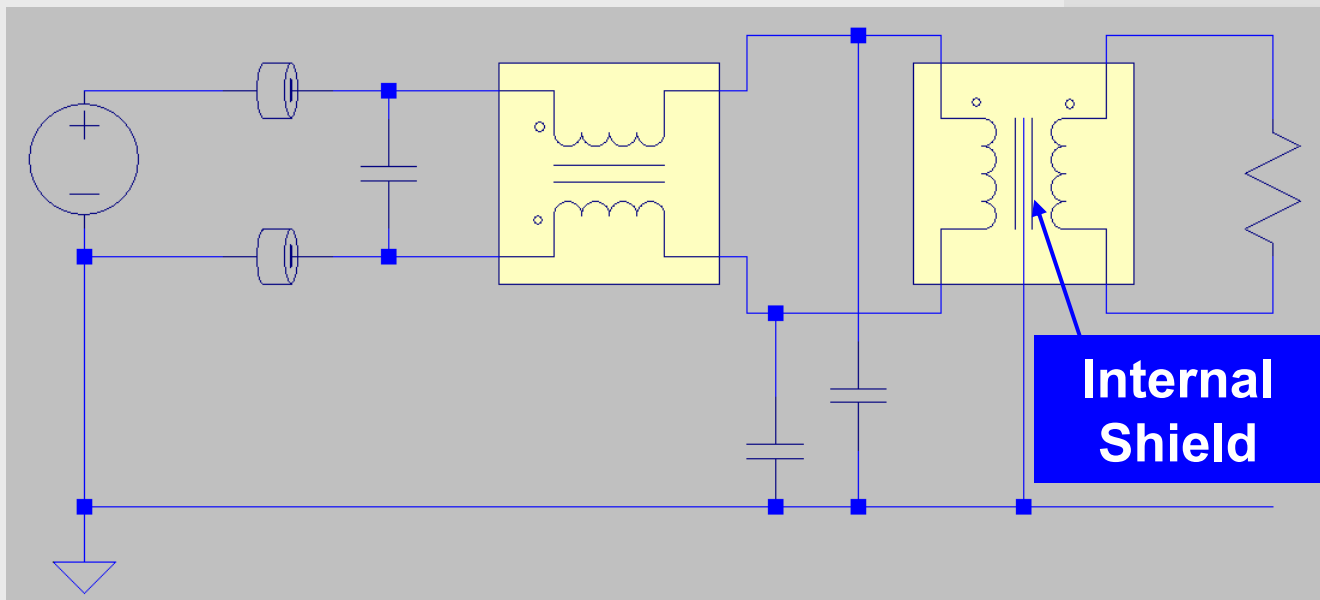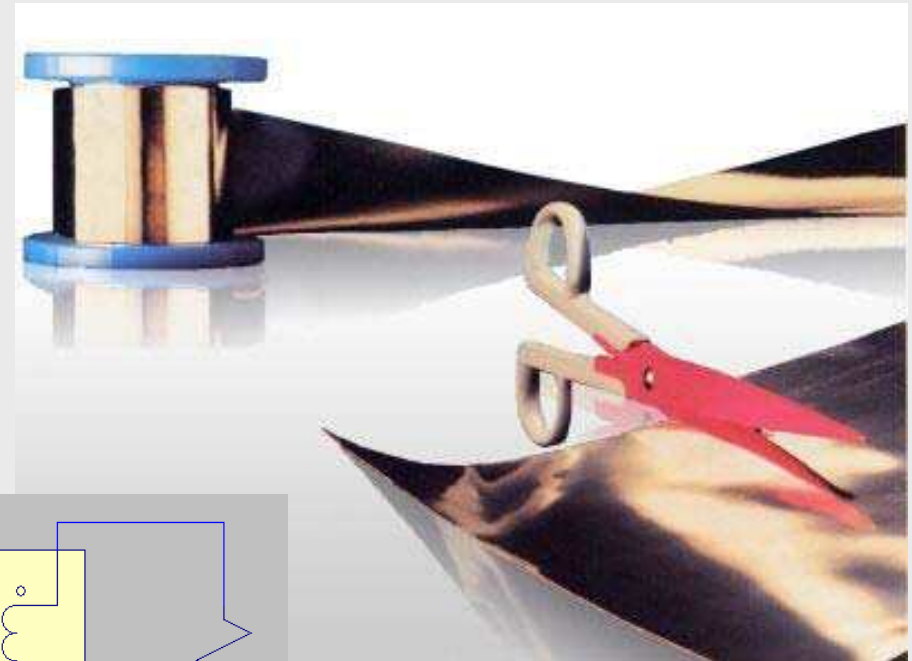
- Shield both Conducted and Radiated Noise
- Copper Foil or Wound Magnet Wire?
- Copper Foil Shields – Expensive, Why?
 - Must Build Shield
 - Must be Cuffed with Tape
 - Winding Machine Stopped to Apply
- All Shields Take Away from Winding Area



Transformers for EMC – External Shields




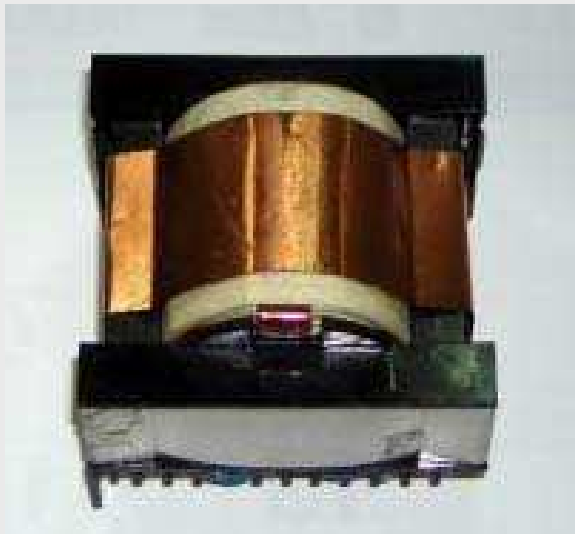- **How Do External Shields Differ from Internal Shields?**
- **Shield Radiated Noise ONLY!**
- **As Expensive as Internal Shields**




Transformers for EMC – Multi-layer Primary Termination

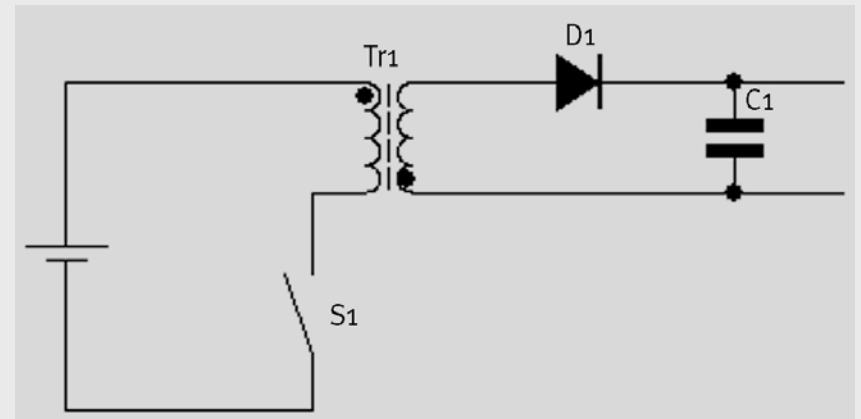- How does One Terminate a Multi-layer Primary?
- Terminate Start to Switch so Subsequent Layer/s Shield High dv/dt Windings from outside world.




No Perfectly Fine on
Fi if Consistent. ?

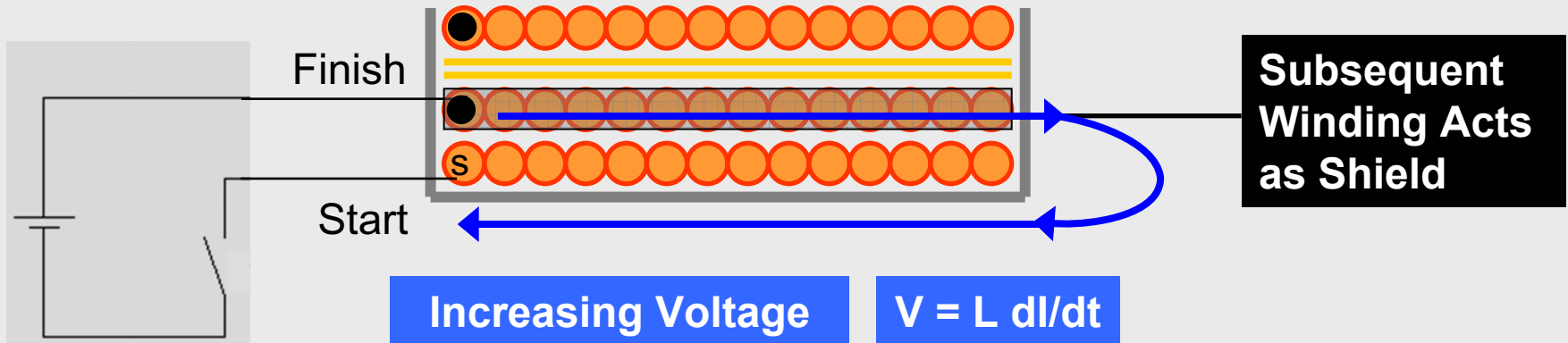

Transformers for EMC – Y-Cap Termination

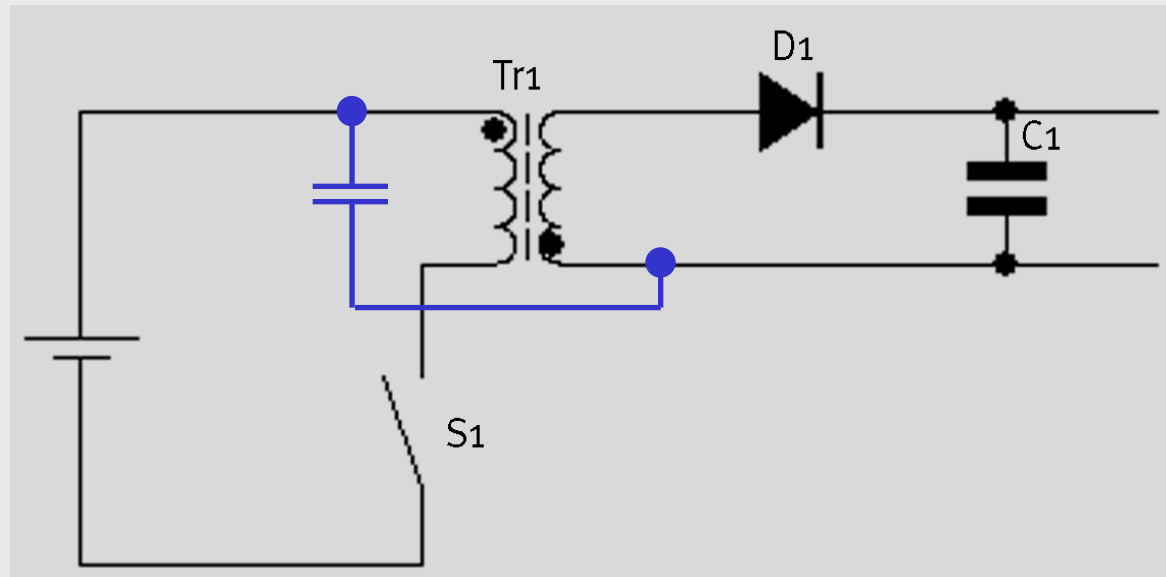- 1. Coupling mode
- 2. Attenuation
- 3. Emissions
- 4. Transformers**



- Noise Couples Through the Transformer via C_{ww}
 - Noise Seeks Path to Primary Circuit
 - Without Path, Noise May Become Conducted Emissions
- Y-Cap Across Transformer Reduces Noise
 - Tune the Capacitor for Optimum Loss vs. Noise Reduction
 - Capacitor Usually in the 2.2nF to 4.7nF range
 - Y-Caps to Transformer Terminals not on Switch nor on Diode
 - Close to Transformer as Possible

What Can We Do?

Decrease C_{ww} ?

What Else Can We Do?

Transformers for EMC – Reducing C_{ww}



1. Coupling mode
2. Attenuation
3. Emissions
- 4. Transformers**

- High C_{ww} Causes Conducted Emissions
- **May Reduce C_{ww} , but What Happens?**
- Leakage Inductance Increases
- L_{LKG} can be Controlled by Snubber but Efficiency and Cost Suffer
- Balance Between C_{ww} and L_{kg}



Transformers for EMC – Reducing C_{ww}

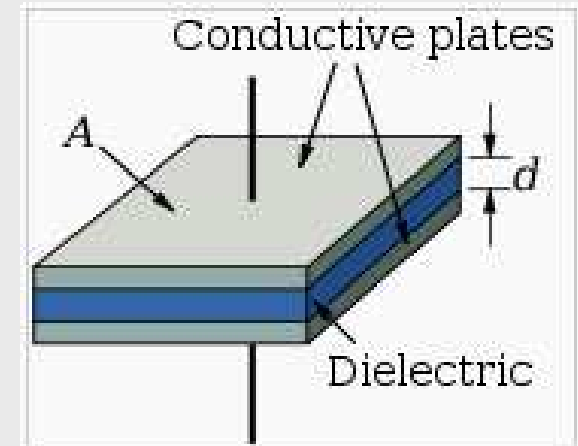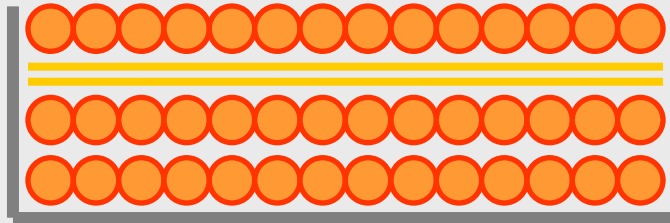1. Coupling mode
2. Attenuation
3. Emissions
4. Transformers



How Do We Reduce Capacitance?

- Multi-section or Narrow Bobbin
 - Reduces Area and Increases Distance
- Lots of Tape
 - Increases Distance
- Reduce Dielectric Constants, **How?**
 - No Potting Compounds or Varnishes
 - Does Not Affect Leakage Inductance


$$C = \epsilon_r \epsilon_0 \frac{A}{d} \text{ (in SI units)}$$

How is L_{Igk} Affected?

Transformers for EMC – No Varnish or Potting



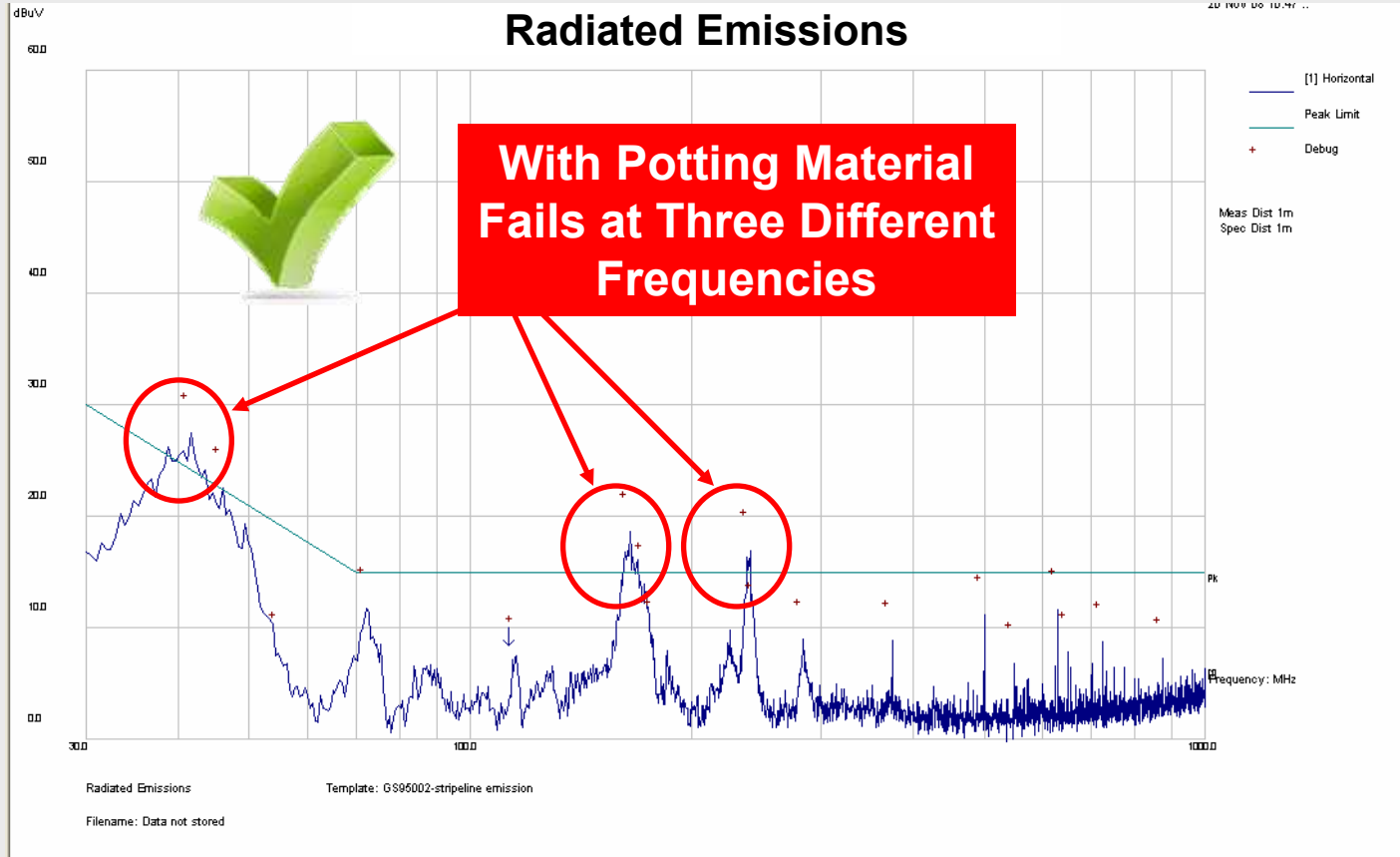- 1. Coupling mode
- 2. Attenuation
- 3. Emissions
- 4. Transformers**



No	Frequency MHz	Raw dBuV	Cable Loss	AF dB	Level dBuV	Measurement Type	Pol	Hgt cm	Azt Deg	Limit dBuV	Margin dB	Pass /Fail	Comments
1	41.640	47.0	10.4	-30.0	27.4	Peak [Scan]	H	100	0	24.2	3.2	Fail	
2	46.005	42.1	10.4	-30.0	22.6	Peak [Scan]	H	100	0	22.4	.1	Fail	
3	54.735	27.2	10.4	-30.0	7.7	Peak [Scan]	H	100	0	19.3	-11.6	Pass	
4	72.195	31.1	10.5	-29.9	11.7	Peak [Scan]	H	100	0	15.0	-3.2	Pass	
5	115.360	26.6	10.6	-29.8	7.4	Peak [Scan]	H	100	0	15.0	-7.5	Pass	
6	164.830	37.4	10.7	-29.5	18.6	Peak [Scan]	H	100	0	15.0	3.6	Fail	

Library of Known Ambients


Transformers for EMC - Small Designs



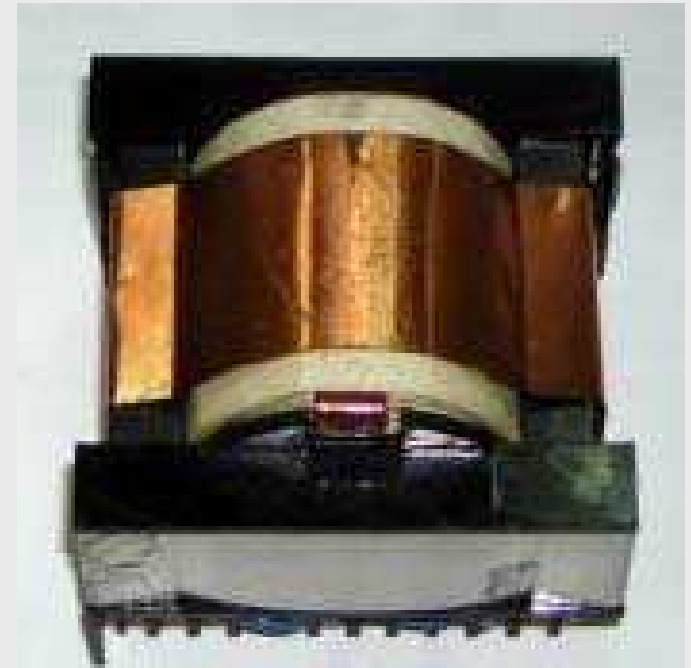
1. Coupling mode
2. Attenuation
3. Emissions
- 4. Transformers**

Why Build Smaller Designs?

- Build Smaller More Compact Transformers
- Smaller Transformers have less Parasitics
 - Less Capacitance
 - Smaller Leads (ie. Smaller Antennas)
 - Smaller Gaps
 - Less Leakage Inductance
- Less Conducted and Less Radiated Noise



Transformers for EMC – Power Supply

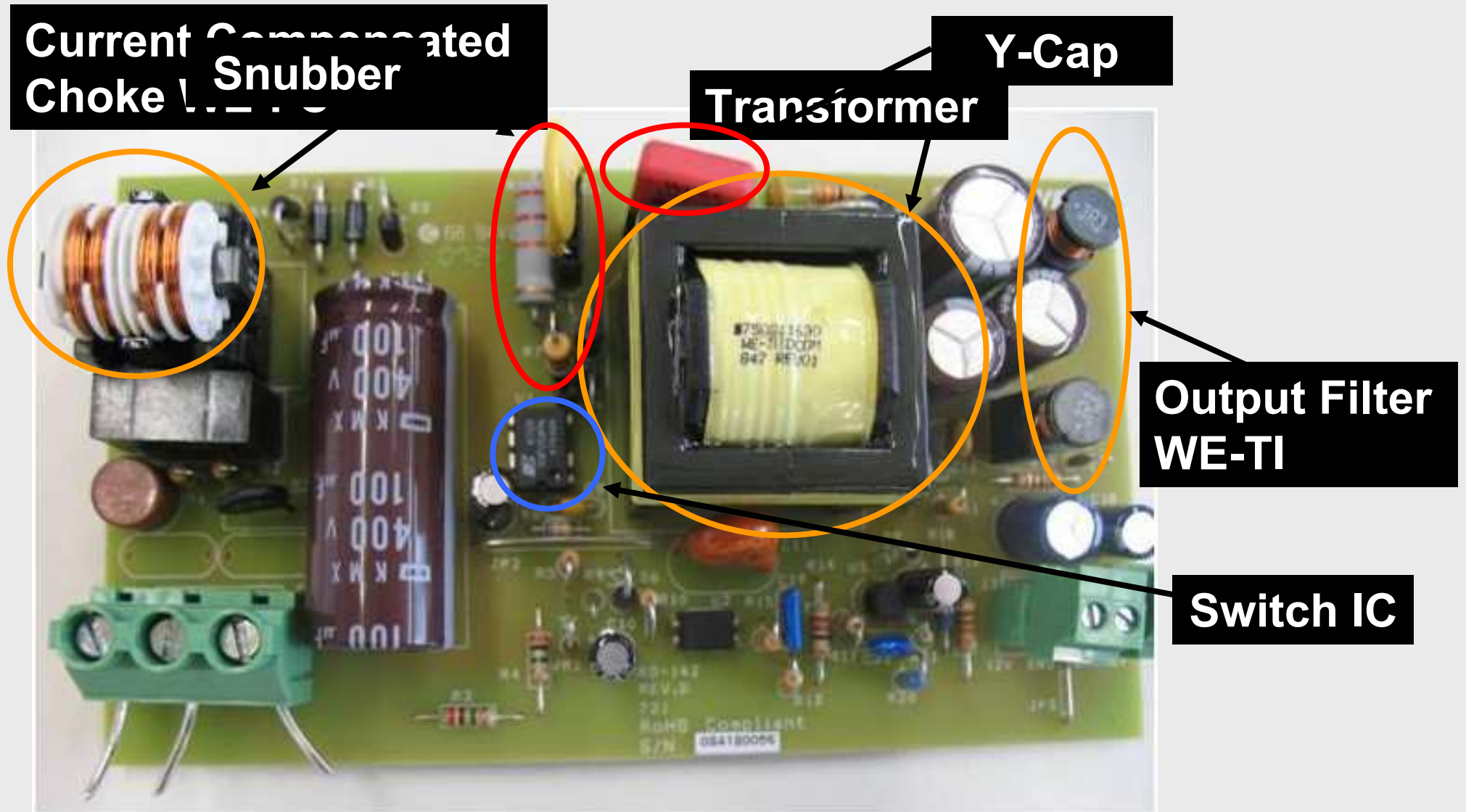




Transformers for EMC – Schematic

Current Compensated Choke WE-FC

Snubber Transformer


Y-Cap

Output Filter WE-TI

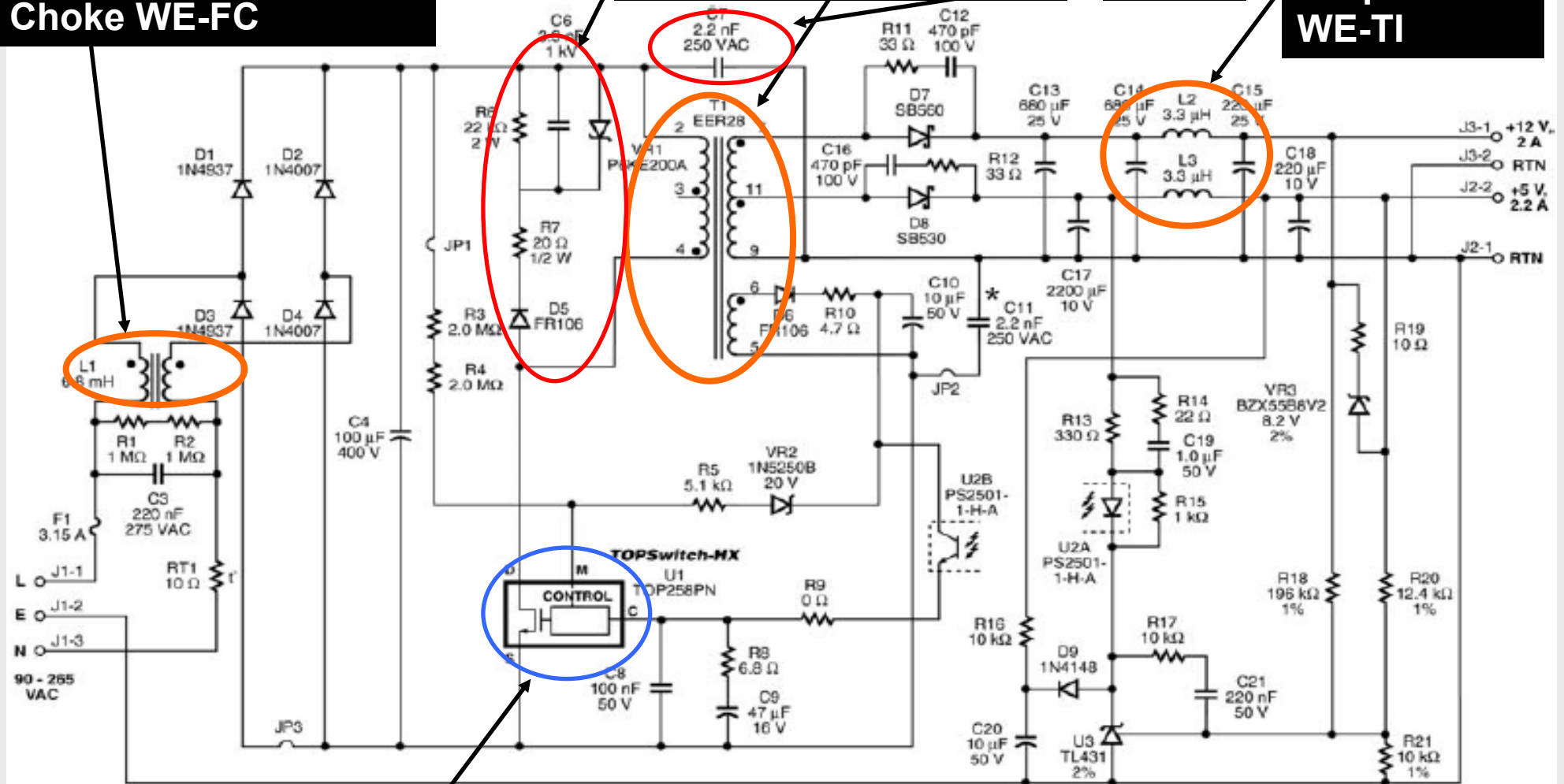

Switch IC

Transformers for EMC – Example 1

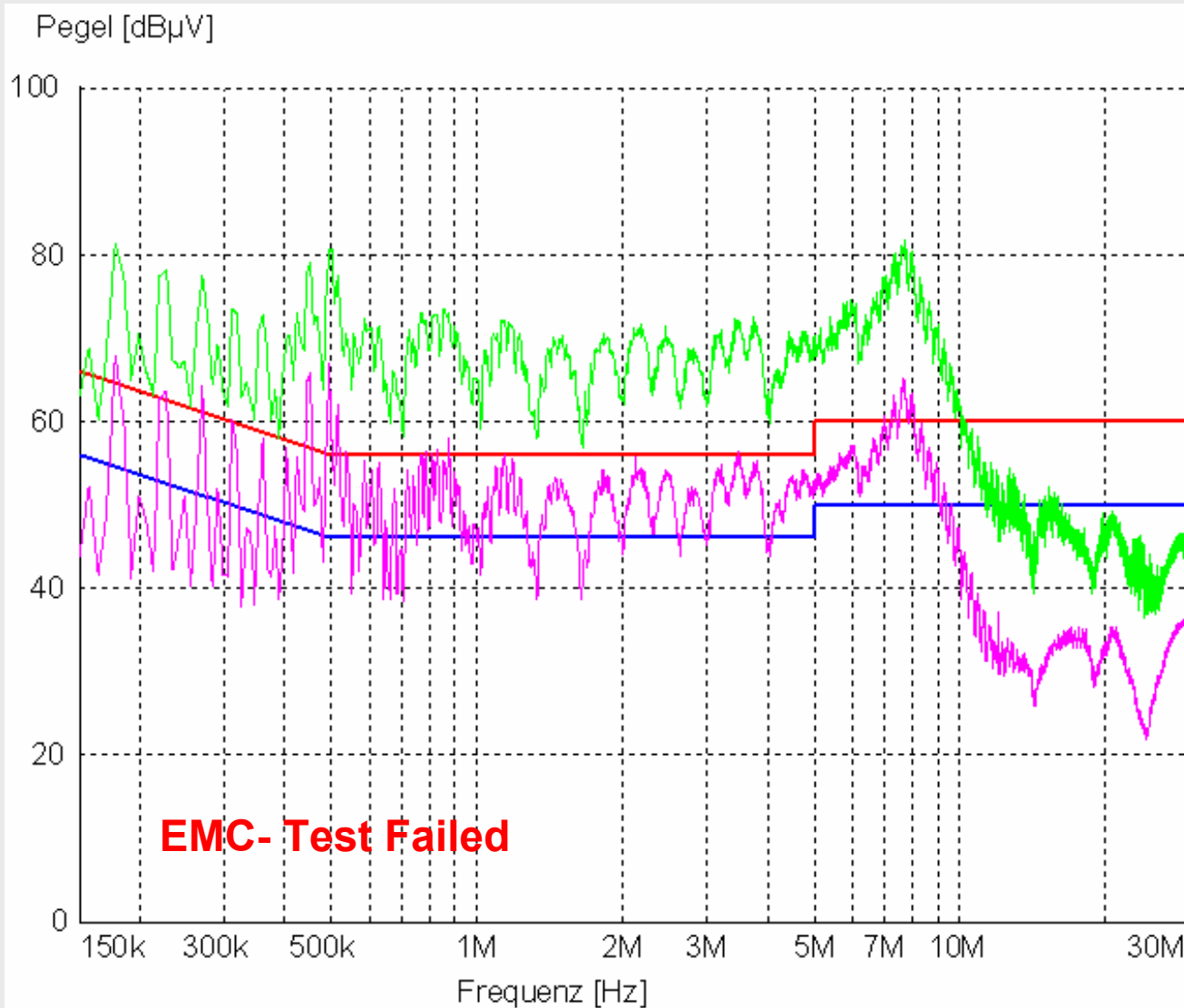

- Without Current Compensated Choke
- With Adjusted Snubber
- Without Adjusted Y-Cap


Peak

Avg.

Peak

Avg.

Transformers for EMC – Example 2

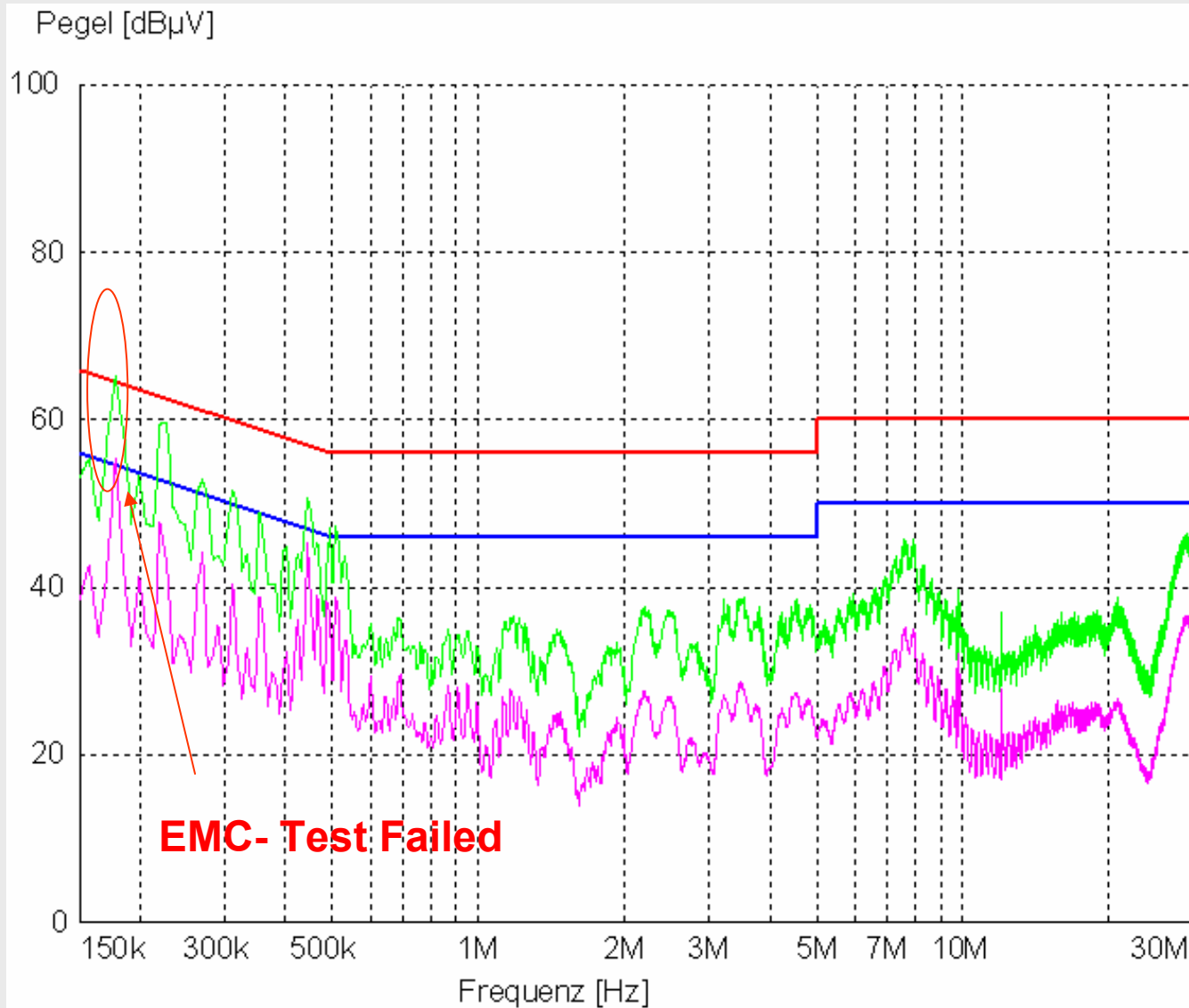

- With Current Compensated Choke
- With Adjusted Snubber
- Without Adjusted Y-Cap


Peak

Avg.

Peak

Avg.

Transformers for EMC – Example 3

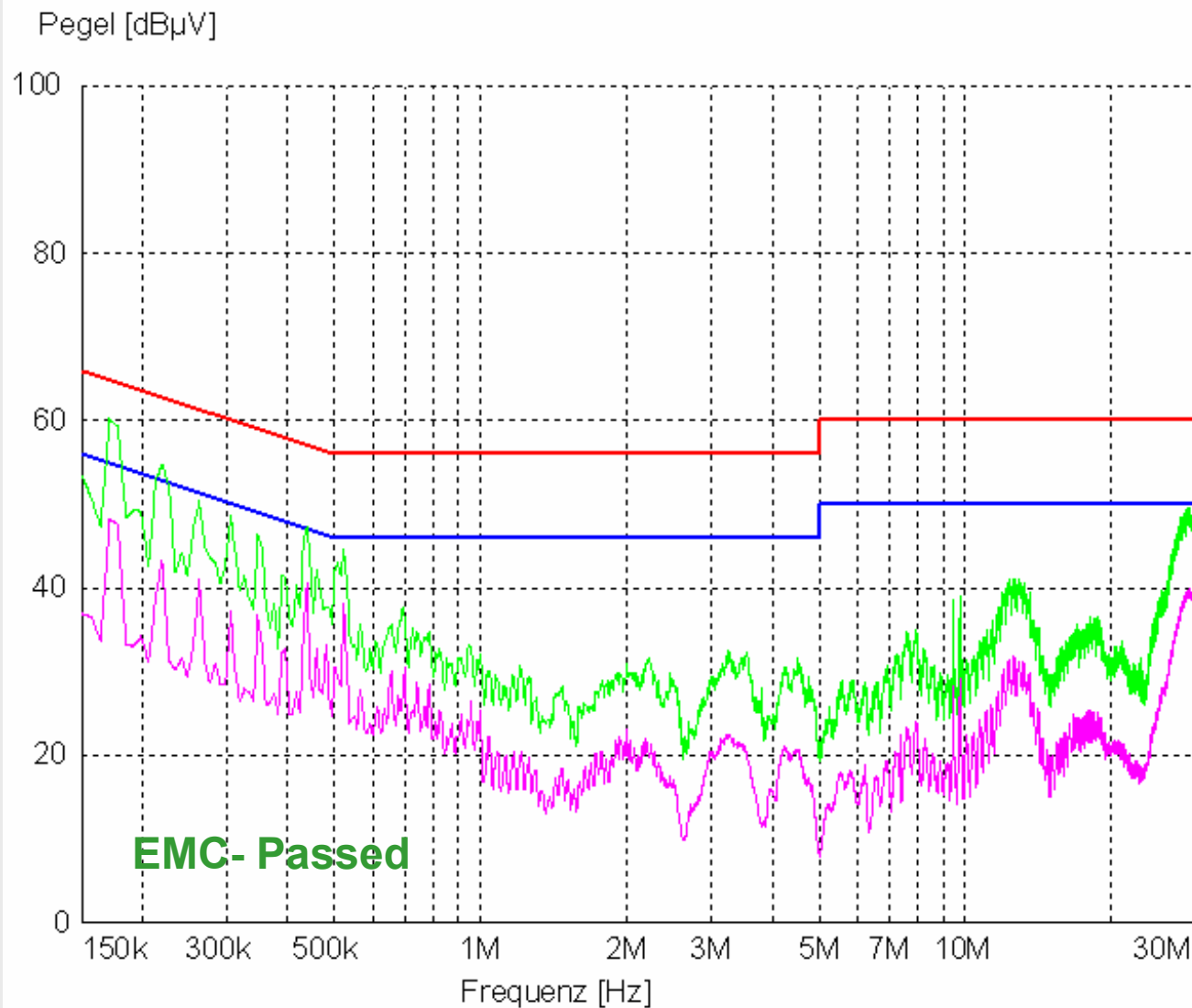

- With Current Compensated Choke
- With Adjusted Snubber
- With Adjusted Y-Cap


Peak

Avg.

Peak

Avg.

Transformers for EMC – Example 4

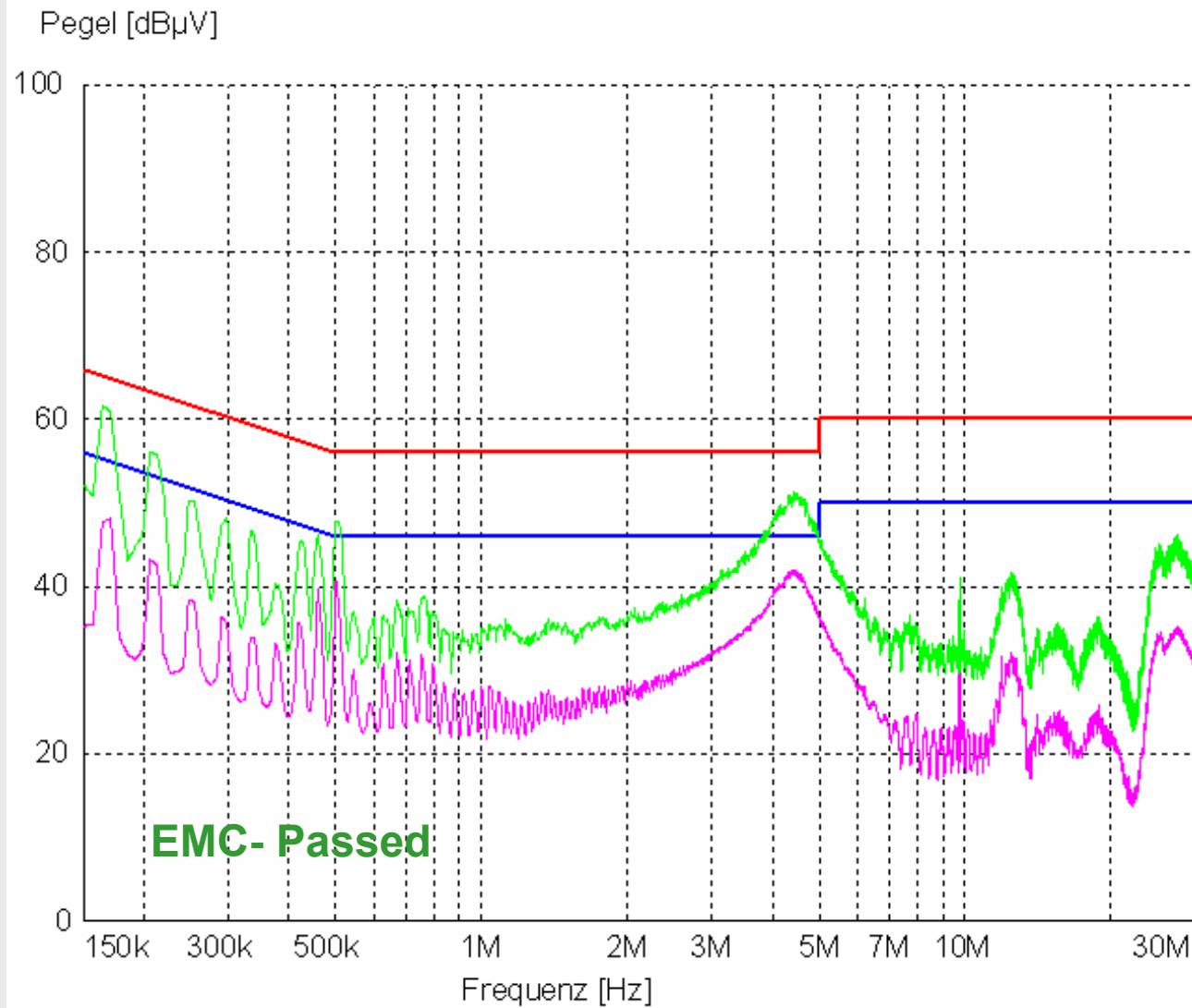

- With Current Compensated Choke
- Without Adjusted Snubber
- With Adjusted Y-Cap

Peak

Avg.


Peak

Avg.

Transformer for EMC – Conclusion for this Supply




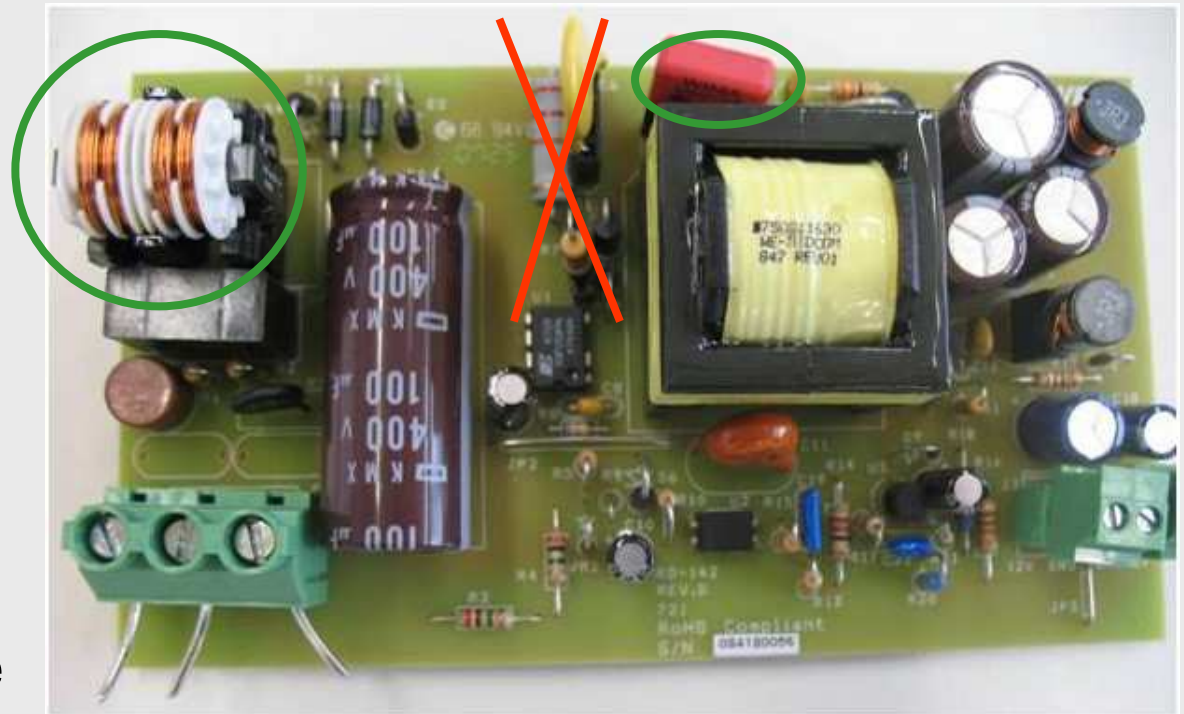1. Coupling mode
2. Attenuation
3. Emissions
- 4. Transformers**



- Necessary to Pass
 - Current Compensated Choke
 - Y-Caps
- Not Necessary to Pass
 - Optimized Snubber

Applications

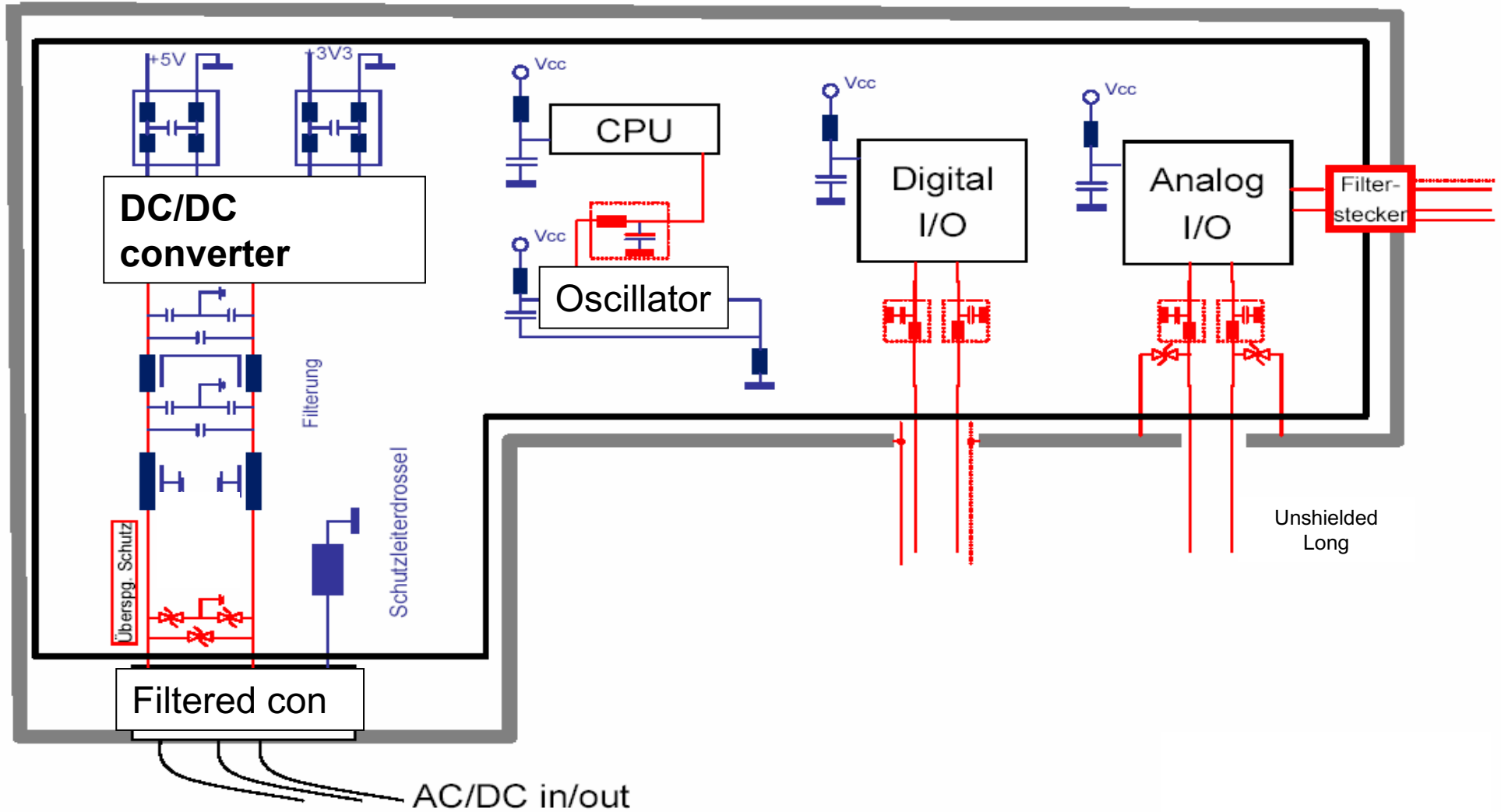



You can reach us:

Tel: +1-605-886-4385

Fax: +1-605-886-4486

midcom@we-online.com

www.we-online.com

