VICOR

Optimizer Based Loop Compensation Of Voltage Mode Buck Regulators

C. R. Swartz; Senior Principal Engineer/Manager /Senior Member IEEE Vicor Advanced Systems Design Engineering IEEE Power Seminar, Long Island, NY 2-NOV-2023

Seminar Roadmap

- The Synchronous Voltage Mode Control Buck Regulator
- The Voltage Mode Control Buck Regulator
- Relevant Waveforms
- Compensation Procedure Classical Approach
- Is there another way? The Optimizer Approach
- Summary
- Questions/Answers

VICOR

Synchronous VMC Buck Regulator





VMC Buck Regulator





Relevant Waveforms – Sync Buck 20A Load









Relevant Waveforms – Sync Buck 1A Load

VICOR

Relevant Waveforms – Sync Buck 1A Ctrl-Out





Relevant Waveforms – Buck 20A Load







Relevant Waveforms – Buck 1A Ctrl-Out

VICOR

Compensation Procedure

We must compensate the feedback loop for the continuous conduction mode case as the converter operates there during most of the load range and since there is a double pole in the output filter, it is the more complex case...



VICOR

VICOR



Determine the modulator gain:

D_{max} := 1

V_{ramp} := 1.0

Where:

Dmax = converter upper MOSFET maximum duty cycle. Vin = the input voltage under the condition tested. Vramp = the peak to peak value of the oscillator ramp for the PWM.

$$G_{mod}(f) := \frac{D_{max} \cdot V_{in}}{V_{ramp}}$$

$$G_{CO}(f) := G_{mod}(f) \cdot Gl(f)$$

VICOR



100

Place the second zero to be equal to the resonant frequency of the LC filter:

 $F_{77} = 1.301 \times 10^4$

$$F_{Z2} := \frac{1}{2 \cdot \pi \cdot \sqrt{L_{ind} \cdot (C_{out})}}$$

Place the first zero to be 75% of the second zero:

 $F_{Z1} := F_{Z2} \cdot 0.75$ $F_{Z1} = 9.759 \times 10^3$

Place the second pole to be 75% of the switching frequency: The first pole is at the origin with a Type 3 amplifier

 $F_{P2} := F_{sw} \cdot 0.75$ $F_{P2} = 3.75 \times 10^5$

Place the third pole to be 50% of the switching frequency:

 $F_{P3} := F_{sw} \cdot 0.5$ $F_{P3} = 2.5 \times 10^5$

50 $0.\log(|G_{type3}(f)|)$ $\operatorname{rg}(G_{\text{type3}}(f)) \cdot \frac{180}{\pi}$ - 50 -1001×103 1×10⁴ 1×10⁵ 1×10⁶ 100 1 10 f

So here is our compensation pole/zero placement strategy as of now.

VICUR

The Type 3 Error Amplifier:

Provides a 3 pole, 2 zero transfer function where one of the poles occurs at the origin. It should be used when there is small ESR in the output filter and the resulting zero is greater than the desired crossover frequency. It can be either an OPAMP or Transconductance Amplifier. We will use an OPAMP.



VICOR

18

+

Zeros/Poles

The transfer function for the type 3 error amplifier is.....

$$GEA(\mathbf{f}) := \frac{(1 + s(\mathbf{f}) \cdot R5 \cdot C2) \cdot [1 + s(\mathbf{f}) \cdot (R3 + R4) \cdot C4]}{s(\mathbf{f}) \cdot R3 \cdot (C2 + C3) \cdot (1 + s(\mathbf{f}) \cdot R4 \cdot C4) \cdot \left[1 + s(\mathbf{f}) \cdot R5 \cdot \left(\frac{C2 \cdot C3}{C2 + C3}\right)\right]}$$

The poles and zeros are symbolically:



or **19**



VICOR

Calculate the component values:

Since C4 affects both a pole and a zero and affects the midband gain, choose it in an arbitrary manner:

 $C4_{select} := 2.2 \cdot 10^{-9}$

Pick the crossover frequency:

Fcrossover := \$0000

Calculate R4 based on the frequency of the second pole:

 $R4_{calc} := \frac{1}{(2 \cdot \pi \cdot F_{P2} \cdot C4_{select})} \qquad \qquad R4_{calc} = 192.915$

Calculate R3 based on the frequency of the second zero:

 $R_{3}_{calc} := \frac{1}{(2 \cdot \pi \cdot F_{Z2} \cdot C_{4}^{4}_{select})} - R_{4}^{4}_{calc} \qquad R_{3}_{calc} = 5.367 \times 10^{3}$

Calculate R6 to obtain the correct output voltage:

$$R6_{calc} := \frac{R3_{calc} \cdot V_{ref}}{V_{out} - V_{ref}} \qquad R6_{calc} = 5.367 \times 10^{3}$$

Calculate R5 to set the mid band gain for the crossover frequency:

$$R5_{calc} := \frac{2 \cdot \pi \cdot F_{crossover} \cdot L_{ind} \cdot C_{out} \cdot V_{ramp}}{V_{in} \cdot C^4_{select}} \qquad R5_{calc} = 2.848 \times 10^3 \qquad (C2023 \, Vicor) \qquad 2$$



Calculate C2 based on the first zero and R5:

 $C2_{calc} \coloneqq \frac{1}{2 \cdot \pi \cdot R5_{calc} \cdot F_{Z1}} \qquad C2_{calc} = 5.725 \times 10^{-9}$

Finally, calculate C3 based on the third pole and R5:

 $C_{3}_{calc} := \frac{1}{2 \cdot \pi \cdot R_{5}_{calc} \cdot F_{P3}}$ $C_{3}_{calc} = 2.235 \times 10^{-10}$



VICOR

©2023 Vicor



VICOR

©2023 Vicor

VICOR

Is There Another Way?

One can see the classical approach is well established and works fairly well. However, it can be math intensive and still require some iteration as there are tradeoffs that must be applied due to available components. So you might ask, is there another way?

Let's ask the simulator!

Optimization

- Is a type of goal seeking algorithm simulation where components are given initial values and the simulator is given a goal. The goal could be measured data or a curve. All components are parametric in nature.
- Components are adjusted until the error between the result and the goal is reduced to a minimum.
- Optimization can provide significant insight into a chosen design topology.
- Can be done using AC, DC or transient analysis





VICOR

©2023 Vicor



VICOR



VICOR



THIS CIRCUIT WILL GENERATE MY DESIRED REFERENCE FOR THE OPTIMIZER CIRCUIT. I WILL FEED THE GAIN AND PHASE DATA VIA FILE INTO THE OPTIMIZER CIRCUIT. THIS CIRCUIT EMULATES THE MODULATOR AND OUTPUT FILTER GAIN AND THEN INPUTS IT INTO THE LAPLACE BLOCK. THE LAPLACE BLOCK IS SET UP AS A TYPE 3 AMPLIFIER WITH TWO POLES AND TWO ZEROS WITH A POLE AT THE ORIGIN. IN THE OPTIMIZER SCHEMATIC, I WILL REPLACE THE LAPLACE BLOCK WITH AN AMPLIFIER MODELED BY A VCVS WITH AN OPEN LOOP GAIN OF 100K. I WILL USE THE OPTIMIZER TO CALCULATE THE VALUES NEEDED TO MATCH THE AC RESPONSE OF THE REFERENCE CIRCUIT.



Frequency, gain and phase data is simulated based on only the pole and zero locations and adjustment of the gain to match my desired crossover frequency and phase margin. This data is saved to a text file directly from the bode plot.

VICOR

©2023 Vicor



THIS CIRCUIT IS BEING OPTIMIZED SO THAT THE BODE PLOT FROM THIS CIRCUIT MATCHES THE REFERENCE PLOT. THE IDEA IS TO LET SIMETRIX DETERMINE THE VALUES OF THE COMPRENSATOR BASED ON THE LAPLACE BLOCK. THE PARTS IN CURLY BRACES ARE THE ONES TO BE CALCULATED BY THE OPTIMIZER. THE FILE THAT IS USED TO MATCH THE CURVE COMES FROM THE OTHER CIRCUIT.





THIS CIRCUIT IS BEING OPTIMIZED SO THAT THE BODE PLOT FROM THIS CIRCUIT MATCHES THE REFERENCE PLOT. THE IDEA IS TO LET SIMETRIX DETERMINE THE VALUES OF THE COMPENSATOR BASED ON THE LAPLACE BLOCK. THE PARTS IN CURLY BRACES ARE THE ONES TO BE CALCULATED BY THE OPTIMIZER. THE FILE THAT IS USED TO MATCH THE CURVE COMES FROM THE OTHER CIRCUIT.





THIS CIRCUIT IS BEING OPTIMIZED SO THAT THE BODE PLOT FROM THIS CIRCUIT MATCHES THE REFERENCE PLOT. THE IDEA IS TO LET SIMETRIX DETERMINE THE VALUES OF THE COMPENSATOR BASED ON THE LAPLACE BLOCK. THE PARTS IN CURLY BRACES ARE THE ONES TO BE CALCULATED BY THE OPTIMIZER. THE FILE THAT IS USED TO MATCH THE CURVE COMES FROM THE OTHER CIRCUIT.



Circuit D:\cswartz\Seminar_IEE	E_Nov2023\TYPE3_OP	MIZER.sxsch		Detach Open
Parameters			Optimiser Options	
Name Initial Value 1 R4 1k 2 C4 2.2n 3 C3 7.5p 4 C2 47p 5 R5 1k	Minimum Value 1 10p 1p 10p 10 10	Maximum Value 00k u u u 00k	Algorithm Absolute tolerance Relative tolerance Enable iteration lim Show progress message Write HTML Report	NELDER_MEAD Show experimental 1n 1n it 5000

VICOR







VICOR







Here I selected R3 to be 10k and R6 to be 1k. With proper separation of the zero and pole I can get a very good match as to my desired response. So the Optimizer method shows that an OTA does not have the same flexibility as an OPAMP when used as a type 3 amplifier configuration with low output voltage. This would work well for a higher voltage output like 10V or 12V. The Optimizer provides good insight into design limitations and quickly.

©2023 Vicor



Here is the target response (red) vs the type 3 gm amplifier designed by the Optimizer with R3 = 10k and R6 = 1k to show what can be achieved.

©2023 Vicor

Summary

Today we have discussed:

- Basic waveforms and transfer functions of the buck regulator using equations and SIMPLIS
- Basic loop compensation of a buck regulator using a classical approach to calculate component values.
- Use of a simulation based optimizer (SIMetrix Optimizer) to calculate all of the component values for both OPAMP based and OTA based type 3 amplifiers with data generated by knowing pole and zero locations and a gain term.
- The optimizer approach has flexibility to work with other topologies and amplifier configurations.
- That the optimizer approach can add significant insight to the chosen design topology and can aid in the selection of the proper choice of compensator.



References

SIMetrix/SIMPLIS(www.simplistechnologies.com)Powersim/Altair(www.altair.com)Infineon Application Note AN-1162 (www.infineon.com)



VICOR

Thank you

Questions?

The information contained herein and presented by Vicor is for general informational purposes only. Vicor assumes no responsibility for inaccuracies, errors or omissions in this presentation. Users of power supply products remain responsible for the design, testing and operational safeguards related to such use.

PSIM[®] is a registered trademark of Altair Inc. SIMPLIS is a registered trademark SIMPLIS Technologies, Inc. SIMetrix is a registered trademark SIMetrix Technologies Ltd

All other trademarks, product names, logos and brands are property of their respective owners.