



# Primer on Power Supply Topologies

Lee Sirio


Director of Engineering

11/2/23

*Inspiring Innovation*




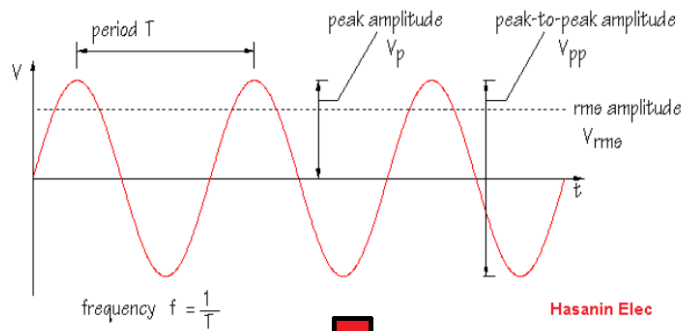
# Transformer Coupled Rectifier Supply (AC to DC)




Hasanin Elec


AC INPUT

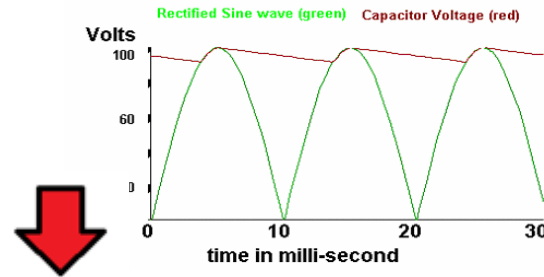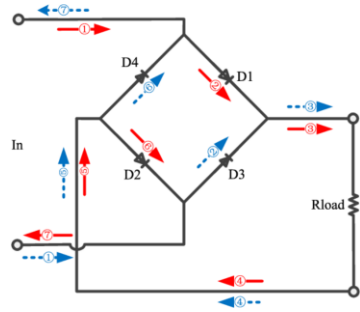


UNREGULATED  
"MIDBUS"

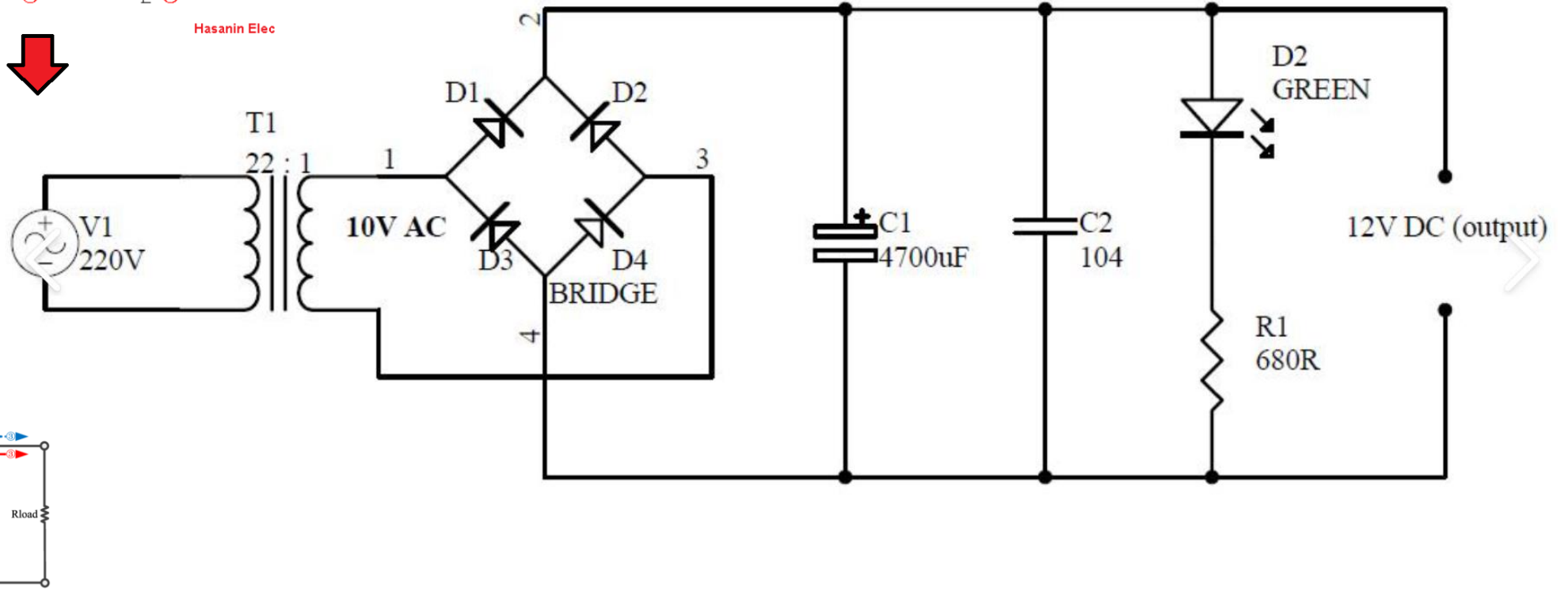
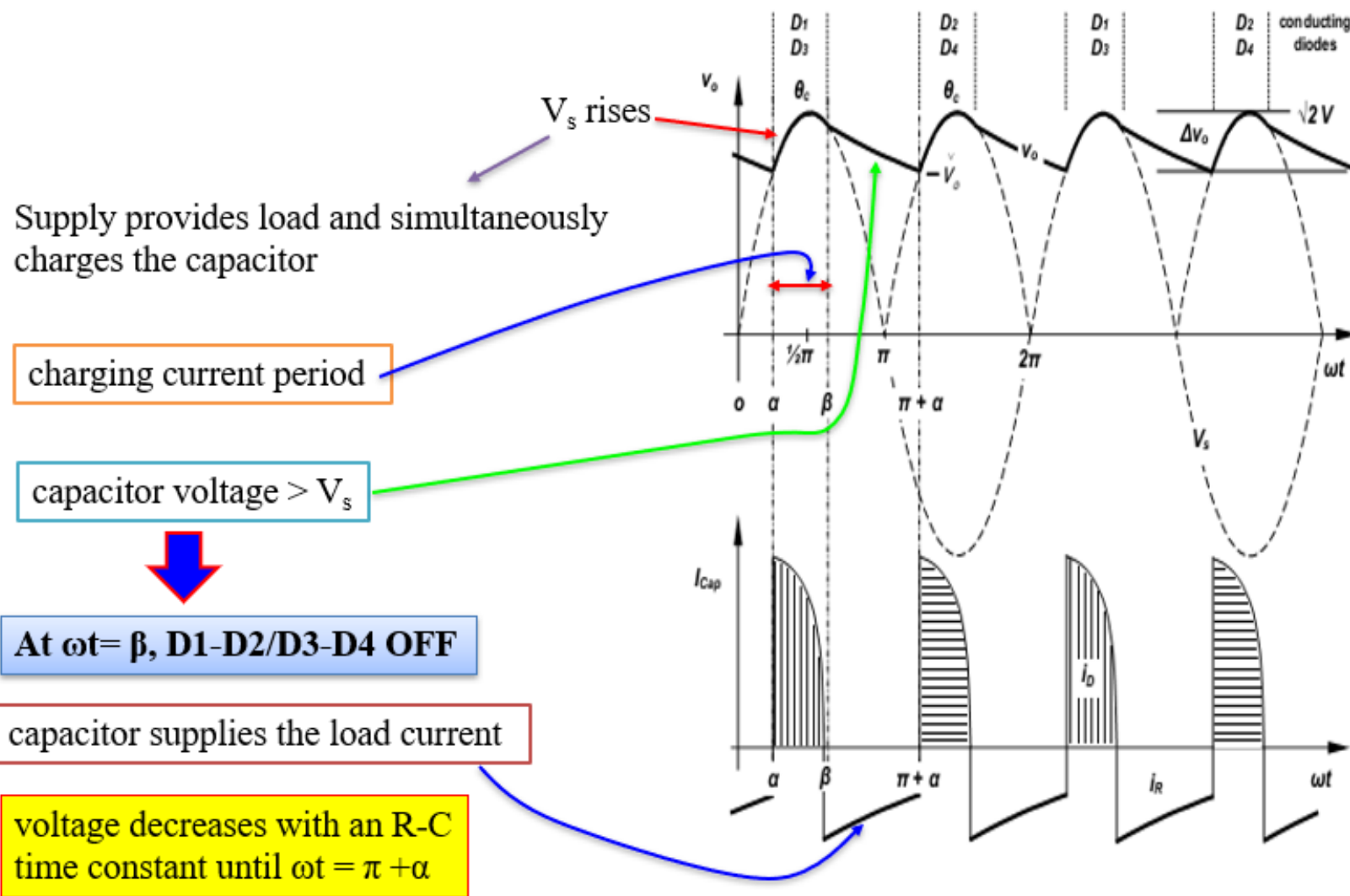
### Single-phase full-wave bridge rectifier circuit with a C-filter





## Development of Ripple Expressions

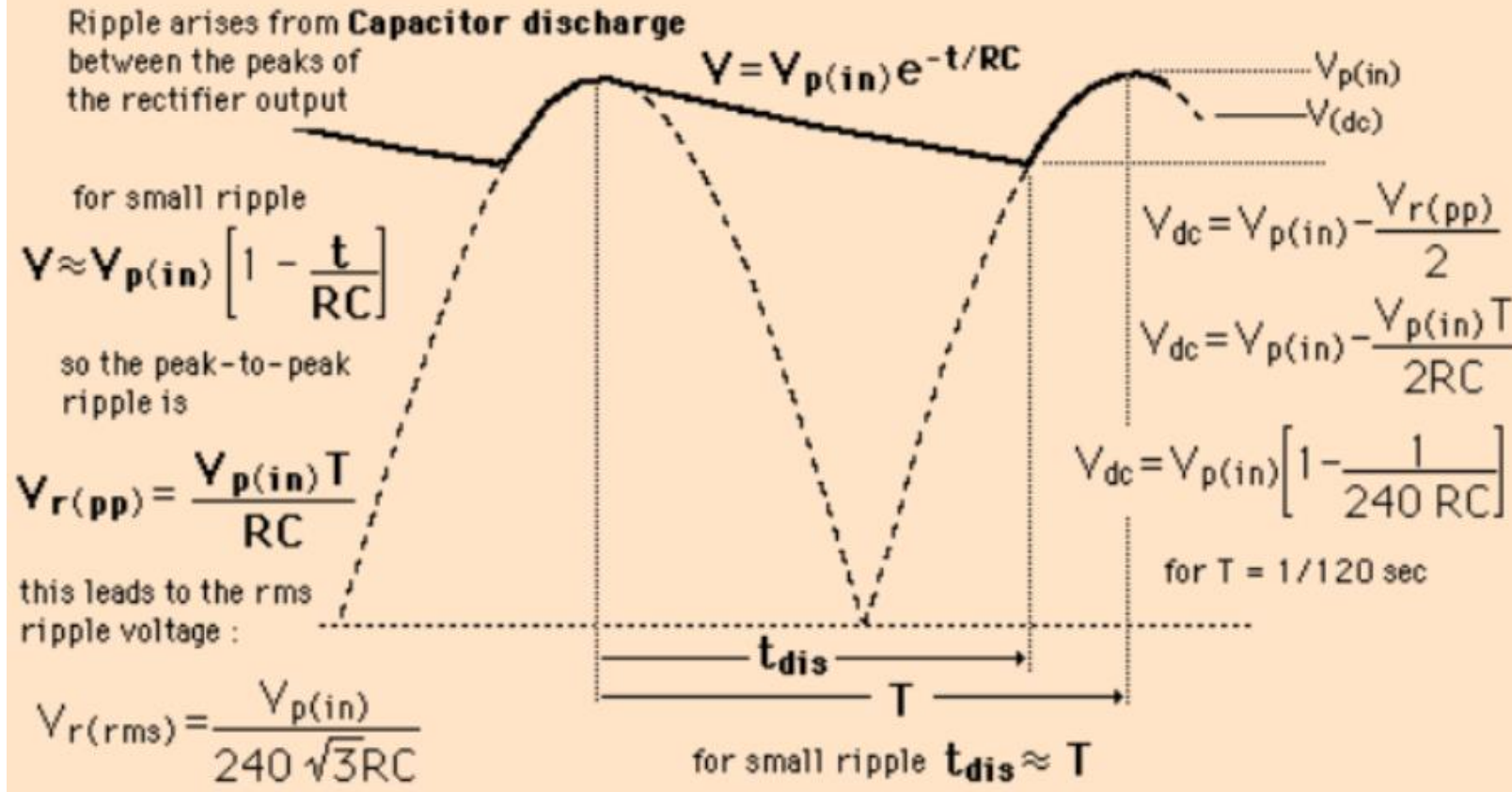




## TRANSFORMER COUPLED VOLTAGE DOUBLER

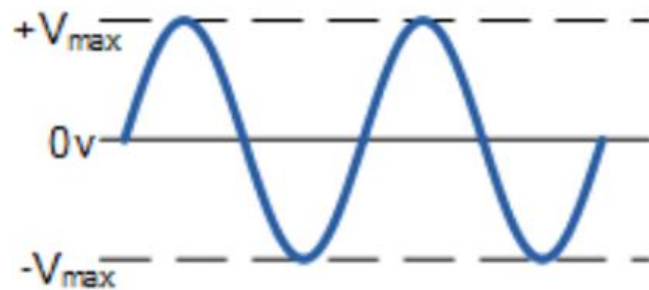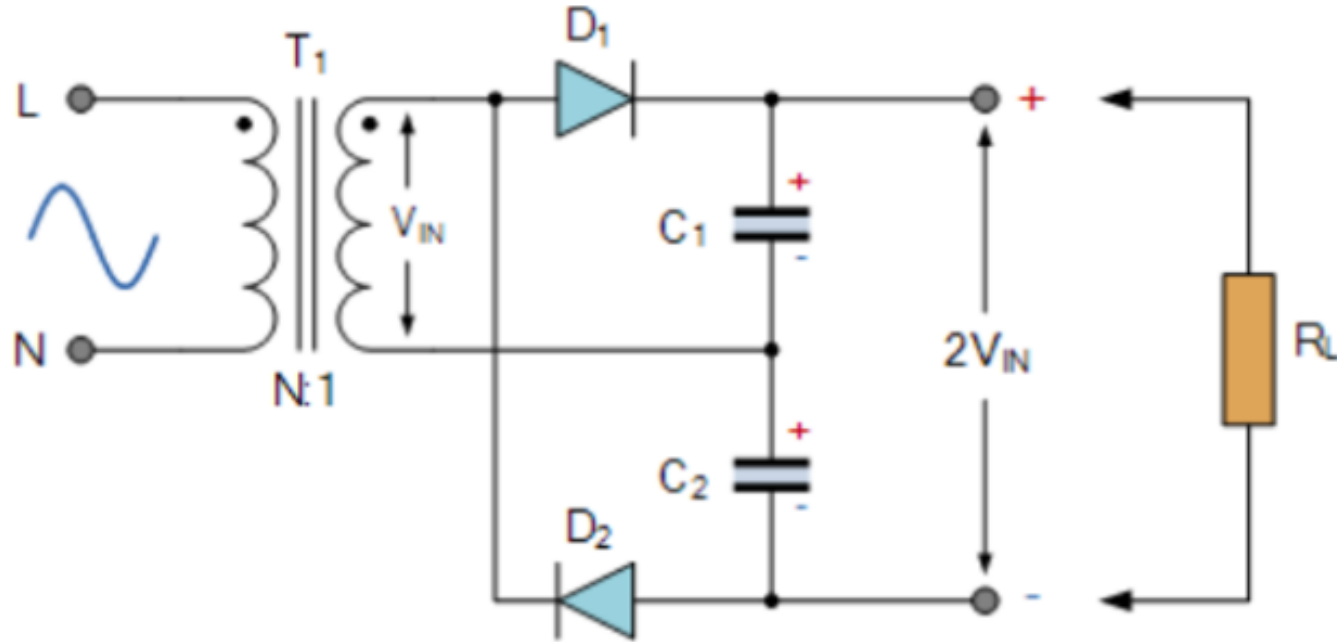


AC Input Waveform

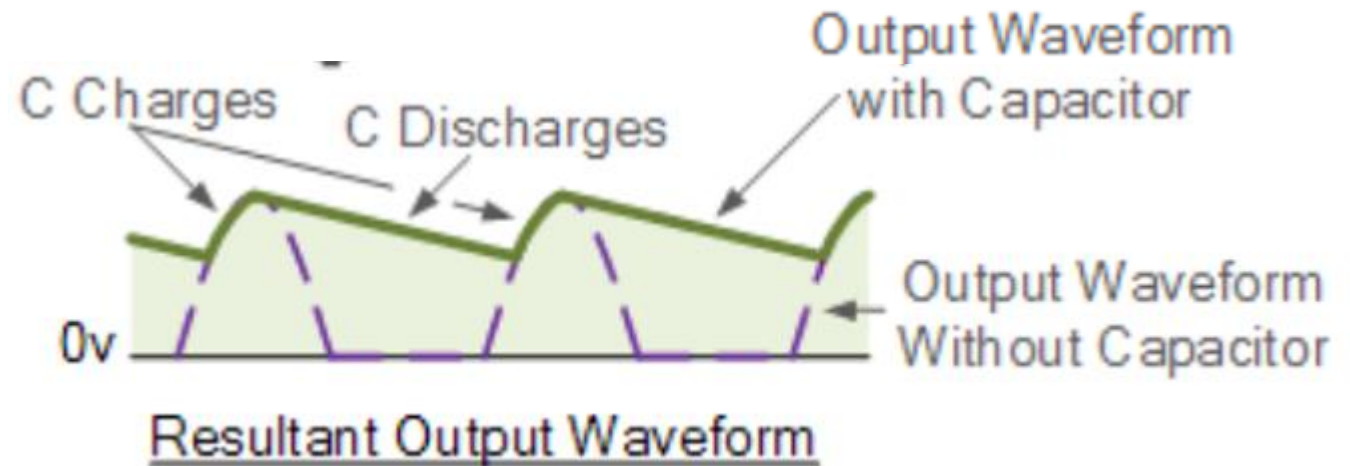

Resultant Output Waveform


## Voltage Doubler

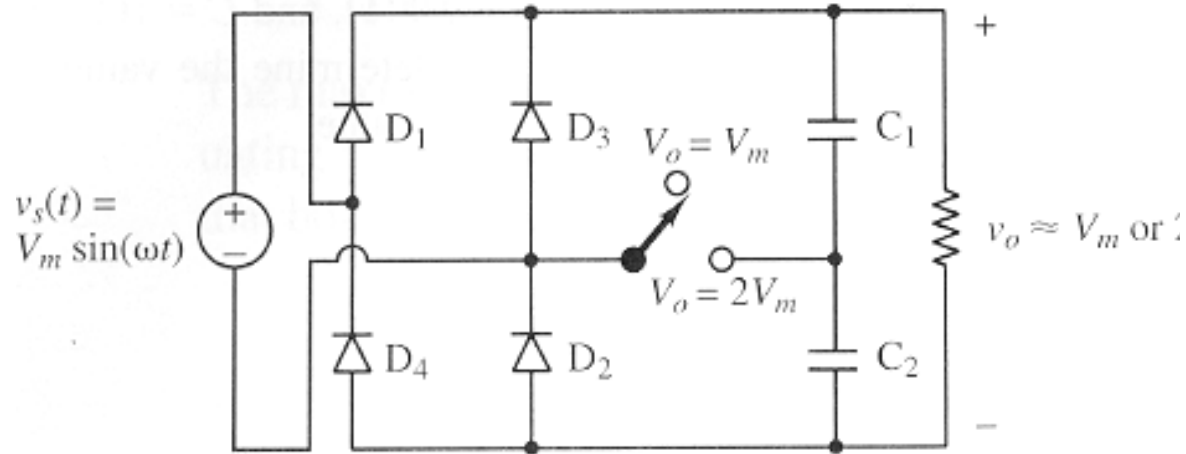

115/230  
SWITCH



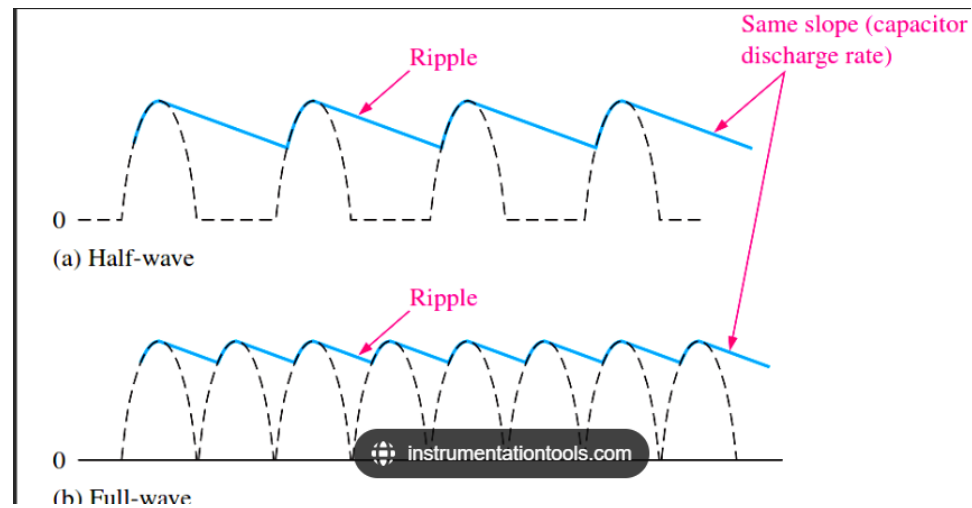Dual voltage rectifier = full-wave rectifier (sw. open) + voltage Doubler (sw. closed)



**US Voltages 90VRMS-132VRMS**


**Switch closed**  $V_o = 2 * \text{SQRT}(2) * \text{VRMS}$   
= 254V DC to 373 VDC

**Europe 230V+/- 23V VRMS**


**Switch open**  $V_o = \text{SQRT}(2) * \text{VRMS}$   
= 293V DC to 348 VDC
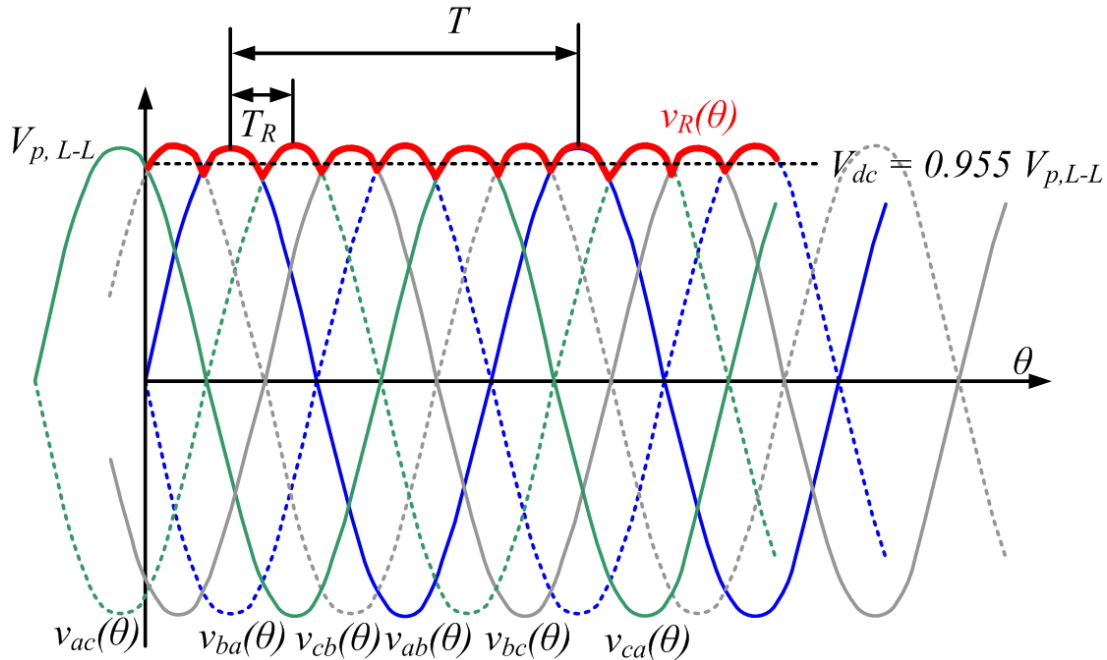
# Three-phase Bridge Rectifier with Resistive Load

- The output voltage ripple frequency is six times that of the input voltage waveforms (**60 degree intervals \* 6 per cycle**).



**6 DIODES!**

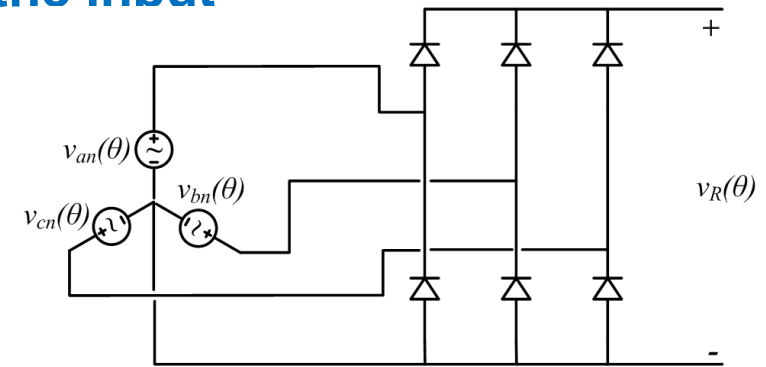

Supply Voltages Phase to Neutral (Peak):

$$v_a = \sqrt{2} V_{PH} \sin(\omega t)$$


$$v_b = \sqrt{2} V_{PH} \sin(\omega t - 2\pi / 3)$$

$$v_c = \sqrt{2} V_{PH} \sin(\omega t - 4\pi / 3)$$

$$V_{dc} = 0.955 * \text{SQRT}(6) * 115V \text{ RMS} = 270VDC$$


$$V_{dc} = \frac{1}{T_R} \int_0^{T_R} v_R(t) dt = \frac{V_{p,L-L}}{2\pi / 6} \int_{\pi/3}^{2\pi/3} \sin(\theta) d\theta = \frac{3V_{p,L-L}}{\pi} = 0.955V_{p,L-L} = \frac{3\sqrt{3}V_{p,L-n}}{\pi} = 0.955 * \text{SQRT}(6) * V_{RMS} (L-N)$$

- Capacitive + Resistive Load

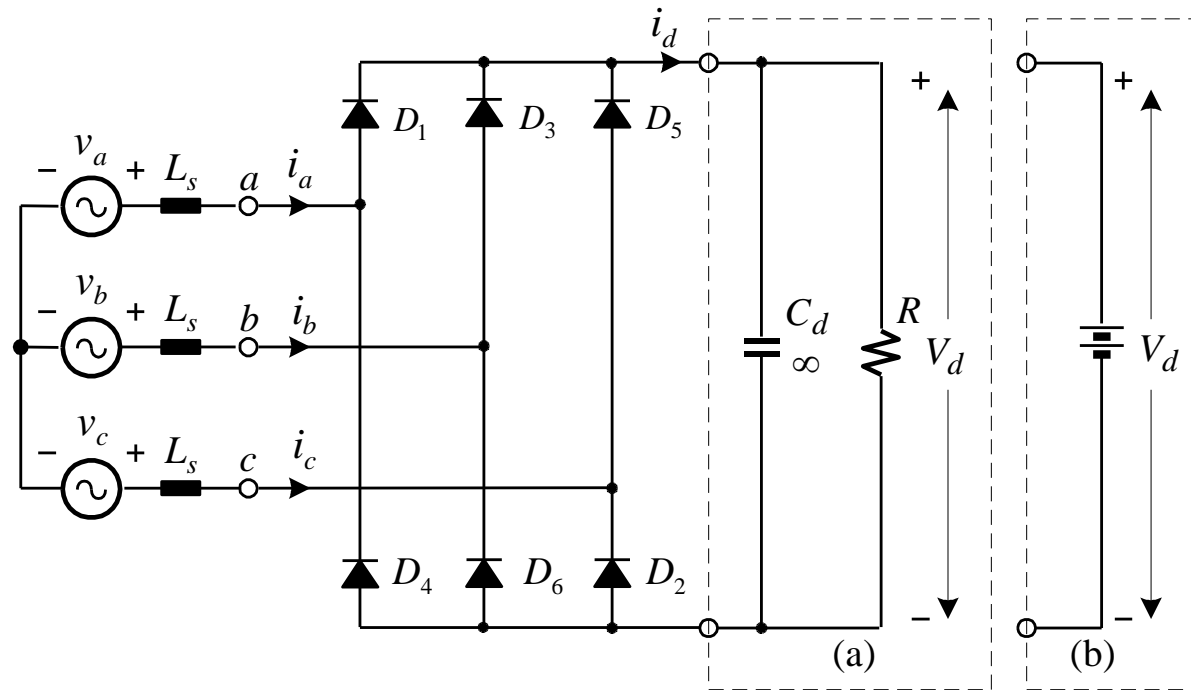

Assumption:
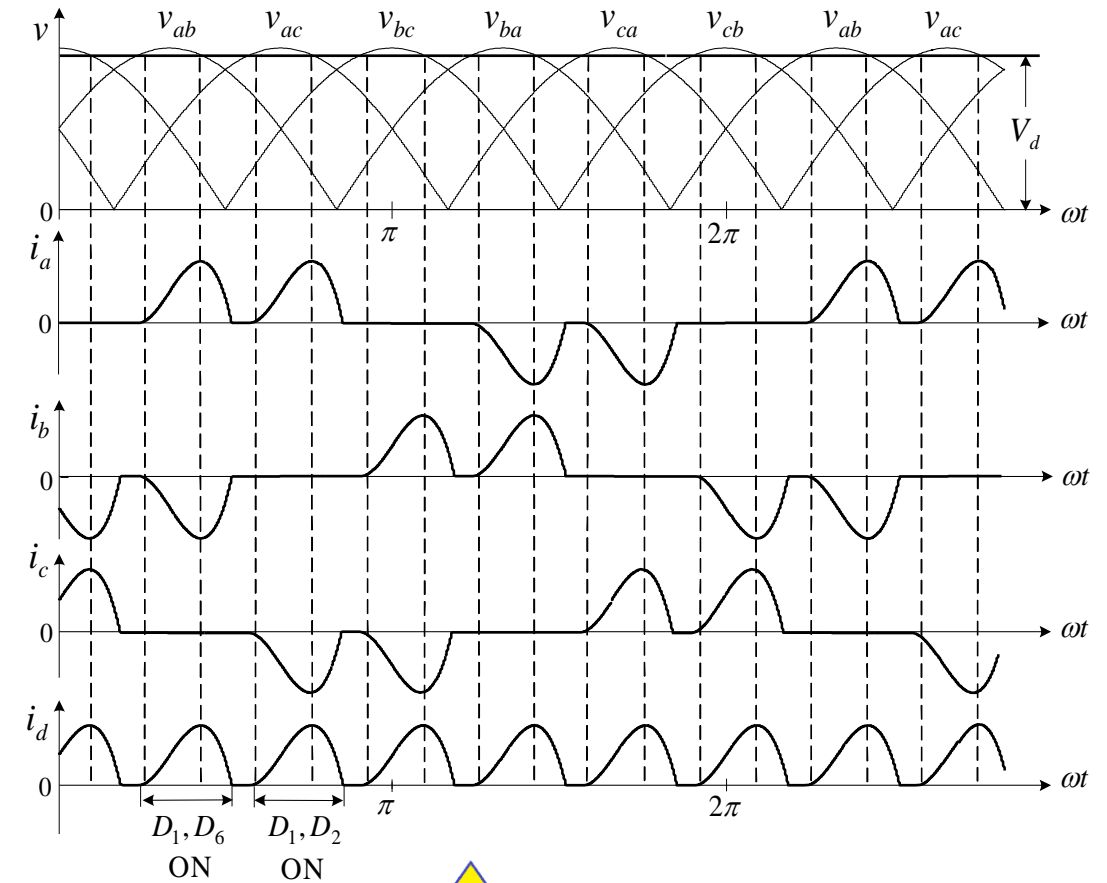
$$C_d = \infty \Rightarrow V_d = \text{constant}$$



Input Current Looks like a sinewave cap




# ***Multi-pulse Diode Rectifiers***

## Why Use Multi-pulse Diode Rectifiers?

- To reduce line current THD;
- To improve input power factor; and
- To avoid semiconductor devices in series.

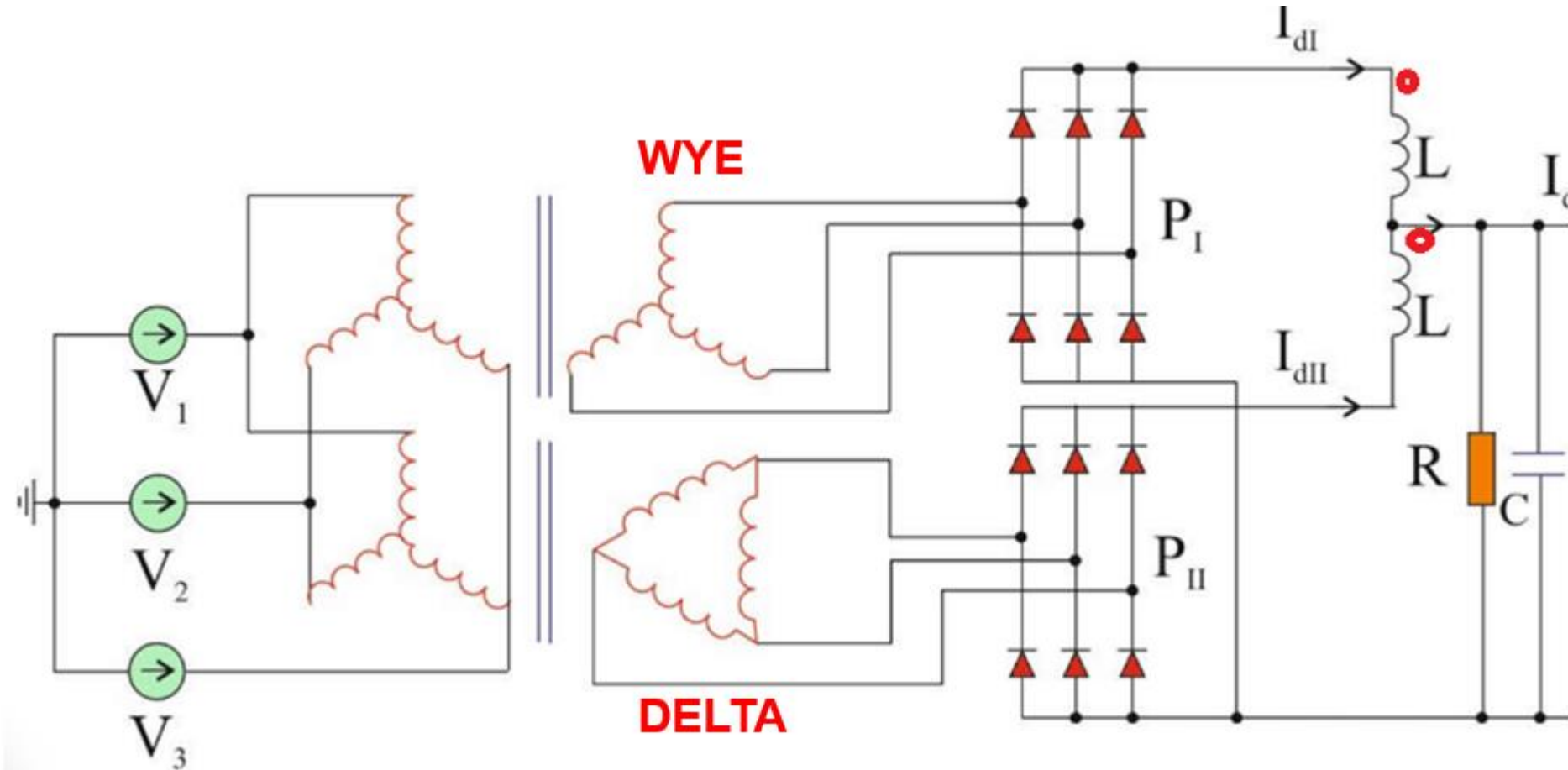
## Three Phase Transformer Rectifier Supply

- The output voltage ripple frequency is 12 times that of the input voltage waveforms.




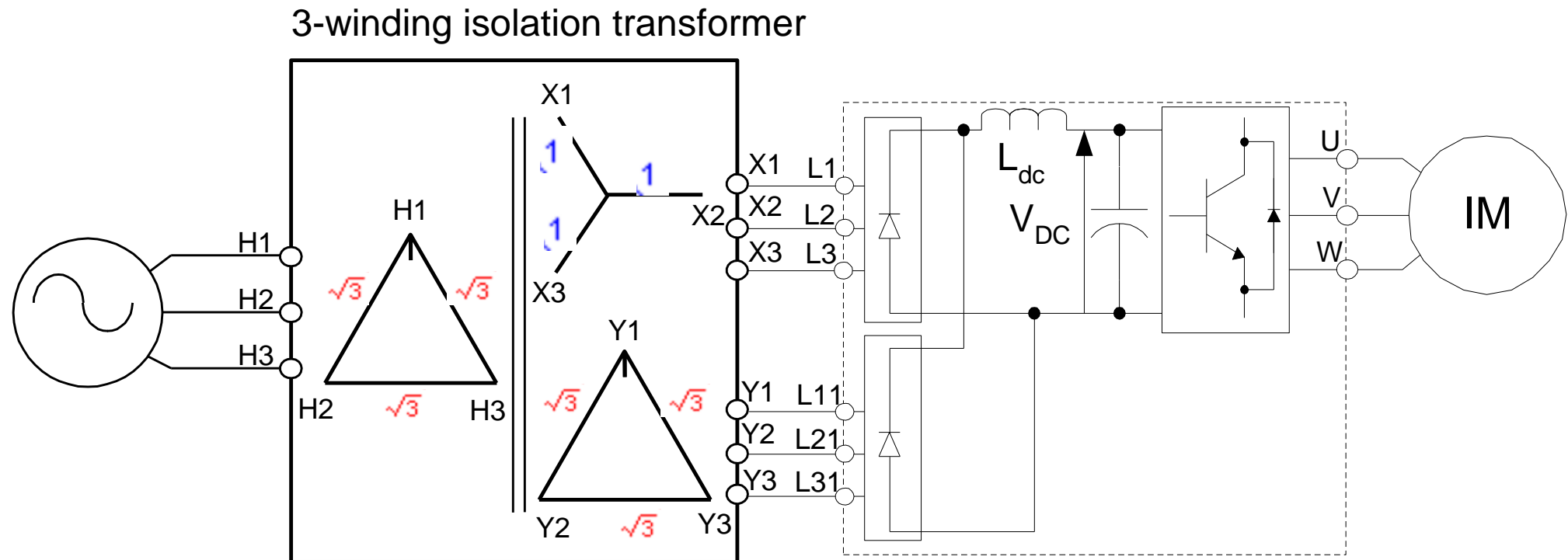
# Three Winding 12-pulse Scheme (Transformer Rectifier)

- Rated for full power operation – bulky but ONLY option when input is medium voltage and drive is of low voltage rating (very high power applications)



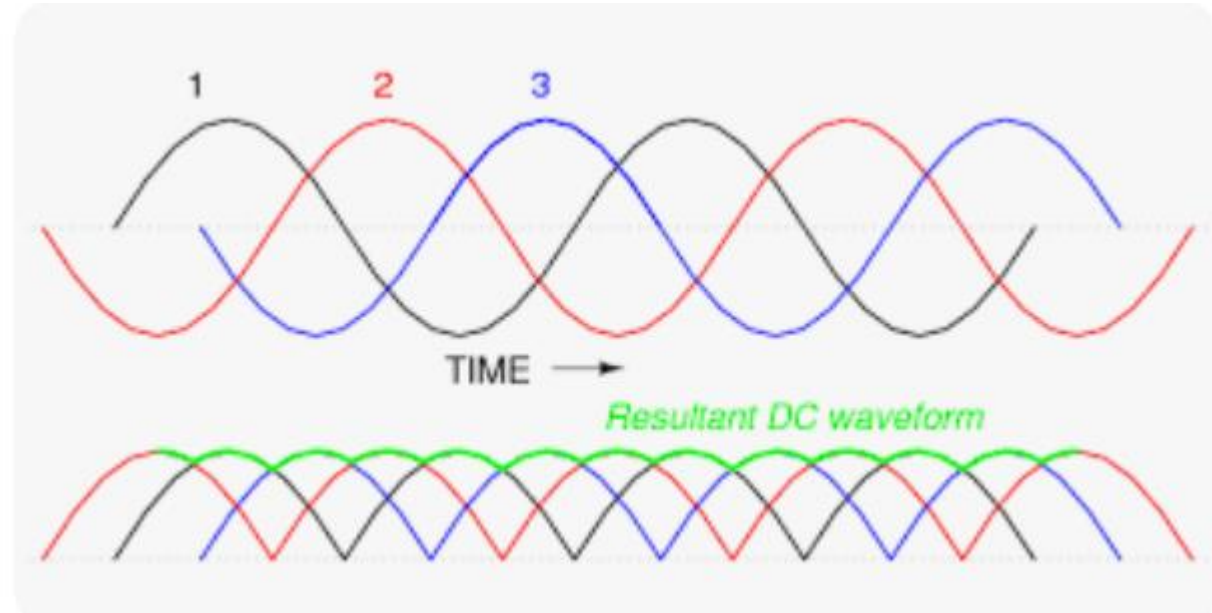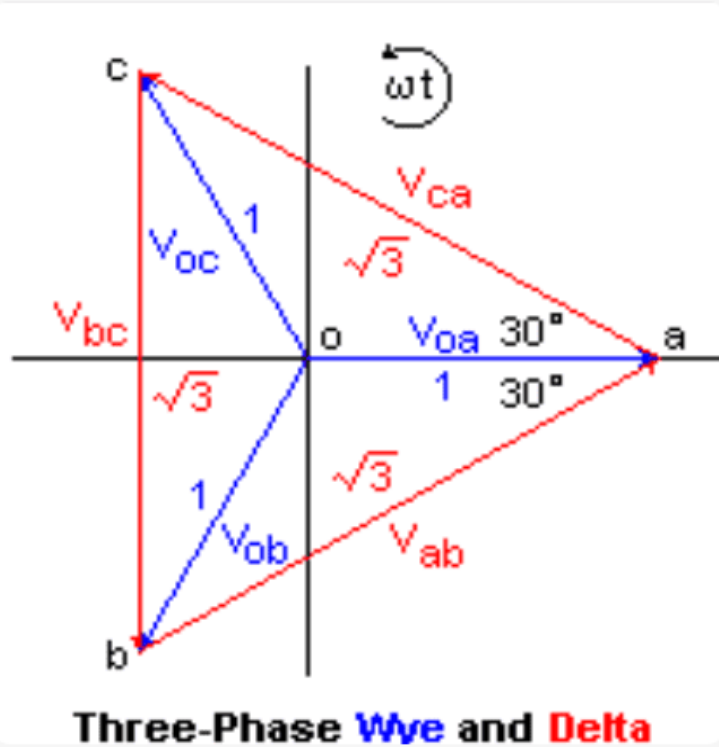
## 30 Degree Phase Shift between Delta and Wye



**\*\*With turns ratio Equalized**

Line-to-neutral voltages are in blue and line-to-line voltages in red. Note that the magnitude of the line-to-line is  $\sqrt{3}$  times larger, and  $\pm 30$  degrees different in phase compared to line-to-neutral.

# Three Winding 12-Pulse Waveforms

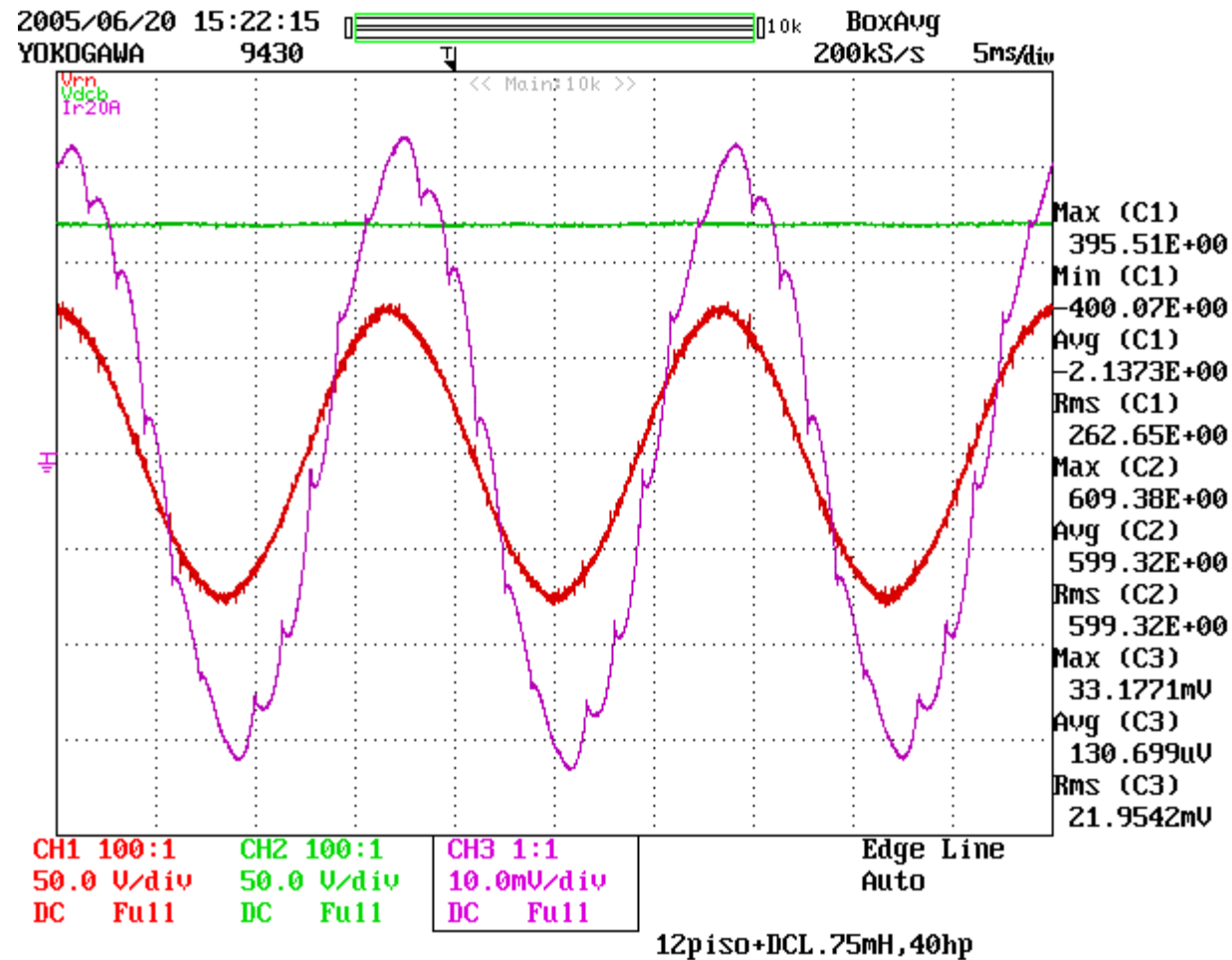


Load= 40hp  
THD= 13.4%




## Example: Three Phase 6-PULSE SCR Rectifier Supply (Alpha=30 degrees)


3 phase full wave controlled rectifier

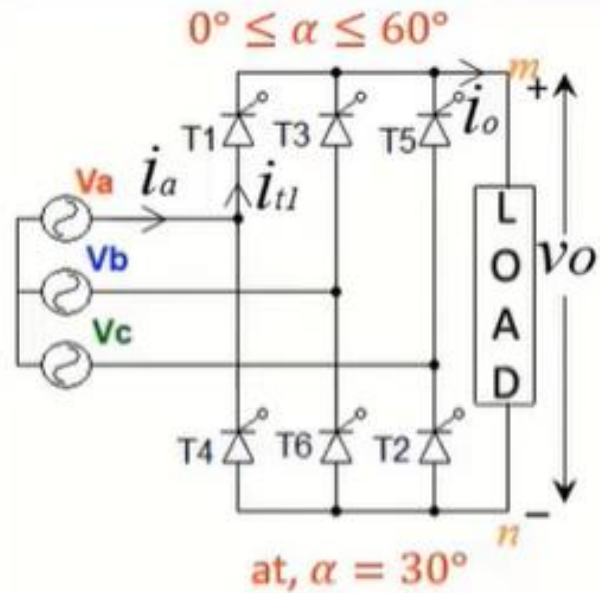

ALPHA= "Firing Angle"

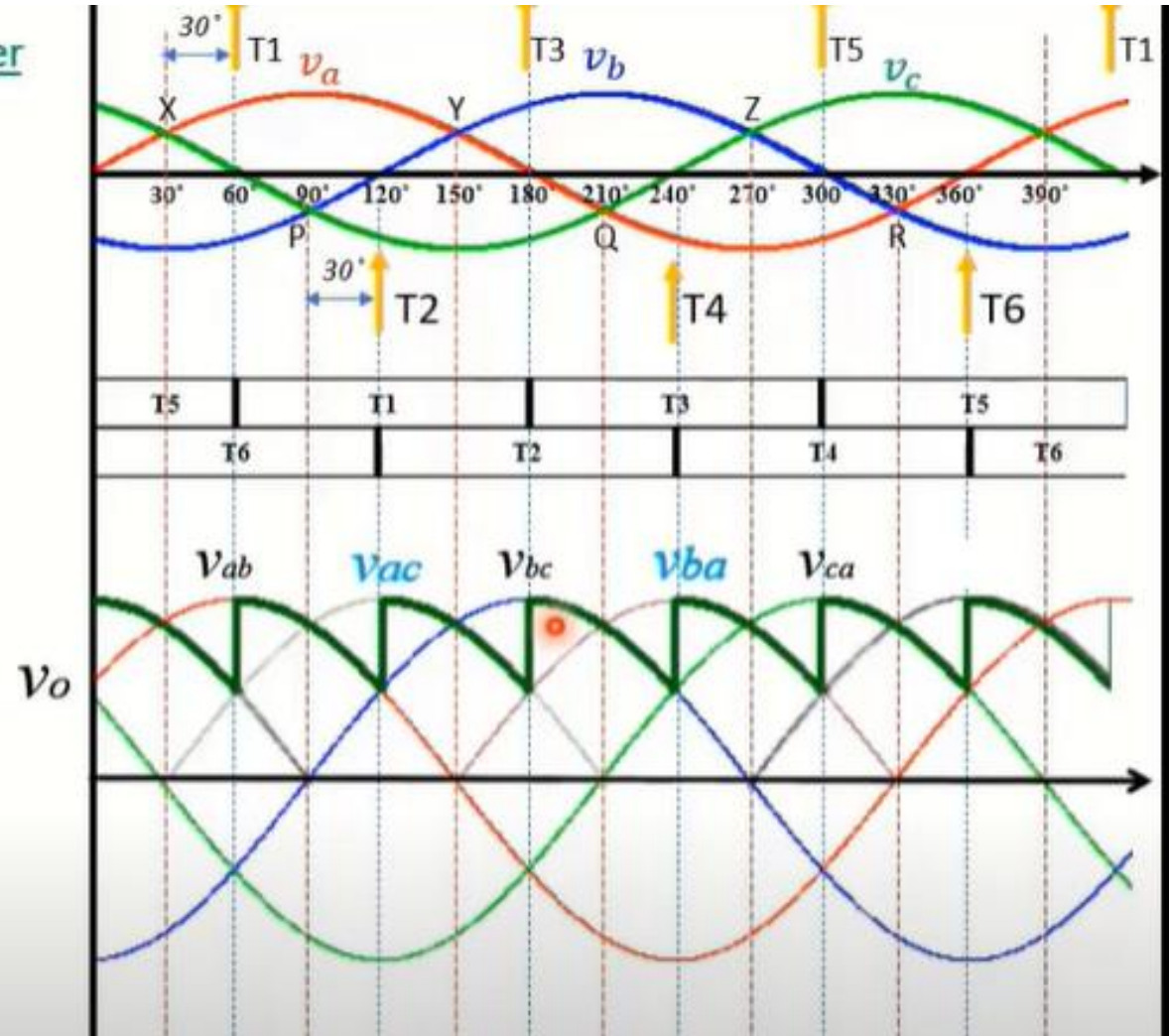

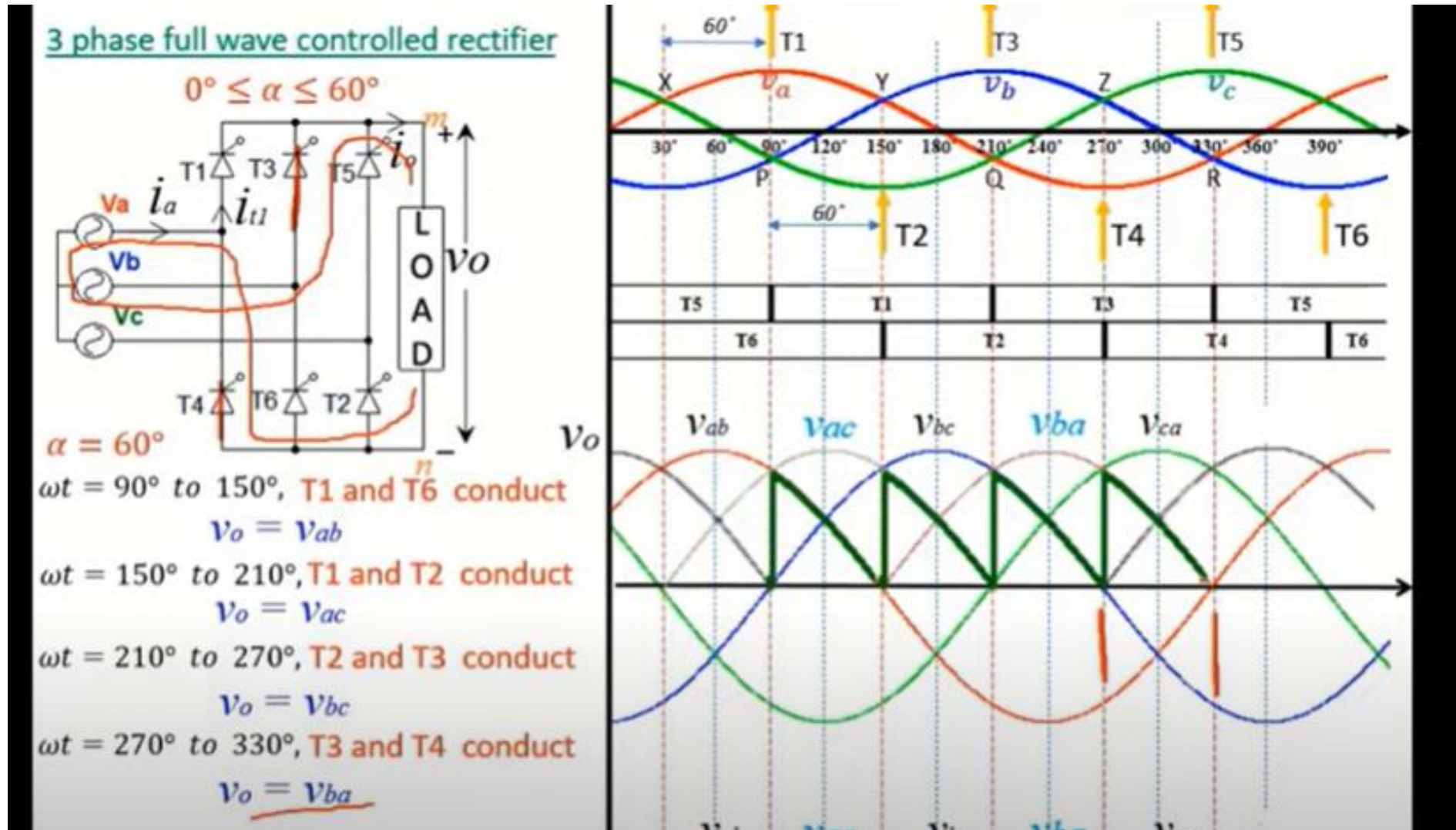
# Three Phase 6-PULSE SCR Rectifier Supply (Alpha=60 degrees)



# Programmable Three Phase 12-Pulse SCR Supply (MATLAB)

## Model

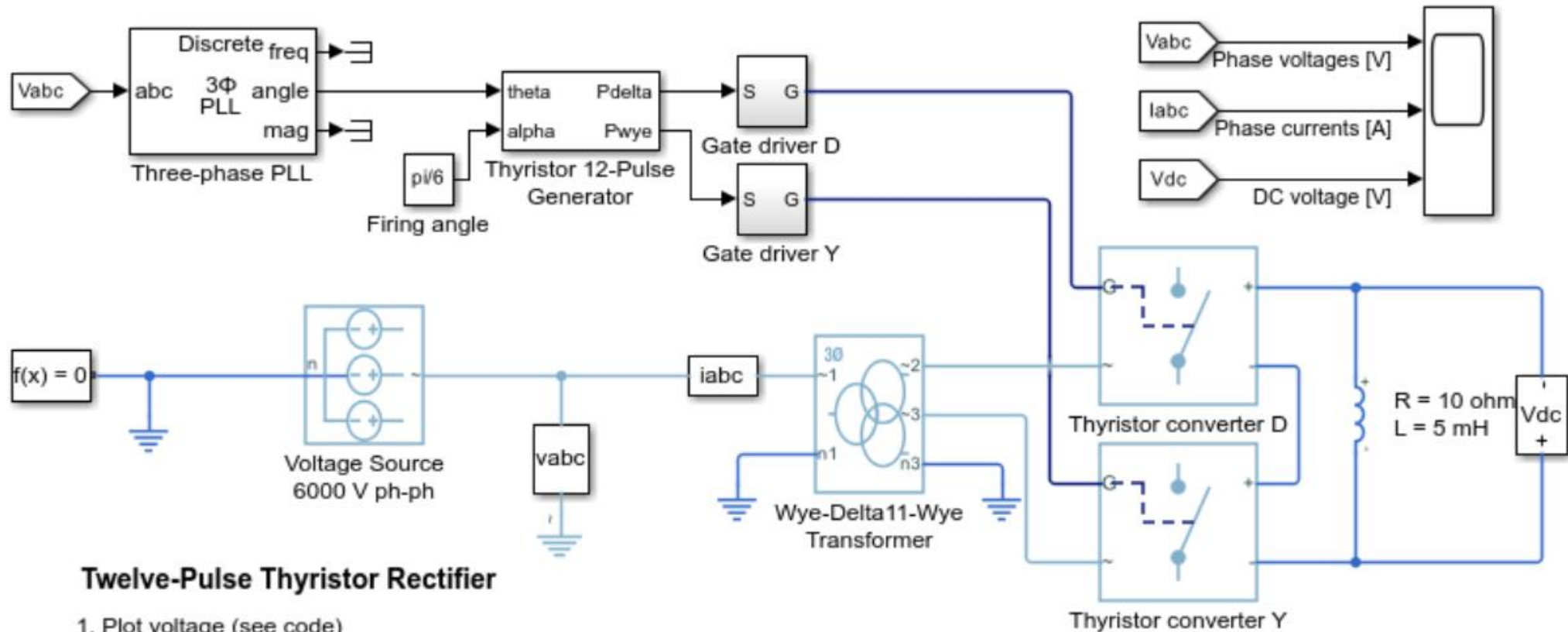


### Twelve-Pulse Thyristor Rectifier

1. Plot voltage (see code)
2. Explore simulation results using Simscape Results Explorer
3. Learn more about this example

Copyright 2015-2023 The MathWorks, Inc.


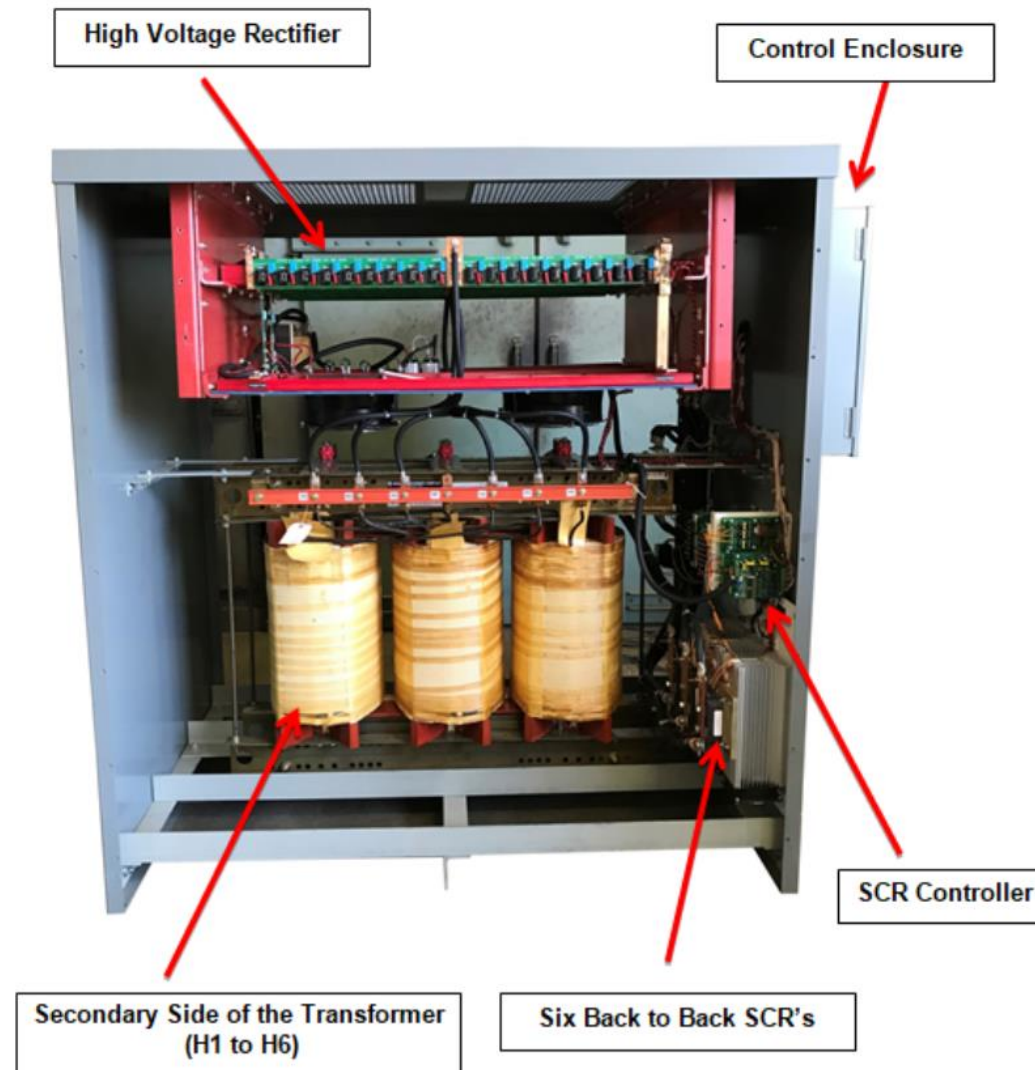
## Example: Three Phase 6 Pulse SCR Rectifier Supply



# ***Linear Supplies***

## Why Use Linear Supplies?

- Simplicity
- Low Noise
- Reliability
- Low Cost
- Feedback Loop: Easy to Control

## Disadvantages?


- Poor SWAP (Size, Weight and Power)
- Poor Efficiency




# Low Efficiency of Linear Regulators
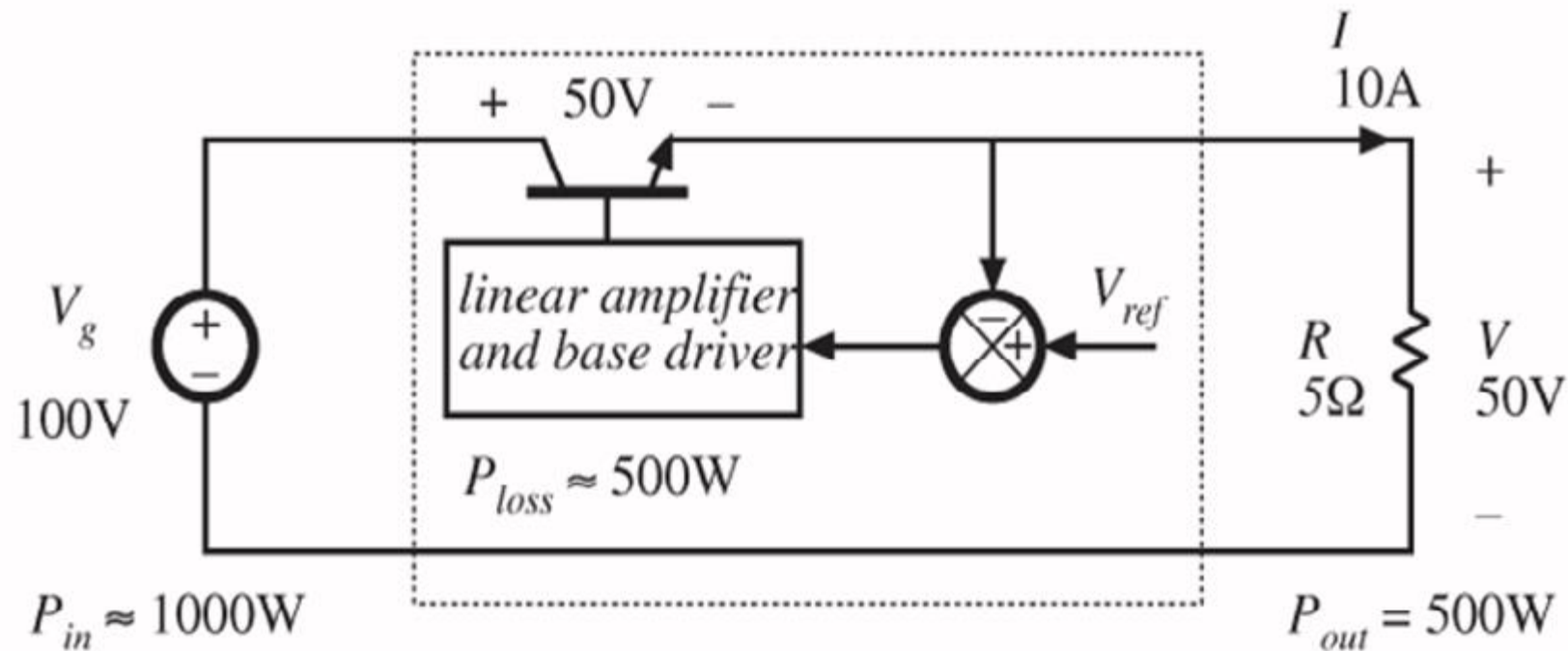
## Dissipative realization

Series pass regulator: transistor operates in active region



# Introducing the Switch-Mode Supply

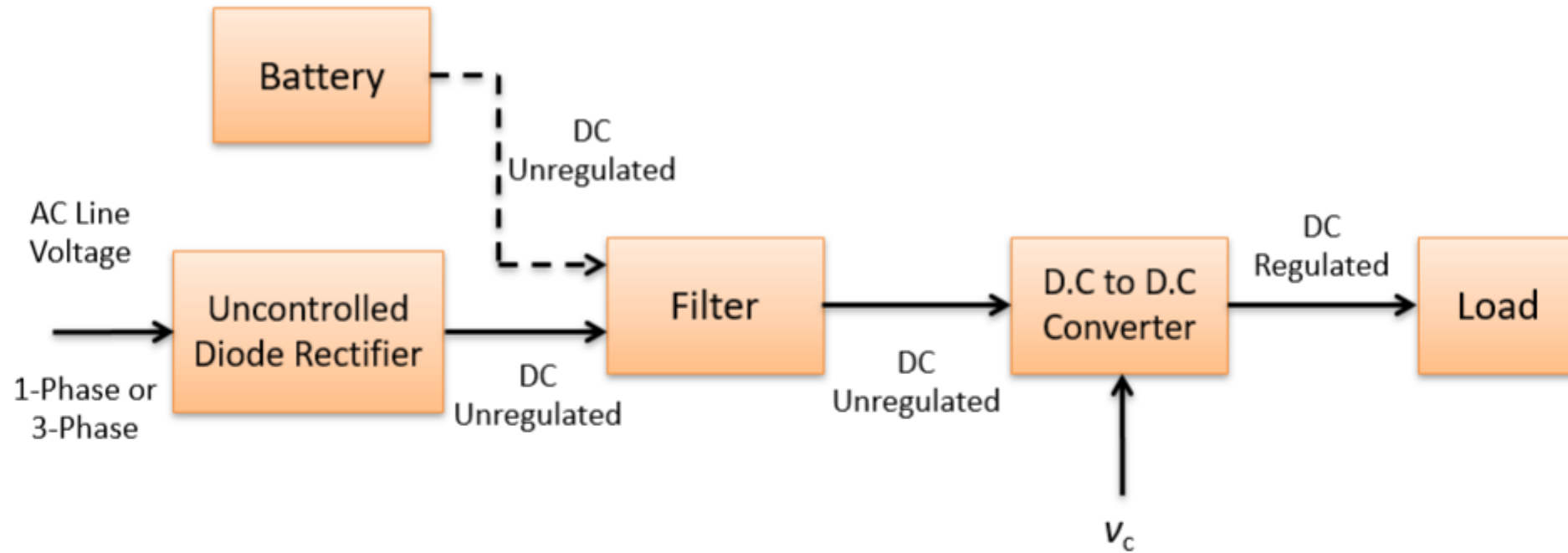


**D.C to D.C Converter System**

# Typical Switch-mode Supply Topology Components
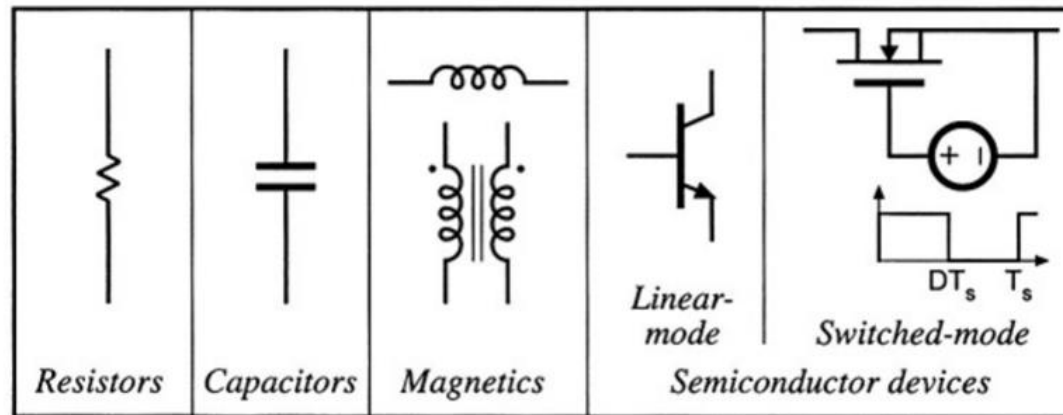
## Efficiency & Power Losses

- The various conventional circuit elements are illustrated in Following figure.



- The available circuit elements fall broadly into the classes of resistive elements, capacitive elements, magnetic devices including inductors and transformers, semiconductor devices operated in the linear mode and semiconductor devices operated in the switched mode.

# Maxwell's Equations

$$\oint_S \mathbf{E} \cdot d\mathbf{A} = \frac{q}{\epsilon_0} \quad \text{Gauss's law (electric)} \Rightarrow \text{electrostatic case}$$

~~$$\oint_S \mathbf{B} \cdot d\mathbf{A} = 0 \quad \text{Gauss's law in magnetism} \quad \text{Don't need}$$~~

Maxwellian Electrodynamics ↓


$$\underbrace{\oint \mathbf{E} \cdot d\mathbf{s}}_{\text{volts}} = - \frac{d\Phi_B}{dt} \quad \text{Faraday's law} \Rightarrow V = L \cdot dI/dt$$

$$\oint \mathbf{B} \cdot d\mathbf{s} = \mu_0 I + \epsilon_0 \mu_0 \frac{d\Phi_E}{dt} \quad \Rightarrow I = C \cdot dV/dt \quad \text{Ampere-Maxwell law}$$

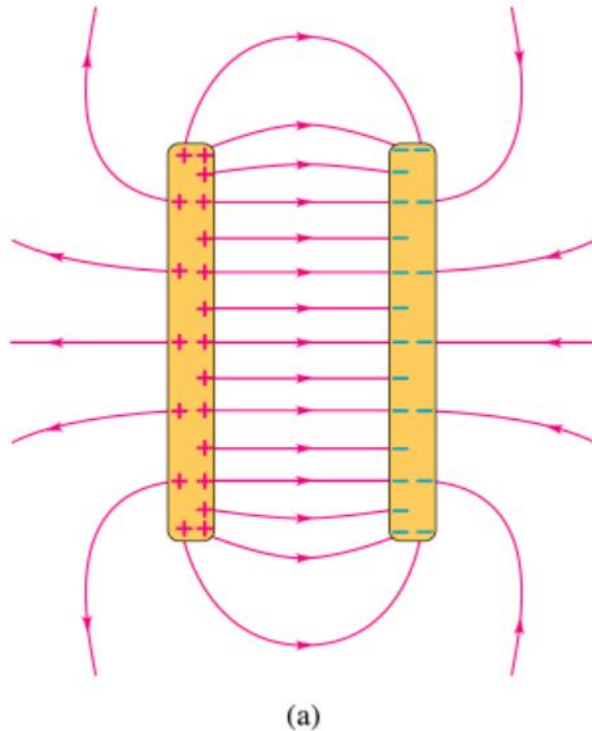
# Basic Physics of a Capacitor

GAUSS'S LAW

$$\oint_{S_1} \vec{E} \cdot d\vec{A} = EA = \frac{\sigma A}{\epsilon_0}$$



Copyright © Addison Wesley Longman, Inc.

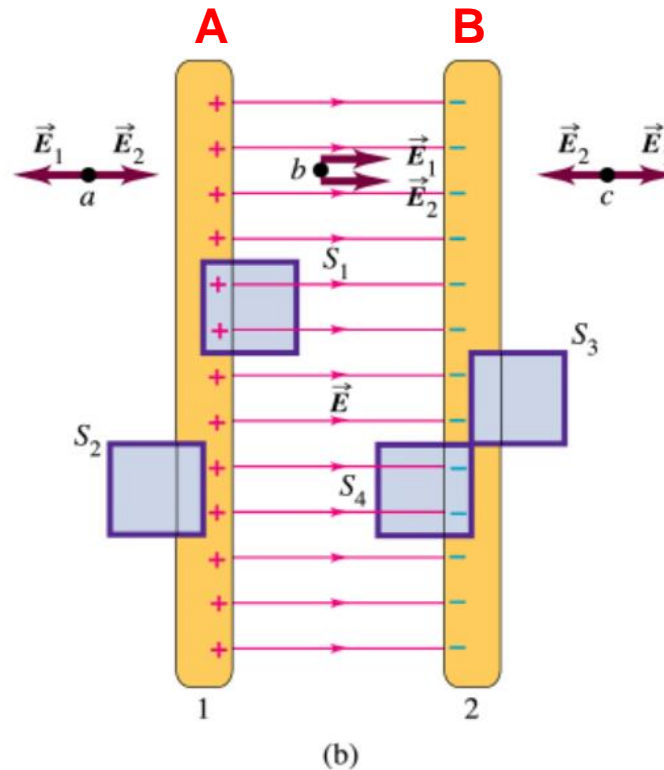

$$V_B - V_A = - \int_A^B \vec{E} \cdot d\vec{l},$$

$$\epsilon = \epsilon_0 \epsilon_r,$$

$$C = \epsilon \frac{A}{d};$$

- $Q = CV$

$$1F = \frac{1C}{1V}.$$


$$i = C \frac{dv}{dt} = C * (\text{rate of change of voltage})$$

$$I = \frac{dq}{dt}$$




# Waveforms of a Capacitor

## Energy Storage: Capacitor

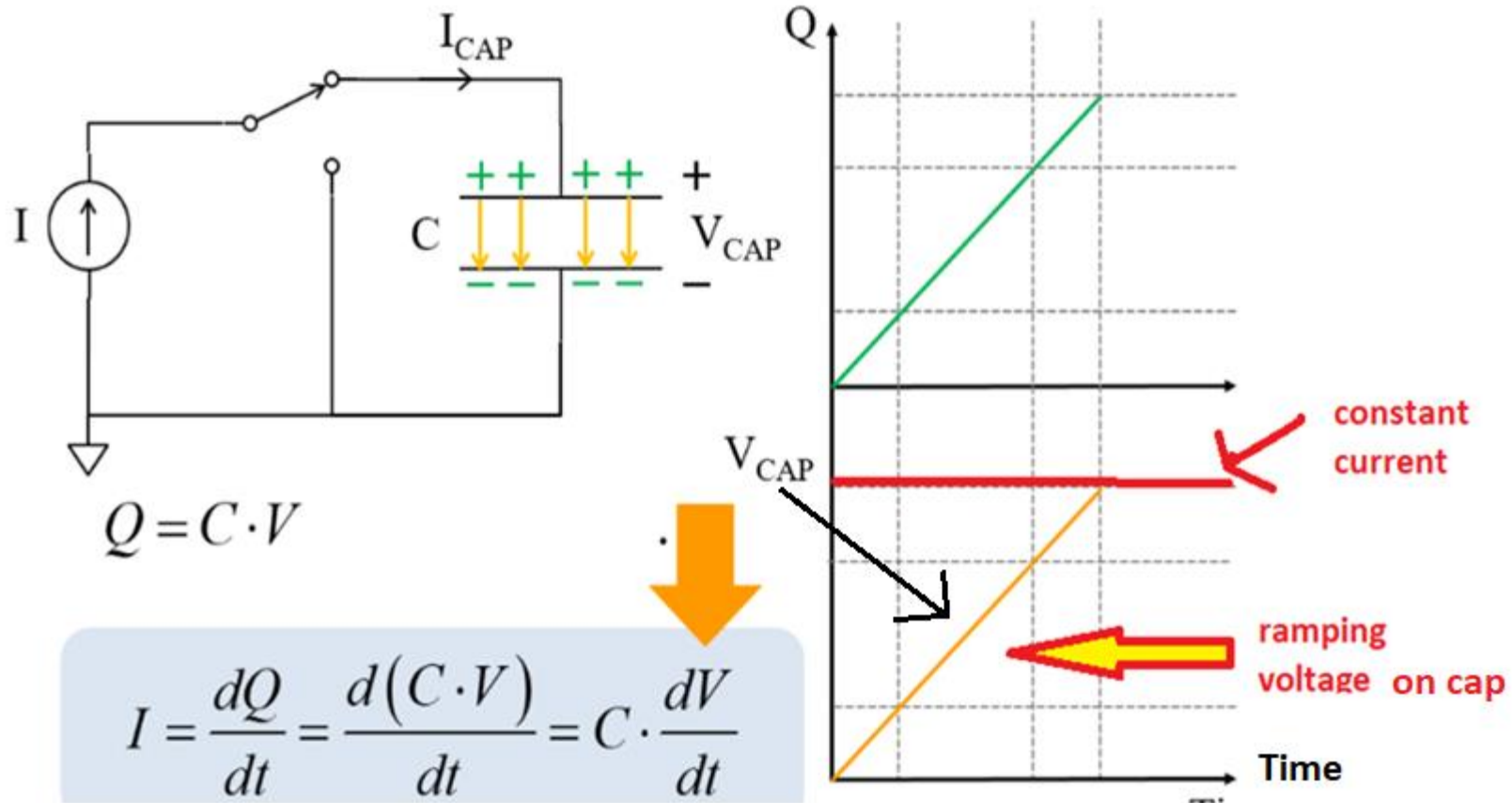

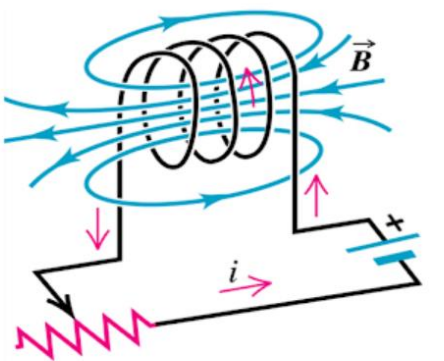
# Basic Physics of an Inductor

**Self Induction** – the production of e.m.f. in a circuit due to the change of current in the circuit itself




- Running a changing current (by changing R), creates a changing magnetic field, which creates an induced emf that fights the change
- Unit: Henry ( $V \cdot s \cdot A^{-1}$ )

## Energy Storage: Inductor

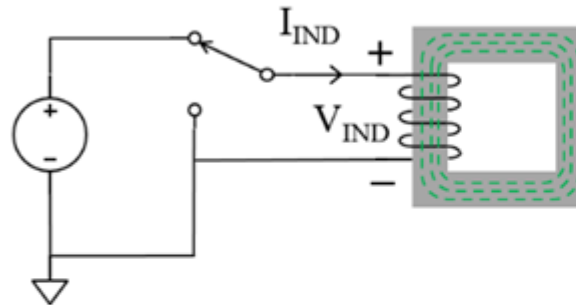

$$\lambda = L \cdot I \quad E = \frac{1}{2} \cdot L \cdot I^2$$
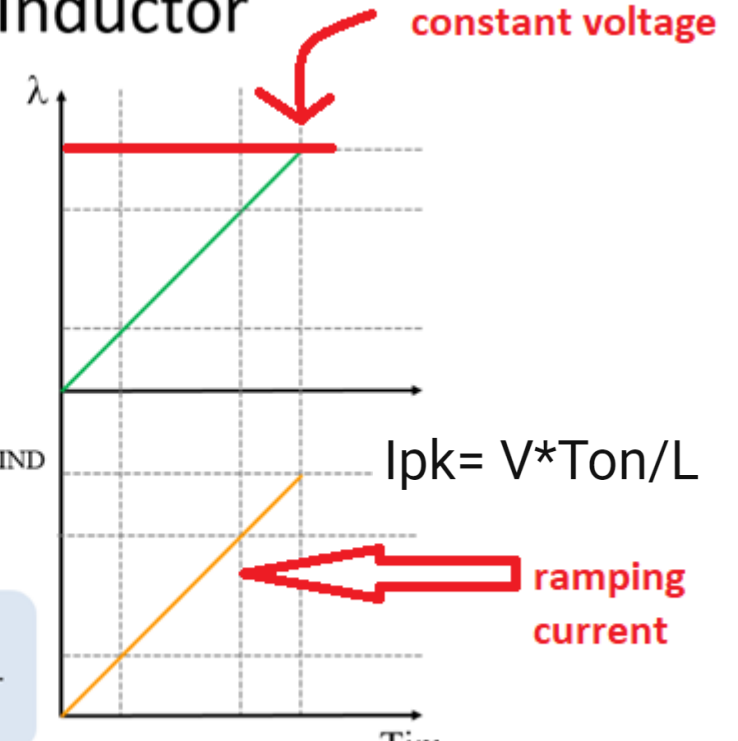
$$V = \frac{d\lambda}{dt} = \frac{d(L \cdot I)}{dt} = L \cdot \frac{dI}{dt}$$




**NOTE:** Real Inductor has series R which makes the current follow an exponential rather than linear function

# Basic Physics of an Transformer


## Transformer Magnetizing Current

\*Leakage Inductance Omitted

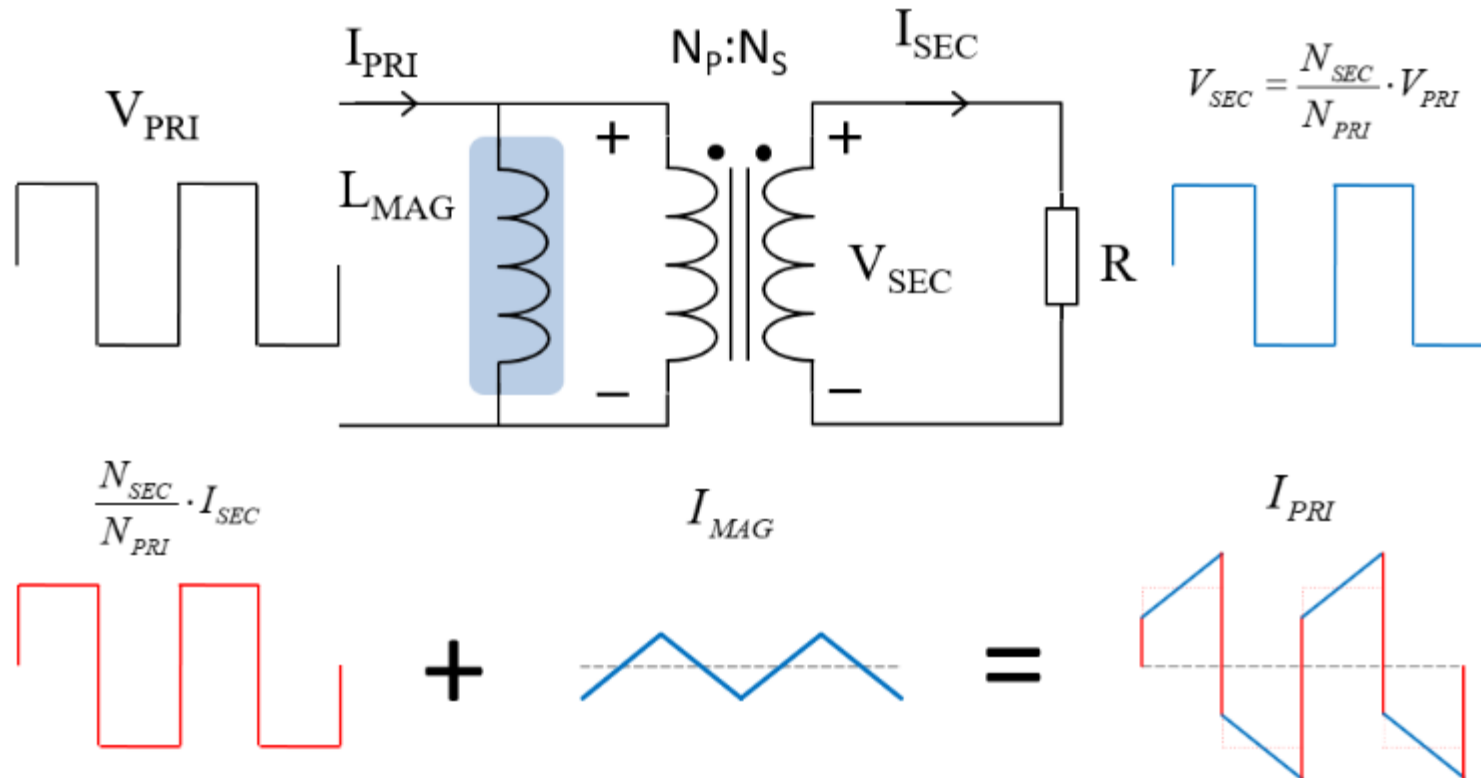

# Basic Switch-Mode Concept

## Switch Mode Concept

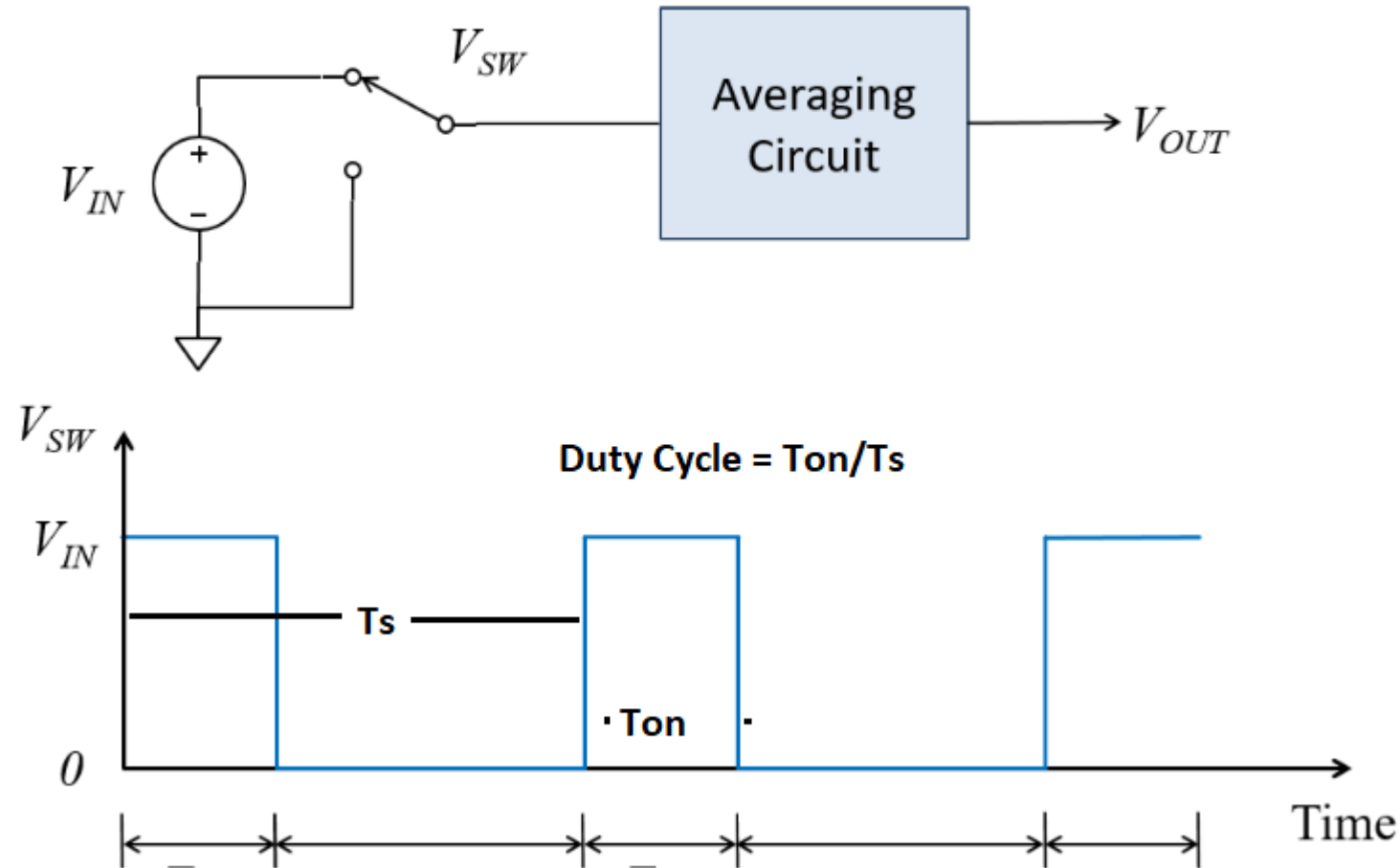

$D$  = switch duty cycle  
 $0 \leq D \leq 1$

$T_s$  = switching period

$f_s$  = switching frequency  
 $= 1 / T_s$


## ***Power Loss in an Ideal Switch:***

Switch closed:  $v(t) = 0$

Switch open:  $i(t) = 0$


In either event:  $p(t) = v(t) i(t) = 0$

Ideal switch consumes zero power

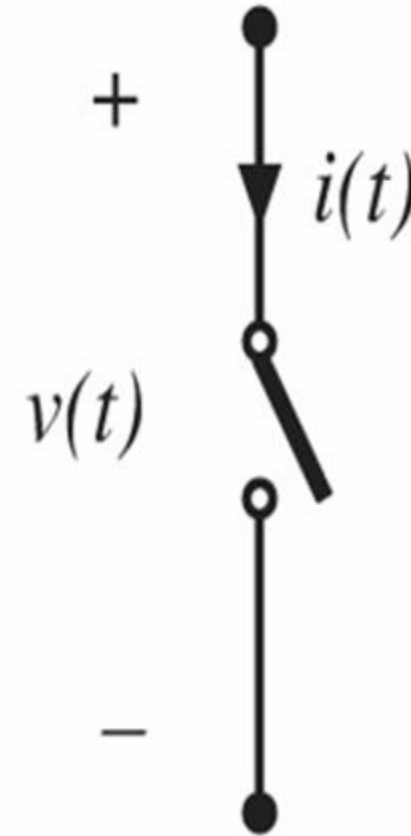



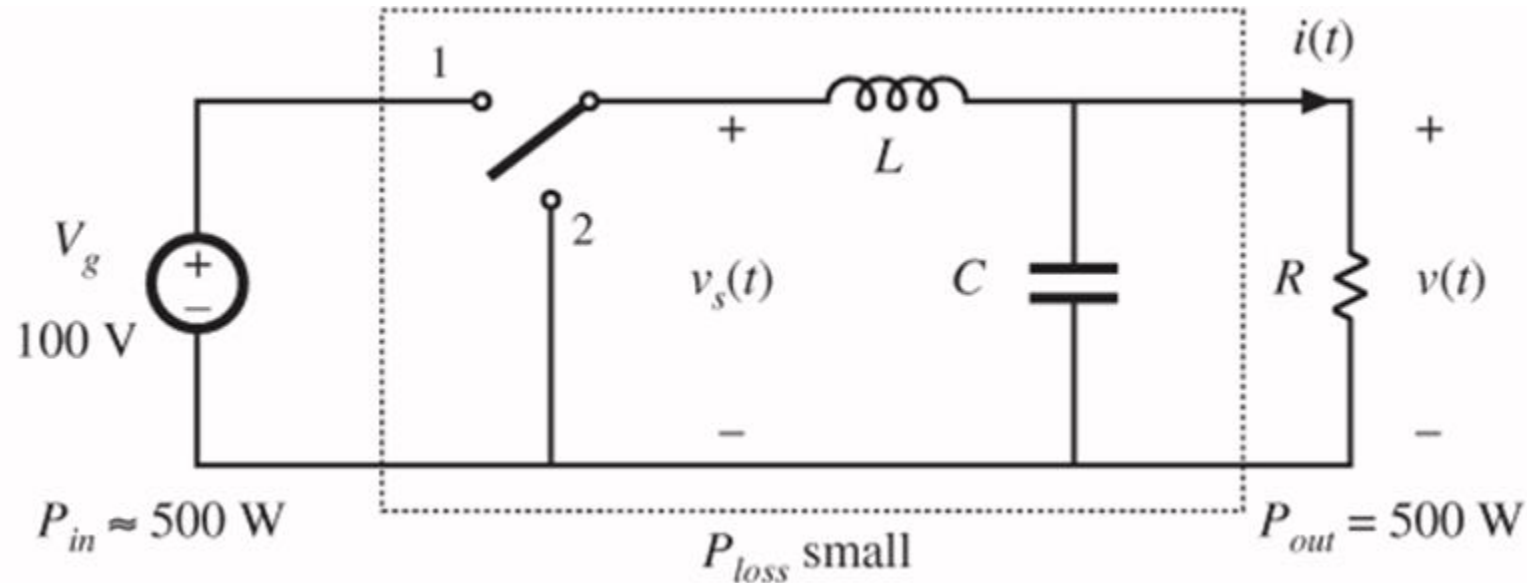
## Now Add a Lossless L-C Low Pass Filter




**\*\*Filter cutoff frequency is chosen to be significantly smaller than the Switching Frequency.**

**This is called the “Buck Converter” in  
which we now have a “clean” DC  
output voltage!**
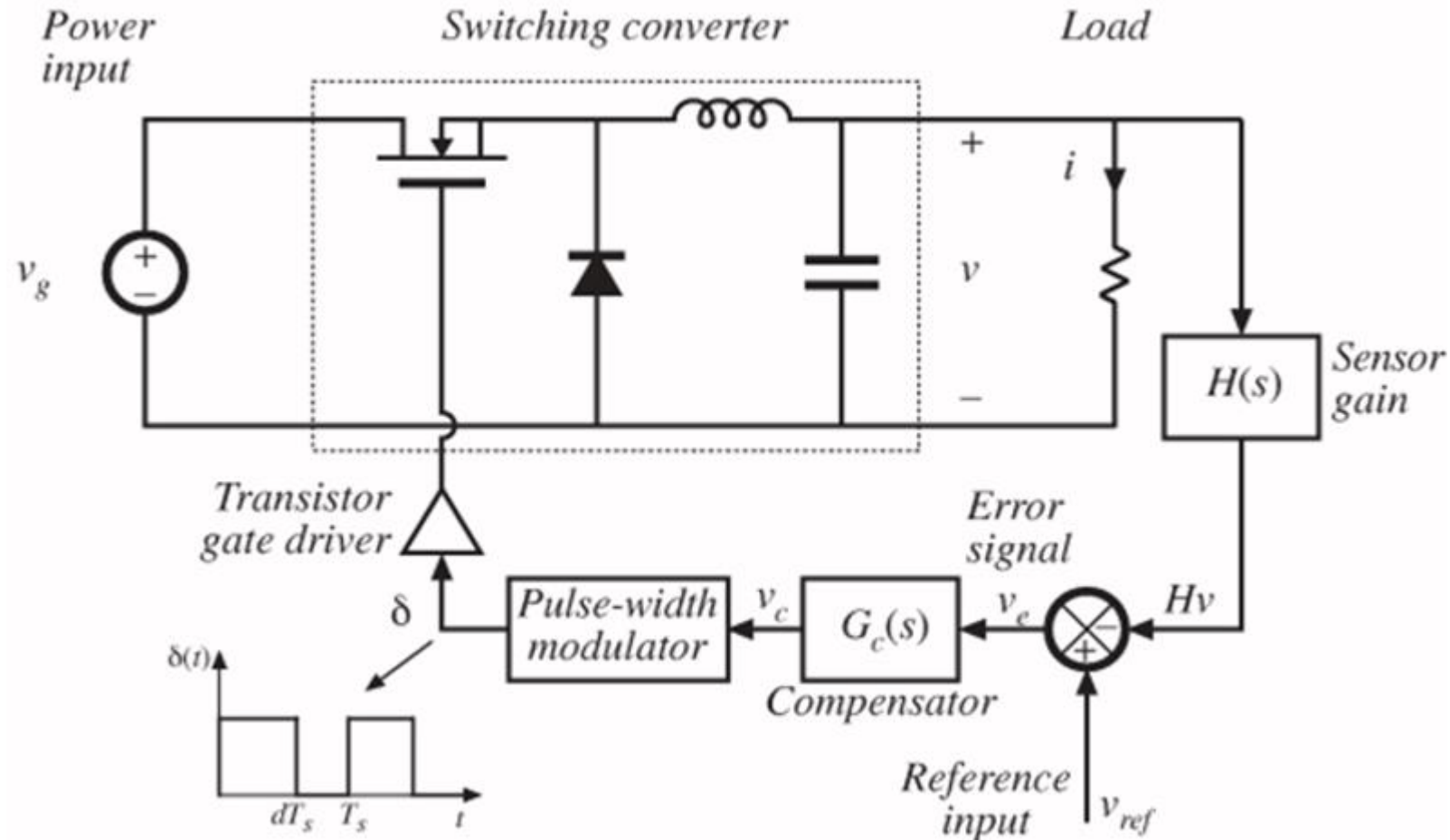
# Addition of Control System for Regulation of Output Voltage




## 3 Basic Non-Isolated DC-DC Converters

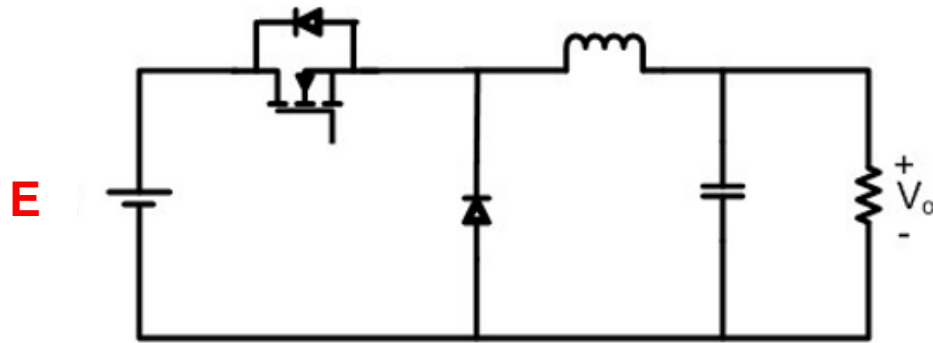


- *Buck converter*

$$V_o = DE$$

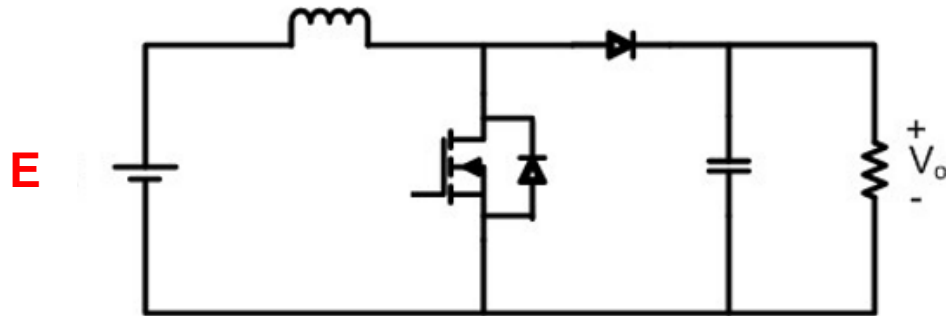

- *Boost converter*

$$V_o = \frac{E}{1-D}$$


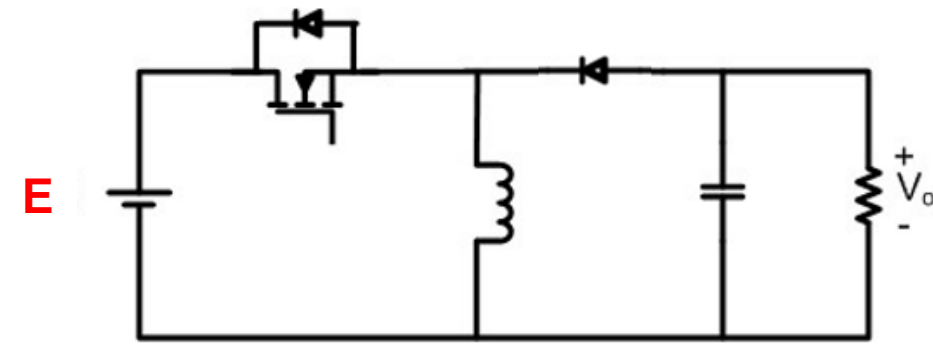


- *Buck-boost converter*



$$V_o = -\frac{DE}{1-D}$$

# Non-Isolated DC-DC Converters (Continued)<sup>32</sup>



Buck converter

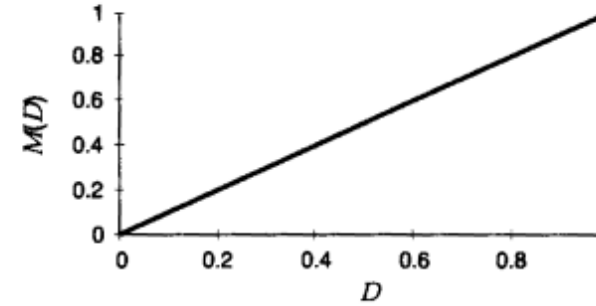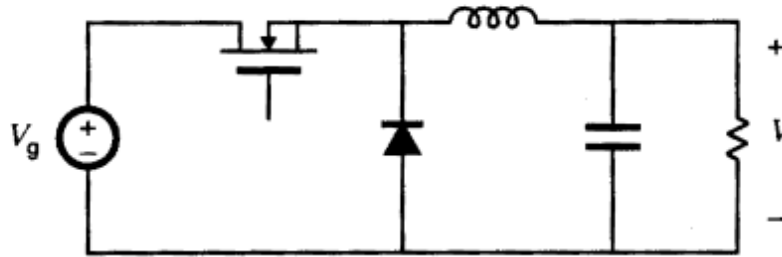





Boost converter

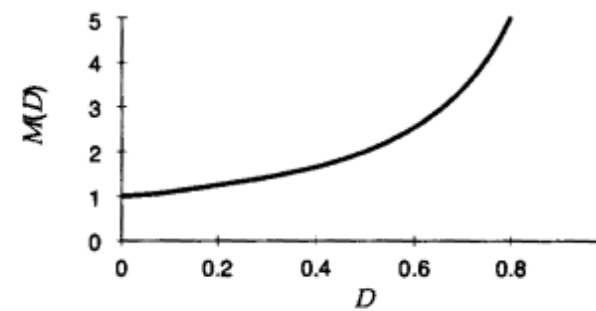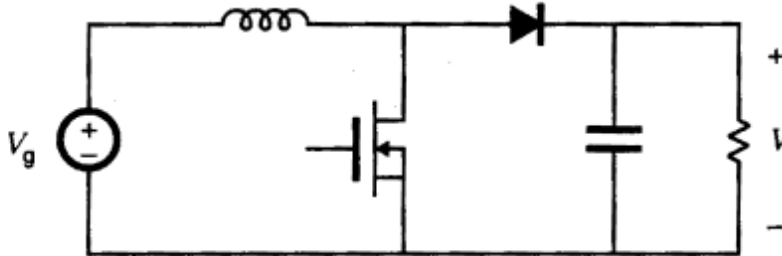

Buck-boost converter

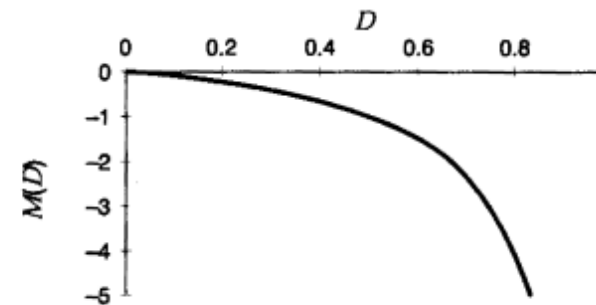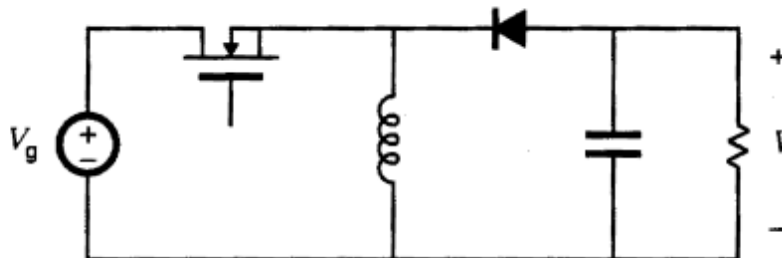
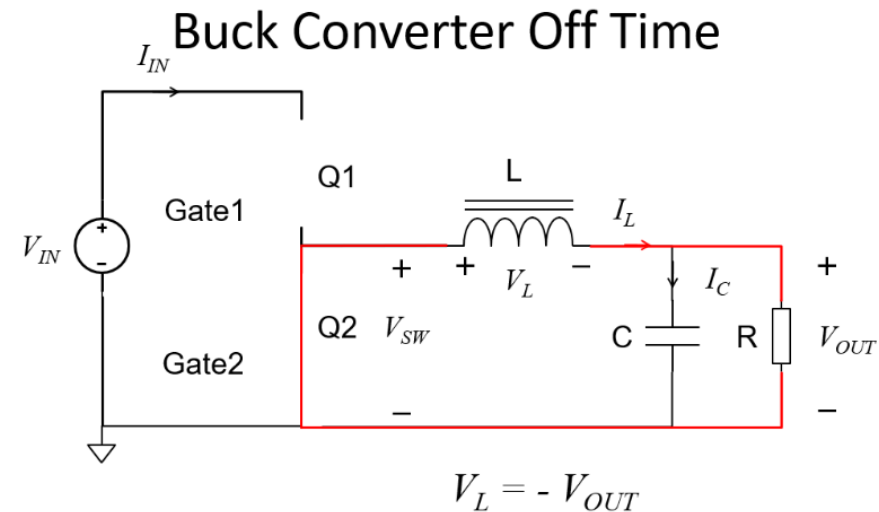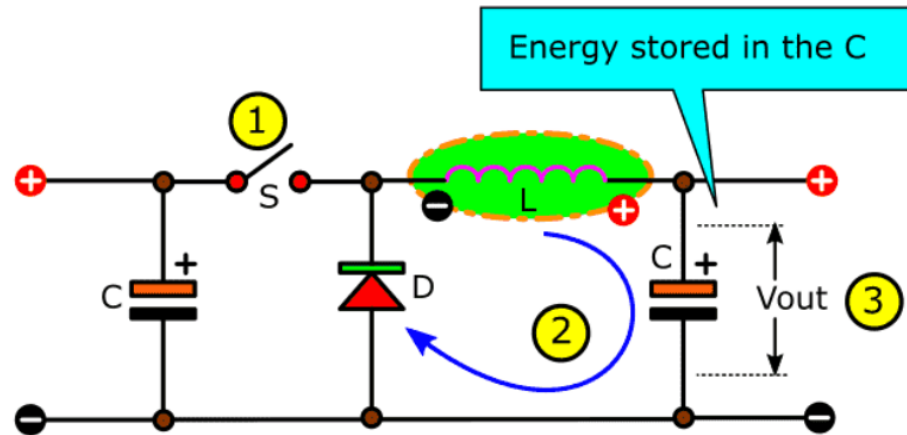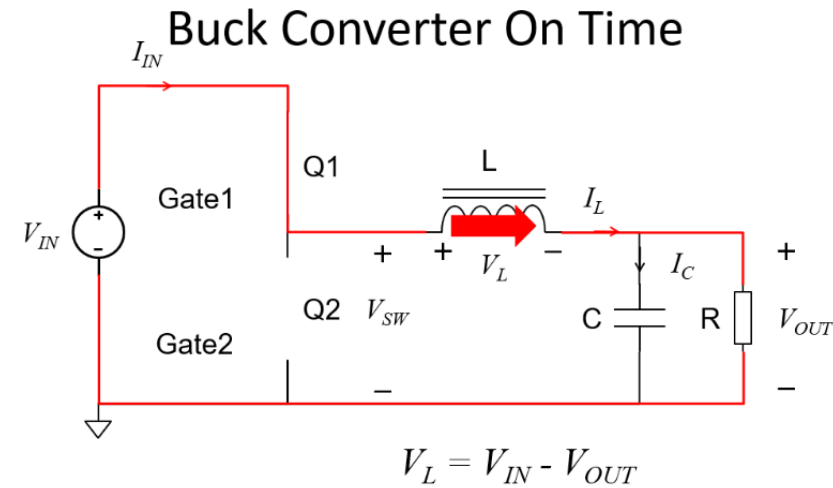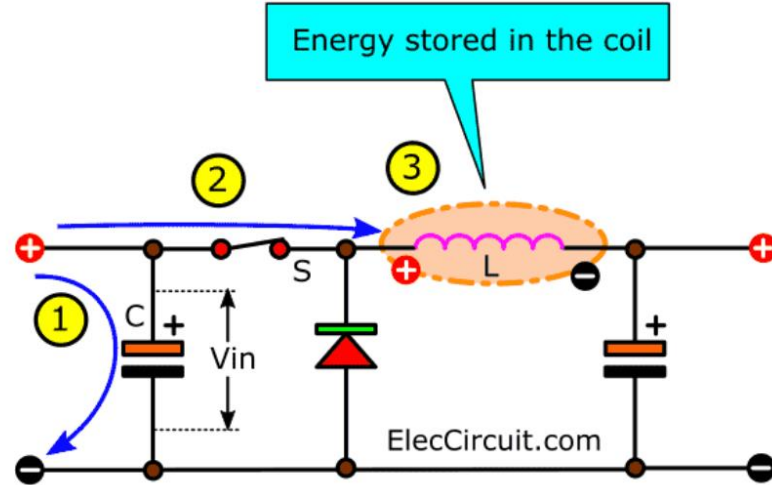
# The “BUCK” - Most Basic Switch-mode Converter






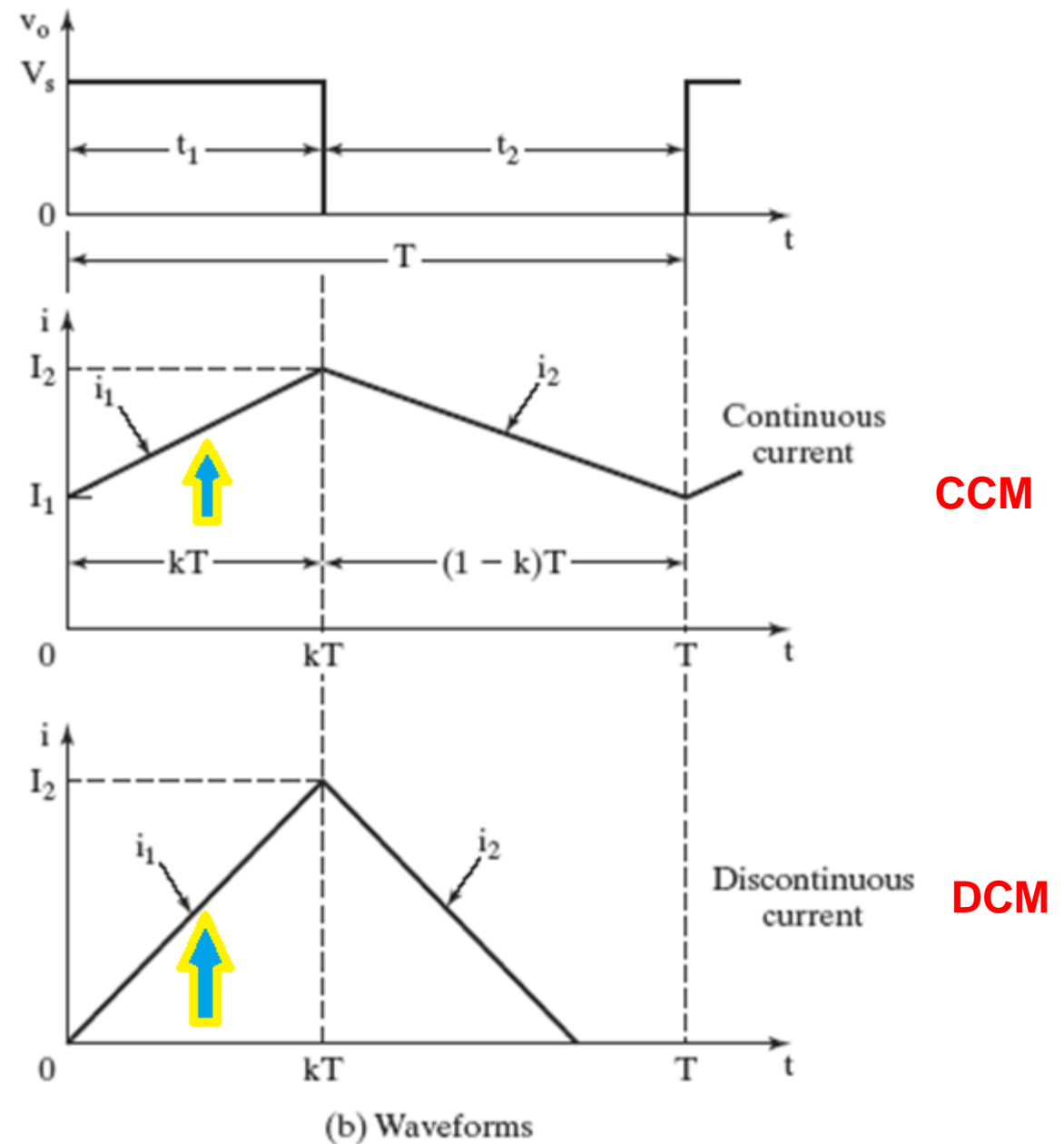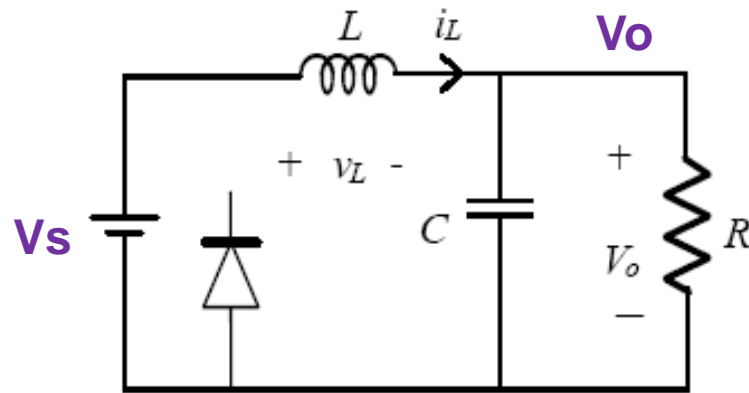
# BUCK (Continued)

Switch is CLOSED



- When switch is **CLOSED**
- $V_L = V_s - V_o = L \frac{di}{dt}$
- $\frac{di}{dt} = \frac{V_s - V_o}{L}$


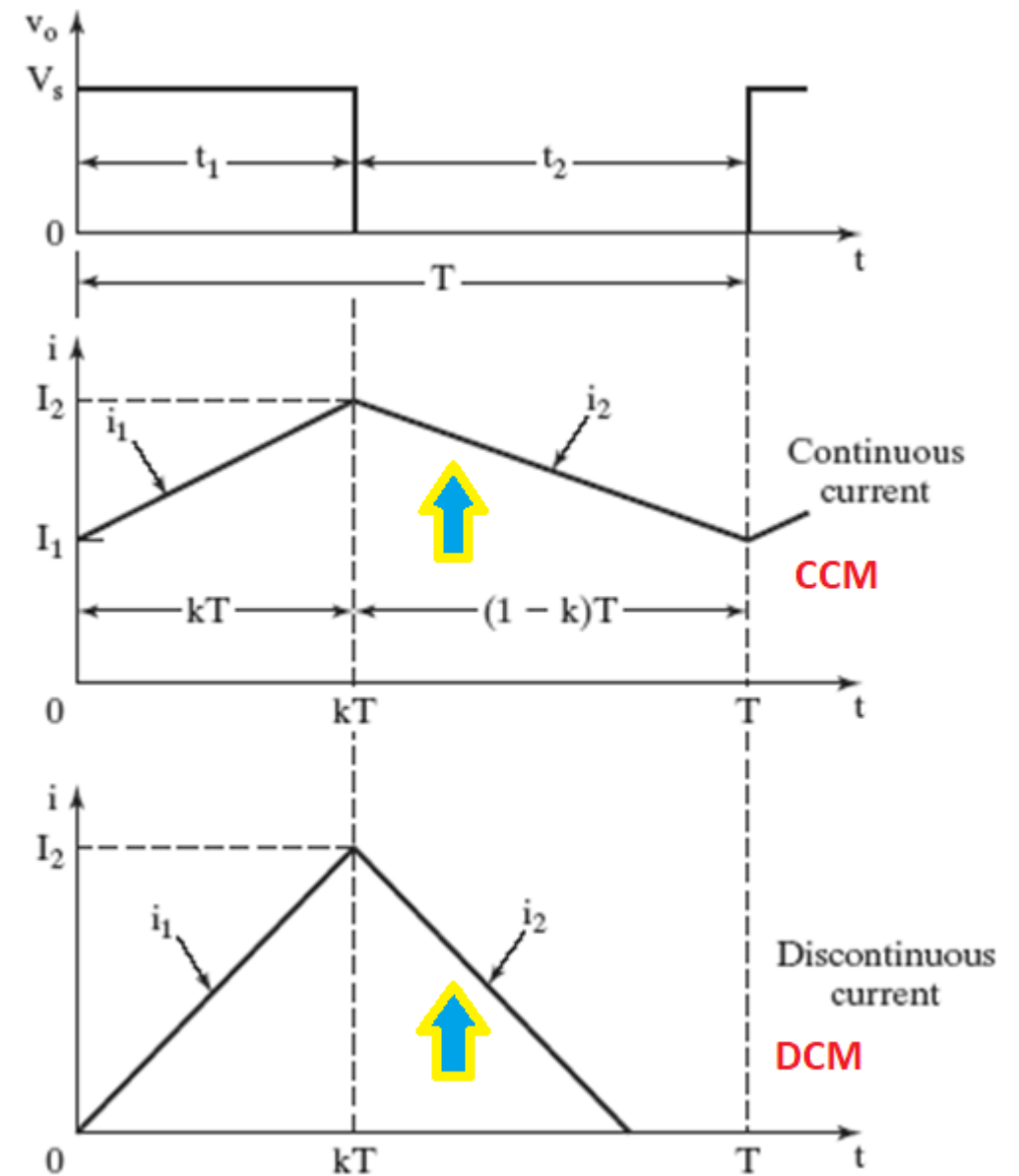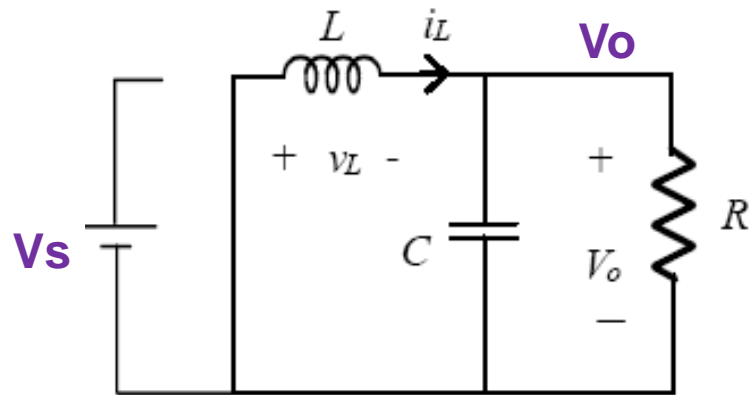
# BUCK (Continued)

Switch is OPEN

- When switch is **OPEN**
- $V_L = -V_o = L \frac{di}{dt}$
- $\frac{di}{dt} = -\frac{V_o}{L}$



(b) Waveforms

# BUCK (Continued)


## Buck Converter Math

$$V_o = DV_s$$

$$\Delta I_L = \frac{(1-D)V_o T}{L}$$




$$L_{min} = \frac{(1-D)R}{2f} \quad \text{for continuous operation}$$
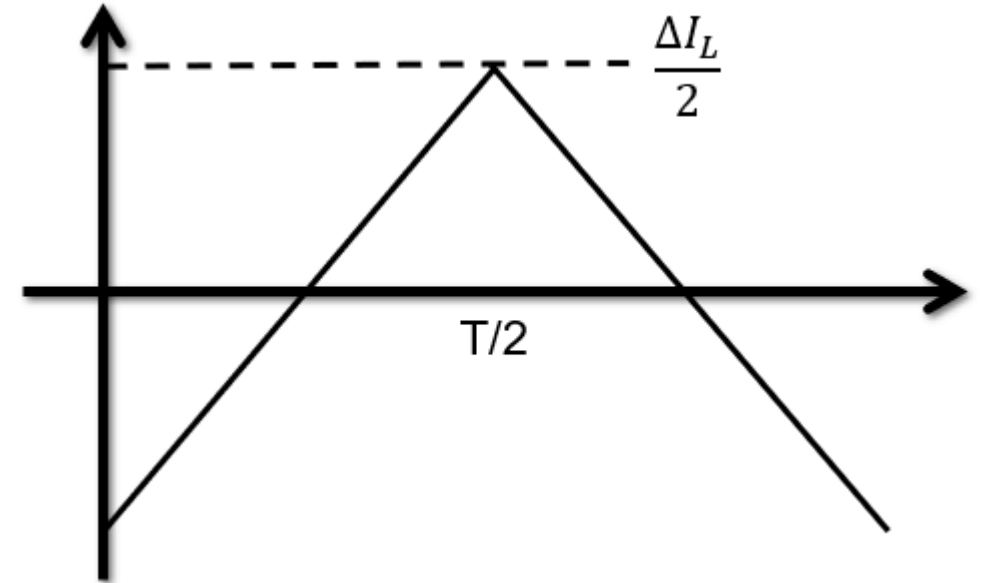
$$\bullet I_{max} = V_o \left( \frac{1}{R} + \frac{(1-D)T}{2L} \right)$$




$$\bullet I_{min} = V_o \left( \frac{1}{R} - \frac{(1-D)T}{2L} \right)$$

# Boost Converter Waveforms

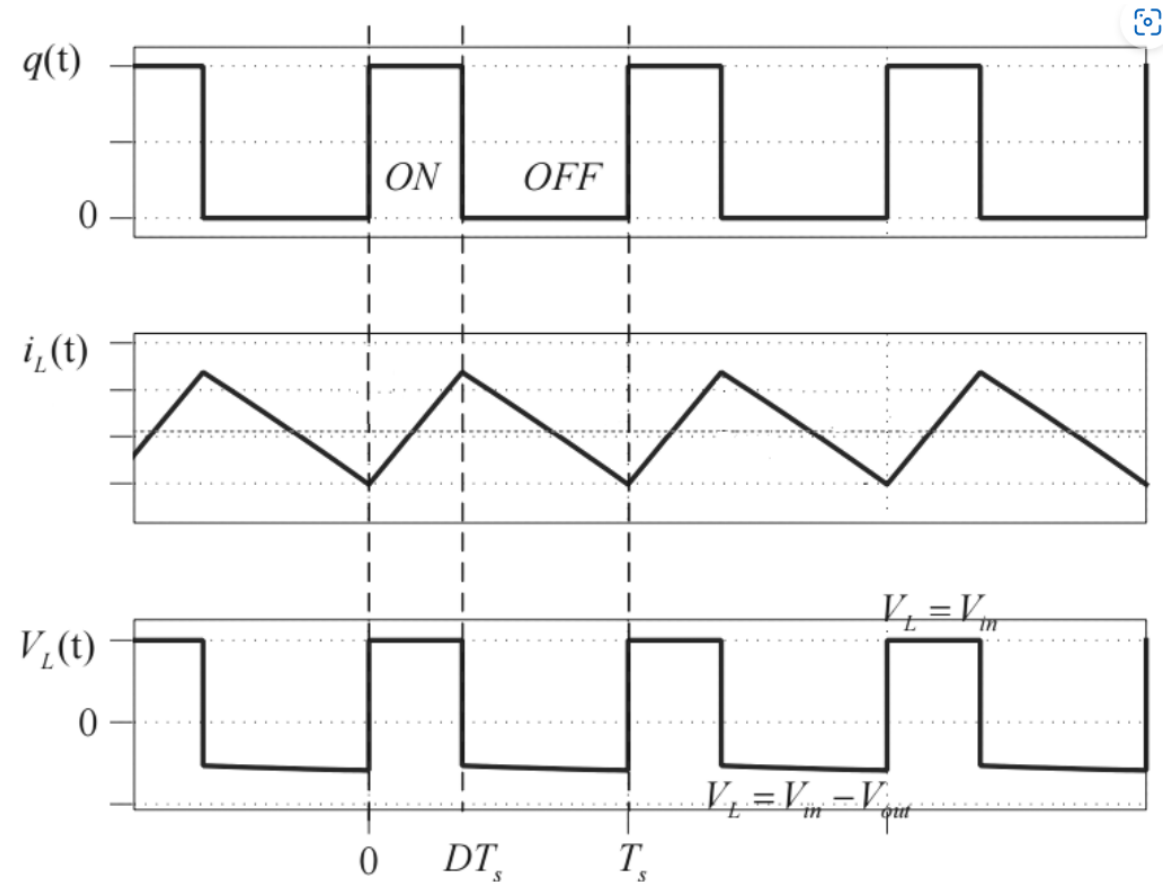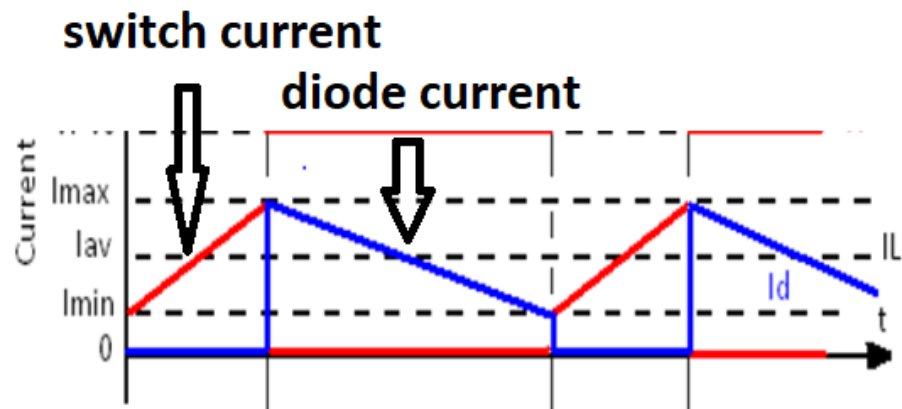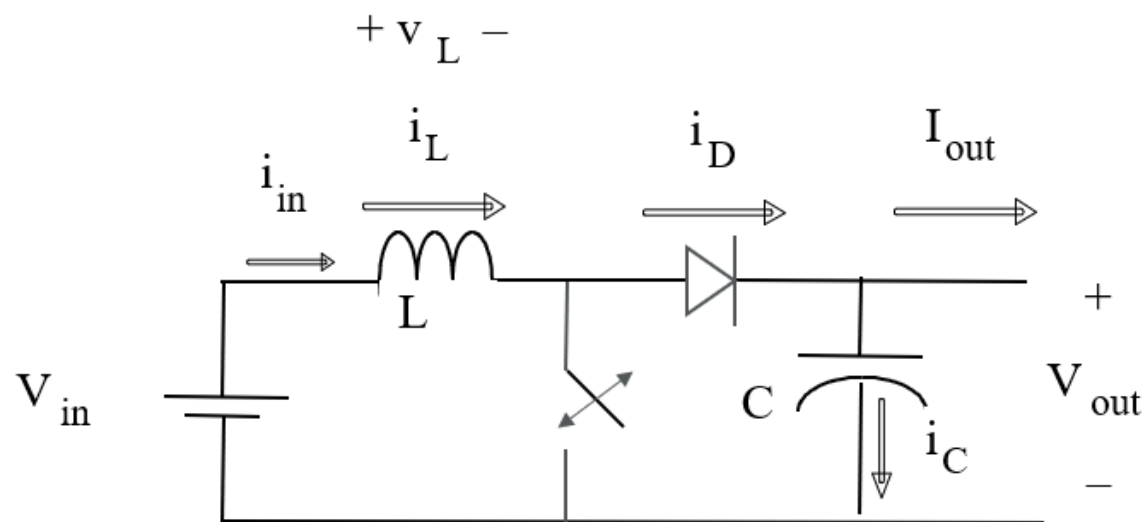

$$V_{out} = \frac{V_{in}}{1-D}$$

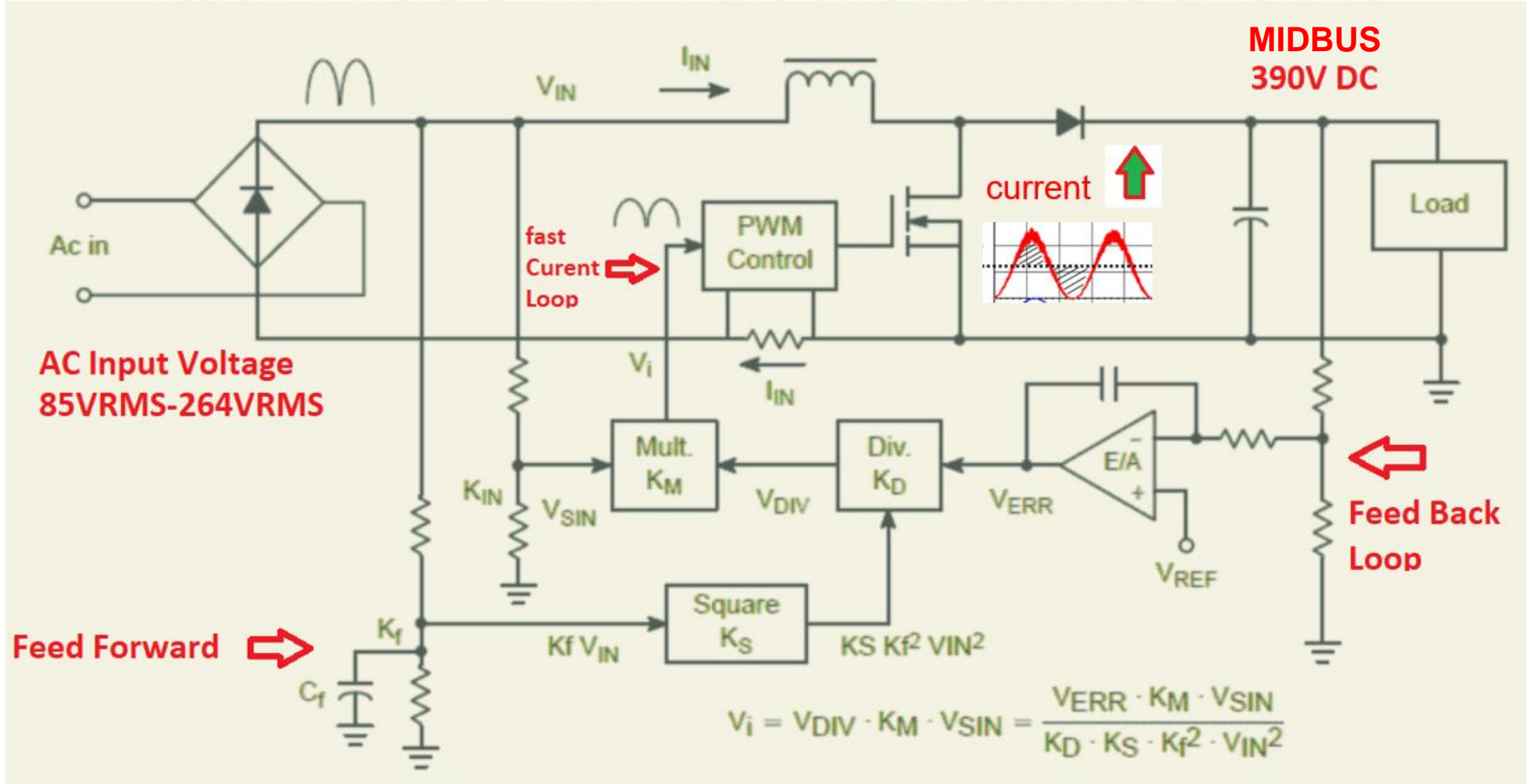
# Active Power Factor Correction (Boost converter)



Continuous Conduction Mode (CCM), and controlled by Average Current Mode Control (ACMC)



# The Buck-Boost converter (CCM)

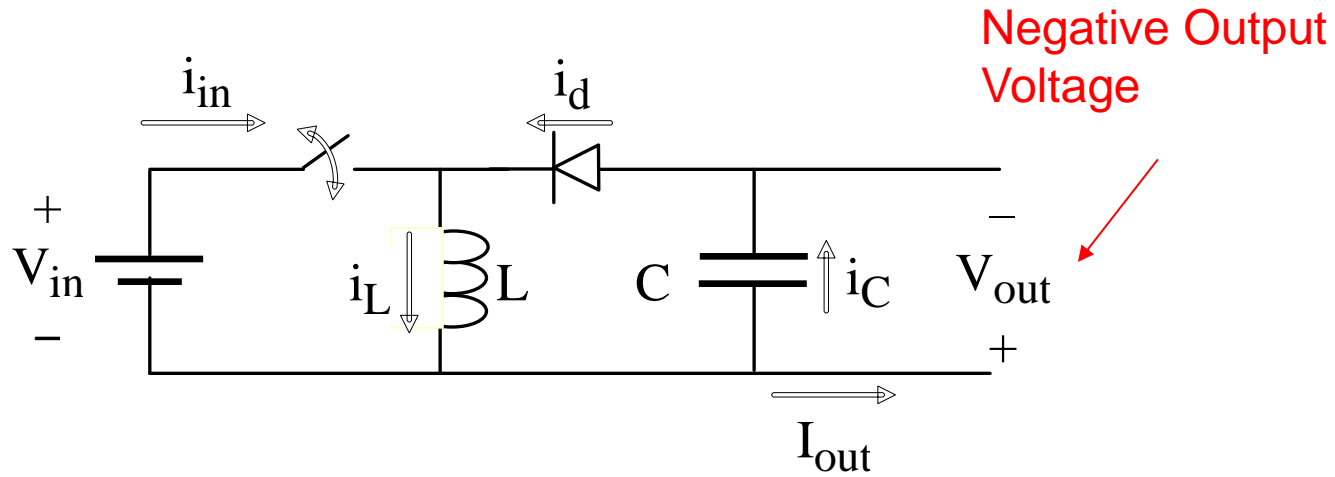

Output Voltage Boost (Up) or Buck(Down)  
(relative to input voltage)

$$V_{out} = \frac{DV_{in}}{1-D}$$

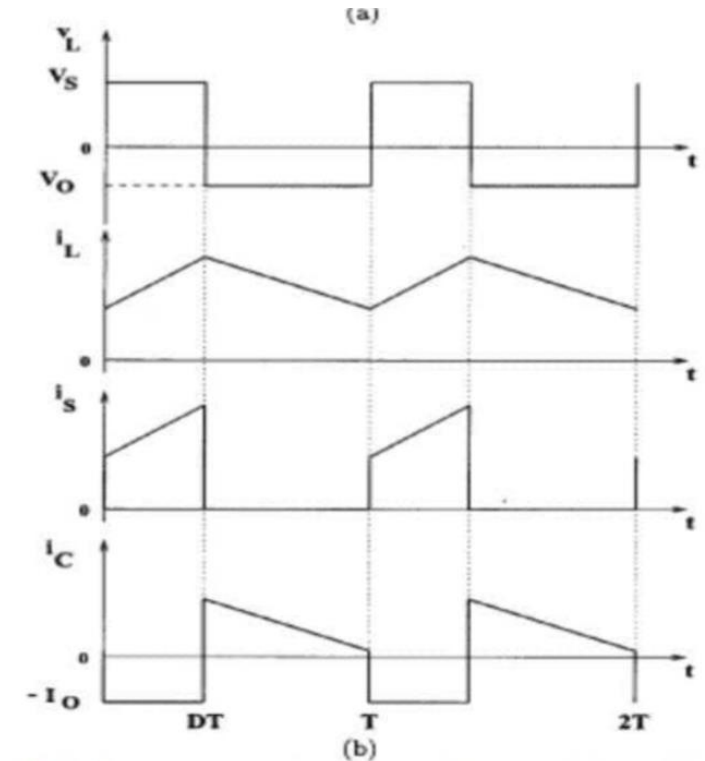


Fig.1 Buck-boost converter: (a) circuit diagram; (b) wave

# Power Supply Control Discussion



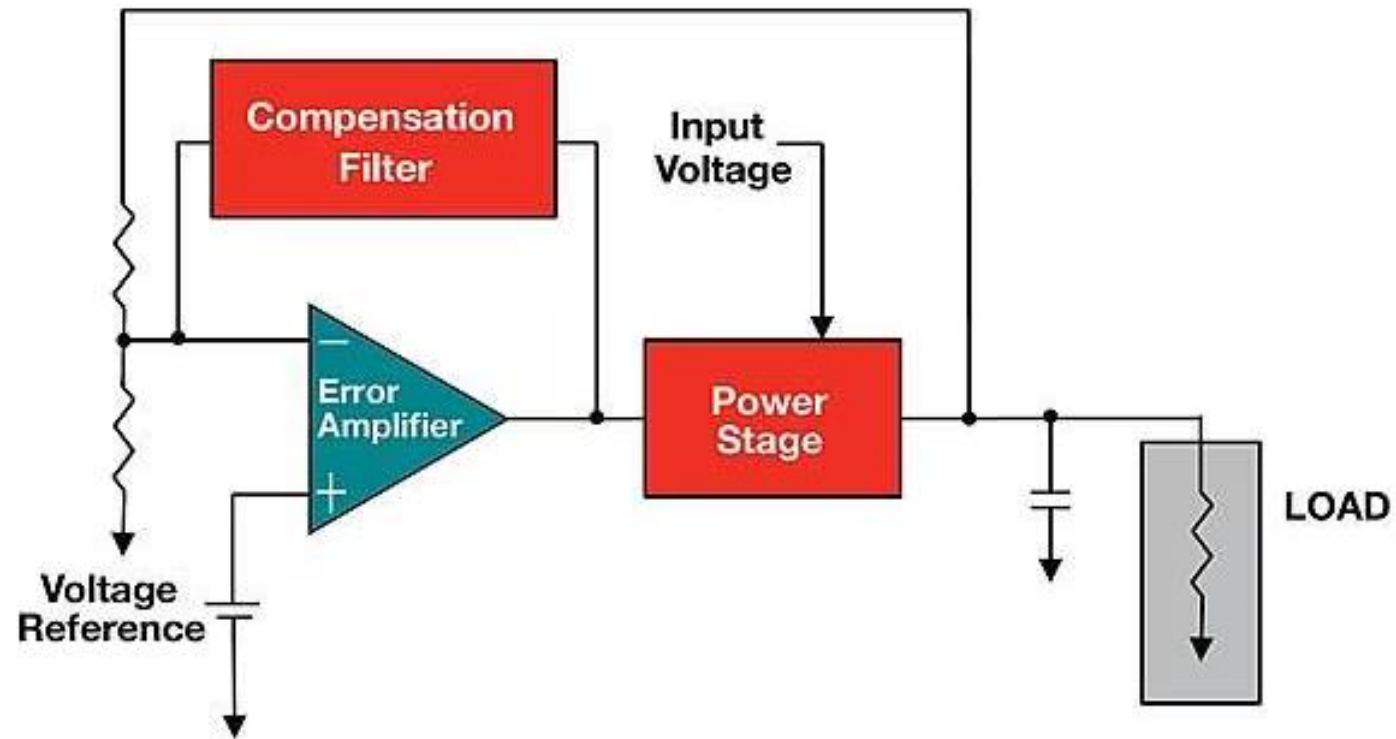
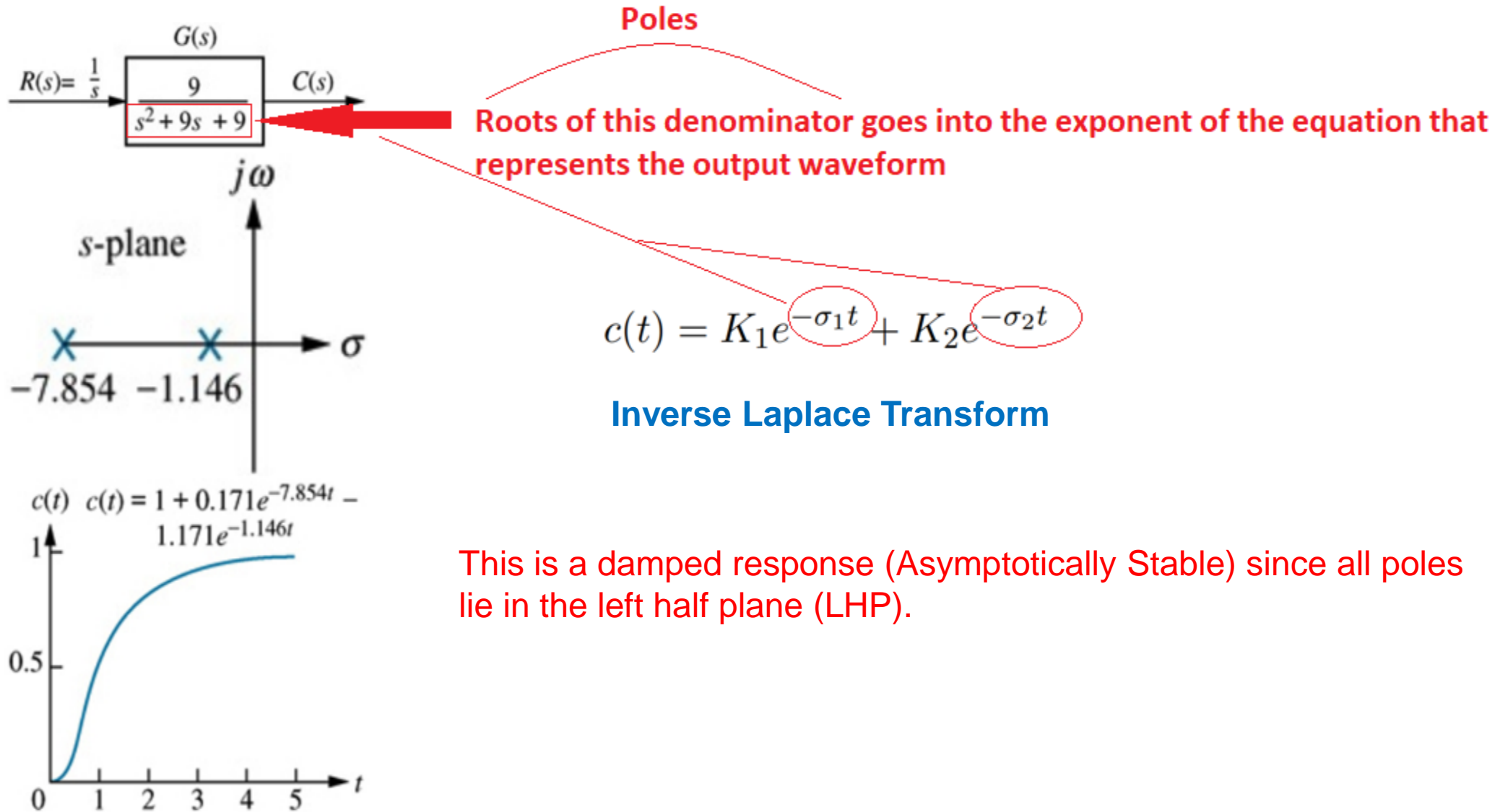
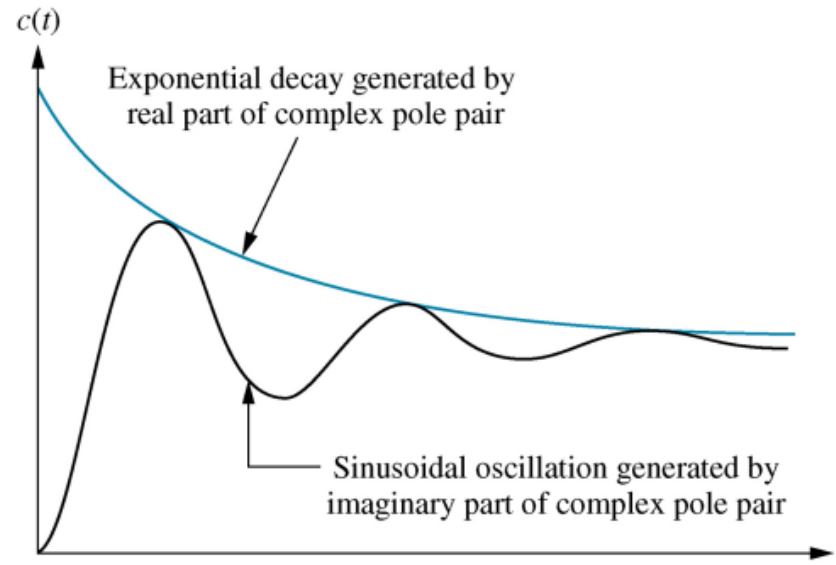


Figure 1. A typical power supply control loop.

# Solving the “Characteristic Equation”

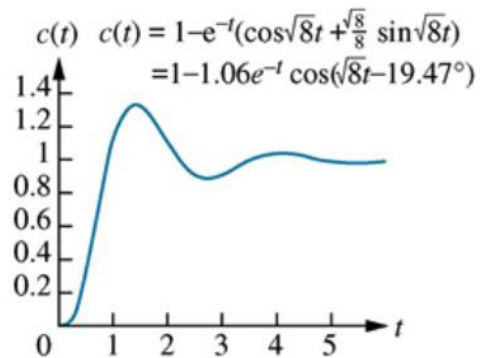

# SOLVING the “Characteristic Equation”


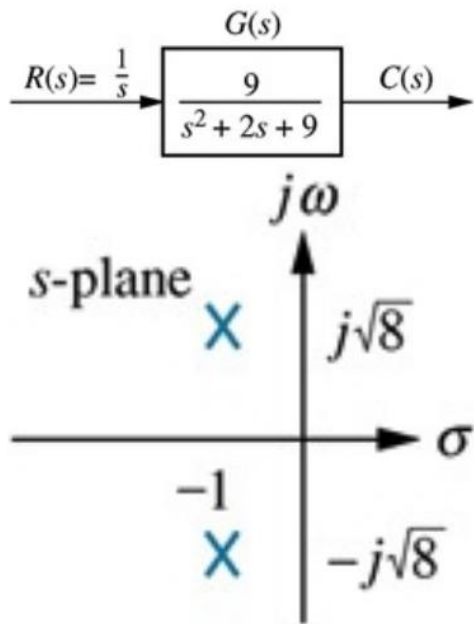


- Natural response: Damped sinusoid with an exponential envelope

**Inverse Laplace Transform**

$$c(t) = K_1 e^{-\sigma_d t} \cos(\omega_d t - \phi)$$


# Roots of “Characteristic Equations”- 2<sup>nd</sup> Order Systems

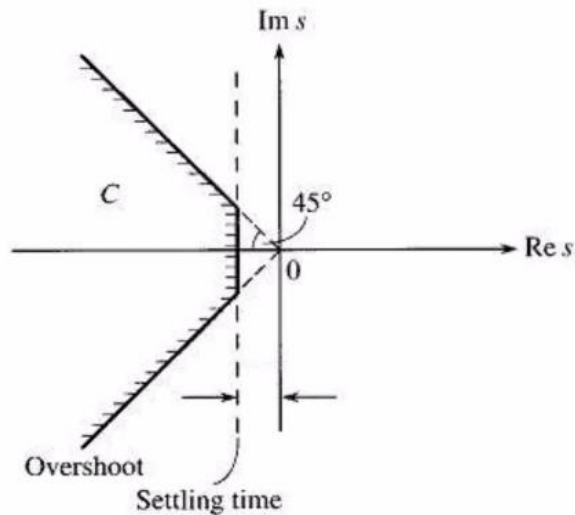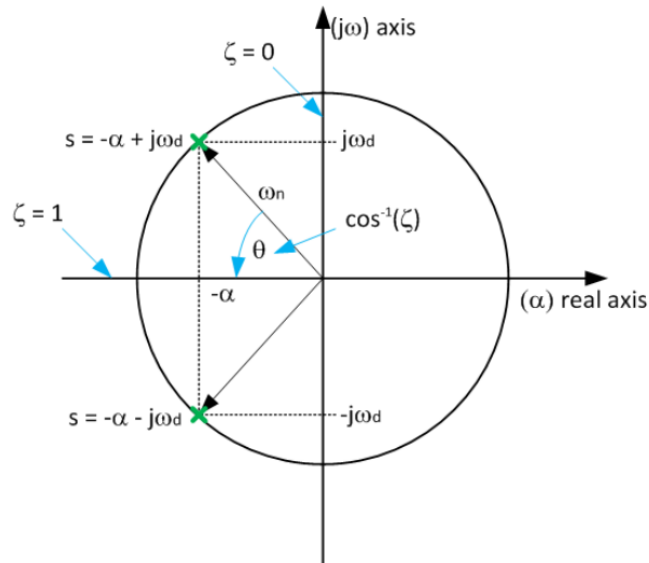

**Table:** 2<sup>nd</sup>-order response as a function of damping ratio

$\zeta$	Poles	Step response
0	<p><math>j\omega_n</math> <math>-j\omega_n</math></p>	<p>Undamped</p>
$0 < \zeta < 1$	<p><math>j\omega_n \sqrt{1 - \zeta^2}</math> <math>-j\omega_n \sqrt{1 - \zeta^2}</math> <math>-\zeta\omega_n</math></p>	<p>Underdamped</p>
$\zeta = 1$	<p><math>-\zeta\omega_n</math></p>	<p>Critically damped</p>
$\zeta > 1$	<p><math>-\zeta\omega_n + \omega_n \sqrt{\zeta^2 - 1}</math> <math>-\zeta\omega_n - \omega_n \sqrt{\zeta^2 - 1}</math></p>	<p>Overdamped</p>

# Practical Feedback Realization (Buck)

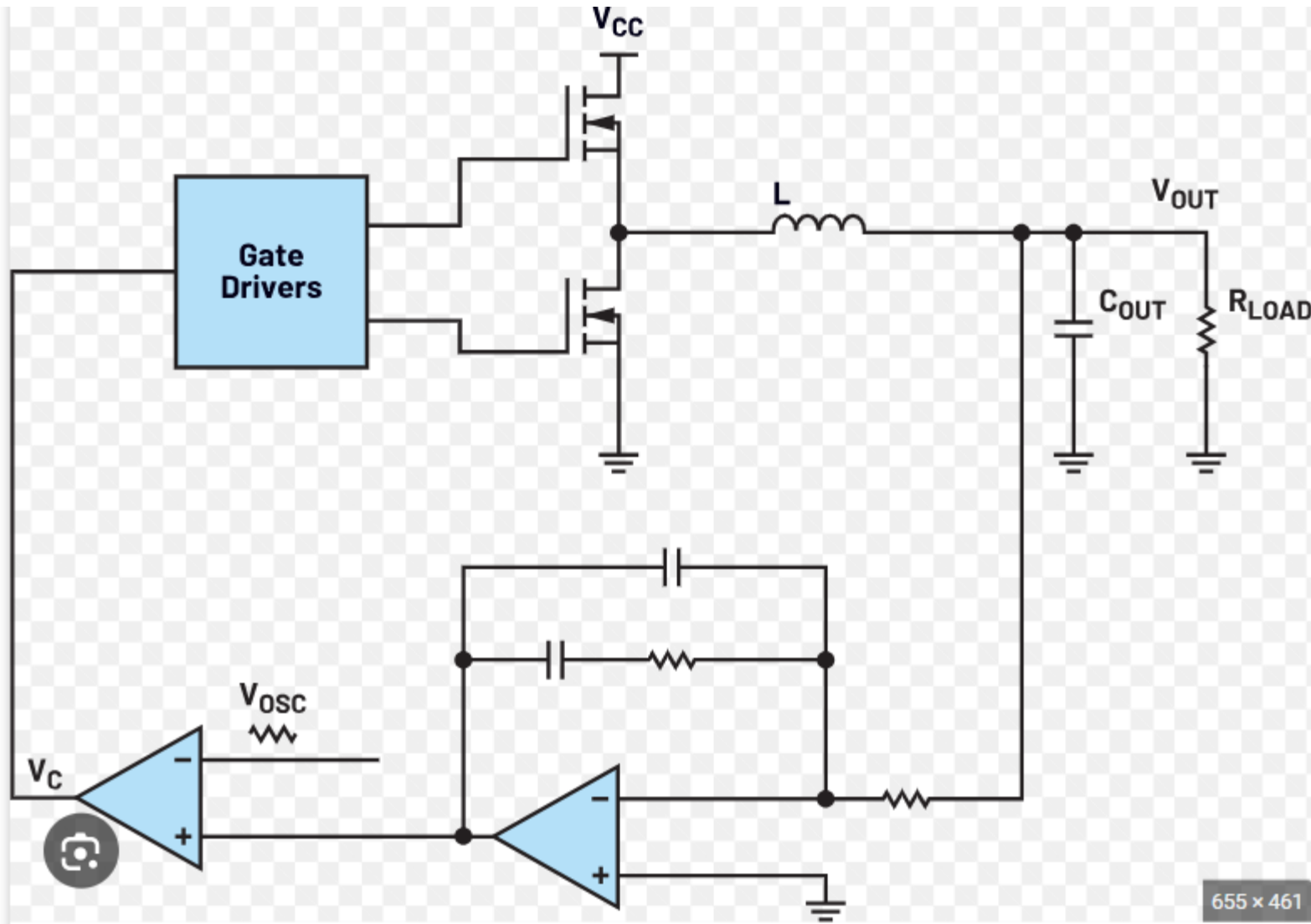



# Simple "Proportional" Feedback

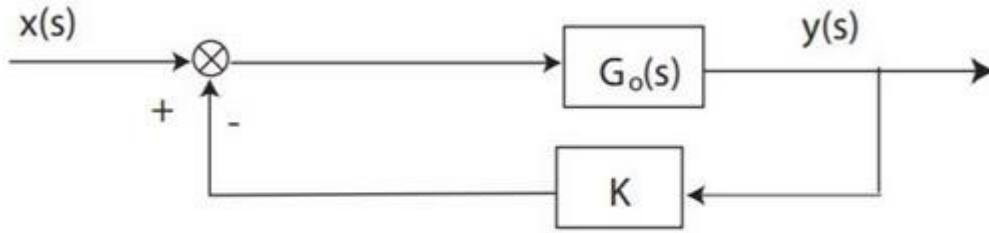


Figure 1: The proportional feedback control system.

Linearized Boost CCM model

$$\frac{V_{out}(s)}{D(s)} = H_0 \frac{\left(1 + \frac{s}{\omega_{z_1}}\right) \left(1 - \frac{s}{\omega_{z_2}}\right)}{1 + \frac{s}{\omega_0 Q} + \left(\frac{s}{\omega_0}\right)^2} \quad \omega_{z_1} = \frac{1}{r_c C_2} \quad \omega_{z_2} \approx \frac{(1-D_0)^2 R_{load}}{L_1}$$


$G_o(s) = N(s)/D(s)$  **➡ OPEN LOOP (No Feedback)**

$$f_{RHP\_zero} = \frac{R}{2\pi L} \cdot \left(\frac{V_{IN}}{V_o}\right)^2$$

$T(s) = \frac{KN(s)}{D(s) + KN(s)}$  **➡ CLOSED LOOP TRANSFER FUNCTION (Feedback)**

**Important NOTE:** At  $K = 0$  the roots of the “Characteristic Equation” start at the Open Loop Poles and migrate towards the Open Loop Zeros at  $K = \text{Infinity}$ .
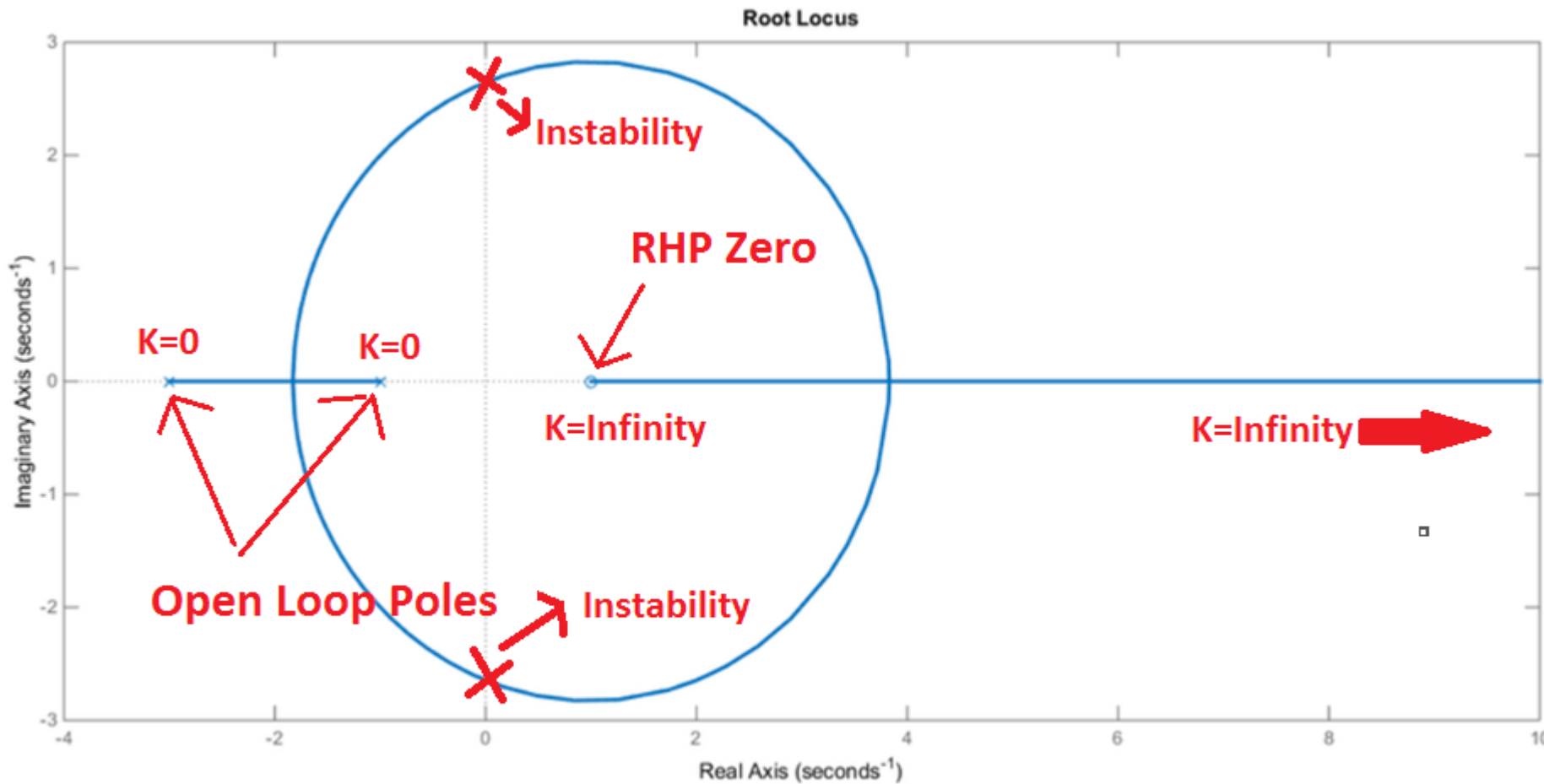
# Boost Converter Root Locus (CCM) with Proportional Feedback




Root locus of the closed loop system of boost converter with proportional controller and two real negative roots.
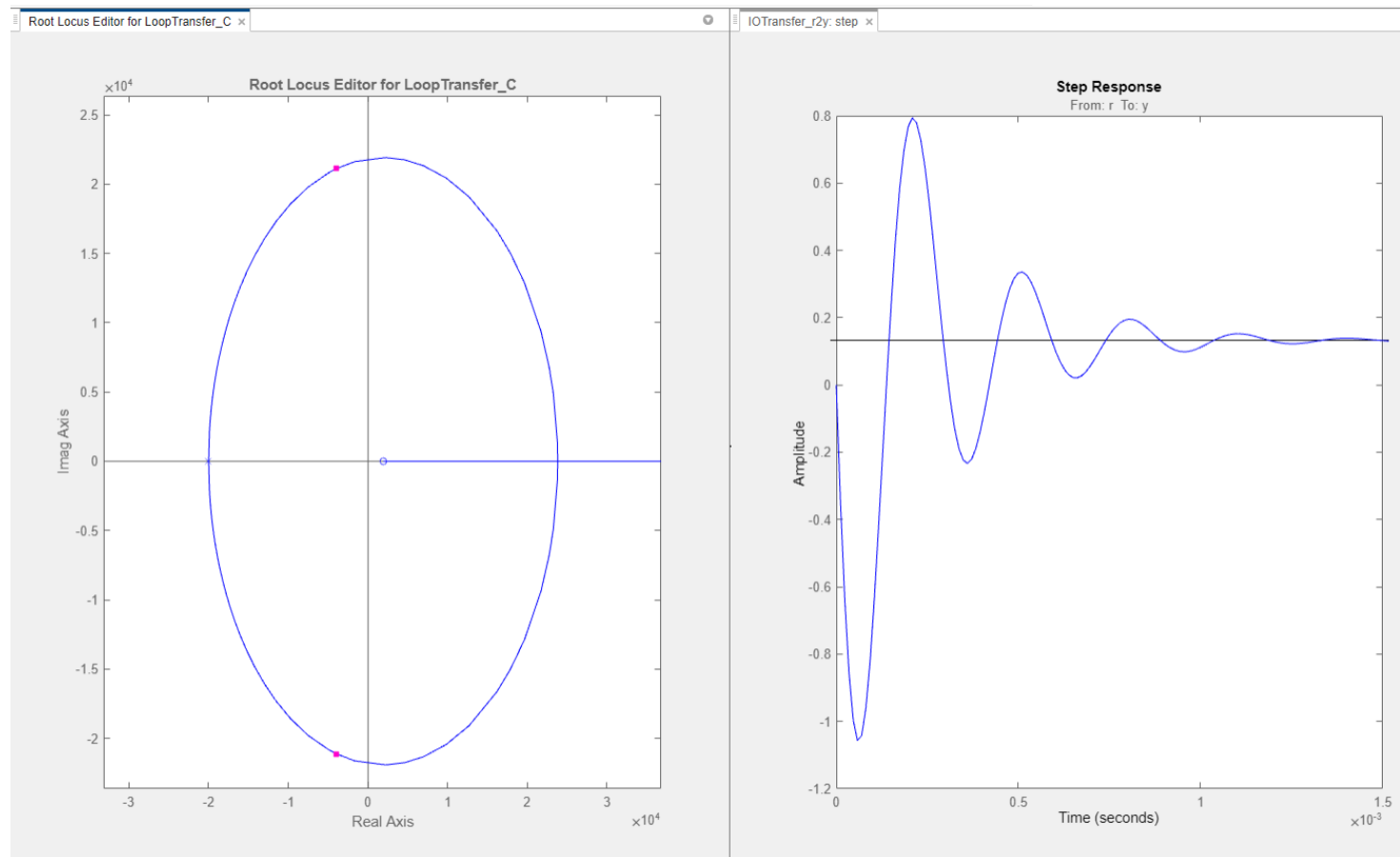
# MATLAB Boost Converter Root Locus (CCM)

```
>> controlSystemDesigner('rlocus',tf_boost);
>> tf_boost=(Ro*(1-d)/(2*Rsense))*(1-s/(2*3.14*Frhpz))/((1+s/(2*3.14*Fp))^2)
```

$$G_{PS}(S) = \frac{R_O \times (1-D)}{2 \times R_{sense}} \times \frac{\left(1 + \frac{S}{2 \times \pi \times f_{ESRZ}}\right) \left(1 - \frac{S}{2 \times \pi \times f_{RHPZ}}\right)}{\left(1 + \frac{S}{2 \times \pi \times f_P}\right)^2}$$



Note: Plot does not contain the ESR Zero

## Stability Summary (Voltage Mode)

Buck, Boost and Buck Boost (DCM- Discontinuous Conduction Mode) are all single Pole Functions for  $dV_{out}(s)/dV_{in}(s)$  and  $dV_{out}(s)/dD(s)$



### BUCK (CCM):

Fixed Pole Pair for both  $dV_{out}(s)/dV_{in}(s)$  and  $dV_{out}(s)/dD(s)$  located near  $1/\text{SQRT}(L*C)$

No RHP




### Boost and Buck-Boost: (CCM- Continuous Conduction Mode)

$dV_{out}(s)/dV_{in}(s)$  -Variable Pole Pair near  $(1-D)^2/\text{SQRT}(L*C)$  and RHP Zero for  $dV_{out}(s)/dD(s)$




# The Fly-back converter

- Buck-Boost converter:

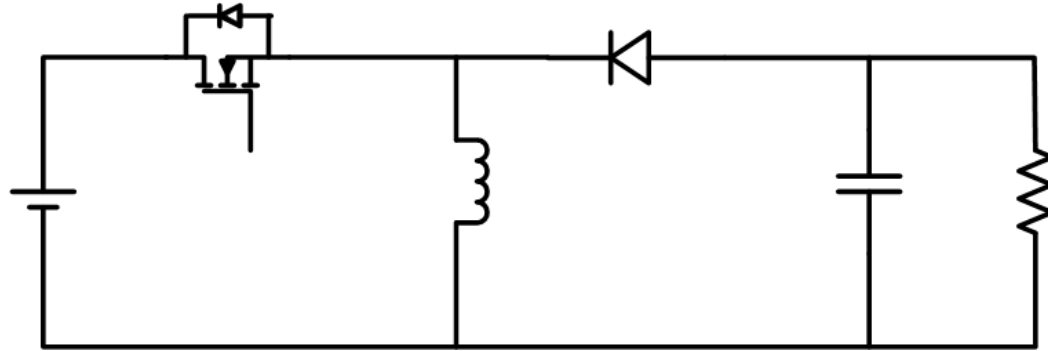


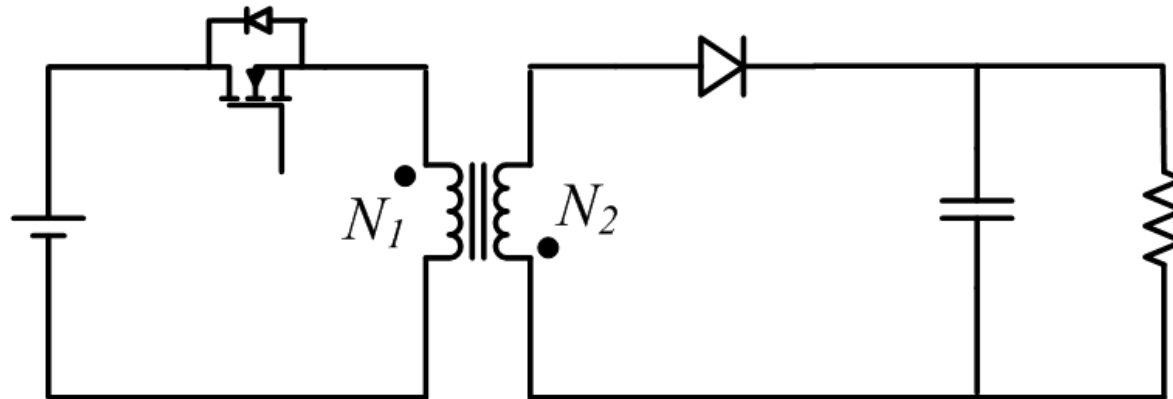Equivalent (isolated) version using magnetically coupled inductors:



Flyback Converter

## The Fly-back converter (Continued)

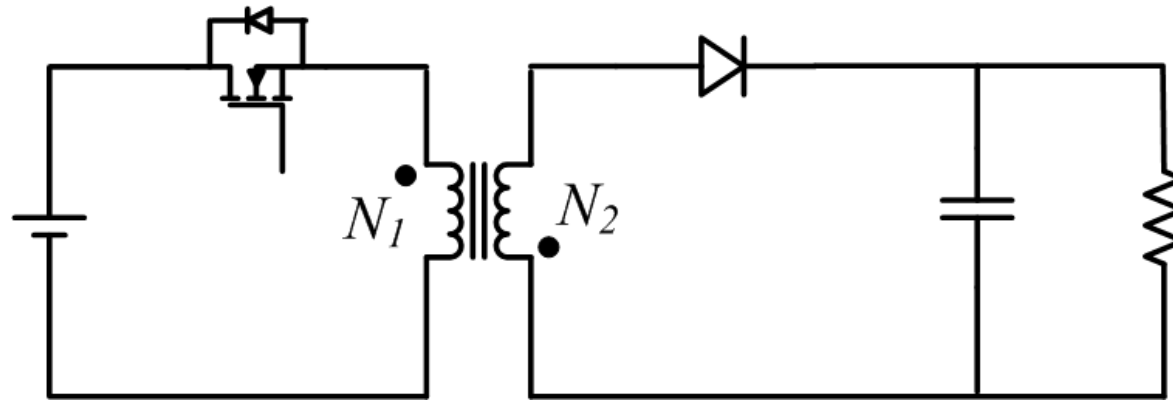


- The coupled inductors is an energy storage device (as opposed to a traditional transformer)
- Output side is galvanically isolated from the input side


$$V_{out} = \frac{N_2}{N_1} \frac{DV_{in}}{1-D}$$



# Fly-back Converter Waveforms (CCM)


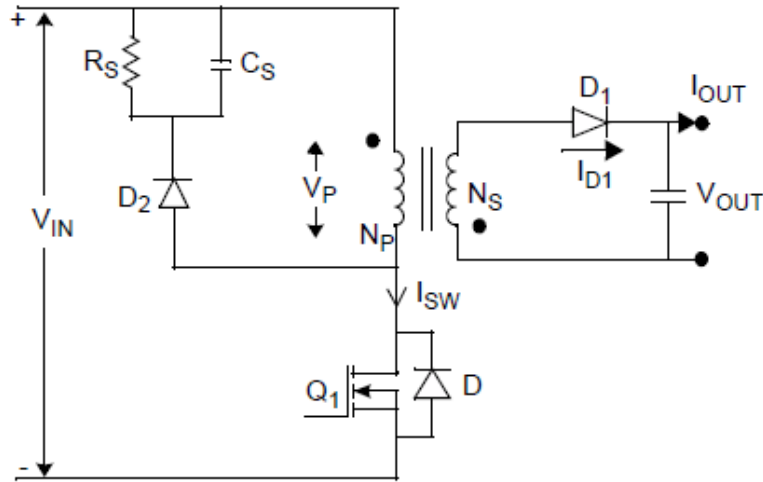


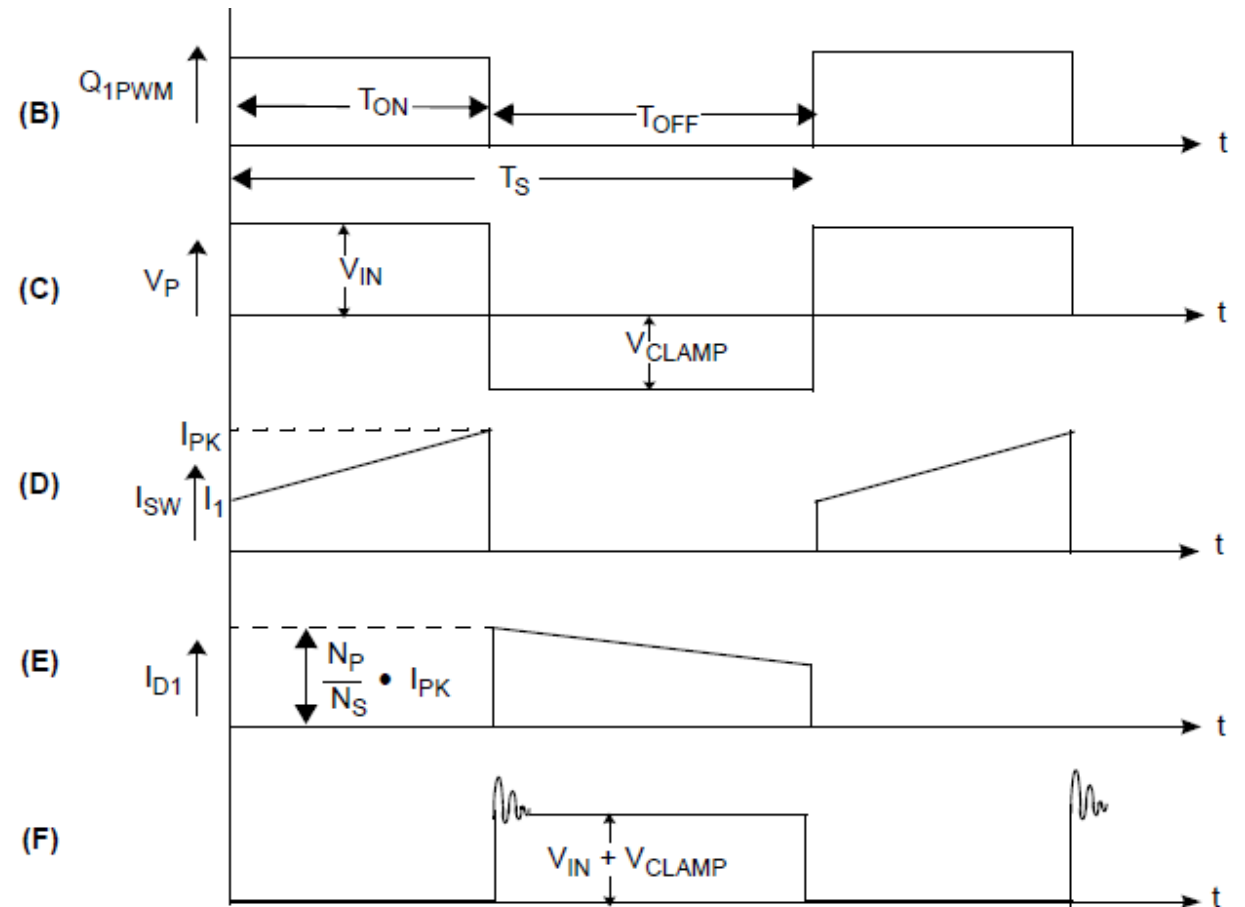- (A) = Flyback converter power circuit
- (B) = Gate pulse for the MOSFET  $Q_1$
- (C) = Voltage across the primary winding
- (D) = Current through MOSFET  $Q_1$
- (E) = Current through the diode  $D_1$
- (F) = Voltage across the MOSFET  $Q_1$



# Power Electronic Converters in Electric Drive Systems


## DC DRIVES

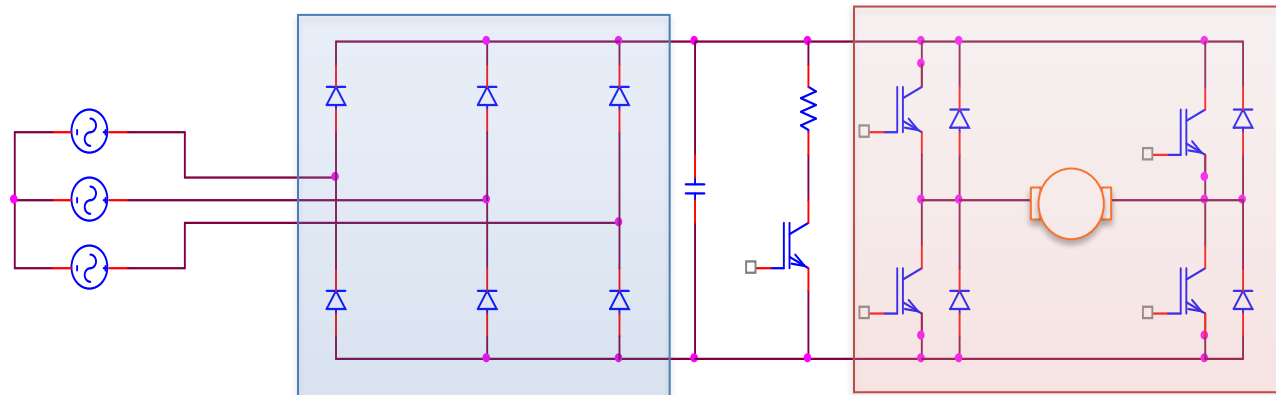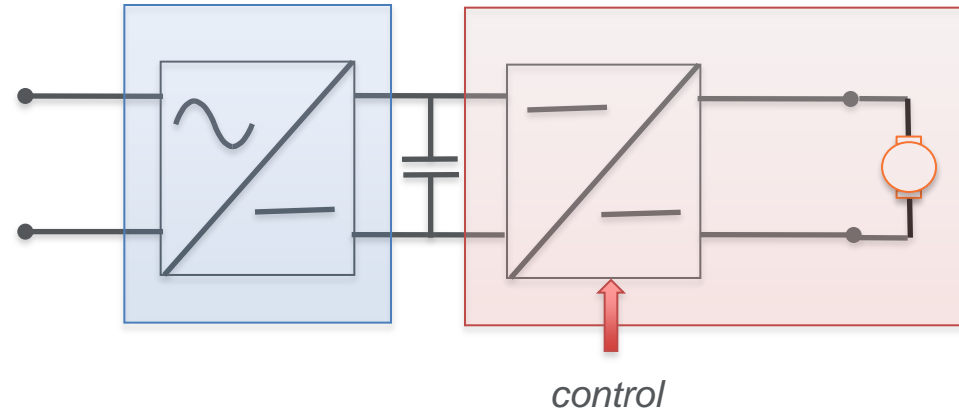


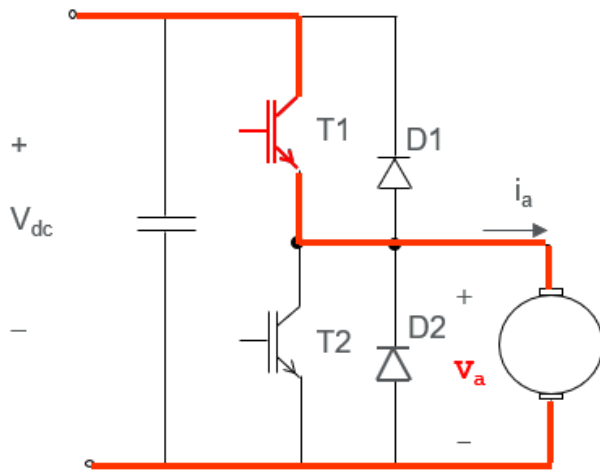
# Power Electronic Converters in Electric Drive Systems

Two-quadrant Converter


Motor can deliver energy to the supply input bus!



T1 conducts  $\rightarrow v_a = V_{dc}$

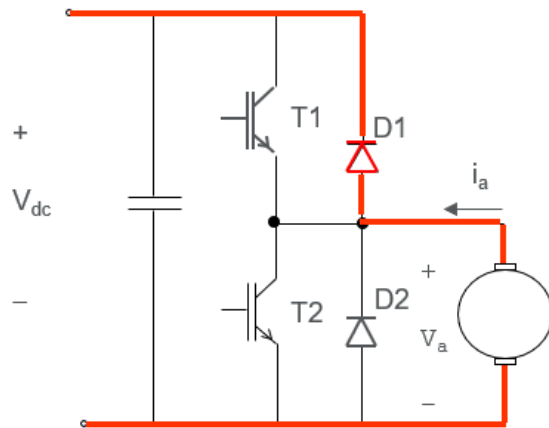
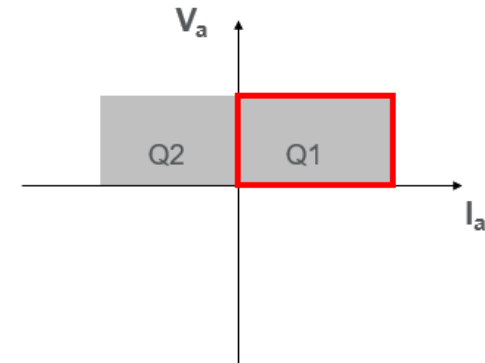


D1 conducts  $\rightarrow v_a = V_{dc}$

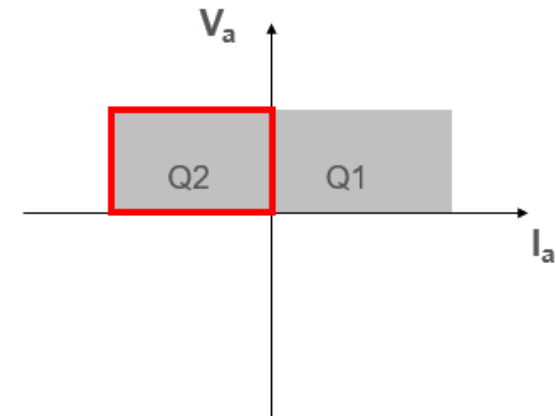

# Power Electronic Converters in Electric Drive Systems

## DC-DC: Four-quadrant Converter

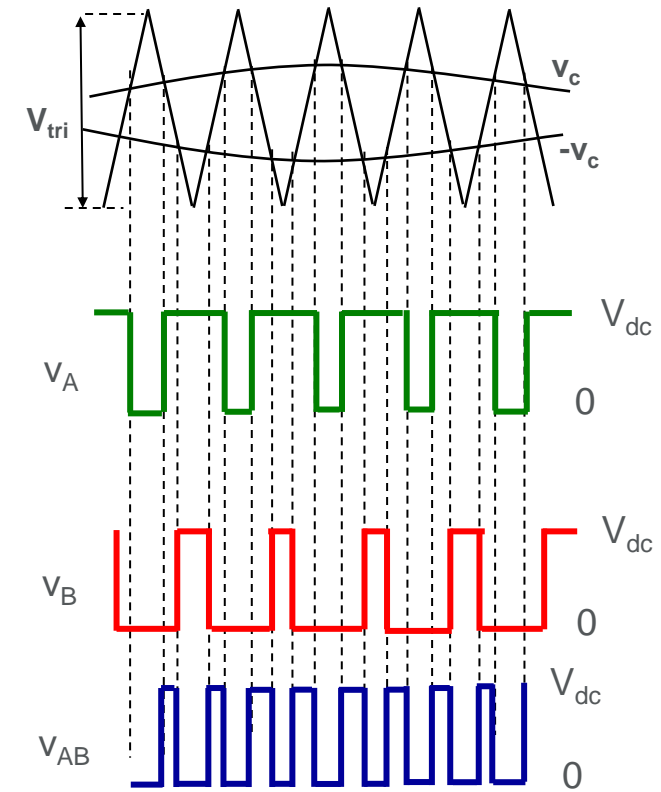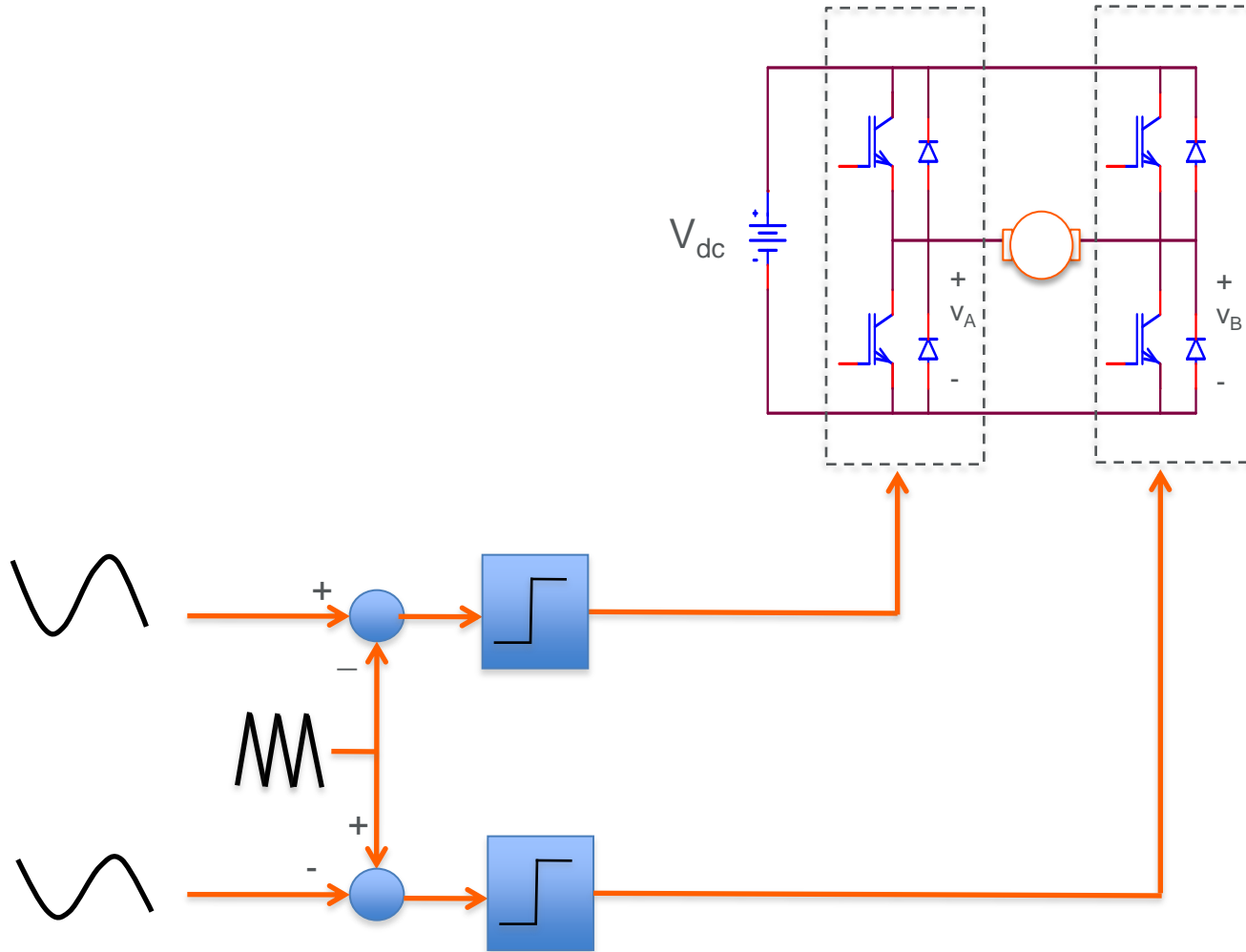



***TTM Technologies***

*Inspiring Innovation*