

Load power sources for peak efficiency

James Colotti

Eaton Corp, Melville, NY

When attempting to load a power source, you might instinctively make the load resistance equal to the Thevenin-equivalent power-supply resistance. This approach, however, yields only 50% efficiency. There's a better way.

A derivation of the maximum efficiency for the simplified circuit shown in Fig 1 leads to the trivial solution of infinite load resistance. A more realistic power source (Fig 2), however, constantly dissipates power through R_p .

Now you can find a unique, finite value for R_L . Consider the circuit shown in Fig 3. With all

resistances represented in terms of the series resistance R_s (ie, $R_p = \alpha R_s$ and $R_L = \beta R_s$),

$$\begin{aligned} \text{OUTPUT POWER} &= P_{\text{OUT}} \\ &= \left(\frac{V}{R_s}\right)^2 \frac{\alpha^2 \beta R_s}{(\alpha + \beta + \alpha\beta)^2} \end{aligned} \quad (1)$$

$$\text{INPUT POWER} = P_{\text{IN}} = \frac{V^2 (\alpha + \beta)}{R_s (\alpha + \beta + \alpha\beta)} \quad (2)$$

$$\begin{aligned} \text{EFFICIENCY} &= \frac{P_{\text{OUT}}}{P_{\text{IN}}} \times 100\% \\ &= \frac{100\%}{\frac{1}{\beta} + \frac{2}{\alpha} + 1 + \frac{\beta}{\alpha^2} + \frac{\beta}{\alpha}} \end{aligned} \quad (3)$$

$$f(\beta) = \frac{1}{\beta} + \frac{2}{\alpha} + 1 + \frac{\beta}{\alpha^2} + \frac{\beta}{\alpha} \quad (4)$$

$$\frac{df(\beta)}{d\beta} = -\frac{1}{\beta^2} + \frac{2}{\alpha^2} + \frac{1}{\alpha} = 0. \quad (5)$$

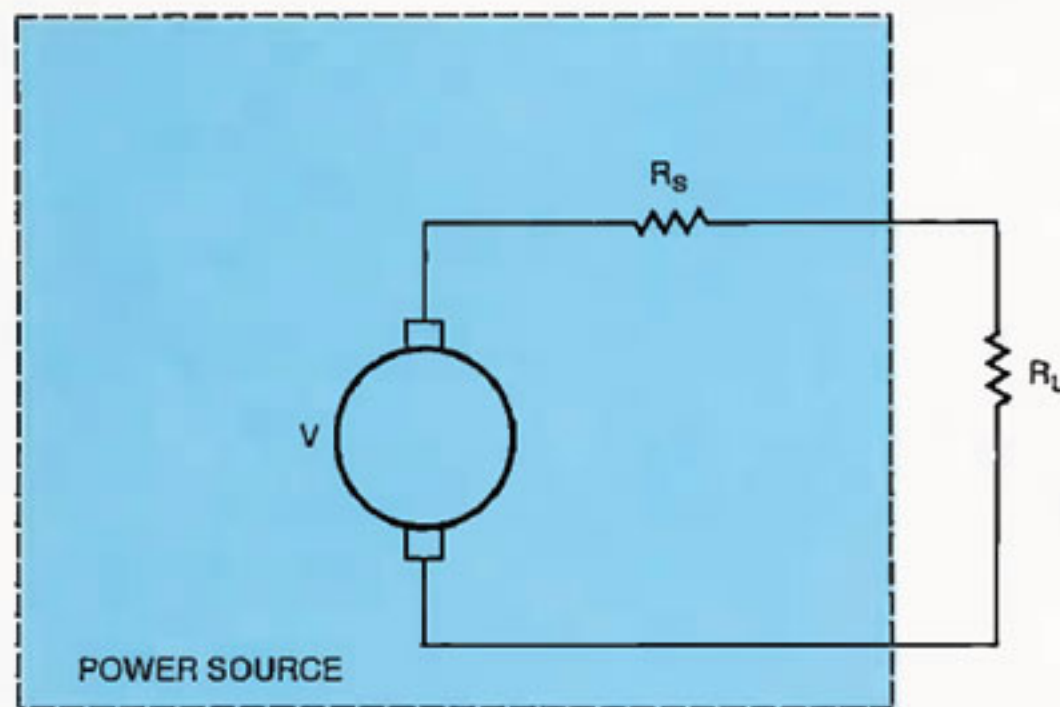


Fig 1—A simplified power-source model produces a trivial solution for load resistance.

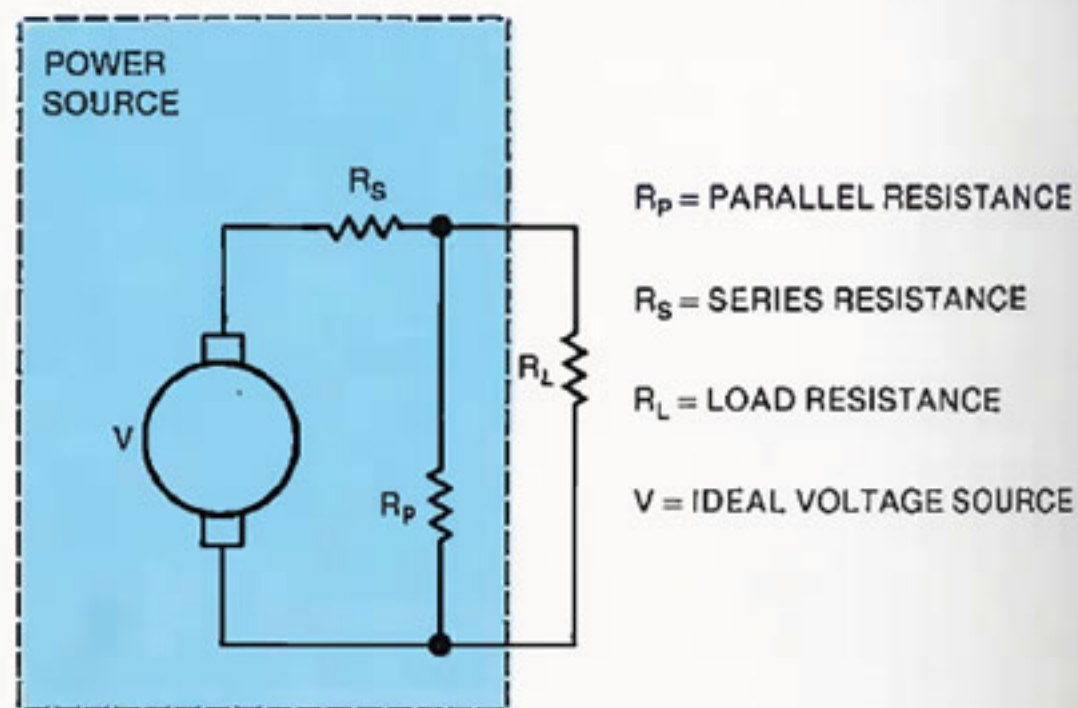


Fig 2—A more realistic power-source model constantly dissipates power through R_p .

Design Ideas

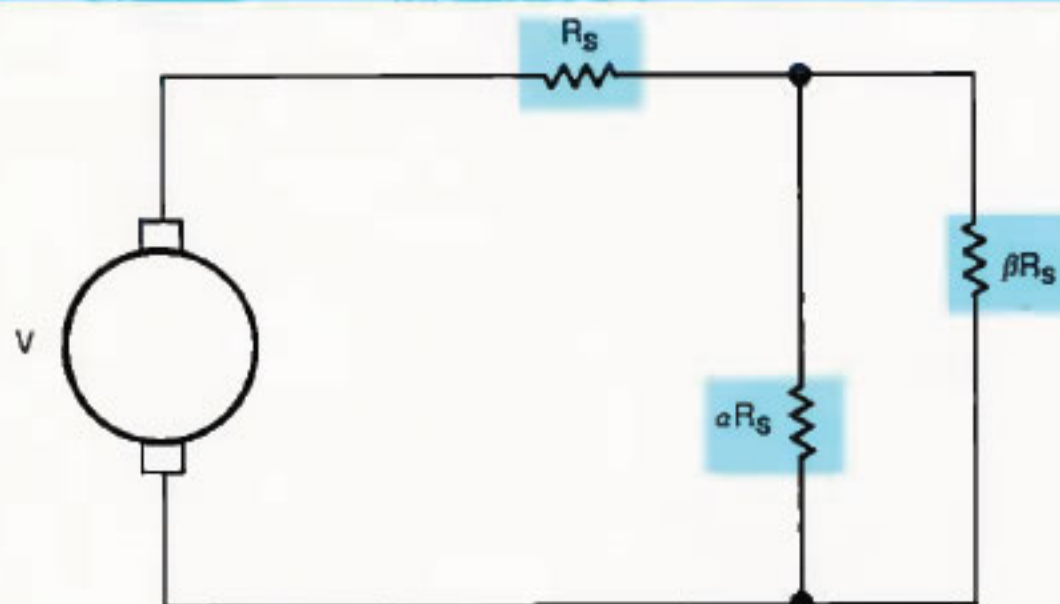


Fig 3—Determination of optimum loading starts with a representation of all resistances in terms of the series resistance.

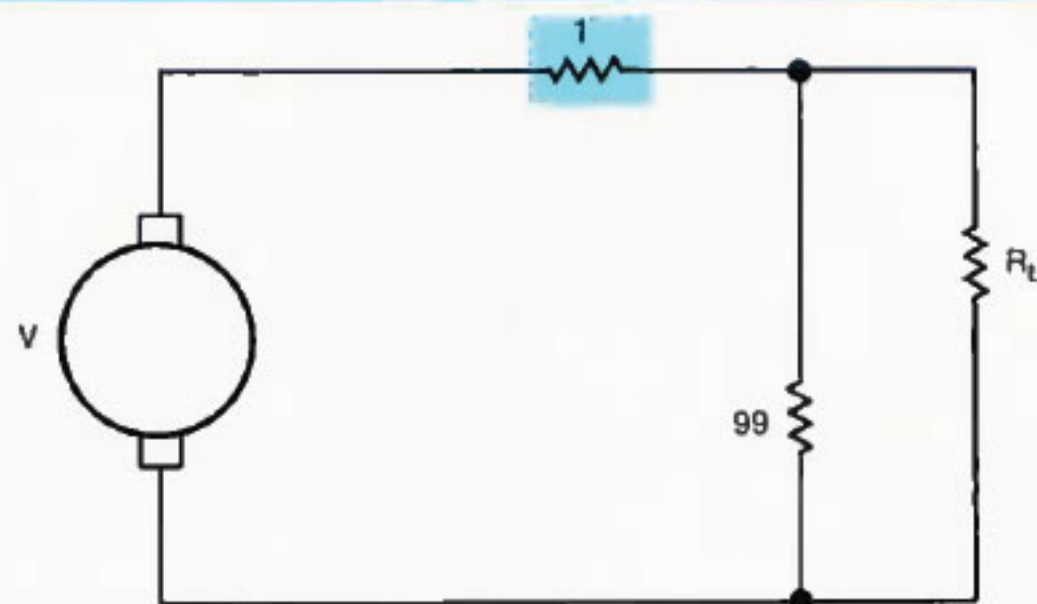


Fig 4—The sought-after series resistance is the open-loop resistance; closed-loop resistance can appear to be several orders of magnitude less than the actual resistance.

Thus, the efficiency reaches a maximum value for the value of β where $f(\beta)$ has a minimum. This relationship implies that for maximum efficiency,

$$b = \frac{\alpha}{\sqrt{1 + \alpha}} \quad (6)$$

As an example, calculate the value of R_L that provides the maximum efficiency for the circuit shown in **Fig 4**:

$$\begin{aligned} R_s &= 1 \Omega \\ \alpha &= \frac{99}{1} = 99 \\ \therefore \beta &= \frac{99}{\sqrt{1 + 99}} = 9.9 \end{aligned}$$

MAX EFFICIENCY

$$\begin{aligned} &= \frac{100\%}{\frac{1}{9.9} + \frac{2}{9.9} + 1 + \frac{9.9}{(99)^2} + \frac{9.9}{99}} \\ &= 82\% \end{aligned}$$

$$R_L = \beta R_s = (9.9)(1) = 9.9 \Omega.$$

Note that when determining R_s , you are seeking the open-loop resistance. In a closed loop, the power-source series resistance can appear to be several orders of magnitude less than the actual resistance. As illustrated in **Fig 5**, the larger you make α (the ratio of parallel resistance to series

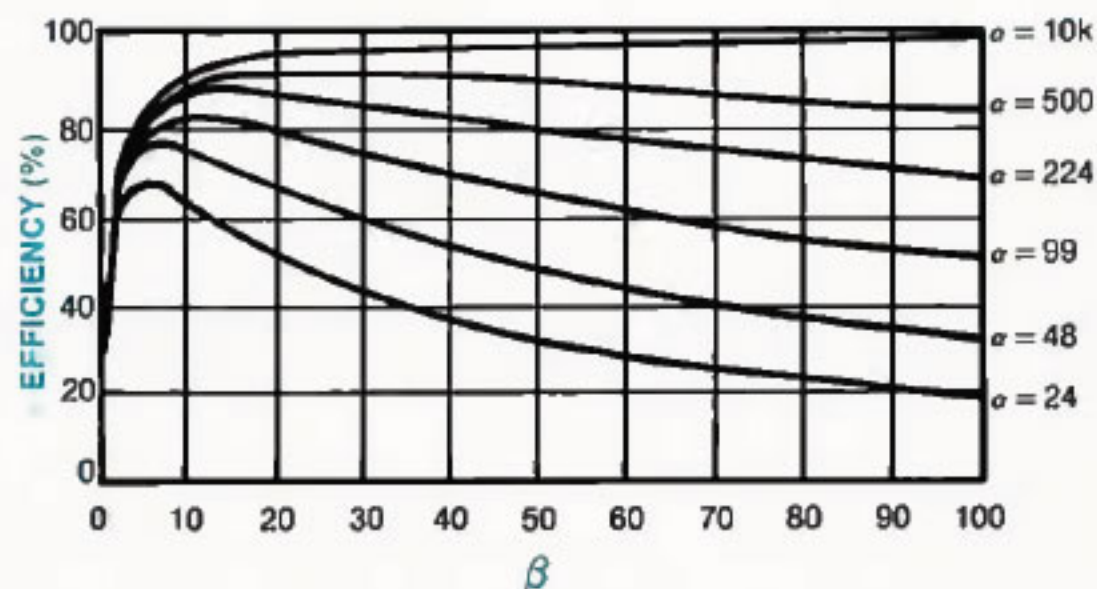


Fig 5—Compare loading efficiency to load resistance for a range of losses.

resistance) the more slowly the efficiency varies with respect to β . Reducing α —increasing parallel losses—lowers the peak efficiency.

Consider the case where $\alpha=24$. The maximum efficiency obtained would be 67% when $R_L=4.8R$. If you reduce R_L from $4.8R$ to $2R$, the efficiency drops to 59%. However, when you increase α to 10k, the maximum efficiency obtained is 98% when $R_L=100R$. R_L can now vary by $\pm 75\%$ and change the efficiency by no more than -2.1% .

EDN

To Vote For This Design, Circle No 456