

# Chapter 10


## Input Filter Design

---


- 10.1 Introduction
  - 10.1.1 Conducted EMI
  - 10.1.2 The Input Filter Design Problem
- 10.2 Effect of an Input Filter on Converter Transfer Functions
  - 10.2.1 Discussion
  - 10.2.2 Impedance Inequalities
- 10.3 Buck Converter Example
  - 10.3.1 Effect of Undamped Input Filter
  - 10.3.2 Damping the Input Filter
- 10.4 Design of a Damped Input Filter
  - 10.4.1  $R_f$ - $C_b$  Parallel Damping
  - 10.4.2  $R_f$ - $L_b$  Parallel Damping
  - 10.4.3  $R_f$ - $L_b$  Series Damping
  - 10.4.4 Cascading Filter Sections
  - 10.4.5 Example: Two Stage Input Filter
- 10.5 Summary of Key Points

# 10.1.1 Conducted Electromagnetic Interference (EMI)

Input current  $i_g(t)$  is *pulsating*.

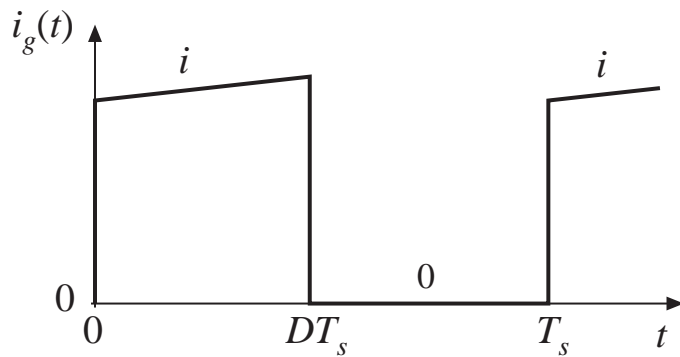

*Buck converter example*

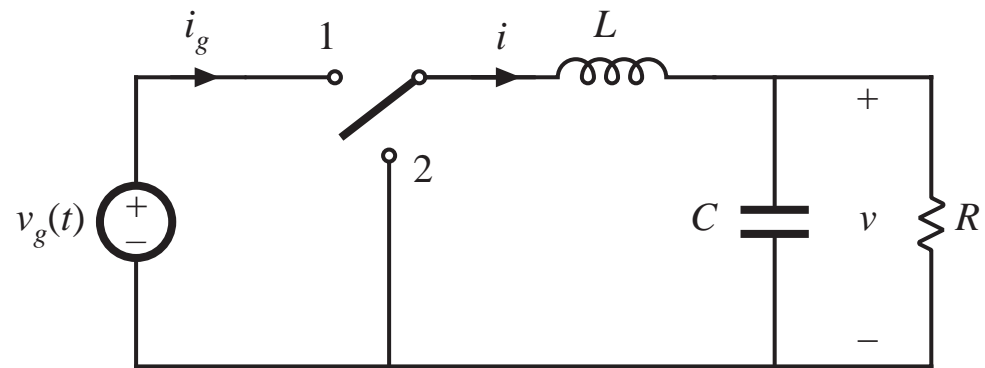


Approximate Fourier series of  $i_g(t)$ :

$$i_g(t) = DI + \sum_{k=1}^{\infty} \frac{2I}{k\pi} \sin(k\pi D) \cos(k\omega t)$$

High frequency current harmonics of substantial amplitude are injected back into  $v_g(t)$  source. These harmonics can interfere with operation of nearby equipment. Regulations limit their amplitude, typically to values of 10  $\mu\text{A}$  to 100  $\mu\text{A}$ .

# Addition of Low-Pass Filter

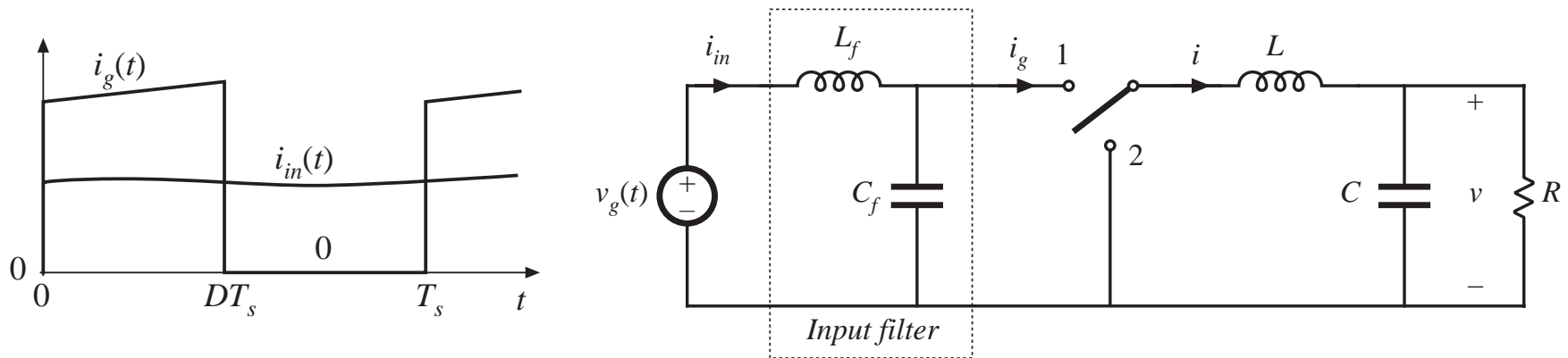

Magnitudes and phases of input current harmonics are modified by input filter transfer function  $H(s)$ :

$$i_{in}(t) = H(0)DI + \sum_{k=1}^{\infty} \|H(kj\omega)\| \frac{2I}{k\pi} \sin(k\pi D) \cos(k\omega t + \angle H(kj\omega))$$


The input filter may be required to attenuate the current harmonics by factors of 80 dB or more.

# Electromagnetic Compatibility

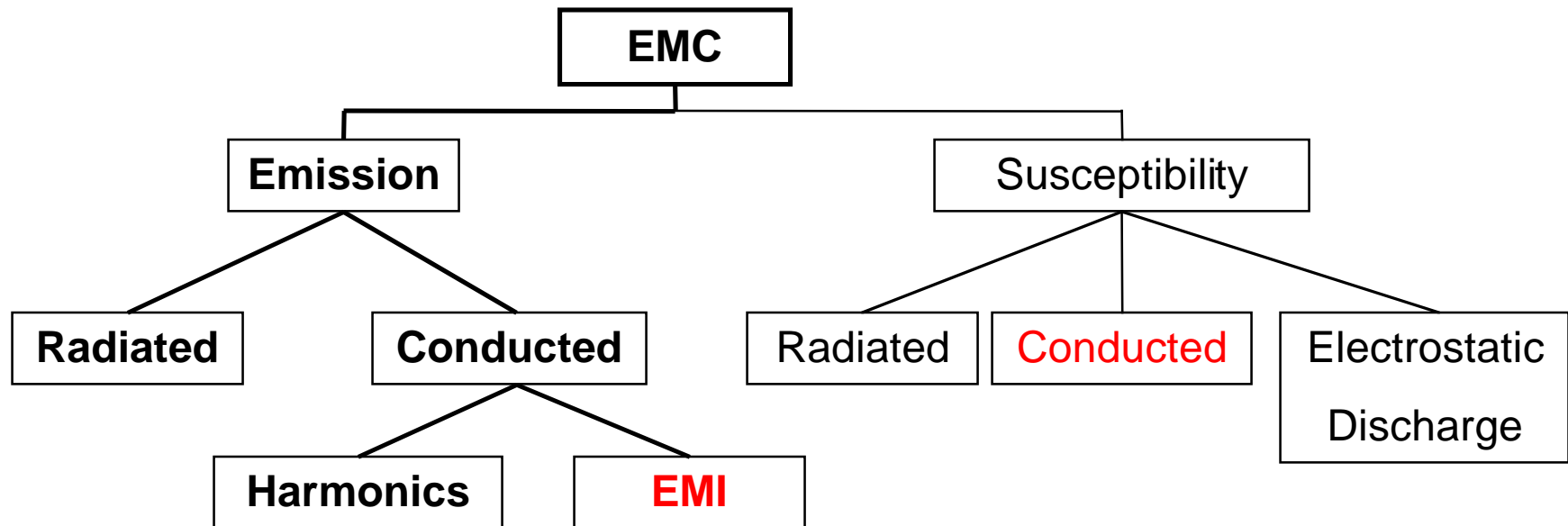
## Ability of the device (e.g. power supply) to:

function satisfactorily in its electromagnetic environment  
(susceptibility or immunity aspect)

without introducing intolerable electromagnetic disturbances (**emission** aspect)



# Conducted EMI

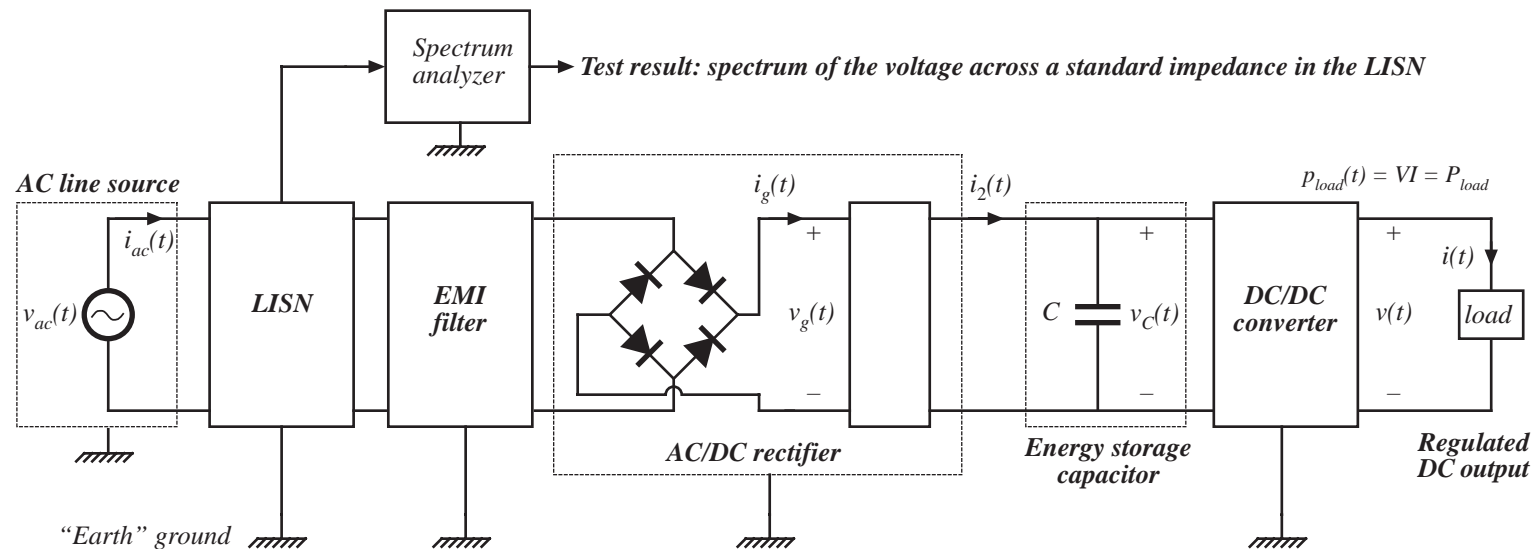


## Sample of EMC regulations that include limits on radio-frequency emissions:

European Community Directive on EMC: Euro-Norm EN 55022 or 55081, earlier known as CISPR 22

National standards: VDE (German), FCC (US)


# LISN

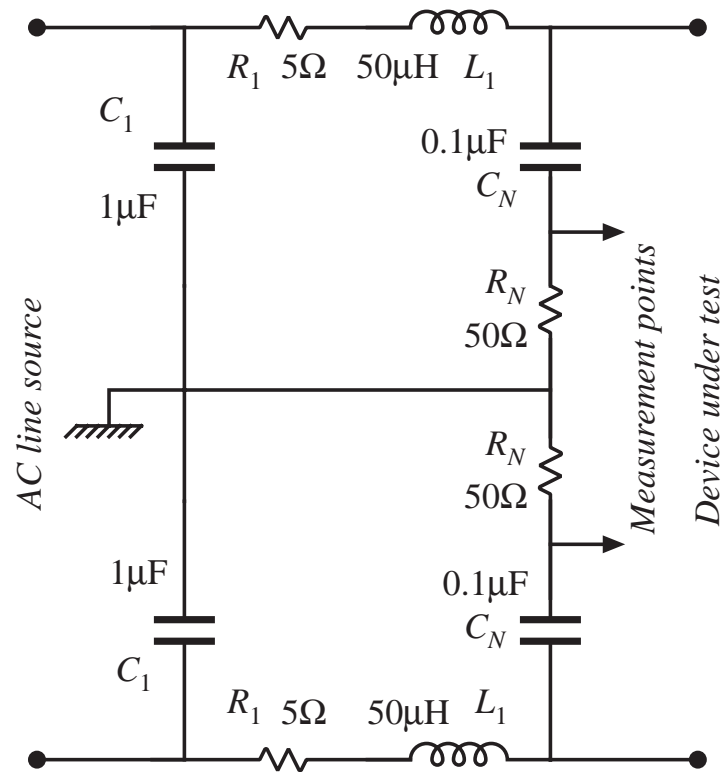

LISN example


- **LISN:** “Line Impedance Stabilization Network,” or “artificial mains network”
- **Purpose:** to standardize impedance of the power source used to supply the device under test
- Spectrum of conducted emissions is measured across the standard impedance (50  $\Omega$  above 150kHz)

# An Example of EMI Limits

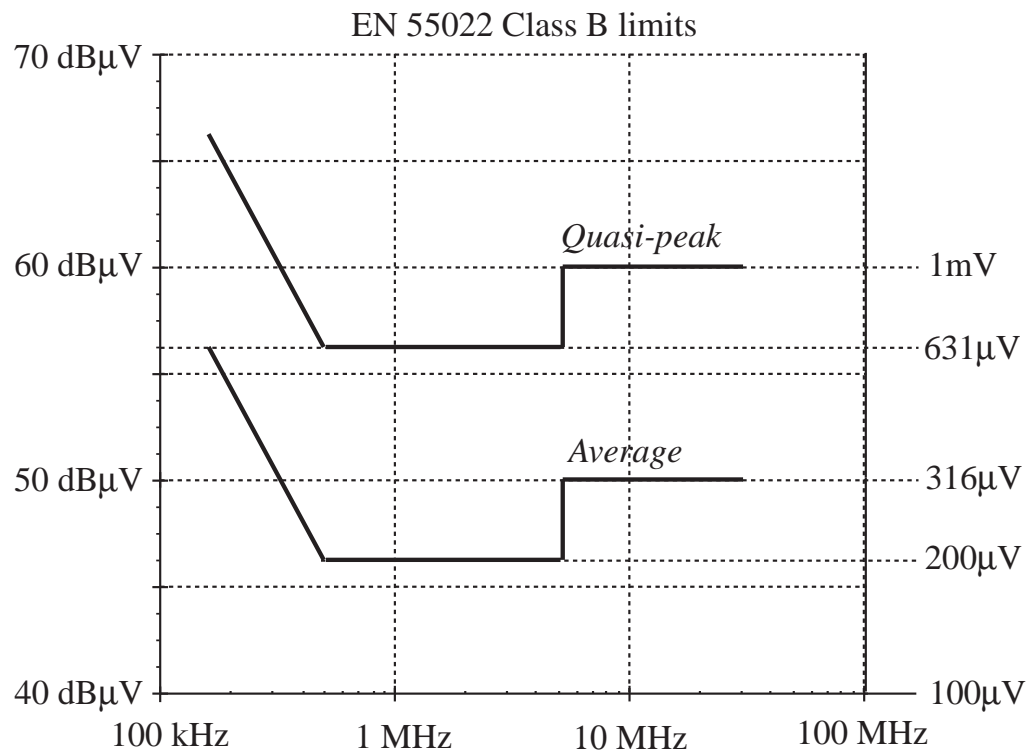

- Frequency range: 150kHz-30MHz
- Class B: residential environment
- Quasi-peak/Average: two different setups of the measurement device (such as narrow-band voltmeter or spectrum analyzer)
- Measurement bandwidth: 9kHz

# Differential and Common-Mode EMI

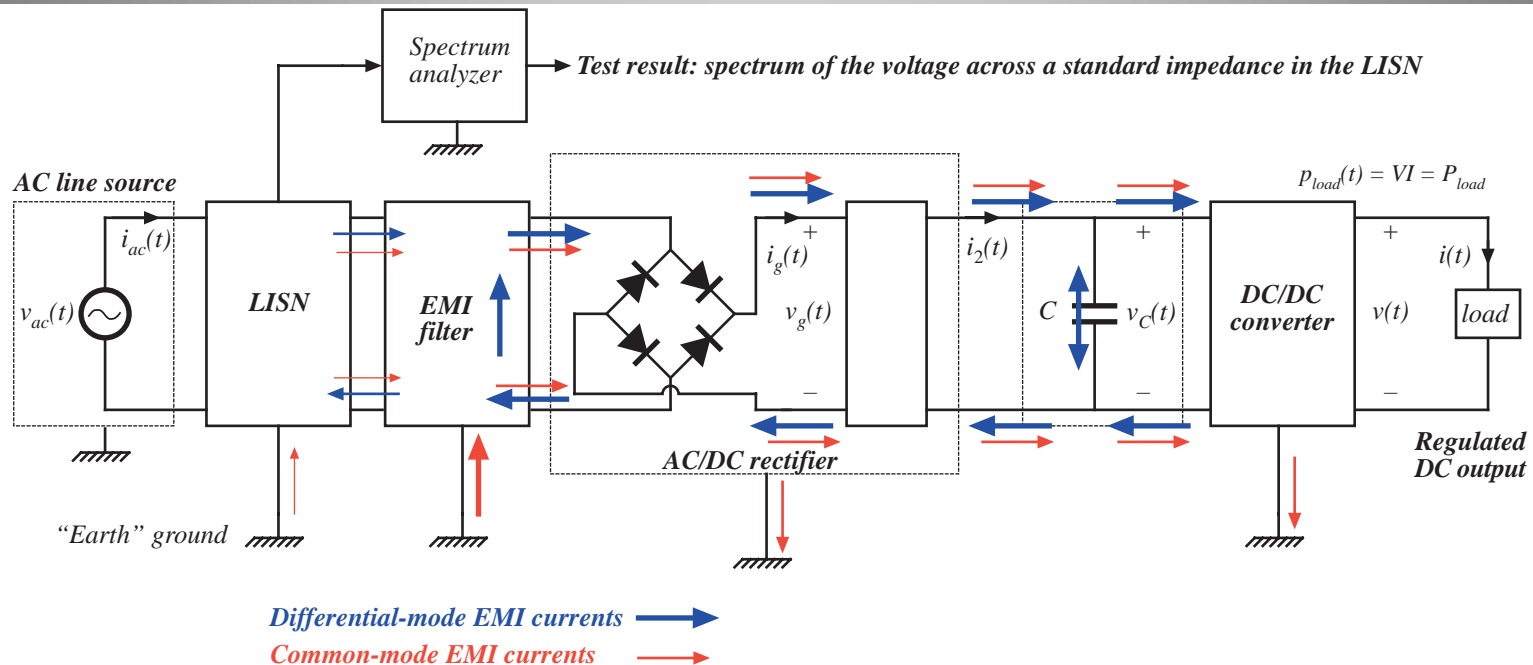


- **Differential mode EMI:** input current waveform of the PFC. Differential-mode noise depends on the PFC realization and circuit parameters.
- **Common-mode EMI:** currents through parasitic capacitances between high  $dv/dt$  points and earth ground (such as from transistor drain to transistor heat sink). Common-mode noise depends on:  $dv/dt$ , circuit and mechanical layout.



## 10.1.2 The Input Filter Design Problem

A typical design approach:

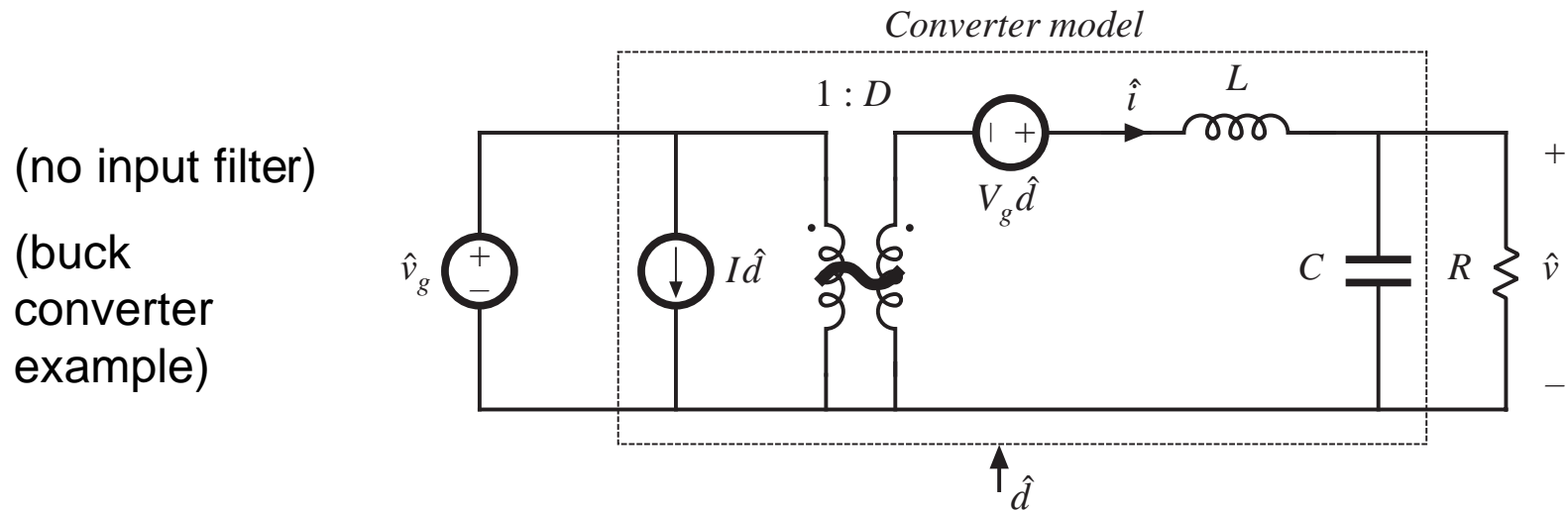
1. Engineer designs switching regulator that meets specifications (stability, transient response, output impedance, etc.). In performing this design, a basic converter model is employed, such as the one below:




## Input Filter Design Problem, p. 2

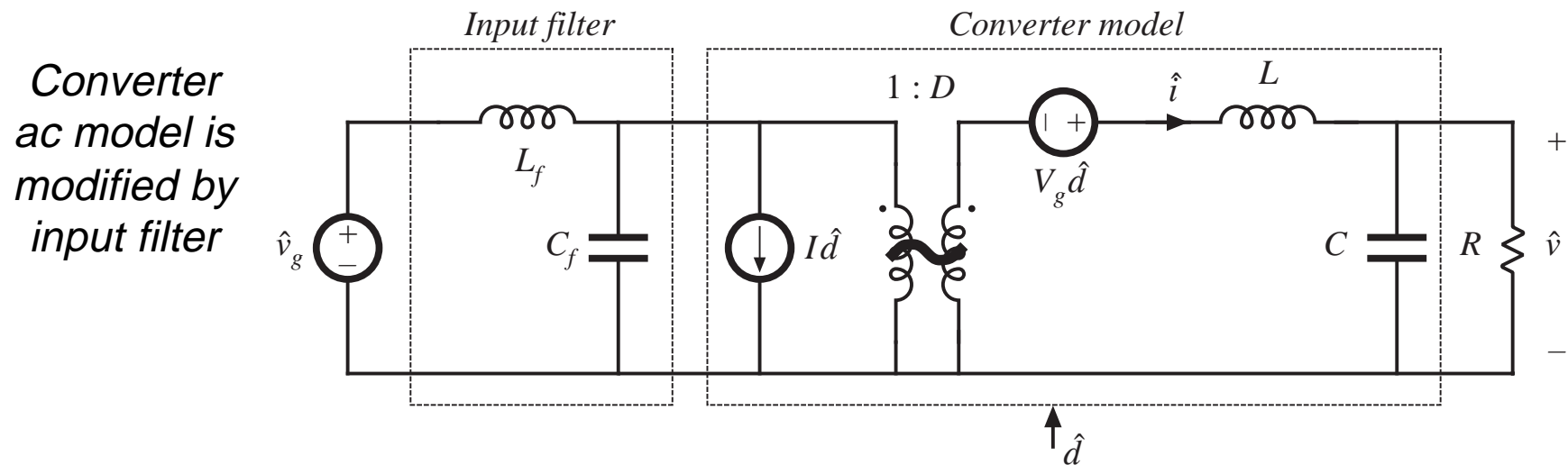2. Later, the problem of conducted EMI is addressed. An input filter is added, that attenuates harmonics sufficiently to meet regulations.
3. A new problem arises: the controller no longer meets dynamic response specifications. The controller may even become unstable.

Reason: input filter changes converter transfer functions



# Input Filter Design Problem, p. 3

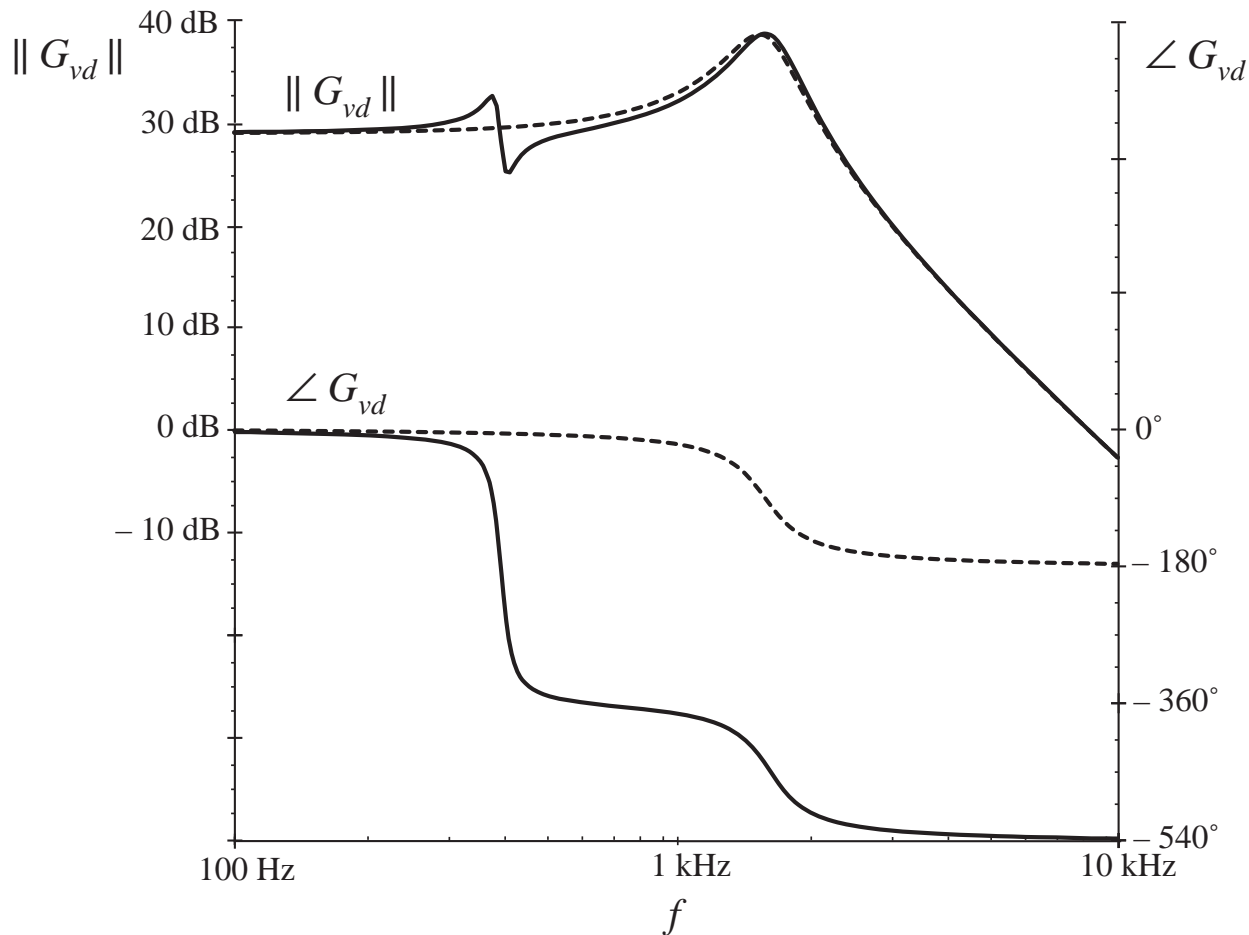


Effect of  $L$ - $C$  input filter on control-to-output transfer function  $G_{vd}(s)$ , buck converter example.

*Dashed lines:* original magnitude and phase

*Solid lines:* with addition of input filter
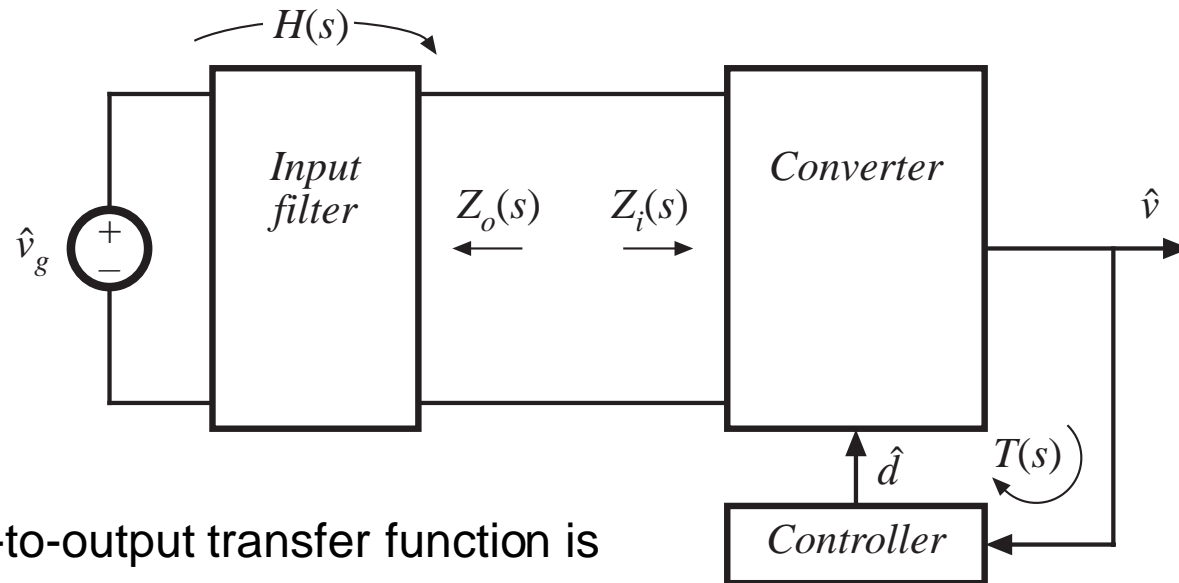
## 10.2 Effect of an Input Filter on Converter Transfer Functions



Control-to-output transfer function is


$$G_{vd}(s) = \frac{\hat{v}(s)}{\hat{d}(s)} \Big|_{\hat{v}_g(s)=0}$$

# Determination of $G_{vd}(s)$

$$G_{vd}(s) = \left. \frac{\hat{v}(s)}{\hat{d}(s)} \right|_{\hat{v}_g(s)=0}$$

$\hat{v}_g(s)$  source  $\rightarrow$  short circuit

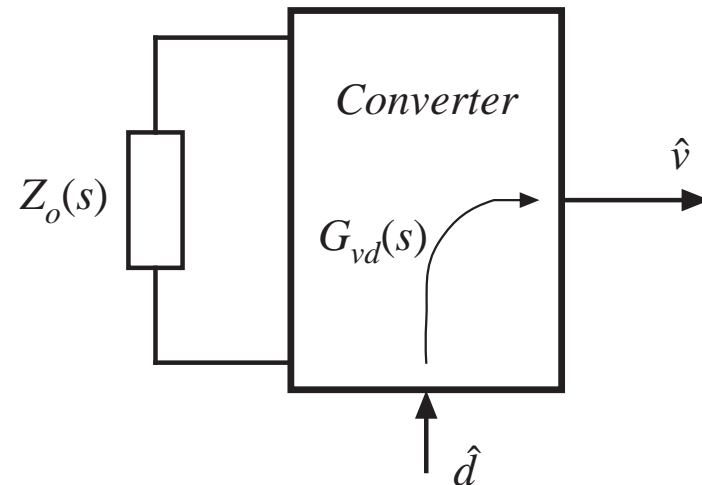$Z_o(s)$  = output impedance of  
input filter



We will use Middlebrook's Extra Element Theorem to show that the input filter modifies  $G_{vd}(s)$  as follows:

$$G_{vd}(s) = \left( G_{vd}(s) \Big|_{Z_o(s)=0} \right) \frac{\left( 1 + \frac{Z_o(s)}{Z_N(s)} \right)}{\left( 1 + \frac{Z_o(s)}{Z_D(s)} \right)}$$

# How an input filter changes $G_{vd}(s)$

## Summary of result

---

$$G_{vd}(s) = \left( G_{vd}(s) \Big|_{Z_o(s)=0} \right) \frac{\left( 1 + \frac{Z_o(s)}{Z_N(s)} \right)}{\left( 1 + \frac{Z_o(s)}{Z_D(s)} \right)}$$

$G_{vd}(s) \Big|_{Z_o(s)=0}$  is the original transfer function, before addition of input filter

$Z_D(s) = Z_i(s) \Big|_{\hat{d}(s)=0}$  is the converter input impedance, with  $\hat{d}$  set to zero

$Z_N(s) = Z_i(s) \Big|_{\hat{v}(s) \xrightarrow{\text{null}} 0}$  is the converter input impedance, with the output  $\hat{v}$  nulled to zero

(see Appendix C for proof using EET)

# Design criteria for basic converters

**Table 10.1** Input filter design criteria for basic converters

| Converter  | $Z_N(s)$  | $Z_D(s)$  | $Z_e(s)$         |
|------------|---|---|------------------|
| Buck       | $-\frac{R}{D^2}$  | $\frac{R}{D^2} \frac{\left(1 + s\frac{L}{R} + s^2LC\right)}{\left(1 + sRC\right)}$                      | $\frac{sL}{D^2}$ |
| Boost      | $-D'^2R \left(1 - \frac{sL}{D'^2R}\right)$              | $D'^2R \frac{\left(1 + s\frac{L}{D'^2R} + s^2\frac{LC}{D'^2}\right)}{\left(1 + sRC\right)}$             | $sL$             |
| Buck–boost | $-\frac{D'^2R}{D^2} \left(1 - \frac{sDL}{D'^2R}\right)$ | $\frac{D'^2R}{D^2} \frac{\left(1 + s\frac{L}{D'^2R} + s^2\frac{LC}{D'^2}\right)}{\left(1 + sRC\right)}$ | $\frac{sL}{D^2}$ |

## 10.2.2 Impedance Inequalities

---

$$G_{vd}(s) = \left( G_{vd}(s) \Big|_{Z_o(s)=0} \right) \frac{\left( 1 + \frac{Z_o(s)}{Z_N(s)} \right)}{\left( 1 + \frac{Z_o(s)}{Z_D(s)} \right)}$$

The *correction factor*  $\frac{\left( 1 + \frac{Z_o(s)}{Z_N(s)} \right)}{\left( 1 + \frac{Z_o(s)}{Z_D(s)} \right)}$  shows how the input filter modifies the transfer function  $G_{vd}(s)$ .

The correction factor has a magnitude of approximately unity provided that the following inequalities are satisfied:

$$\begin{aligned} \|Z_o\| &\ll \|Z_N\|, \quad \text{and} \\ \|Z_o\| &\ll \|Z_D\| \end{aligned}$$

These provide design criteria, which are relatively easy to apply.



# Effect of input filter on converter output impedance

---

A similar analysis leads to the following inequalities, which guarantee that the converter output impedance is not substantially affected by the input filter:


$$\|Z_o\| \ll \|Z_e\|, \quad \text{and} \\ \|Z_o\| \ll \|Z_D\|$$

The quantity  $Z_e$  is given by:

$$Z_e = Z_i \Big|_{\hat{v}=0}$$

(converter input impedance when the output is shorted)



## 10.2.1 Discussion

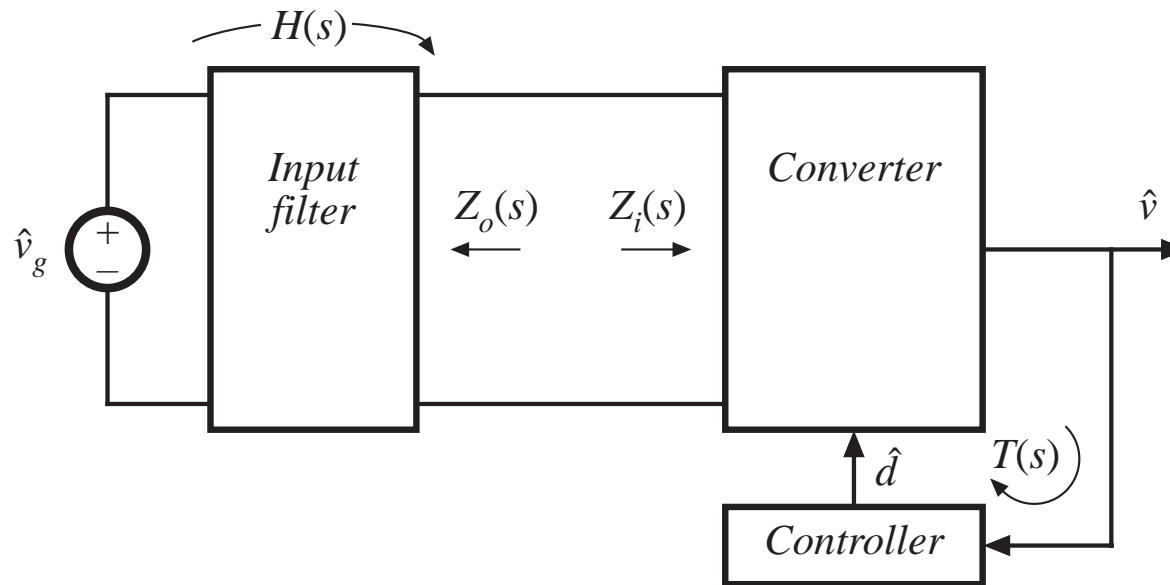

$Z_N(s) = Z_i(s) \Big|_{\hat{v}(s) \xrightarrow{\text{null}} 0}$  is the converter input impedance, with the output  $\hat{v}$  nulled to zero

Note that this is the same as the function performed by an ideal controller, which varies the duty cycle as necessary to maintain zero error of the output voltage. So  $Z_N$  coincides with the input impedance when an ideal feedback loop perfectly regulates the output voltage.
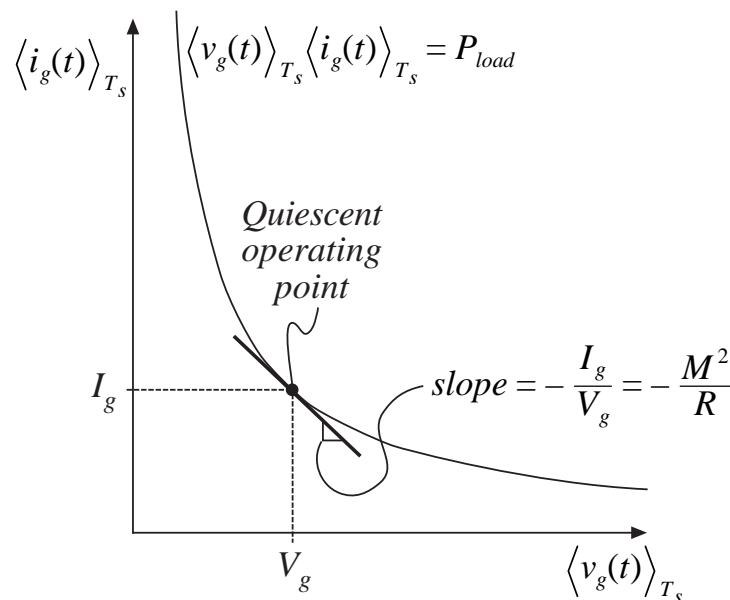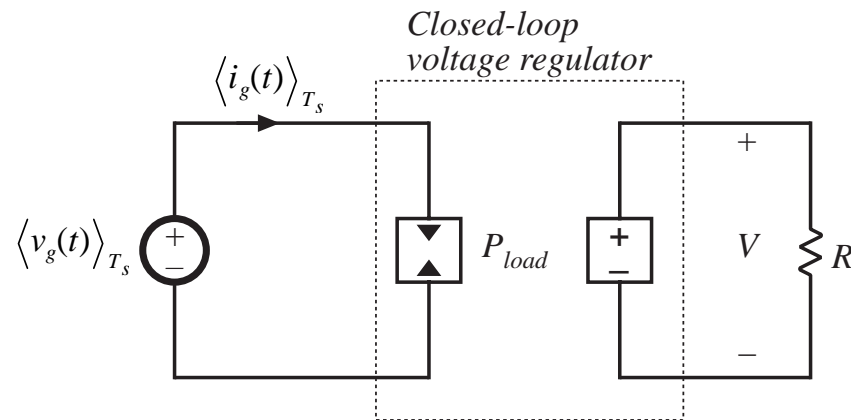
# When the output voltage is perfectly regulated



- For a given load characteristic, the output power  $P_{load}$  is independent of the converter input voltage
- If losses are negligible, then the input port  $i-v$  characteristic is a power sink characteristic, equal to  $P_{load}$ :

$$\langle v_g(t) \rangle_{T_s} \langle i_g(t) \rangle_{T_s} = P_{load}$$

- Incremental input resistance is negative, and is equal to:

$$-\frac{R}{M^2}$$

(same as dc asymptote of  $Z_N$ )

# Negative resistance oscillator

---

It can be shown that the closed-loop converter input impedance is given by:

$$\frac{1}{Z_i(s)} = \frac{1}{Z_N(s)} \frac{T(s)}{1 + T(s)} + \frac{1}{Z_D(s)} \frac{1}{1 + T(s)}$$

where  $T(s)$  is the converter loop gain.


At frequencies below the loop crossover frequency, the input impedance is approximately equal to  $Z_N$ , which is a negative resistance.

When an undamped or lightly damped input filter is connected to the regulator input port, the input filter can interact with  $Z_N$  to form a *negative resistance oscillator*.


# 10.3 Buck Converter Example

## 10.3.1 Effect of undamped input filter

Buck converter with input filter


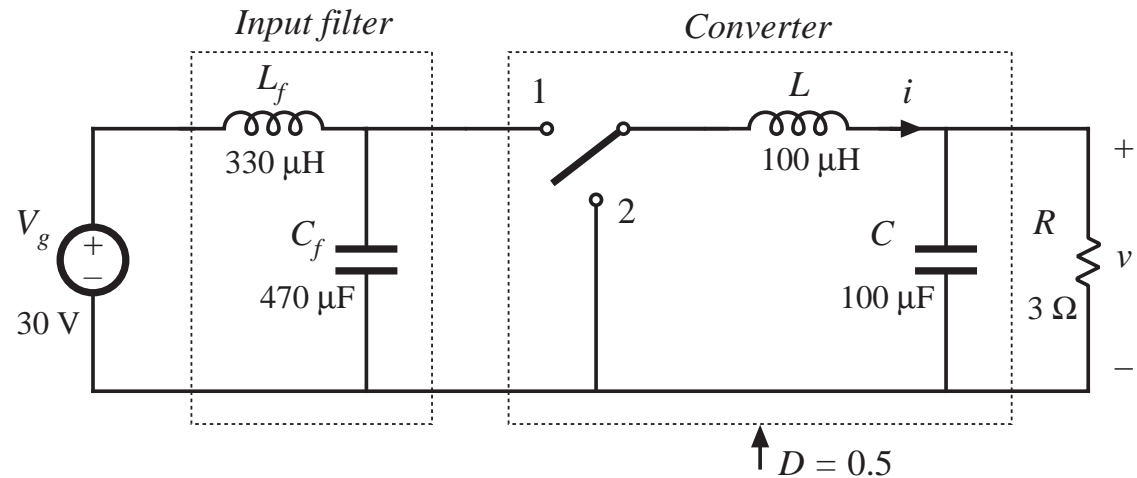


Small-signal model

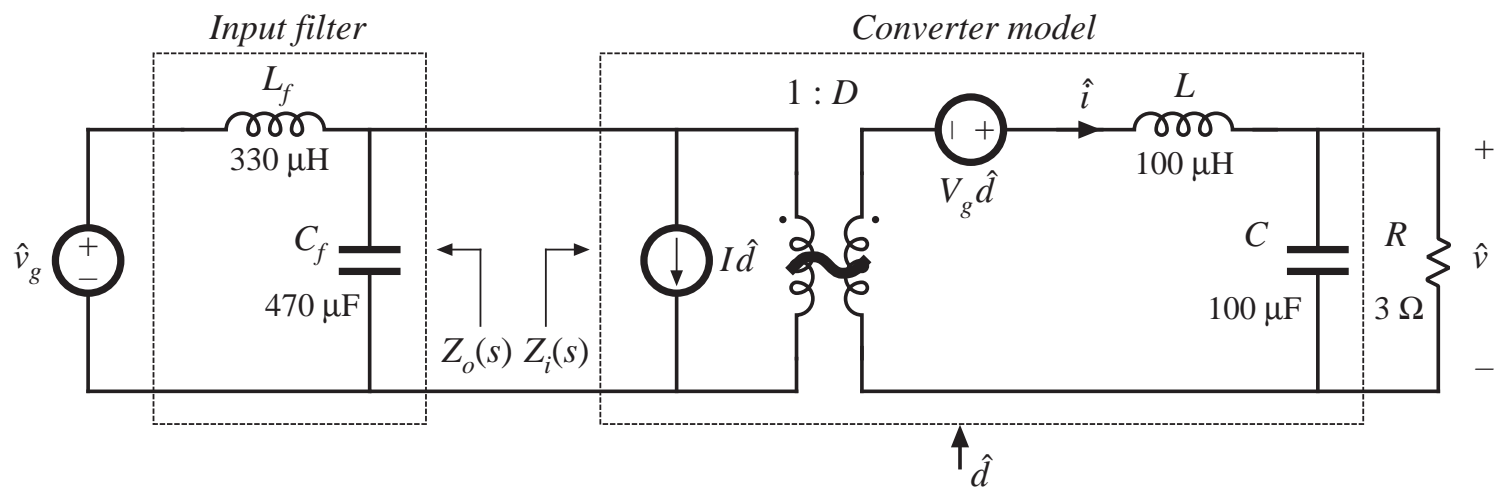

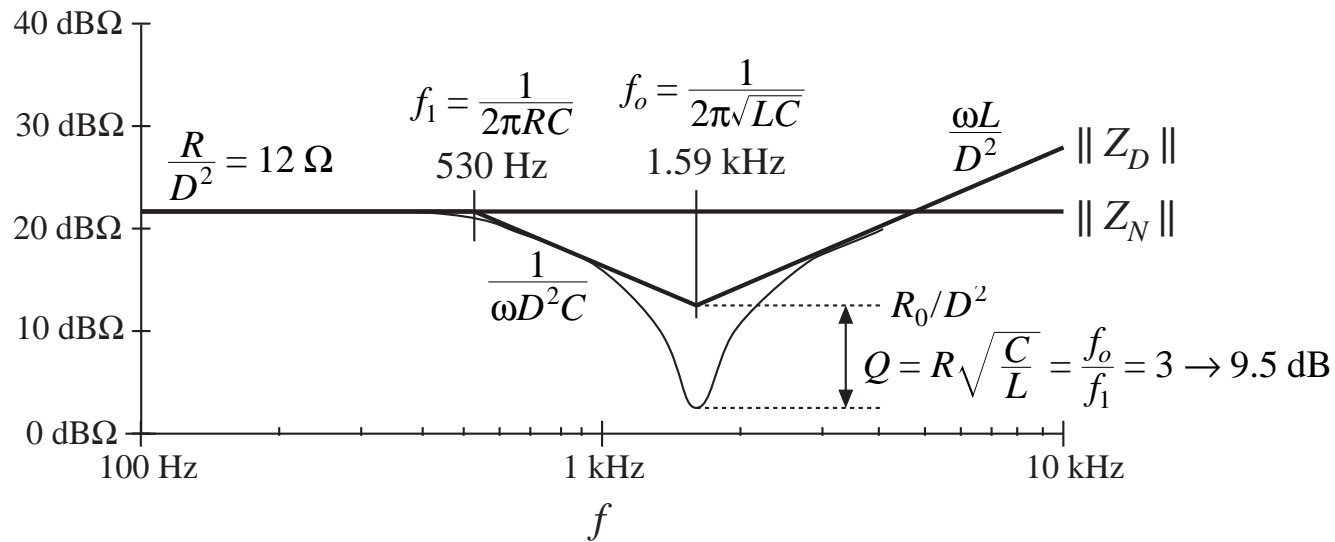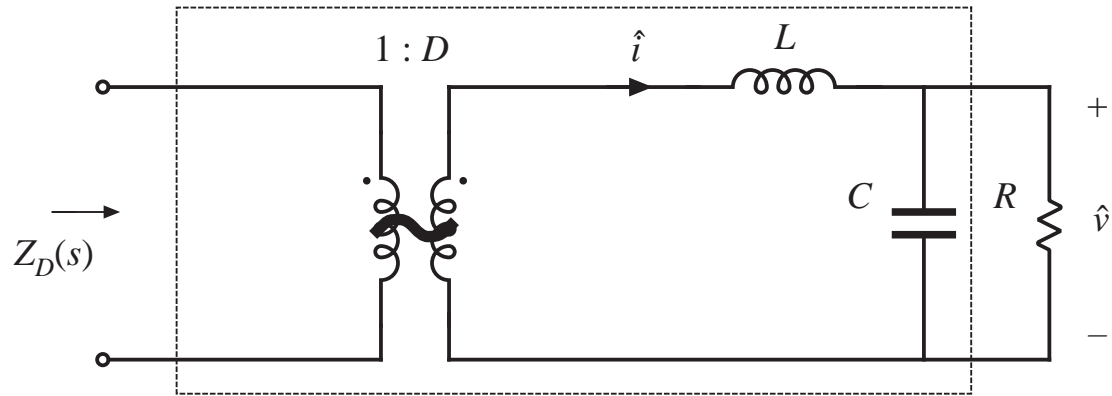
# Determination of $Z_D$

$$Z_D(s) = \frac{1}{D^2} \left( sL + R \parallel \frac{1}{sC} \right)$$



# Determination of $Z_N$

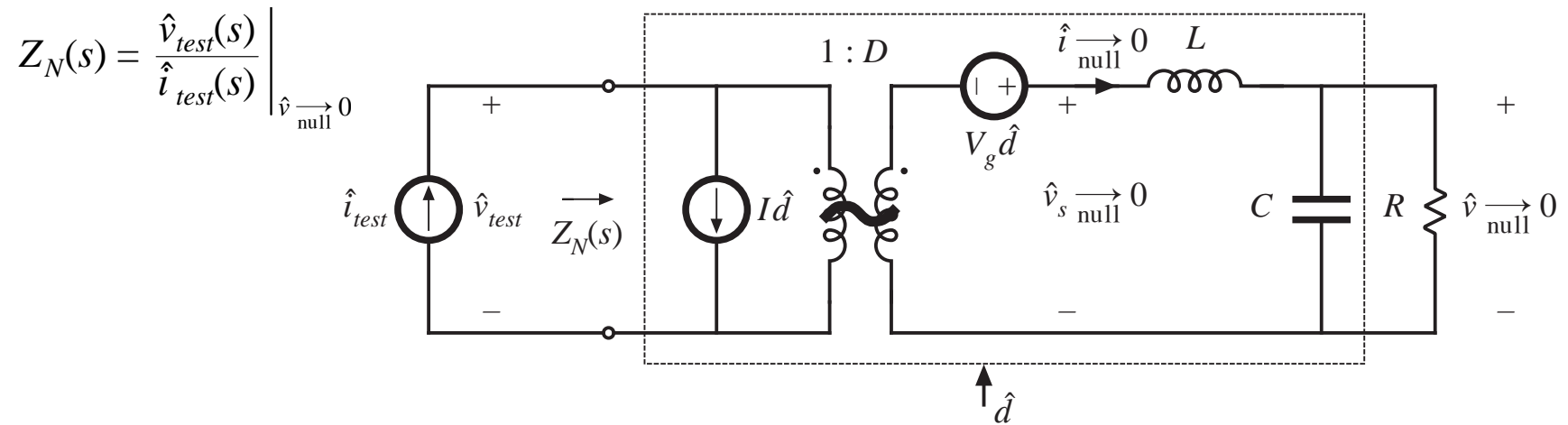

Solution:


$$\hat{i}_{test}(s) = I\hat{d}(s)$$

$$\hat{v}_{test}(s) = -\frac{V_g\hat{d}(s)}{D}$$


Hence,

$$Z_N(s) = \frac{\left(-\frac{V_g\hat{d}(s)}{D}\right)}{I\hat{d}(s)} = -\frac{R}{D^2}$$

# $Z_o$ of undamped input filter

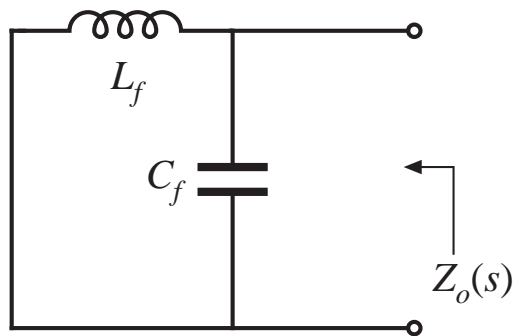
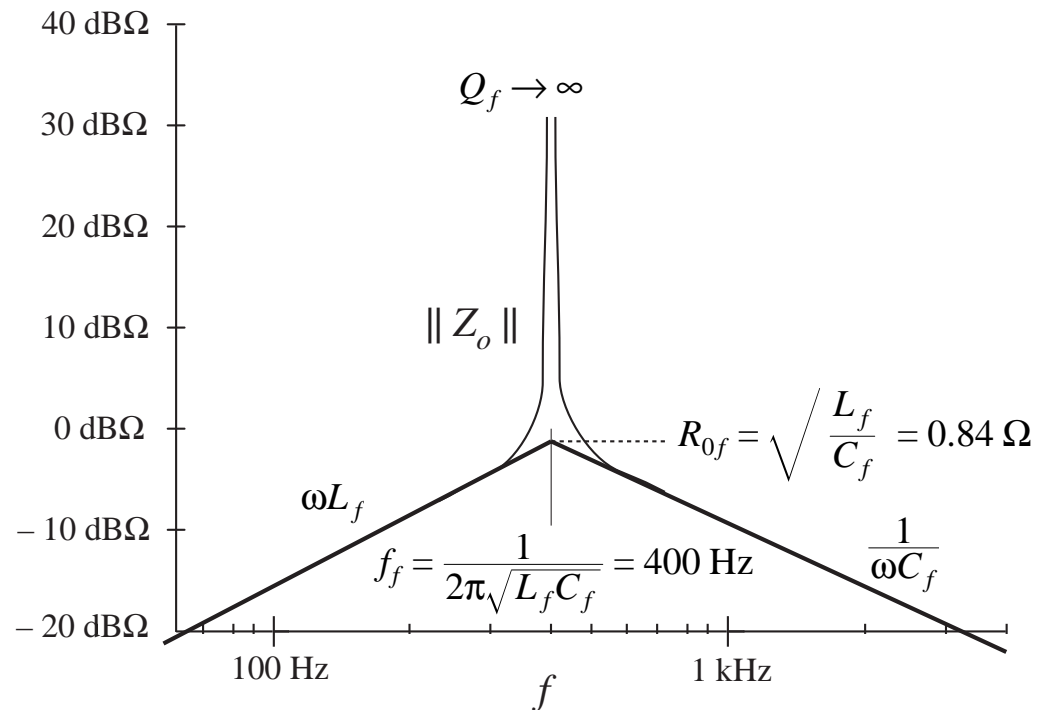
$$Z_o(s) = sL_f \parallel \frac{1}{sC_f}$$



No resistance, hence poles are undamped (infinite  $Q$ -factor).


In practice, losses limit  $Q$ -factor; nonetheless,  $Q_f$  may be very large.



Design criteria

$$\|Z_o\| \ll \|Z_N\|, \text{ and}$$


$$\|Z_o\| \ll \|Z_D\|$$

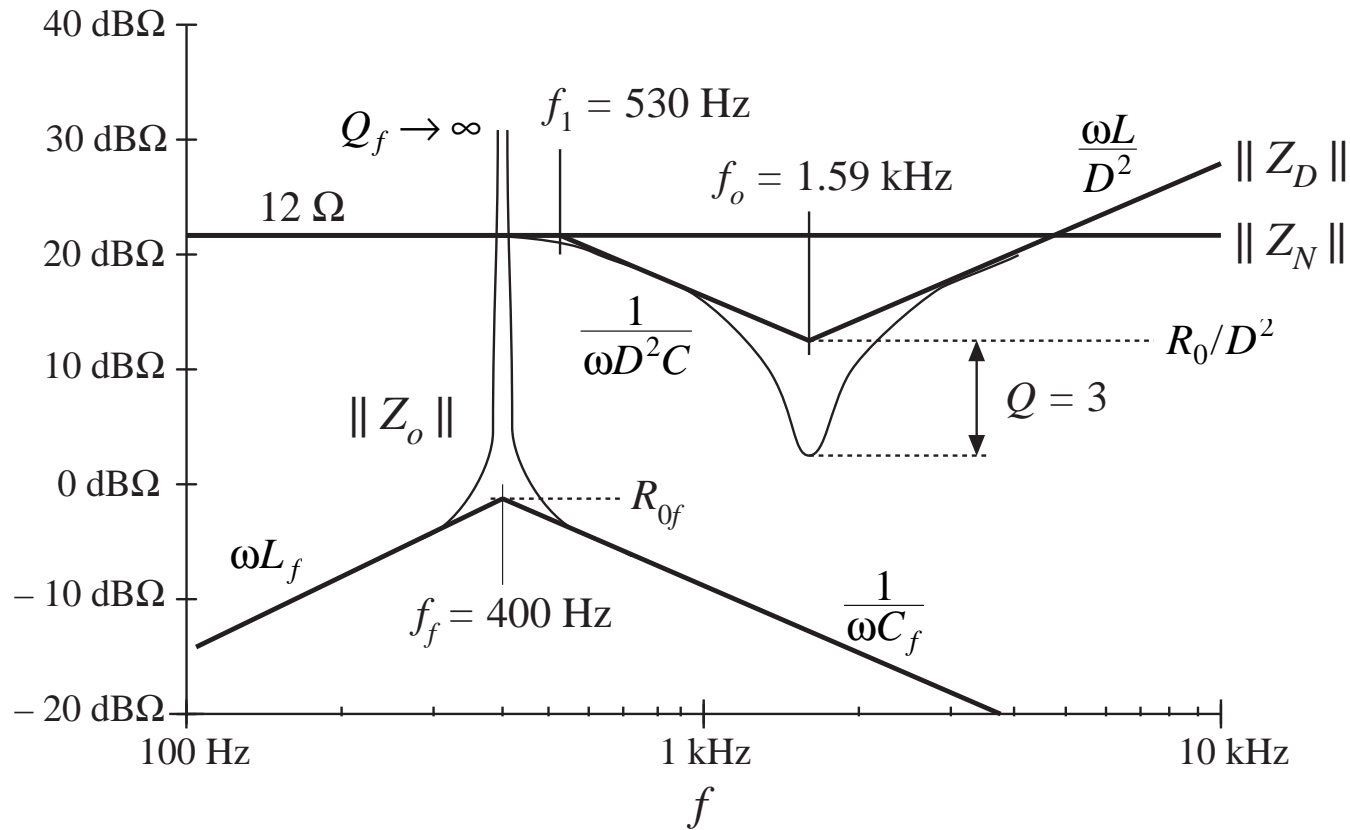


Can meet inequalities everywhere except at resonant frequency  $f_f$

Need to damp input filter!

# Resulting correction factor

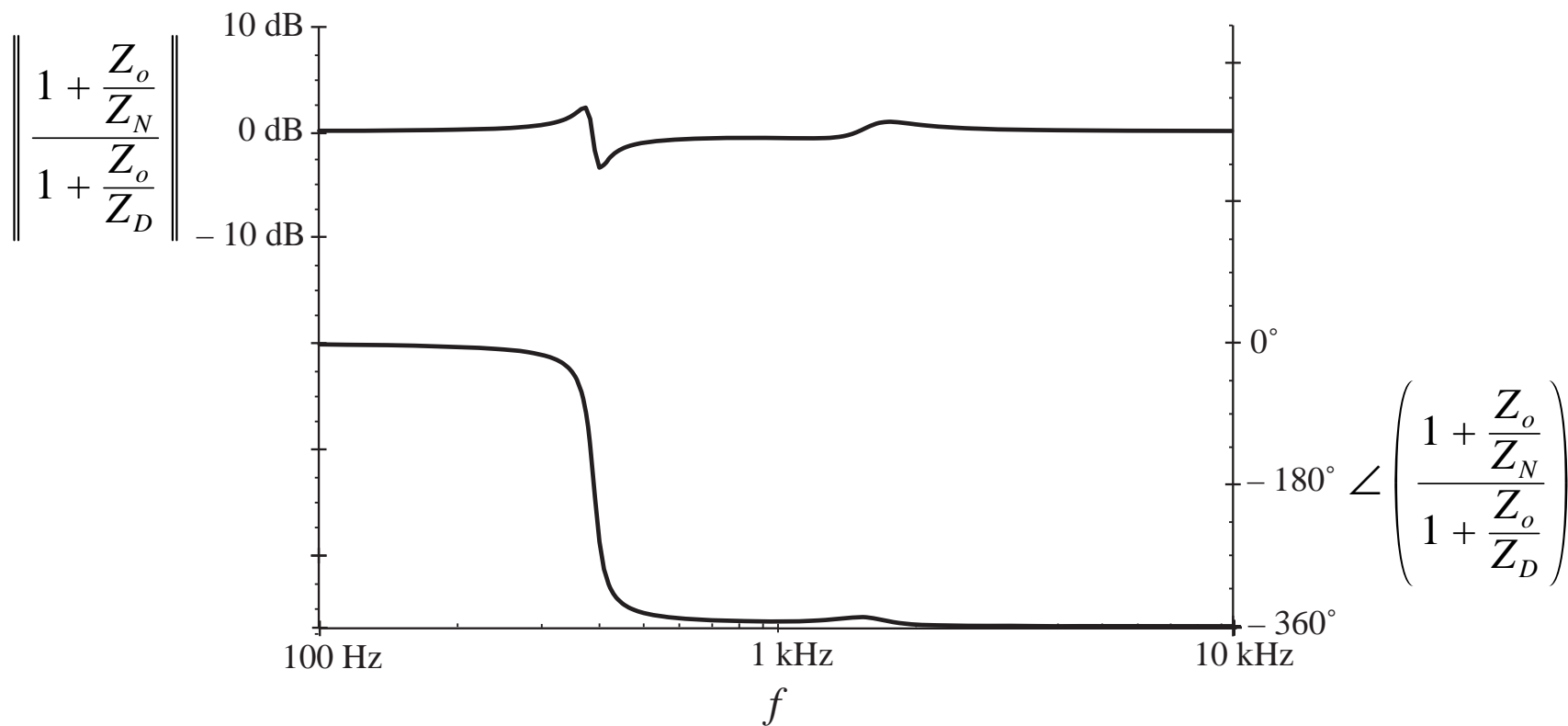


# Resulting transfer function

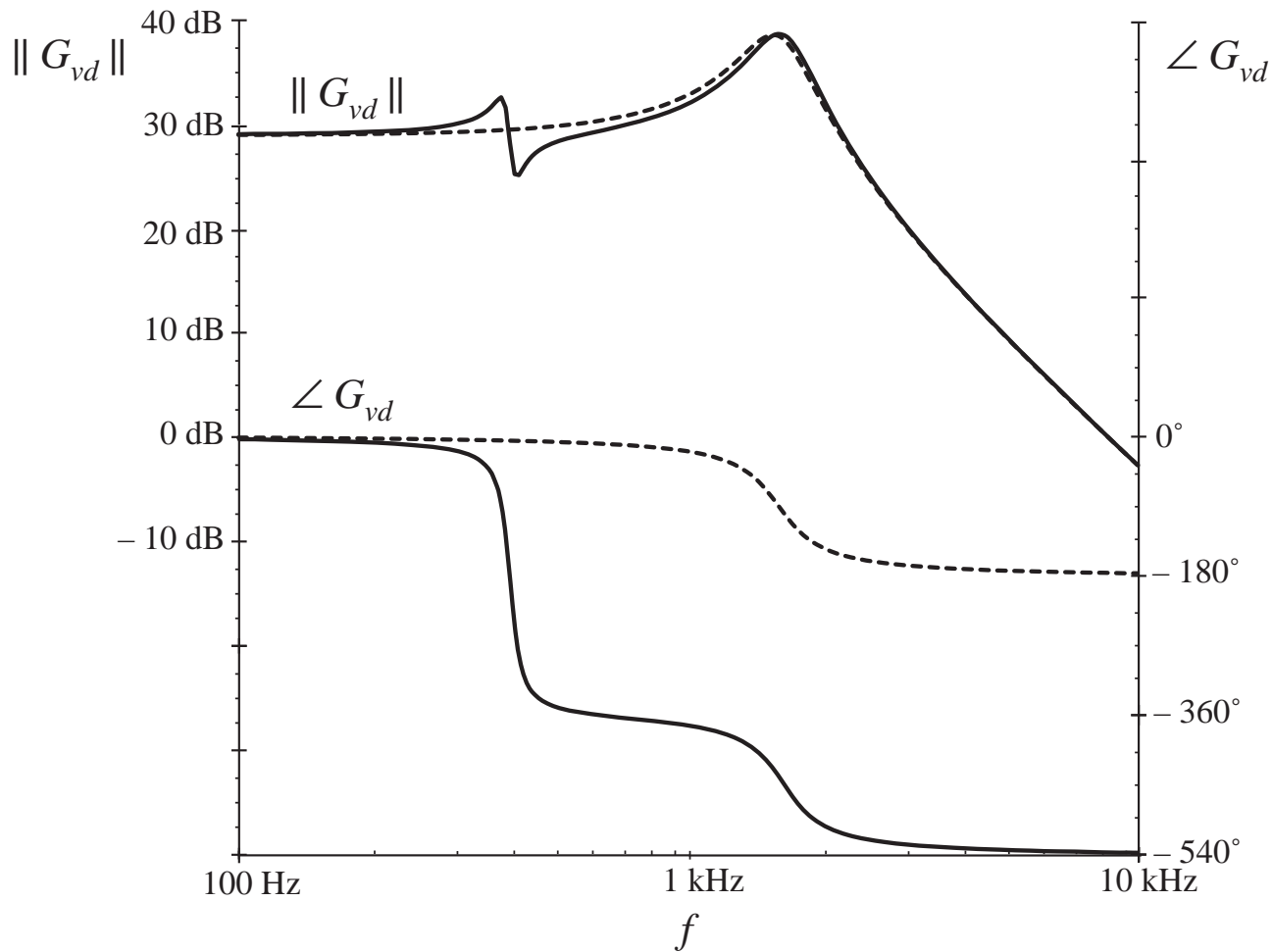



*Dashed lines:* no input filter  
*Solid lines:* including effect of input filter

## 10.3.2 Damping the input filter

Undamped filter:

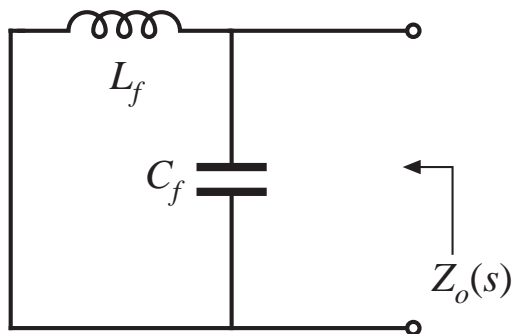

Two possible approaches:

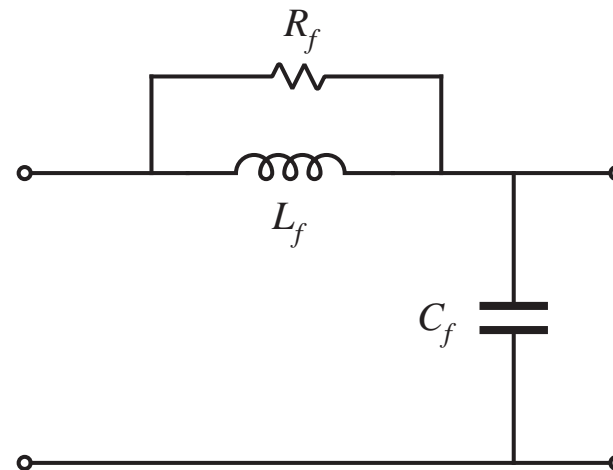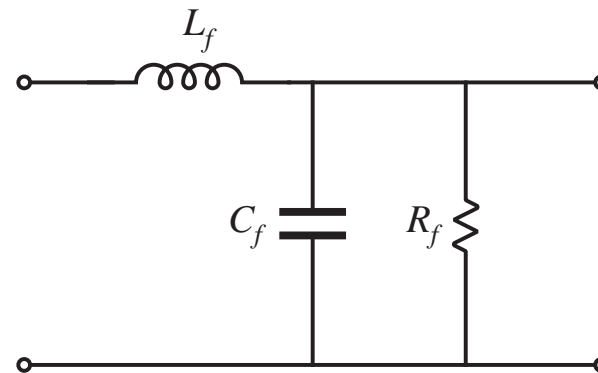

## Addition of $R_f$ across $C_f$



To meet the requirement  $R_f \ll \|Z_N\|$ :

$$R_f \ll \frac{R}{D^2}$$


The power loss in  $R_f$  is  $V_g^2 / R_f$ ,  
which is larger than the load power!

A solution: add dc blocking  
capacitor  $C_b$ .

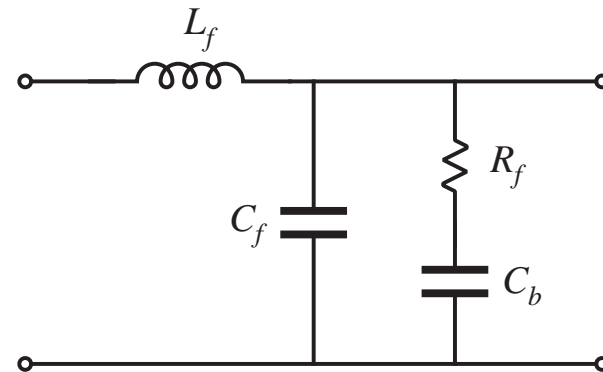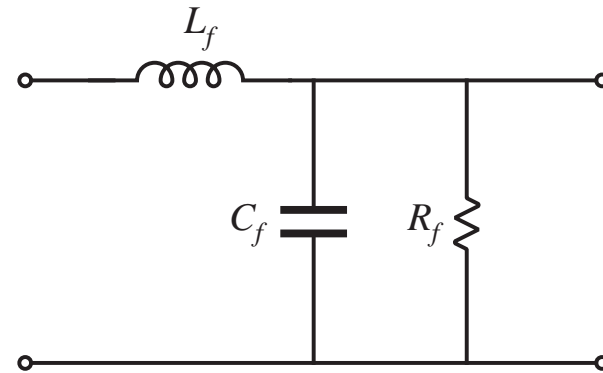
Choose  $C_b$  so that its impedance is  
sufficiently smaller than  $R_f$  at the  
filter resonant frequency.




# Damped input filter

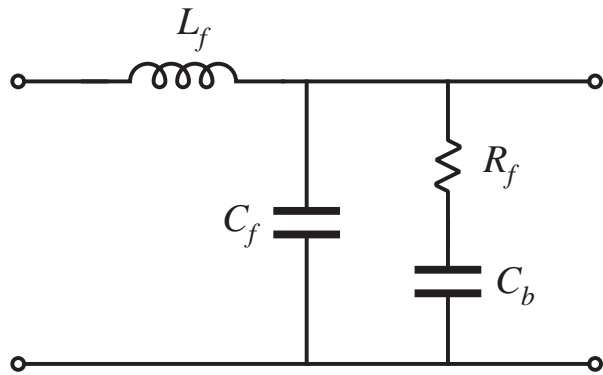


$\|Z_o\|$ , with large  $C_b$

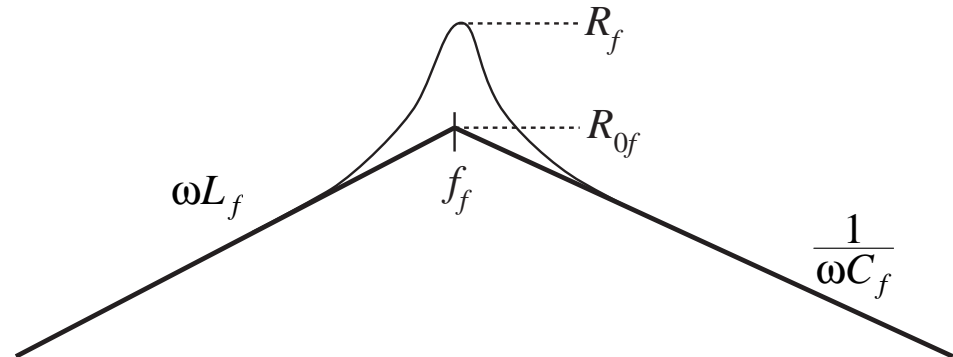
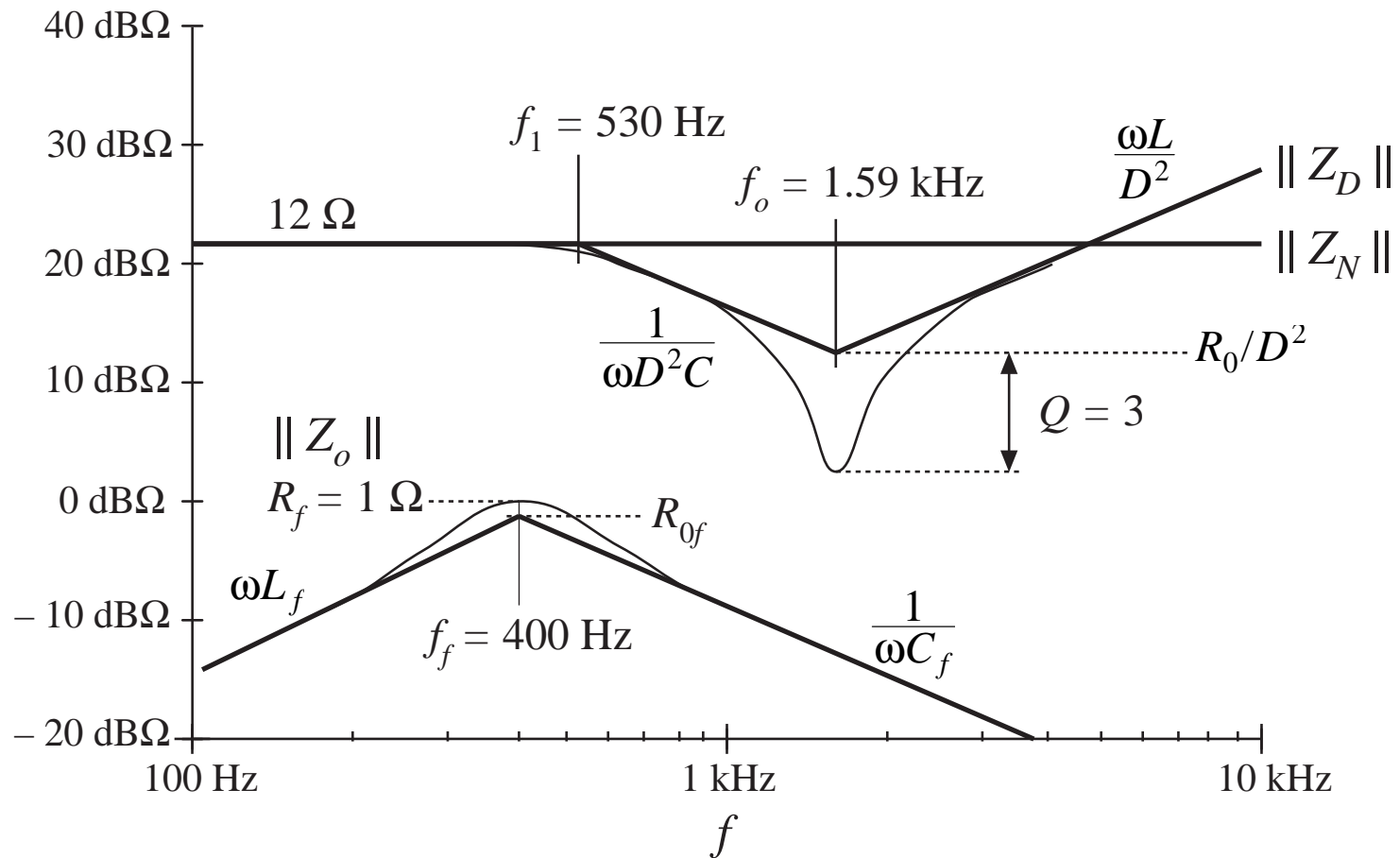
# Design criteria, with damped input filter




# Resulting transfer function

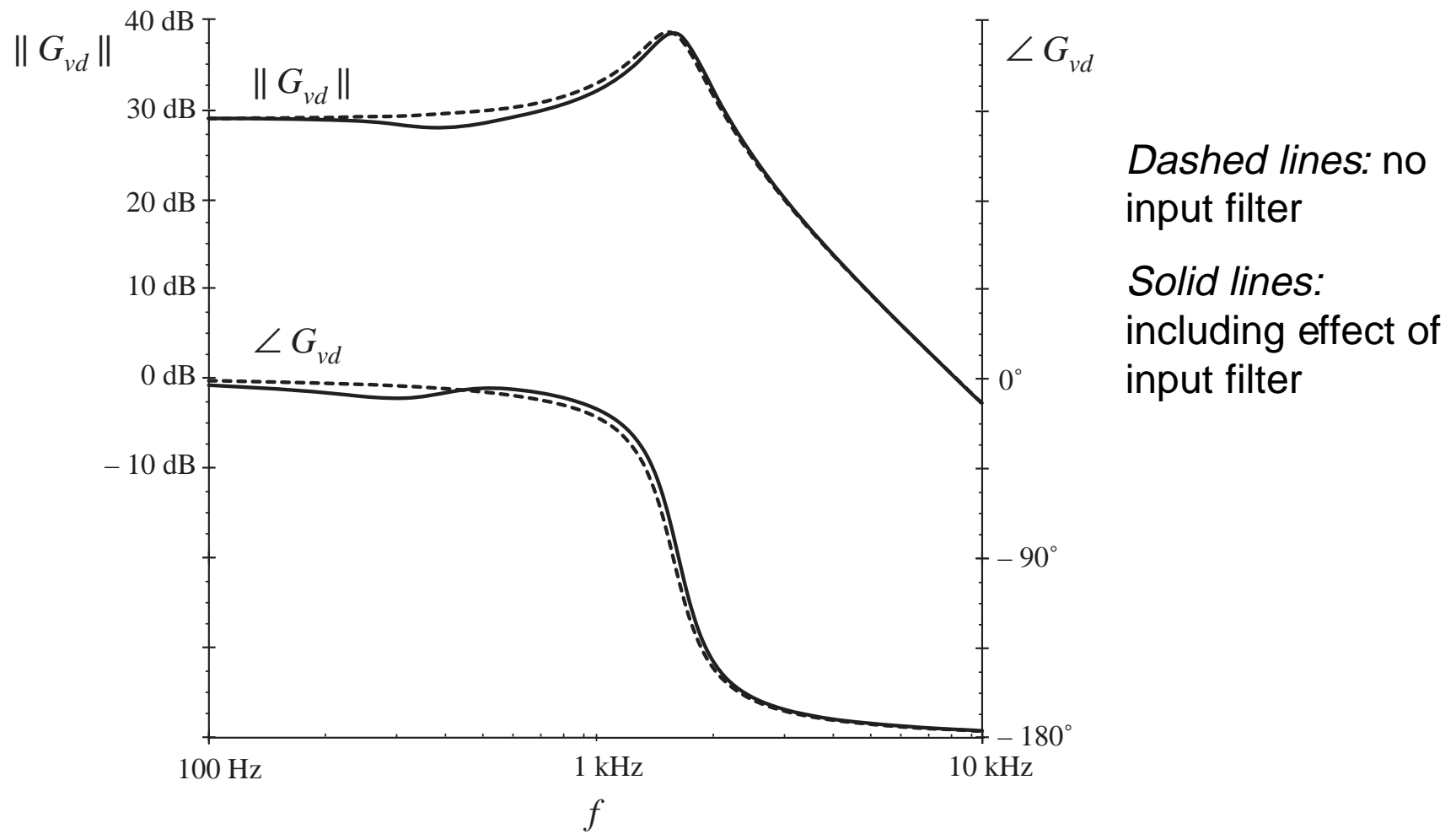




# 10.4 Design of a Damped Input Filter


$R_f$ - $C_b$  Parallel Damping

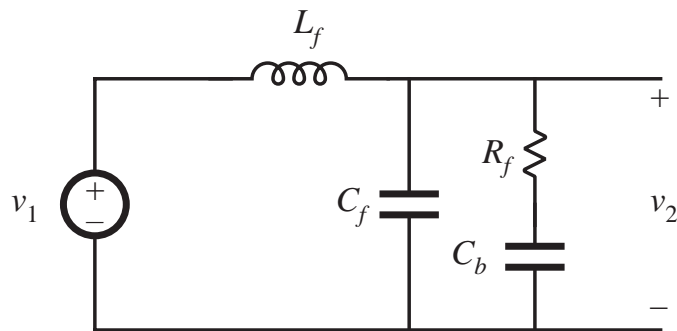

$R_f$ - $L_b$  Series Damping

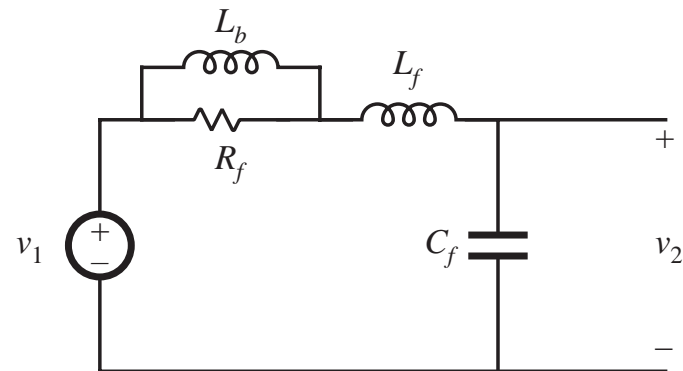


$R_f$ - $L_b$  Parallel Damping

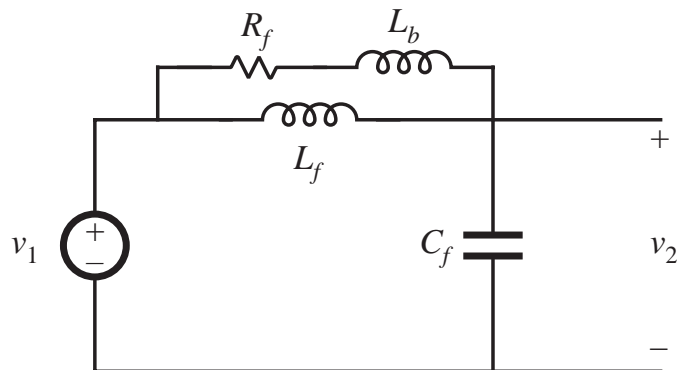

- Size of  $C_b$  or  $L_b$  can become very large
- Need to optimize design


# Dependence of $\|Z_o\|$ on $R_f$

## $R_f-L_b$ Parallel Damping

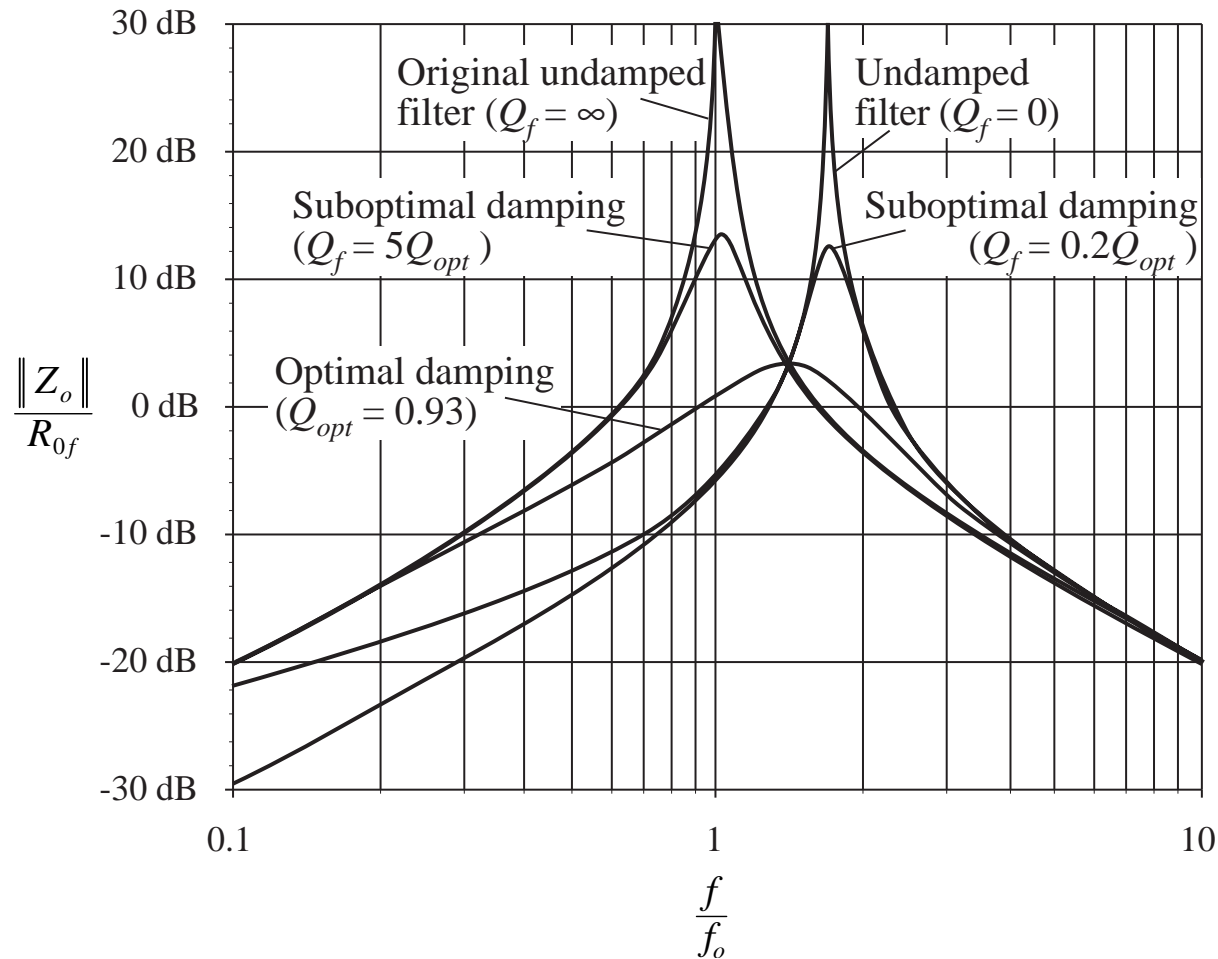

For this example,  
 $n = L_b/L = 0.516$

## 10.4.1 $R_f$ - $C_b$ Parallel Damping

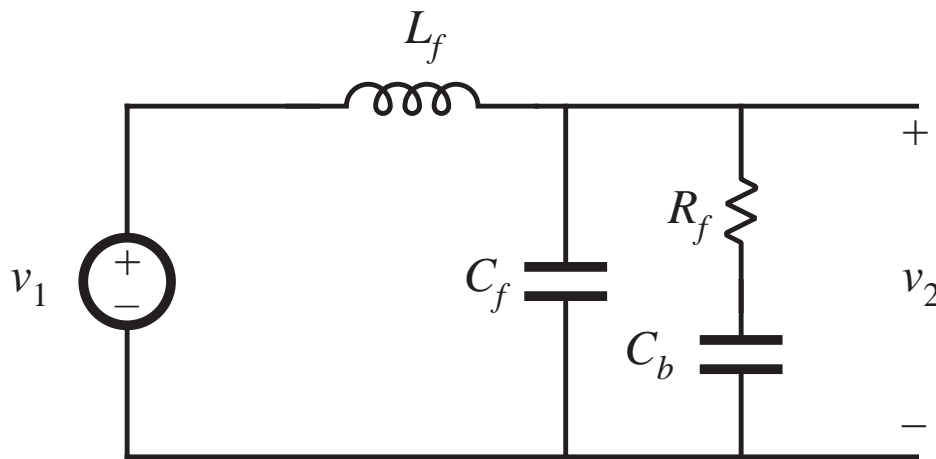

- Filter is damped by  $R_f$
- $C_b$  blocks dc current from flowing through  $R_f$
- $C_b$  can be large in value, and is an element to be optimized

# Optimal design equations

## $R_f$ - $C_b$ Parallel Damping

---

Define  $n = \frac{C_b}{C_f}$

The value of the peak output impedance for the optimum design is

$$\|Z_o\|_{\text{mm}} = R_{of} \frac{\sqrt{2(2+n)}}{n} \quad \text{where } R_{of} = \text{characteristic impedance of original undamped input filter}$$

Given a desired value of the peak output impedance, can solve above equation for  $n$ . The required value of damping resistance  $R_f$  can then be found from:

$$Q_{opt} = \frac{R_f}{R_{of}} = \sqrt{\frac{(2+n)(4+3n)}{2n^2(4+n)}}$$

The peak occurs at the frequency

$$f_m = f_f \sqrt{\frac{2}{2+n}}$$


# Example

## Buck converter of Section 10.3.2

$$n = \frac{R_{0f}^2}{\|Z_o\|_{\text{mm}}^2} \left( 1 + \sqrt{1 + 4 \frac{\|Z_o\|_{\text{mm}}^2}{R_{0f}^2}} \right) = 2.5 \quad R_f = R_{0f} \sqrt{\frac{(2+n)(4+3n)}{2n^2(4+n)}} = 0.67 \Omega$$


Comparison of designs

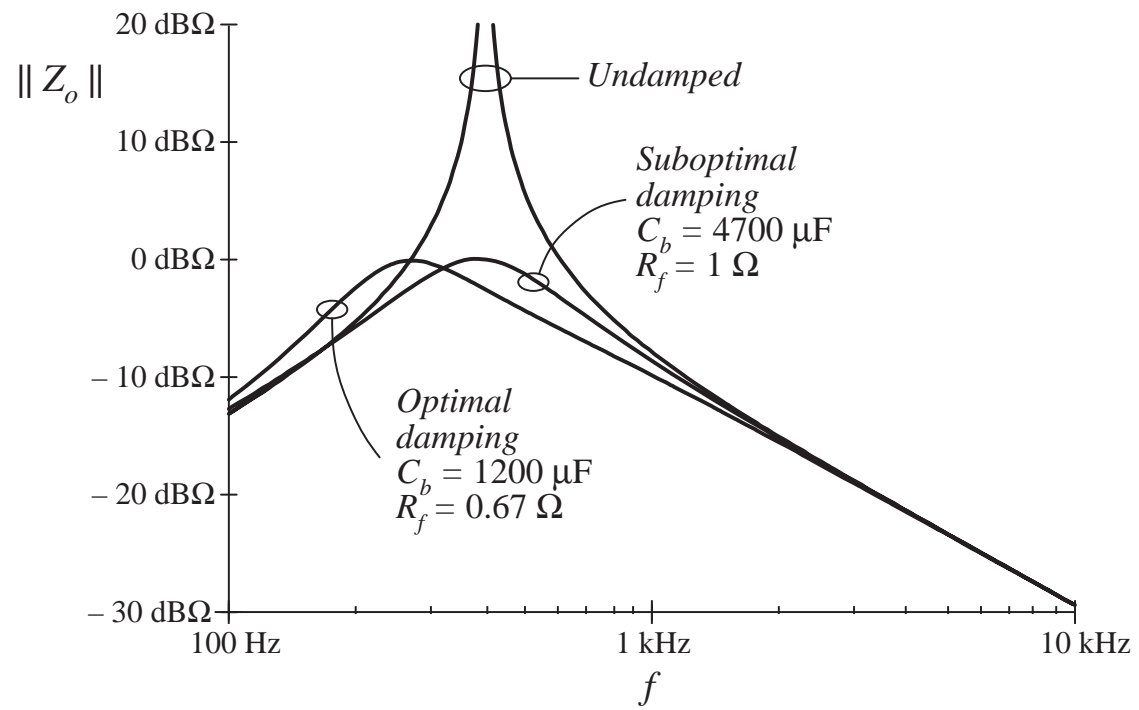Optimal damping achieves same peak output impedance, with much smaller  $C_b$ .



# Summary

## Optimal $R$ - $C_d$ damping

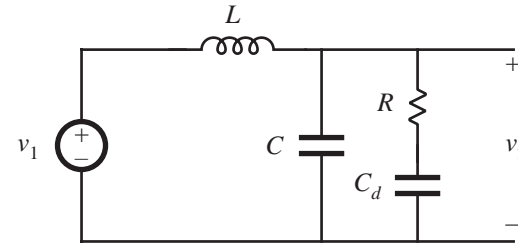

### Basic results

$$Q_{opt} = \frac{R}{R_0} = \sqrt{\frac{(2+n)(4+3n)}{2n^2(4+n)}}$$


$$\frac{\|Z\|_{mm}}{R_0} = \frac{\sqrt{2(2+n)}}{n}$$

with


$$n = \frac{C_d}{C}$$

$$R_0 = \sqrt{\frac{L}{C}}$$

- Does not degrade HF attenuation
- No limit on  $\|Z\|_{mm}$
- $C_d$  is typically larger than  $C$

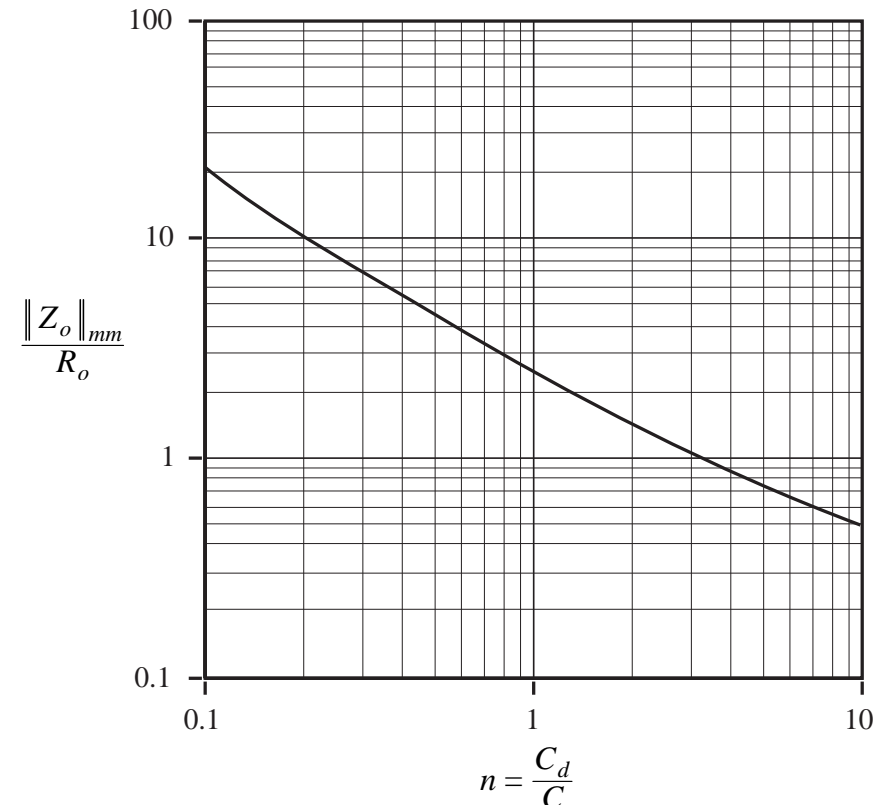

# Optimal $R$ - $L_d$ damping

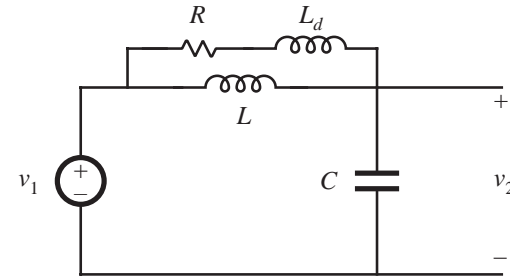

## Basic results


$$Q_{opt} = \sqrt{\frac{n(3+4n)(1+2n)}{2(1+4n)}}$$

$$\frac{\|Z\|_{mm}}{R_0} = \sqrt{2n(1+2n)}$$


with

$$Q_{opt} = \frac{\text{optimum value of } R}{R_0}$$
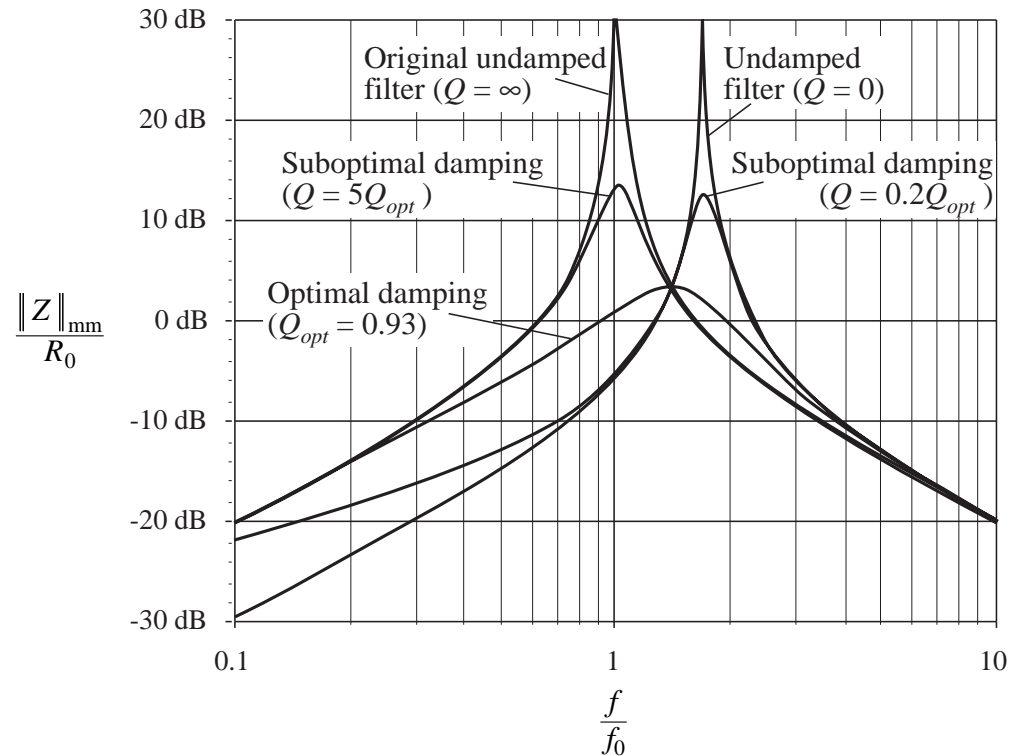
$$n = \frac{L_d}{L} \quad R_0 = \sqrt{\frac{L}{C}}$$



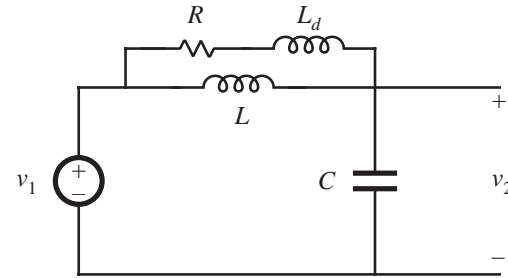
# Discussion: Optimal $R$ - $L_d$ damping



- $L_d$  is physically very small
- A simple low-cost approach to damping the input filter
- Disadvantage:  $L_d$  degrades high-frequency attenuation of filter, by the factor


$$\frac{L}{L \parallel L_d} = 1 + \frac{1}{n}$$

- Basic tradeoff: peak output impedance vs. high-frequency attenuation
- Example: the choice  $n = 1$  ( $L_d = L$ ) degrades the HF attenuation by 6 dB, and leads to peak output impedance of  $\|Z\|_{mm} = \sqrt{6} R_0$

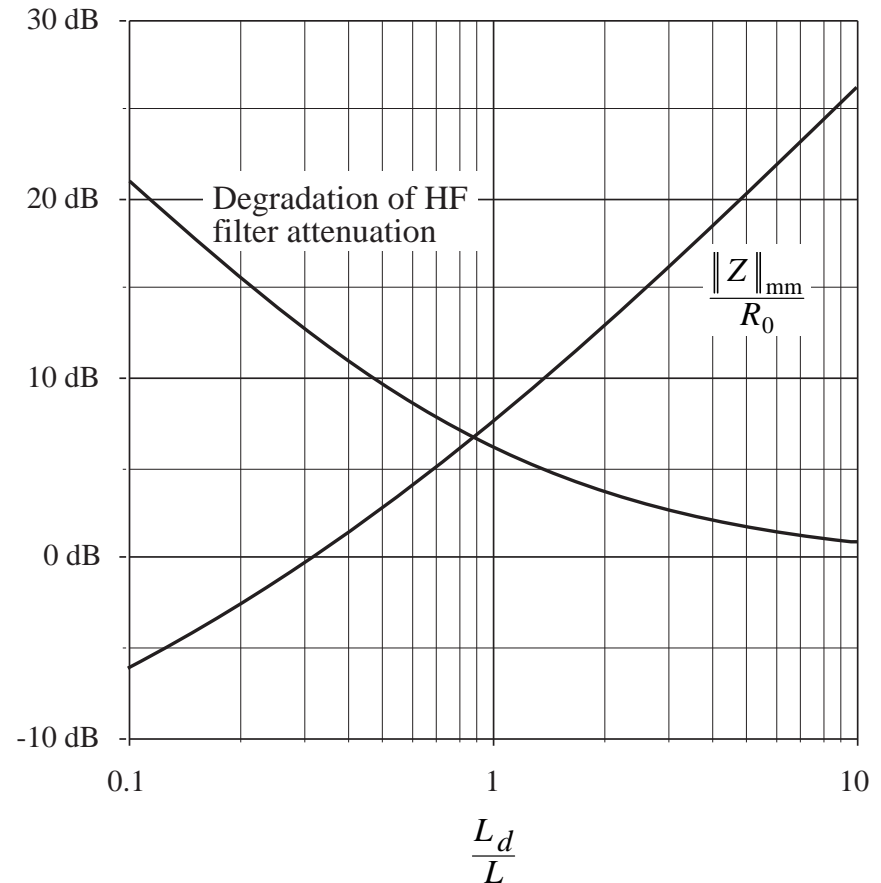



# Optimal $R$ - $L_d$ series damping

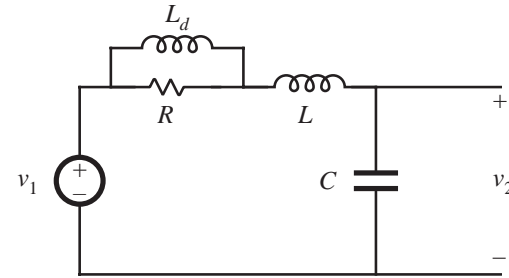

## Basic results

$$Q_{opt} = \frac{R_0}{R} = \left(\frac{1+n}{n}\right) \sqrt{\frac{2(1+n)(4+n)}{(2+n)(4+3n)}}$$


$$\frac{\|Z\|_{mm}}{R_0} = \sqrt{\frac{2(1+n)(2+n)}{n}}$$

with

$$n = \frac{L_d}{L}$$

$$R_0 = \sqrt{\frac{L}{C}}$$

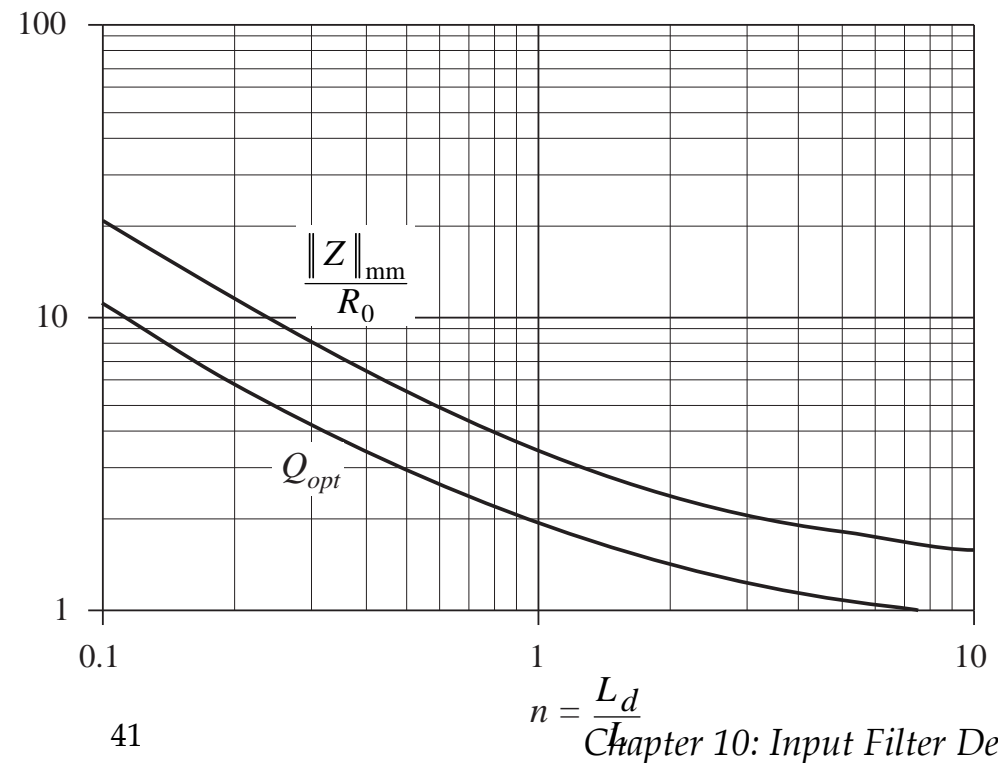- Does not degrade HF attenuation
- $L_d$  must conduct entire dc current
- Peak output impedance cannot be reduced below  $\sqrt{2} R_0$




## 10.4.4 Cascading Filter Sections

---

- Cascade connection of multiple  $L$ - $C$  filter sections can achieve a given high-frequency attenuation with much smaller volume and weight
- Need to damp each section of the filter
- One approach: add new filter section to an existing filter, using new design criteria
- Stagger-tuning of filter sections

# Addition of filter section

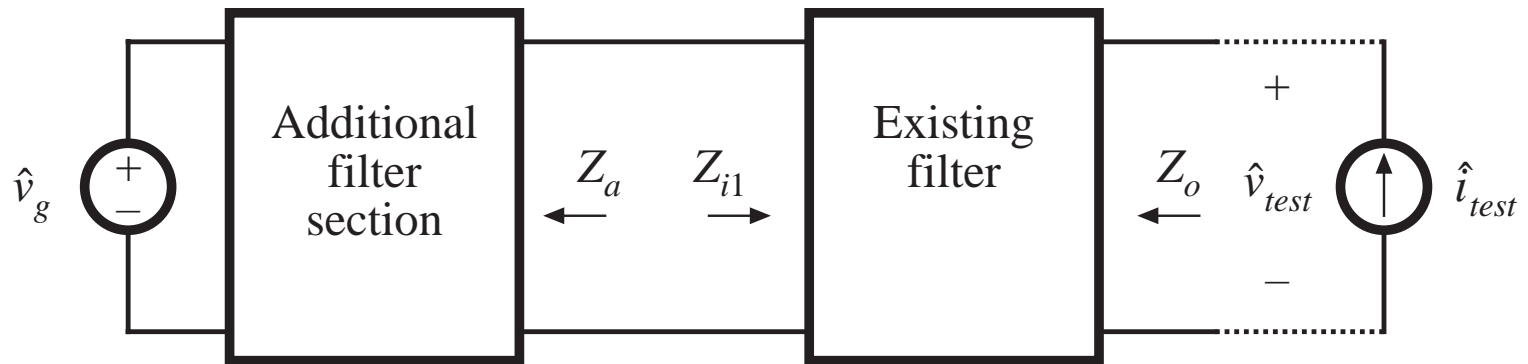


How the additional filter section changes the output impedance of the existing filter:

$$\text{modified } Z_o(s) = \left[ Z_o(s) \right]_{Z_a(s)=0} \frac{\left( 1 + \frac{Z_a(s)}{Z_{N1}(s)} \right)}{\left( 1 + \frac{Z_a(s)}{Z_{D1}(s)} \right)}$$

$$Z_{N1}(s) = Z_{i1}(s) \Big|_{\hat{v}_{test}(s) \xrightarrow{\text{null}} 0} \quad Z_{D1}(s) = Z_{i1}(s) \Big|_{\hat{i}_{test}(s) = 0}$$

# Design criteria

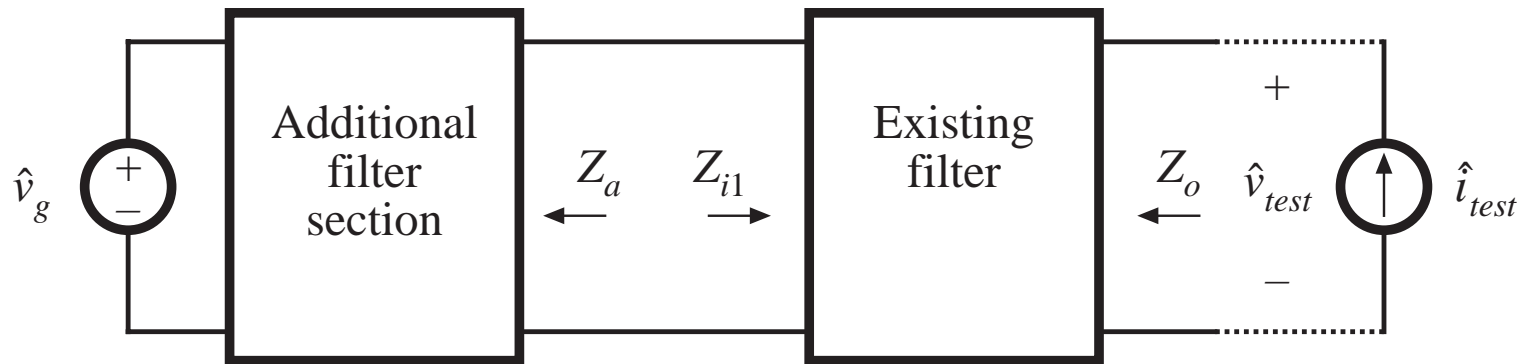

$$Z_{N1}(s) = Z_{i1}(s) \Big|_{\hat{v}_{test}(s) \xrightarrow{\text{null}} 0} \quad (\text{with filter output port short-circuited})$$

$$Z_{D1}(s) = Z_{i1}(s) \Big|_{\hat{i}_{test}(s) = 0} \quad (\text{with filter output port open-circuited})$$

The presence of the additional filter section does not substantially alter the output impedance  $Z_o$  of the existing filter provided that



$$\|Z_a\| \ll \|Z_{N1}\| \quad \text{and} \\ \|Z_a\| \ll \|Z_{D1}\|$$

# 10.4.5 Example

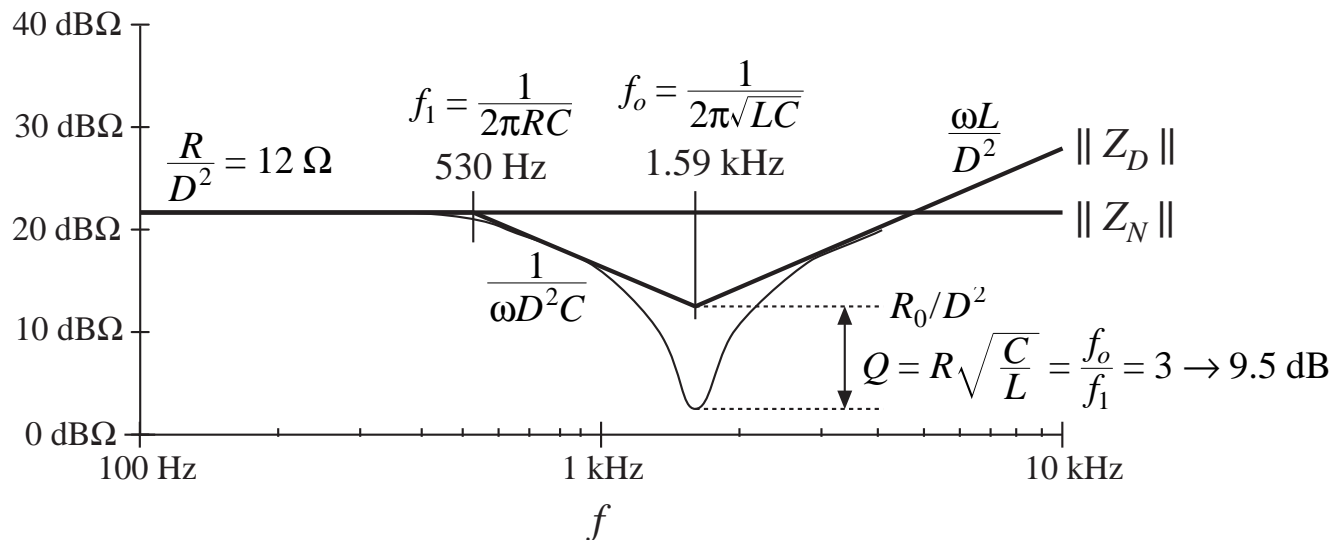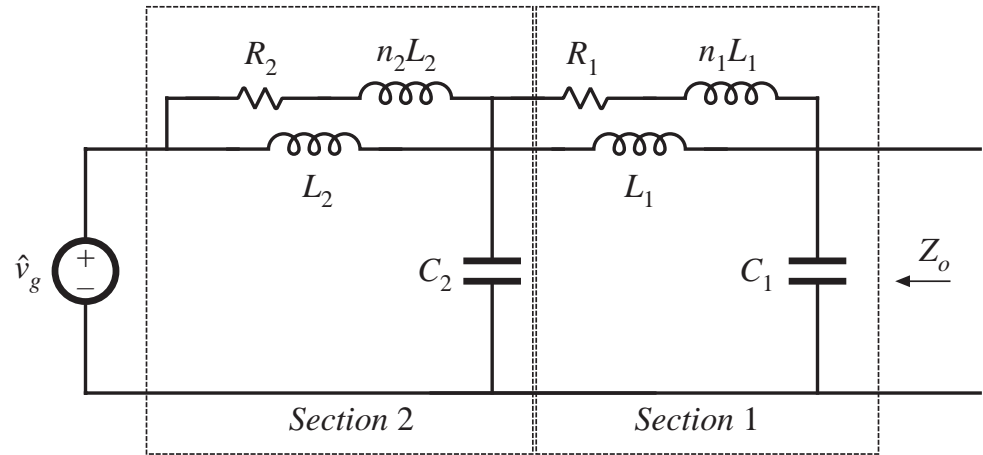
## Two-Stage Input Filter

*Requirements:* For the same buck converter example, achieve the following:

- 80 dB of attenuation at 250 kHz
- Section 1 to satisfy  $Z_o$  impedance inequalities as before:



## Section 2 impedance inequalities

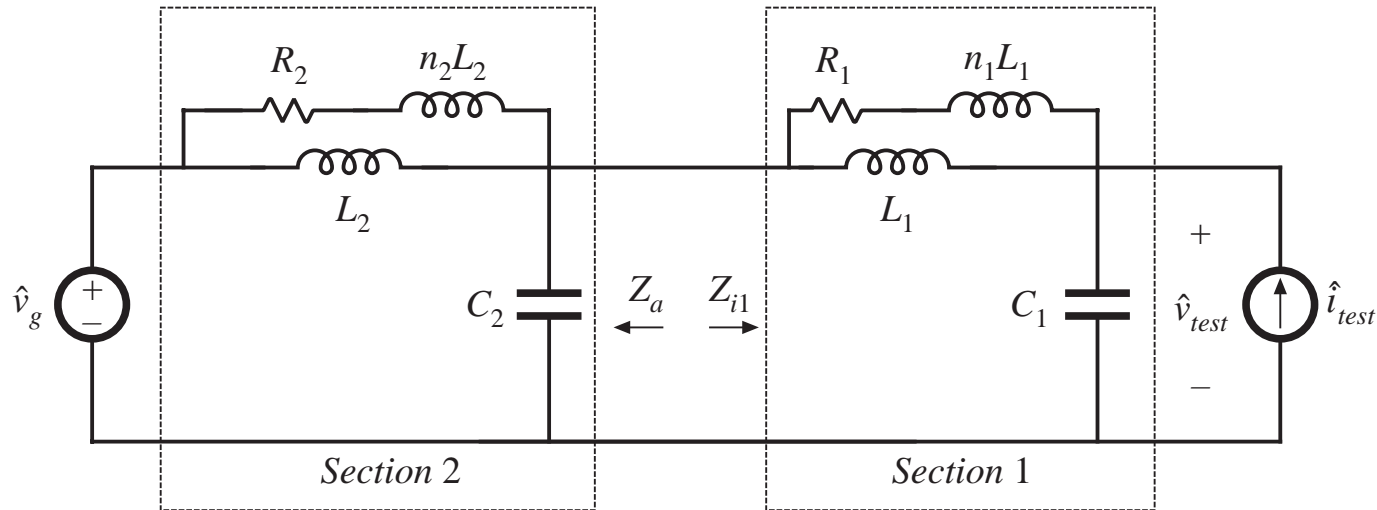


To avoid disrupting the output impedance  $Z_o$  of section 1, section 2 should satisfy the following inequalities:


$$Z_a \ll Z_{N1} = Z_{i1} \Big|_{\text{output shorted}} = (R_1 + sn_1L_1) \parallel sL_1$$

$$Z_a \ll Z_{D1} = Z_{i1} \Big|_{\text{output open-circuited}} = \frac{1}{sC_1} + (R_1 + sn_1L_1) \parallel sL_1$$

# Plots of $Z_{N1}$ and $Z_{D1}$

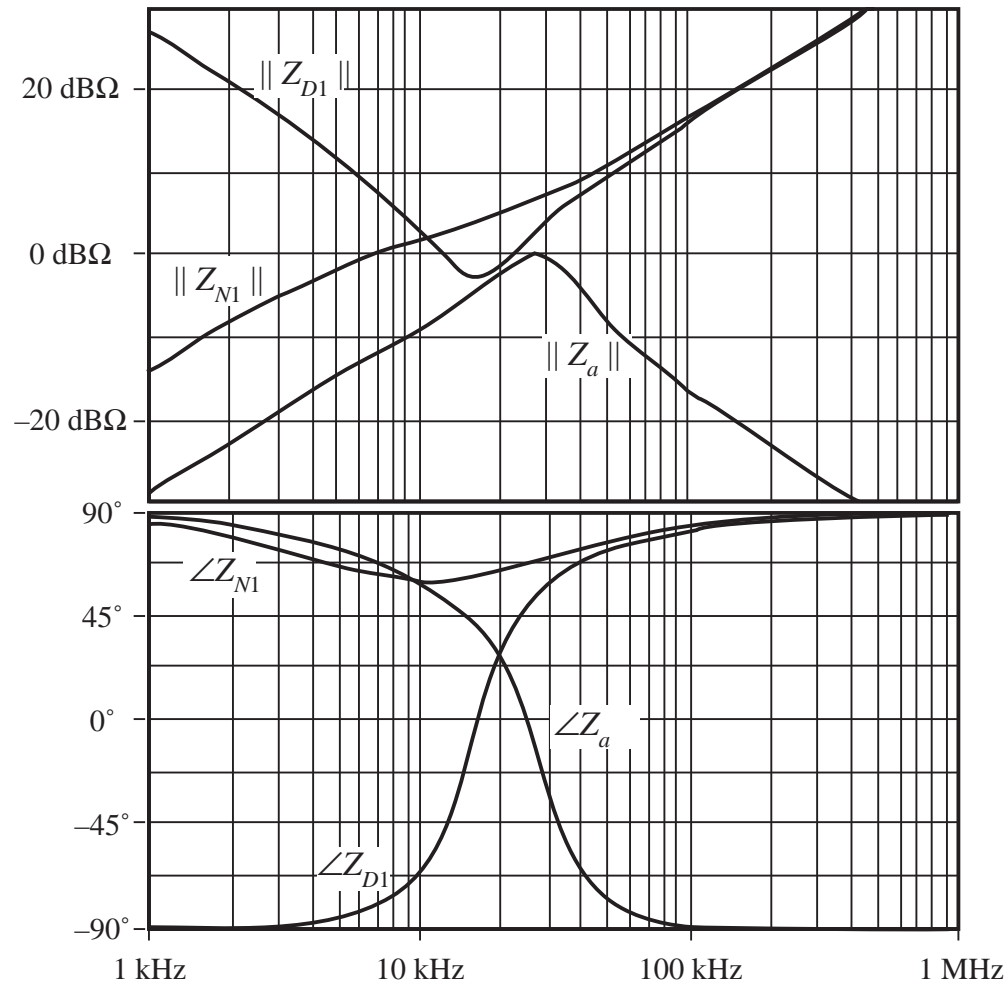

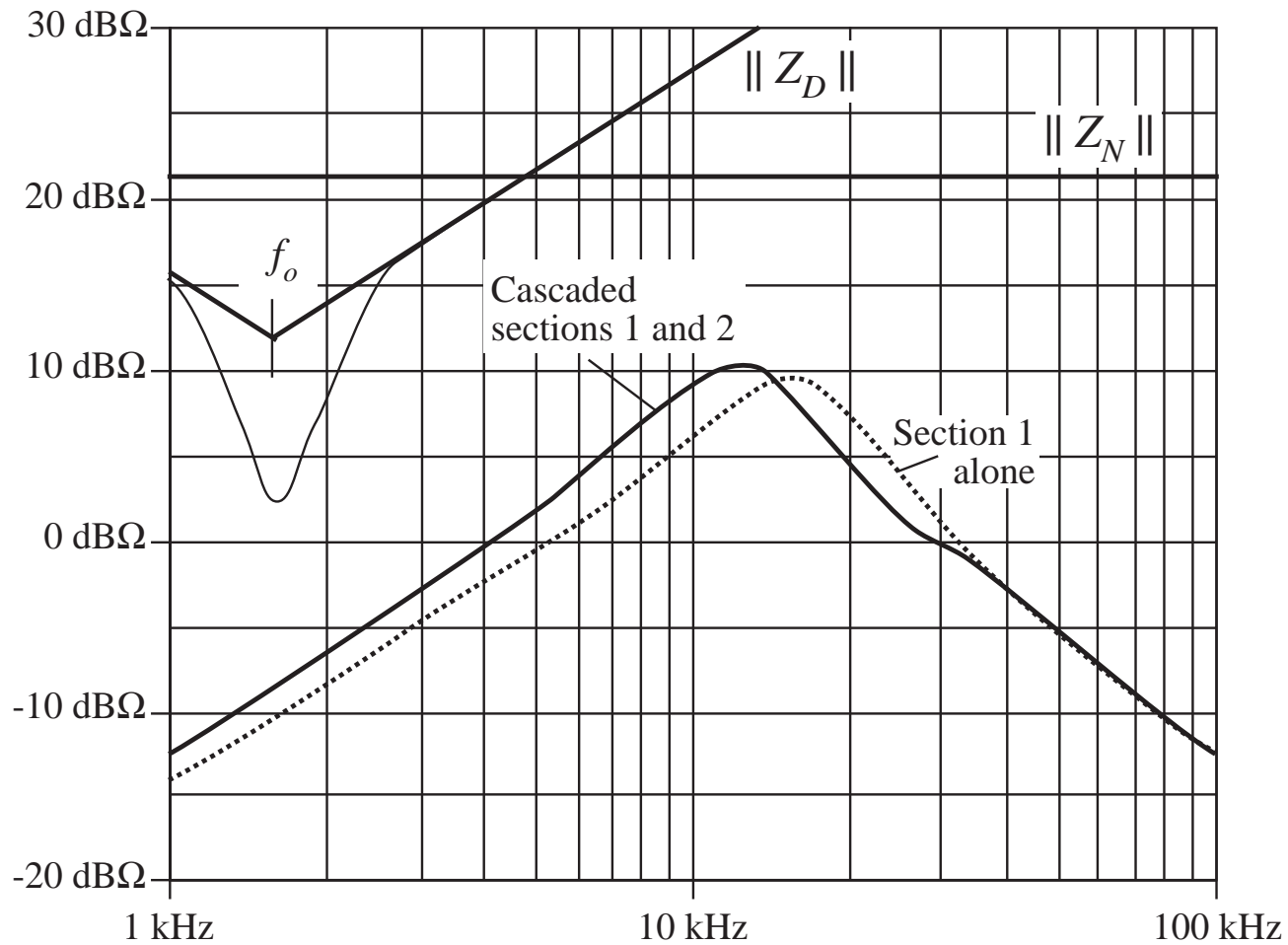
# Section 1 output impedance inequalities





# Resulting filter transfer function

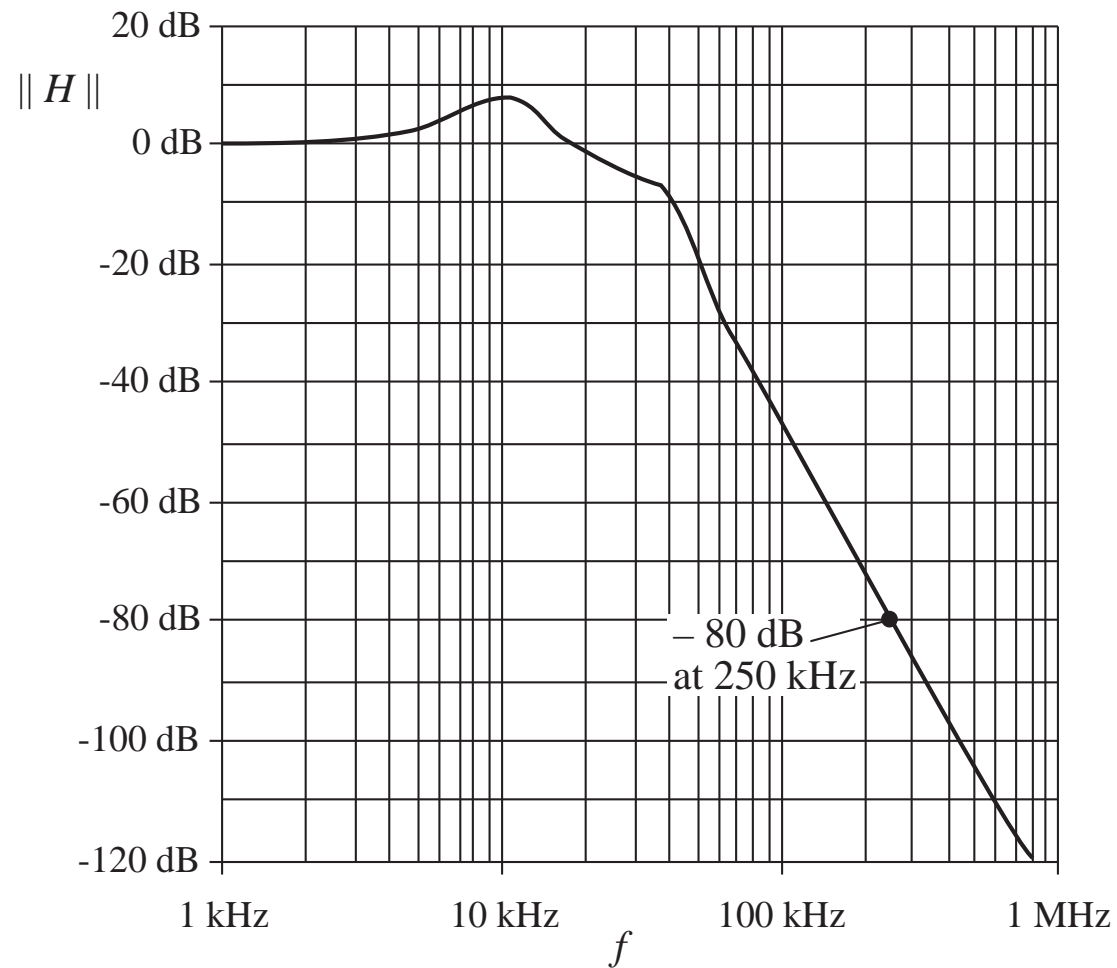

# Comparison of single-section and two-section designs

