


# Analyzing Feedback Systems with Signal-Flow Graphs

Tuesday April 26 2016


# PURPOSE

- Signal flow graphs facilitate finding transfer functions of linear systems
- They aid with an intuitive understanding
- Once the flow graph is drawn Mason's gain formula allows writing the transfer function by inspection of the graph
- They don't aid in analyzing the effects of nonlinearities or initial conditions

# BLOCK DIAGRAM

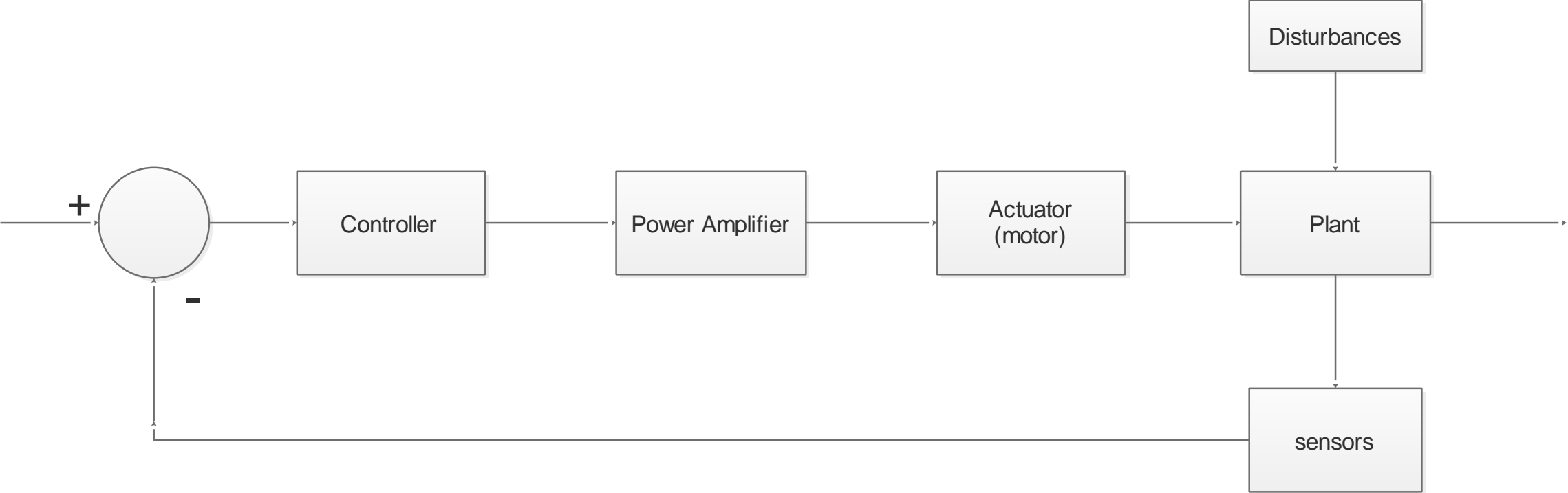

# CURRENT AMPLIFIER

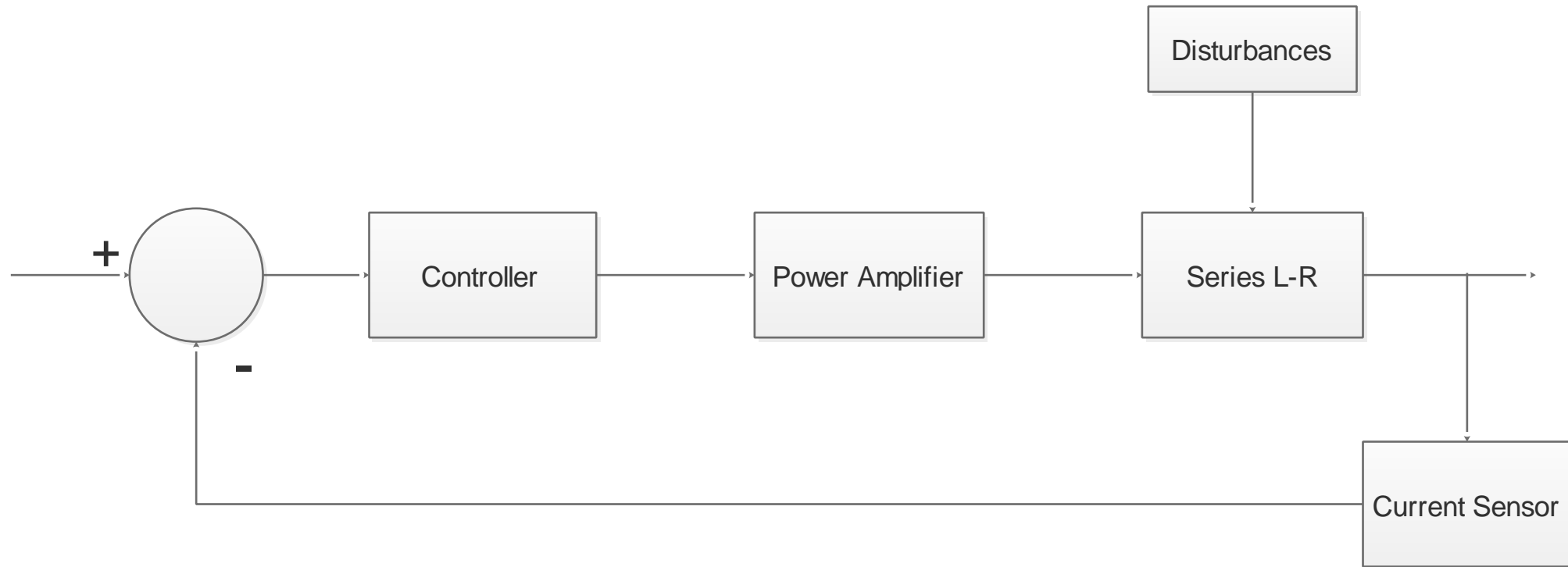

# SIGNAL-FLOW GRAPHS


Consists of nodes and branches:

- Signals flow along branches in direction of arrows
- Node signal is sum of all signals entering
- Signals at node drive all outgoing branches
- The signal at the output of a branch is the product of the signal on the node driving it times the transmittance of the branch


# MASON'S GAIN FORMULA

- $G = \frac{\sum G_k \Delta_k}{\Delta}$
- $\Delta = 1 - \sum L1 + \sum L2 - \dots$
- $G_k$  = gain of  $k$ th forward path
- $\Delta_k$  = Value of  $\Delta$  not touching  $k$ th forward path

# INVERTING OP-AMP

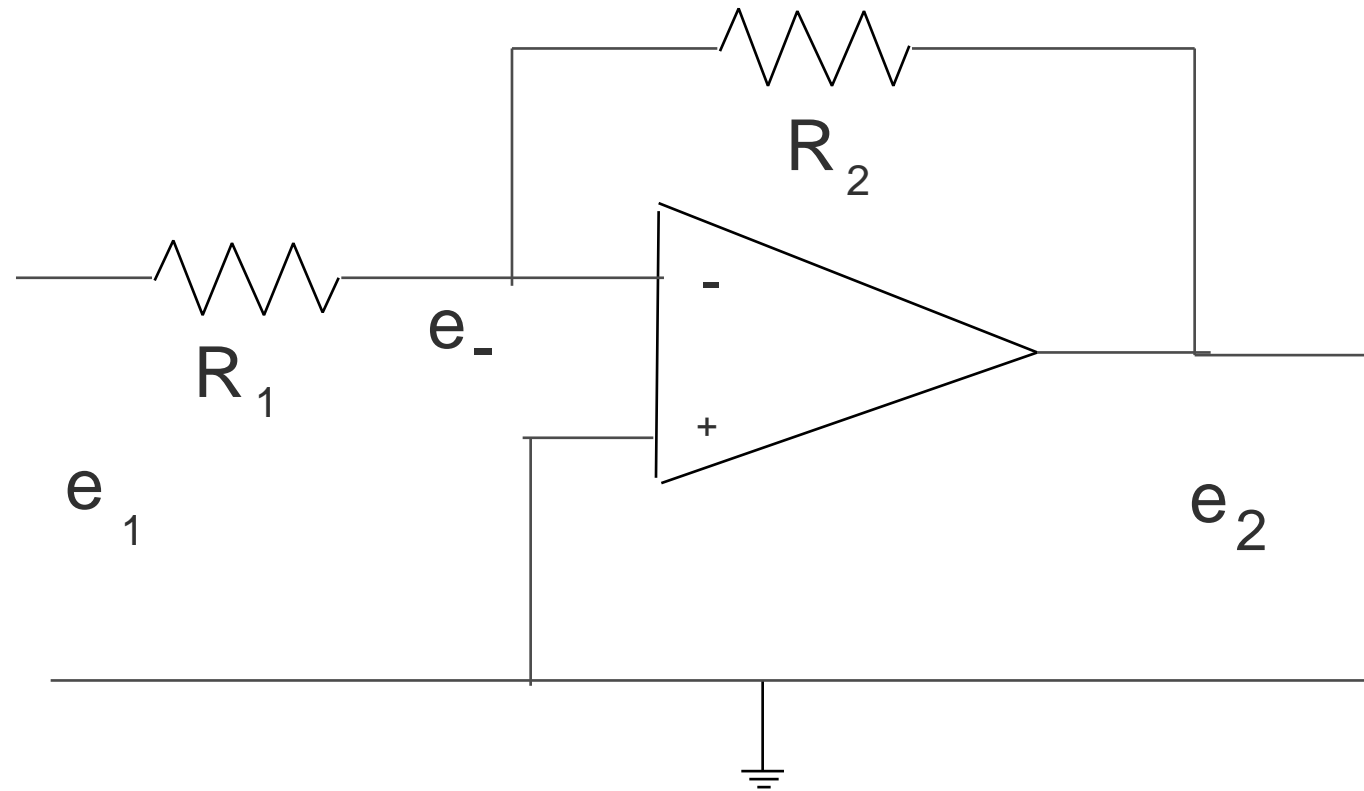

# SIGNAL-FLOW GRAPH

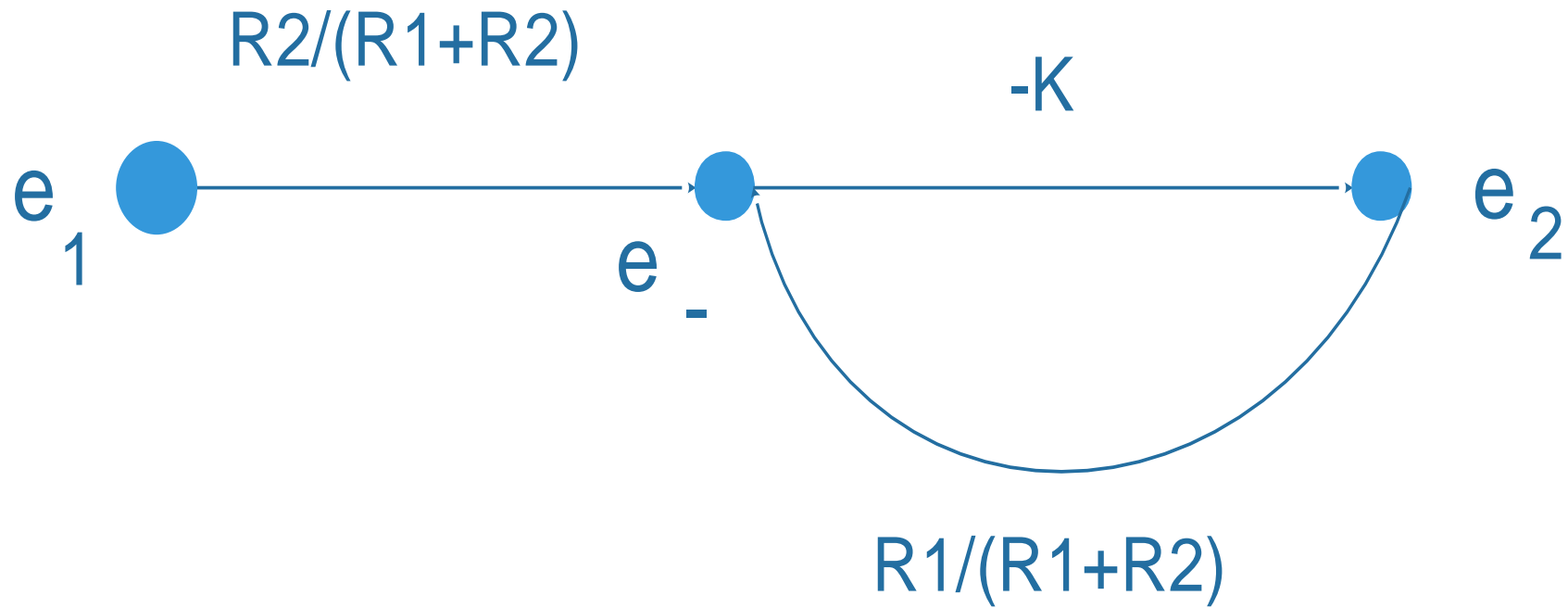




# INVERTING AMPLIFIER TRANSFER FUNCTION

- $\frac{e_2}{e_1} = \frac{-KR_2/(R_1+R_2)}{1+KR_1/(R_1+R_2)}$
- For  $kR_1/(R_1+R_2) \gg 1$
- $\frac{e_2}{e_1} = -\frac{R_2}{R_1}$

# INVERTING AMPLIFIER

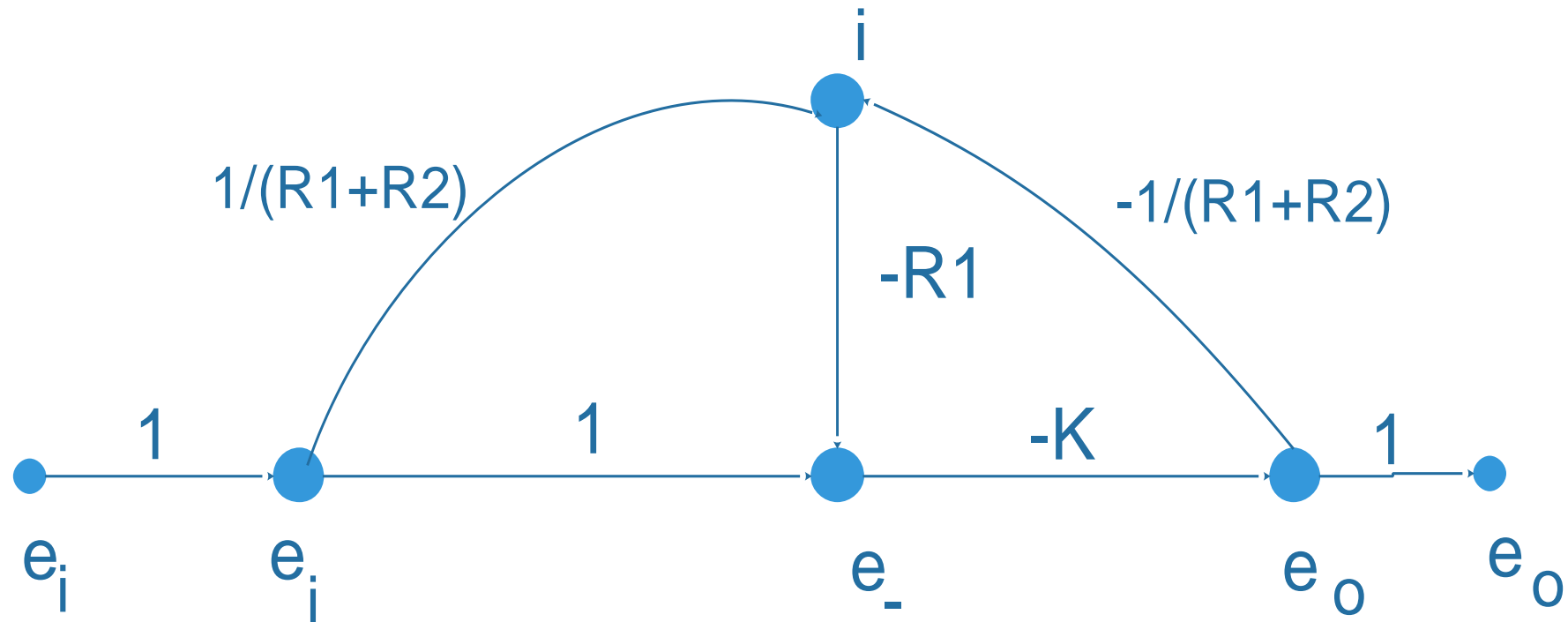


# INVERTING AMPLIFIER TRANSFER FUNCTION

- $$\frac{e_o}{e_i} = \frac{K\left(\frac{R_1}{R_1 - R_2} - 1\right)}{1 + \frac{R_1 K}{R_1 + R_2}} = \frac{R_2 / (R_1 + R_2)}{R_1 / (R_1 + R_2)} = \frac{R_2}{R_1}$$


# INTEGRATER

- $\int f(t) dt \longleftrightarrow 1/s$
- Substitute  $z=1/sc$  for R2
- $G(s) = 1/R1cs = 1/s$

# NONINVERTING OP-AMP

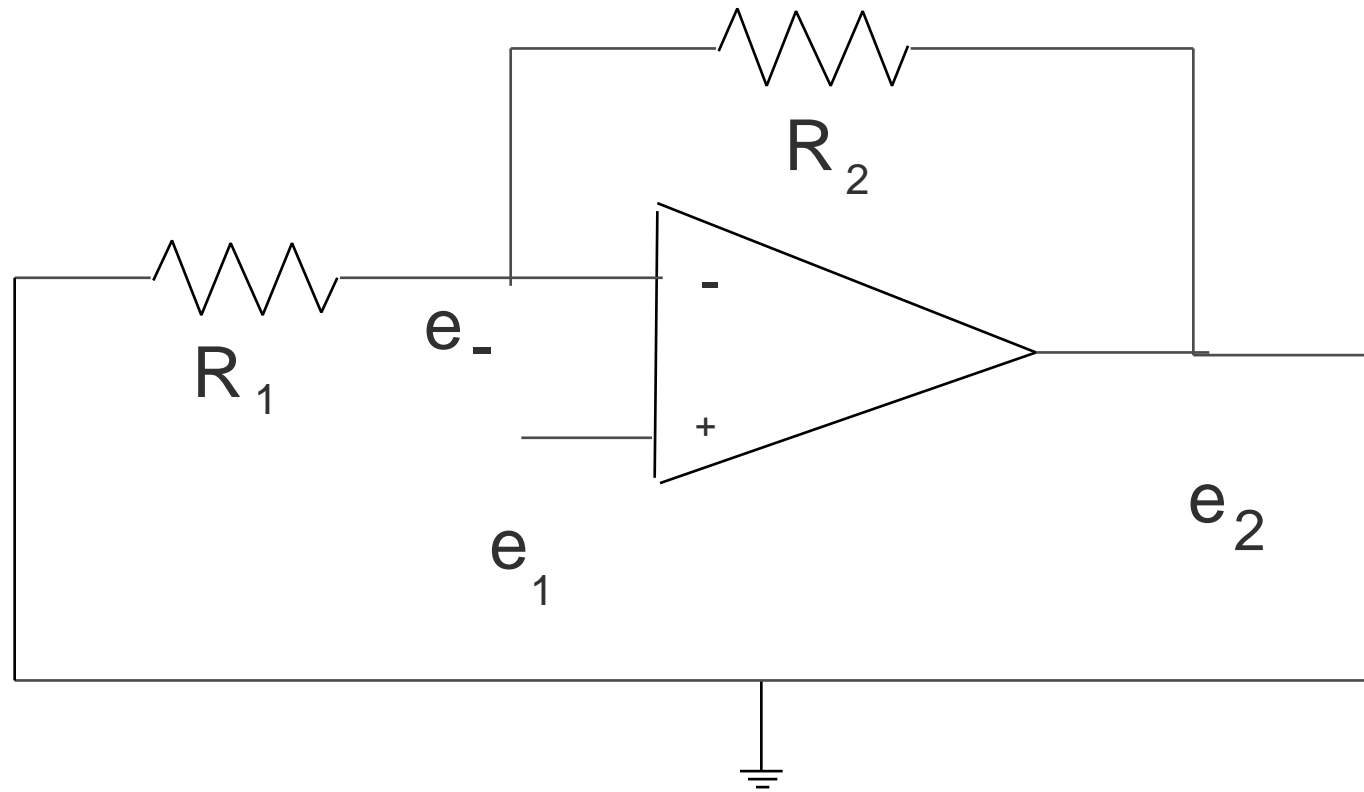


# FLOW GRAPH NONINVERTING OP-AMP

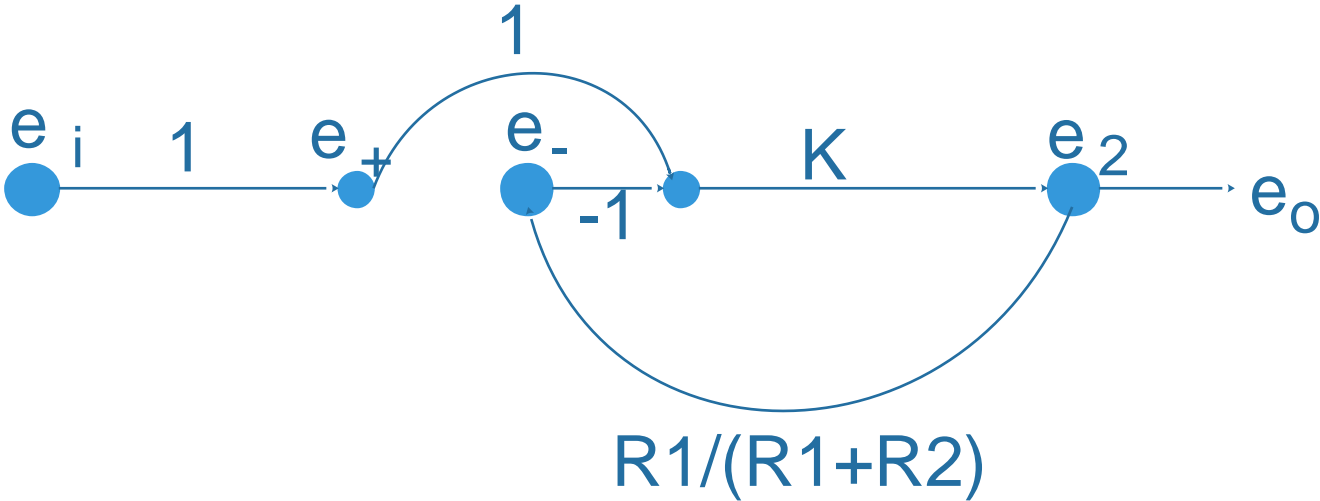

# NONINVERTING AMPLIFIER TRANSFER FUNCTION


- $$\frac{e_o}{e_i} = \frac{K}{1 + KR1/(R1 + R2)} = 1 + \frac{R2}{R1}$$

# LEAD-LAG NETWORK

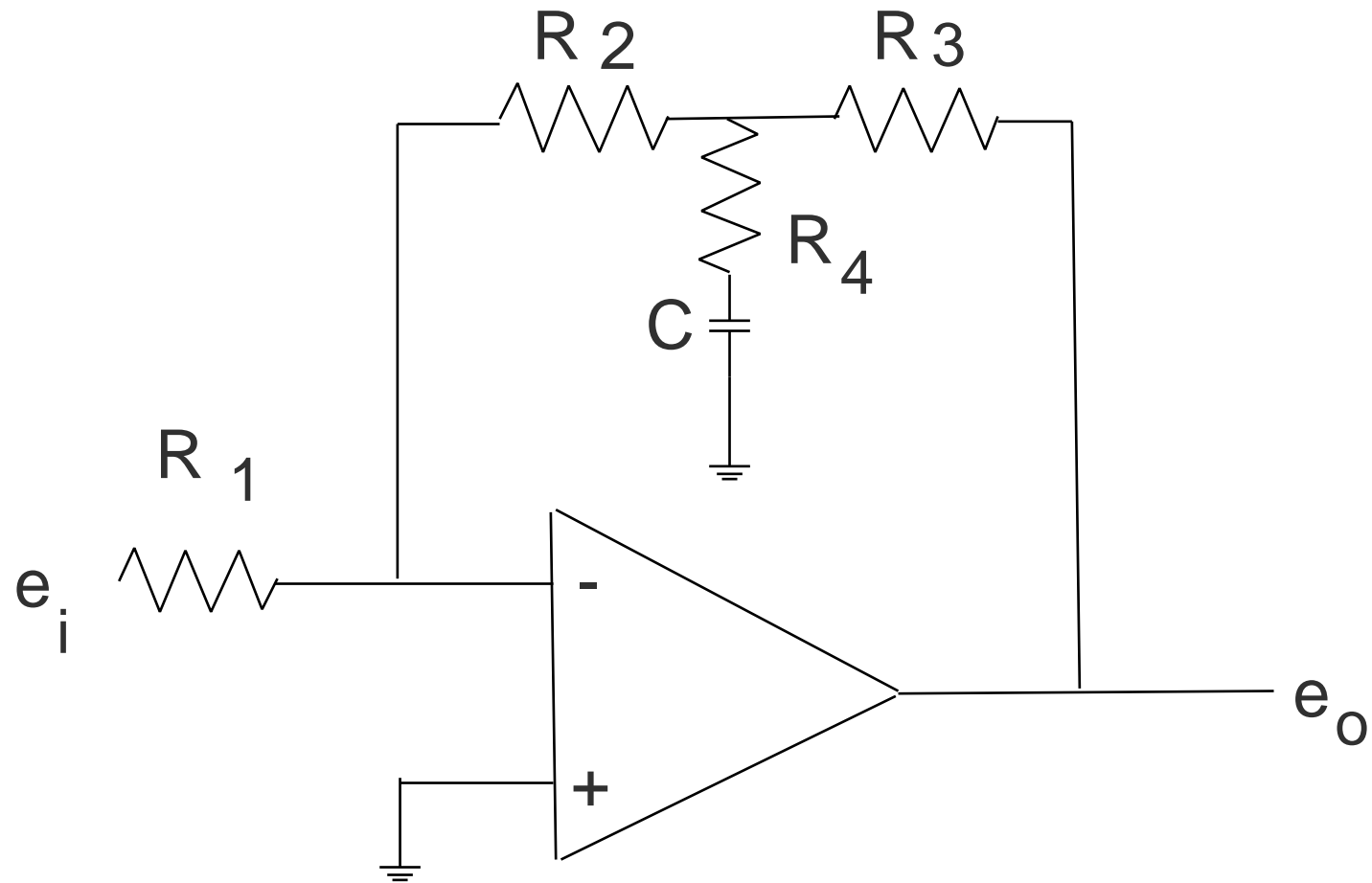



# FLOW GRAPH NONINVERTING AMPLIFIERS

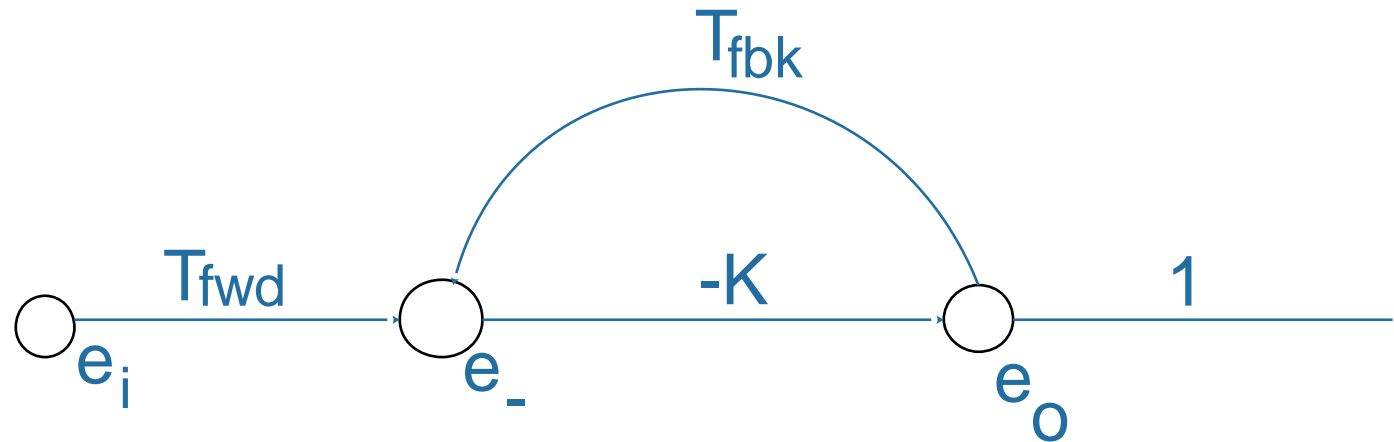

# TRANSFER FUNCTION

- $\frac{e_o}{e_i} = \frac{T_{fwd}(-K)}{1-KT_{fbk}} = \frac{-T_{fwd}}{T_{fbk}}$
- Let  $Z_4 = R_4 + 1/sC$
- $\frac{e_o}{e_i} = \frac{R_2+R_3Z_4/(R_3+Z_4)}{R_1Z_4/(R_3+Z_4)} = \frac{R_2+R_3}{R_1}$  For  $Z_4 \rightarrow \infty$
- $\frac{e_o}{e_i} = \frac{\frac{R_2R_3}{R_2+R_3} + Z_4}{Z_4} \frac{R_2+R_3}{R_1}$
- $\frac{e_o}{e_i} = \frac{\frac{(R_2R_3)}{R_2+R_3} + R_4 + 1/sC}{R_4 + 1/sC} \frac{R_2+R_3}{R_1} = \frac{sC \left[ \frac{R_2R_3}{R_2+R_3} + R_4 \right] + 1}{sCR_4 + 1} \frac{R_2+R_3}{R_1}$

# GENERAL FORM OF LEAD-LAG EQUATION

- $A \frac{(sTl_d + 1)}{(sTl_g + 1)}$

- General form networks:

$$\frac{A \prod(\text{Complex Conjugate roots}) \prod(sTi + 1)}{\prod(\text{Complex Conjugate roots}) \prod(sTk + 1)}$$

MOST NETWORK TRANSFER FUNCTIONS

$$G(S) = A \frac{\prod(sTi + 1)}{\prod(sTk + 1)}$$


GAIN THAT IS A FUNCTION OF FREQUENCY ALSO IMPLIES PHASE THAT IS A FUNCTION OF FREQUENCY

## CONTINUED


- Examine term  $(ST + 1)$  as  $S \rightarrow j\omega$
- Term becomes  $(j\omega T + 1)$
- At  $j\omega T$  equal 1 amplitude is  $\sqrt{2}$  and phase is 45 degrees
- When this term is in numerator phase positive
- When in denominator phase is negative

# GRAPH db VERSUS LOG OF FREQUENCY


- Asymptotic gain versus frequency

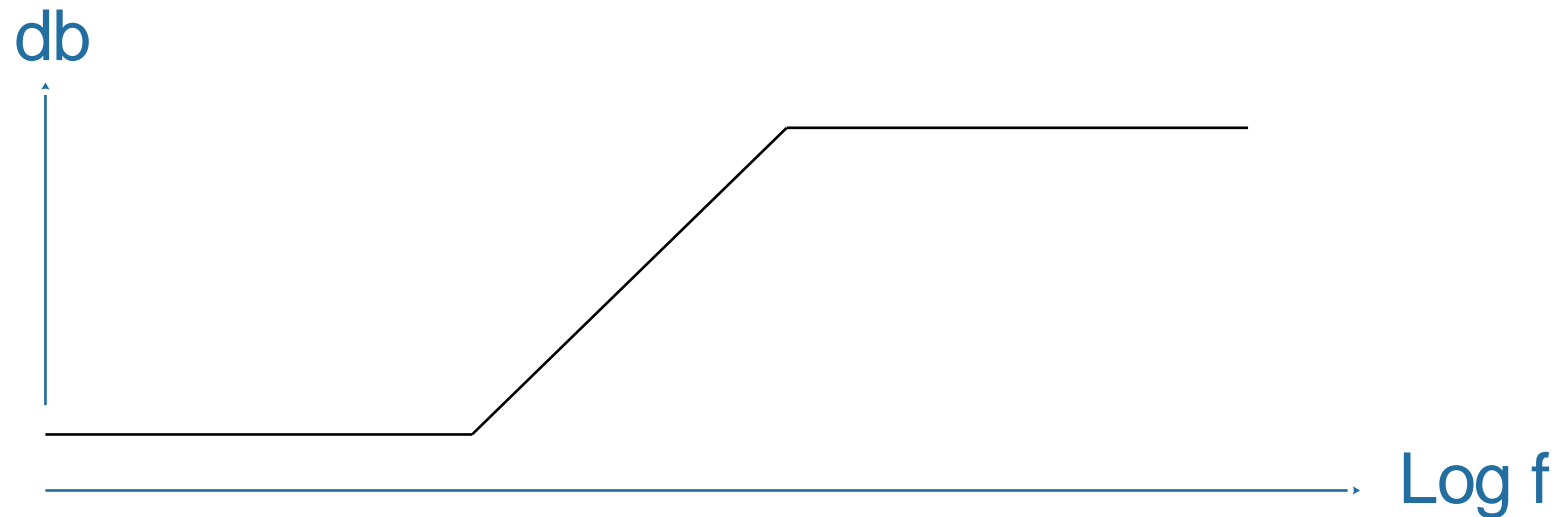

# OP-AMP LOADED WITH CABLE CAPACITANCE

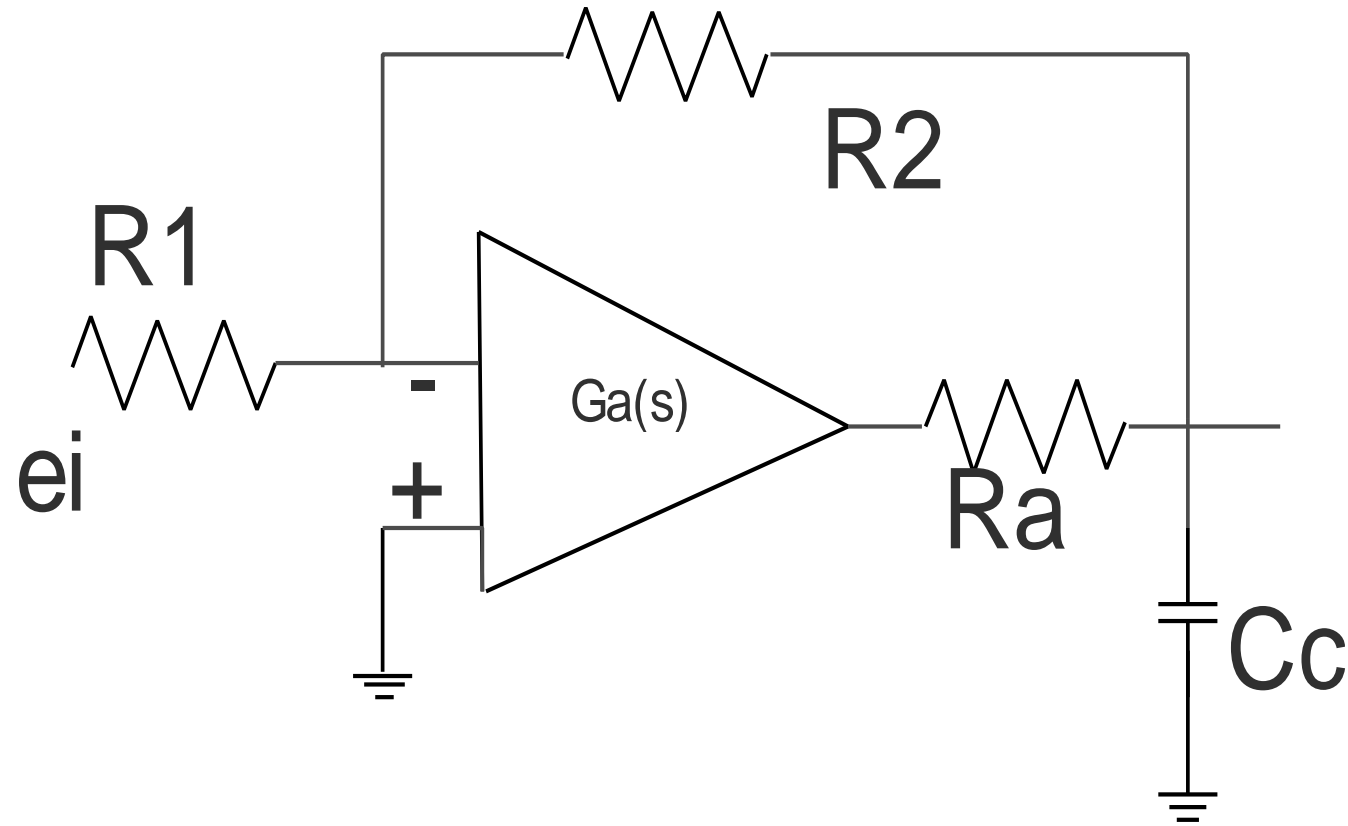

# FLOW GRAPH

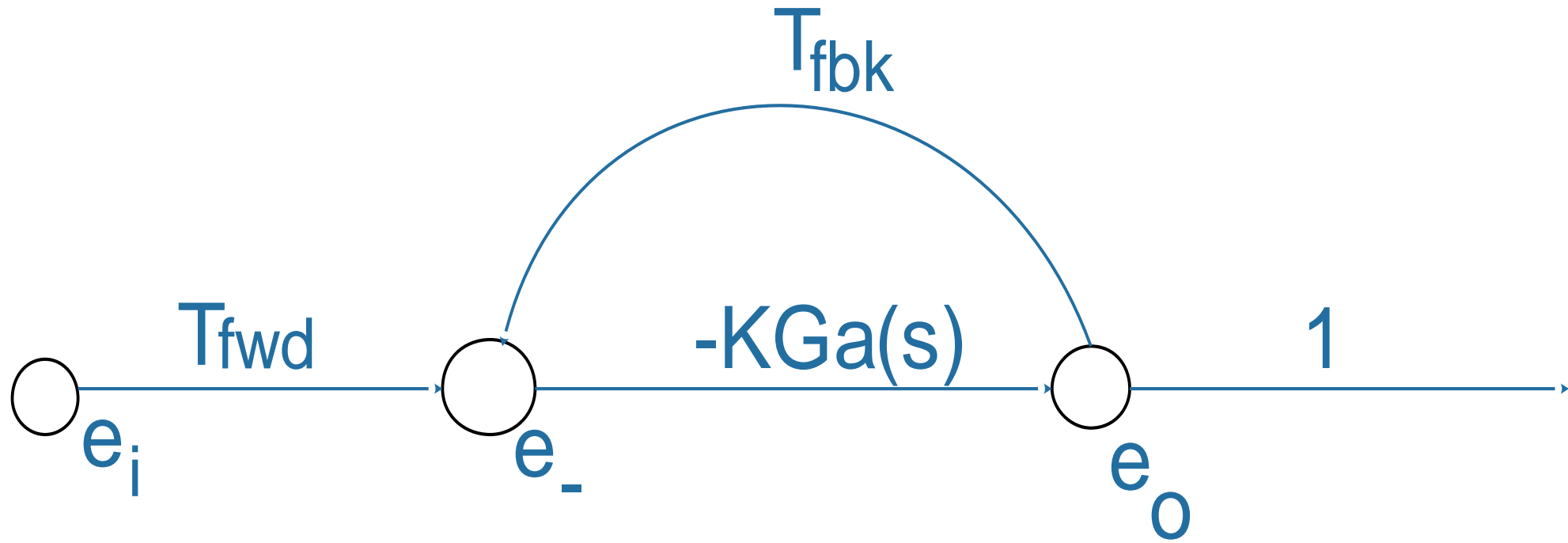

# OPEN LOOP GAIN

- $G(s)_{oL} = -kG_a(s) \cdot T_{fbk}$

- TYPICAL:

- $G_a(s) = \frac{1}{(sTd+1) \prod (sTi+1)}$

equals 1

*the terms  $\prod (sTi + 1)$  are above gain*

- $T_{fbk} = \frac{R1/(R1+R2+Ra)}{\frac{sCc(R1+R2)Ra}{(Ra+R1+R2)} + 1}$

- $(R2+R1) \gg Ra$

- $T_{fbk} = \frac{R1/(R1+R2)}{(sCcRa+1)}$



# STABILITY

- At the frequency where  $T_{fbk} \cdot K \cdot G_a(s)$ , the open loop gain, equals 1 the phase should be significantly positive (say 45 degrees). If it is negative oscillation grows. Much below 45 degrees circuit rings on noise.

## OPEN LOOP GAIN (CONT)

- $$G(S) = \frac{\frac{R1}{R1+R2}}{(sCcRa+1)} \bullet \frac{K}{(sTd+1) \prod (sTi+1)}$$
- The  $(sTi + 1)$  terms add negative phase shift and limit maximum amplifier bandwidth
- $CcRa$  is time constant caused by cable capacitance
- If it occurs before gain falls to one it adds between 45 and 90 degrees additional phase shift causing the amplifier to become unstable