

# Designing Switched-Mode Power Supplies in the High di/dt Era

*Dan Schwartz*

*2018.11.08*

*Application Engineer, Keysight EEsof EDA*



# Trends in Switched-mode Power Supplies (SMPs)

Consumer demand for:

- lower cost
- smaller size
- lighter weight

...is driving the industry to higher switching speeds “high di/dt”

 


Image courtesy of Transphorm

Traditional (cut-and-try) design methods don't work for high di/dt

- $V_{\text{spike}} = L_{\text{parasitic}} \frac{di}{dt}$
- Need to add a field solver to extract layout parasitics into an EM-based model

# Switched-Mode Power Supply (SMPS)


## SIMPLE EXAMPLE: HARD-SWITCHED BUCK CONVERTER

Heat sink

Inductor


Capacitor

Image courtesy of Transphorm

 

LC low pass filter  
 $f_{knee} = \frac{1}{\sqrt{LC}} \cdot \frac{1}{2\pi}$


$$V_{out} = D \cdot V_g$$

 

 
# Higher Frequency Can Lead to Higher Switching Loss

UNLESS THE EDGE SPEED IS INCREASED AS WELL


Low frequency  
Slow edges  
Switching loss 3.5%



 Higher frequency  
Same slow edges  
Switching loss 15.3%





 Higher frequency  
Faster edges  
Switching loss 3.3%





If you want to *reduce* switching loss,  
you have to improve the edge speed  
*even more dramatically* than  
improving the switching frequency

# Current Loops: Schematic View

 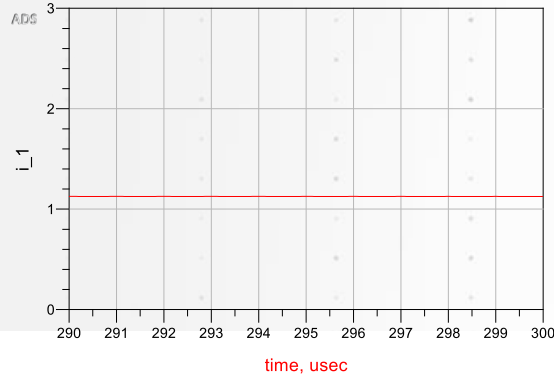

High  $di/dt$  in  
switched  
loop

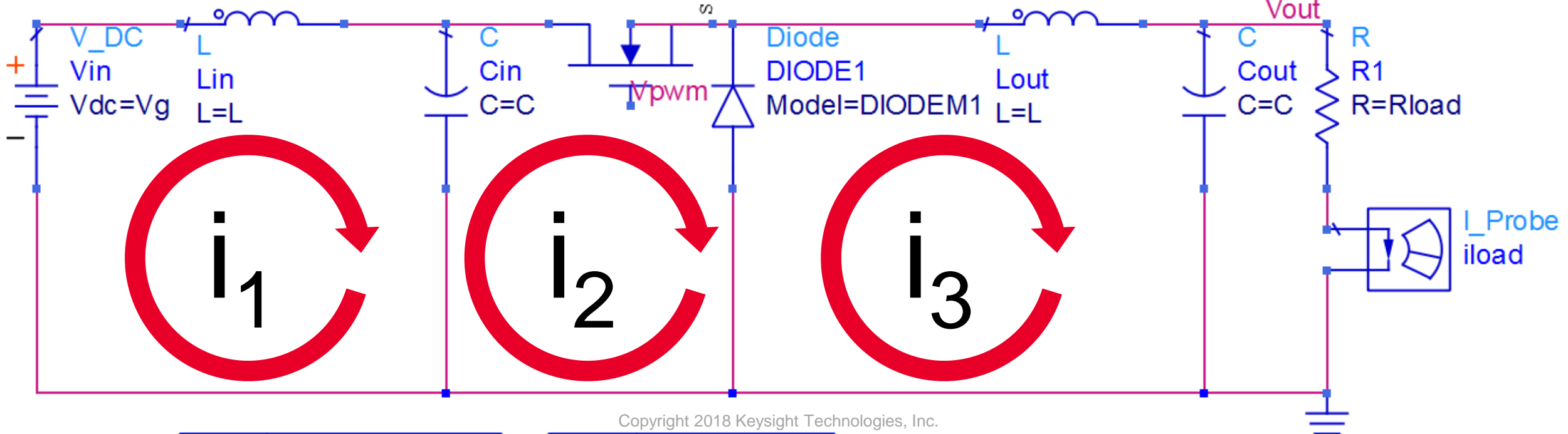 


# Current Loops: Layout View

When does the layout of the switched loop become important?

$$V_{\text{spike}} = L_{\text{parasitic}} * \frac{di}{dt}$$
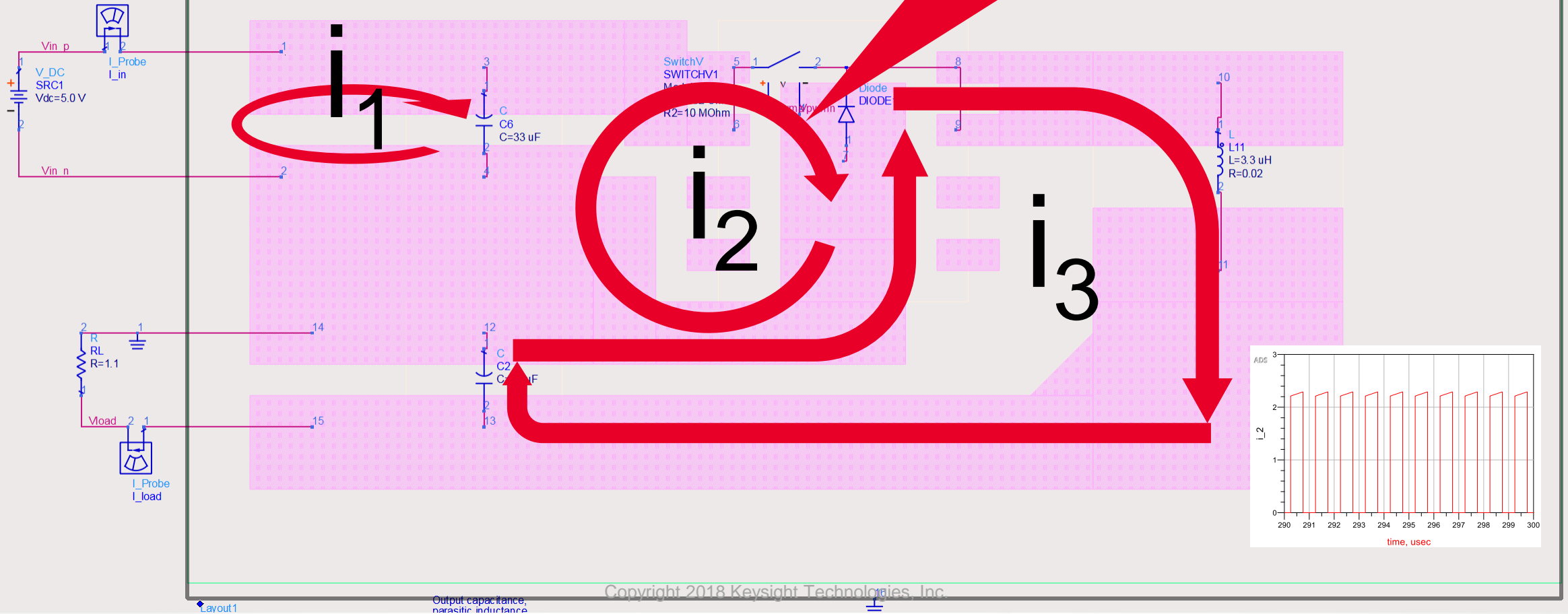
$$V_{\text{spike}} = L_{\text{parasitic}} * I_{\text{on}}/\tau$$



$$V_{spike} = L_{parasitic} \frac{I_{on}}{\tau}$$

Definition of inductance  
Linear ramp di/dt

$$\frac{V_{spike}}{V_{off}} = L_{parasitic} \frac{I_{on}}{\tau V_{off}}$$

Divide both sides by Voff

$$10\% = L_{10\%} \frac{I_{on}}{\tau V_{off}}$$

What inductance will give us a  
overstress spike that is, say,  
10% of Voff?

$$L_{10\%} = \frac{0.1\tau V_{off}}{I_{on}}$$


Rearrange, plug in some numbers  
10 ns, 20V, 4A answer is 5 nH  
Few mm of wire is 5 nH!


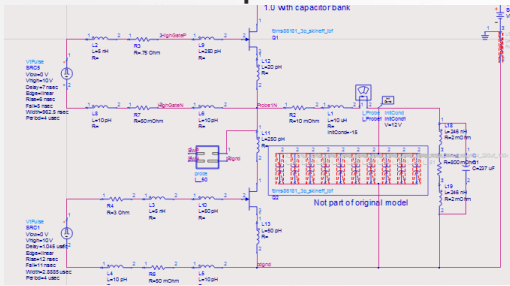
# Traditional Low Speed Design Approach

PRE-LAYOUT SPICE, THEN “CUT AND TRY”

Pre-layout schematic  
SPICE simulation:  
“Best Case” performance



First prototype has some excess ringing. Cut-and-try until “best case” approached



 
 
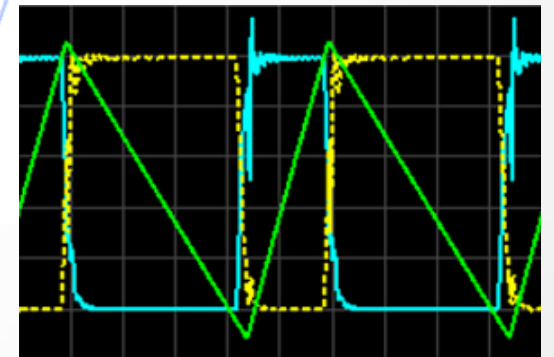


Image courtesy of ST Microelectronics

 2-6 spins  
\$6k-\$60k/spin  
3-8 weeks slip/spin




 
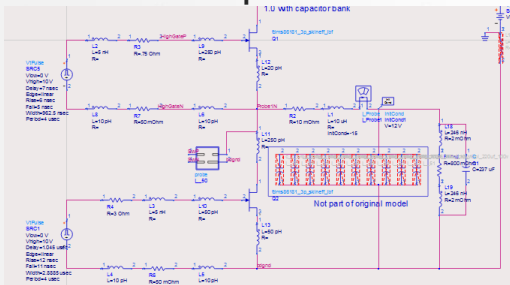
# Traditional Design Approach Applied to High Speed

PRE-LAYOUT SPICE, THEN “CUT AND TRY”


Pre-layout schematic  
SPICE simulation:  
“Best Case” performance



First prototype has destructive failure.




# What next?

 

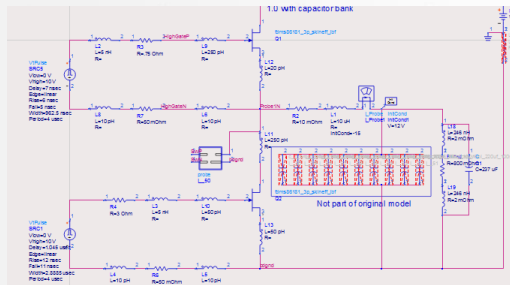
# Recommended High Speed Design Approach

Pre-layout schematic  
SPICE simulation:  
“Best Case” performance



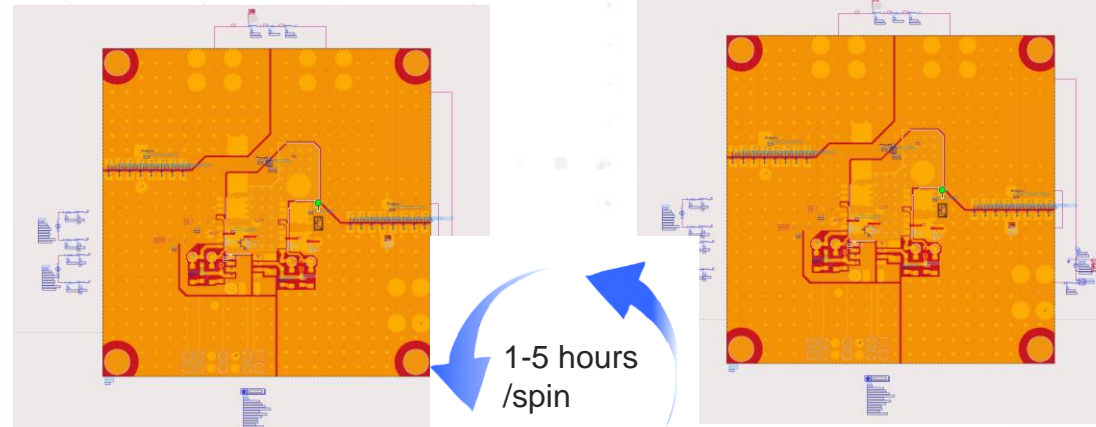
Post-layout: Integrated EM-circuit co-sim  
First “virtual” prototype has some excess ringing.  
“White box” – data display – 3D visualization  
Explore design space until “best case” approached



First pass success




 Power Device Gate Drive and Inductor Current (cycle view)





Power Device Gate Drive

 The inductor current increases while is on and decreases while FET2 is or.



  Power Device Gate Drive and Inductor Current (cycle view)






# Today's Modern EDA Solutions

NEW PROBLEMS REQUIRE DIFFERENT TOOLS

# State of the EDA Industry for PE

LARGELY A COLLECTION OF POINT TOOLS

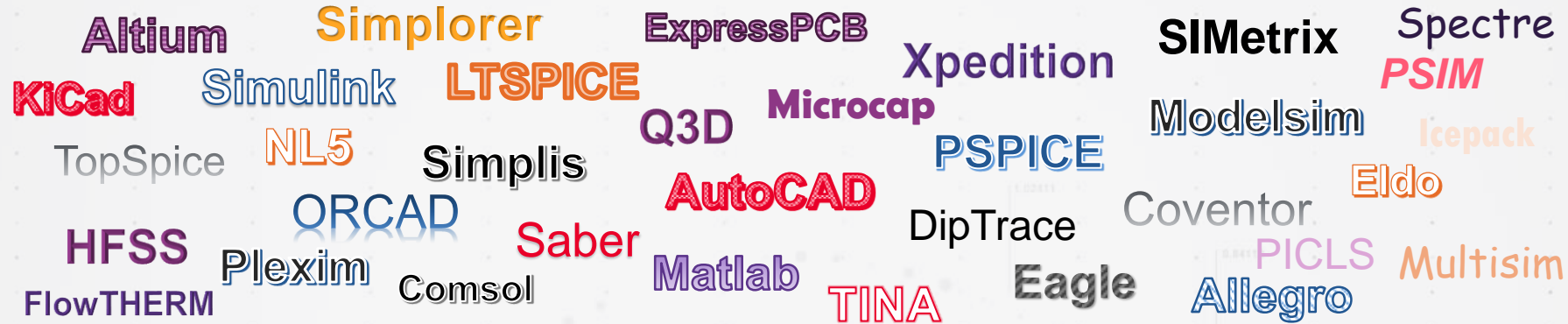


- A myriad of “point tools” exist, each fixed on a piece of the design process
- The biggest EDA tool issues power electronics designers mention:
  - Being limited on what they can analyze
  - Having to know and move among multiple tools to work

## ***High Speed Power Converter Tool Requirements:***


- 1) Integrated schematic and layout
- 2) Integrated circuit simulator (SPICE/Harmonic Balance)
- 3) Integrated EM engine



# Using ADS for EM-circuit Co-simulation

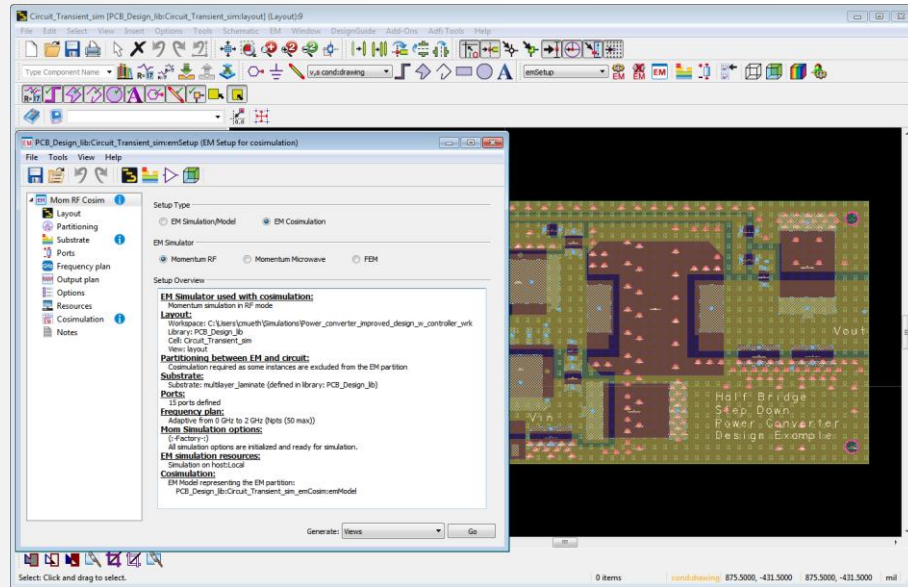

Layout and schematic are tied together


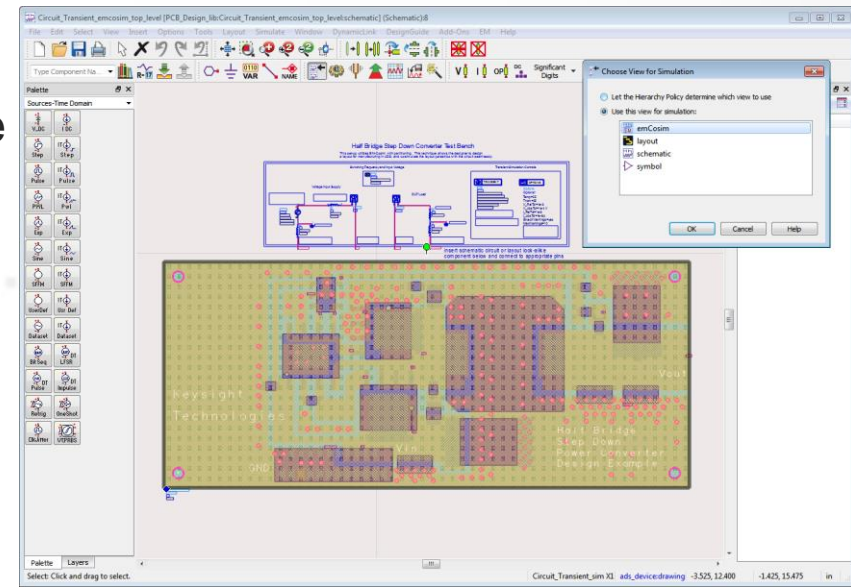


- Field solver extracts EM-based model of the layout parasitics
- Method of Moments provides the best balance of speed and accuracy for PCB/packages

- Compact, EM-based model of layout parasitics is added to the familiar transient (SPICE-like) circuit sim
 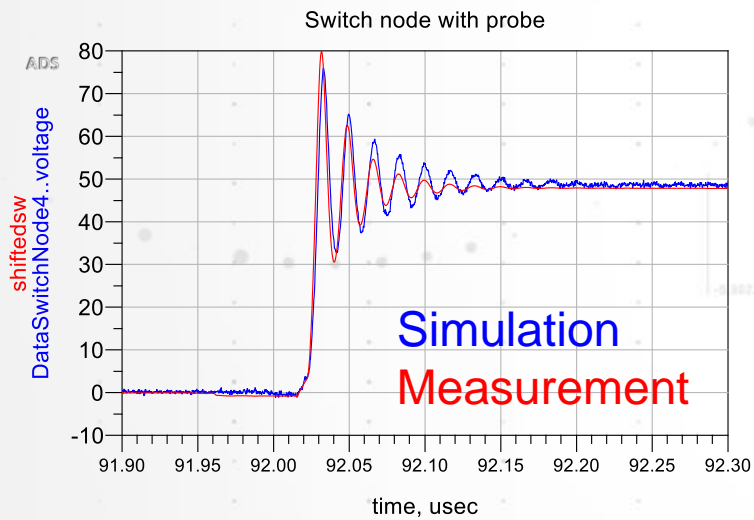
# Results from EM-circuit Co-simulation


- EM-model informs the circuit simulation
- Circuit excitation informs the EM post-simulation visualization display




# Keysight Integrated Power Electronics Solution

## ADVANCED DESIGN SYSTEM (ADS)


### W2240 Power Electronics Bundle

 


Schematic

 


Layout

 


3D viewer

 

Transient/convolution

 

Linear simulator

 


Momentum

**New!**

**PWM\_DUAL**  
**PWMD1**  
Freq=1 MHz

**Power Electronics Library**

 


Data display


```
// Motor
45 module motor(p, n, shaft, velo);
46   parameter real km = 4.5; // motor k
47   parameter real kf = 6.2; // flux c
48   parameter real kv = 1.0; // velocity
49   parameter real j = 0.004; // inertia
50   parameter real d = 0.1; // drag (frict
51   parameter real r = 5.0; // motor windi
52   parameter real l = 1e-4; // motor i
53   input p, n, shaft, velo;
54   electrical p, n, velo;
55   rotational_omega shaft;
56
57   analog begin
58     V(p,n) <= km*Omega(shaft) + r*I(p,
59     Tau(shaft) <= kf*I(p,n) - d*Omega
60     V(velo) <= kv*Omega(shaft);
61   end
62 endmodule
```

Verilog-A


### Product Options

 

W2342 FEM Simulator

 

W2300 Harmonic Balance Simulator

 


W2349 Electro-Thermal Simulator



# W2375 Power Electronics Library
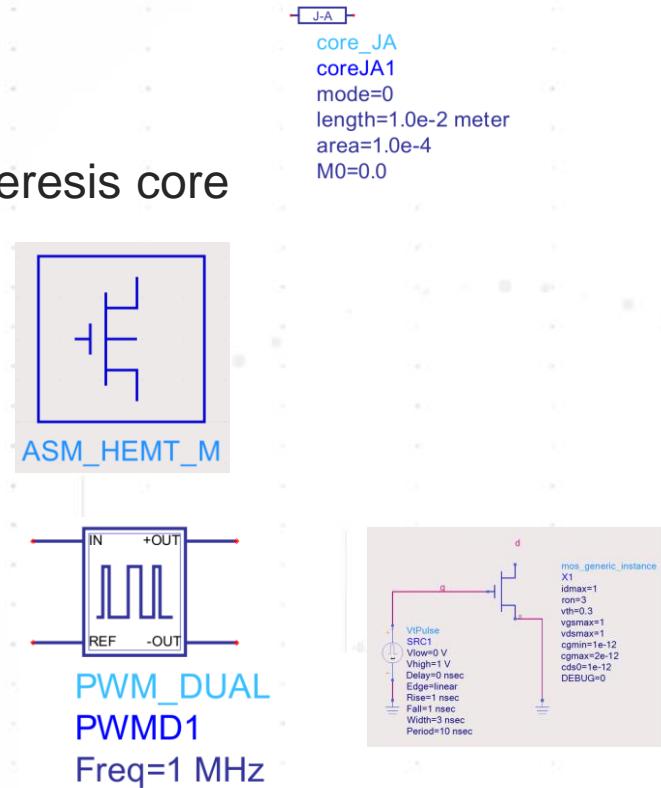
## NEW IN ADS 2017 UPDATE 1

- Non-linear magnetics
  - MMF-flux circuits
  - Jiles-Atherton saturation/hysteresis core
- Power device models
  - ASM GaN
  - PowerMOS SiC
  - Si IGBT
- “Pre-selection” components
  - PWM
  - Gate Driver
  - Generic MOSFET





# Power Electronics Library Etc. in ADS 2019

ADDITIONAL CAPABILITY SCHEDULED FOR NOV 1<sup>ST</sup> RELEASE

- Power Electronics “personally” in ADS:
  - [ADS Main Window]→Options→Work Flow Configurations→Power Electronics
  - Examples library (see next slide)
- Analog behavior of logic gates for digital loop compensators
  - BUF, INV, AND, OR, XOR, NAND, NOR, NXOR, D/SR Flip-flops, Schmitt
  - Compatible with equivalent components in LTspice and PSpice
- “Pre-selection” components
  - Voltage-controlled ideal transformer for “circuit average” abstraction method – duty cycle varies turns ratio in closed loop
  - 5-pin opamp: pwr/gnd rail noise, slew, bandwidth, etc.

**Note:** Please preview and influence future releases by joining our beta program (“Early Access Program” EAP)

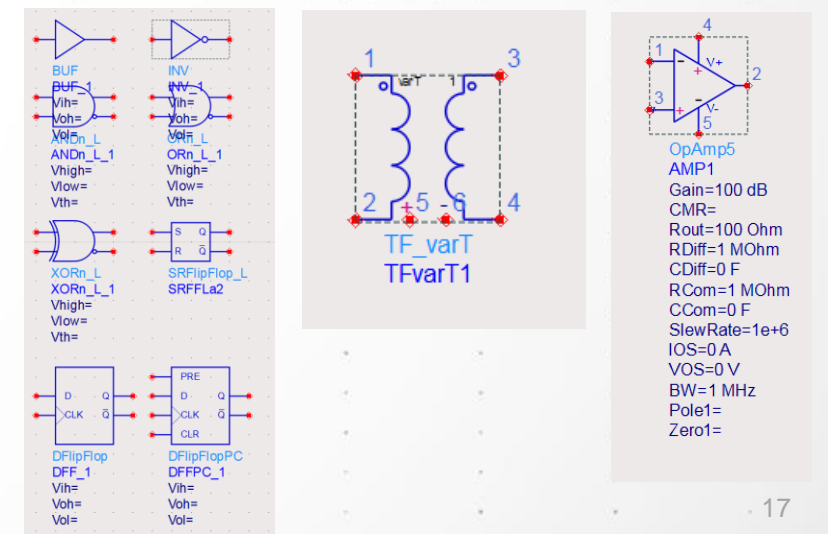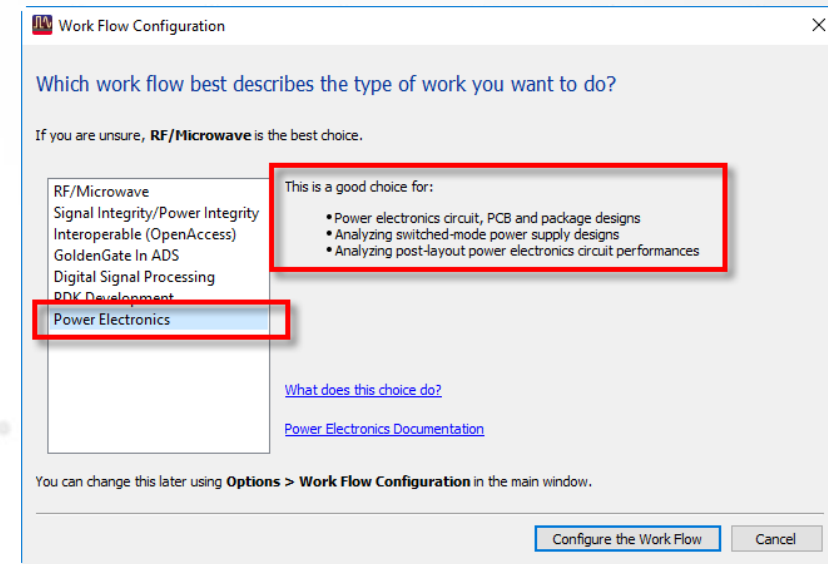Contact your local Field Engineer or Application Engineer for details



# Examples Library Expanded in ADS 2019

Open Example

Power Electronics Design Examples

Home > Design Flow Examples > Power Electronics Design

**Simulation of Nonlinear Magnetic Components**  
This example demonstrates the use of nonlinear magnetic components in Power Electronics Library of ADS.  
[Open documentation](#)  
[Open workspace: Nonlinear\\_magnetics\\_wrk.7zads](#)

**Simulation of Power Electronics Logic Gate**  
This example shows the usage of Power Electronics library logic gates: BUFFER, INVERTER and AND.  
[Open documentation](#)  
[Open workspace: PE\\_Logic\\_Gates\\_wrk.7zads](#)


**Simulation of Pulse-Width Modulator**  
This example demonstrates the behavior of pulse-width modulator model under different input signals in DC/transient/HB simulations.  
[Open documentation](#)  
[Open workspace: PWM\\_example\\_wrk.7zads](#)

**Simulation of Generic Gate Driver Model**  
This example demonstrates the behavior of generic gate driver model under different input signals in transient simulation.  
[Open documentation](#)  
[Open workspace: GateDrv\\_Example\\_wrk.7zads](#)


**Simulation of Keysight IGBT Model**  
This example illustrates the use of Keysight IGBT Model.  
[Open documentation](#)  
[Open workspace: IGBT\\_Example\\_wrk.7zads](#)

**Simulation of Buck Converter with Current Programmed Control**  
Includes Power Electronics simulation examples available in ADS.  
[Open documentation](#)  
[Open workspace: buck\\_srff\\_wrk.7zads](#)
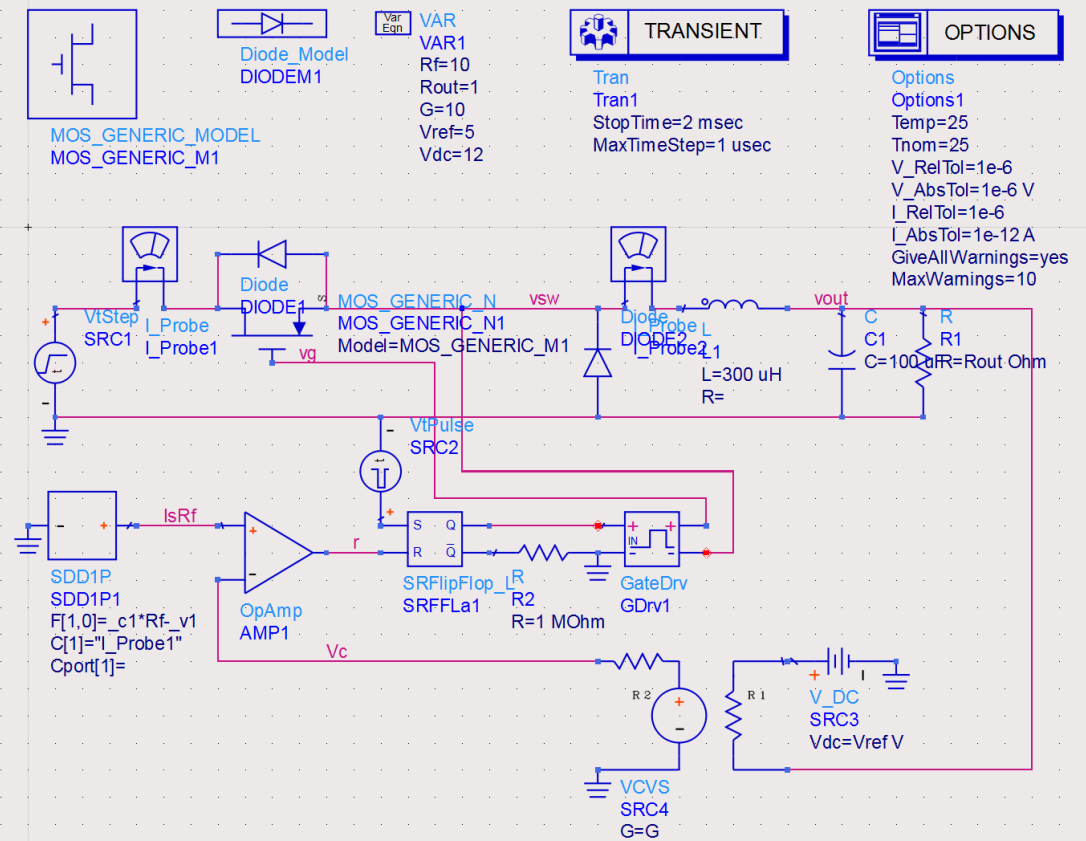
## Buck converter with current programmed control



# Complete Work Flow

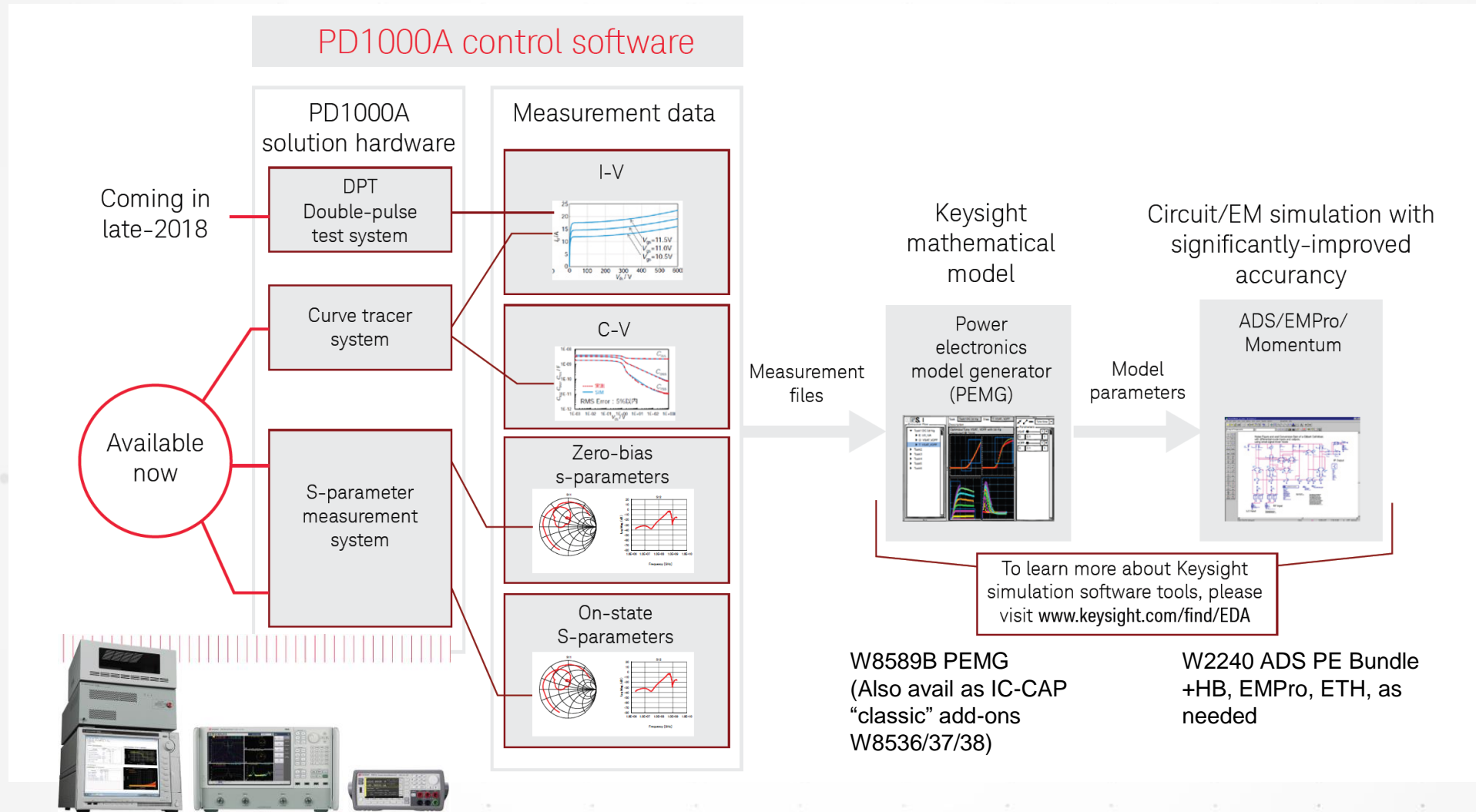

# Switched-Mode Power Supply (SMPS)


WE GO WHEREVER THE POWER/ENERGY GOES

## Sub-circuit simulation

Native ADS gate driver, analog/digital control loop incl. PWM
 
## Electrothermal

Solves for interaction of temperature rise on device heat output



## Power Device Model Generation And Simulation

IGBT, PowerMOS incl. SiC, ASM GaN

## Device and sub-circuit models for third-party tools

Import SPICE decks in non-ADS dialects: PSPICE, LTspice, etc.

## Connector simulation


Finite Element Method  
Finite-Difference Time-Domain Technology

## Non-linear magnetics

MMF-flux magnetic circuits  
Jiles-Atherton saturation/hysteresis model

## EM-based models: Package and board level parasitic extraction

Method-of-Moments Technology

 

## EMI/EMC

Copyright 2018 Keysight Technologies, Inc.

Center image credit: Transphorm




# Keysight EDA Power Electronics Key Investment Areas

```
1 .MODEL mydiode D
2 + RS=1.0000E-3
3 + CJO=1.0000E-12
4 + M=.3333
5 + VJ=.75
6 + ISR=100.00E-12
7 + BV=100
8 + IBV=100.00E-6
9 + TT=5.0000E-9
10
```

 
## Multi-lingual model import

- Dialects of SPICE
- Verilog-AMS
- VHDL-AMS


 
## Closed-loop analysis

- Bode plot
- Impedance analysis
- Stability in the presence of noise



## PathWave

- Connect device measurement, device modeling, circuit design, simulation, prototype characterization test, and manufacturing pass/fail test




## Multi-discipline, multi-nature support for motor control etc.

- Electrical: voltage/current
- Magnetic: MMF/flux
- Kinematic: position/velocity/force or velocity/force
- Rotational: angle/angular v./torque
- Thermal: temperature/power
- Logic: discrete or analog behavioral



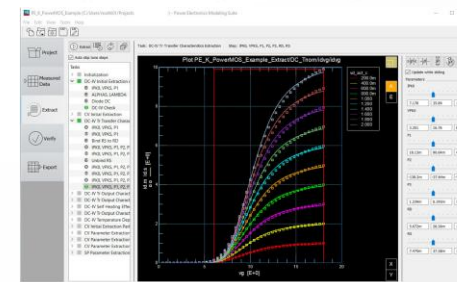
## Power device model generation

- IC-CAP: Full featured for device modelers
- PEMG: Simplified flow for circuit designers, models from a PDF datasheet


 
## Post-layout EM extraction

- PEPro (application-specific EM)
- Momentum (general purpose EM)
- EMI/EMC analysis





# Case Studies

WIDE-BAND GAP POWER DEVICES ENABLE HIGH  $di/dt$




# Predictive Results Can Be Obtained

REFERENCE DESIGN: POWER MOS + PACKAGE + PCB

On Semiconductor



On Semiconductor Test Board

 FDMS86181  
PowerTrench® MOSFET  
ADS package model



Customers often do not believe they can obtain predictive results. They Can!

Image courtesy of ON Semiconductor

  

# Enabling Semiconductor Technologies

## POWER SEMICONDUCTOR FIGURE OF MERIT (FOM)

Switching loss dominates conduction loss in high speed converters

Power Device Switching Loss:

$$P_{loss} = R_{ds(on)} (I_D)^2 (rms) + I_D V_D (Q_{sw}/IG) fs + 1/3 Q_{ds} V_D fs$$


Transistor FOM:

On resistance ( $R_{on}$ ) x gate charge ( $Q_g$ )

Low  $R_{on}$  = low  
transistor loss

Low  $Q_g$  allows the device to  
switch on and off faster


*Small FOM = fast dv/dt switching*

 

Sources:  
Kalfass - Keysight workshop (2015)  
Catrene (2013)

# Enabling Semiconductor Technologies
 
## HIGH SPEED POWER CONVERTER APPLICATION AREA



Rise/fall time and di/dt also increasing

# Utilizing Modern Design Methodologies for Wide-Bandgap Power Electronics

IMAGE LICENSED BY INGRAM PUBLISHING



*Predictive simulation techniques to save time and money*

by Chris Mueth  
and Rakesh K. Lal




ith the introduction of new gallium nitride (GaN)  
power switches into the market, designers have more  
device options open to them for creating efficient and

 
 
IEEE Power Electronics Magazine, June 2017 pp.46-55



$$\Delta V = Ri + L \frac{di}{dt}$$

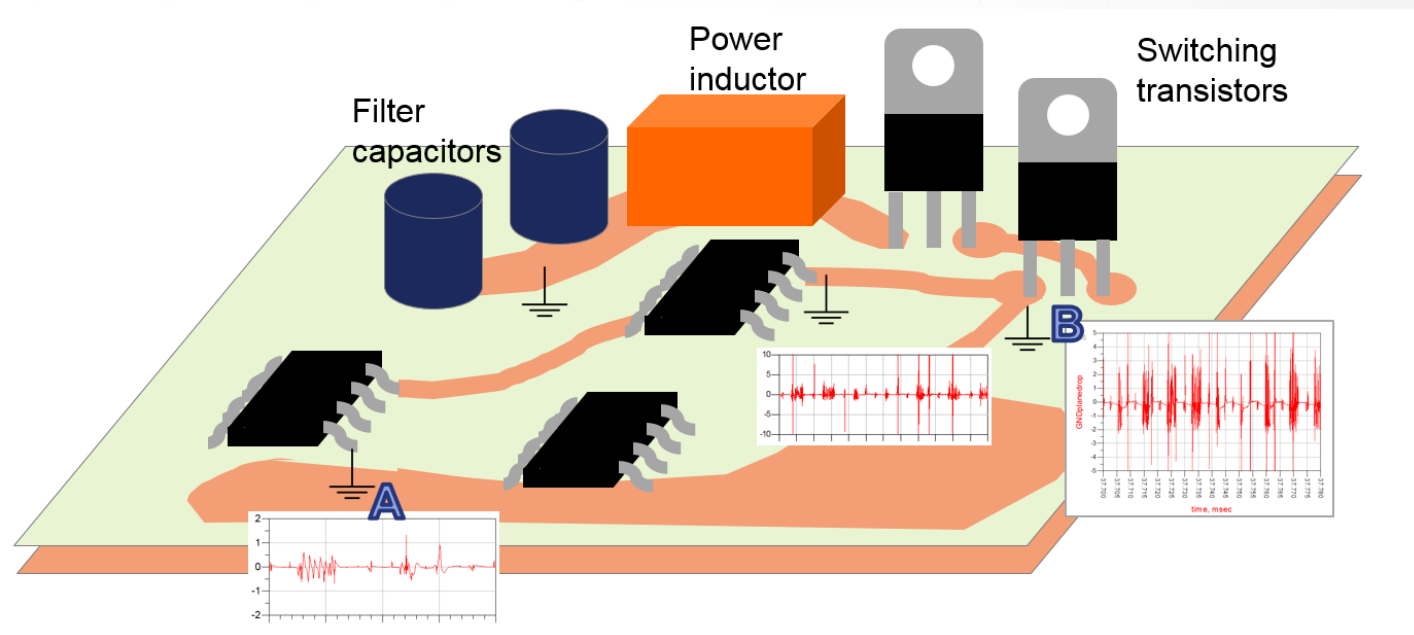



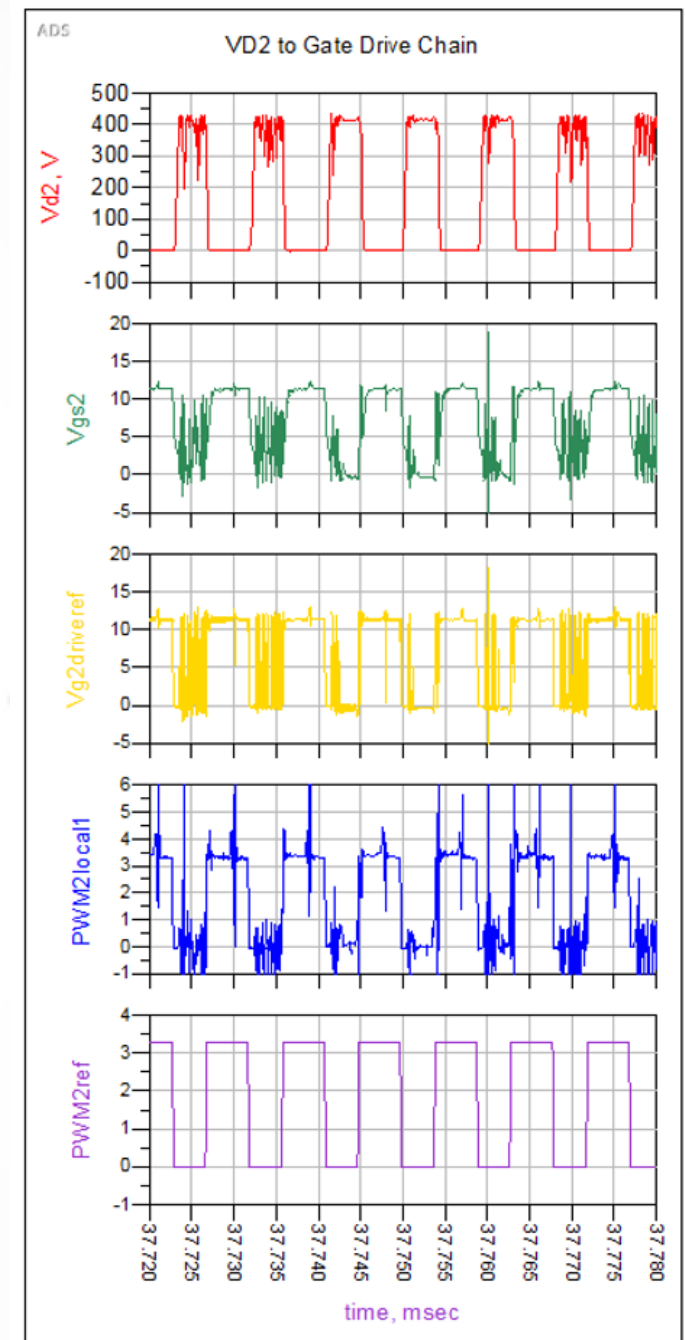 


# Identify the Limits of a Design

 
## MULTI-PULSE TESTING

Transphorm


IEEE Power Electronics Magazine,  
June 2017 pp.46-55



ADS Simulated  
Multi-Pulse Test

 

Lab Measured  
Multi-Pulse Test

 

Designers using GaN devices often experience failures they blame on the devices. It is their layout which is at fault!







# 3 kW Multi-Phase PFC – Failure Analysis

ST Microelectronics

NOISE IMMUNITY IS COMPROMISED


Pre-layout  
Schematic  
Only

  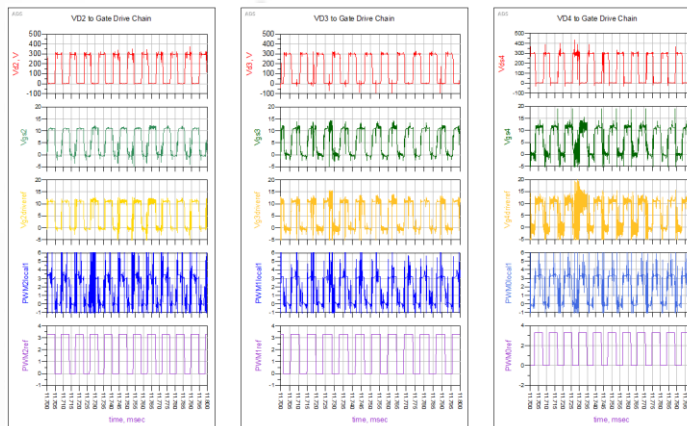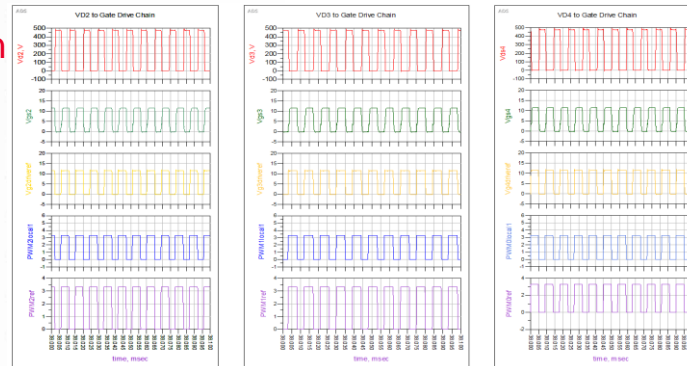Power device drain  
Power device gate  
Gate driver output  
Gate driver input  
PWM output



1<sup>st</sup> pass success of modified design

 - 52W/cubic inch
- Pout = 3kW @ Vin = 230Vac
- Vout = 400V
- PF > 0.98 @ 20% load
- THD < 5% @ 20% load




# EMC Analysis

REASONABLE CORRELATION WITH MEASURED RESULT!

EMC compliance testing is expensive and no insights are given on how to correct issues

International Conference on  
Electronics Packaging 2016:  
*Importance of Switched-Mode  
Power Supply IC Model for  
Conductive EMI Noise  
Simulation*  
CISPR, part 25

Rohm

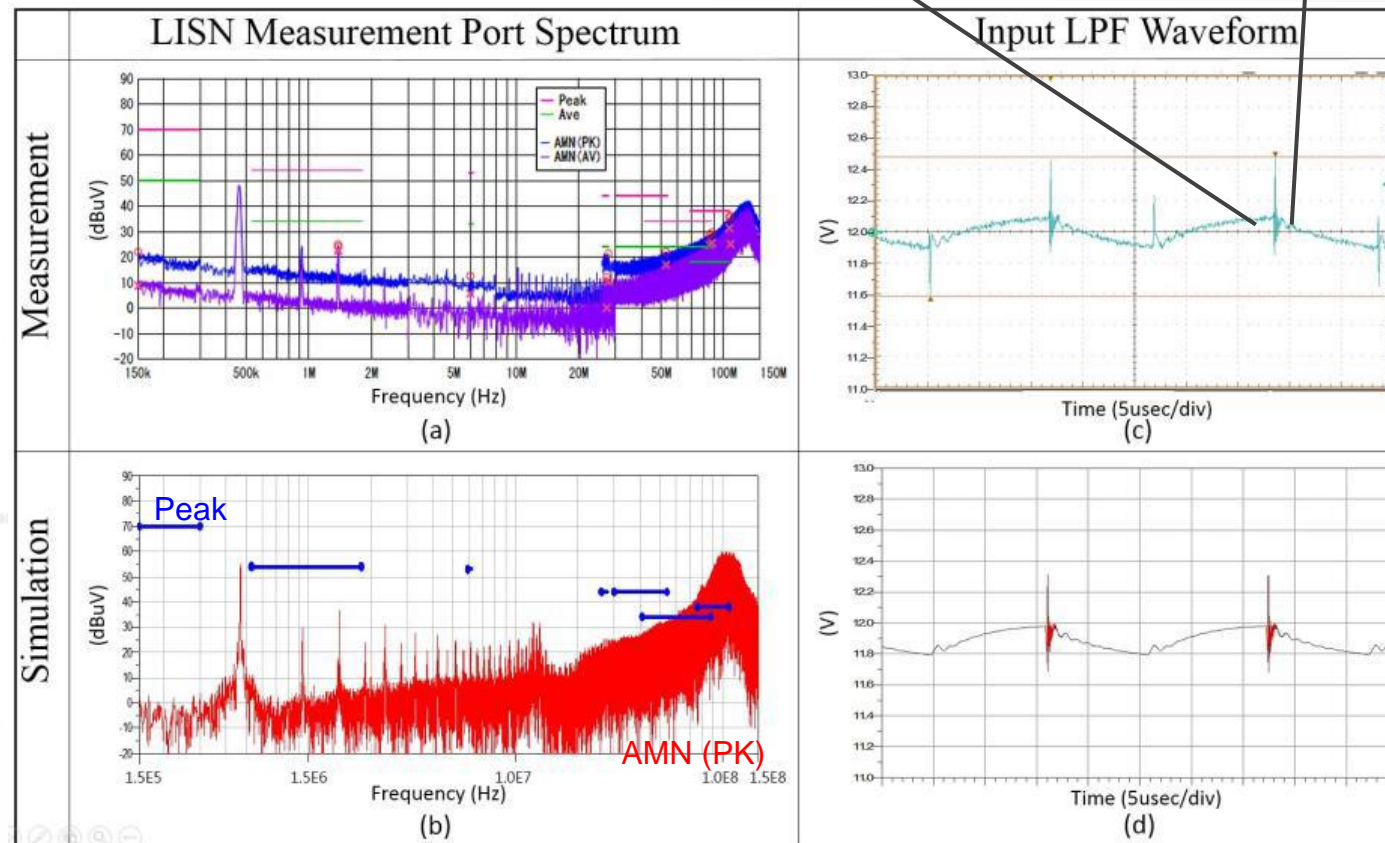

# Thermal Floorplanning


## SIC POWER MODULE ANALYSIS – ALL WITHIN ADS

Device	ICEPAK Point tool	ADS Electro- Thermal	Delta [K]
Q1	172.4	169.0	3.4
Q2	169.8	168.1	1.7
Q3	168.4	167.5	0.9
Q4	168.4	167.5	0.93

Temperatures are often difficult to measure in the lab, and thermal tools are difficult to use and too slow to be practical.

**Simulation time  
~25 seconds!**

## On Semiconductor

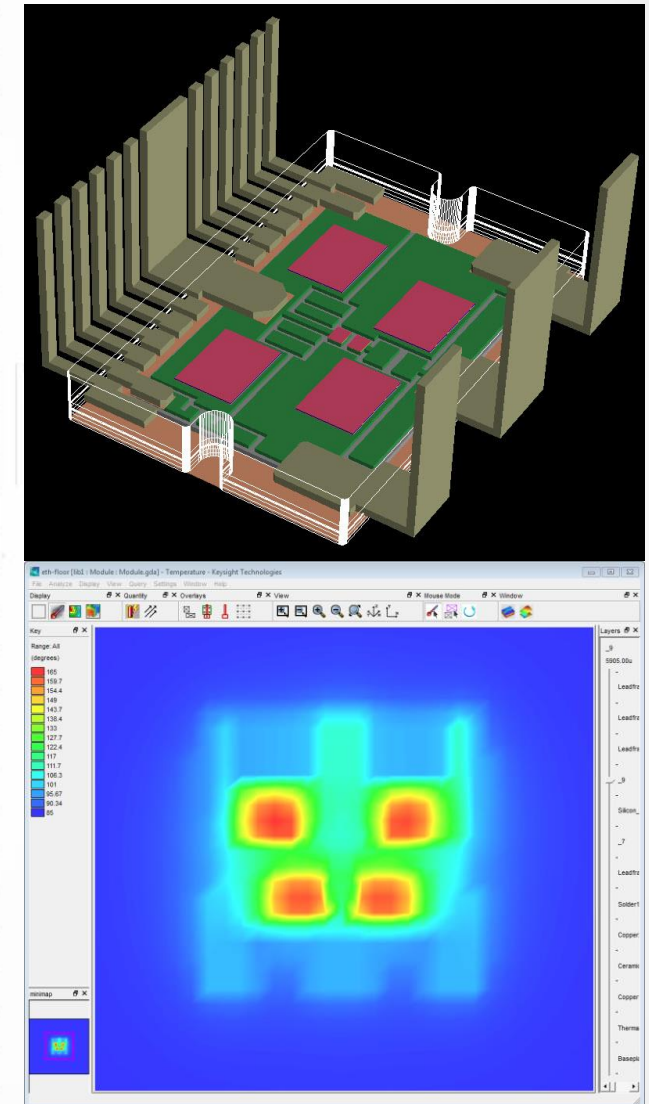

# Conclusions

- Increasing power density trends are pushing up switching speed
- High switching speed introduces a whole new class of challenges
  - Parasitic effects destroy performance and are costly
- EM Co-simulation provides the best predictive analysis you can get
  - An integrated workflow provides more capability and streamlines the workflow
  - Quick Start Guide for ADS in Power Electronics

<https://literature.cdn.keysight.com/litweb/pdf/5992-2514EN.pdf>