 




Do GaN FETs have Internal Diodes?

Brian Miller Nov. 2023
brian.miller@epc-co.com



Agenda – Diodes in GaN Devices?


- Motivation: Why use GaN power devices?
- Do GaN FETs have a “diode”?
- GaN Reverse Conduction (“diode”) Advantages & Disadvantages
- Optimizing Design
- A Look Forward: GaN Advances

This talk is approved for CEU/PDH credit. Web link to apply for it:
www.ieee.li/forms/2871

Motivation for Wide Band Gap Devices


The potential of wide band gap

 - **SiC** and **GaN**: theoretical much smaller size for a given $R_{DS(on)}$
- Can this potential be realized?
 - **Silicon MOSFETs** **have** reached their potential. Real-world devices match the **green line**
 - What about **GaN** FETs? What advancement is seen?



Why use GaN FETs?

 
- From the previous graph:
 - Lower On Resistance
 - Smaller
- Faster – lower switching loss
- Lower System Cost – higher freq. → smaller L, C
- Reliability



GaN FET Structure – Is there a Diode?


A Review – GaN Structure

 - Low voltage GaN are typically lateral devices
- MOSFETs have parasitic p-n diodes in their structure
- GaN FETs do not have this p-n parasitic diode element
- So... no diode in GaN?
- Not exactly...




Various GaN FET Symbols




 
- Schematic symbol varies among GaN FET manufacturers
- EPC shows a diode
- GaN Systems doesn't show a diode
- Navitas Semi. doesn't show a diode
- Transphorm, Innoscience, TI, etc.



Cascode Schematic Symbol

 


Cascode Device Structure

    

Another way to turn on GaN

 - The “regular” way of turning on: Voltage from Gate to Source
 - $V_{gs} = 5\text{-}6\text{ V}$
- Alternate way: voltage from Gate to Drain, V_{gd}
 - Still must respect V_{gs} limits (varies by GaN FET manufacturer)
 - Assume $V_{gs} = 0\text{V}$
 - Drain goes negative
- Diode behavior!



GaN Characteristics

- No Reverse Recovery (Q_{rr})
 - No parasitic p-n diode
- Reverse “diode” conduction
- V_{th} (gate threshold): very small temperature variation



 


Figure 8: Reverse Drain-Source Characteristics

 


“diode” voltage vs. V_{gs}

 - The GaN “diode” voltage is a function of:
 - Threshold voltage... varies within a range
 - V_{gs}
- Approximate, typical equation:
 - For EPC GaN FETs
 - $V_{sd} = 2.5 \text{ V} - V_{gs}$



Graph

 - Example graph:
- If V_{gs} is negative
 - Reverse conduction voltage drop increases with negative V_{gs}
 - So, a GaN FET can be used as bi-directional block
 - for 3.3 V power supply:
 - $V_{gs} = -3$ V: blocks 3.3 V
 - $V_{gs} = 5$ V: on
 - Not commonly done...



Graph from GaN Systems:

<https://gansystems.com/wp-content/uploads/2018/02/gan-enhancement-mode-1500x861.jpg>

GaN “Diode”: Advantages & Disadvantages

GaN Diode vs. MOSFET's diode

- GaN “diode” Advantages
 - Zero Reverse Recovery (no Q_{rr})
 - Very Fast
 - Current Rating high
 - Uses main channel
- GaN “diode” Disadvantages
 - High voltage drop
 - Thus, potential thermal concerns for long conduction times

GaN “Diode” vs. MOSFET’s diode

- Qrr (MOSFET) vs. GaN “diode” drop: which is worse?
 - EPC did a paper
 - Built boards and tested
- MOSFETs: **red** & **black**
- GaN FET: **blue**

 


Fig. 11. Effect of $t_{d,on}$ on losses of test converters of Fig. 10.

Optimizing Design

Optimizing a GaN Design for Diode


Can we overcome “diode” high voltage drop?

- Reduce “diode” voltage? How about a V_{gs} bias?
 - No, due to V_{th} variation. Risk of conduction
 - Maybe there is a way??
- Short dead time
 - Minimizes loss in diode
 - Loss proportional to dead time
 - Virtual zero dead time
- Parallel Diode?
 - Trade-off: capacitance of added Schottky
 - Benefit at low frequencies

Optimizing a GaN Design for Diode


- Short dead time

 - Minimizes loss in diode
 - Loss proportional to dead time
- Examples: Renesas' [ISL81806](#) (buck) & [ISL81807](#) (boost) controllers
 - 15-20 ns dead time




- Near-Zero Dead time

 - Example: Analog Devices' [LTC7890](#) (buck)
 - Made-for-GaN
 - “smart near zero dead times”



Optimizing a GaN Design for Diode

 - Parallel Diode?
 - Trade-off: capacitance of added Schottky
 - Still no reverse recovery
 - But: some controllers need this
- Example: LT8390A
 - 4-FET buck/boost
 - Works well with GaN FETs, IF switch node not too negative
 - Schottky D2 added



From Analog Devices' LTC7800 data sheet

A Look Forward

an update from last year...

A look at future GaN advancements

GaN future advancements coming:

- Generational Improvement
 - 2021: GaN FETs are 300x away from theoretical performance limit
 - 2023: Approaching a 2x improvement vs. 2021
 - This leaves 150x for future years
- GaN power ICs
 - Now: Power FETs + gate drivers
 - Future: other functions, higher voltage, etc.
 - Leading to wider adaption
- Other Advances: NexGen, GaNPower, GaN Systems, etc.

A look at future GaN advancements



- Other advancements...
 - Made-for-GaN controllers and drivers
 - DC-DC, Motor drivers, synchronous rectification, etc.
 - New packaging
 - Automotive-approved GaN FETs and GaN ICs
 - To standard AEC-Q101 and –Q100
 - Radiation Hardened GaN FETs & GaN ICs
- Analog LTC789x family
- Rad-Hard
- bi-directional blocking, thermal

GaN Compatible Gate Drivers

Single Drivers

- LMG1020 & -25^a : ultra fast
- UCC27611 – with LDO
- LM5114
- 1EDB7275F* – isolated


Half Bridge Drivers

- uP1966E[‡] (80 V)
- LMG1205[‡] (90 V)
- MP8699B[‡] (100 V)

- LM5113-Q1^a (100 V)
- MPQ1918^a (100 V)

- LMG1210 (200 V)
- 1EDN71x6U (200 V)
- NCP51820 & -10 (650, 150 V)
- STDRIVEG600 (600 V)

 - Si827xGB1-IM^{*a} (650 V)
- ADuM4221A* (>600 V)
- 2EDB7259Y* (>600 V)




Additional Gate drivers in development

*isolated ‡ Footprint compatible
^a automotive

A look at GaN advancements

Reliability Advances → data sheet specifications

 
- GaN FETs: end of life often determined by $R_{DS(on)}$ increase
- Main factor is V_{DS}
- What about V_{DS} transients?
- Study → increased transient rating



GaN Reliability: Temperature

Testing a 100 V GaN FET at various temperatures

 - Temperatures:
 - 35 C (dark green)
 - 90 C (red)
 - 150 C (light green)
- Note the reliability at 90 C > reliability at 35 C & 150 C.
 - For $V_{ds} < 100$ V.



A look at GaN advancements


GaN future advancements coming:

- Navitas: protection features
- GaN Systems: next gen
- EPC: GaN ICs



GaN Integration

 Lateral FETs allow various voltages and $R_{ds,on}$ FETs on one die:



A look at GaN advancements


EPC's Gen 6 vs. Gen 5

- Same Size: **orange** & **green**
 - ~ same parasitics
 - Gen 6: 40% lower $R_{ds,on}$
- Same $R_{ds,on}$: **blue** & **green**
 - Lower parasitics
 - **Green**: smaller, lower cost
- Optimizes efficiency for a wider range

No heatsink, 1000-1500 LFM
Data shown for $T_{Case} \leq 110^\circ\text{C}$

$$V_{IN} = 48\text{ V}, V_{OUT} = 12\text{ V}$$
$$1\text{ MHz}, L = 2.2\text{ }\mu\text{H}$$

Buck Converter

 



Click on images to learn more




How To GaN Video Series

epc-co.com




3rd Edition Textbook

 

eGaN[®] FETs and ICs

Evaluation Kits



 


Layout Advances







- GaN FETs are faster than Silicon MOSFETs
- Good layout needed... or layout can limit performance!
 - GaN FETs' speed "forces" focus on layout
- Goal: minimizing inductances.
 - Let's review...

Impact of Power Loop Inductance

   


Layout Comparisons

    


Top Layer

Lateral

 

Top Layer Bottom Layer


External Vertical

 


Top Layer Inner Layer 1

Internal Vertical


Layout Inductance Comparison

 



Lateral

 

Ext. Vertical

 


**Int. Vertical
Best Choice**

  

Getting to a Low Inductance Layout

 1. Components: Vertically close
2. Vias: Close to the innermost electrical connection
3. Substrate: Thinnest permissible thickness between outer and first inner layer
4. Via Connections: Spread out at innermost connect
5. Ground Return: doesn't need to carry full current



Getting to a Low Inductance Layout

Variations: vertically rotate caps & FETs

- Original: Caps → top FET → bottom FET
 - Ground on 2nd layer
- Variation 1: top FET → bottom FET → caps
 - Vin on 2nd layer
- Variation 2: bottom FET → caps → top FET
 - Switch node on 2nd layer.. Buried
 - FETs a bit separated, better for thermals

