

Matching Network Design Using Non-Foster Impedances

Stephen E. Sussman-Fort, Ph.D.

Antenna Products and Technologies
EDO Electronic Systems Group
Bohemia, New York USA 11716

Dept. Electrical and Computer Engineering
State University of NY at Stony Brook

stephen.sussman-fort@dp.ail.com

- Introduction
- Stability
- Laboratory Measurements: High-Q Negative Elements for Receive
- Laboratory Measurements: Non-Foster Monopole and Dipole
- Technology Development

Introduction

Motivation

- **Requirement:** broadband, efficient, *electrically-small* antennas ($l \ll \lambda$)
- **Electrically-short monopole:** characterized by *large reactance* and *low radiation resistance* (varies rapidly with frequency)
- **Wheeler and Chu (1947):**
 - Electrically-small antennas have almost the same directivity as larger antennas and can in principle perform as well as the larger ones
 - Problem is in *transferring power* to and from small antennas, which are very difficult to impedance match
- **With conventional matching technology, small antennas suffer from:**
 - *Poor gain* due to mismatch loss or lossy impedance matching (when attempting a broadband match)
 - *Narrow bandwidth* due to the high Q of the antenna (when attempting to maximize gain)


Consider:

- An electrically-small broadband VHF antenna with typical gain 20-30 dB below isotropic
- A MIL receiver, designed for best compromise in sensitivity & dynamic range (noise figures of 6-8 dB)

In such a system:

- It is receiver noise –*not external noise*– that limits sensitivity
- ***Greater sensitivity will result from increasing antenna gain via non-Foster matching***
- Passive matching limited by gain-bandwidth constraints

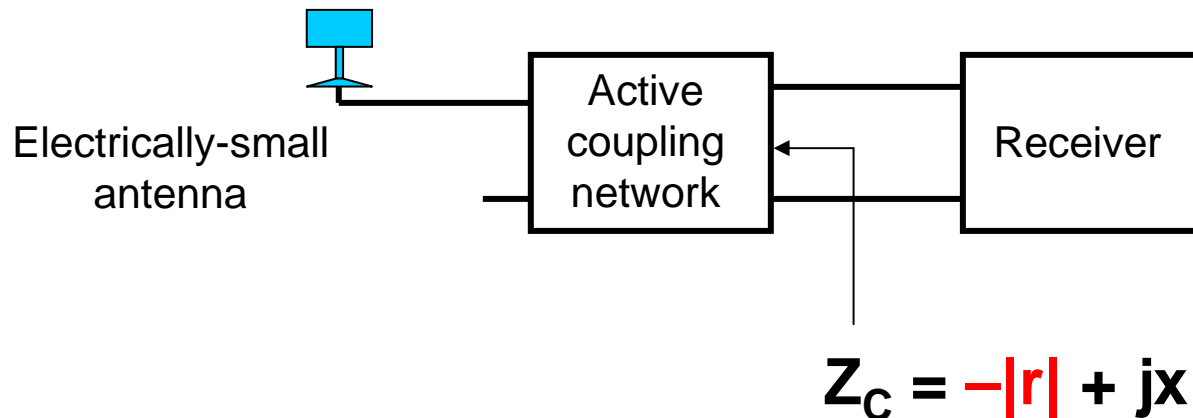
- 1971: First mention of using *negative inductance* for bandwidth extension of dipole antennas (Poggio and Mayes)
- 1977: First use of an active coupling network with *negative resistance* to improve noise figure (Bahr)




Non-Foster impedance matching employs negative reactive elements ($-L, -C$)

- **The Fano-Youla gain-bandwidth theory:**
 - for matching networks containing positive RLC or distributed elements
 - gives limits on the achievable bandwidth
 - implies that certain sources and loads (e.g. electrically-small antennas) cannot achieve a good match, regardless of circuit complexity
- **Circuits containing *negative elements* (“non-Foster” networks):**
 - are not constrained by gain-bandwidth theory
 - can achieve wide matching bandwidths with “difficult” loads arising from electrically-short antennas

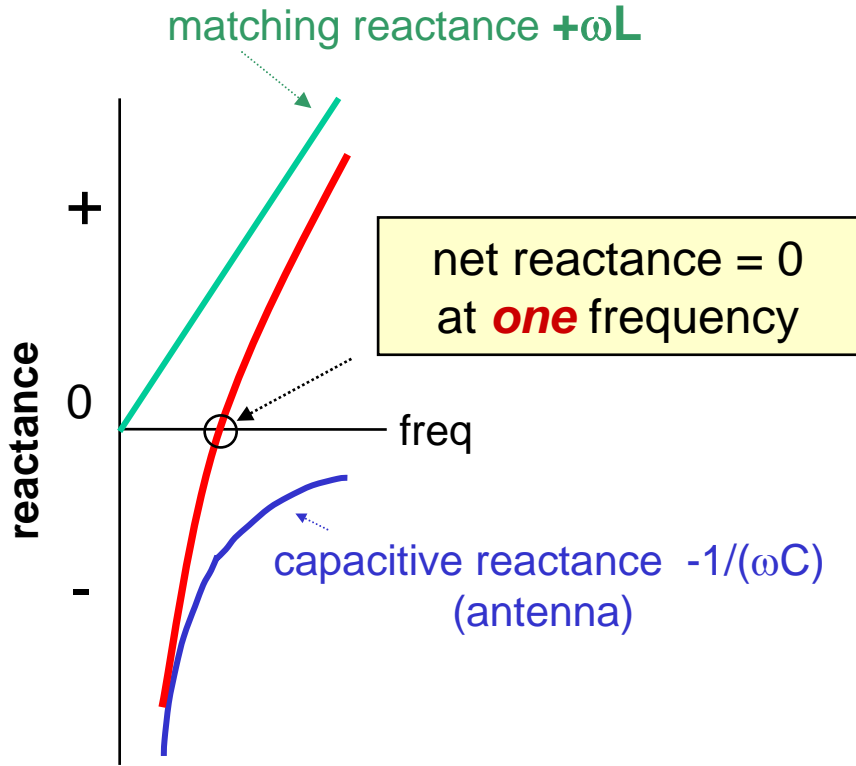Conventional vs. Negative Impedance Matching




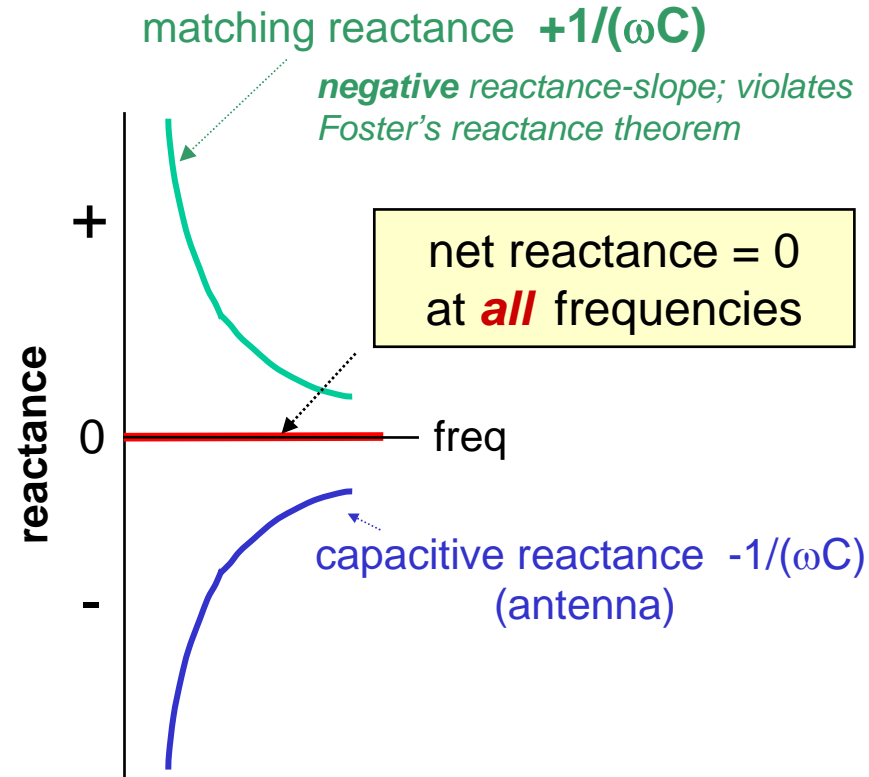Resonate $+C$ with a **positive inductor**




Resonate $+C$ with a **negative capacitor**


Antenna Model

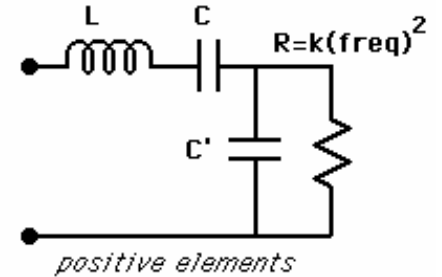

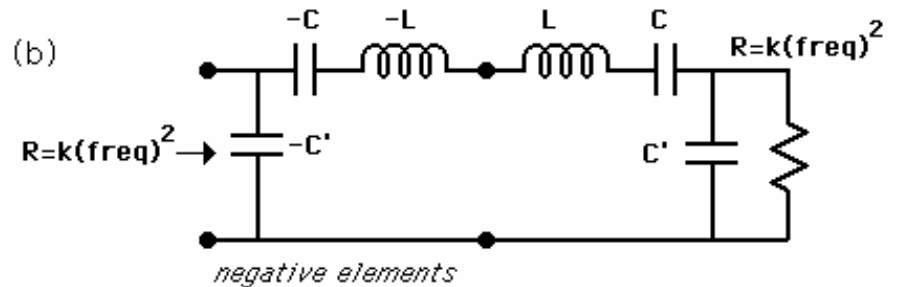Antenna model with L, C, and C' canceled by $-L$, $-C$, and $-C'$



Inductive-T completes the match to 50Ω

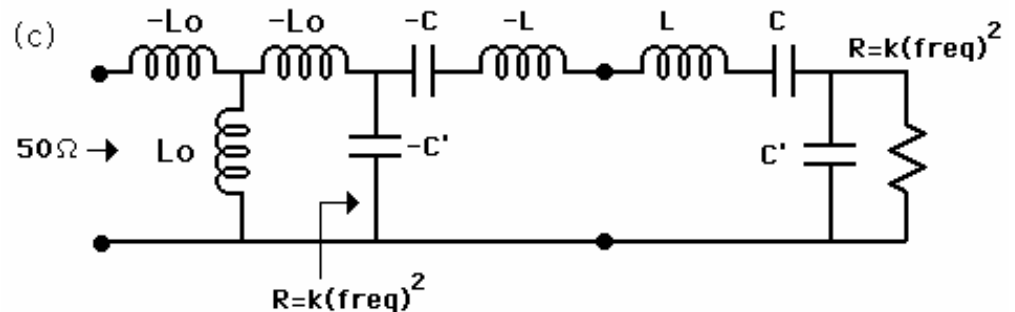

Dualizer

- For the tee and pi L networks shown

$$Z_{in} = \omega^2 L_o^2 / Z_L$$



- If Z_L is the frequency-dependent resistance

$$Z_L = k\omega^2$$

and if we want the input impedance Z_{in} to be the real and constant value R_o , we choose


$$L_o^2 = kR_o$$

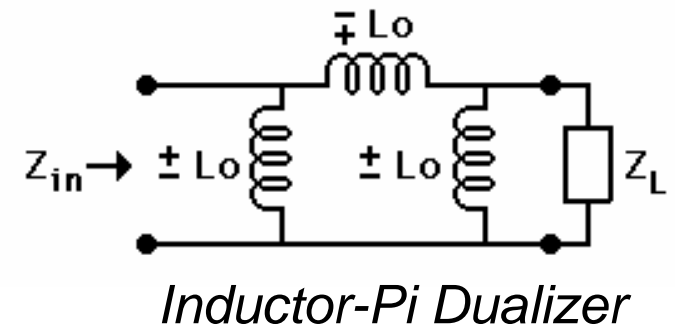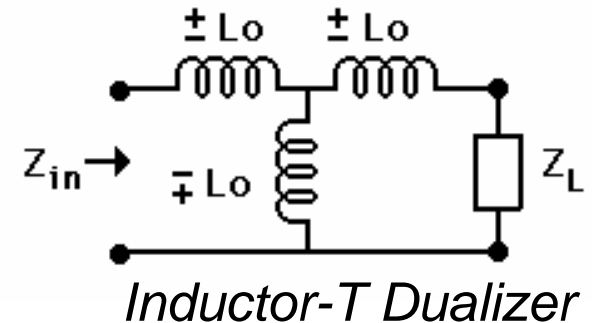(also used in coupled-resonator filter design)




Realizing Negative Elements

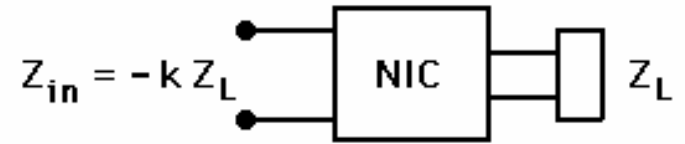
A *negative* element is produced by terminating a *negative impedance converter* (NIC) with a corresponding *positive* element



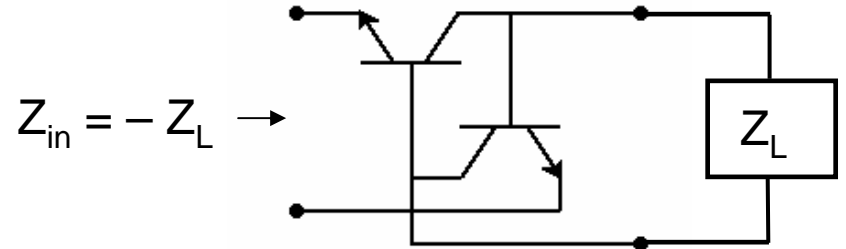
Floating negative impedance
(Linvill, 1953)



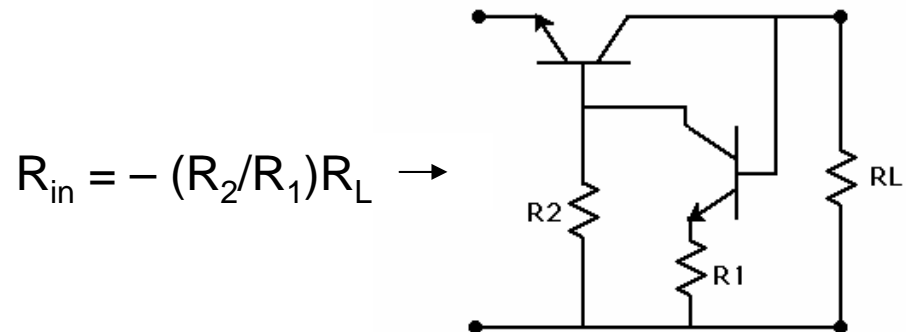Grounded negative resistance
(Linvill, 1953)




How a Voltage-Inversion NIC Works

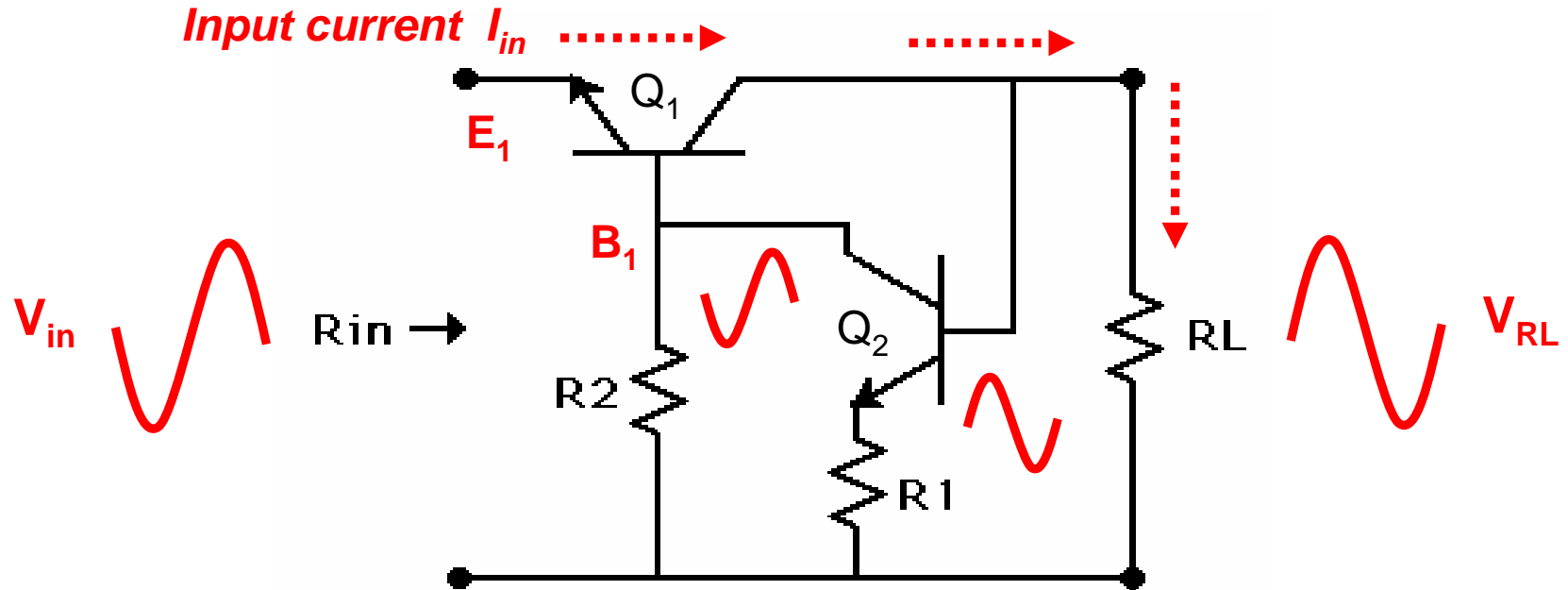


- Input current flows through Q_1 producing V_{RL} across R_L
- V_{RL} fed back through CE stage Q_2 producing 180° phase inversion at B_1
- Voltage at E_1 , V_{in} , appears in phase with voltage at B_1
- $R_{in} = V_{in} / I_{in}$ seen to be negative of R_L : because current is same, but voltages are inverted

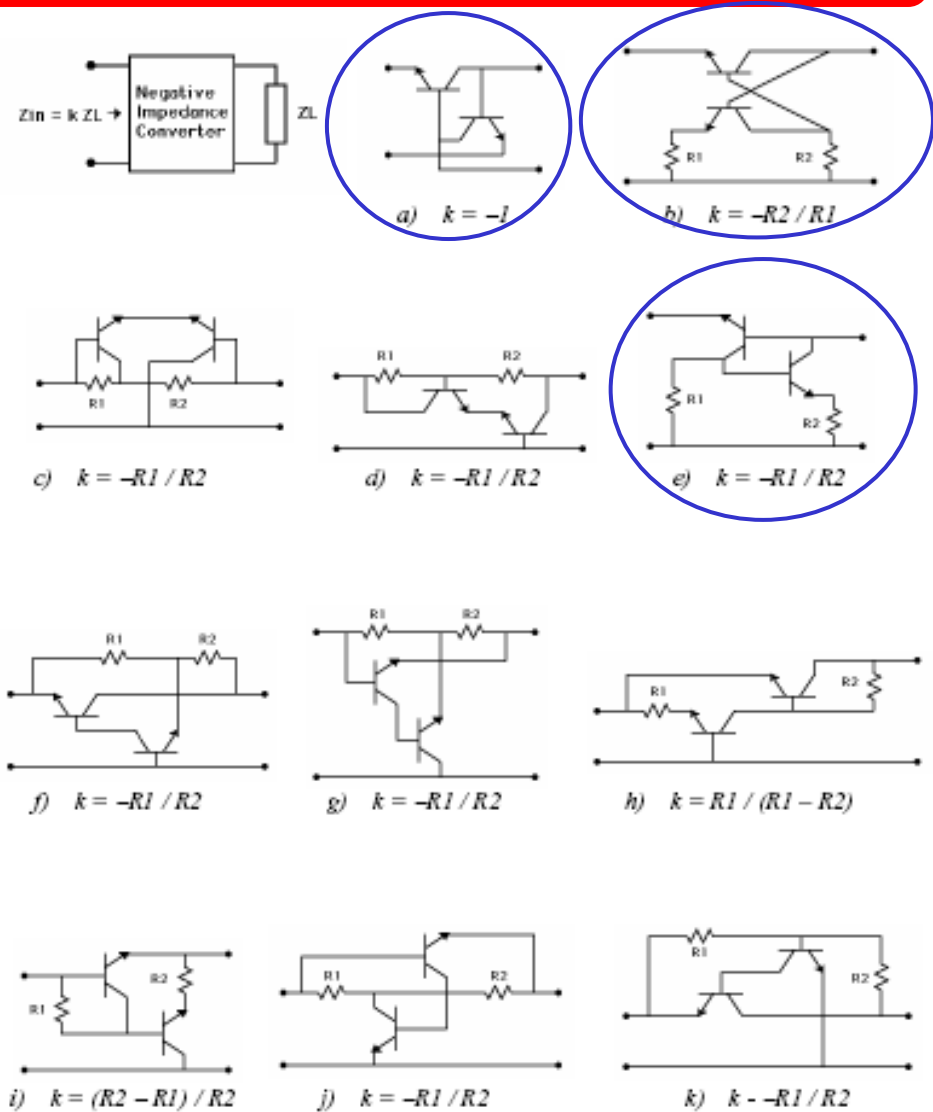
- Of the many NICs that have been proposed, only the *Linvill* and *Yanigisawa* circuits have been built and tested
- Some other circuits can be shown to possess inconsistent phasing with practical devices



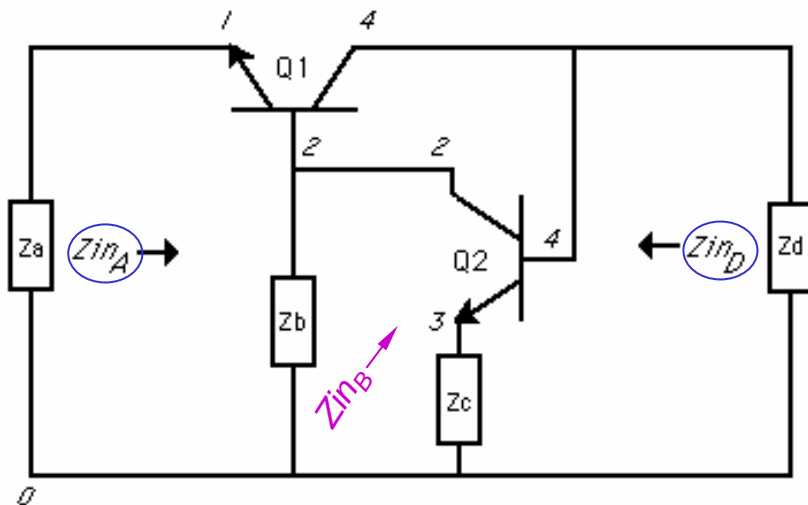Both the Linvill and Yanagisawa NICs are derived from the same terminated or “augmented network”



Augmented network

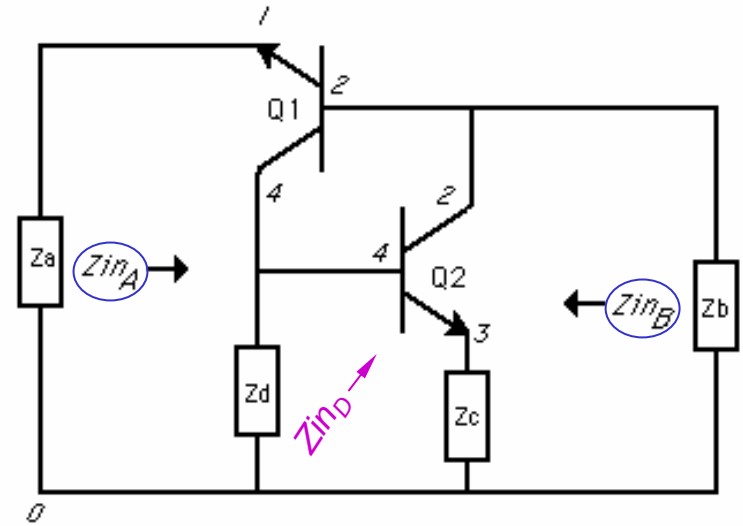

Augmented network, redrawn, but otherwise identical

Linville OCS: $Z_{in_A} = -(Z_b / Z_c) Z_d$

Linville SCS: $Z_{in_D} = -(Z_c / Z_b) Z_a$


Yana OCS: $Z_{in_A} = -(Z_d / Z_c) Z_b$

Yana SCS: $Z_{in_B} = -(Z_c / Z_d) Z_a$


The Linvill and Yanagisawa OCS configurations are, in fact, the same circuit

Early Use of NICs

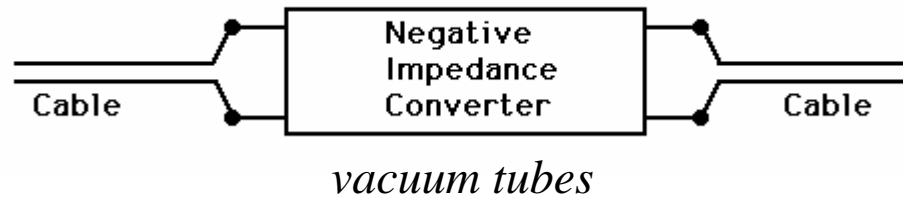G. Crisson (1931): Developed *negative impedance repeaters* to reduce loss on telephone lines



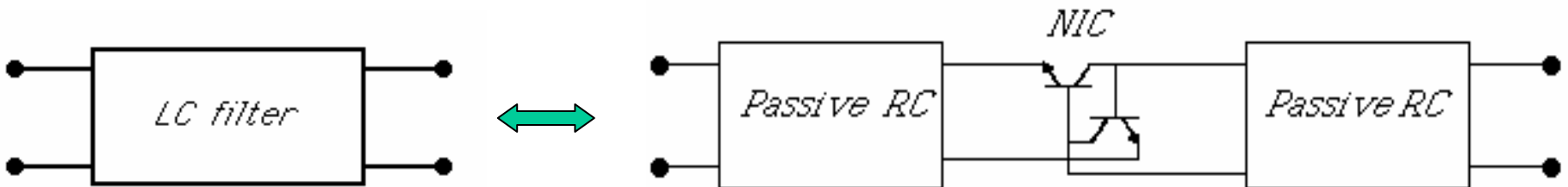J. G. Linvill (1954): First active-RC filter



The transfer function of any LC filter is realizable via an *RC-NIC-RC* structure

- Active RC filters (*NICs, gyrators, FDNRs are fundamental elements*)
- Q-enhancement of passive resonators in active filters
- **Broadband matching of electrically-small antennas**


Stability

Theorem: Negative Impedance Converters are *open circuit stable* at one port and *short-circuit stable* at the other port

Brownlie, 1965; Hoskins, 1966


Open-circuit stable:

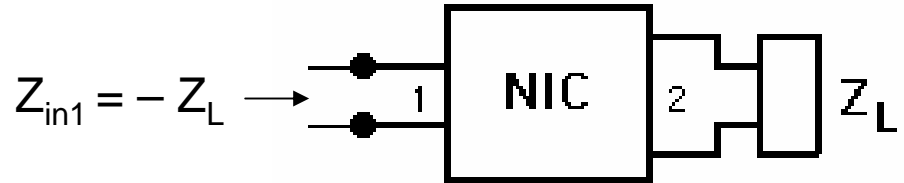For any passive impedance Z_L at port 2, the network defined by *open-circuiting port 1* is stable




Short-circuit stable:

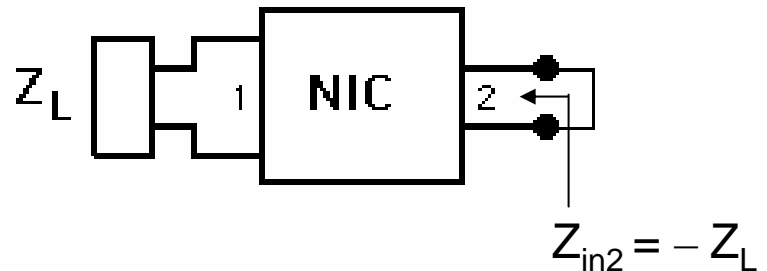For any passive impedance Z_L at port 1, the network defined by *short-circuiting port 2* is stable



Stability of NICs - 2

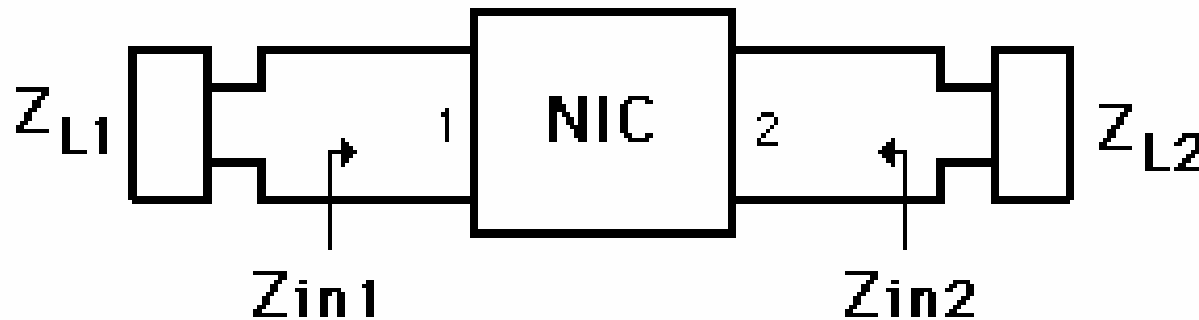The inherent conditional stability of an NIC constrains the *magnitude of the impedances* that can be connected to the *open-circuit-stable* port and to the *short-circuit-stable* port



Open-circuit-stable port:
requires $|Z_{L1}| \geq |Z_{in1}|$


Short-circuit-stable port:
requires $|Z_{L2}| \leq |Z_{in2}|$

By what margins? – depends upon nature of Z_{L1} and Z_{L2}

- NICs must be terminated properly for stability
- In addition, the natural frequencies of any network containing NICs must reside in left-half s-plane
- *In practice, the natural frequencies cannot be allowed to get very close to the j-axis*

For network stability, loop impedances must be positive

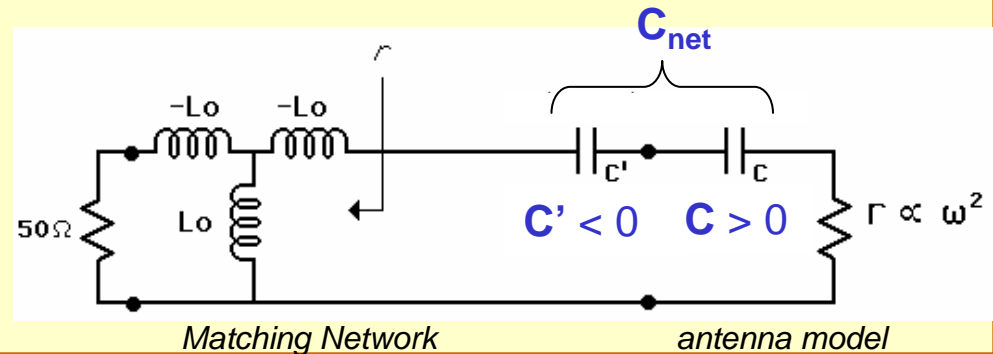e.g. **C** is positive : **C'** is negative
but **C_{net}** = (**C** in series with **C'**)
must be positive




Predicting Stability in NIC Circuits

- Transfer function of an NIC: $T = A / (1 + A\beta)$
- The feedback loop in an NIC must provide *gain and/or phase margin* for stability:

$$|A\beta| < 1 \quad \angle A\beta < 180^\circ$$

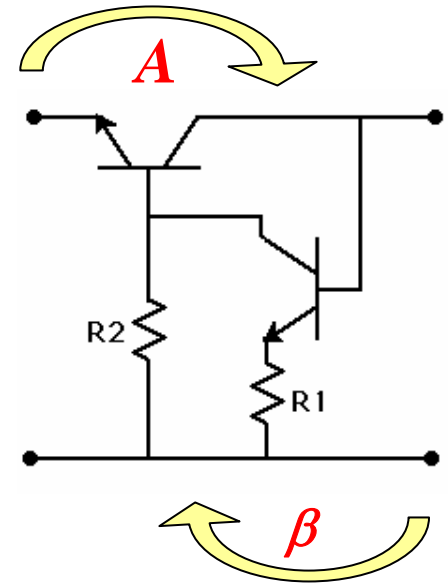- Middlebrook's technique permits accurate evaluation of $A\beta$ with all loading effects
- *Idea:* break feedback loop; perform current-gain and voltage-gain analyses, combine results to yield $A\beta$
- With adequate component simulation *models*, the technique is an excellent predictor of stability for both the NICs and the overall network




Linvill Grounded NIC

Laboratory Measurements: *High-Q Negative Elements for Receive*

- Historical results for negative-R and active filters: ***good***
- Results for negative L,C: ***poor*** (low-Q elements)
- **EDO has developed broadband, stabilized NICs and high-Q negative L, C elements**
- Experimental results follow for representative circuits

Grounded Negative Capacitors and Inductors

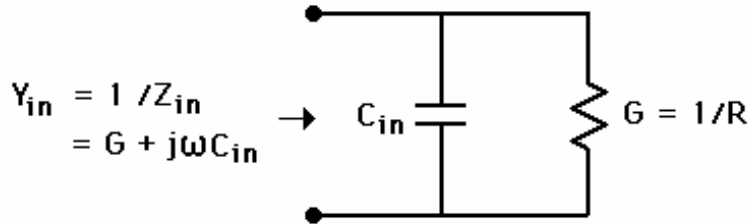Capacitor modeled as an ideal C_{in} in parallel with a conductance G




Capacitor Q: *magnitude* of $\frac{\omega C_{in}}{G}$

C_{in} is negative

G may be positive or negative

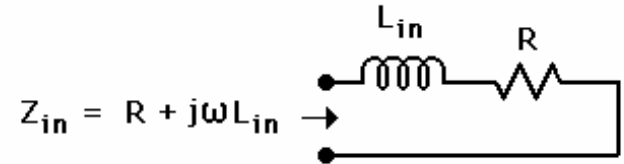Inductor modeled as an ideal L_{in} in series with a resistance R




Inductor Q: *magnitude* of $\frac{\omega L_{in}}{R}$

L_{in} is negative

R may be positive or negative

Linville OCS
Negative
Capacitor


$$C_{in} = -(R_1/R_2)C_L$$

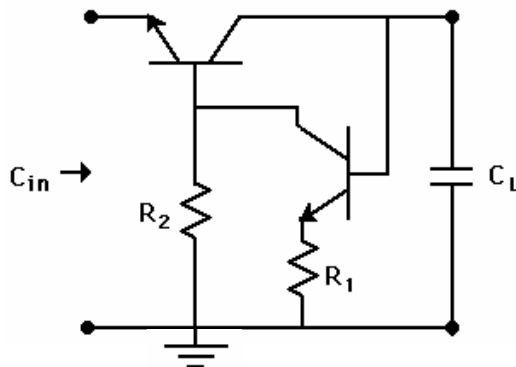

Linville SCS
Negative
Inductor


w/capacitive inversion

$$L_{in} = -R_1 R_2 C_L$$

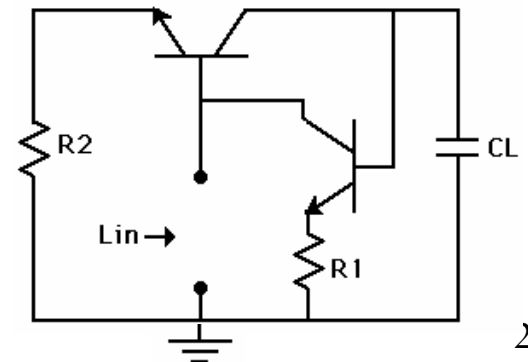


Experimental Results for Negative Capacitor


Capacitance C_{in}

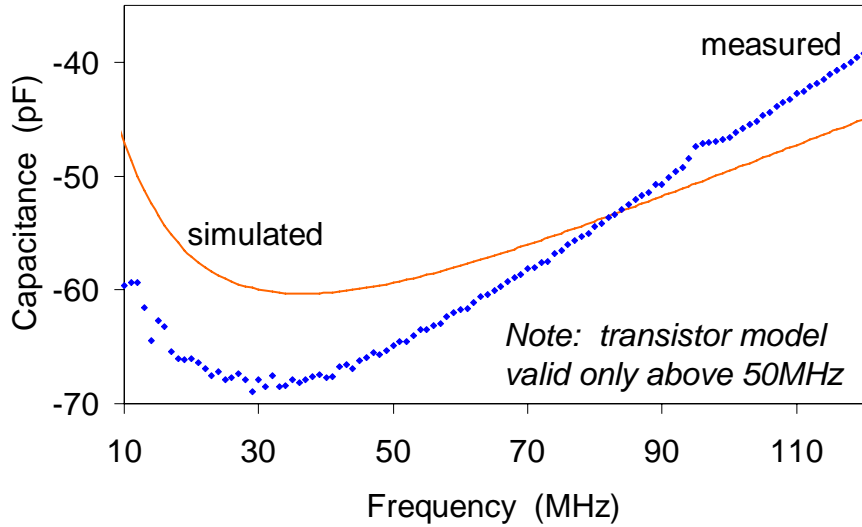


Q

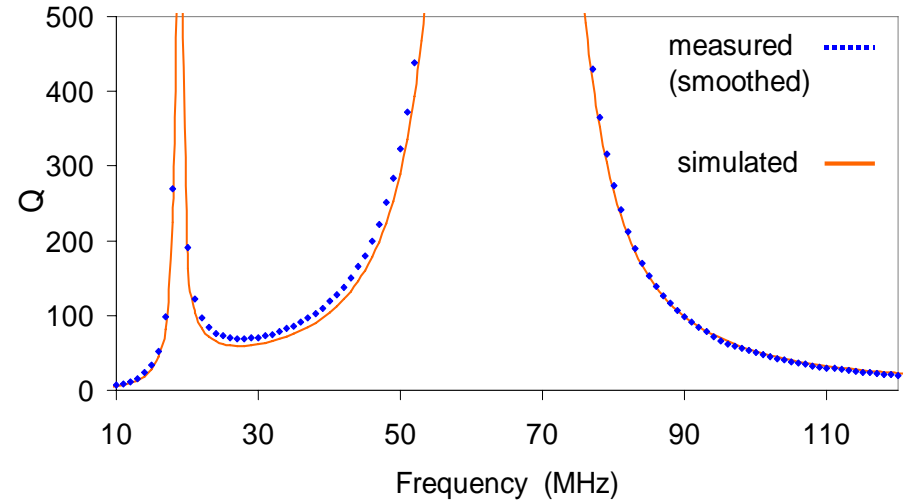





Conductance G

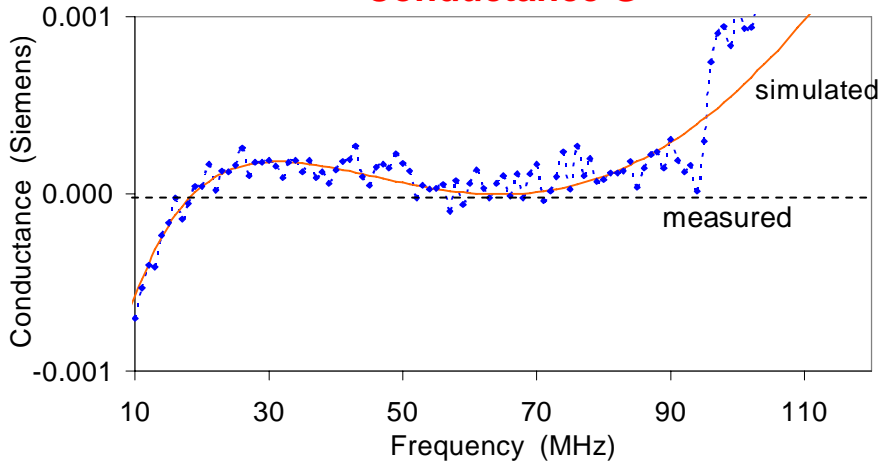


Spectrum Analyzer Meas. of Noise Power

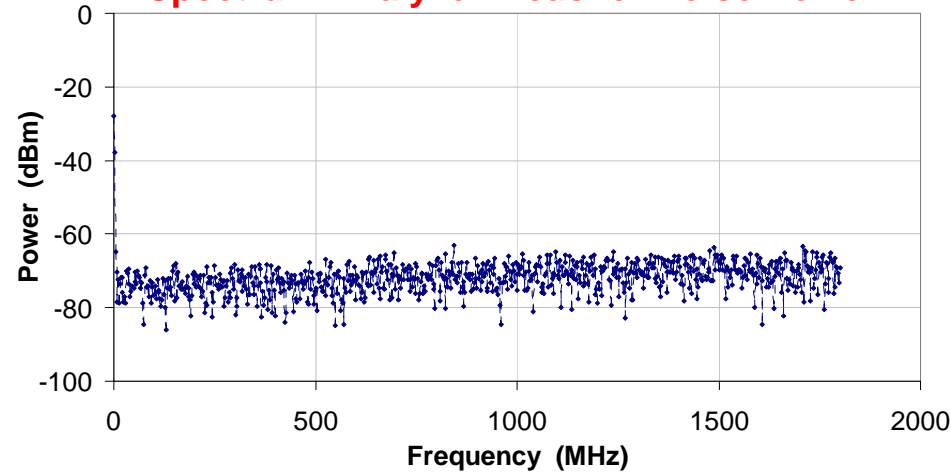

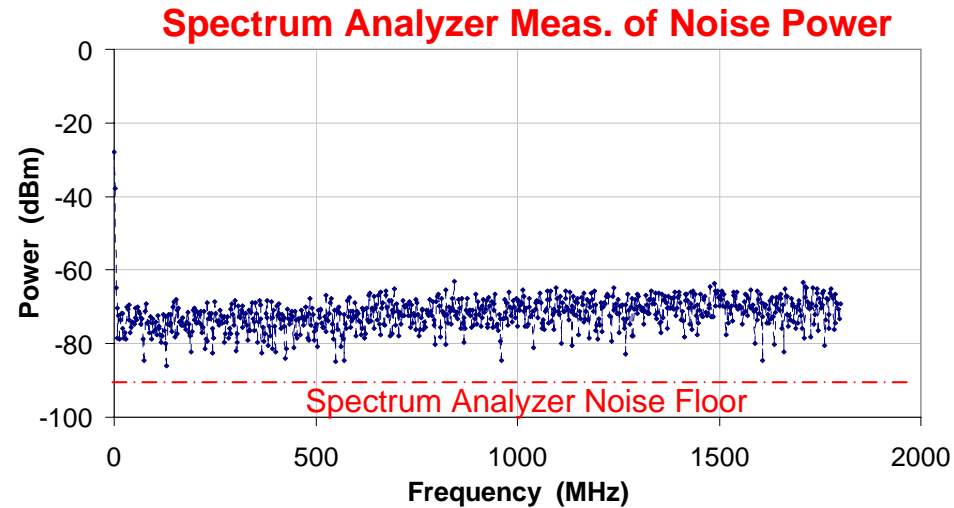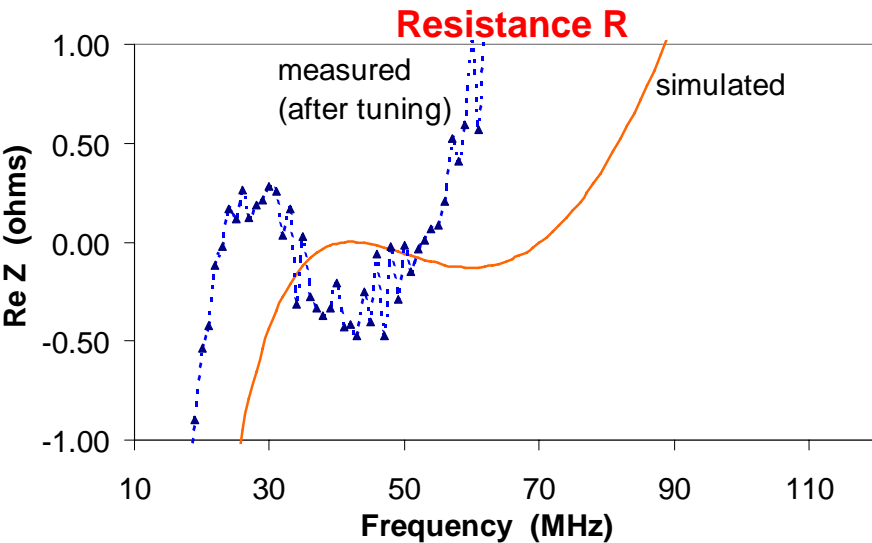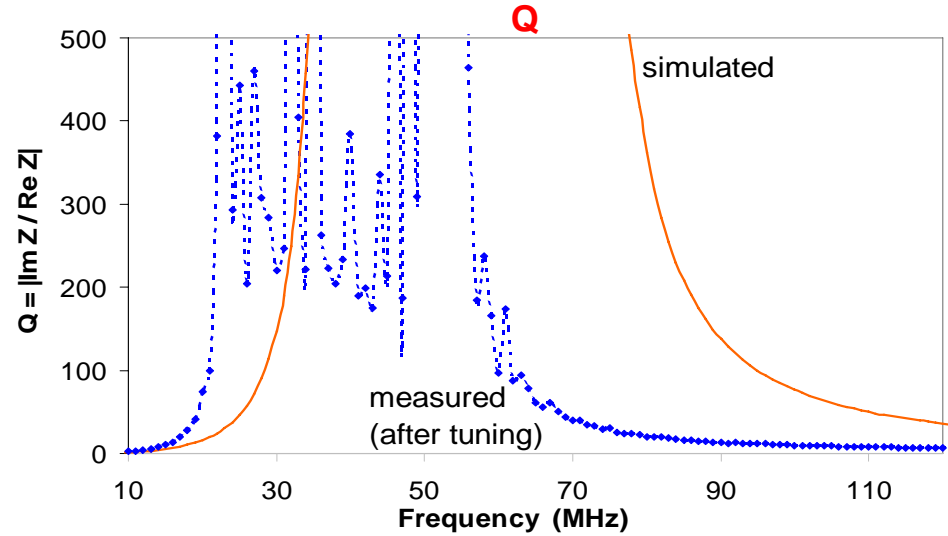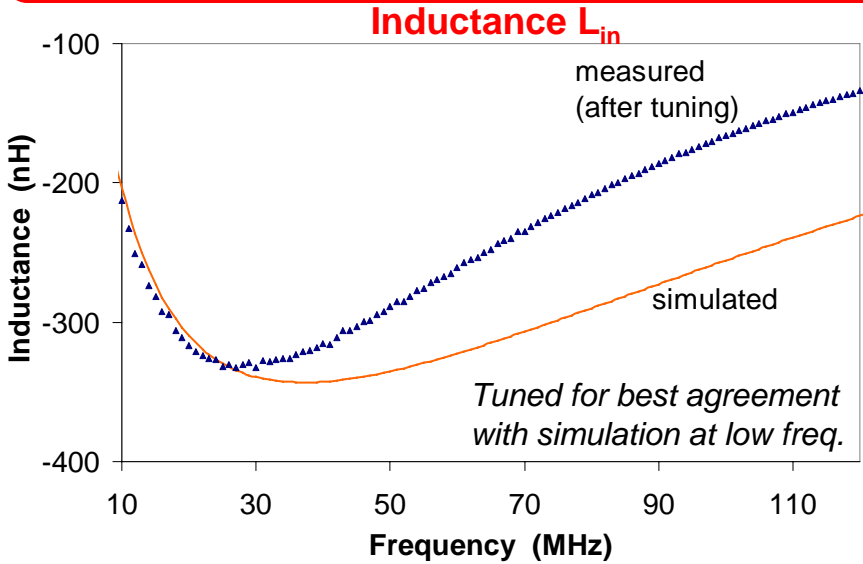
Experimental Results for Negative Inductor



Floating Negative Elements

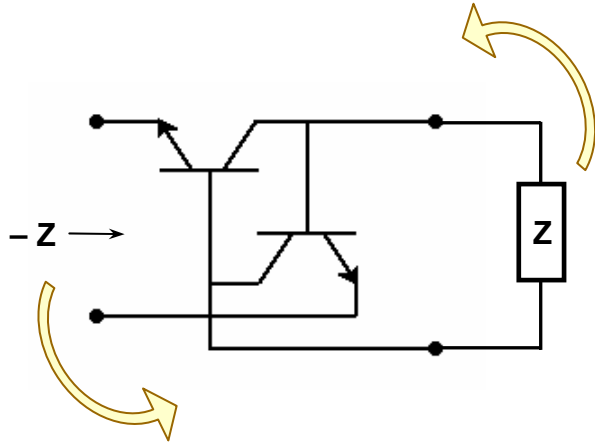

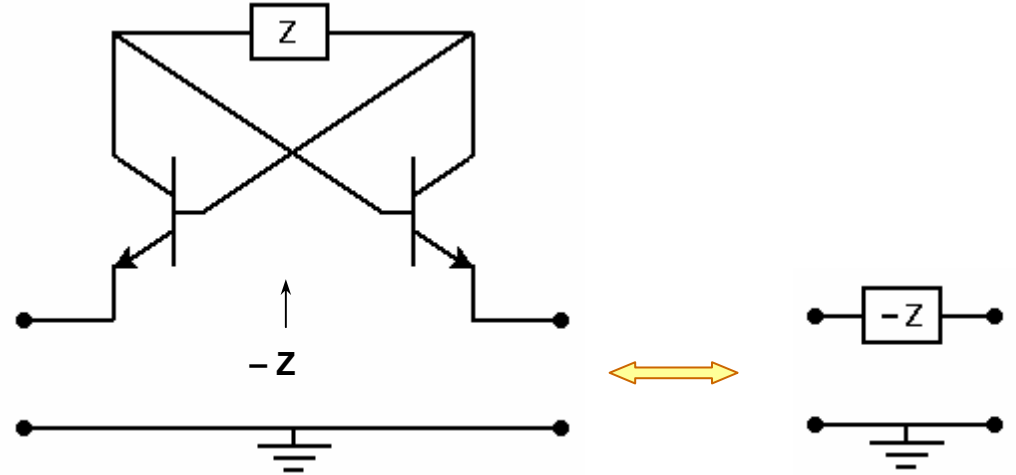Linvill Floating *Negative Impedance Converter*
Terminated in Z



Linvill Floating NIC Terminated in Z used as
Series Negative Element

Series negative *capacitor* used in impedance matching of electrically-short monopole and dipole

Laboratory Measurements: *Non-Foster Monopole and Dipole**


*work performed for US Army I2WD (CECOM)

Experimental demonstration of partial non-Foster impedance matching with a monopole antenna:


- Negative capacitor cancels the reactance of a electrically-short 6” monopole (partial matching)
- Measured improvement in signal-to-noise ratio with non-Foster-matched electrically-short monopole: up to **9 dB** at 30 MHz (as compared to lossy-matched blade antenna of *twice* the size; receiver NF 8 dB)

Measurement of Signal-to-Noise Ratio on the Antenna Range

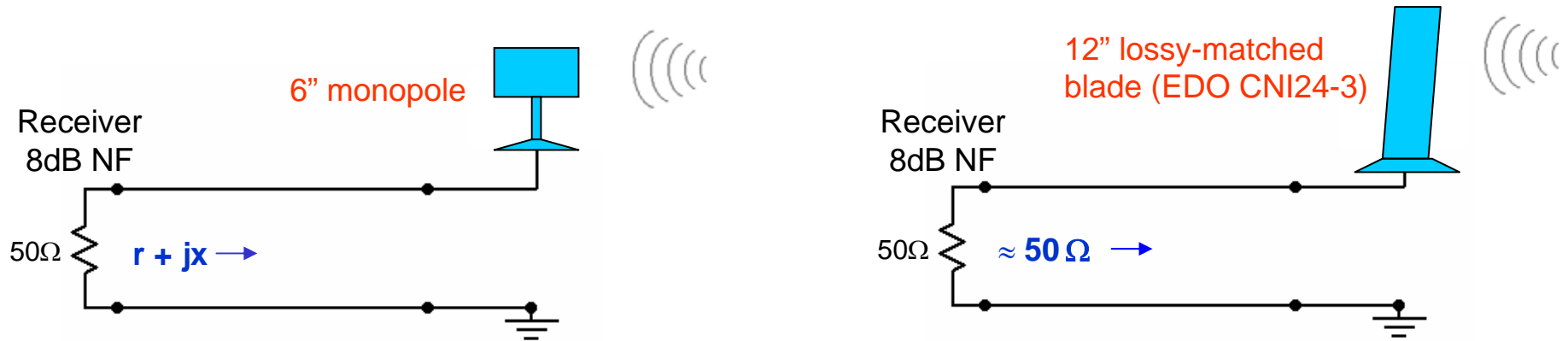6" and lossy 12" reference antennas: behaved almost identically




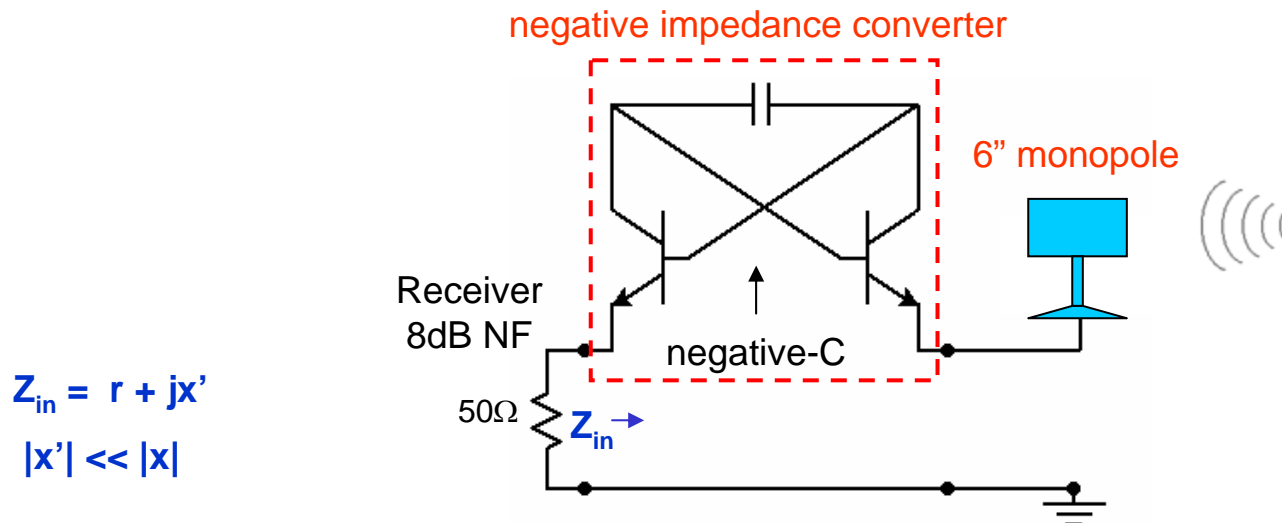6" monopole with non-Foster matching improves signal-to-noise ratio



Measured Improvement in Horizon Gain

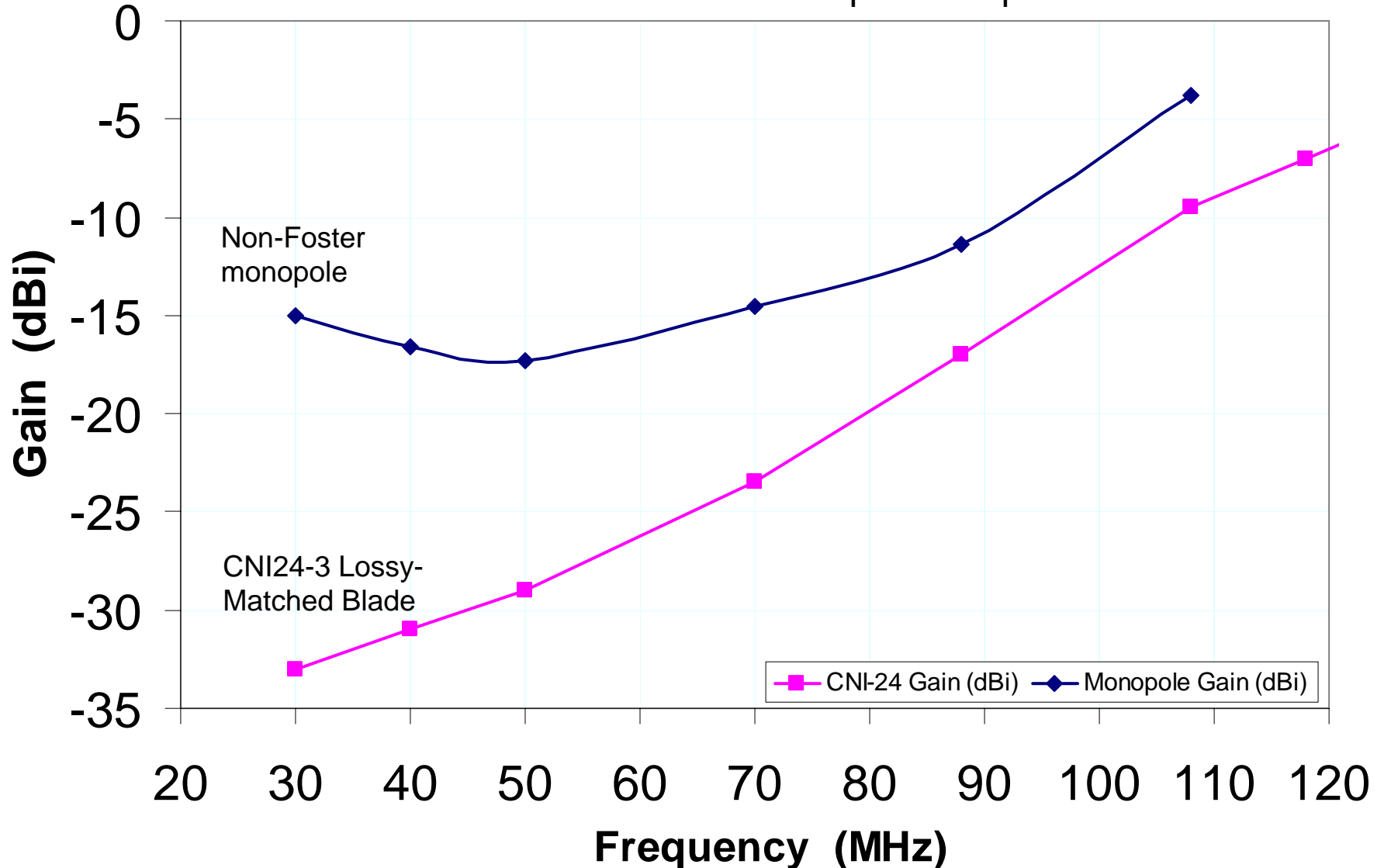
Horizon Gain: Non-Foster Monopole compared to CNI24-3



Measured Improvement in Signal-to-Noise Ratio

Low noise receiver: 8 dB noise figure

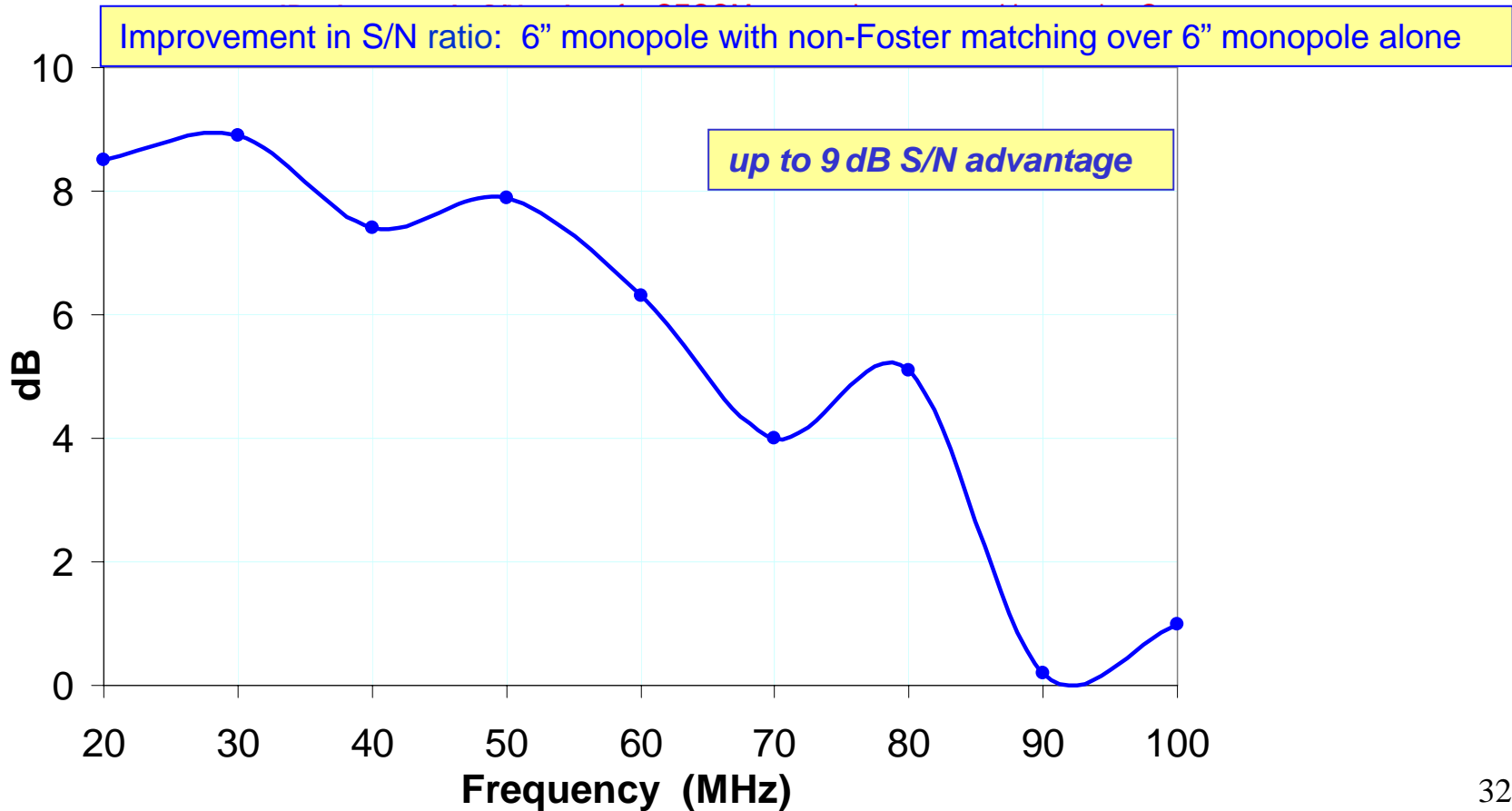Measurements taken at discrete 10 MHz intervals; Excel curve-fit produces plot




Experimental demonstration of partial non-Foster impedance matching with a dipole antenna:

- Negative capacitor cancels the large portion of reactance of an electrically-short dipole, 12” total length
- Measured improvement in signal-to-noise ratio with non-Foster-matched electrically-short dipole: up to **20 dB** (see graphs) as compared to 12” lossy-matched blade monopole antenna


Measurement of Signal-to-Noise Ratio on the Antenna Range

12" monopole reference antenna

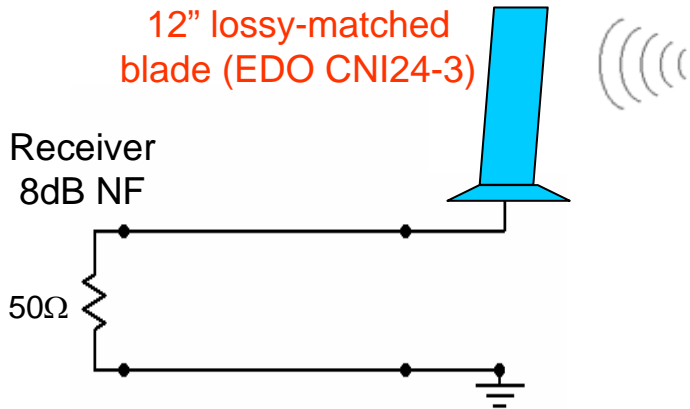12" dipole antenna (6" per arm) with non-Foster matching improves signal-to-noise ratio




Swept-frequency measurements

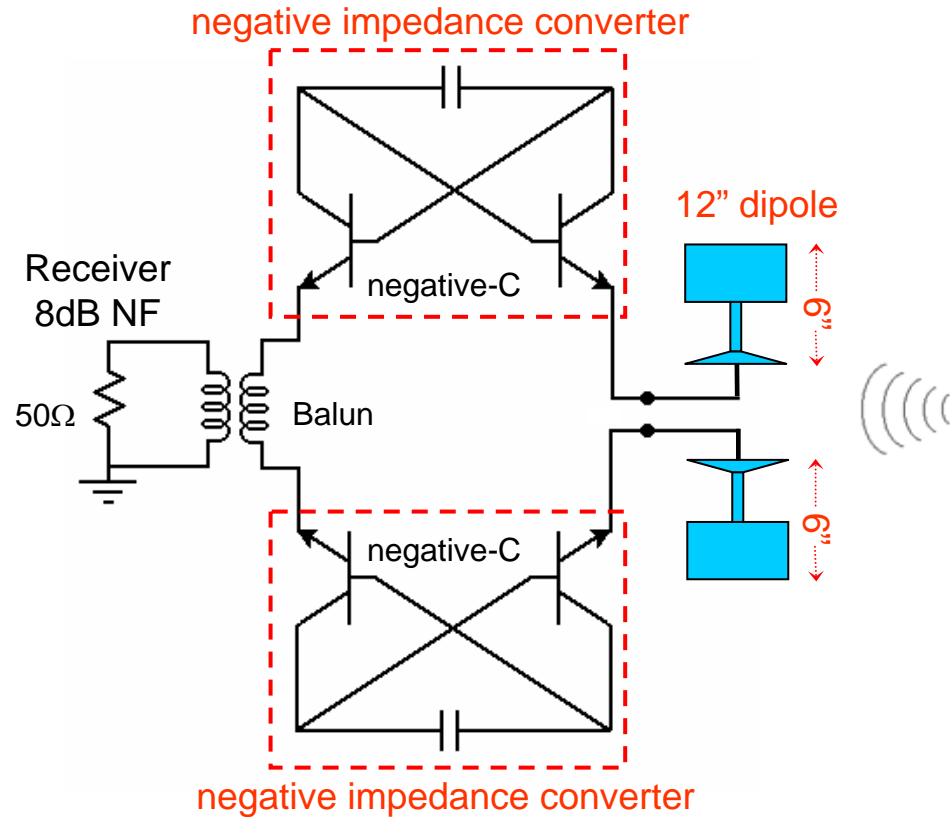


Measured Improvement in Horizon Gain

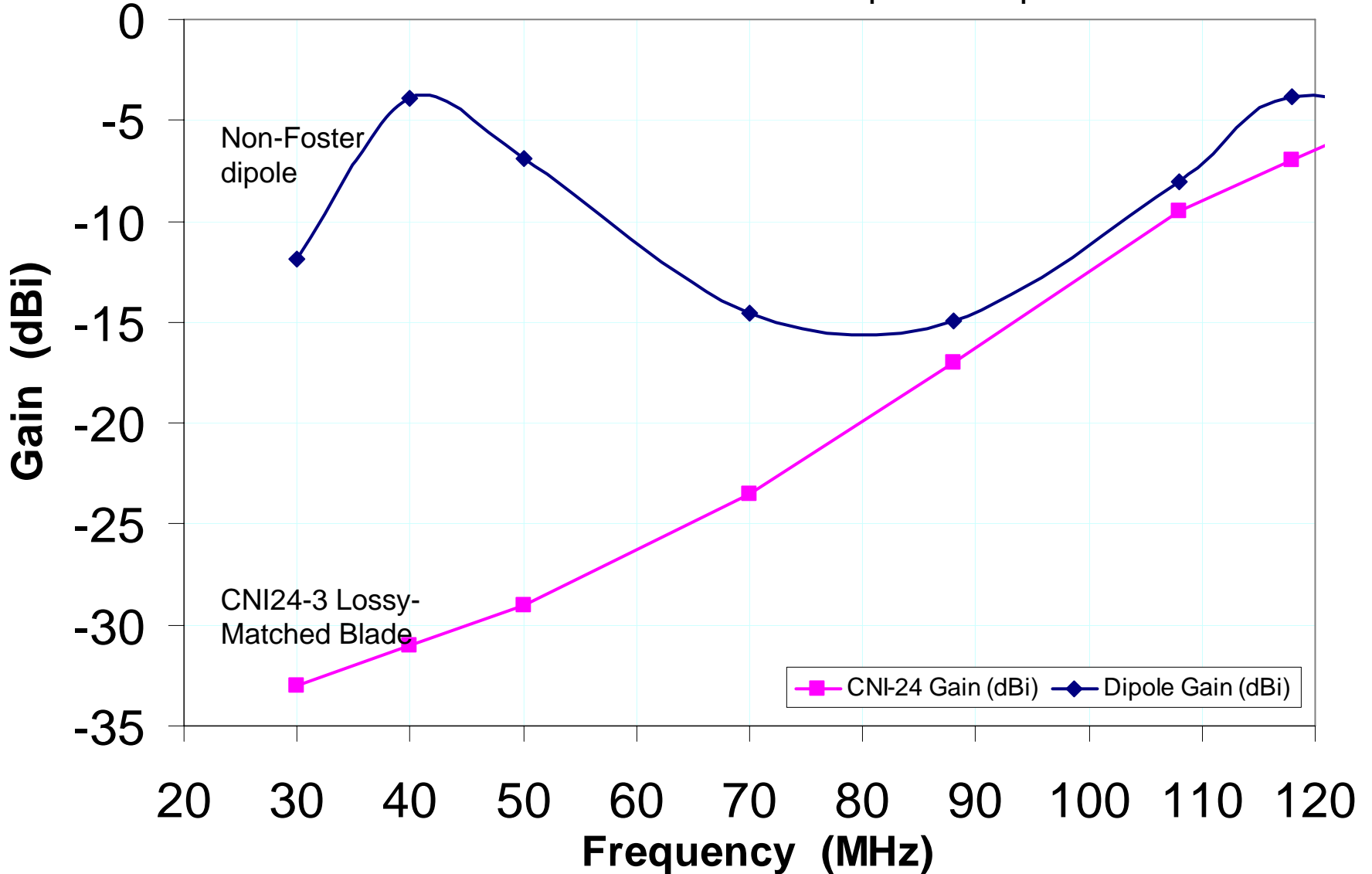
Horizon Gain: Non-Foster Dipole compared to CNI24-3



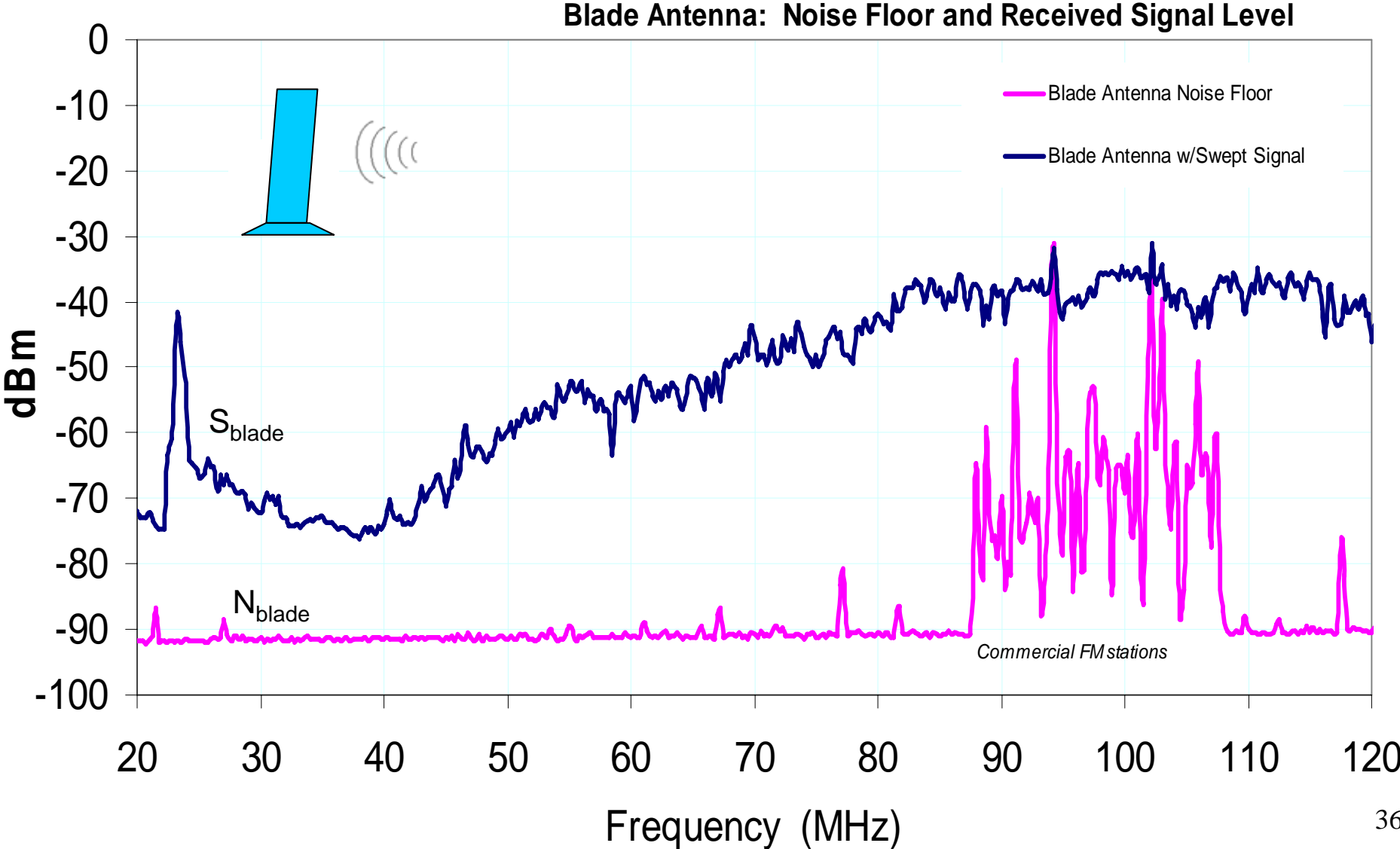
Blade Antenna: Noise Floor and Received Signal



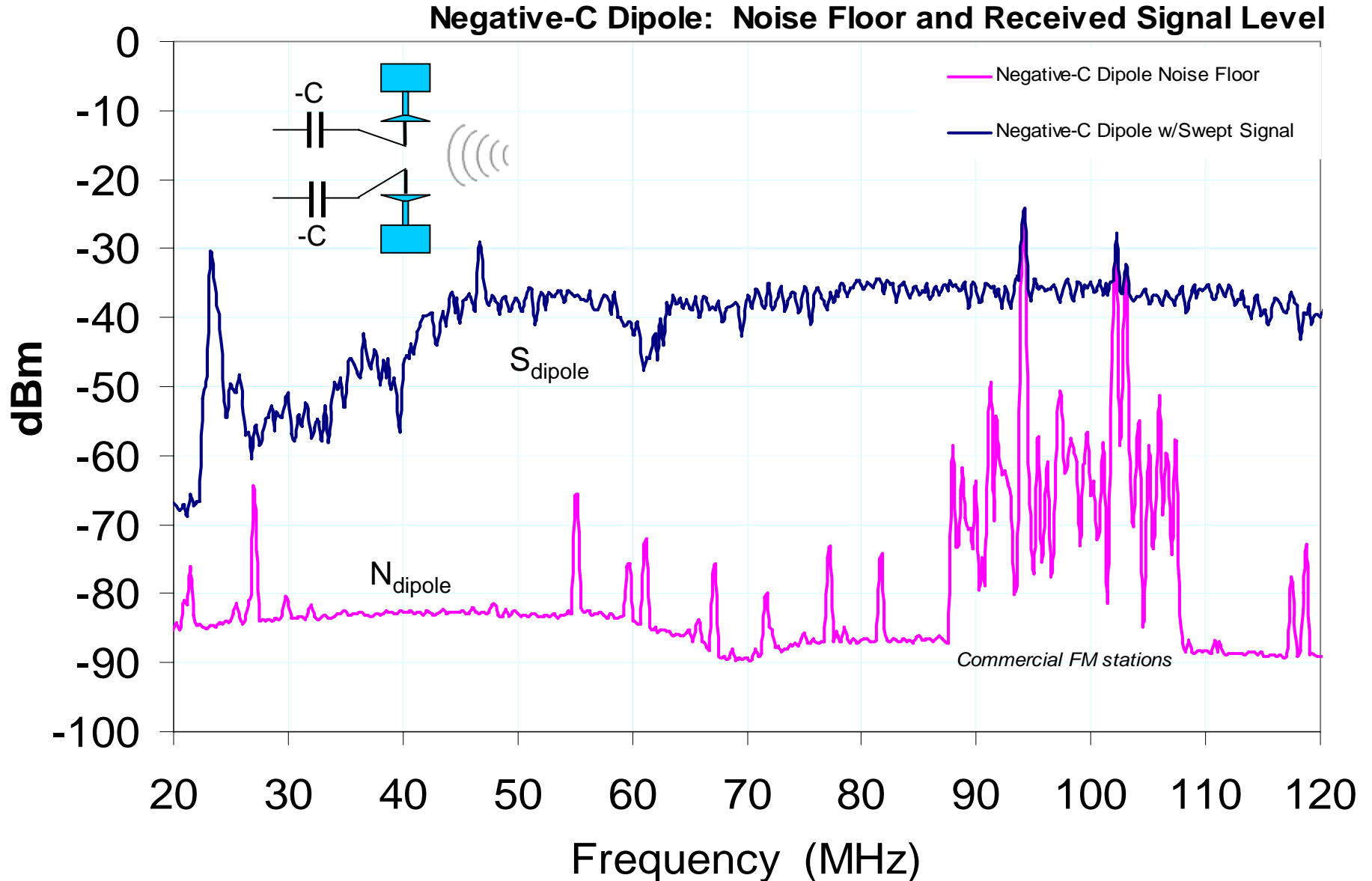Negative-C Dipole: Noise Floor and Received Signal




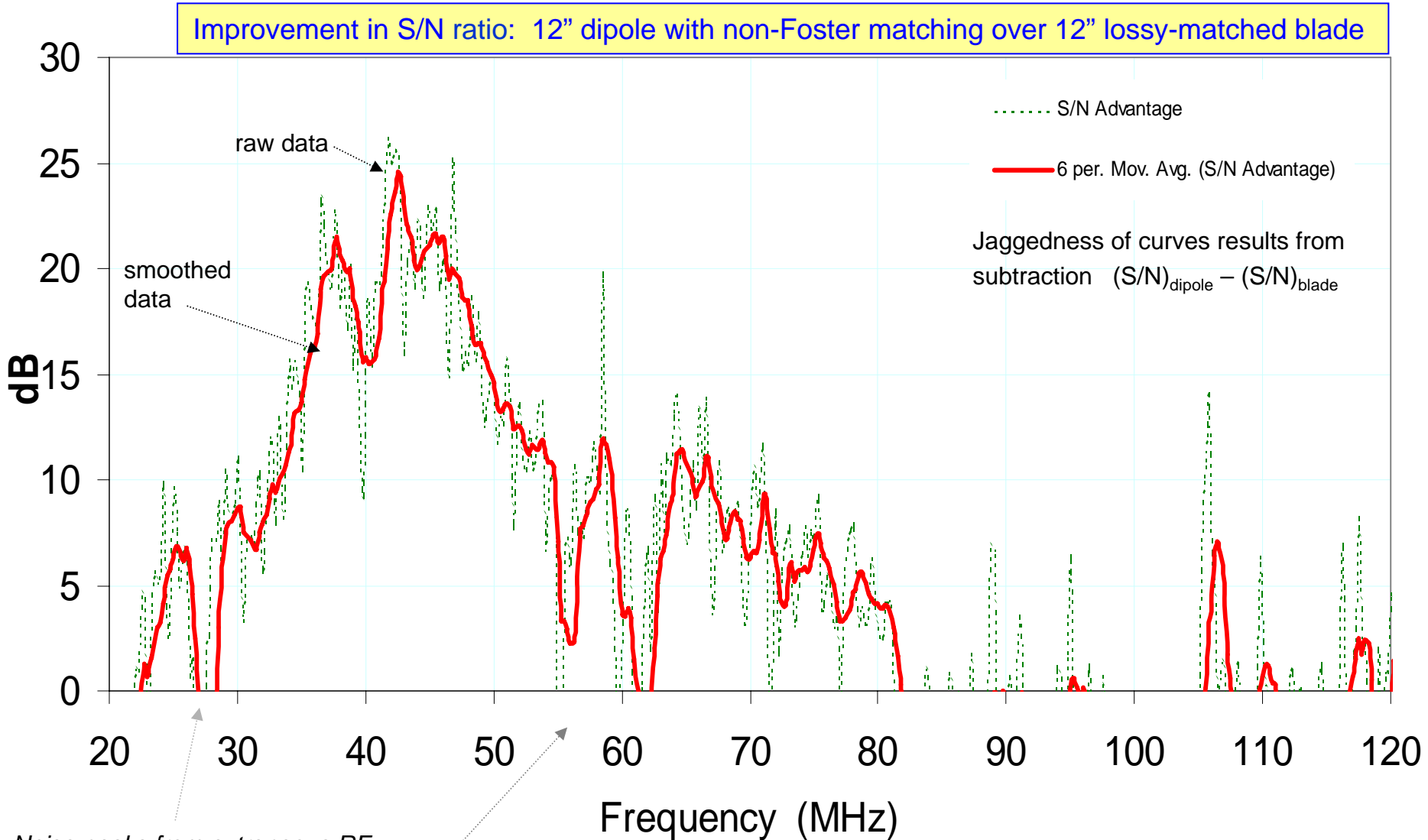Signal-to-Noise Advantage, 12" Negative-C Dipole over 12" Lossy-Matched Blade Monopole Antenna




Noise peaks from extraneous RF sources cause loss of S/N advantage

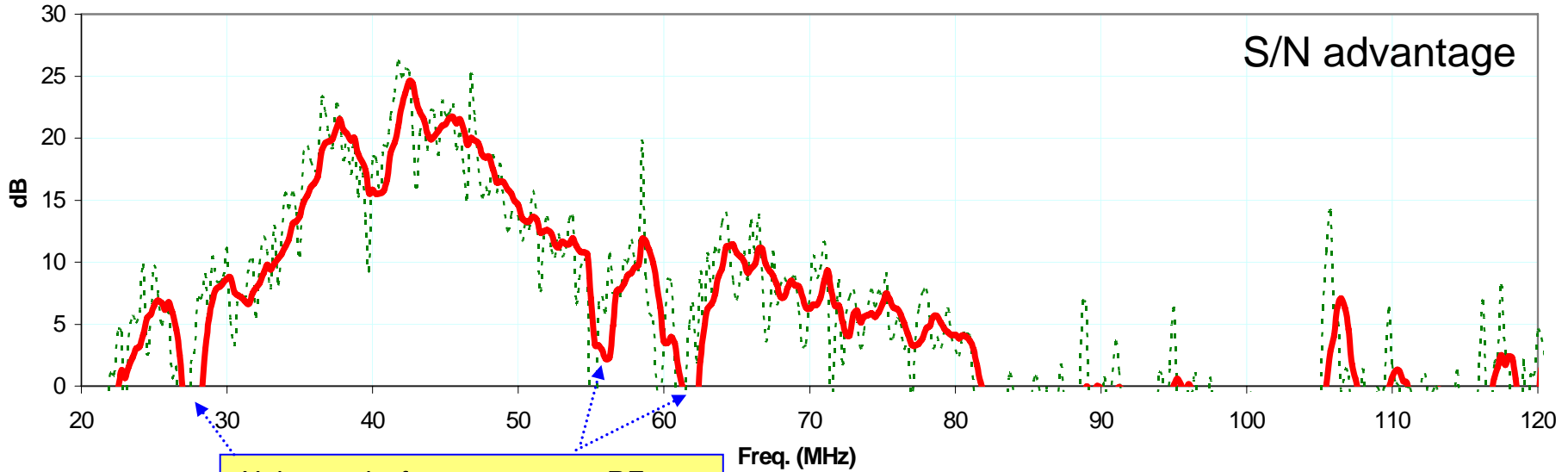No S/N Advantage When External Noise Dominates



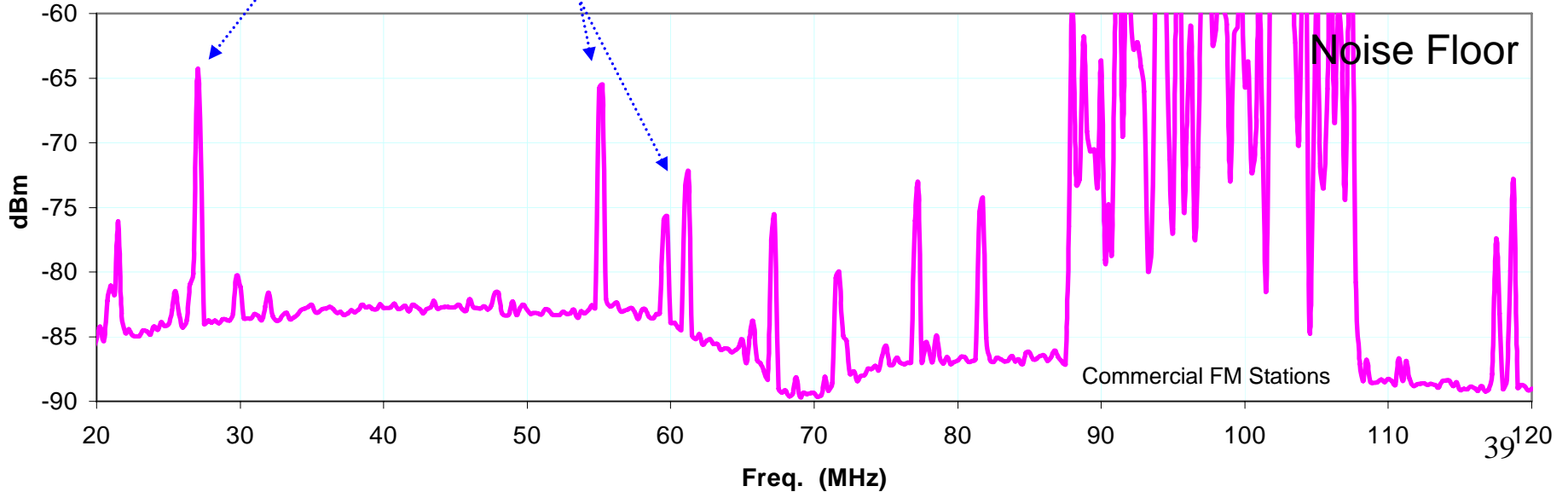
Noise peaks from extraneous RF sources cause loss of S/N advantage



CECOM Dipole on Test Range




Side view

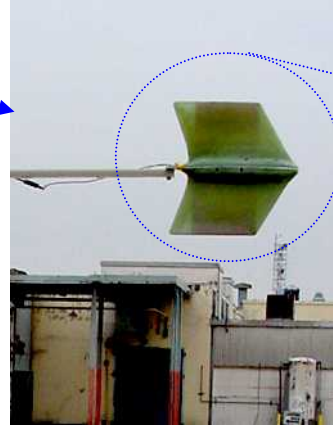


Head-on
view

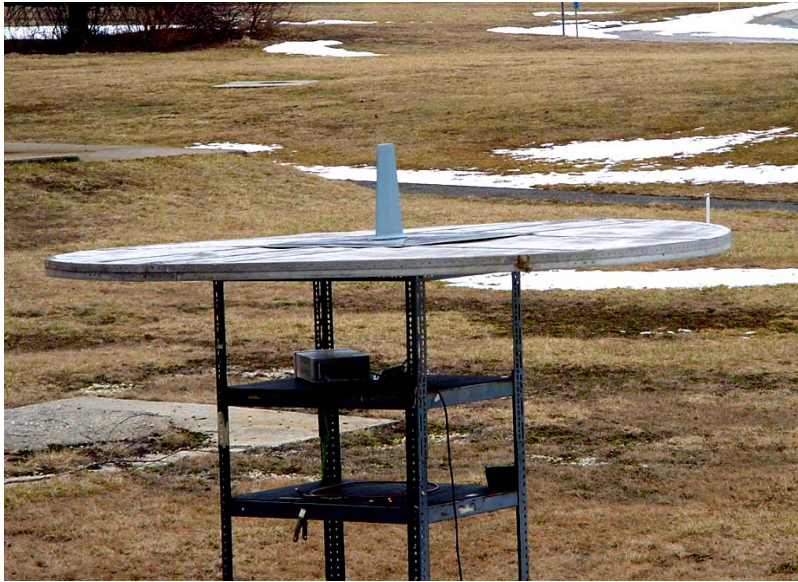CECOM Dipole Compared to CNI-24 Monopole Blade on 8 ft. Ground Plane



Blade on ground plane

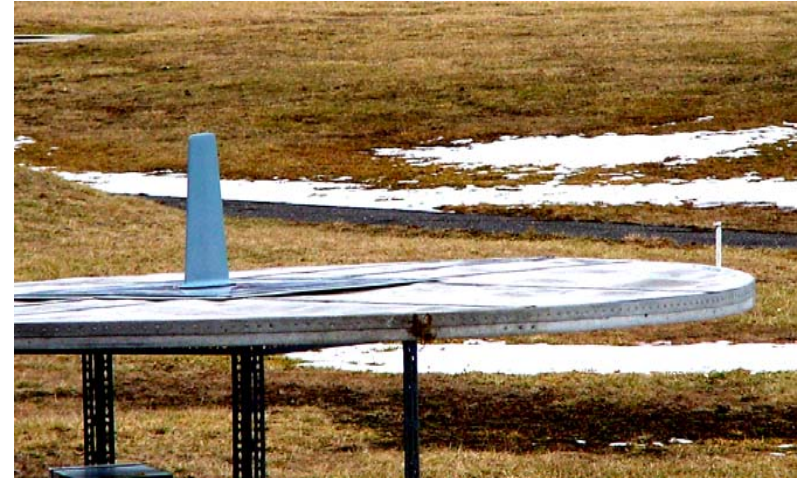

Technology Development

1. Investigate using additional negative elements in a non-Foster matching circuits
2. Determine the optimal tradeoff among the design parameters to obtain the largest improvement in signal-to-noise ratio over the broadest bandwidth
3. Develop additional types of negative circuit elements, especially negative inductors for electrically-small loop and flush cavity antennas
4. Acquire or develop accurate device models to design low-noise FET NICs
5. Auto-tuning / self-adjusting circuitry
6. Investigate alternative matching network topologies – *NIC bracketing vs. individual negation of elements*
7. Transmit applications – a special problem