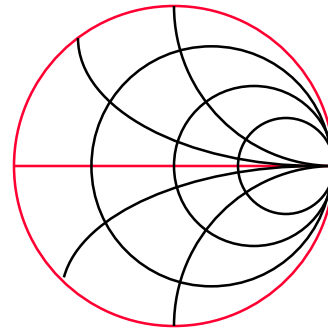


Smith Charts



Phillip H. Smith


1905 - 1987



Frank A. Lynch
W4FAL

| NAME | TITLE | COLL. NO. |
|------------------------|--|-----------|
| SMITH CHART FORM 12-71 | COLDR BY J. COLDR, UNIVERSITY OF FLORIDA, '80' | DATE |

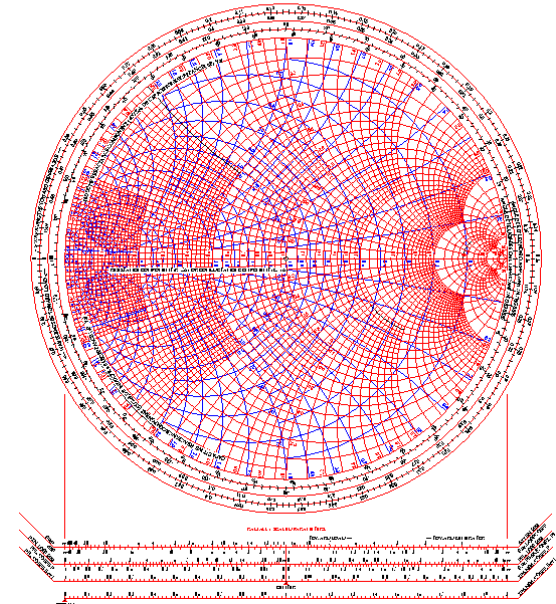NORMALIZED IMPEDANCE AND ADMITTANCE COORDINATES



Smith Chart History

- Invented by Phillip H. Smith in 1939
- Used to solve a variety of transmission line and waveguide problems

Basic Uses

For evaluating the rectangular components, or the magnitude and phase of an input impedance or admittance, voltage, current, and related transmission functions at all points along a transmission line, including:

- Complex voltage and current reflections coefficients
- Complex voltage and current transmission coefficients
- Power reflection and transmission coefficients
- Reflection Loss
- Return Loss
- Standing Wave Loss Factor
- Maximum and minimum of voltage and current, and SWR
- Shape, position, and phase distribution along voltage and current standing waves

Basic Uses (continued)

For evaluating the effects of line attenuation on each of the previously mentioned parameters and on related transmission line functions at all positions along the line.

For evaluating input-output transfer functions.

Specific Uses

- Evaluating input reactance or susceptance of open and shorted stubs.
- Evaluating effects of shunt and series impedances on the impedance of a transmission line.
- For displaying and evaluating the input impedance characteristics of resonant and anti-resonant stubs including the bandwidth and Q.
- Designing impedance matching networks using single or multiple open or shorted stubs.
- Designing impedance matching networks using quarter wave line sections.
- Designing impedance matching networks using lumped L-C components.
- For displaying complex impedances verses frequency.
- For displaying s-parameters of a network verses frequency.

The Formula!

$$Z_x = Z_0 \frac{Z_L + Z_0 \tanh \gamma x}{Z_0 + Z_L \tanh \gamma x}$$

$$\gamma = \alpha + j\beta$$

This is why the chart was developed.. Before calculators and computers the above formula's were impossible! They're still not easy today.

The Smith Chart

$$Z = R \pm j X$$


Impedance

The chart is normalized (Z_n) so that any characteristic impedance (Z_0) can be used.

$$Z_n = \frac{R}{Z_0} \pm j \frac{X}{Z_0}$$


$$Y = G \pm j B$$

Admittance

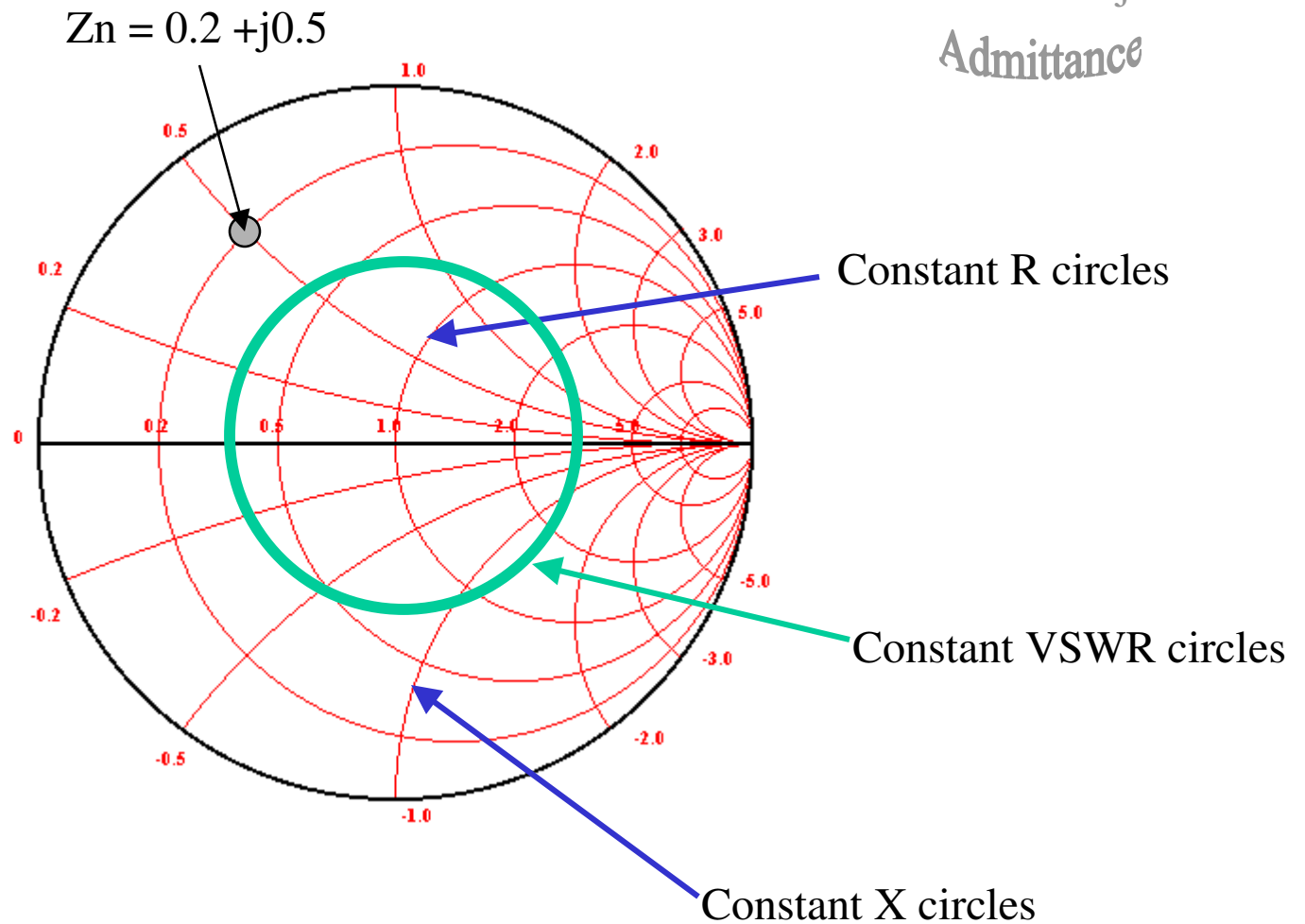

Building the Smith Chart


Start with circle of radius U .

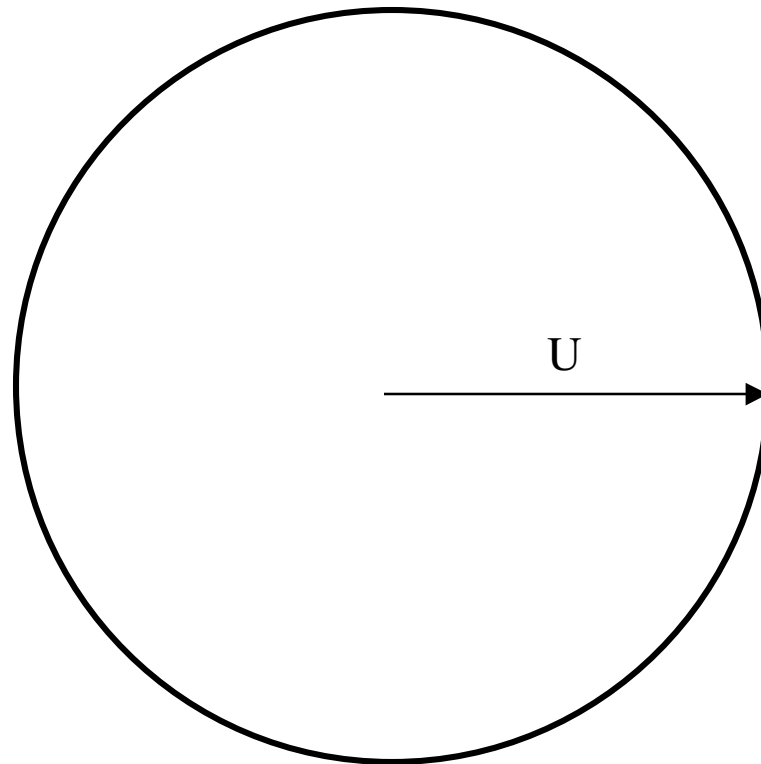

This forms the outer boundary of the Smith Chart. It is in fact the $R = 0$ constant resistance circle.

Building the Smith Chart

Now add the $X = 0$ axis.

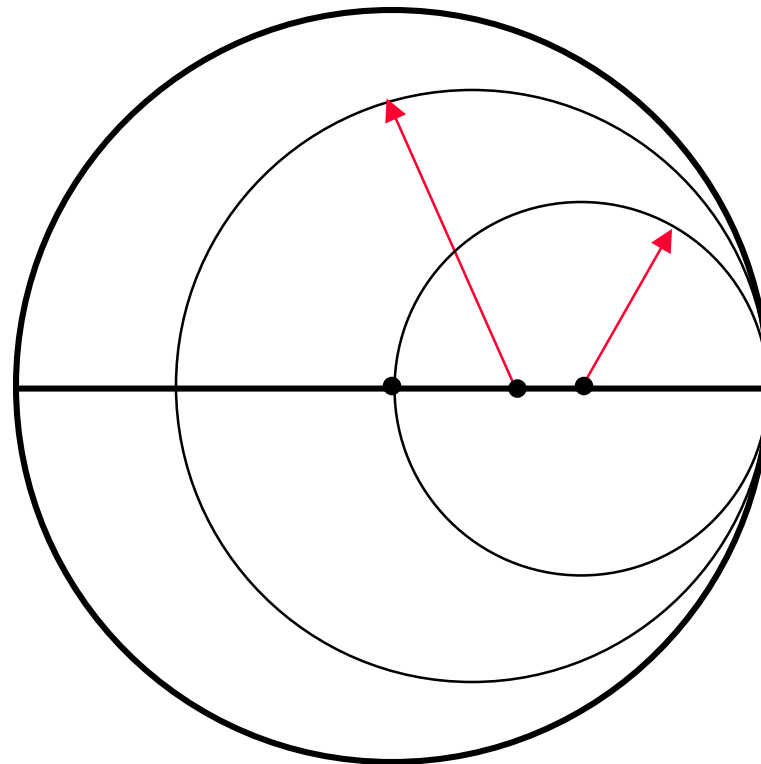

Then start adding constant resistance circles. All circles pass through the $R = \text{infinity}$ point and have a radius of:


$$\frac{1}{1 + \frac{R}{Z_0}}$$

Building the Smith Chart


Now add constant reactance circles

The radius of each of these circles is:


$$\frac{1}{\frac{X}{Z_0}}$$

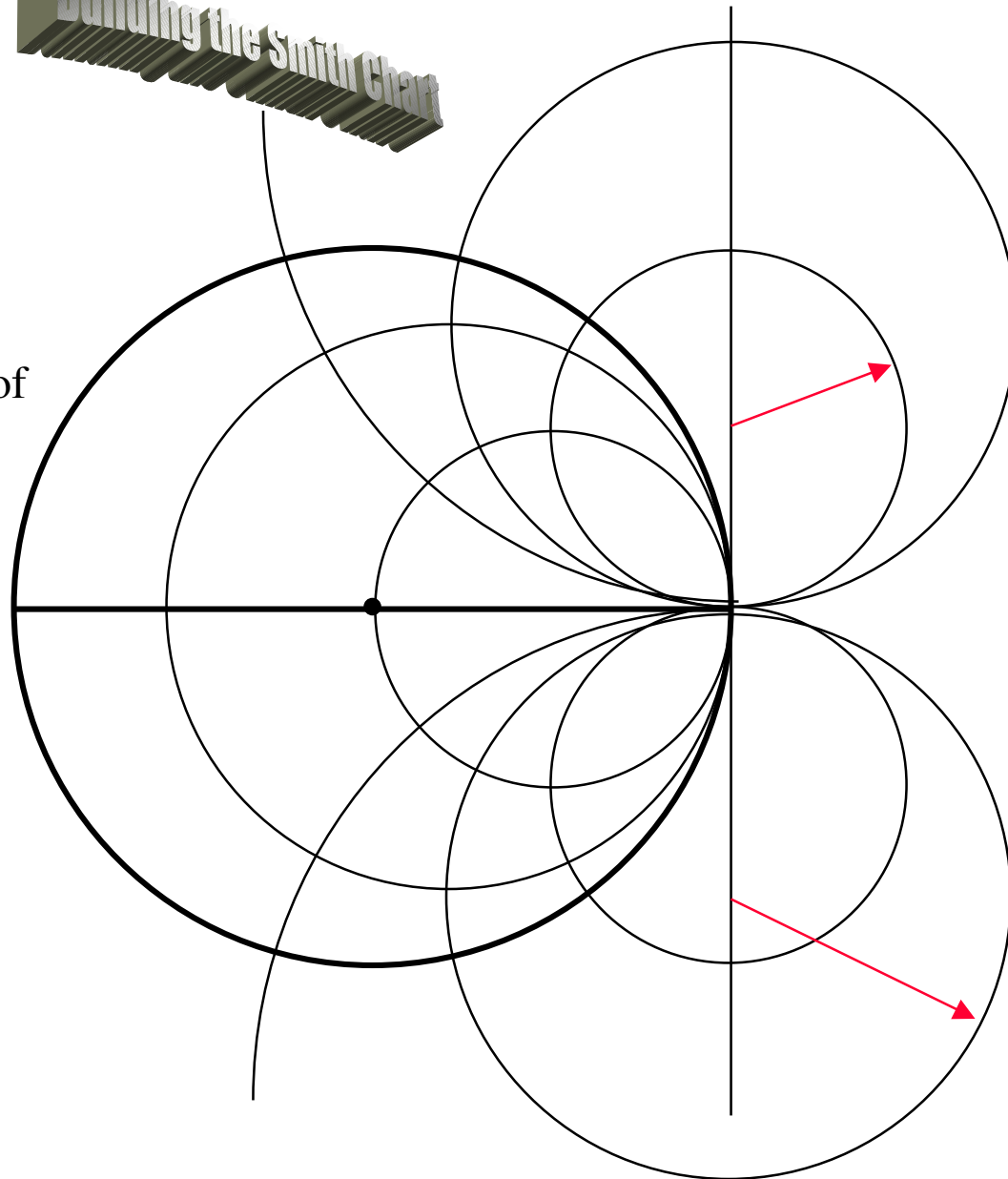

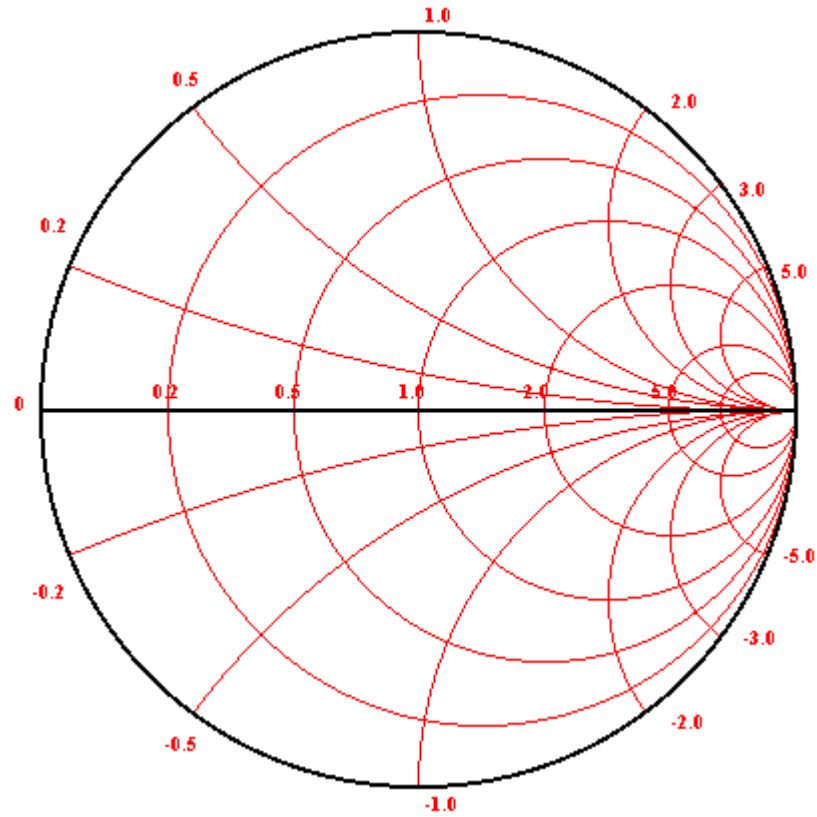When it's complete we have something that looks like this



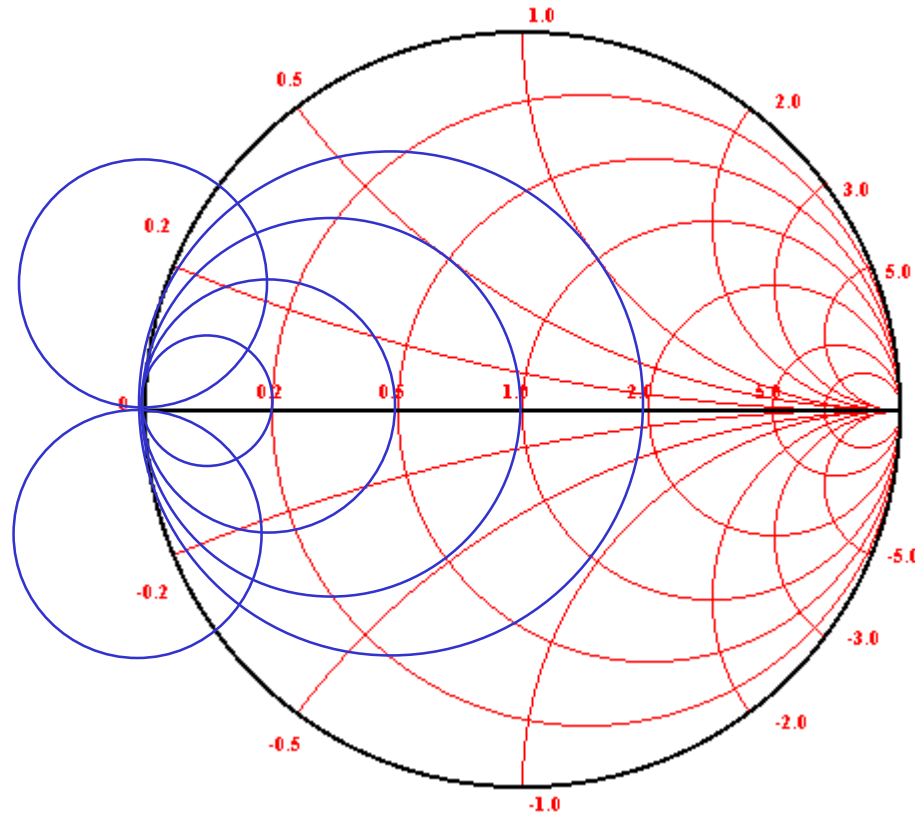
There's also a mirror image of the chart that instead of having constant resistance circles, and constant reactance curves, has instead constant conductance circles and constant susceptance curves.



| NAME | TITLE | DWG. NO. |
|--------------------------|---|----------|
| SMITH CHART FORM CY-6-41 | COLOR BY J. COLVIN, UNIVERSITY OF FLORIDA, 1967 | DATE |

The official version!

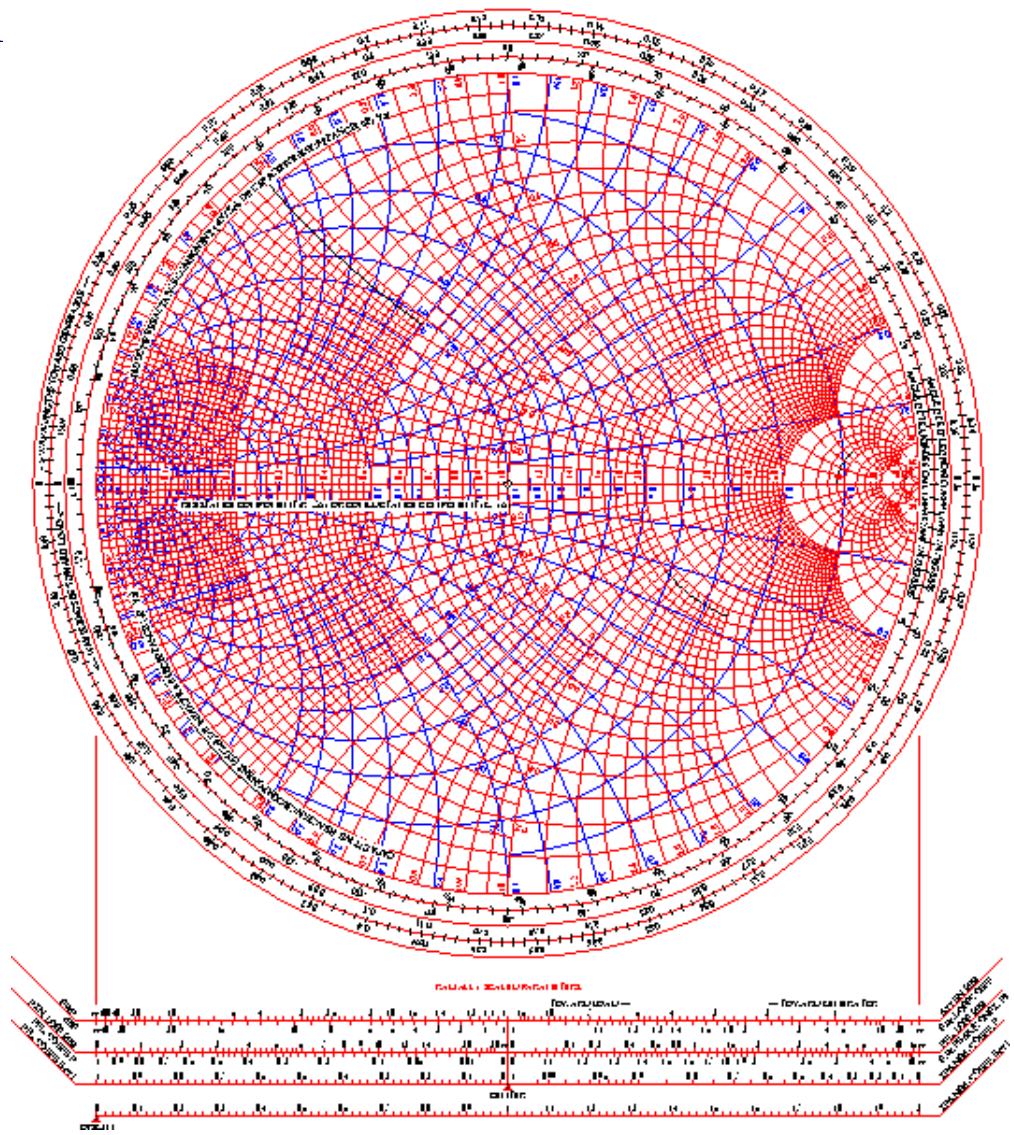NORMALIZED IMPEDANCE AND ADMITTANCE COORDINATES




Using the Smith Chart to solve impedance matching problems

The Smith Chart can be used to design a lumped (L-C) matching network to match one impedance to another.

Each LC element behaves in a certain way on the chart


Typical LC elements include:

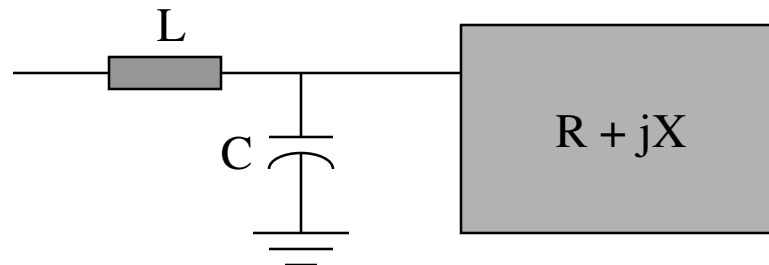- Series Inductors
- Series Capacitors
- Shunt Inductors
- Shunt Capacitors




Series Inductors

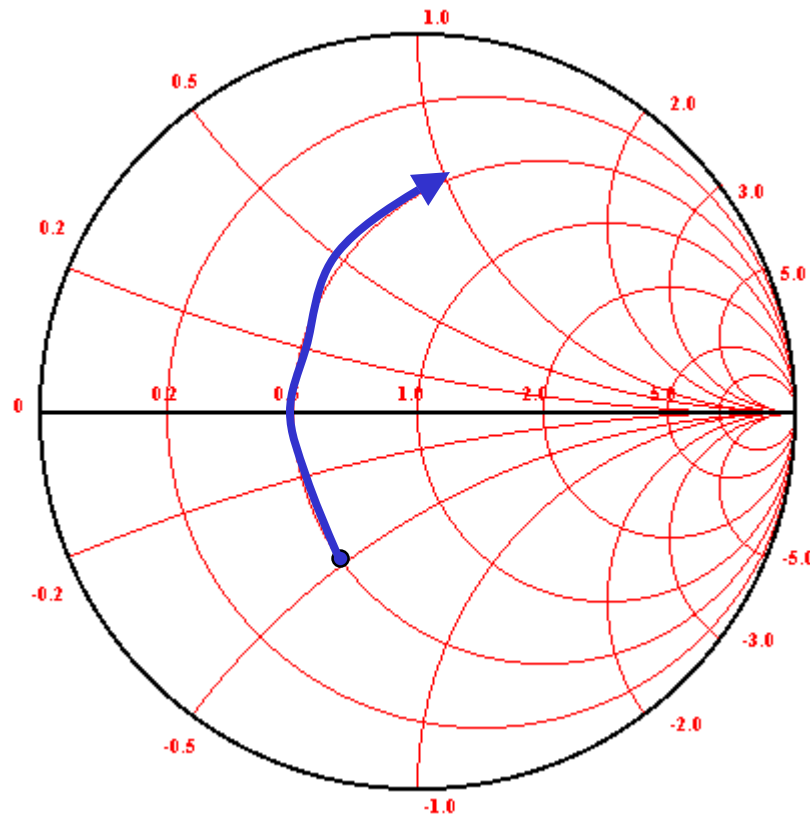Moves clockwise along circles of constant **resistance**




Series Capacitors

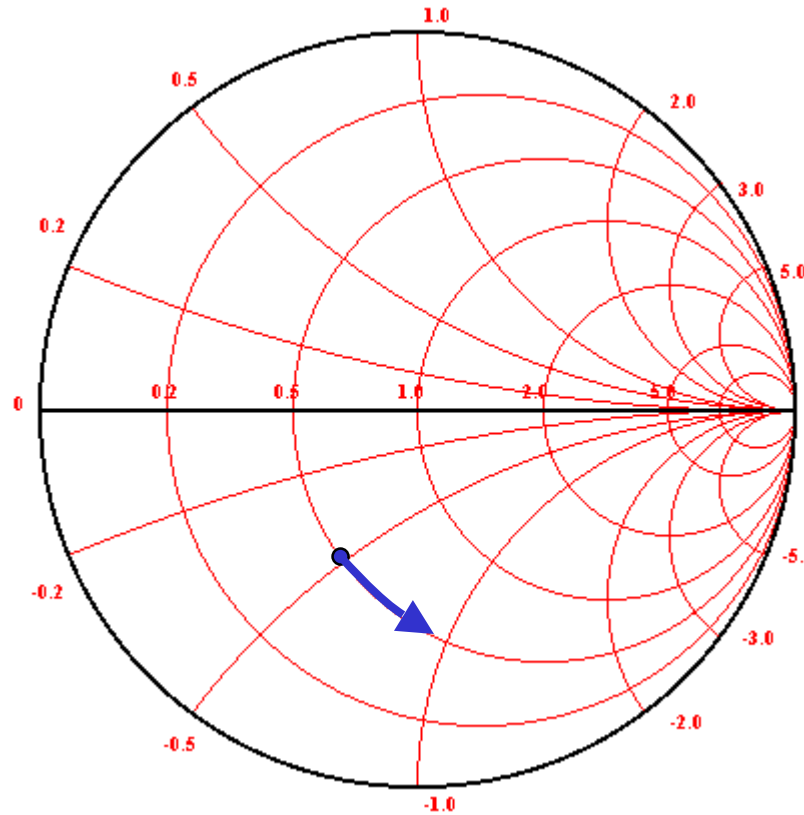Moves counter-clockwise along circles of constant resistance




Shunt Inductors

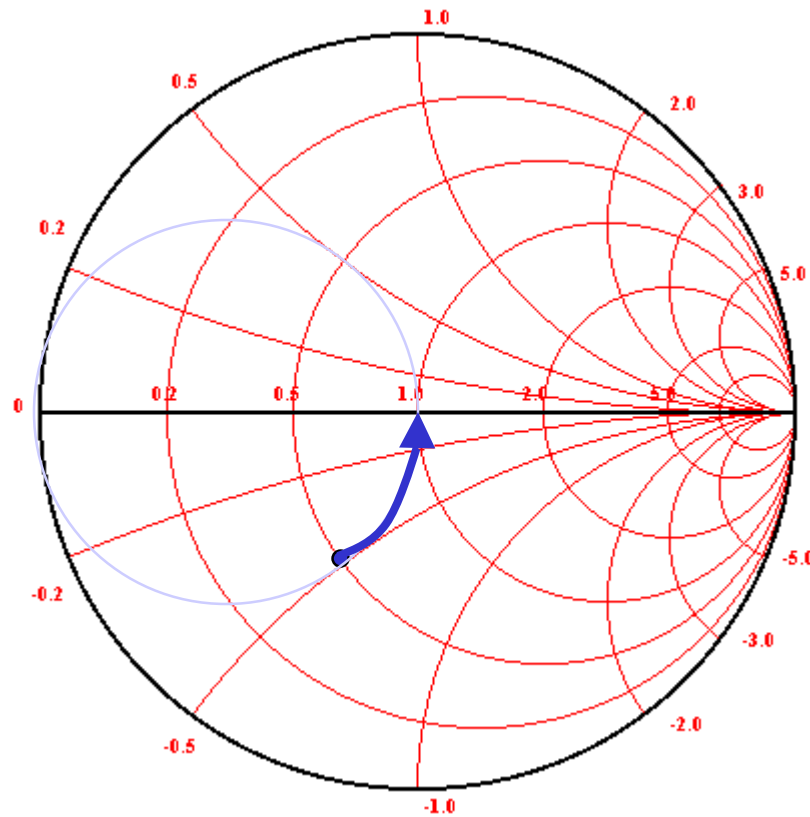Moves counter-clockwise along circles of constant conductance



Shunt Capacitors

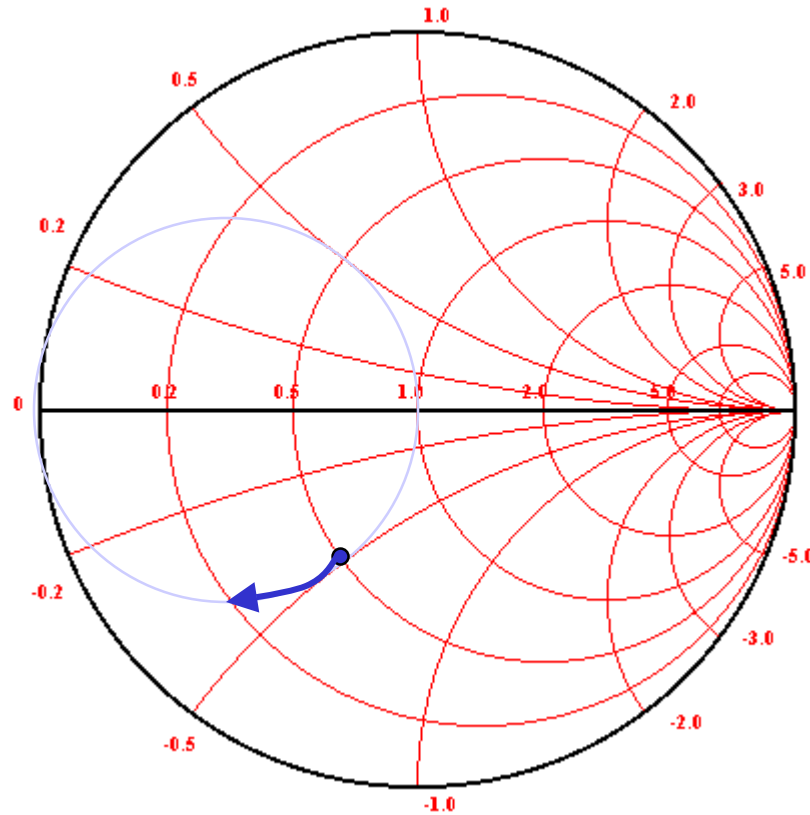Moves clockwise along circles of constant **conductance**



How do I calculate physical values of
Inductance and Capacitance from normalized values on the chart

Series L $+jX_{\text{norm}} = (2\pi fL)/Z_0$

Series C $-jX_{\text{norm}} = 1/2\pi fCZ_0$

Series R $R_{\text{norm}} = R/Z_0$


Parallel L $-jB_{\text{norm}} = Z_0/(2\pi fL)$

Parallel C $+jB_{\text{norm}} = 2\pi fCZ_0$

Parallel R $G_{\text{norm}} = Z_0/R$

Since I know what Z_0 is,
and I know what the frequency is,
I can solve for real values of R, C,
and L.

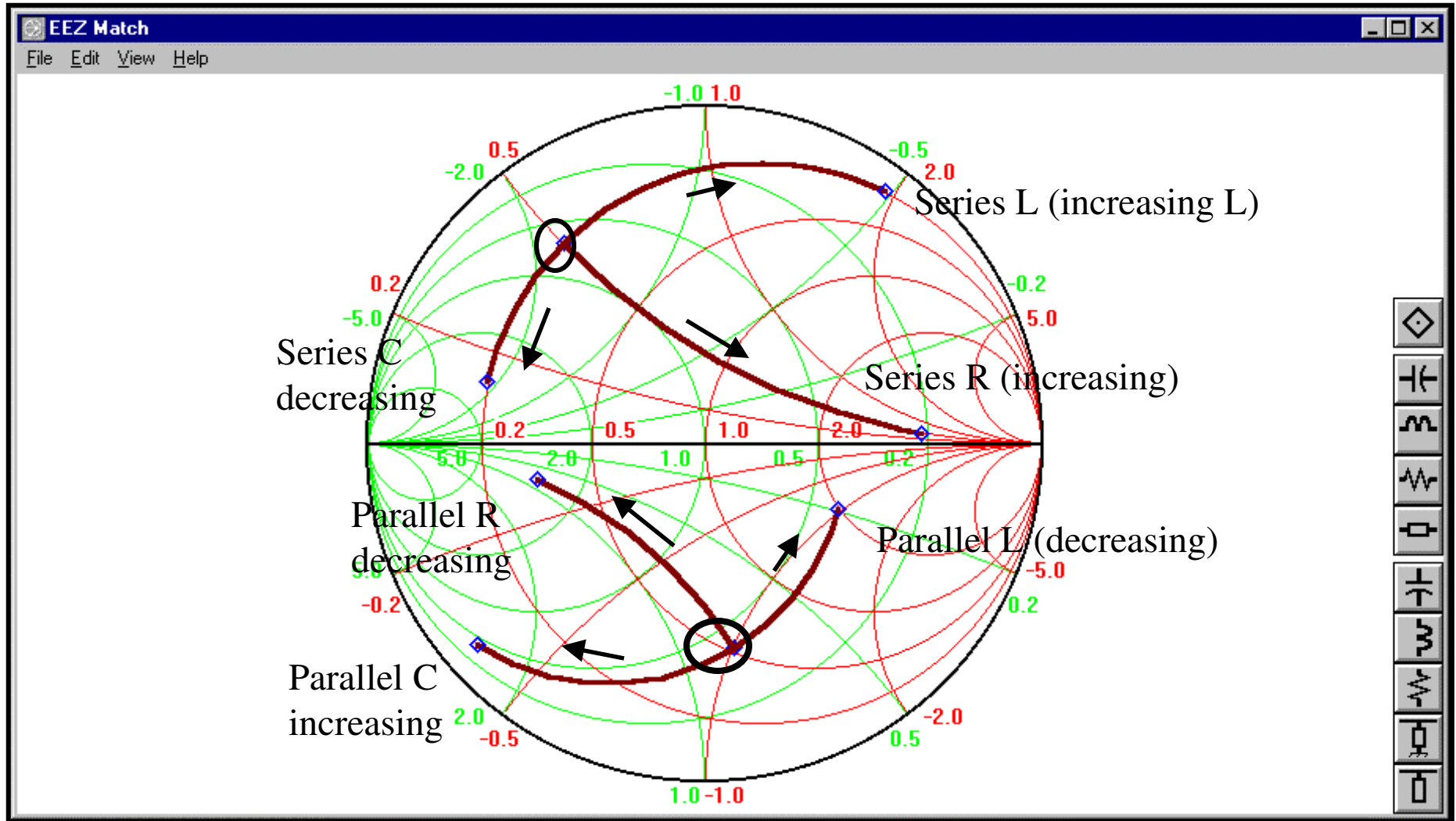
What Components do on the Smith Chart....



Remember that all values on the chart are NORMALIZED to Z_0 !
Component values on the chart will be Reactances or Susceptances,
the actual values must be computed based on the Freq and Z_0 ...

Example: Find X_1 and X_2 to match to 50 ohms

Freq = 28 MHz

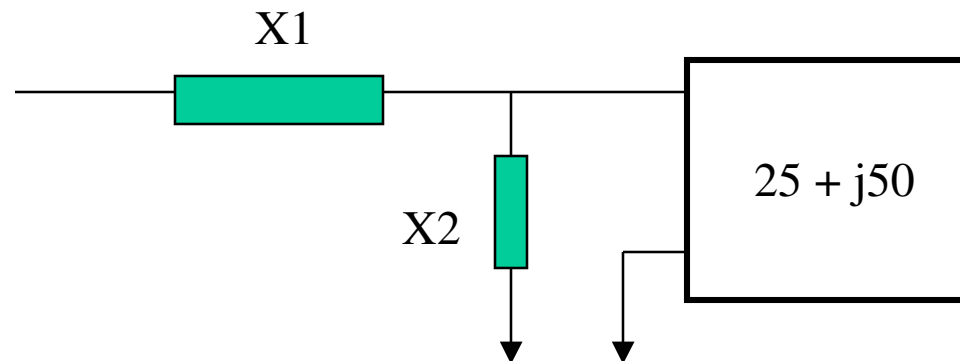

Let's do some matching with L's and C's



Pick Z_0 (50 Ohms sounds OK...)

Frequency is 28 MHz


The shunt Cap, transforms the R part of the Z to 1 (on the unit R circle..) from there a simple series C will take out the inductive reactance..

Easy as π

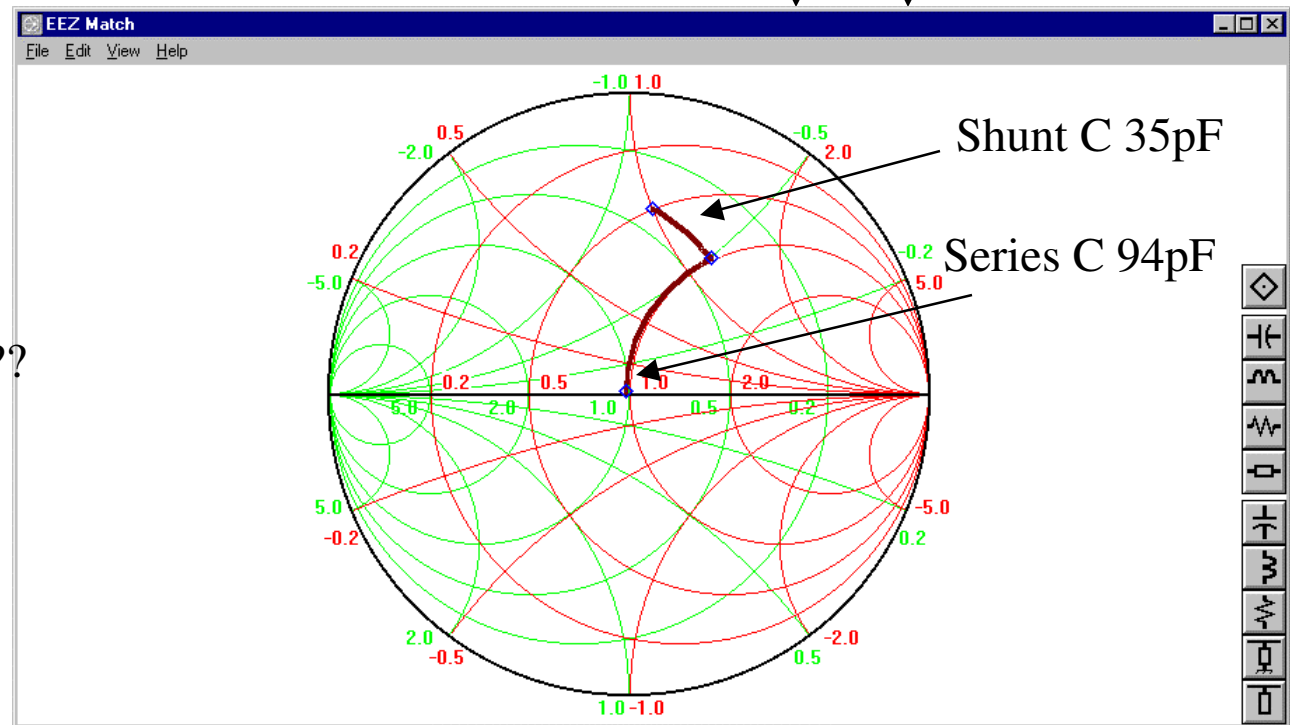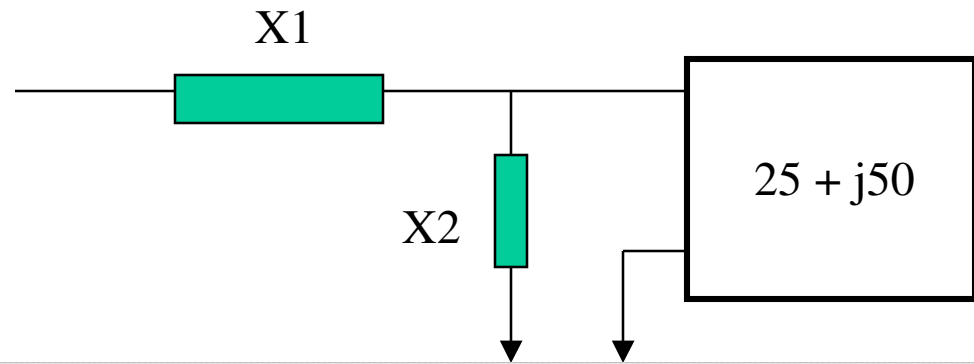Are there other ways to match this same impedance??



More than one way to skin a cat!

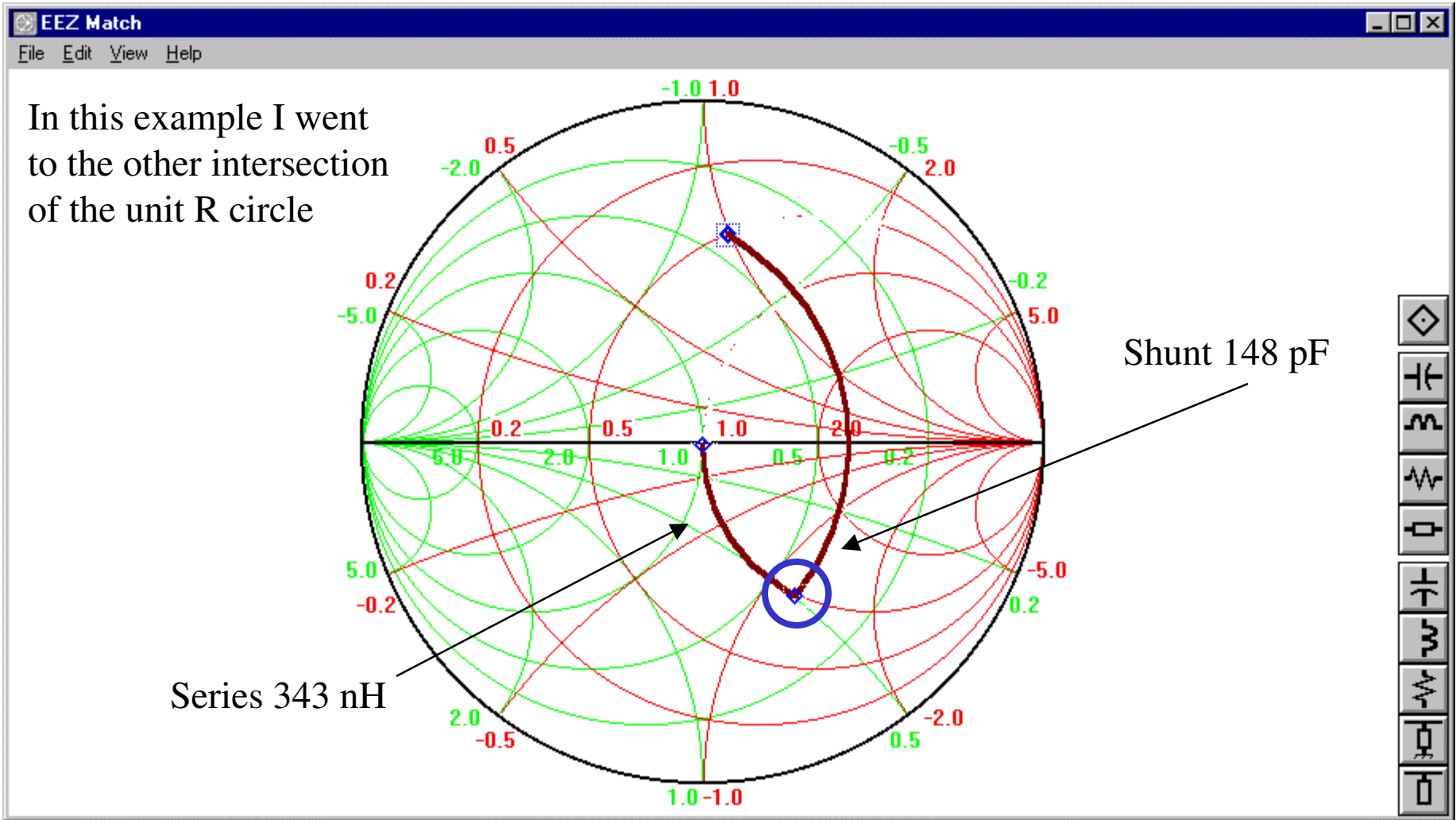


Distributed Elements


- Last but **NOT** least, transmission lines, microstrips, striplines and waveguides can all be made to perform impedance transformation and matching functions just like their lumped element cousins...
- There are some important differences that are best seen on the Smith Chart.
- Observe how series transmission lines of various Z_0 's and physical lengths transform the impedance...
- Also notice the effect of shunt sections of transmission lines (these are called stubs). Stubs can be either open circuited or short circuited...

Here we have a transmission line in series with the same load. Note that the behavior is different.. The impedance is transformed along constant VSWR circles (something new!). In this example the impedance was transformed to a completely new value by a 120 degree (about 3.6m at this freq), piece of 50 ohm coax cable.


What do stubs do?

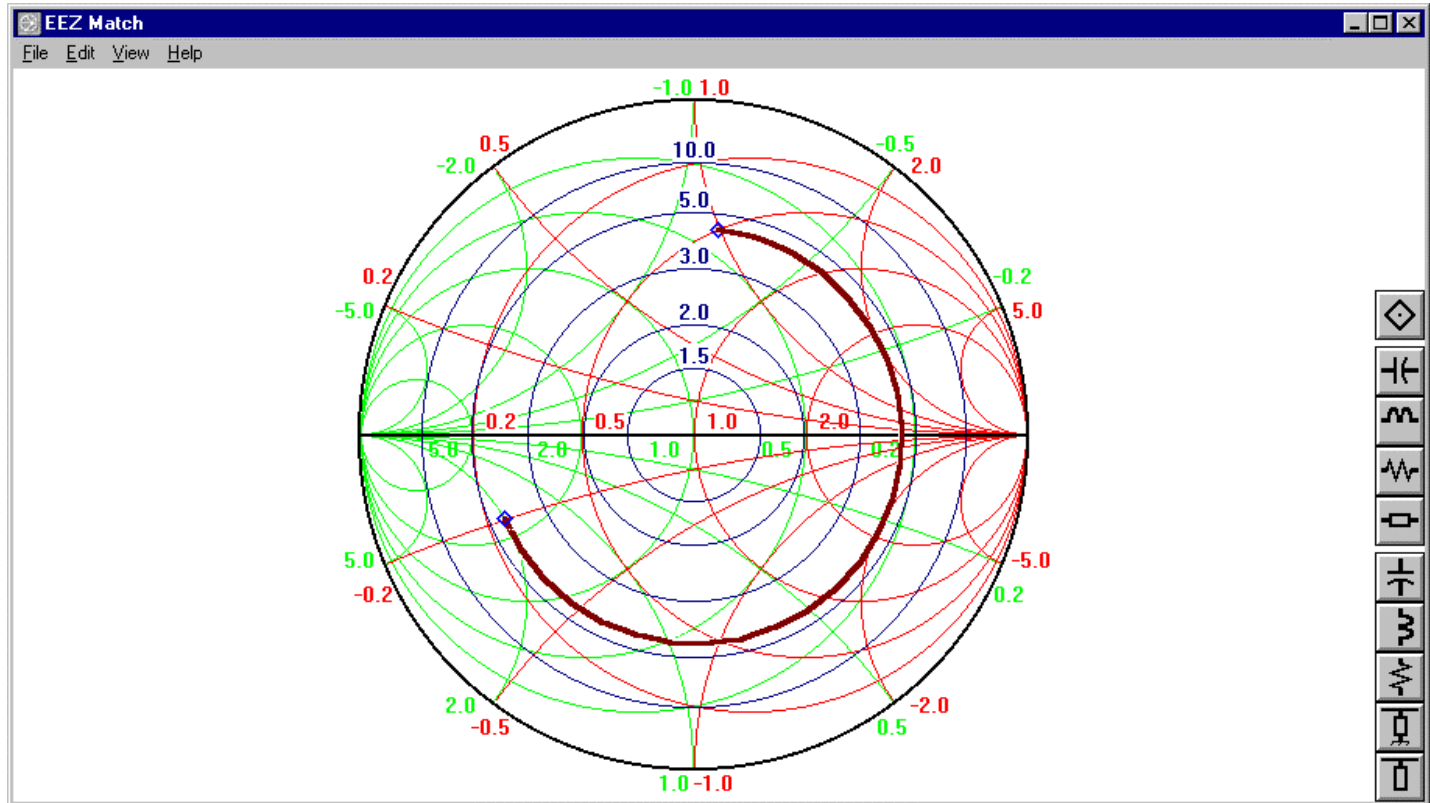

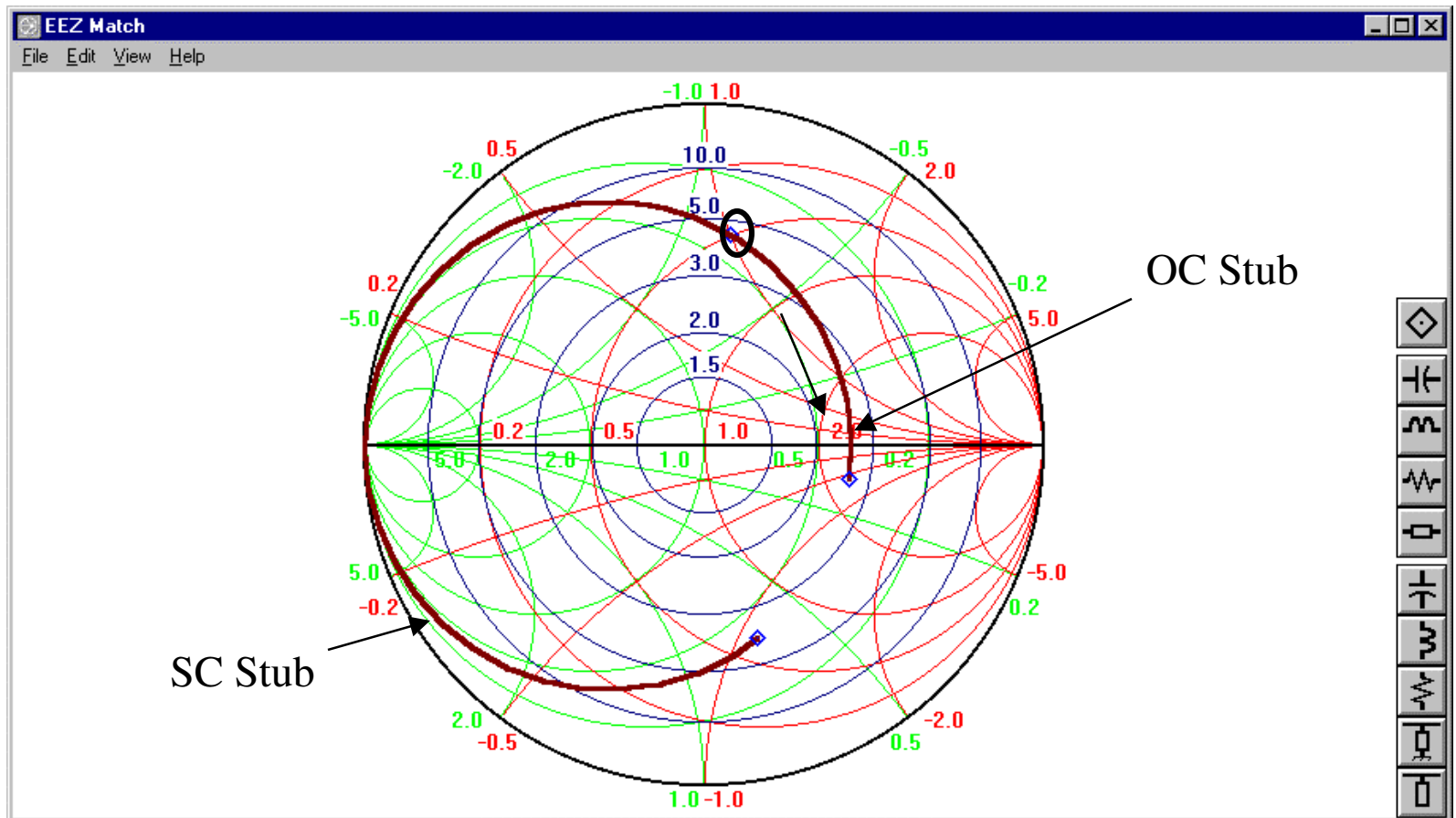Stubs can rotate all the way around the chart (unlike shunt L's and C's), but along circles of constant conductance (Like L's and C's).




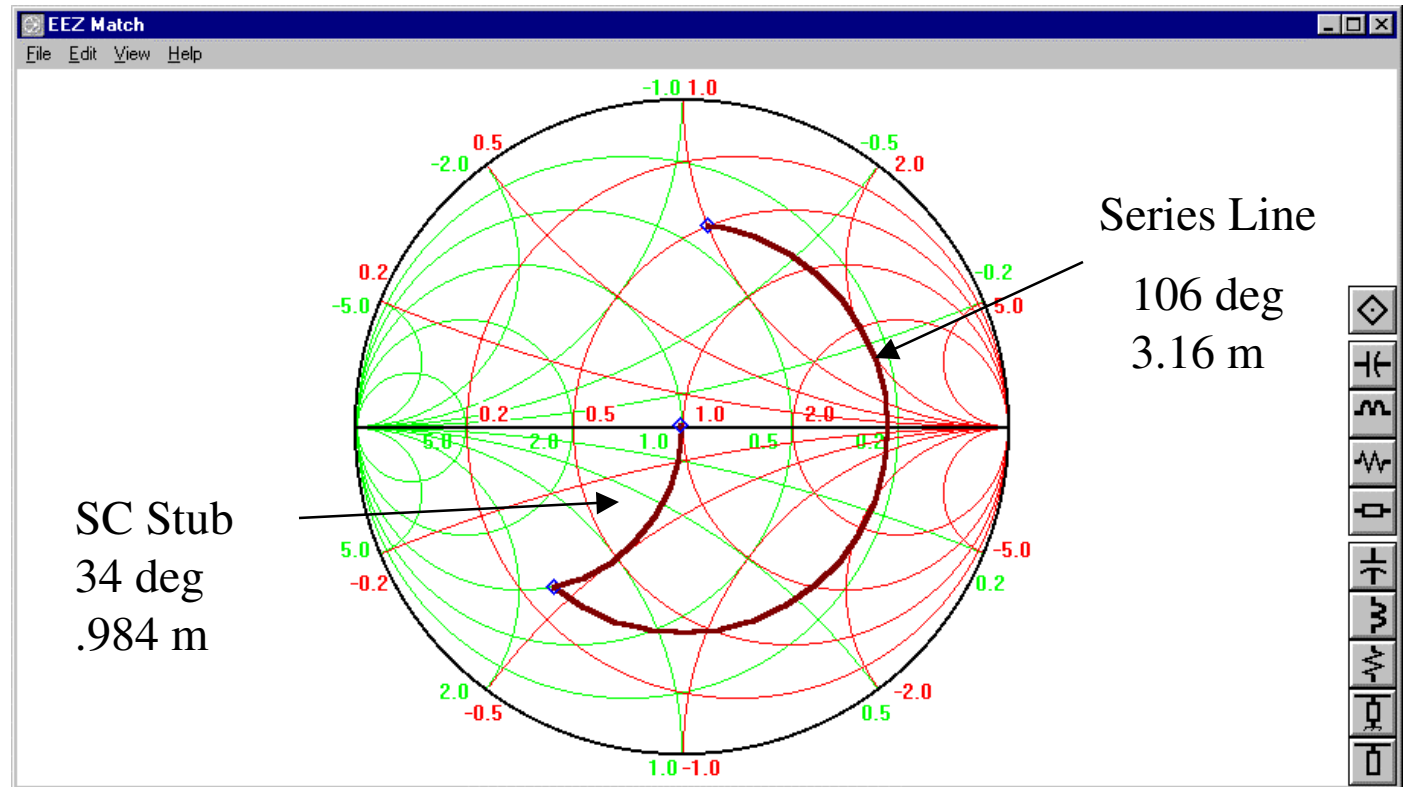Matching can be done entirely with Transmission Line Sections
50 Ohm Line is used




Matching can be done entirely with Transmission Line Sections

This time with 75 Ohm

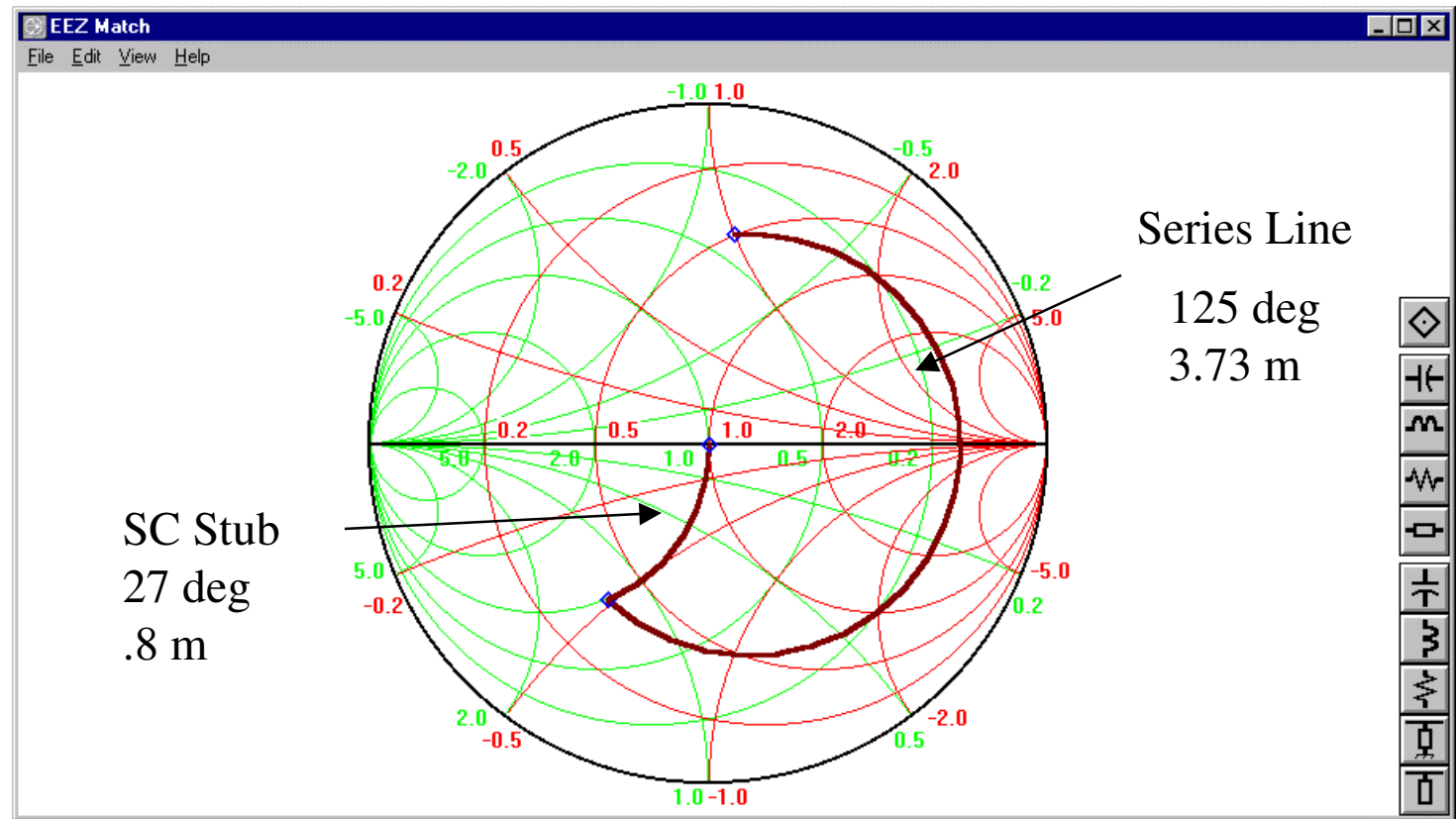


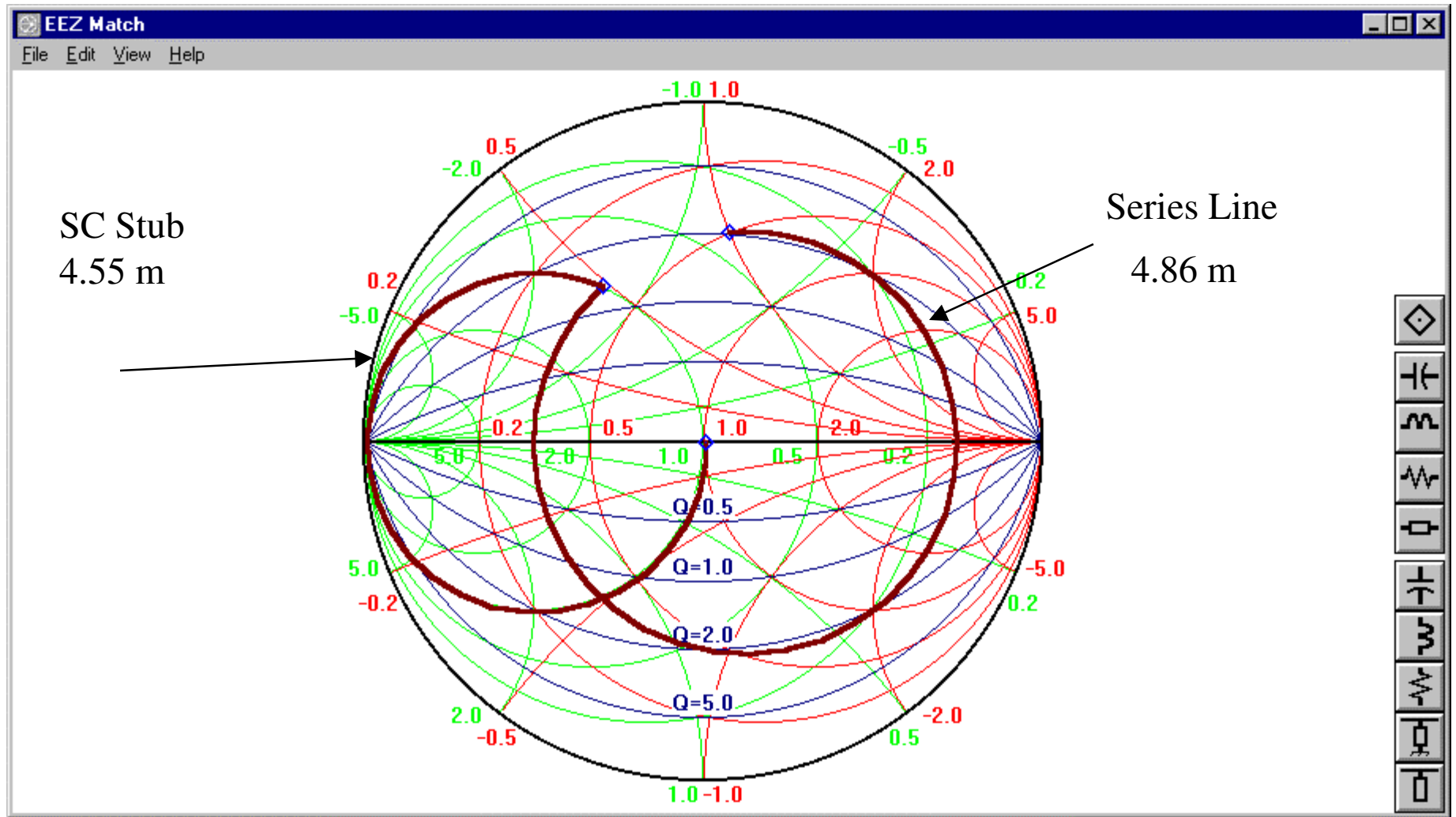And if you want to waste coax.... There are almost always more than one way to achieve a match!



Using Many Lumped Elements

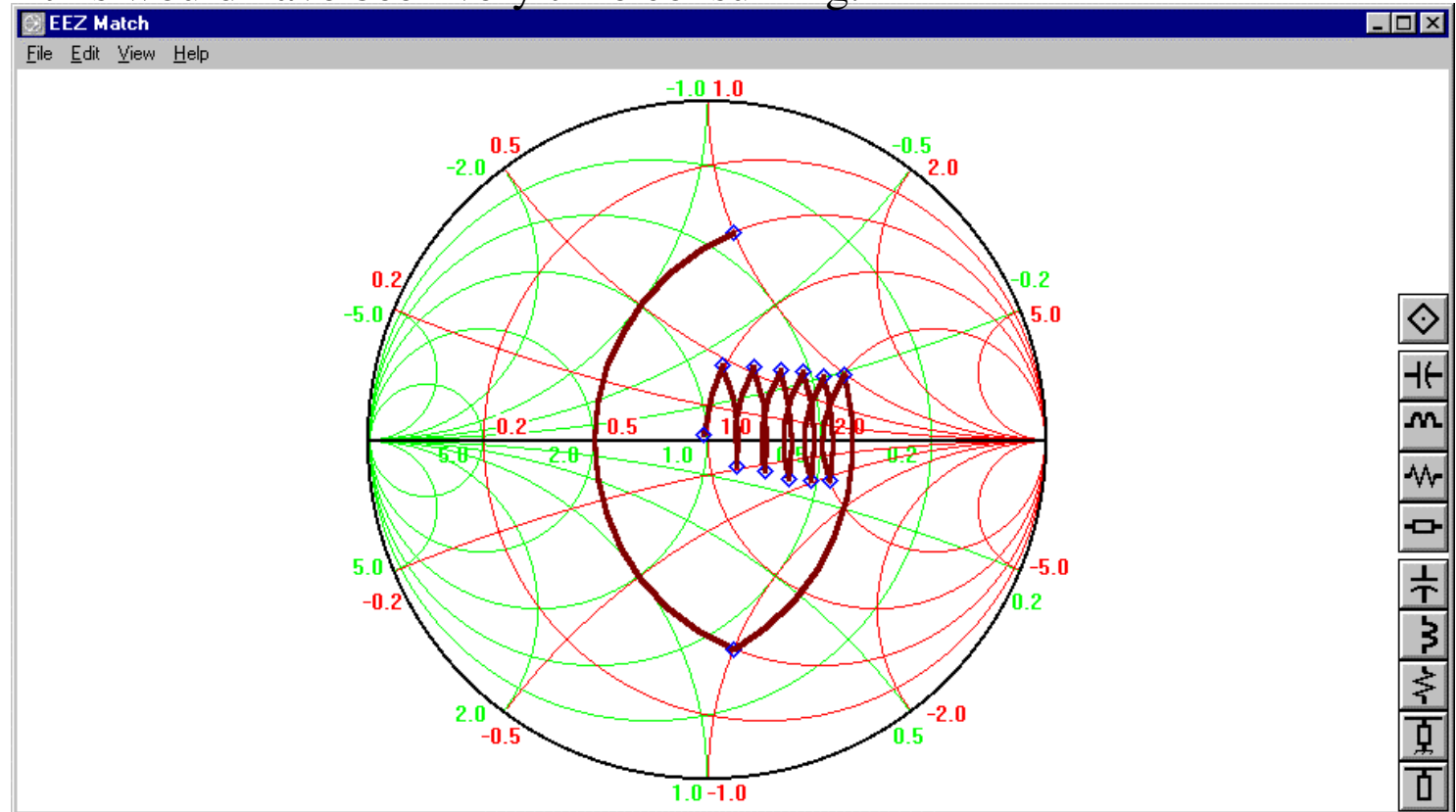Although the graph below was done on a software program, this complex (5L's, 5C's) matching network could have easily been done on a paper smith chart. The same calculations to do this would have been very time consuming.



Plotting vector data VS frequency

Vector Data : Data that has both real and imaginary parts ($R \pm jX$)
or Magnitude and Phase (like S- Parameters)

The Smith Chart makes an excellent backdrop for showing how this data varies with frequency. (Bonus.. What are Rieke Diagrams??)