



# BASIC DESIGN PARAMETERS FOR STATIC H-BRIDGE INVERTERS

IEEE Conference 2022

By

Cliff Furcall

## Sample LC Output Filter Criteria from Reference Designs

### **Output filter**

A simple filter on the output (L1, L2) attenuates the switching frequency, producing a clean sinusoidal waveform for output connections in terminals J4 and J5. The filter inductors and capacitors used on the demo board were chosen to provide the optional combination of benefits: low loss, good attenuation of the switching frequency, and small size. Consult the schematic and/or bill of materials to verify values; but in general, the cutoff frequency will be around 5kHz - 10kHz to accommodate 100Hz switching. The inductors have powder cores with relatively low permeability (60-90) and soft saturation characteristics. The inductors and/or capacitors can be changed to evaluate different filter designs.

Based on the Simulink simulation results we have selected a resonant frequency in the range: 600 to 900 Hz.

Having the resonant frequency we are able to select values of the inductor and capacitor. To achieve the required resonant frequency of the filter we have plenty of variants of L and C distribution. The values of the components have to be selected with consideration of their size, cost and availability. Considering the components available in the market, we have chosen following combination:

- L506 = 5 mH
- C605 = 6.8  $\mu$ F

The resonant frequency of such a circuit is 863 Hz and falls in our range.

# Basic H-Bridge Inverter Schematic

- Familiar H\_Bridge Configuration

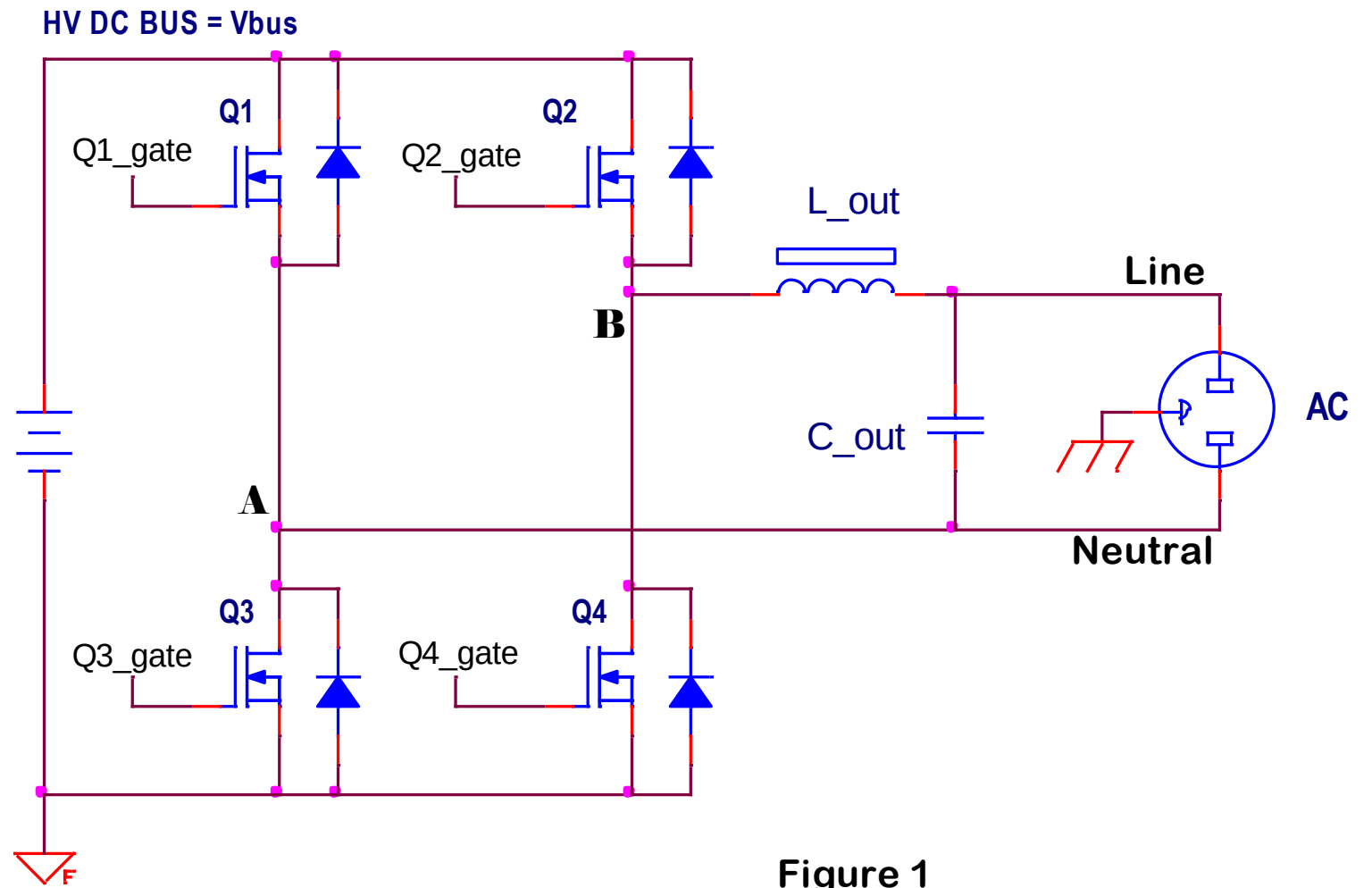


Figure 1

# Bipolar Conduction

- For bipolar modulation, both legs of the H-Bridge (noted as A and B in Figure 1) switch at high frequency. In this configuration Q2 and Q3 conduct simultaneously and Q1 and Q4 conduct simultaneously. Refer to the Bipolar Waveforms timing diagram. During the positive half cycle of an AC output voltage waveform, we define the “on time” when Q2 and Q3 are conducting and the “off time” when Q1 and Q4 are conducting. Referring to Figure 2, during  $t_{on}$ , the voltage on  $L_{out}$  equals  $V_{bus}$  minus the instantaneous output voltage. Referring to Figure 3, during  $t_{off}$ , the inductor voltage equals the instantaneous output voltage plus  $V_{bus}$ .

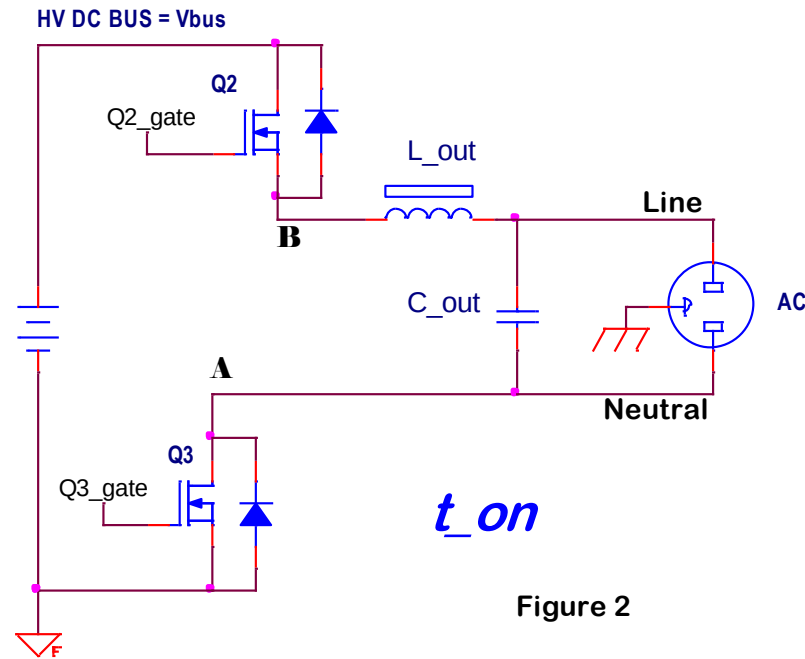


Figure 2

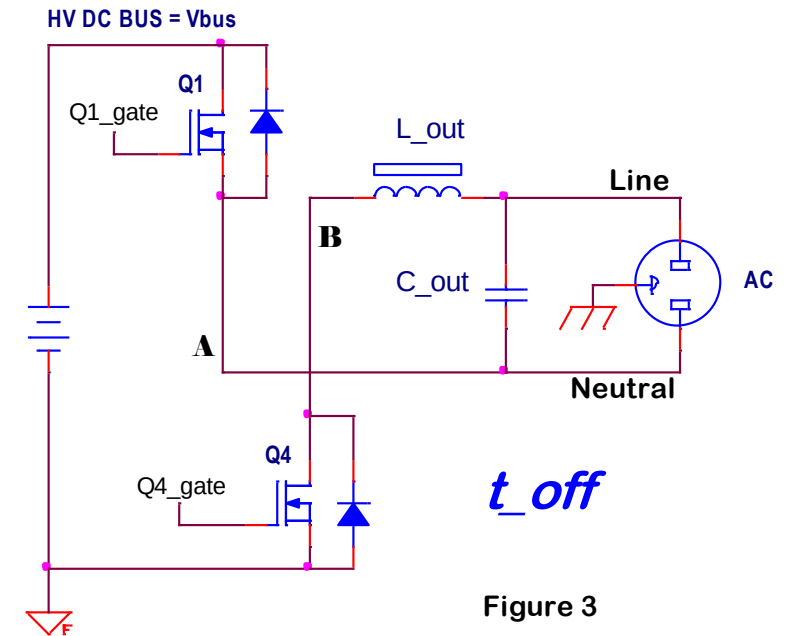


Figure 3

# BIPOLAR WAVEFORMS

Q2, Q3\_gates


Q1, Q4\_gates

B

A

Positive half of AC cycle

Negative half of AC cycle

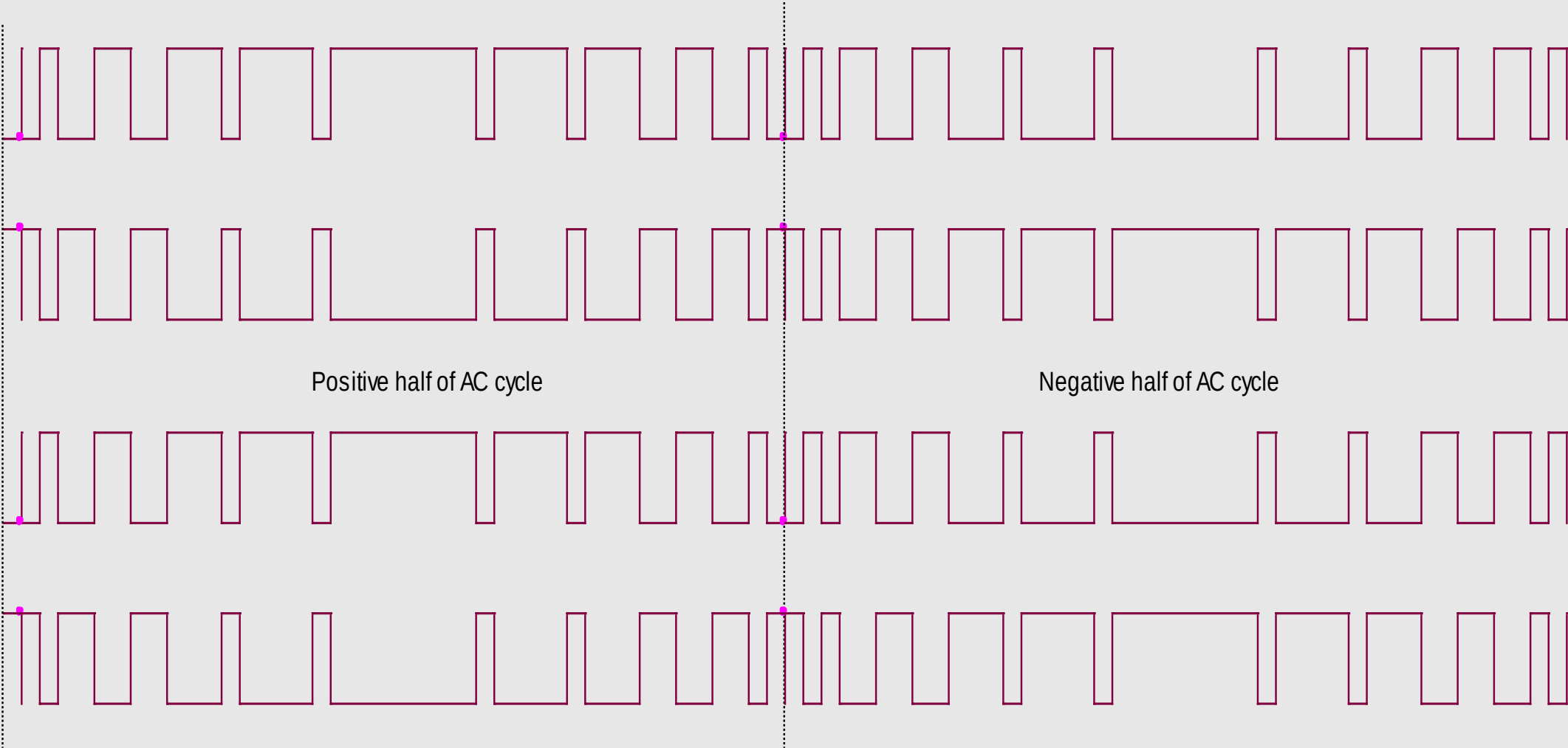

## Bipolar Modulation Duty Cycle

- During the on-time, the pk-pk inductor current is given by –

$$\Delta I_{on} := \frac{(V_{bus} - V_{oi})}{L_{out}} \cdot t_{on} \quad \text{eq1}$$

- During the off-time, the pk-pk inductor current is given by –

$$\Delta I_{off} := \frac{(V_{bus} + V_{oi})}{L_{out}} \cdot t_{off} \quad \text{eq 2}$$

- Since the magnitude of the pk-pk inductor during the on time must be equal to the magnitude of the pk-pk current during the off time, eq 1 and eq 2 must be equal in magnitude (though opposite in polarity), we can equate eq 1 and eq 2 and solve for the duty cycle with respect to the instantaneous output  $V_{oi}$  –

$$\frac{(V_{bus} - V_{oi})}{L_{out}} \cdot t_{on} = \frac{(V_{bus} + V_{oi})}{L_{out}} \cdot t_{off}$$

- By definition,  $t_{on} = \delta \cdot T$  and  $t_{off} = (1 - \delta) \cdot T$  and by substituting into the above equation, we can solve for the duty cycle

$$\delta := \frac{1}{2} + \frac{V_{oi}}{2 \cdot V_{bus}}$$

eq 3

## Bipolar Modulation Pk-Pk Current

- Using the definition  $t_{on} = \delta / f_{sw}$  we can substitute for  $t_{on}$  in eq 1

$$\Delta I_{pk\_pk} := \frac{(V_{bus} - V_{oi})}{L_{out}} \cdot \frac{\delta}{f_{sw}} \quad \text{eq 4}$$

- Substituting eq 3 for the duty cycle into eq 4 results

$$\Delta I_{pk\_pk} := \frac{(V_{bus} - V_{oi})}{L_{out} \cdot f_{sw}} \cdot \left[ \frac{1}{2} + \frac{V_{oi}}{2 \cdot V_{bus}} \right] \quad \text{eq 5}$$

- Solving for  $\Delta I_{pk\_pk}$

$$\Delta I_{pk\_pk} := \frac{V_{bus}^2 - V_{oi}^2}{2 \cdot L_{out} \cdot f_{sw} \cdot V_{bus}} \quad \text{eq 6}$$

## Bipolar Modulation Output Inductor

- To determine the point where maximum  $\Delta I_{pk-pk}$  occurs, let the derivative of  $\Delta I_{pk-pk}$  (eq 6) with respect to  $V_{oi}$  equal 0 and then solve for  $V_{oi}$ . The derivative is

- $$\frac{-V_{oi}}{L_{out} \cdot f_{sw} \cdot V_{bus}} = 0 \quad V_{oi} := 0 \quad \text{eq 7}$$

As a general design practice, we select a value for the output inductor that allows a worst case pk-pk current in the inductor to be between 10% and 40% of the maximum peak load current. The peak load current is given by the expression

$$I_{pk\_ac} := \frac{\sqrt{2} \cdot P_{out}}{V_{rms}} \quad \text{eq 8}$$



## Bipolar Inductor

- We can define a factor ILfac to be ratio of pk-pk inductor current to the peak AC load current.
- i.e. ( $0.10 < ILfac < 0.40$ ) for a pk-pk current of 10% to 40% of the peak load current.

$$\Delta I_{pk\_pk} := ILfac \cdot I_{pk\_ac}$$

eq 9

- Applying the ILfac of eq 9 to the AC output current of eq 8 yields eq 10.

$$\Delta I_{pk\_pk} := ILfac \cdot \frac{\sqrt{2} \cdot P_{out}}{V_{rms}}$$

eq 10


- Equating eq 10 for  $\Delta I_{pk\_pk}$  to eq 1 for  $\Delta I_{on}$  and solving for  $L_{out}$  yields eq 12.

$$L_{out} := \frac{V_{bus} \cdot V_{rms}}{2 \cdot \sqrt{2} \cdot P_{out} \cdot f_{sw} \cdot ILfac}$$

$$L_{out} := \frac{0.353 \cdot V_{bus} \cdot V_{rms}}{P_{out} \cdot f_{sw} \cdot ILfac}$$

eq 12

# UNIPOLAR WAVEFORMS

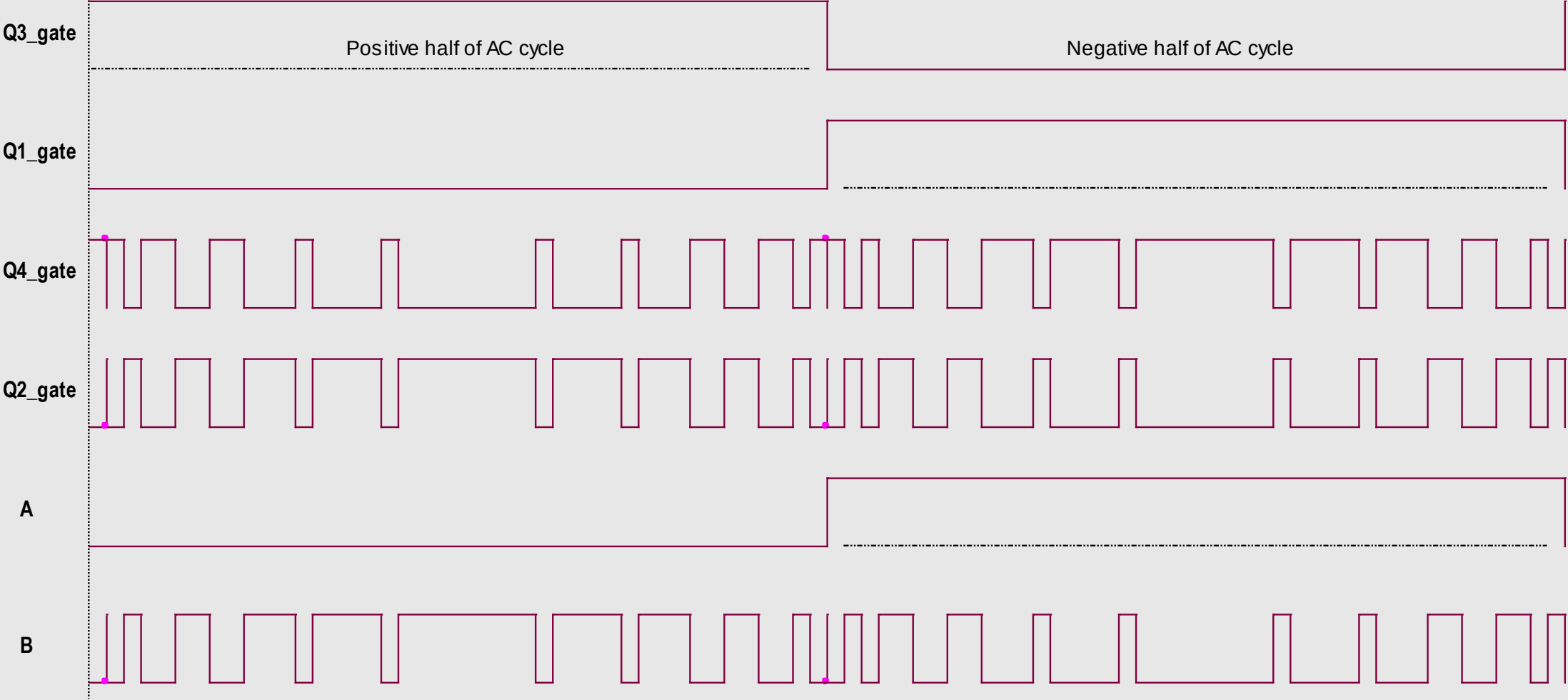

# Unipolar Conduction

- The equivalent schematics for H-bridge on-time and off-time are shown in Figure 4 and Figure 5 respectively. The relevant waveforms for unipolar modulation are shown below. The left side (the "A" leg) of the bridge switches at the fundamental frequency of the AC output i.e. 50Hz or 60 Hz. The right side of the bridge (the "B" leg) is pulse width modulated at high frequency to produce an AC output waveform. During the positive half of the AC output waveform, Q3 is on, Q1 is off and point A is connected to the negative of the HV DC BUS. Q2 and Q4 then switch in a manner like a synchronous buck regulator. Note that Q2 and Q4 are driven in a complimentary manner i.e. when Q4 is on, then Q2 is off and vice versa.

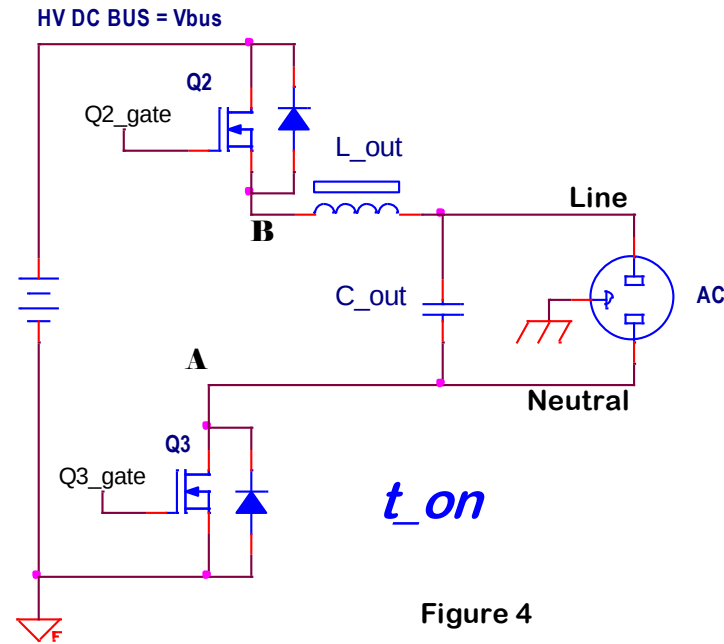


Figure 4

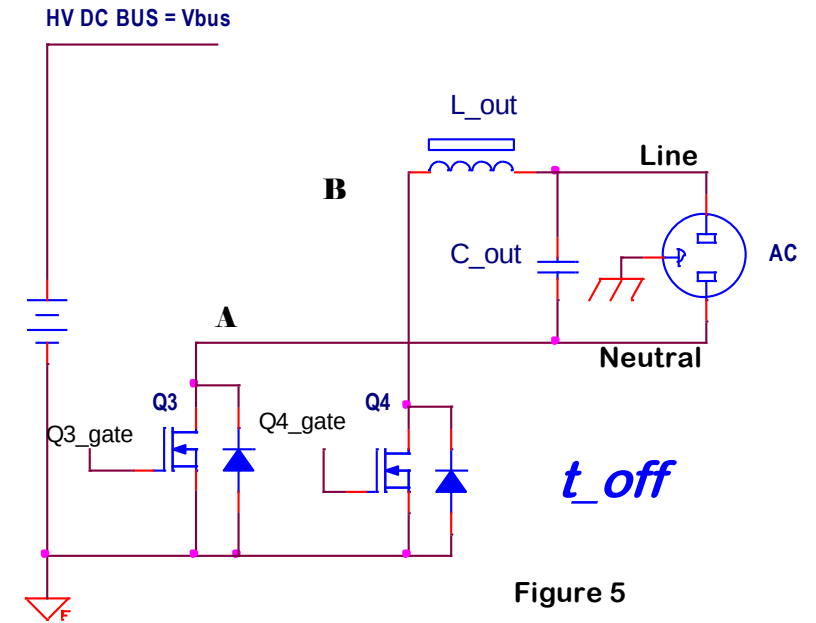


Figure 5

## Unipolar Modulation Duty Cycle

- During the on-time, the pk-pk inductor current is given by – 
$$\Delta I_{on} := \frac{(V_{bus} - V_{oi})}{L_{out}} \cdot t_{on}$$
 eq 13

- During the off-time, the pk-pk inductor current is given by – 
$$\Delta I_{off} := \frac{(V_{oi})}{L_{out}} \cdot t_{off}$$
 eq 14

- We can equate eq 13 and eq 14 and solve for the duty cycle with respect to the instantaneous output  $V_{oi}$

- $$\frac{(V_{bus} - V_{oi})}{L_{out}} \cdot t_{on} = \frac{(V_{oi})}{L_{out}} \cdot t_{off}$$

Substituting  $t_{on} = \delta * T$ , and  $t_{off} = (1 - \delta) * T$ , and solving for the duty cycle

$$\delta := \frac{V_{oi}}{V_{bus}}$$

eq 15

## Unipolar Modulation Pk-Pk Current

- Using the definition  $t_{on} = \delta / f_{sw}$  we can substitute for  $t_{on}$  in eq 13

$$\Delta I_{pk\_pk} := \frac{(V_{bus} - V_{oi})}{L_{out}} \cdot \frac{\delta}{f_{sw}} \quad \text{eq 16}$$

- Substituting eq 15 for the duty cycle into eq 16 results in

$$\Delta I_{pk\_pk} := \frac{(V_{bus} - V_{oi})}{L_{out} \cdot f_{sw}} \cdot \left[ \frac{V_{oi}}{V_{bus}} \right] \quad \text{eq 17}$$

- Solving for  $\Delta I_{pk\_pk}$

$$\Delta I_{pk\_pk} := \frac{V_{bus} \cdot V_{oi} - V_{oi}^2}{L_{out} \cdot f_{sw} \cdot V_{bus}} \quad \text{eq 18}$$

## Unipolar Modulation Output Inductor

- To determine the point where maximum  $\Delta I_{pk} = -pk$  occurs, let the derivative of eq 18 with respect to  $V_{oi}$  equal 0 and then solve for  $V_{oi}$ . The derivative is

$$\circ \quad \frac{1}{L_{out} \cdot f_{sw}} \cdot \frac{-2 \cdot V_{oi}}{L_{out} \cdot f_{sw} \cdot V_{bus}} = 0$$

$$V_{oi} := \frac{V_{bus}}{2} \quad \text{eq 19}$$

- The solution shown for eq 19 yields the point where the pk-pk current is at a maximum. The maximum pk-pk output current occurs when  $V_{oi} = V_{bus}/2$ , i.e. when the instantaneous AC output voltage is half of the DC bus voltage. Note from eq 15 that when  $V_{oi} = V_{bus}/2$ , the duty cycle is 0.5.

## Unipolar Inductor

- The peak load current is given by the expression

$$I_{pk\_ac} := \frac{\sqrt{2} \cdot P_{out}}{V_{rms}} \quad \text{eq 20}$$

- We can define a factor ILfac to be ratio of pk-pk inductor to the peak AC load current.
- i.e. ( $0.10 < ILfac < 0.40$ ) for a pk-pk current of 10% to 40% of the peak load current.

$$\Delta I_{pk\_pk} := ILfac \cdot I_{pk\_ac} \quad \text{eq 21}$$

- Substituting eq 20 into eq 21 yields

$$\Delta I_{pk\_pk} := ILfac \cdot \frac{\sqrt{2} \cdot P_{out}}{V_{rms}} \quad \text{eq 22}$$


- Substituting eq 22 into eq 13 for  $\Delta I_{on}$  and solving for  $L_{out}$

$$L_{out} := \frac{V_{bus} \cdot V_{rms}}{4 \cdot \sqrt{2} \cdot P_{out} \cdot f_{sw} \cdot ILfac} \quad \text{eq 23}$$

$$L_{out} := \frac{0.177 \cdot V_{bus} \cdot V_{rms}}{P_{out} \cdot f_{sw} \cdot ILfac}$$
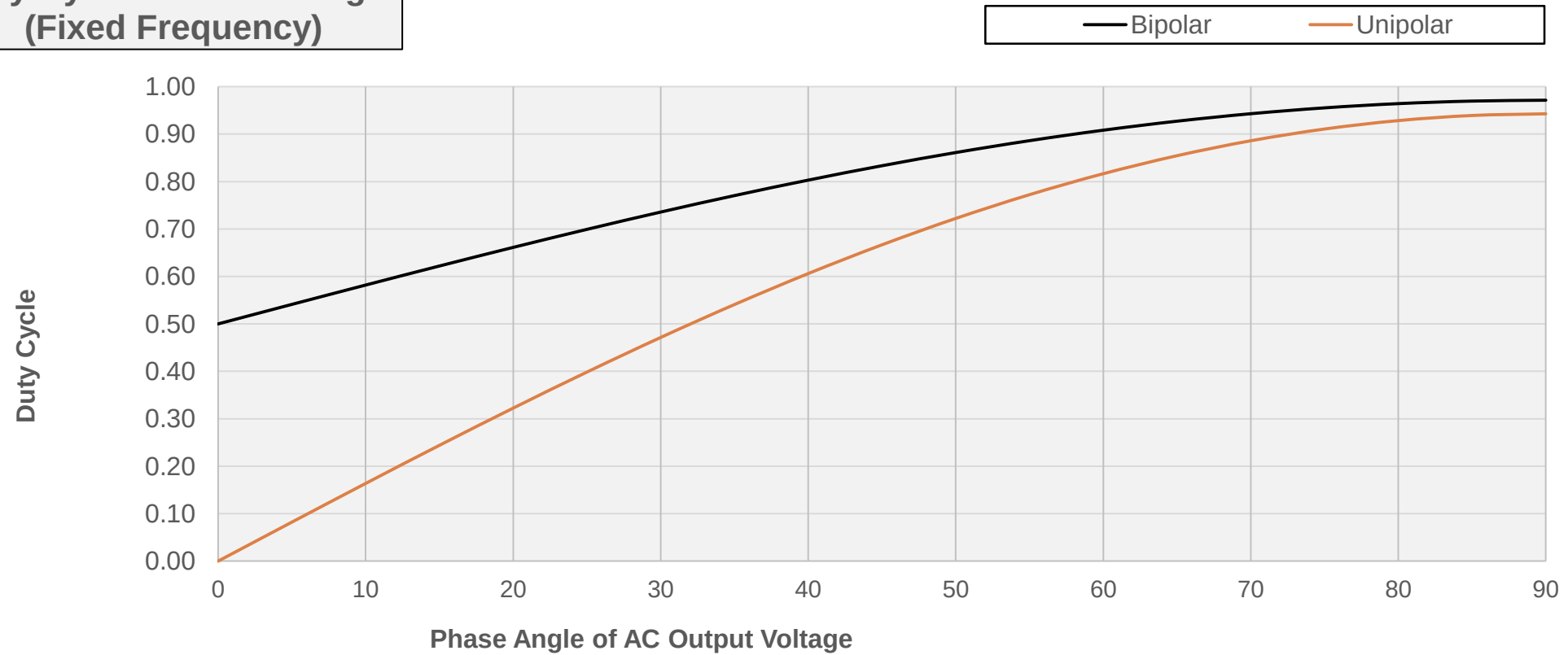
# Bipolar vs Unipolar Duty Cycle


Duty Cycle vs Phase Angle  
(Fixed Frequency)




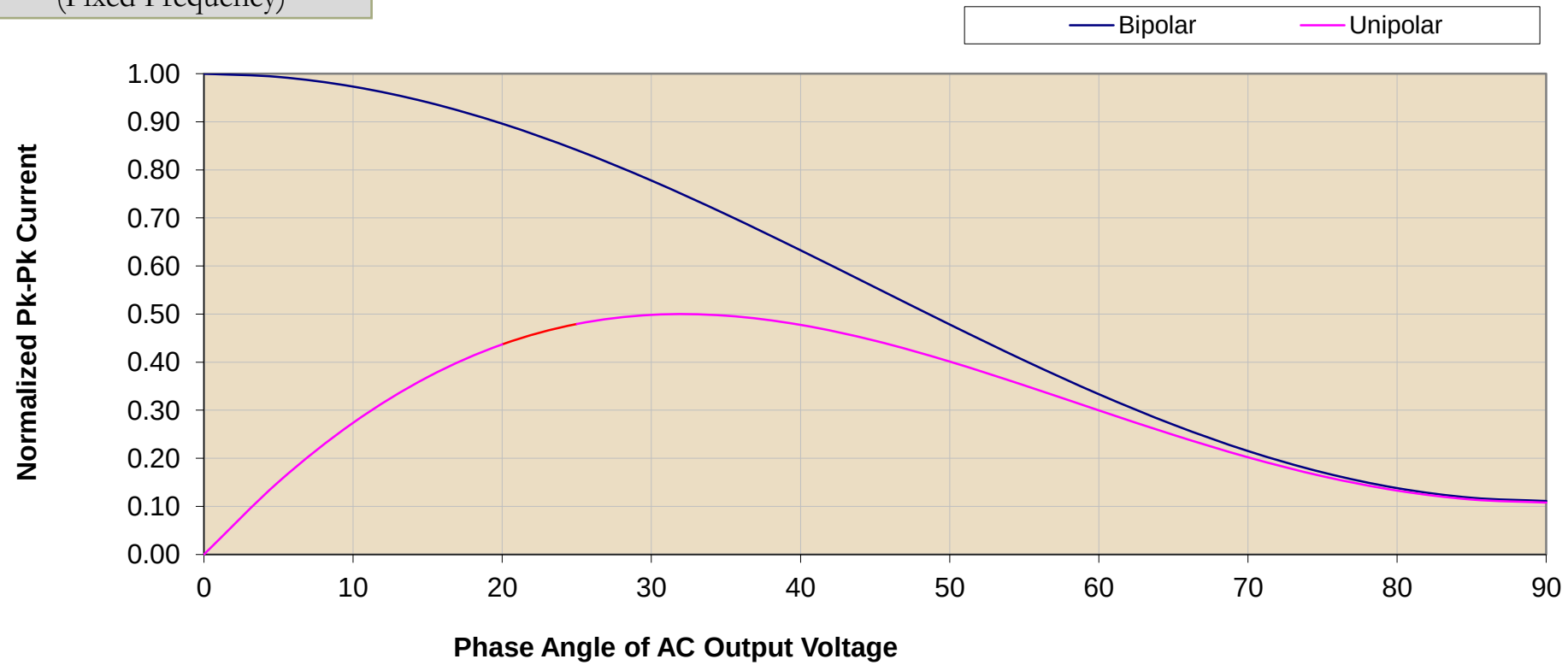
# Normalized Bipolar vs Unipolar Pk-Pk Current

Pk-Pk Current vs Phase Angle  
(Fixed Frequency)



## Summary – Bipolar vs Unipolar

| Bipolar Modulation                                                                             | Unipolar modulation                                                                               |
|------------------------------------------------------------------------------------------------|---------------------------------------------------------------------------------------------------|
| $\delta := \frac{1}{2} + \frac{V_{oi}}{2 \cdot V_{bus}}$                                       | $\delta := \frac{V_{oi}}{V_{bus}}$                                                                |
| $\Delta I_{pk\_pk} := \frac{V_{bus}^2 - V_{oi}^2}{2 \cdot L_{out} \cdot f_{sw} \cdot V_{bus}}$ | $\Delta I_{pk\_pk} := \frac{V_{bus} \cdot V_{oi} - V_{oi}^2}{L_{out} \cdot f_{sw} \cdot V_{bus}}$ |
| Maximum $I_{pk-pk}$ occurs at $V_{oi} = 0$                                                     | Maximum $I_{pk-pk}$ occurs at $V_{oi} = V_{bus}/2$                                                |
| $L_{out} := \frac{0.353 \cdot V_{bus} \cdot V_{rms}}{P_{out} \cdot f_{sw} \cdot IL_{fac}}$     | $L_{out} := \frac{0.177 \cdot V_{bus} \cdot V_{rms}}{P_{out} \cdot f_{sw} \cdot IL_{fac}}$        |

# Output Capacitor

- I will discuss three different criteria to be considered in selecting the value of the inverter output capacitor.

First criteria - The minimum output capacitor value required to limit the output ripple voltage to a specified value, defined as  $\Delta V_{cap}$ .

$$C_{out} := \Delta I_{pk\_pk} \cdot \frac{\Delta t}{\Delta V_{cap}}$$

eq 25

Using the expression

$$\Delta I_{pk\_pk} := IL_{fac} \cdot \frac{\sqrt{2} \cdot P_{out}}{V_{rms}}$$

eq 22

$$C_{out} := \frac{0.707 \cdot P_{out} \cdot IL_{fac}}{V_{rms} \cdot f_{sw} \cdot \Delta V_{cap}}$$

eq 26

Using the expression

$$\Delta I_{pk\_pk} := \frac{(V_{bus} - V_{oi})}{L_{out} \cdot f_{sw}} \cdot \left[ \frac{V_{oi}}{V_{bus}} \right]$$

eq 17

$$C_{out} := \frac{V_{bus}}{4 \cdot L_{out} \cdot f_{sw}^2 \cdot \Delta V_{cap}}$$

eq 27

## Output Capacitor continued

- Second Criteria - The preload current is generally required to implement a current mode control scheme so that there is a non-zero signal for the feedback with no load on the inverter output. Too large a capacitor will increase losses as there will be large, low frequency circulating currents in the H-bridge.

$$C_{out} := \frac{IC_{fac} \cdot P_{out}}{2 \cdot \pi \cdot F_{out} \cdot V_{rms}^2}$$

eq

- Third criteria - Calculate the resonant frequency that the output inductor and output capacitor produce. As a rule of thumb, the resonant frequency should be at least a decade lower than the switching frequency (for good filtering), and a decade higher than the AC output frequency to have enough loop gain to regulate the output voltage at the highest output frequency

$$C_{out} := \frac{1}{4 \cdot \pi^2 \cdot L_{out} \cdot f_{reas}^2}$$

eq 29

# Conclusion

- 1 – Design equations are derived for the duty cycle and the peak to peak inductor currents for both bipolar and unipolar modulation schemes.
- 2 – Criteria for determining the output inductance and output capacitance are derived for both bipolar and unipolar modulation schemes.
- 3 – The unipolar modulation scheme requires an output inductor half the value required in a bipolar modulation scheme for a given peak to peak inductor current.
- 4 – The unipolar modulation scheme practically eliminates the switching losses in one leg of the bridge (the low switching frequency leg) which allows for a significant improvement in efficiency.

- Thank you.