

IEEE 2025

Switch-mode power converter
compensation made easy

Authors

Louis Diana

Robert Sheehan






Agenda

- Compensation design and objective
- Explanation of poles and zeros
- Power stage characteristics
- Error amplifier and transconductance amplifier
- Isolated feedback with opto-coupler
- Compensation examples
- Circuit limitations and other issues



Compensation design and objectives

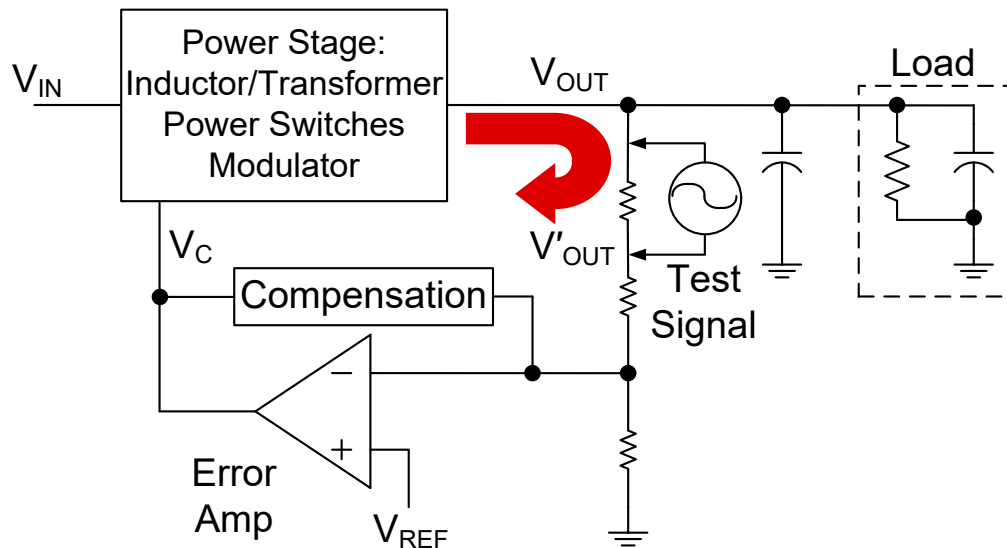Why do we need feedback and why do we need compensation?




- Feedback is needed to regulate the output voltage
- The control loop bandwidth influences the response time

Control loop response

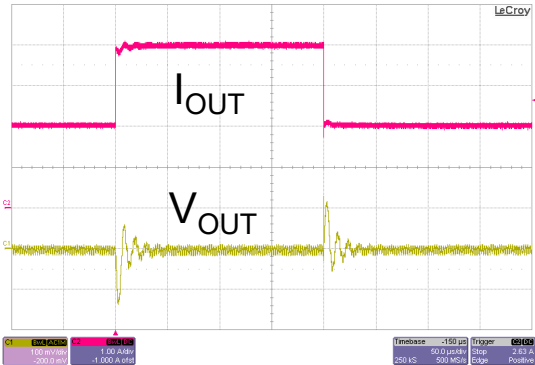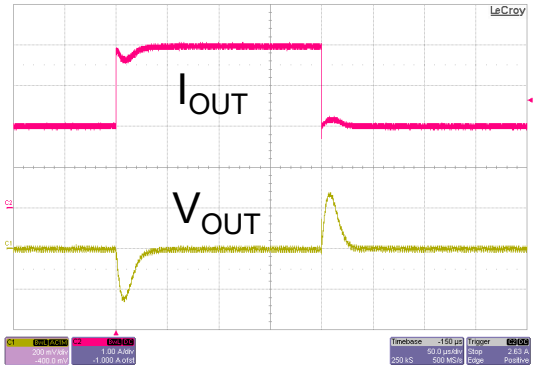Poor transient response	Objective	Good transient response
 LeCroy Timebase: 50.0 μs/div Stop: 2.63 A 250 MS 500 MS/div Edge: Positive Response is under-damped causing oscillatory behavior	- Maximize crossover frequency for fastest transient response - Adjust compensation for best setting behavior	 LeCroy Timebase: 50.0 μs/div Stop: 2.63 A 250 MS 500 MS/div Edge: Positive Response is well damped with good setting behavior


Phase margin and gain margin

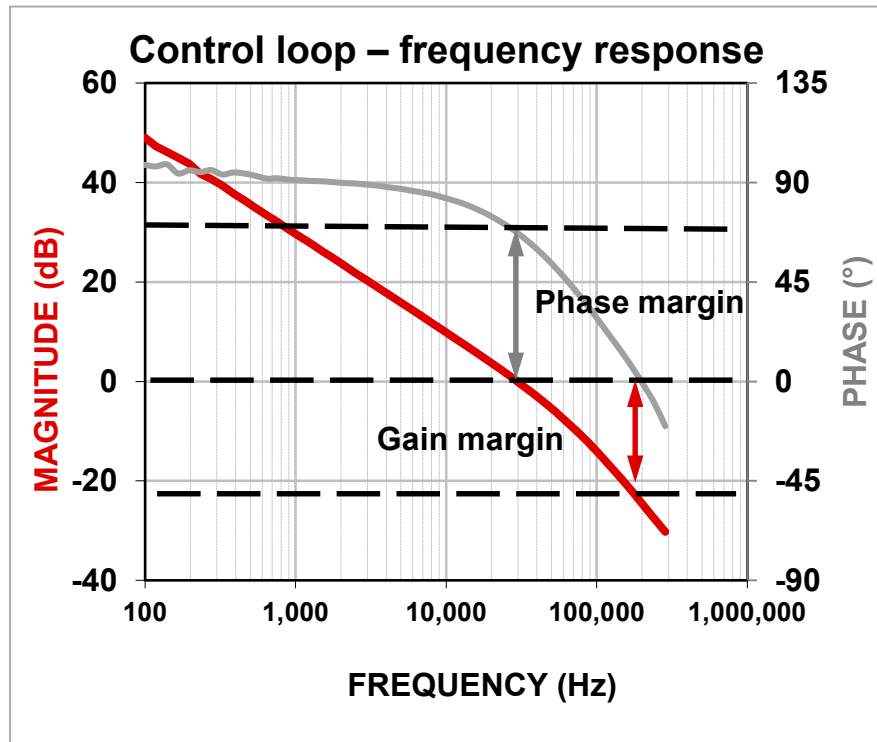

Phase margin and stability

- Sufficient phase margin needed to prevent oscillation (45° min.)
- Gain margin goal of 10 dB min.
- Slope of -20dB/decade when passing through 0 dB
- Bandwidth rule of thumb is 1/5 to 1/10 of switching frequency


Poles, zeros and right-half-plane zeros

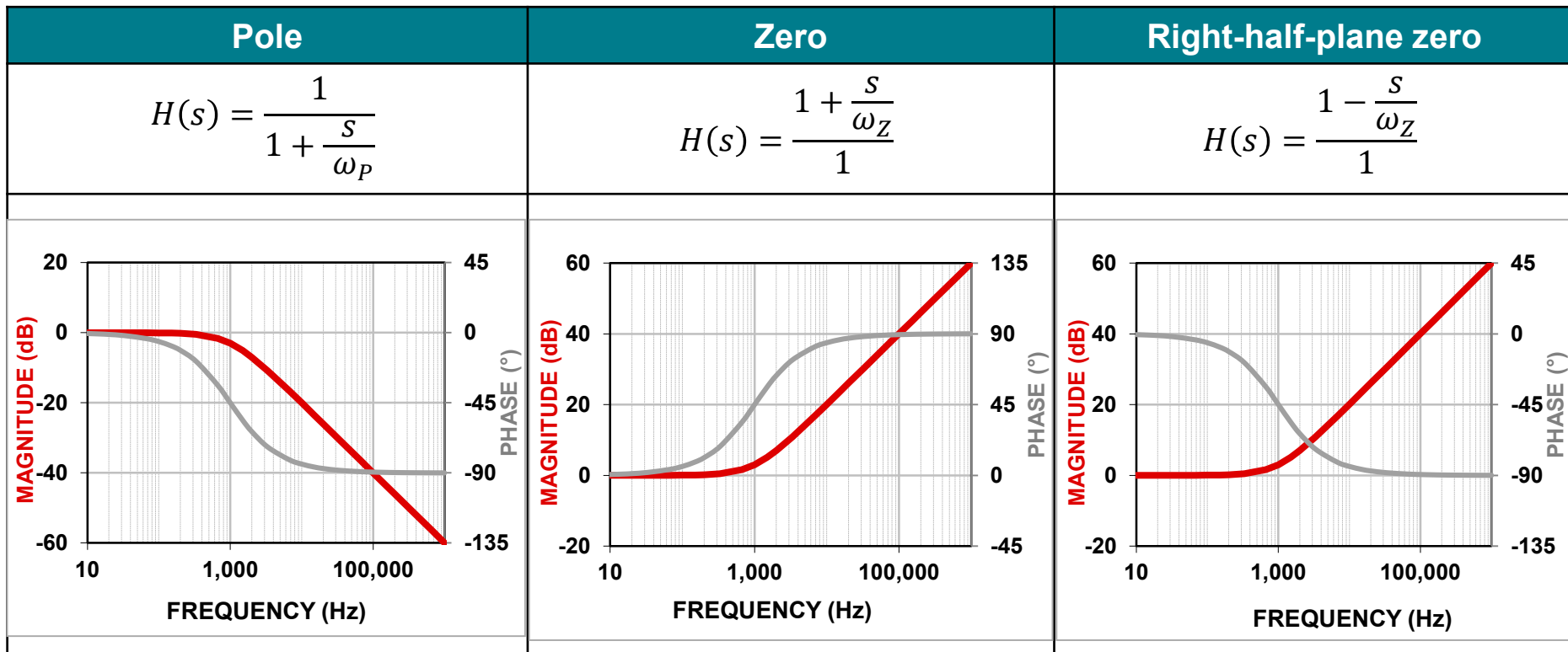

Complex conjugate pole and ESR zero


Complex conjugate pole
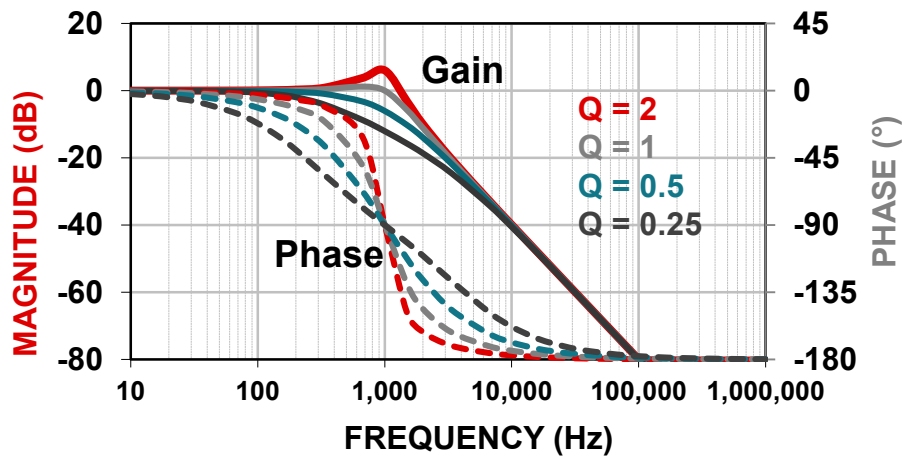
$$H(s) = \frac{1}{1 + \frac{s}{Q_0 \cdot \omega_0} + \frac{s^2}{\omega_0^2}}$$



With ESR zero
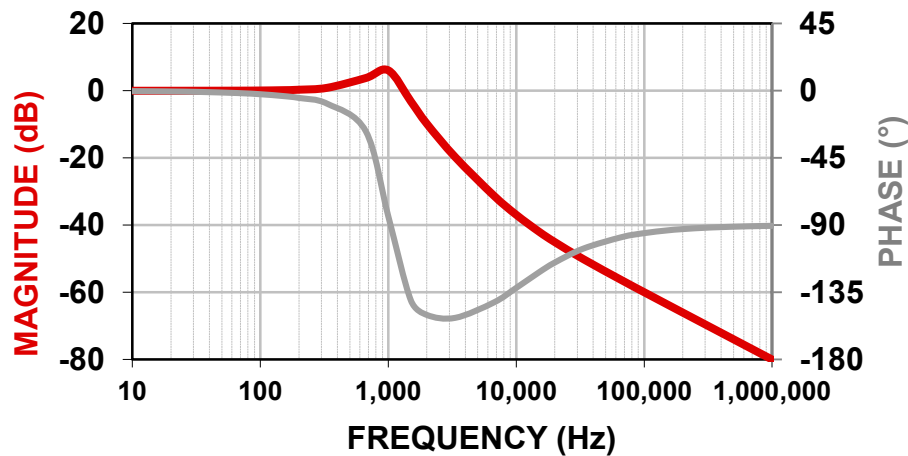
$$H(s) = \frac{1 + \frac{s}{\omega_Z}}{1 + \frac{s}{Q_0 \cdot \omega_0} + \frac{s^2}{\omega_0^2}}$$





Control methods and operating modes

Control methods

- Voltage-mode control
- Current-mode control

Operating modes

- Fixed frequency
- Continuous conduction-mode (CCM)


Switching frequency and period

- Switching frequency – f_{sw}
- Switching period – T


$$T = \frac{1}{f_{sw}}$$




DCM vs CCM

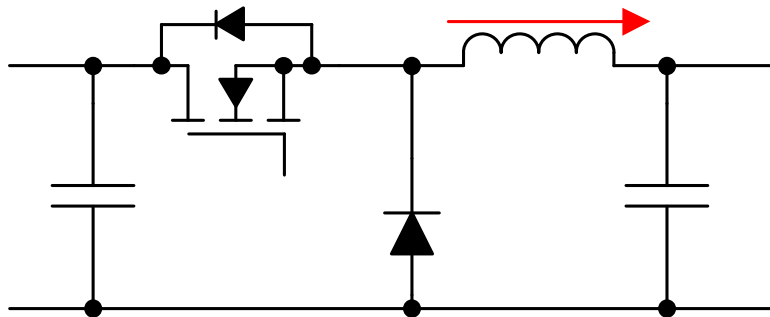

Discontinuous Conduction Mode (DCM)

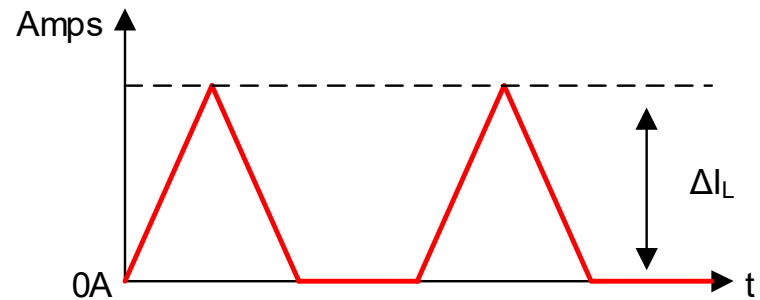


Continuous Conduction Mode (CCM)

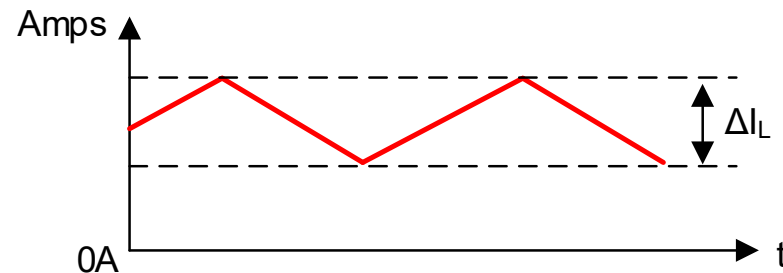




Buck, boost, and buck-boost derived topologies

Buck, forward, push-pull, bridge

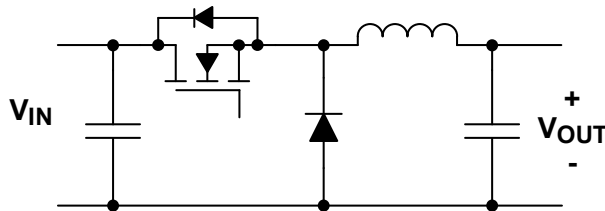


$$V_{OUT} = V_{IN} \times D$$

Boost

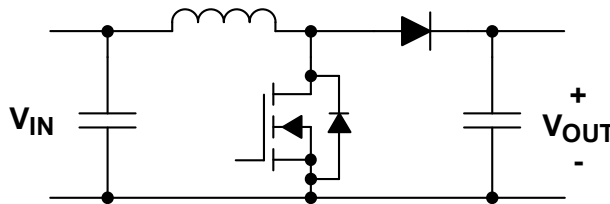



$$V_{OUT} = V_{IN} \times \frac{1}{1 - D}$$

Buck-boost, SEPIC, flyback

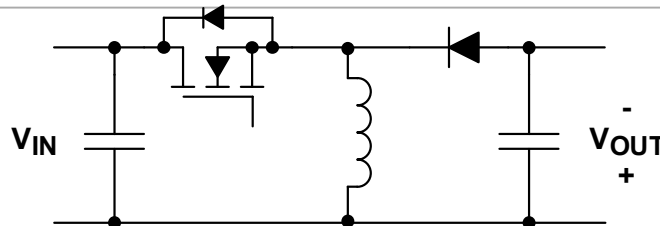

$$V_{OUT} = V_{IN} \times \frac{D}{1 - D}$$

Voltage-mode buck power stage

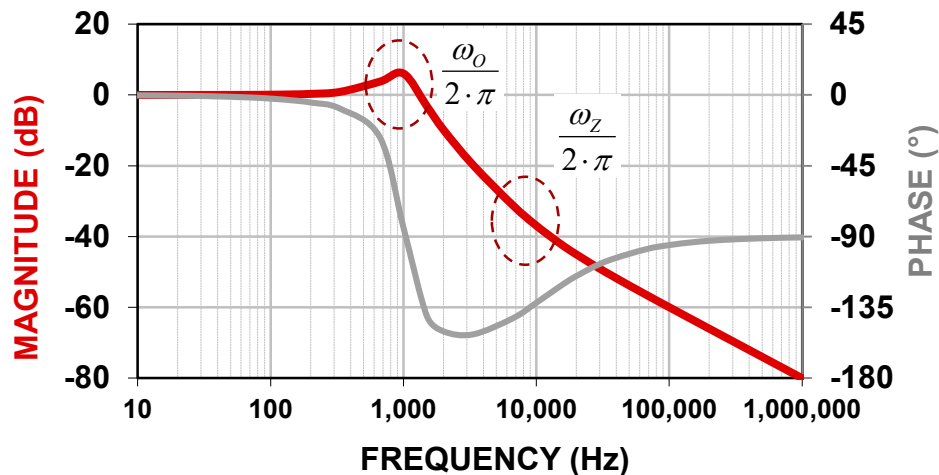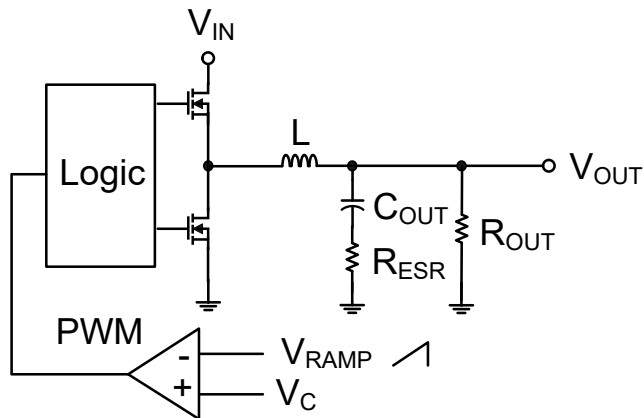

$$A_{VC} = \frac{V_{IN}}{V_{RAMP}}$$



$$\omega_o = \frac{1}{\sqrt{L \cdot C_{OUT}}}$$

$$Q_o = \frac{R_{OUT}}{\sqrt{L/C_{OUT}}}$$

$$\omega_z = \frac{1}{R_{ESR} \cdot C_{OUT}}$$

$$\frac{\hat{v}_{OUT}}{\hat{v}_C} = A_{VC} \cdot \frac{1 + \frac{s}{\omega_z}}{1 + \frac{s}{Q_o \cdot \omega_o} + \frac{s^2}{\omega_o^2}}$$

Current-mode buck power stage

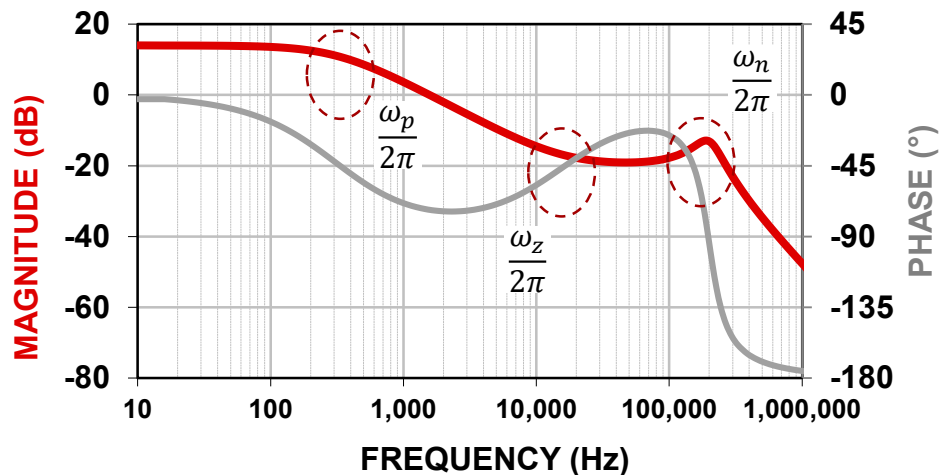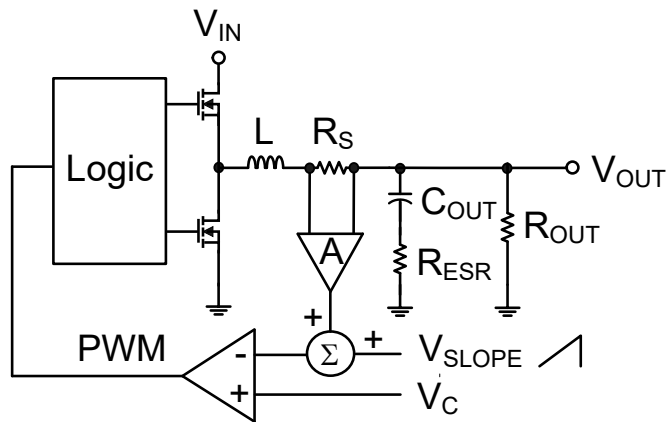

$$\omega_p \approx \frac{1}{C_{out} \cdot R_{out}}$$

$$\omega_z = \frac{1}{R_{ESR} \cdot C_{out}}$$

$$A_{VC} \approx \frac{R_{out}}{R_i} = \frac{R_{out}}{A \cdot R_S}$$


$$F_h(s) = \frac{1}{1 + \frac{s}{\omega_n \cdot Q_p} + \left(\frac{s}{\omega_n}\right)^2}$$

$$\omega_n = \frac{\omega_{fsw}}{2}$$

at D = 0.5

$$\frac{\hat{v}_{out}}{\hat{v}_c} \approx A_{VC} \cdot \frac{1 + \frac{s}{\omega_z}}{1 + \frac{s}{\omega_p}} \cdot F_h(s)$$

Current-mode boost power stage

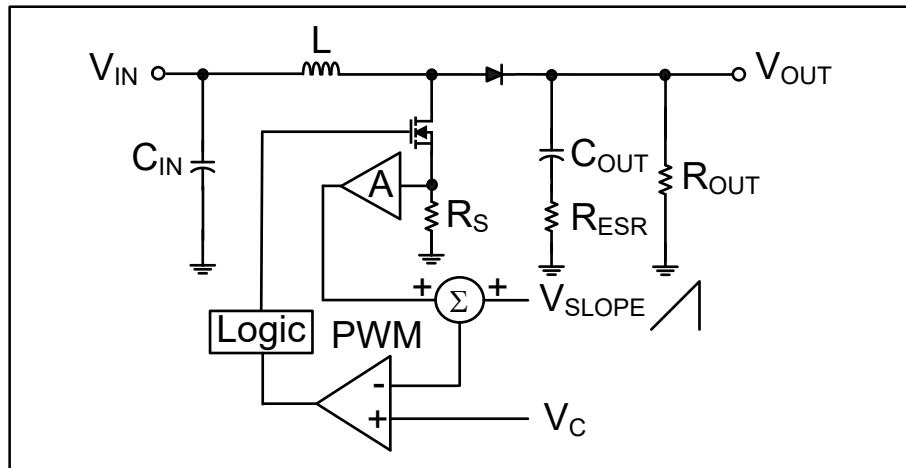


$$R_i = A \cdot R_S$$

$$\omega_r \approx \frac{R_{out} \cdot (1 - D)^2}{L} \quad \omega_n = \frac{\omega_{fsw}}{2}$$

$$A_{VC} \approx \frac{R_{out} \cdot (1 - D)}{R_i}$$



$$\omega_z = \frac{1}{R_{ESR} \cdot C_{OUT}} \quad \text{at } D = 0.5$$
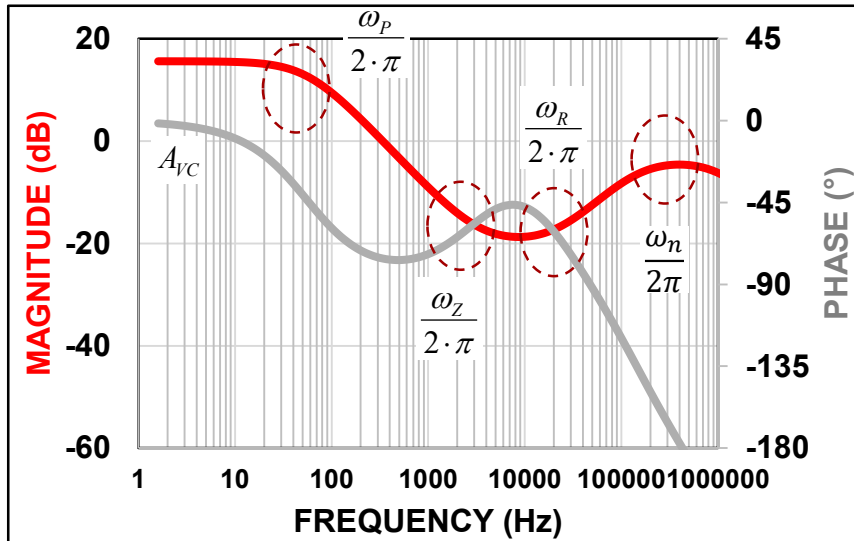
$$\omega_p \approx \frac{2}{C_{OUT} \cdot R_{OUT}} \quad F_h(s) = \frac{1}{1 + \frac{s}{\omega_n \cdot Q_p} + \left(\frac{s}{\omega_n}\right)^2}$$



$$\frac{\hat{v}_{out}}{\hat{v}_c} \approx A_{VC} \cdot \frac{\left(1 + \frac{s}{\omega_z}\right) \left(1 - \frac{s}{\omega_r}\right)}{1 + \frac{s}{\omega_p}} \cdot F_h(s)$$

Current-mode buck-boost power stage

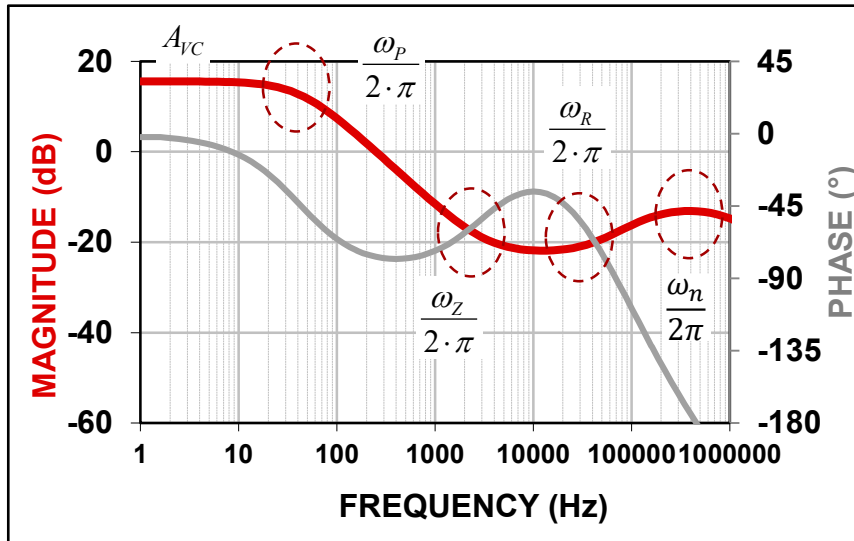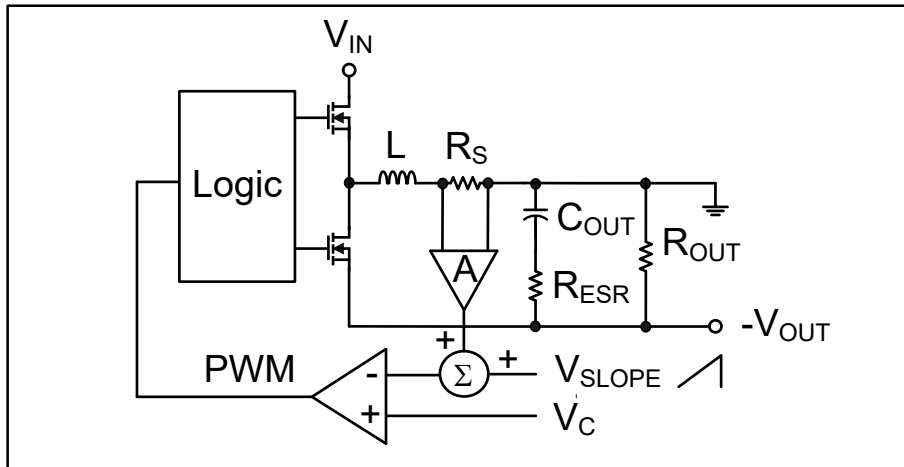

$$R_i = A \cdot R_s$$

$$\omega_r \approx \frac{R_{out} \cdot (1 - D)^2}{L \cdot D}$$

$$A_{VC} \approx \frac{R_{out} \cdot (1 - D)}{(1 - D) \cdot R_i}$$

$$\omega_z = \frac{1}{R_{ESR} \cdot C_{OUT}}$$


$$\omega_p \approx \frac{1 + D}{C_{OUT} \cdot R_{OUT}}$$

$$F_h(s) = \frac{1}{1 + \frac{s}{\omega_n \cdot Q_p} + \left(\frac{s}{\omega_n}\right)^2}$$

at D = 0.5

$$\frac{\hat{v}_{out}}{\hat{v}_c} \approx A_{VC} \cdot \frac{\left(1 + \frac{s}{\omega_z}\right) \left(1 - \frac{s}{\omega_r}\right)}{1 + \frac{s}{\omega_p}} \cdot F_h(s)$$


Current-mode flyback power stage

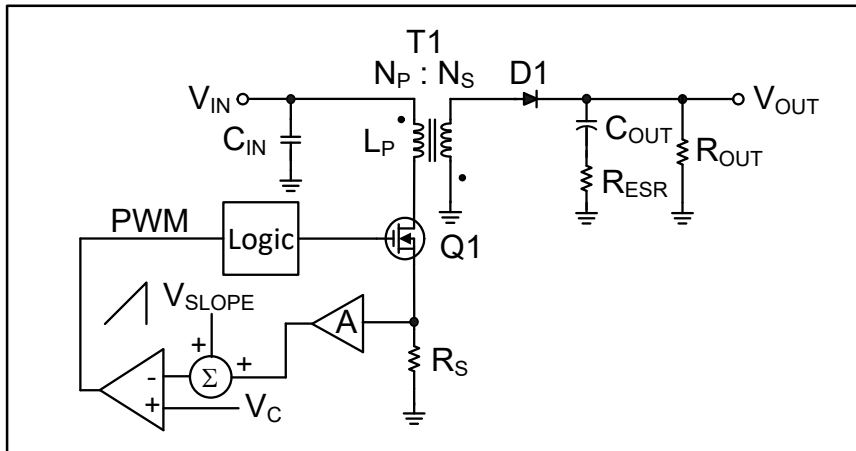

$$R_i = A \cdot R_S \quad \omega_r \approx \frac{R_{out} \cdot (1-D)^2}{L \cdot D}$$


$$A_{VC} \approx \frac{R_{out} \cdot (1-D)}{(1-D) \cdot R_i} \cdot \frac{N_P}{N_S} \quad \omega_z = \frac{1}{R_{ESR} \cdot C_{OUT}} \quad \text{at } D = 0.5$$
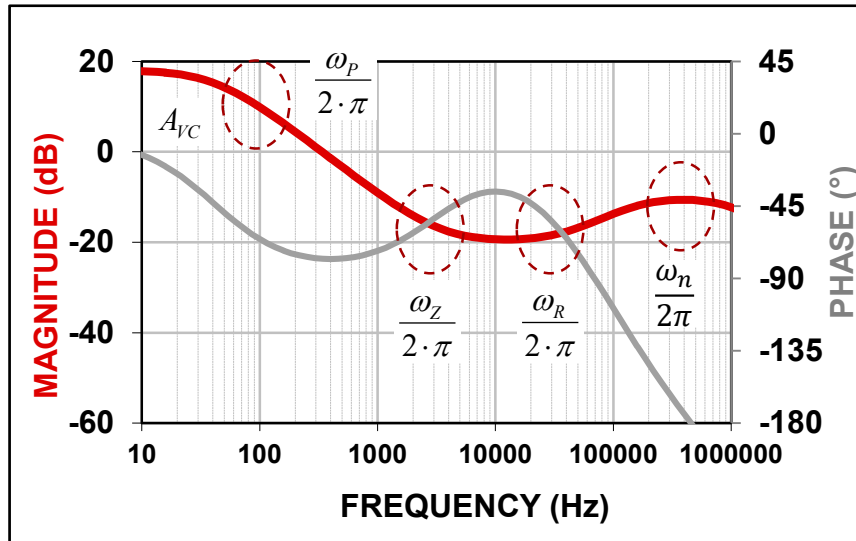
$$\omega_p \approx \frac{1+D}{C_{OUT} \cdot R_{OUT}} \quad F_h(s) = \frac{1}{1 + \frac{s}{\omega_n \cdot Q_p} + \left(\frac{s}{\omega_n}\right)^2}$$




$$\frac{\hat{v}_{out}}{\hat{v}_c} \approx A_{VC} \cdot \frac{\left(1 + \frac{s}{\omega_z}\right) \left(1 - \frac{s}{\omega_r}\right)}{1 + \frac{s}{\omega_p}} \cdot F_h(s)$$

Type I error amplifier

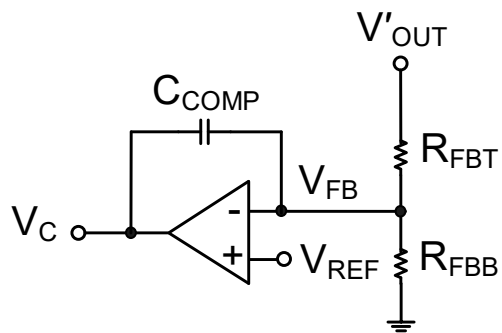

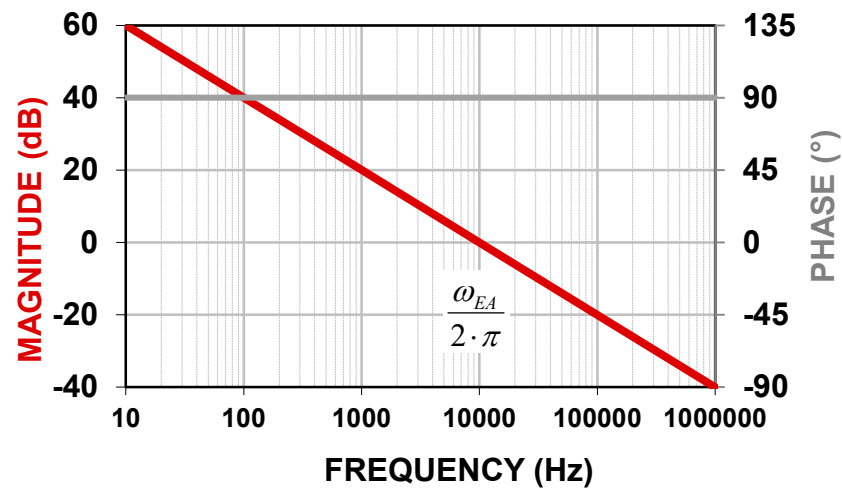
$$\omega_{EA} = \frac{1}{R_{FBT} \cdot C_{COMP}}$$



$$\frac{\hat{v}_C}{\hat{v}'_{OUT}} \approx -\frac{\omega_{EA}}{s}$$

Type II error amplifier

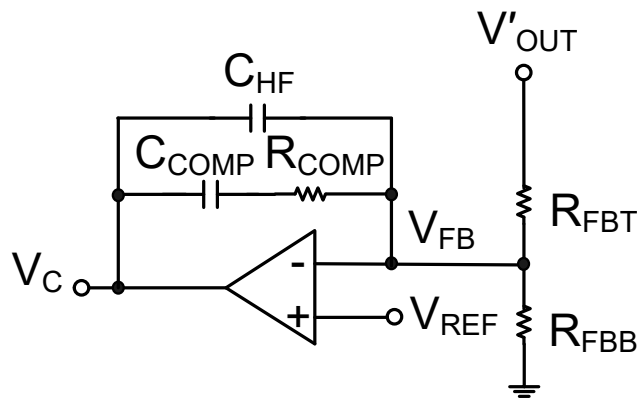


$$A_{VM} \approx \frac{R_{COMP}}{R_{FBB}}$$

$$\omega_{HF} \approx \frac{1}{R_{COMP} \cdot C_{HF}}$$


$$\omega_{ZEA} = \frac{1}{R_{COMP} \cdot C_{COMP}}$$

Assumption: $C_{COMP} \gg C_{HF}$

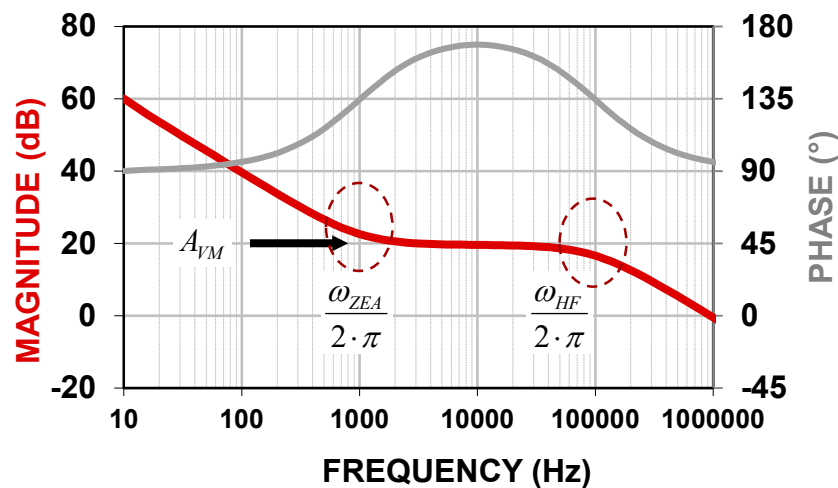

$$\frac{\hat{v}_c}{\hat{v}'_{out}} \approx - \frac{A_{VM} \cdot \omega_{ZEA}}{s} \cdot \frac{1 + \frac{s}{\omega_{ZEA}}}{1 + \frac{s}{\omega_{HF}}}$$

Type II transconductance amplifier

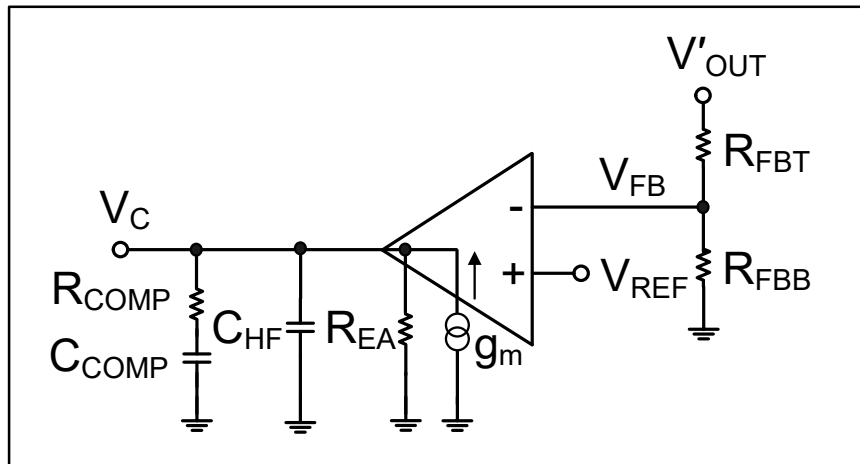

$$A_{VM} = K_{FB} \cdot g_m \cdot R_{COMP}$$


$$\omega_{ZEA} = \frac{1}{R_{COMP} \cdot C_{COMP}}$$

$$\omega_{HF} \approx \frac{1}{R_{COMP} \cdot C_{HF}}$$

Assumptions: $C_{COMP} \gg C_{HF}$ & $R_{EA} \gg R_{COMP}$



$$K_{FB} = \frac{R_{FBB}}{R_{FBB} + R_{FBT}}$$

$$A_{OL} = g_m \cdot R_{EA}$$

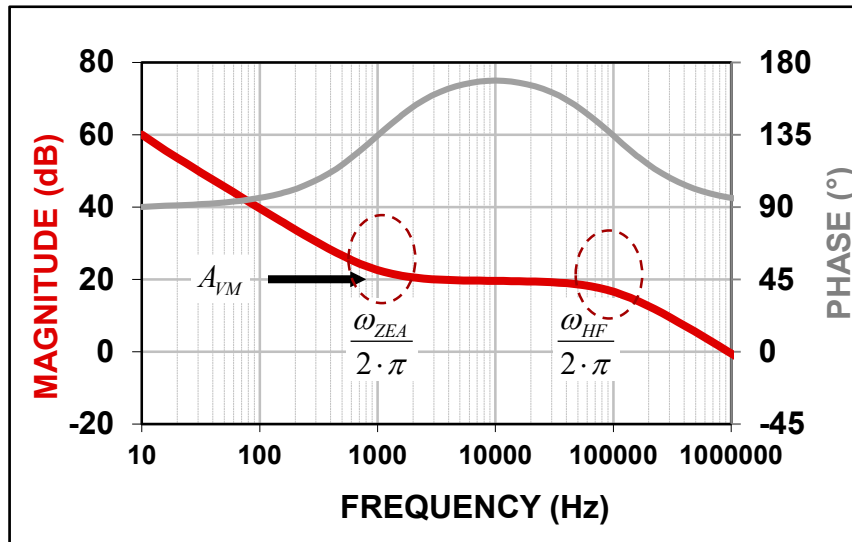

$$\frac{\hat{v}_c}{\hat{v}'_{out}} \approx - \frac{A_{VM} \cdot \omega_{ZEA}}{s} \cdot \frac{1 + \frac{s}{\omega_{ZEA}}}{1 + \frac{s}{\omega_{HF}}}$$

Type III error amplifier

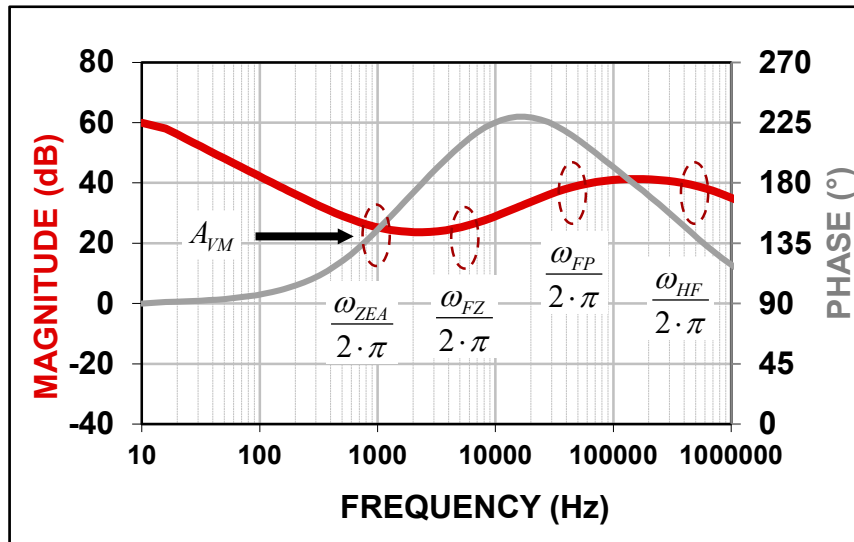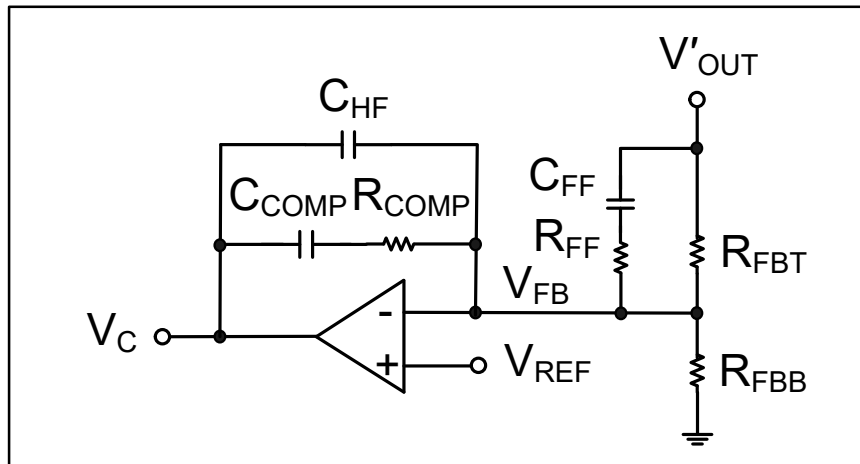



$$A_{VM} \approx \frac{R_{COMP}}{R_{FBT}} \quad \omega_{ZEA} = \frac{1}{R_{COMP} \cdot C_{COMP}} \quad \omega_{FP} = \frac{1}{R_{FF} \cdot C_{FF}}$$

$$\omega_{FZ} \approx \frac{1}{R_{FBT} \cdot C_{FF}} \quad \omega_{HF} \approx \frac{1}{R_{COMP} \cdot C_{HF}}$$

Assumptions: $C_{COMP} \gg C_{HF}$ & $R_{FBT} \gg R_{FF}$

$$\frac{\hat{v}_c}{\hat{v}'_{out}} \approx -\frac{A_{VM} \cdot \omega_{ZEA}}{s} \cdot \frac{\left(1 + \frac{s}{\omega_{ZEA}}\right) \cdot \left(1 + \frac{s}{\omega_{FZ}}\right)}{\left(1 + \frac{s}{\omega_{FP}}\right) \cdot \left(1 + \frac{s}{\omega_{HF}}\right)}$$

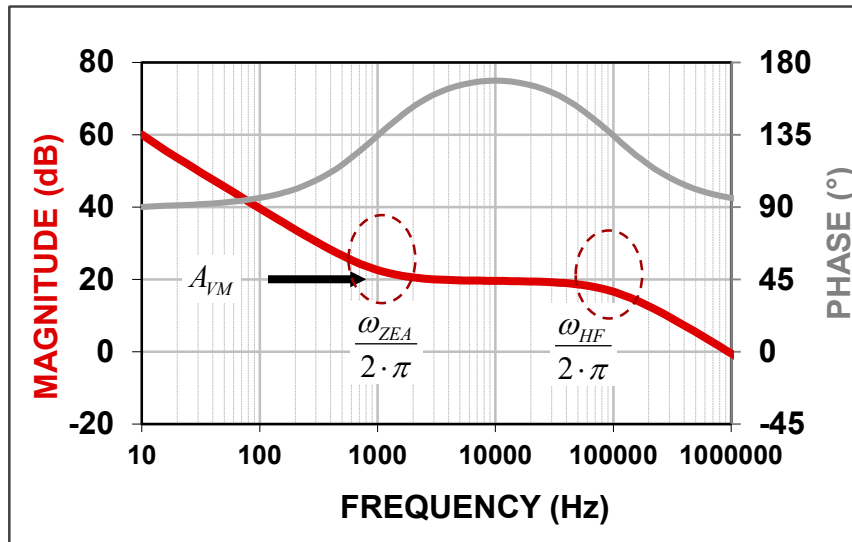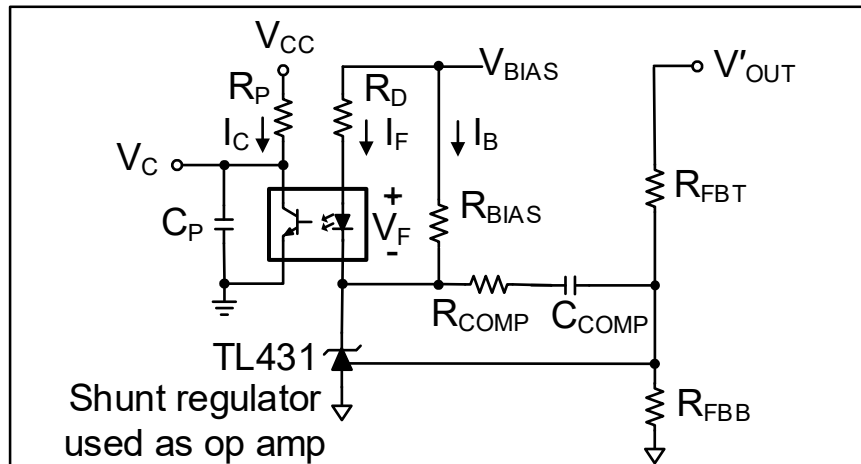Type II isolated feedback with fixed bias





$$A_{VM} = CTR \cdot \frac{R_P}{R_D} \quad CTR = \frac{I_C}{I_F}$$

$$\omega_{ZEA} = \frac{1}{R_{COMP} \cdot C_{COMP}} \quad \omega_{HF} = \frac{1}{R_P \cdot C_P}$$

$$\frac{\hat{v}_C}{\hat{v}'_{OUT}} \approx \frac{A_{VM} \cdot \omega_{EA}}{s} \cdot \frac{1 + \frac{s}{\omega_{EA}}}{1 + \frac{s}{\omega_{HF}}}$$

Type II isolated feedback with Vout bias

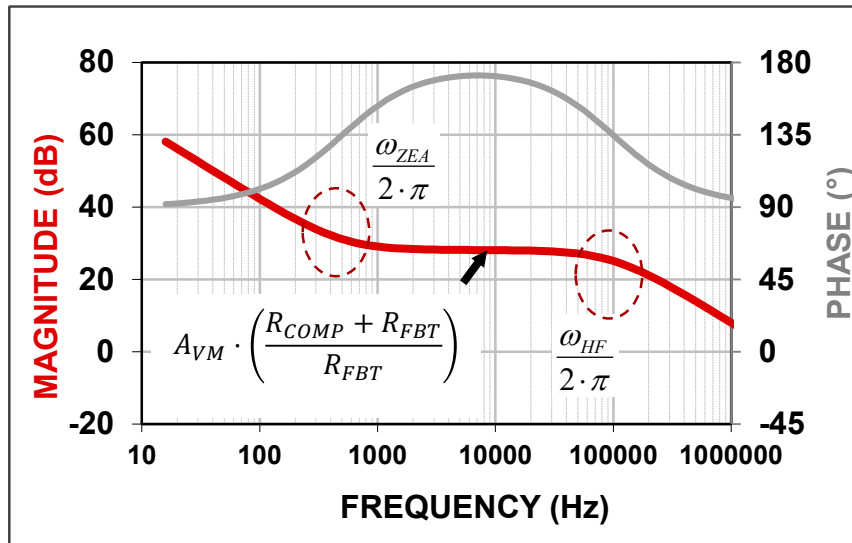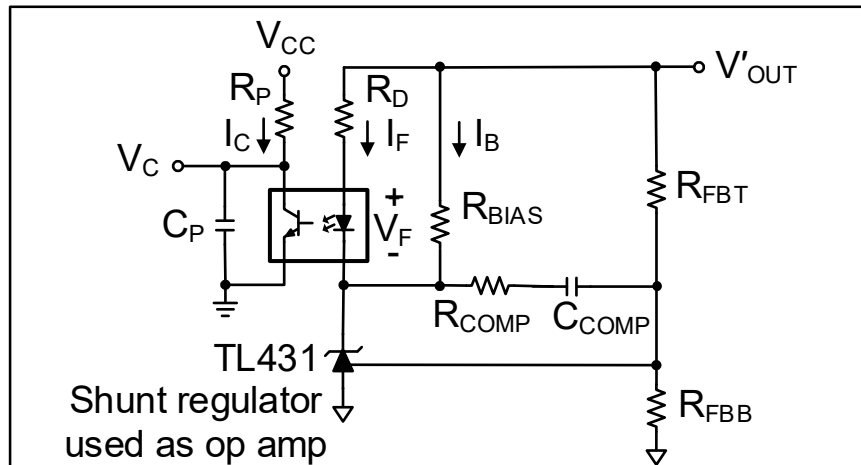

$$A_{VM} = CTR \cdot \frac{R_P}{R_D}$$


$$CTR = \frac{I_C}{I_F}$$

$$\omega_{ZEA} = \frac{1}{(R_{COMP} + R_{FBT}) \cdot C_{COMP}}$$

$$\omega_{HF} = \frac{1}{R_P \cdot C_P}$$

$$\frac{\hat{v}_C}{\hat{v}'_{OUT}} \approx \frac{A_{VM} \cdot \omega_{EA}}{s} \cdot \frac{1 + \frac{s}{\omega_{EA}}}{1 + \frac{s}{\omega_{HF}}}$$

Current-mode buck

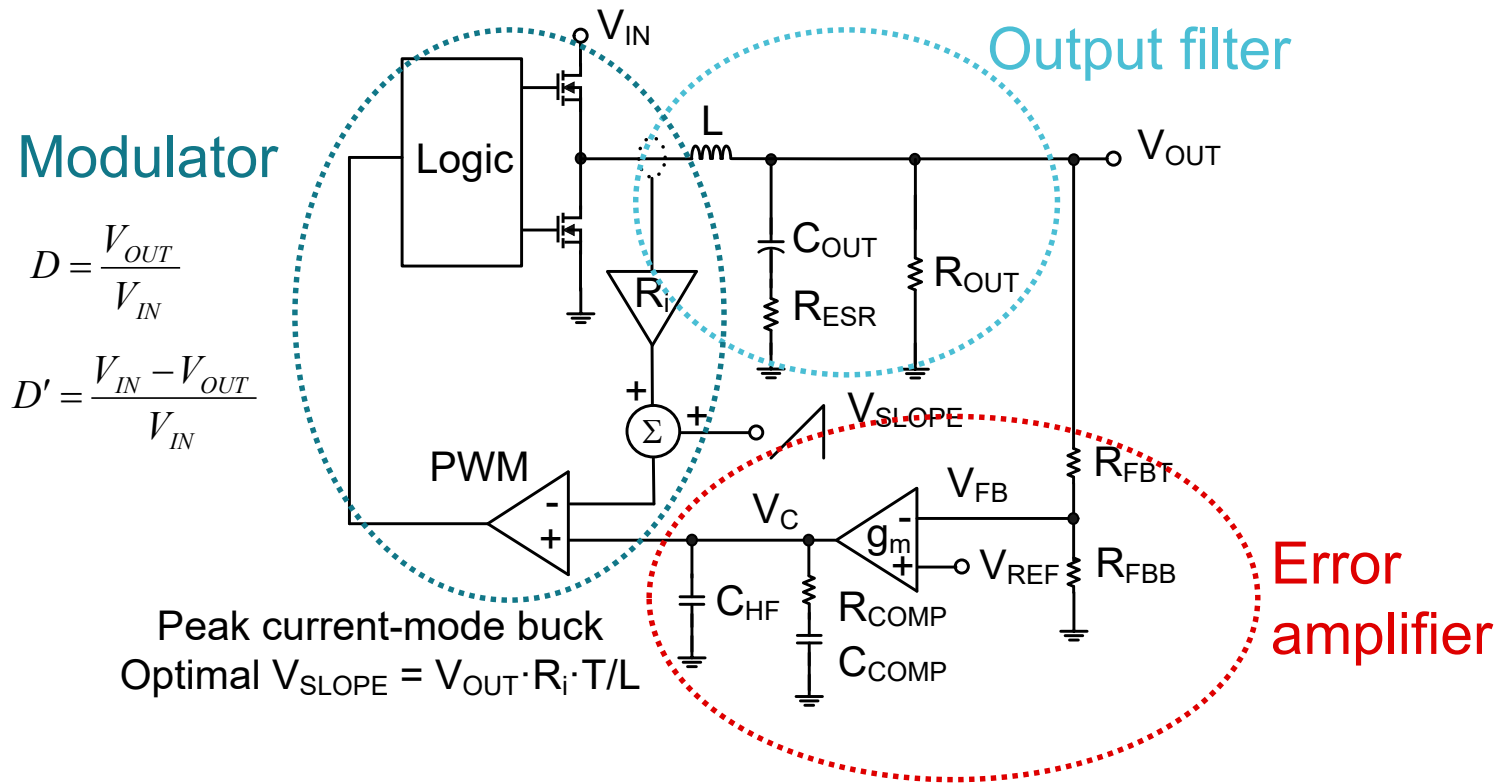

Current-mode buck compensation strategy

- Choose a value for R_{FBT} based on bias current and power dissipation
- Find the modulator transconductance in A/V
- Pick target bandwidth, typically $f_{SW}/10$:
$$\omega_C = 2 \cdot \pi \cdot f_C$$
- Find the mid-band gain A_{VM} to achieve target bandwidth
- Set ω_{ZEA} equal to 1/10 the target crossover frequency:
$$\omega_{ZEA} = \omega_C/10$$
- Set ω_{HF} equal to the ESR zero frequency:
$$\omega_{HF} = \omega_Z$$

$$G_m(\text{mod}) = \frac{1}{R_i}$$

$$A_{VM} = \frac{\omega_C \cdot C_{OUT}}{G_m(\text{mod})}$$

$$R_{COMP} = A_{VM} \cdot R_{FBT} \text{ (op amp)}$$

$$R_{COMP} = \frac{A_{VM}}{g_m \cdot K_{FB}} \text{ (g}_m \text{ amp)}$$


$$C_{COMP} = \frac{1}{\omega_{ZEA} \cdot R_{COMP}}$$

$$C_{HF} = \frac{1}{\omega_{HF} \cdot R_{COMP}}$$

Current-mode buck compensation results


Power stage
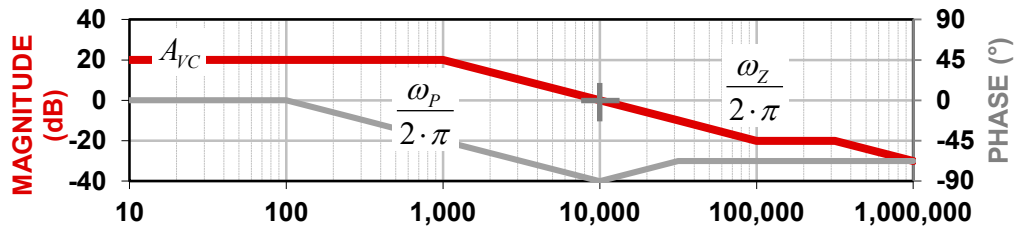
$$\frac{\hat{v}_{out}}{\hat{v}_c} \approx A_{VC} \cdot \frac{1 + \frac{s}{\omega_z}}{1 + \frac{s}{\omega_p}} \cdot F_h(s)$$




Error amplifier
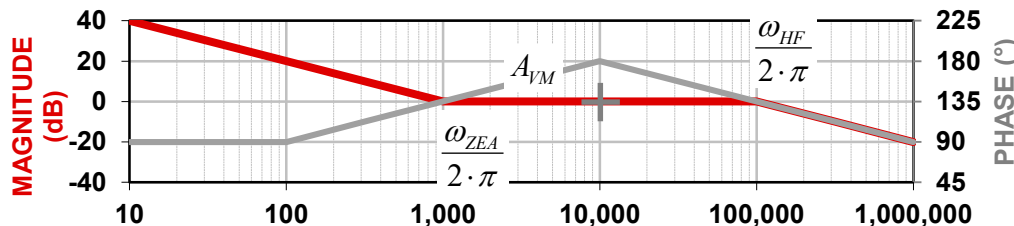
$$\frac{\hat{v}_c}{\hat{v}'_{OUT}} \approx -A_{VM} \cdot \frac{1 + \frac{s}{\omega_{ZEA}}}{1 + \frac{s}{\omega_{HF}}}$$




Control loop
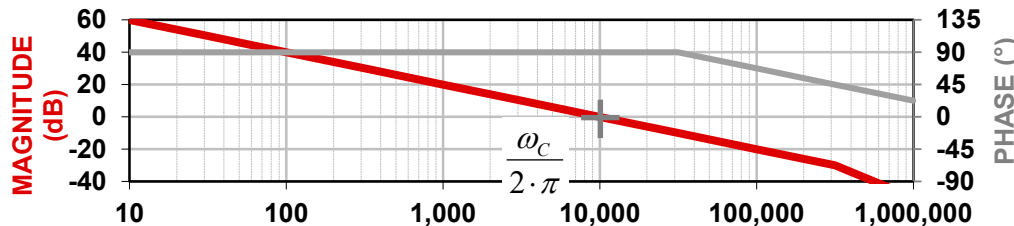
$$\frac{\hat{v}_{OUT}}{\hat{v}'_{OUT}} = \frac{\hat{v}_{OUT}}{\hat{v}_c} \cdot \frac{\hat{v}_c}{\hat{v}'_{OUT}}$$




Bandwidth vs transient response

Current-mode bandwidth

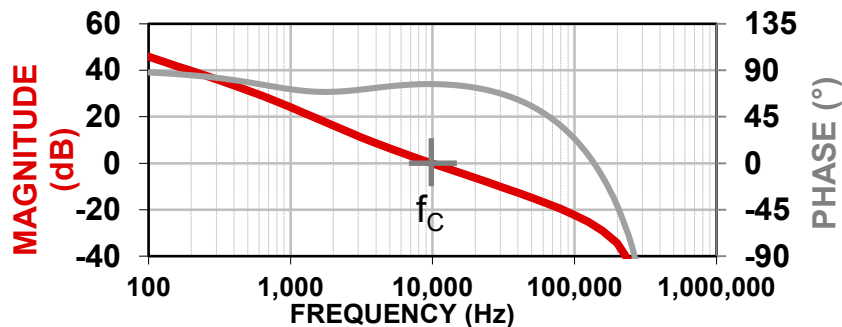

Current-mode transient response

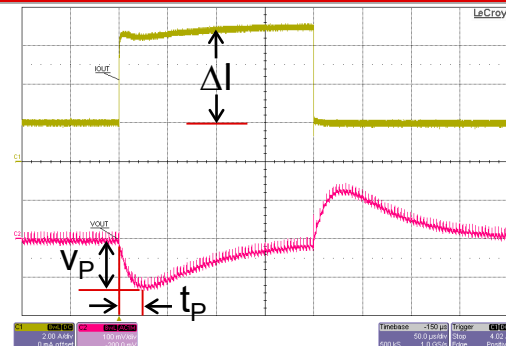

With no ESR, slew rate or duty cycle limiting:

$$t_p = \frac{1}{4 \cdot f_c}$$

Current-mode single pole approximation:

$$V_P = \frac{\Delta I}{2 \cdot \pi \cdot f_c \cdot C_{OUT}}$$

Current-mode critically damped:

$$V_P = \frac{\Delta I}{e \cdot \pi \cdot f_c \cdot C_{OUT}}$$

Voltage-mode:

$$V_P = \frac{\Delta I}{8 \cdot f_c \cdot C_{OUT}}$$


$$t_p = \frac{1}{4 \cdot 10 \text{ kHz}} = 25 \mu\text{s}$$

$$V_P = \frac{5 \text{ A}}{2 \cdot \pi \cdot 10 \text{ kHz} \cdot 440 \mu\text{F}} = 180 \text{ mV}$$





$$V_P = \frac{5 \text{ A}}{e \cdot \pi \cdot 10 \text{ kHz} \cdot 440 \mu\text{F}} = 130 \text{ mV} \text{ shown above}$$

$$V_P = \frac{5 \text{ A}}{8 \cdot 10 \text{ kHz} \cdot 440 \mu\text{F}} = 140 \text{ mV}$$

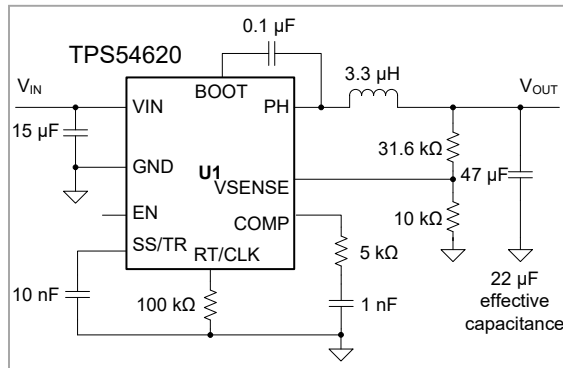
Switching regulator with poor compensation



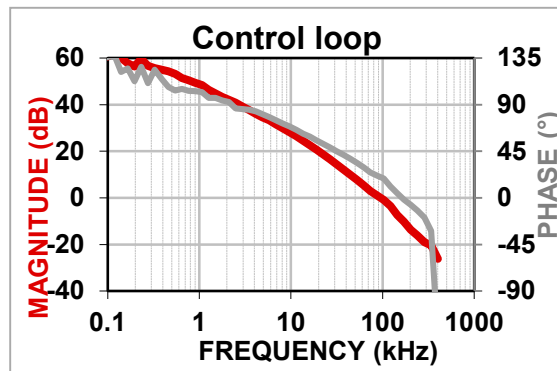
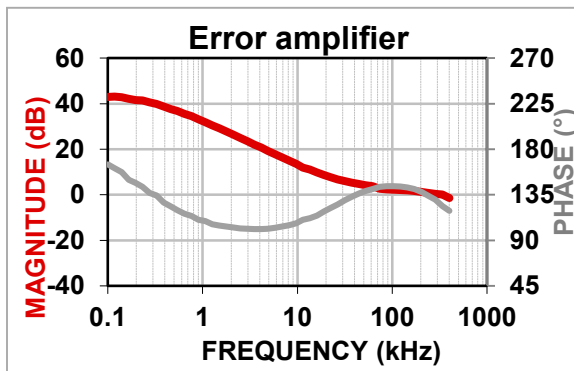
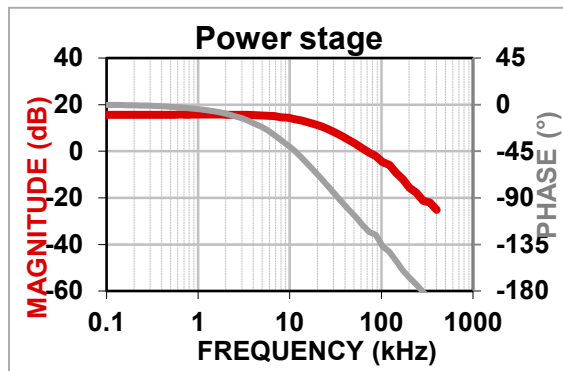
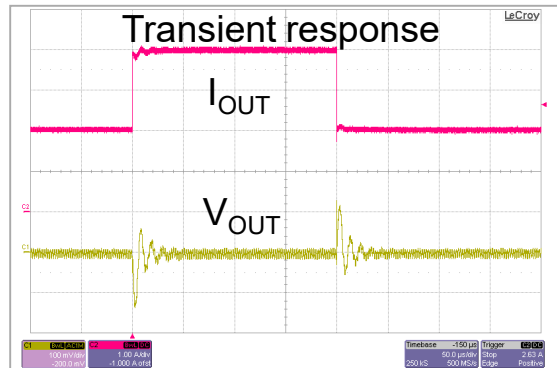
- Power stage: phase at -180° indicates high internal slope compensation
- Error amplifier: zero appears high and mid-band gain is 3 dB
- Control loop: f_C is 95 kHz with only 20° phase margin



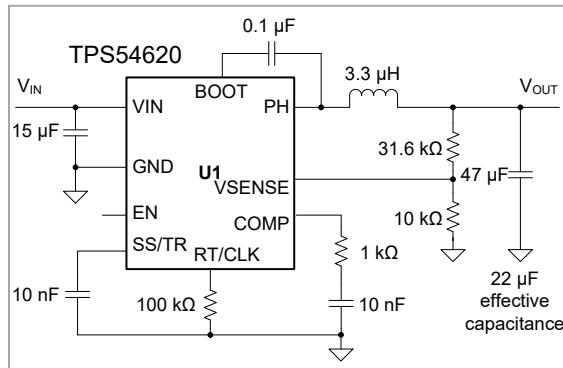Switching regulator with revised compensation




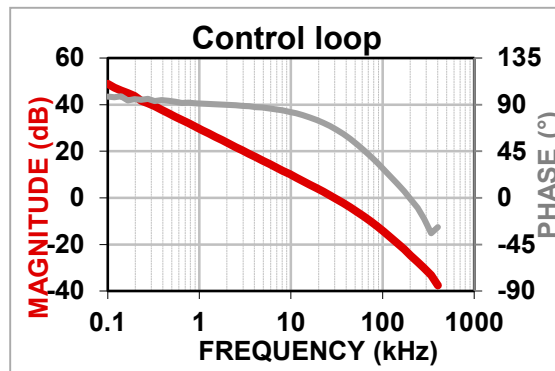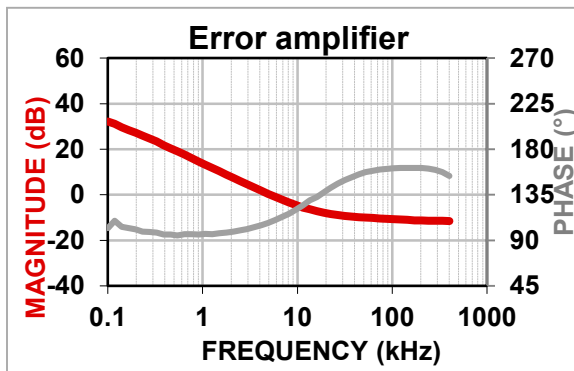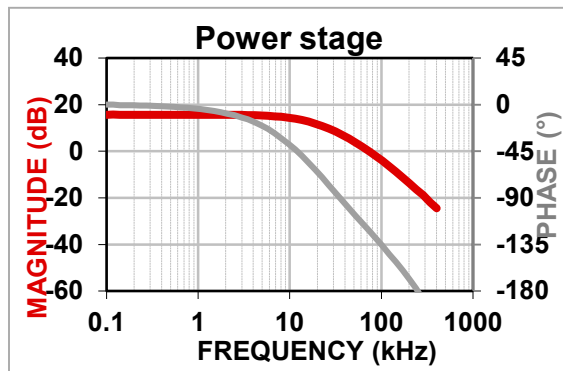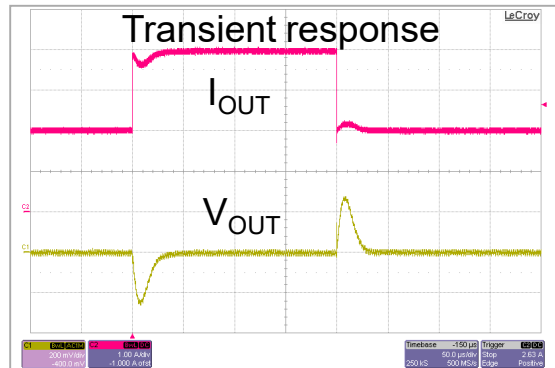- Power stage: cannot change slope compensation
- Error amplifier: decrease R_{COMP} and rescale C_{COMP}
- Control loop: now f_C is 30 kHz with 67° phase margin




Practical limitations

Error amplifier bandwidth

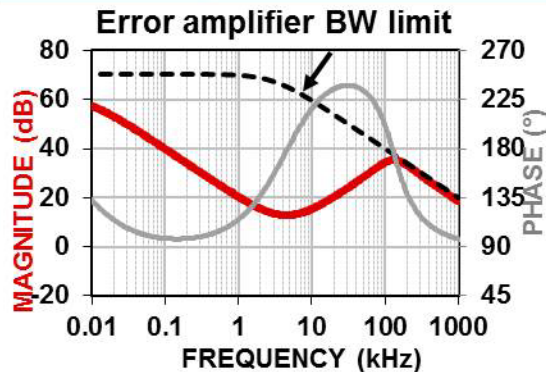


- Error amp BW can limit maximum f_c
- Wider BW op amp needed for voltage-mode due to Type III compensation

Optocoupler bandwidth

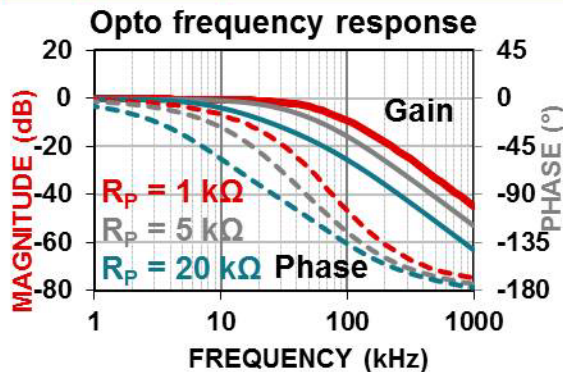


- Resistance seen by output transistor forms a pole in kHz range
- More of an issue for forward topologies at higher f_c

Switching frequency

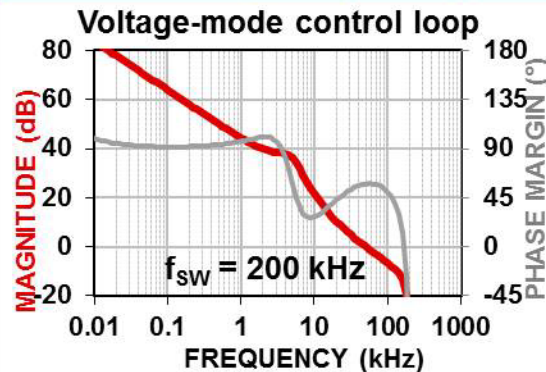



- Maximum f_c is a fraction of f_{SW}
- Rule of thumb is 1/5 to 1/10 of f_{SW}

Measuring transfer functions

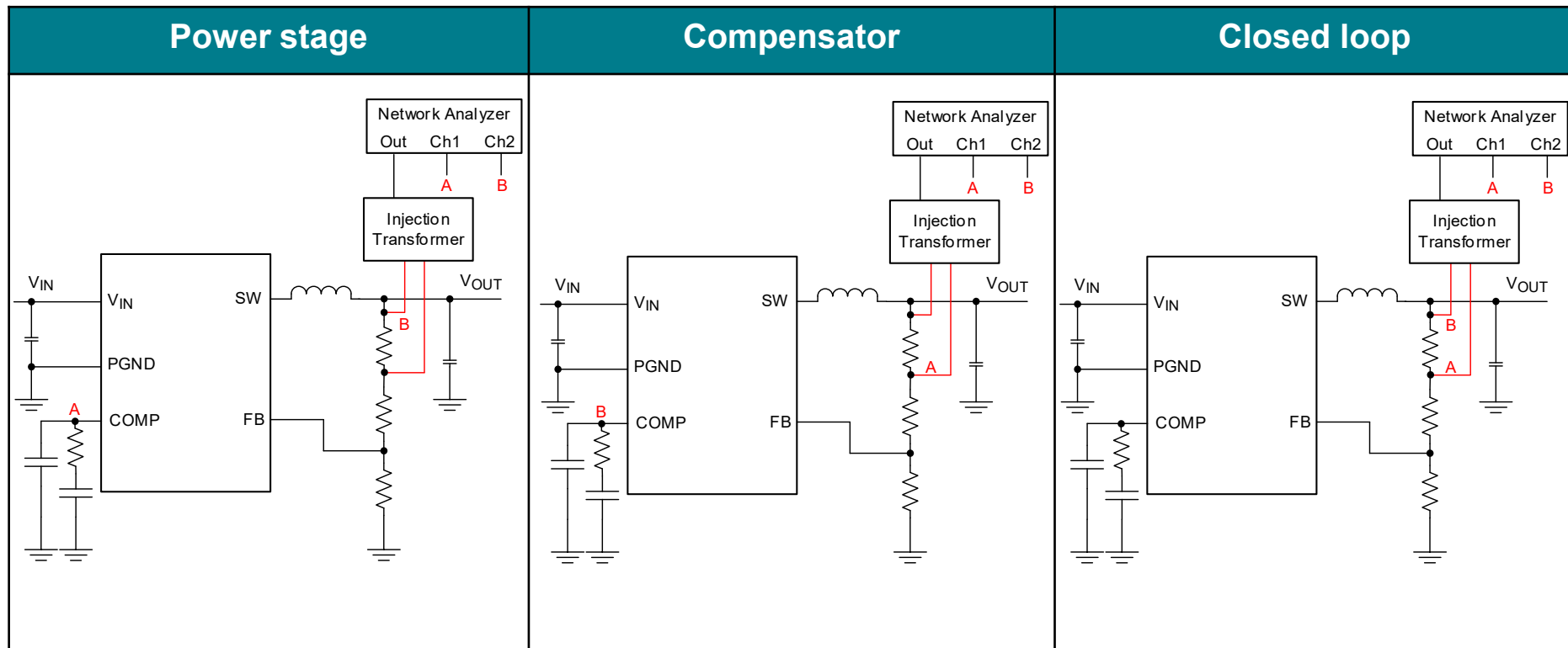

DCM vs CCM characteristics

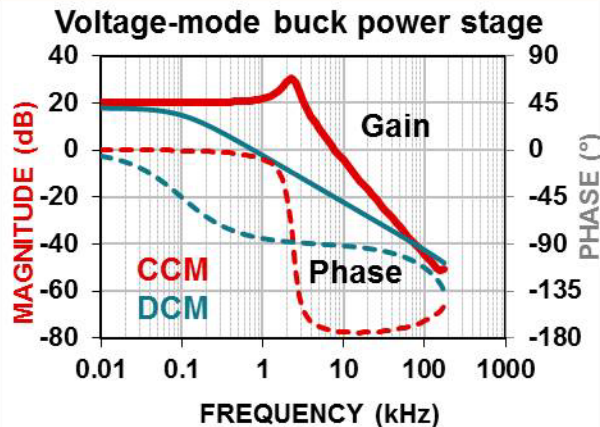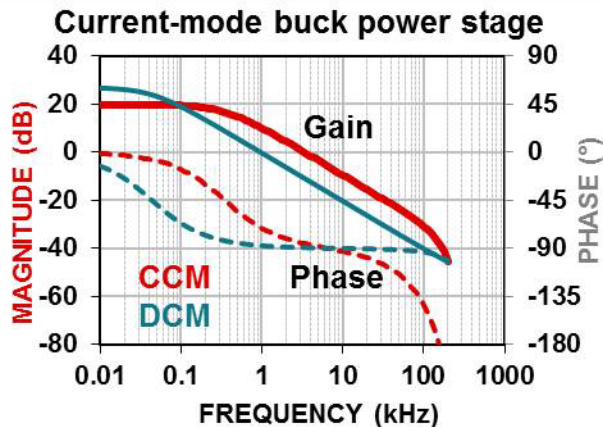Discontinuous vs. continuous conduction-mode



- DCM causes a reduction in loop bandwidth compared to CCM
- Generally, if the loop is stable in CCM, it will be stable in DCM

DCM duty cycle

- Buck

$$D = \sqrt{\frac{2 \cdot L \cdot f_{SW} \cdot I_{OUT} \cdot V_{OUT}}{V_{IN} \cdot (V_{IN} - V_{OUT})}}$$

- Boost


$$D = \frac{\sqrt{2 \cdot L \cdot f_{SW} \cdot I_{OUT} \cdot (V_{OUT} - V_{IN})}}{V_{IN}}$$

- Buck-boost

$$D = \frac{\sqrt{2 \cdot L \cdot f_{SW} \cdot I_{OUT} \cdot V_{OUT}}}{V_{IN}}$$

Filter considerations


Input filter stability

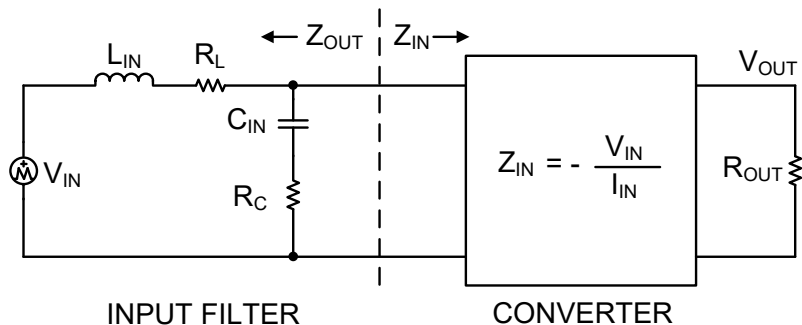

For stability: Filter $Z_{OUT} \ll$ Converter Z_{IN}

- Characteristic impedance $Z_S = \sqrt{\frac{L_{IN}}{C_{IN}}}$
- Damping factor
$$\zeta = \frac{1}{2} \cdot \left(\frac{R_L + R_C}{Z_S} + \frac{Z_S}{Z_{IN}} \right)$$

Second stage filters

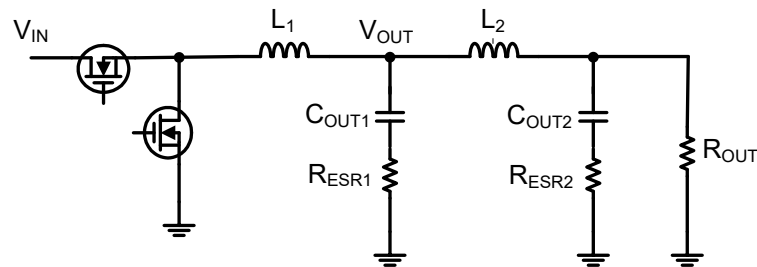

- Capacitors: make C_{OUT1} smaller than C_{OUT2}
- Inductors: make L_2 smaller than L_1
- Resonance: make second stage filter resonance 3 times f_C
- Damping: make second stage filter damped to a Q of 1

Summary

- Identify poles and zeros of the power stage
- Select appropriate compensation network based on control mode and topology
- Tune compensation and loop gain to achieve required loop bandwidth and transient response

Resources and references

- ["Closing the Feedback Loop"](#) by Lloyd Dixon, SEM300
- ["Current-Mode Control of Switching Power Supplies"](#) by Lloyd Dixon, SEM400
- ["The Right-Half-Plane Zero -- A Simplified Explanation"](#) by Lloyd Dixon, SEM500
- ["Isolating the Control Loop"](#) by Robert Mammano, SEM700
- ["Control Loop Design"](#) by Lloyd Dixon, SEM800
- ["Control Loop Cookbook"](#) by Lloyd Dixon, SEM1100
- ["A New Small-Signal Model for Current-Mode Control"](#) by Ray Ridley
- ["Current-Mode Control Modeling"](#) by Ray Ridley
- ["Designing Stable Control Loops"](#) by Dan Mitchell and Bob Mammano, SEM1400
- ["Current-Mode Modeling – Reference Guide"](#) by Robert Sheehan, SNVA542
- ["Understanding and Applying Current-Mode Control Theory"](#) by Robert Sheehan, SNVA555
- ["Frequency Compensation and Power Stage Design for Buck Converters to Meet Load Transient Specifications"](#) by S. Bag, R. Sheehan, et al., APEC 2014
- [Power Tips: Compensating Isolated Power Supplies](#) by Brian King
- [Practical Feedback Loop Analysis for Current-Mode Boost Converter](#) by SW Lee